

Power Tips: Why Is Your LLC Resonant Converter Frequency Way, Way off



Sheng-yang Yu

Have you ever wondered why the measured switching frequency (f_{sw}) of your LLC series resonant converter (LLC-SRC) is far from your calculations in some designs?

To understand the reason for the discrepancy, let's start with a basic isolated LLC-SRC, shown in [Figure 1](#). A basic isolated LLC-SRC consists of a half bridge (S_1 , S_2), a resonant capacitor (C_r), a resonant inductor (L_r) and an ideal transformer (with L_m as magnetizing inductance). Most AC/DC power-supply designers linearize this basic isolated LLC-SRC with sinusoidal approximation to get the input-to-output voltage gain and predict switching frequencies under different conditions. The calculations have been proven close to the actual measurements when f_{sw} is close to the higher resonant frequency ($f_r = 1/(2\pi(L_r C_r)^{0.5})$).

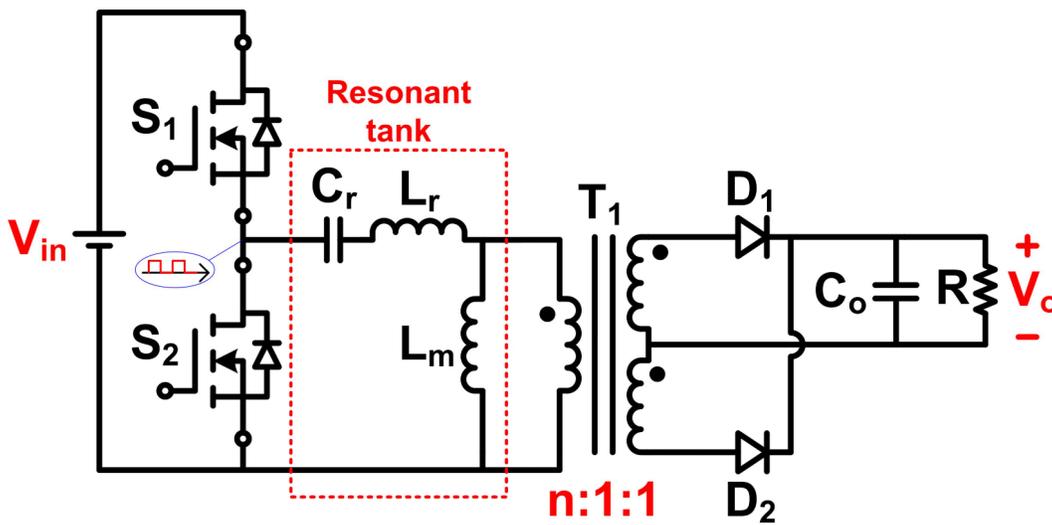


Figure 1. Basic Isolated LLC Series Resonant Converter

However, you may notice that in some of your designs, the measured switching frequencies are far away from the calculation results using the linearization process mentioned above. So why is there still a discrepancy between the calculation and measurement results?

If you check the assumption of the linearization process carefully, you will notice that it assumes an ideal transformer without leakage inductance. Thus, given inevitable leakage inductance in a real transformer, there will be a discrepancy between your measurements and your calculations. The discrepancy increases significantly when a single integrated transformer, such as a transformer leakage inductance, is utilized as the resonant inductor L_r , because the magnetizing inductance of the transformer is no longer much greater than its leakage inductance. To fix this, you will need to remodel the transformer using a transformer model like the one shown in [Figure 2](#).

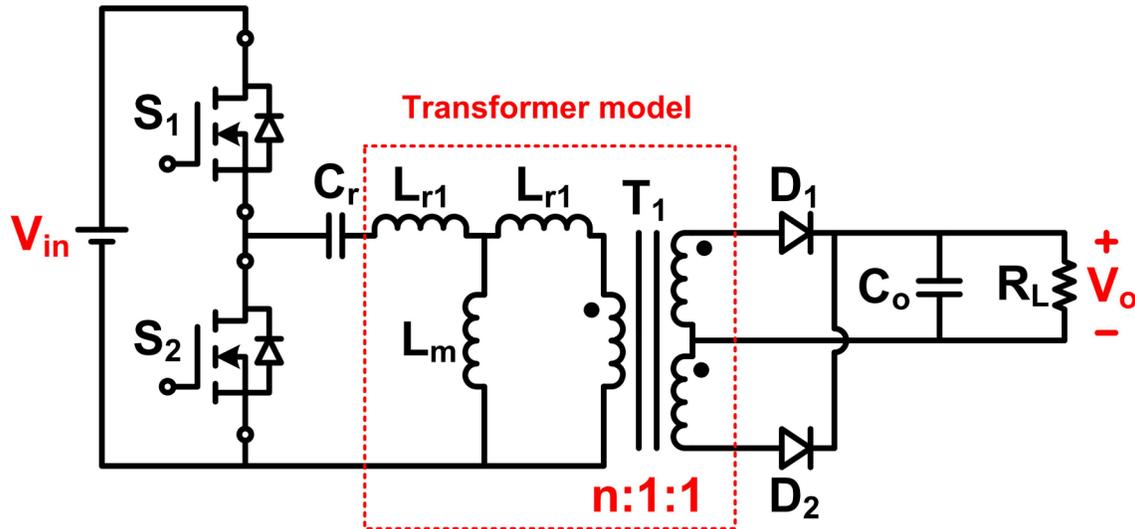


Figure 2. Isolated LLC Series Resonant Converter with Integrated Transformer

If you define the primary inductance of the transformer when the output windings are open to be L_p and the leakage inductance of the transformer when the output windings are shorted to be L_{lk} , you can express the relationship between L_m , L_{r1} , L_p and L_{lk} as Equations 1 to 3. Where k_{XFMR} is the transformer coupling coefficient.

$$L_m = k_{XFMR} \cdot L_p \quad (1)$$

$$L_{r1} = (1 - k_{XFMR})L_p \quad (2)$$

$$k_{XFMR} = \sqrt{1 - \frac{L_{lk}}{L_p}} \quad (3)$$

By using the integrated transformer model in Figure 2 and equations above, you can check the difference between the calculations and measurements.

The [Low-Line Wide Input LLC Resonant Converter for Consumer Electronics \(12V at 10A\) TI Designs reference design](#) operates with a wide input range (100V_{AC} to 132V_{AC}) and includes an integrated transformer. To maintain good output regulations, the ratio of L_p/L_{lk} ($86.9\mu\text{H}/22.3\mu\text{H} = 3.9$) in the reference design is lower than common off-line LLC-SRC designs. The low L_p/L_{lk} ratio makes the transformer far from ideal, hence, this design is a good example to show how much discrepancy you will get if using the model in Figure 1 on an LLC-SRC with a badly-coupled transformer.

Figure 3 shows the calculation results based on Figure 1 (assuming $L_{lk} = L_r$ and $L_m = L_p - L_{lk}$), as well as Figure 2's model and measurement results. The 12V output was loaded with 6A during the test.

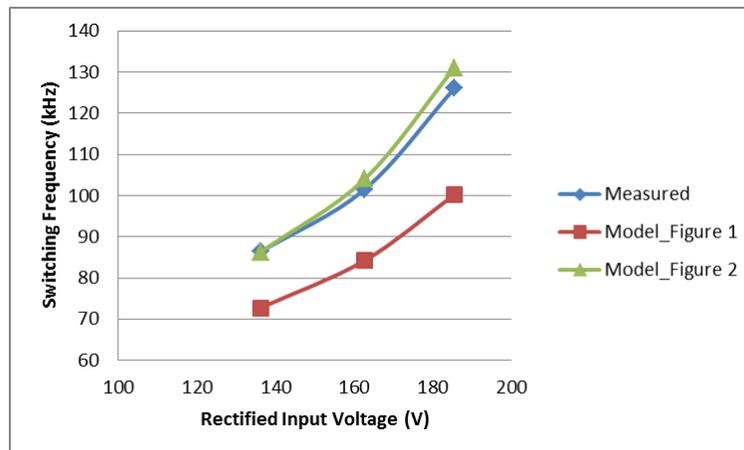


Figure 3. Comparison between Calculated and Measured Switching Frequencies of PMP8762

As you can see, the calculation results using the transformer model in [Figure 1](#) are far from the actual measurements. Instead, by using a proper transformer model in [Figure 2](#), the calculation results are much closer to the actual switching frequency.

So the next time you begin an LLC-SRC design, once you've decided to use an external L_r with a well-coupled transformer or single integrated transformer, be sure to use the correct transformer model.

Additional Resources

- [PowerLab Notes: Get to know LLC series resonant converter design](#)
- [PowerLab: How much can a LLC series resonant converter do?](#)
- [Power Tips: Designing an LLC resonant half-bridge power converter](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated