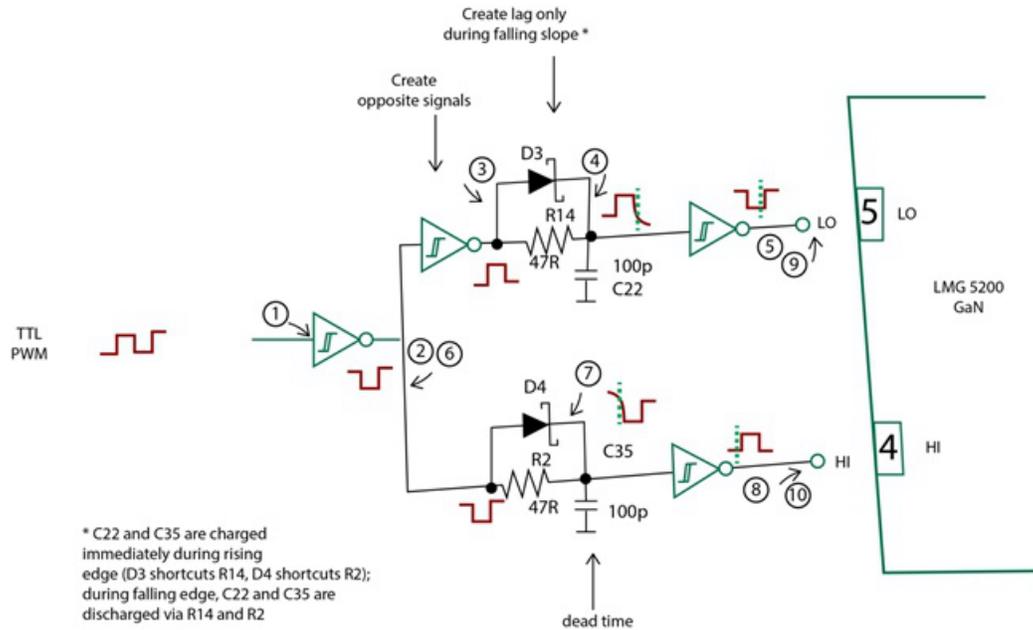




of a square wave, TI designers adapted the board so that it only inserts the delay on the rising edges. And that's exactly the behavior you need.

### The Dead-time Generator Schematics

The [user's guide](#) documents the full schematics of the evaluation board. [Figure 3](#) shows the module that generates the high and low drive signals with the dead time.

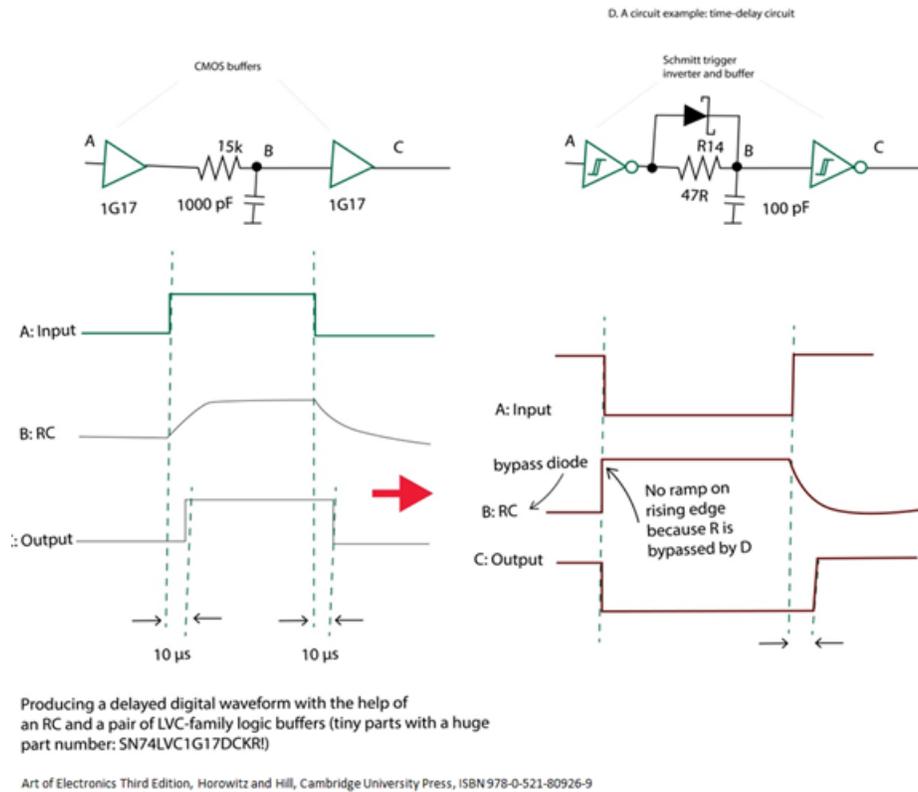


**Figure 3. Dead Time Generator Schematic**

If you abstract away the diodes, resistors and capacitors, the circuit generates an in-phase and an inverted signal from the PWM input. There will always be one side of the half bridge that's on and one side that's off. The passive components will generate that dead time for you, so let's dig a little deeper into that part.

### “The Art of Electronics”

In Chapter 1 of “The Art of Electronics,” the authors present a time-delay circuit. It uses an RC circuit – flanked by two complementary metal-oxide semiconductor (CMOS) buffers – to glue a short delay to both flanks of a PWM signal ([Figure 4](#)).

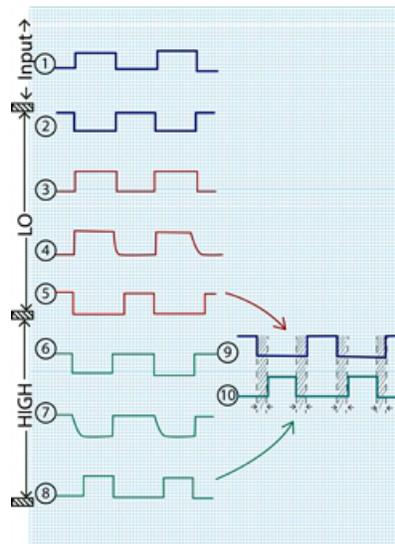


**Figure 4. Comparison of Time-delay Circuit from “Art of Electronics” and TI Asymmetric Delay Generator**

In [TI's reference design](#), a fast-switching Schottky diode in parallel with the resistor bypasses the RC delay during one of the edges.

### The High and Low Signals with Dead Time

Let's follow the HI signal path of the evaluation board schematics (D4, R2 and C35 in [Figure 3](#)). Diode D4 bypasses R2 during the falling edge of input A (signal 1 in [Figure 3](#) and [Figure 5](#)). At the output of the first inverter (signal 6), this input signal's falling edge becomes a rising edge. The diode conducts and the R component of the RC circuit is almost 0. The RC constant is also almost 0. So the circuit adds virtually no delay to that flank (signal 7). After the second inverter, this becomes a falling flank again (signals 8 and 10).

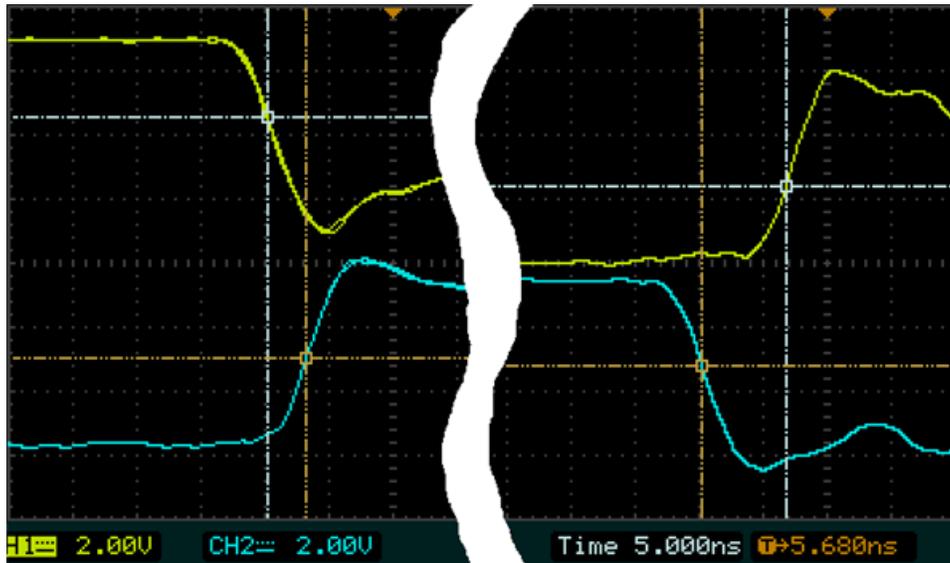


**Figure 5. Signal Transformation from Simple Input to Inverted Outputs with Dead Time**

When the input signal rises (again at signal 1), the signal after the inverter becomes a falling edge (signal 6). The diode D4 blocks and leaves R2 alone. You get a real RC circuit with  $47\Omega$  and  $100\text{pF}$ . That will turn the edge into a ramp (signal 7). The Schmitt trigger front end of the second inverter will ensure that the output signal flips at a predictable voltage (and at a predictable time). So the result is that the rising edge at the output (signals 8 and 10) will lag compared to the input signal. And that was the effect I was after.

The LO signal path does exactly the same. An additional inverter at the input of this path ensures that both sides see and process an opposite signal: one to drive the high-side FET and one to drive the low-side FET. As a result, you'll get two related signals, as shown in [Figure 2](#). A signal only turns high after the other one switches off, and after that dead time has passed, which was our ultimate goal.

[Figure 6](#) shows the capture of both inputs of the [LMG5200](#) at the two transitions.



**Figure 6. Capture of HI-LO and LO-HI Transition of Both Driver Signals.**

You can vary the duty cycle and the frequency of the input signal as required. The dead time will stay constant.

By using a classic time delay circuit, you can safely drive a GaN half-bridge power stage with a simple PWM signal and control its output with variable duty cycle. What is your approach to generate dead times in your switching applications?

#### Additional Resources

- [Learn to use the LMG5200 with the GaN Half-Bridge Power Stage EVM User's Guide](#)
- [Get to know the user-friendly interface of the LMG5200](#)
- [Keep up with Jan & Martin's Project Pick of the Month](#) and Jan's projects on [Launch Your Design](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated