

Akshay Mehta

LED technology is ubiquitous in the automotive industry, used for everything from headlamps to cabin backlight panels. Some automotive LED applications such as blinker signals are very space-constrained because of a fixed form factor. As a result, simple devices with a lower pin count and smaller size are required. But as these systems are still connected to the car battery, they must be capable of higher voltages to withstand load dump. Finding buck converters with 40V capability, good performance and very small size can be difficult. The [LMR14006](#) is a new device from the [SIMPLE SWITCHER® family of buck converters](#) that is a good fit for blinker/turn-signal applications, rated for 40V and 600mA.

Traditional LED drivers are preferred over voltage regulators for LED applications because they allow for a higher rate of turn on and turn off, which would require a very small soft-start time and very low or no output capacitor in devices using a buck topology. A higher rate of turn on and turn off helps to reduce the current through the LEDs dynamically without the human eye detecting turn on and turn off. However, to blink the LEDs one would have to turn the power on and off at a relatively lower frequency, necessitating the use of a regulator with a relatively longer soft-start time.

A voltage regulator like the [LMR14006](#) operates on the peak current-mode principle. Since automotive designs have strict electromagnetic interference (EMI) requirements, a DC/DC regulator with fixed frequency makes EMI mitigation easier. The [LMR14006](#) has a 2.1MHz switching-frequency option that makes component sizes smaller and also helps keep the switching noise out of the AM band. The [LMR14006](#) also has a very low bill-of-materials (BOM) count, which simplifies its design.

The [LMR14006](#) has an SHDN pin, which when pulled low disables the device and when pulled above 2.1V enables the device. To blink the LEDs, you simply feed a pulsing waveform of the required threshold values to the SHDN pin. You can also achieve the same results by toggling the V_{IN} pin. But as the V_{IN} pin is the power input to the regulator, toggling the V_{IN} pin means that the input current to the IC is also switching on and off. This can cause issues if the board layout is not optimal because of the limiting form factor of the blinker, such as large voltage spikes at the input. Sustained large spikes at the input can cause damage to the IC and/or instability in the device's regular operation; suppressing these spikes may require additional circuitry. Meanwhile, the SHDN pin sees no significant current and toggling it on/off would not cause any problems related to voltage spikes. [Figure 1](#) shows the [LMR14006](#) in an LED blinker application.

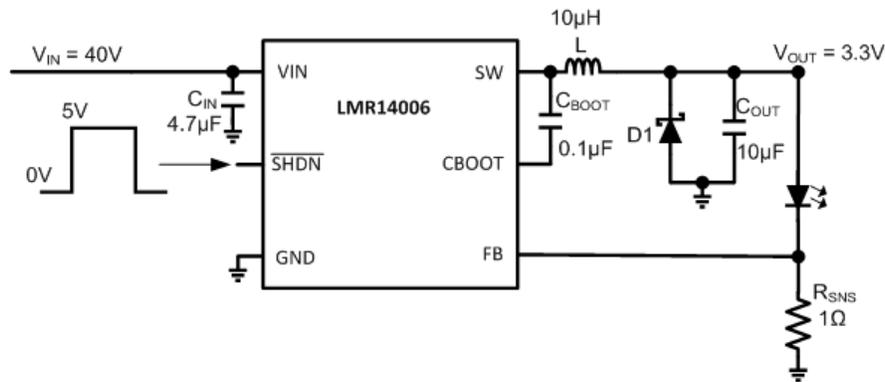


Figure 1. The [LMR14006](#) As an LED Blinker.

The R_{SNS} resistor and feedback reference voltage of the [LMR14006](#) control the current through the LEDs. The reference voltage of the [LMR14006](#) is 765mV, much lower than traditional voltage regulators. [Equation 1](#) expresses the power dissipated in the sense resistor:

$$P_D = \frac{V_{REF}^2}{R_{SNS}} \quad (1)$$

Therefore, a lower reference voltage would result in lower power dissipated in the sense resistor, ultimately resulting in higher efficiency.

Thus, for simple LED blinker applications, low-pin, low-BOM-count [SIMPLE SWITCHER buck regulators](#) are beneficial. Devices such as the [LMR14006](#) and [LMR16006](#) are small in size, high in efficiency and have a low component count. If you require an AEC-Q100 qualified device, the [LMR16006Y-Q1](#) is a pin- and footprint-compatible alternative to the [LMR14006](#).

Additional Resources

- Consider TI's SIMPLE SWITCHER® [LMR14006](#) and [LMR16006](#) for your next design.
- Get more information on all of TI's [SIMPLE SWITCHER buck regulators](#).
- See all [automotive products](#) from TI.
- Start a design in [WEBENCH® Automotive Power Designer](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated