

High-current Amplifier Applications Made Smaller



Aditya Ambardar

Often, when defining a new device to meet rigorous automotive standards, our teams see other systems that require the same capabilities, and we'll design the device to cross all these applications. This is what happened when our team was developing the new [ALM2402](#), a dual high-current operational amplifier (op amp) designed for automotive applications.

While defining the [ALM2402](#), we realized that many automotive and industrial systems require an op amp that can drive high-current capacitive or inductive loads.

In the past, designers have often been required to solve this need with discrete components. To design a simple high-current amplifier with discrete components, you need an amplifier, bipolar junction transistors (BJTs) and diodes. An example of this is shown in [Figure 1](#), which is typically used in a motor drive application. This implementation drives the excitation coil of a resolver, which is used to measure degrees of motor shaft rotation. You can find amplifier designs like driving inductive loads in many automotive and industrial applications. This typical solution creates challenges for the designer around board space and biasing of the output transistor.

Adding to the space challenge of the discrete implementation is the need to provide additional circuitry for overcurrent protection. Without overcurrent protection, the system is “dumb.” It will keep burning power without any protection.

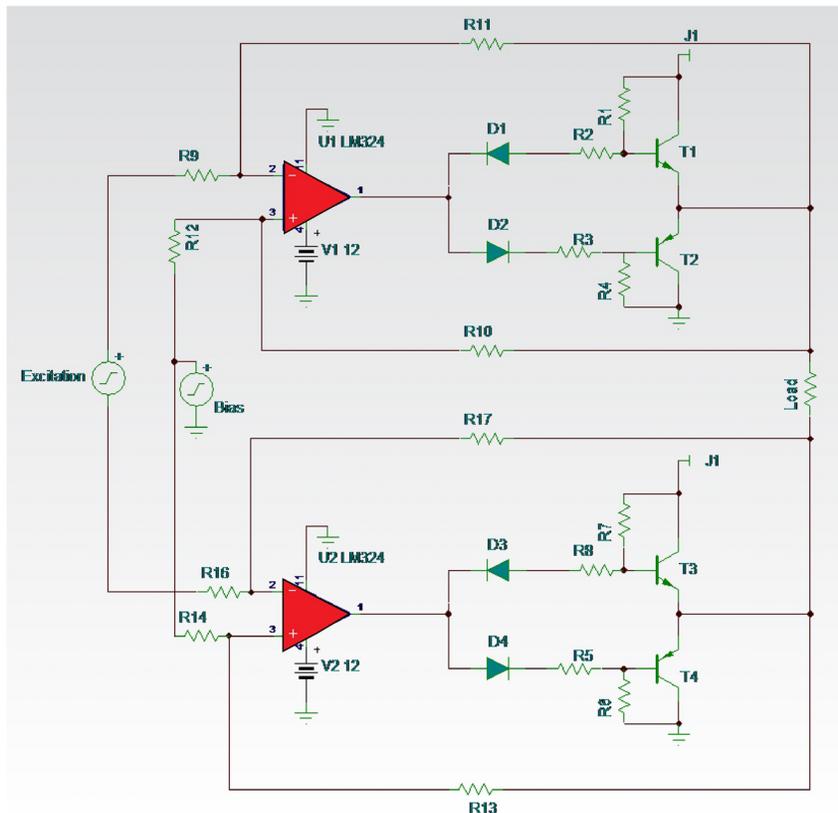


Figure 1. Discrete Implementation of Driving an Excitation Coil

In contrast, let's look at the [ALM2402](#) implementation for driving an excitation coil, shown in [Figure 2](#). Simple, right? No biasing of the external transistor is required, and the [ALM2402](#) can drive up to 400mA through each channel. The circuit is small, housed in a 3-mm x 3-mm DRR package, which allows designers to minimize their overall solution size.

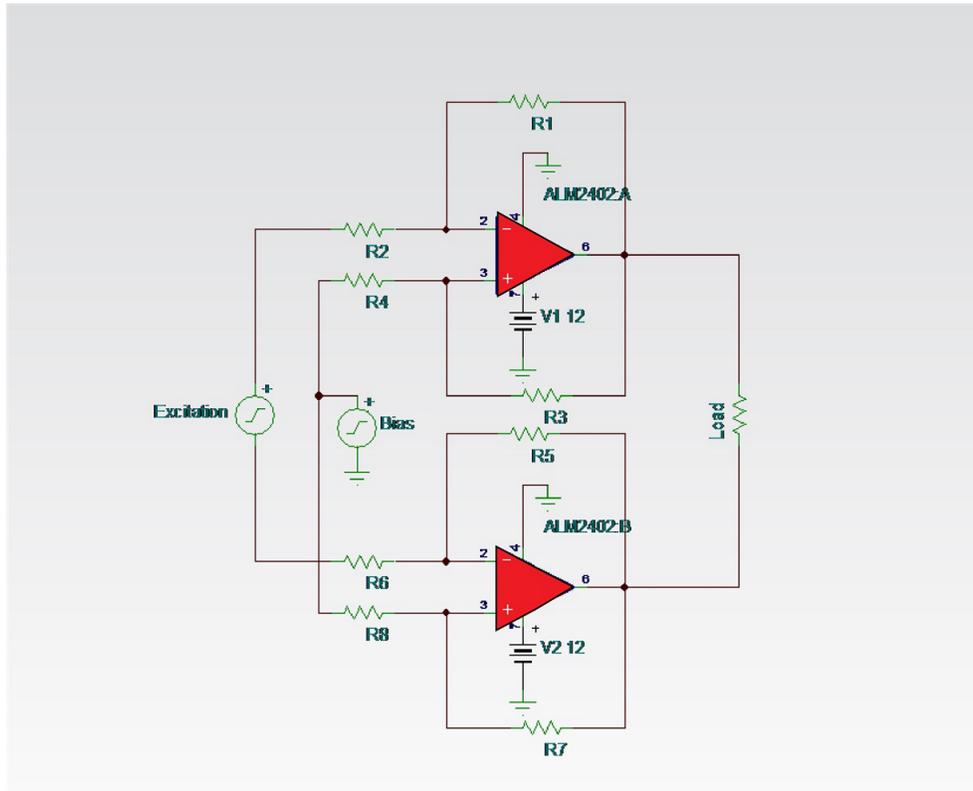


Figure 2. Excitation Coil Drive Using the [ALM2402-Q1](#)

Protection is a critical requirement in high-current driving applications, and the [ALM2402](#) integrates several system protection features, including the following:

- Integrated overcurrent protection
- Output short to battery if a series diode is connected from the battery to the supply pin of the device. Over-temperature protection shuts down the device if there is an error in layout or a higher-than-specified ambient temperature in the system.

In addition, the device's flag pin is a handy feature that serves several purposes. The flag pin goes low when an over-temperature event occurs, allowing users to design a feedback mechanism to shut down the system. These can also externally pull down the flag pin to shut down the op amp, which puts it in sleep mode to consume very low current. This feature is useful for battery applications where power consumption is of utmost importance.

Being a high-current operational amplifier, the [ALM2402](#) could be useful for many applications, in addition to motor drives and LED-driving applications. In future posts, I will discuss additional applications that can be implemented using [ALM2402](#).

Additional Resources

- Datasheet: "[ALM2402-Q1 dual op-amp with high current output](#)"
- "[Designing with dual-power op-amp, ALM2402Q1](#)" application report
- See TI's entire [precision amplifier](#) portfolio

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated