

Tips and tricks for achieving wide operating ranges with LLC resonant converters



Benjamin Lough

Inductor-inductor-capacitor (LLC) resonant converters have a couple of appealing characteristics for applications requiring an isolated DC/DC converter such as minimal switching losses, no reverse recovery when operating below the resonant frequency and the ability to tolerate large leakage inductance within the transformer.

The challenge

A primary challenge when designing an LLC converter with a wide operating range is the behavior of the gain curve with respect to equivalent load resistance. This is because as the quality factor (Q_e), increases, the maximum attainable gain decreases. Conversely, the minimum attainable gain increases as Q_e decreases. This is shown in Figure 1 below.

$$Q_e = \frac{\sqrt{L_r C_r}}{R_e} \quad (1)$$

$$L_n = \frac{L_m}{L_r} \quad (2)$$

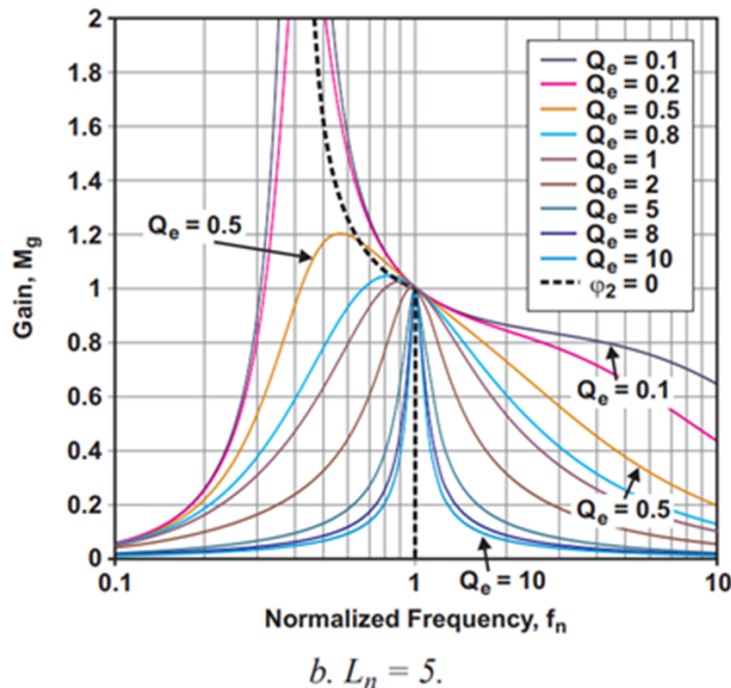


Figure 1. LLC gain curves showing that, as Q_e increases, the maximum attainable gain decreases.
Source: Texas Instruments

This behavior makes it difficult to maintain reasonable root-mean-square (RMS) currents in the power stage and a reasonable switching frequency range. The inductance ratio (L_n) needs to be reduced to reduce the required

frequency range; however, a lower inductance ratio increases the magnetizing current in the power stage. This article will discuss five tips for designing an LLC converter with a wide operating range.

Using a reconfigurable rectifier

One potential way to extend an LLC converter's operating range is to implement a reconfigurable rectifier, as shown in [Figure 2](#).

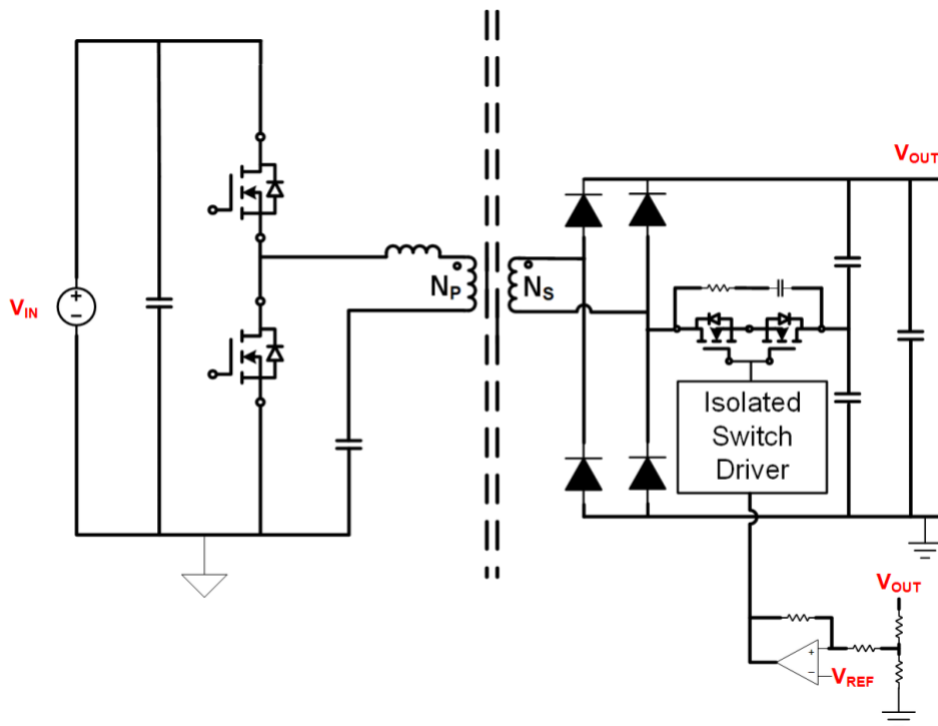


Figure 2. shows an LLC converter with a reconfigurable rectifier, which can be reconfigured as either a full-bridge or a voltage-doubler. Source: Texas Instruments

In this structure, you can configure the rectifier as a full-bridge or a voltage-doubler rectifier by using a comparator to look at the output voltage to decide the mode of operation. When operating as a full-bridge rectifier, Equation 3 calculates the input-to-output transfer function.

$$V_{out} = M_g(f_{sw}) \times \frac{1}{n} \times \frac{V_{in}}{2} \quad (3)$$

When operating as a voltage doubler rectifier, the input-to-output transfer function is:

$$V_{out} = 2 \times M_g(f_{sw}) \times \frac{1}{n} \times \frac{V_{in}}{2} \quad (4)$$

[Figure 3](#) shows the switching frequency versus output voltage for an LLC using the above approach to achieve a 140V to 420V output voltage range from a fixed 450V input. This data is collected with an 800mA load on the output. Notice the jump at 200V where the comparator switches from full-bridge to voltage-doubler mode.

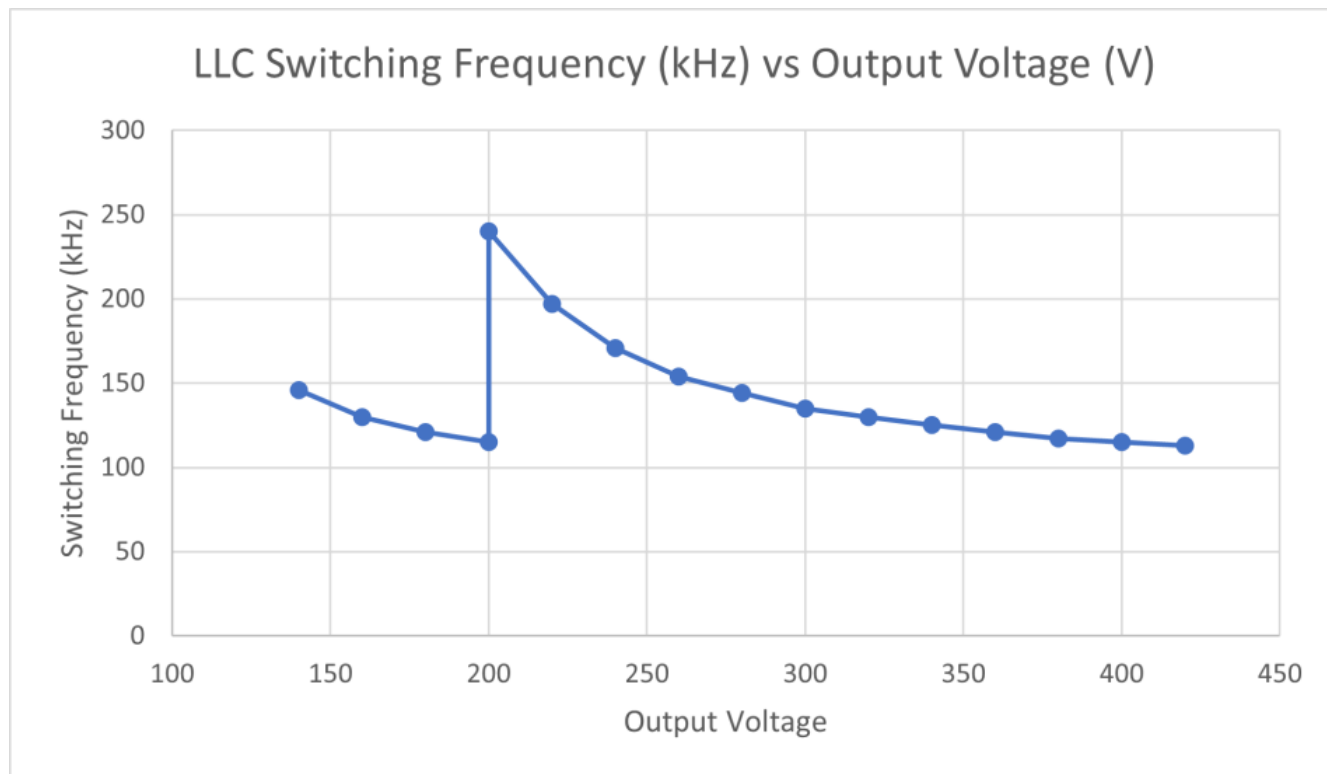


Figure 3. Switching frequency versus output voltage in LED driver reference design. Source: Texas Instruments

Minimizing winding and rectifier capacitance

If the operating point drops below the minimum gain curve, the LLC controller is forced to operate in burst mode to keep the output voltage in regulation. Burst mode results in higher low-frequency output ripple voltage. This is a concern for applications requiring very low output ripple at light load and at the minimum output voltage.

In such cases, the winding capacitance within the transformer and the output capacitance (C_{oss}) or junction capacitance (C_j) of the rectifiers must be minimized. These parasitic capacitances will cause the gain curve to invert when operating above the resonant frequency. [Figure 4](#) shows the traditional first harmonic approximation (FHA) calculation of an LLC gain curve at light load and the same LLC gain curve when accounting for winding the capacitance and C_{oss} of the rectifiers used in the power stage.

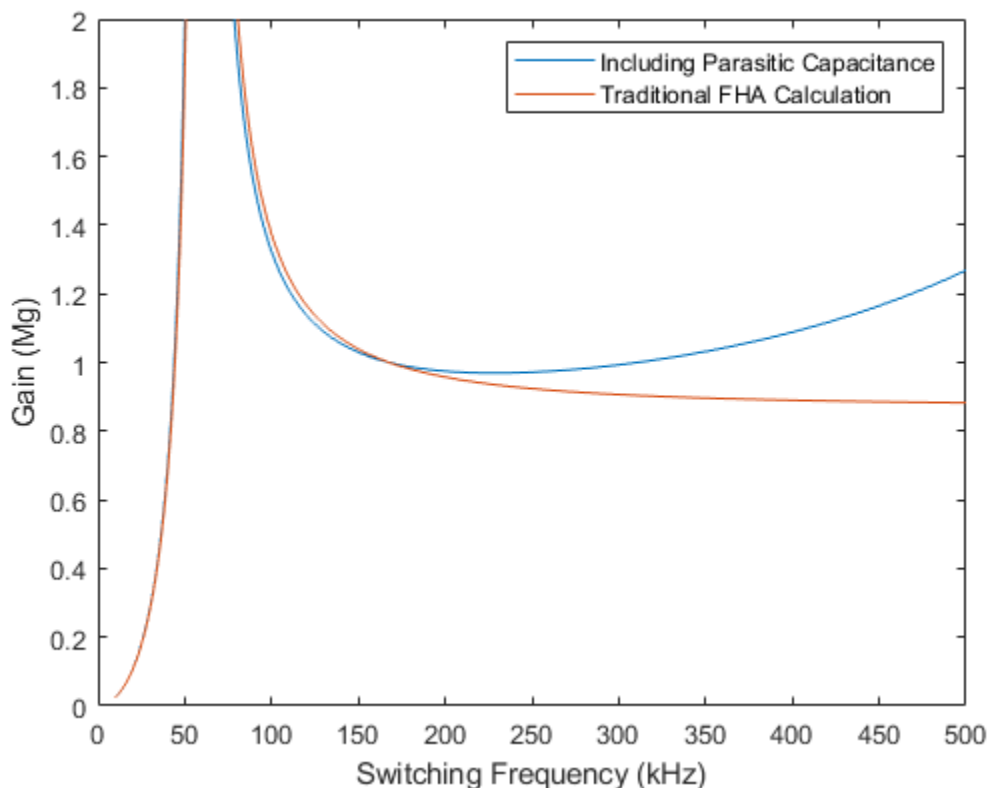


Figure 4. The impact of parasitic capacitance on the LLC gain curve at light load. Source: Texas Instruments

Careful attention to the winding stackup within the transformer and selection of the rectifier components minimizes this gain curve inversion effect. Using wide bandgap devices such as SiC diodes or GaN high electron mobility transistors (HEMTs) as the rectifier can result in considerably lower C_{oss} compared to Si MOSFETs or diodes.

Using LLC controllers with a high-frequency skip mode

A high-frequency skip mode can achieve a lower gain compared to what is achievable with normal switching. Below is an example from a 100W half-bridge LLC converter with an input range of 70V to 450V. In [Figure 5](#), the resonant current is shown in green, and the primary side switch node is shown in blue.

On the right side, the LLC converter is operating in a high-frequency skip mode, omitting every fourth switching cycle. The switching frequency is 260kHz, but it is sub-modulated at a 77kHz burst frequency.

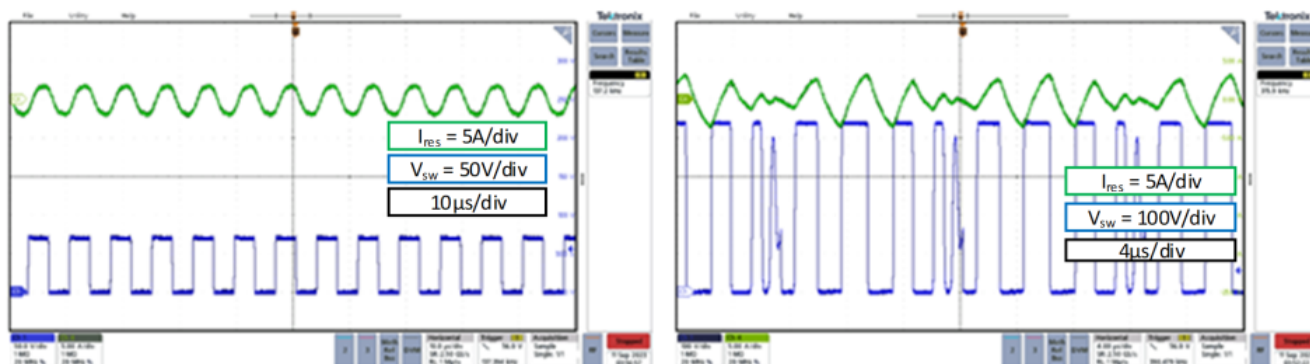


Figure 5. The 100W LLC converter switching behavior at 70V and 450V inputs with resonant current in green and the primary side switch node in blue. Source: Texas Instruments

Managing auxiliary bias voltages

Generating the necessary bias voltages for the primary and secondary sides of the power supply can be done by including auxiliary windings on the LLC transformer. For LLC converters with a variable output voltage, the auxiliary winding voltages will change as the output voltage changes. This is especially true for LLC transformers using sectioned bobbins where the auxiliary windings have poor coupling to the secondary windings. When using a simple low-dropout regulator (LDO) structure to regulate the bias voltage, the efficiency will drop as the output voltage increases. It may require a larger physical package to handle the power dissipation.

In Figure 6, N_{aux1} and N_{aux2} are sized so that at the lowest output voltage, or the VCC bias voltage, is provided through D1, Q1, and D4. As the output voltage increases, the voltage on C2 is limited to the breakdown voltage of Zener D3 minus the gate-source threshold voltage of Q1. As the output voltage is increased further, the voltage generated by N_{aux2} becomes high enough to supply VCC, and Q1 is forced off as the gate-source voltage decreases below the turn-off threshold.

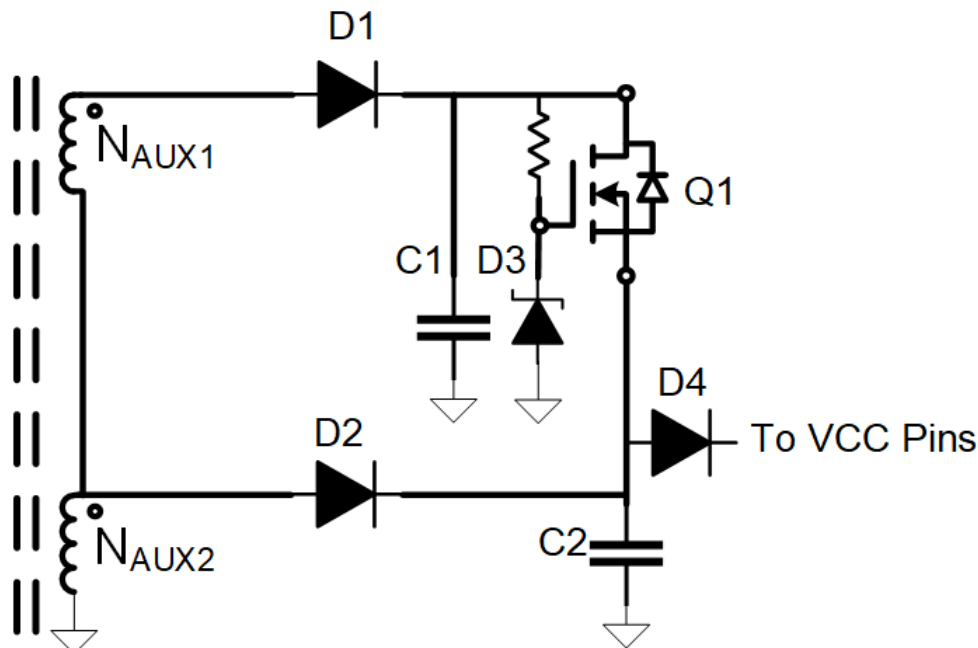


Figure 6. Using auxiliary windings along with an LDO structure to generate the necessary bias voltages for the primary and secondary side of the power supply. Source: Texas Instruments

This approach is more efficient than a single winding + LDO but requires two aux windings. An alternative approach that requires only one aux winding is to use a buck converter or boost converter instead of an LDO.

Managing trickle-charging for deeply discharged batteries

LLC converters used as battery chargers must safely recover deeply discharged batteries by applying a small charging current until the battery pack voltage is high enough to safely take the full charging current. LLCs cannot regulate down to a 0V output with a small output current and therefore struggle to meet this requirement.

This can be managed by including a small constant current circuit with a bypass FET in parallel, as shown in Figure 7. When in trickle-charge mode, the bypass FET turns off, and the output current is supplied by LM317 configured to regulate the output current. This allows the minimum output voltage of the LLC converter to be greater than 0V, even with an output voltage of 0V. This approach allows the LLC transformer to generate the necessary bias voltages on the primary and secondary side and avoid needing a separate bias supply when the output voltage is 0V. Once the battery pack voltage has risen to a high-enough level, a FET with a discrete charge-pump circuit bypasses the constant-current circuit.

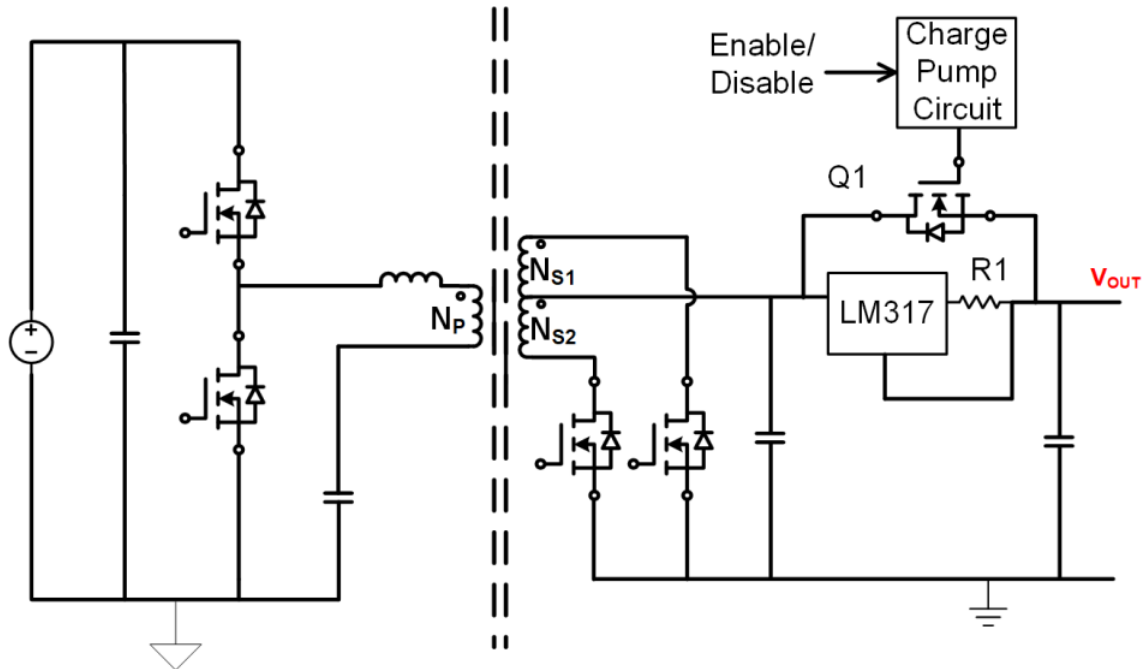


Figure 7. LLC with a trickle charging circuit that can safely recover deeply discharged batteries. Source: Texas Instruments

Wide LLC operation

While achieving a wide operating range with an LLC converter may look difficult due to the nature of the LLC topology, several strategies exist for obtaining a wide operating range easier to achieve. The five simple tips and tricks listed here are analog-control friendly and do not require more complex, digital-control implementations.

Related Content

- [Power Tips #117: Measure your LLC resonant tank before testing at full operating conditions](#)
- [Power Tips #137: Implementing LLC current-mode control on the secondary side with a digital controller](#)
- [Power Tips #84: Think outside the LLC series resonant converter box](#)
- [Power Tips #103: LLC design considerations for audio amplifiers](#)

Previously published on EDN.com.

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2025, Texas Instruments Incorporated