


# How to design a high-voltage DCM inverting charge pump converter



John Betten

A low-current, negative high-voltage is required to bias sensors in advanced driver assistance systems, ultrasonic transducers for sonar applications, and communications equipment. Flyback, Cuk, and inverting buck-boost converters are all possible solutions, but are penalized by bulky transformers (flyback and Cuk) or limited in their maximum negative voltage by the controller's input-voltage rating (inverting buck-boost). In this power tip, I'll detail the operation of a converter that pairs a single inductor with an inverting charge pump operating in discontinuous conduction mode (DCM). Paired with a ground referenced boost controller, a large negative output voltage can be generated at a lower system cost.

Figure 1 shows a simplified power-stage schematic. Note that this schematic is different from a traditional inverting buck-boost converter, which "floats" the controller between  $V_{IN}$  and  $-V_{OUT}$ . In that converter, the maximum  $-V_{OUT}$  achievable is the maximum  $V_{CC}$  of the controller **minus** the maximum input voltage. This would make it nearly impossible to find a controller that can drive an N-channel field-effect transistor (FET) for an output voltage of  $-100V$  or more.

 


**Figure 1. Simplified power stage of an inductor-driven inverting charge pump**

The circuit's operation can be split into three intervals (Figure 2). In the first interval, the FET is on during duty cycle ( $d$ ), which applies  $V_{IN}$  across the inductor, allowing current to ramp up from zero, storing energy. However, in the previous cycle,  $C1$  (which maintains a voltage of approximately equal to  $V_{OUT}$ ) has depleted its excess stored energy, reverse-biasing  $D1$  and  $D2$ . This is why  $D1$ ,  $D2$ , and  $C1$  are not shown in this interval.  $C2$  supplies all load current.


In the next interval,  $d'$ , the FET turns off and the inductor current begins to discharge, causing its voltage polarity to reverse. This greatly increases the voltage present at node  $VFET$ , allowing  $C1$  to recharge through  $D1$ . During this interval, current ramps downward until  $D1$  turns off. However, due to the reverse-recovery characteristics of  $D1$ , current goes negative before it eventually turns off, at which point the inductor current slope changes and its voltage polarity reverses once again.

The third interval,  $d''$ , is when the energy transfer from  $C1$  to  $C2$  takes place. When  $D1$  stops conducting, the inductor voltage is clamped to  $V_{IN}$  because the  $VFET$  node voltage is forced to ground by a current path through the FET's body diode. Current flows through  $D2$  until the voltages across  $C1$  and  $C2$  equalize, but current through the FET's body diode continues until the inductor's current reaches zero. At this point, the voltage across the inductor collapses and resonates with circuit parasitics until the FET turns on again.

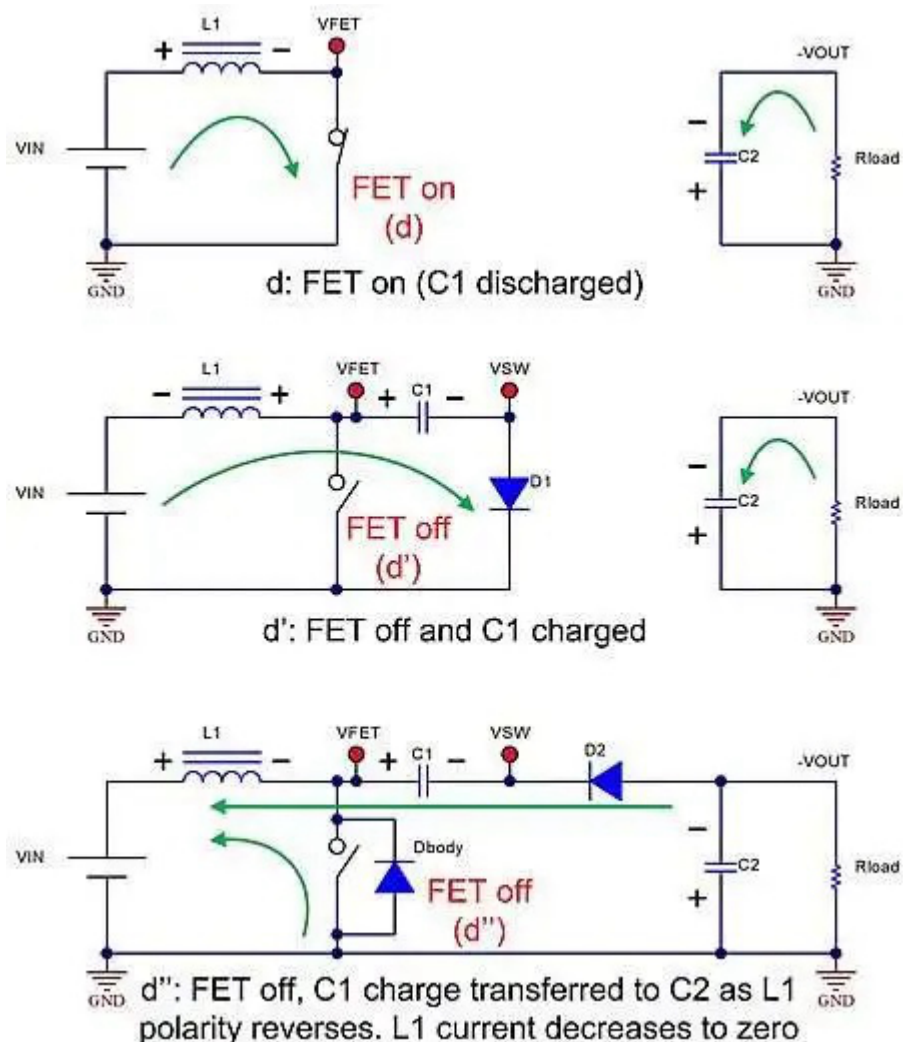

**Figure 2. The three phases of DCM operation**

Figure 3 details the key voltage and current waveforms. DCM operation allows for the smallest possible inductance, but with a higher peak current. Inductance for DCM operation is determined at the maximum duty cycle, minimum  $V_{IN}$  and full load. Carefully check the maximum duty cycle against the controller data sheet, but you can typically choose 60%-90%, or otherwise pulse skipping can occur. Larger inductances will push operation into continuous conduction mode (CCM), since the current will not return to zero before the next switching cycle. This results in using an inductor that may be larger than necessary and requires extra care to prevent subharmonic oscillation.

 

**Figure 3. Key circuit waveforms in DCM**

### Design equations

For DCM operation, Equation 1 satisfies the relationship involving the inductor's stored energy:

$$\frac{1}{2} * L * i_{pk}^2 * f_{sw} = \frac{V_{out}^2}{R_{load} * \eta} \quad (1)$$

where  $i_{pk}$  is the peak inductor current and  $\eta$  is the converter's efficiency. The peak inductor current is then equal to Equation 2:

$$i_{pk} = \sqrt{\frac{2 * V_{out}^2}{R_{load} * L * f_{sw} * \eta}} \quad (2)$$

From the following two equations, Equation 3 expresses the duty cycle (d) in terms of:

$$V_L = L \frac{di}{dt} \text{ and } d = dt * f_{sw}, \text{ then, } d = \frac{di * L * f_{sw}}{V_L} \quad (3)$$

Since  $V_{IN}$  is the voltage across the inductor when the FET is on and  $i_{pk}$  is the inductor current at the end of duty cycle  $d$ , substituting Equation 2 into Equation 3 yields Equations 4 and 5:

$$d = \frac{V_{out}}{V_{in}} \sqrt{\frac{2 * L * f_{sw}}{R_{load} * \eta}} \quad (4)$$

$$\text{or, } L = \frac{V_{in}^2 * d^2 * R_{load} * \eta}{2 * V_{out}^2 * f_{sw}} \quad (5)$$

The average load current is determined by the geometric relationship in Equations 6 and 7 during interval  $d'$ :

$$\frac{V_{out}}{R_{load}} = \frac{i_{pk} + d'r}{2} \quad (6)$$

$$\text{or, } d' = \frac{2 * V_{out}}{i_p * R_{load}} \quad (7)$$


Substituting Equation 2 into Equation 7 provides Equation 8:

$$d' = \sqrt{\frac{2 * L * f_{sw} * \eta}{R_{load}}} \quad (8)$$

The remainder of the period is defined as  $d''$ , which is when the energy transfers into C2 and the remaining inductor current discharges to zero (Equation 9):

$$d'' = 1 - d - d' = 1 - \frac{V_{out}}{V_{in}} \sqrt{\frac{2 * L * f_{sw}}{R_{load} * \eta}} - \sqrt{\frac{2 * L * f_{sw} * \eta}{R_{load}}} \quad (9)$$

Figure 4 shows an example schematic implementing this converter with a voltage doubler, which allows the voltage stress of each power-stage component to be equal to one-half of the full output voltage. This provides a wider selection of components from which to choose. In this application, the inductance was calculated as if the output voltage was one-half, but at twice the load current.

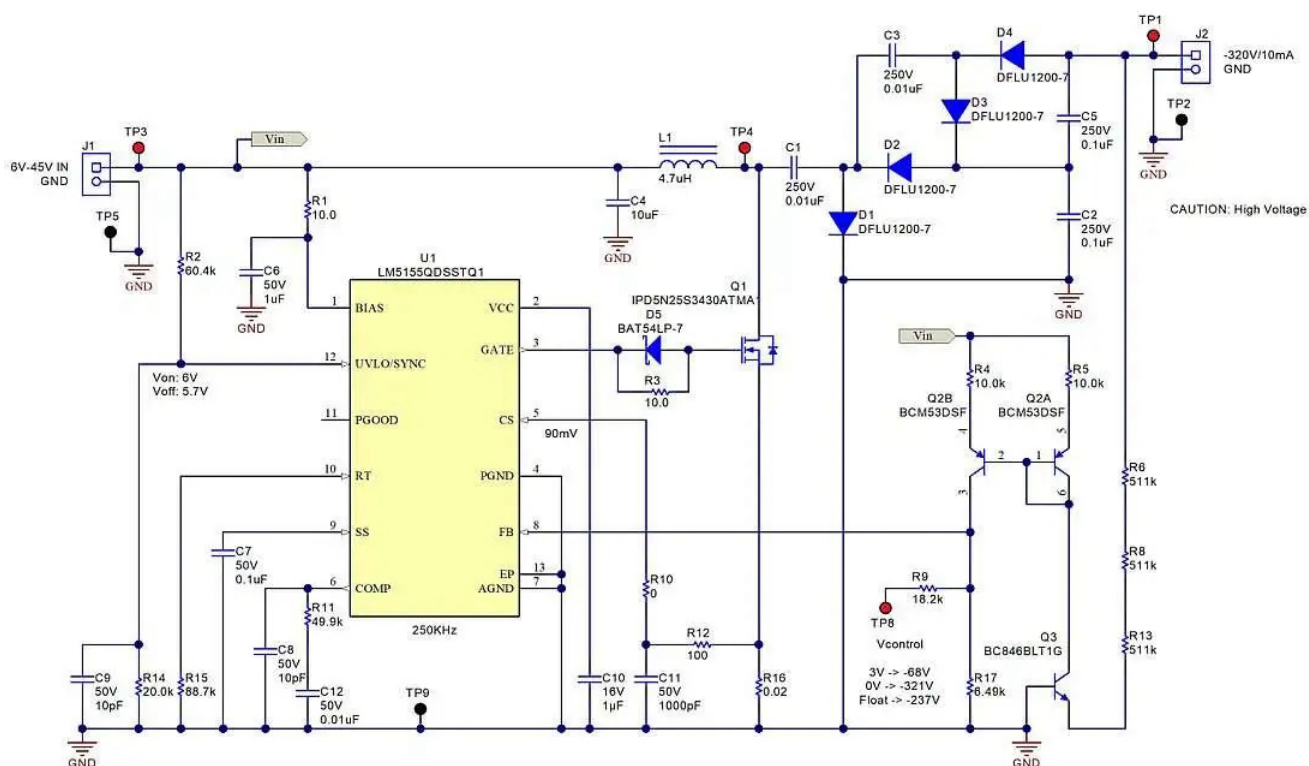

**Figure 4. Inductor-driven inverting charge pump with voltage doubler and level-shifting current mirror schematic**

This converter provides a small, single-inductor solution for generating a large negative voltage. Additionally, it allows the use of an inexpensive ground-referenced boost controller to drive an N-channel FET.

For more Power Tips, check out TI's [Power Tips blog series](#) on Power House.

#### Additional resources

- [Power Tips: Increase your output voltage with a voltage multiplier](#), EEtimes
- [Using the TPS5430 as an Inverting Buck Boost Converter \(Rev. A\)](#), TI Application Report

#### Related articles

- [Charge-pump topology doubles voltage, breaks DC path](#)
- [Modded charge pump extracts power from digital signal](#)
- [The ins and outs of charge-pump-converter ICs](#)
- [SEPIC/Ćuk converter sprouts second output](#)
- [Discontinuous conduction brings issues to current-mode converters](#)

Previously published on EDN.com.

#### Trademarks

All trademarks are the property of their respective owners.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2025, Texas Instruments Incorporated