

Test Report: PMP22343

+/-40-V Inverting Buck-Boost With Auxiliary Output Reference Design



Description

This reference design uses the TPS54560B in an inverting buck-boost topology to generate a -40-V output from a +5-V input. An auxiliary winding generates a +40-V output with reference to the same ground. For applications needing a positive and negative voltage, the buck topology provides a low-noise output with a minimal component count.

 


Figure 1. Board Top



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage Range	+5 V +/- 5%
Output Voltage 1	+40 V +/- 1%
Output Current 1	0.125 A max, 0.03 A typical
Output Voltage 2	-40 V +/- 1%
Output Current 2	0.125 A max, 0.03 A typical

1.2 Considerations

For all tests a resistive load was used for Outputs 1 and 2. Also the input voltage was set to 5 V. Unless otherwise indicated, outputs 1 and 2 were loaded to 0.125 A for all tests.

2 Testing and Results

2.1 Efficiency Chart

		+40Vdc Output		
		0 A	0.03 A	0.125 A
-40 Vdc output	0 A	25.686 %	76.275 %	83.823 %
	0.03 A	74.520 %	79.440 %	84.606 %
	0.125 A	83.642 %	84.392 %	80.730 %

Figure 2. Efficiency chart for various loading conditions

2.2 Efficiency and Cross Regulation Data

+40 V Output			-40 V Output		
Voltage (V)	Current (A)	Power (W)	Voltage (V)	Current (A)	Power (W)
40.381	0.001	0.040	-40.580	-0.001	0.041
39.608	0.030	1.188	-41.355	-0.001	0.041
37.399	0.125	4.675	-43.564	-0.001	0.044
40.604	0.001	0.041	-40.366	-0.030	1.211
40.338	0.030	1.210	-40.618	-0.030	1.219
40.103	0.125	5.013	-40.951	-0.030	1.229
40.835	0.001	0.041	-40.068	-0.125	5.009
40.452	0.030	1.214	-40.443	-0.125	5.055
40.020	0.125	5.003	-40.886	-0.125	5.111

Input			Calculations		
Voltage (V)	Current (A)	Power (W)	Output Power (W)	Efficiency (%)	Losses (W)
5.059	0.062	0.315	0.081	25.686	0.234
5.038	0.320	1.612	1.230	76.275	0.382
4.970	1.133	5.629	4.718	83.823	0.911
5.038	0.333	1.680	1.252	74.520	0.428
5.014	0.610	3.057	2.429	79.440	0.629
4.924	1.498	7.377	6.241	84.606	1.136
4.963	1.216	6.037	5.049	83.643	0.987
4.939	1.504	7.428	6.269	84.392	1.159
4.847	2.585	12.527	10.113	80.730	2.414

Figure 3. Raw data for cross loading conditions

2.3 Waveforms

2.3.1 Switching

The switch node was measured across the rectifier diode (D2). The stresses on D2 were the same as D1 on the +40 V output.

 


Figure 4. Primary Switching Node

2.3.2 Output Voltage Ripple

Measurements were taken using the tip and barrel method across the output cap (C4 for the +40 V output, C11 for the -40 V output).

 


Figure 5. Output voltage ripple of the +40 V output

 


Figure 6. Output voltage ripple of the +40 V output

2.3.3 Load Transients

The output voltage (AC coupled) was measured across the +40 V output capacitor (C4). The -40 V output was loaded to 30 mA (typical loading).

 


Figure 7. Load stepping Output 1 between 0.2 A and 1 A

2.3.4 Control Loop/Stability

The table below shows the bandwidth and phase margin measurements.

 


Figure 8.

Input Voltage (V)	Bandwidth (kHz)	Phase Margin (degrees)
5	4.559	49.95

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated