

Test Report: PMP41006

1-kW Reference Design With CCM TotemPole PFC and Current Mode LLC Realized by C2000 and GaN



Description

This reference design demonstrates a hybrid hysteresis control (HHC) method, a kind of current-mode control method, on half-bridge LLC stage with a C2000 F28004x microcontroller. The hardware is based on TIDA-010062, which is 1-kW, 80 Plus titanium, GaN CCM totem pole bridgeless PFC and half-bridge LLC reference design. A separated sensing card is added for hybrid hysteresis control, which recreates the voltage on the resonant capacitor. This test result shows better transient response and ease-of-control loop design, compared with the single-loop voltage mode control method (VMC).

Features

- 80 plus titanium efficiency, $\eta = > 95\%$ at 20%–100% load
- Fast load transient, V_O change within 300 mV at 2.5-A/ μ s slew rate
- CCM GaN based totem-pole bridgeless PFC stage with $> 99\%$ peak efficiency, enabled by LMG341x GaN FET with integrated driver
- Half-bridge Si MOSFET LLC stage with $> 98\%$ peak efficiency
- Power density 39 W/in₃, 38 mm × 66 mm × 165 mm

Applications


- [Merchant network and server PSU](#)
- [Merchant telecom rectifiers](#)
- [Industrial AC-DC](#)



Top View



Bottom View

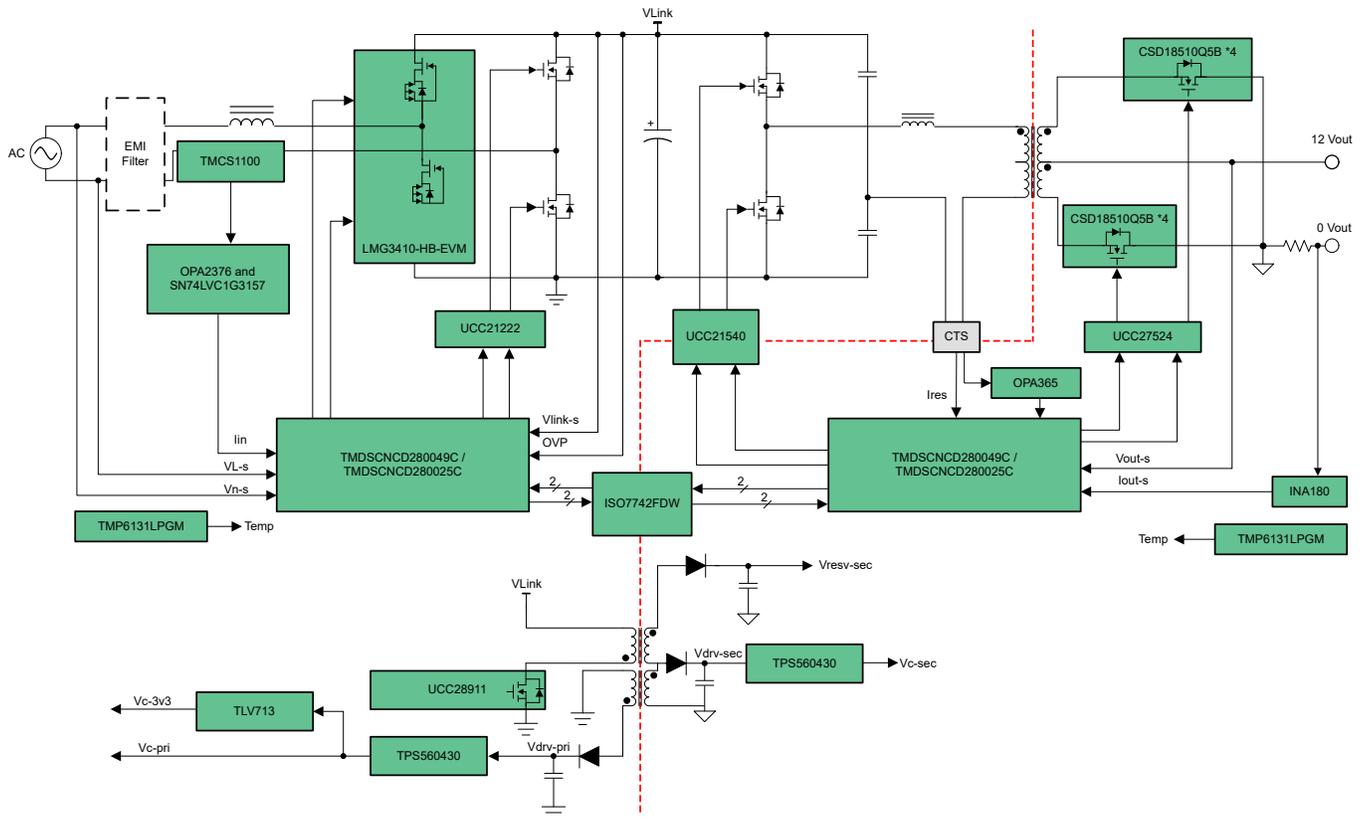

Block Diagram or Simplified Schematic

1 Test Prerequisites

1.1 Key System Requirements

Key System Specifications

Parameter	Test Condition	MIN	NOM	MAX	Units
AC Input voltage (Low line)		100	115	132	V
AC Input voltage (High line)		180	230	264	V
Line Frequency		47		63	Hz
Output voltage	All line and load conditions ($\pm 5\%$)	11.4	12	12.6	V
Output Current				84	A
PF	230V _{in} , 100% load		0.99		
iTHD	10% load			<10%	
	100% load			<2%	
Ripple and noise	12V main output			$\pm 120\text{mV}$	mV
AC holdup time	@ 100% load, within V _{out} regulation	8	10		mS
Dynamic loading and transient response	50% of I _{out-max} , 2.5A/ μs , 3300 μF Capacitive load		$\pm 5\%$		%
Operating ambient		0	25	50	$^{\circ}\text{C}$
OCP of 12-V output	Shut-down, latch-off	110		130	% of I _{omax}
OVP of 12-V output	Shut-down, latch-off	13		14.5	V
Dimension (mm)	Without shell and golden finger		165*66*38		mm
Power density			39		W/in ³

2 Testing and Results

Since this design is generated from TIDA-010062, its power stage performance is the same as the TIDA-010062. This document only highlights the performance related to the HHC LLC control.

2.1 Sensed VCR and Output Voltage Ripple Under Different Loads

The following parameters apply to [Figure 2-1](#) and [Figure 2-2](#).

- CH1: output current
- CH2: VCR feedback signal
- CH3: output voltage
- CH4: PWM1A output

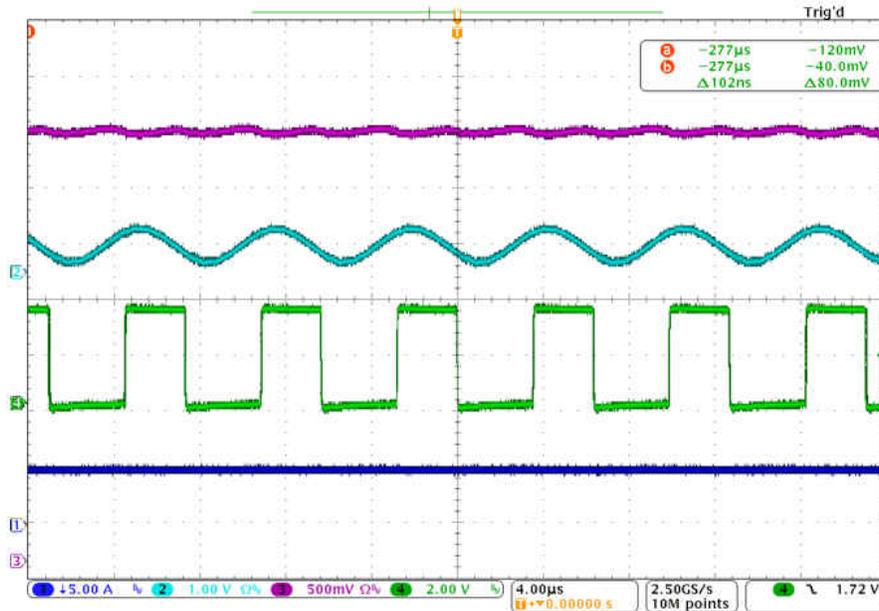


Figure 2-1. Load Current Equals 20 A (24% Load)

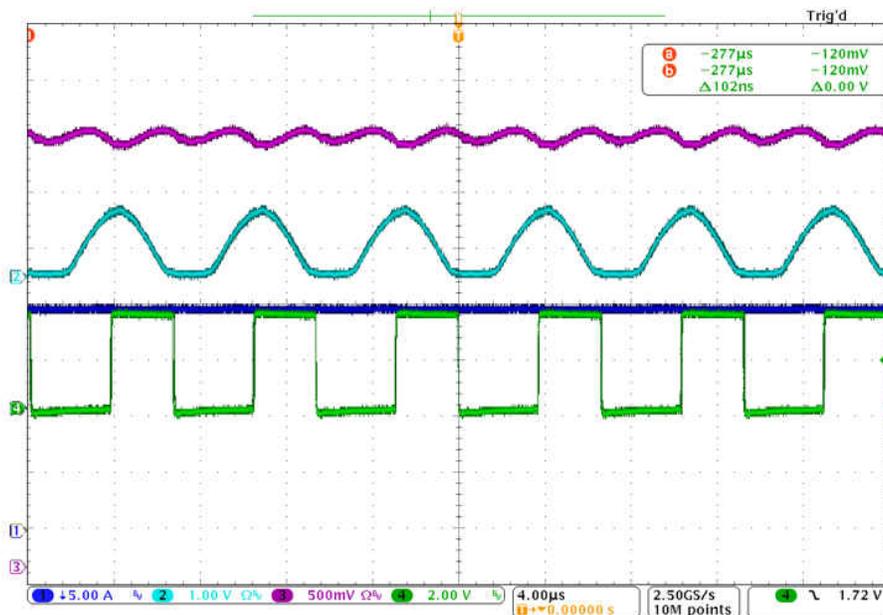


Figure 2-2. Load Current Equals 50 A (60% Load)

2.2 Control Loop Bode Plot Comparison

The voltage control loop bode plot is measured using SFRA (Software Frequency Response Analyzer) based on the C2000 MCU.

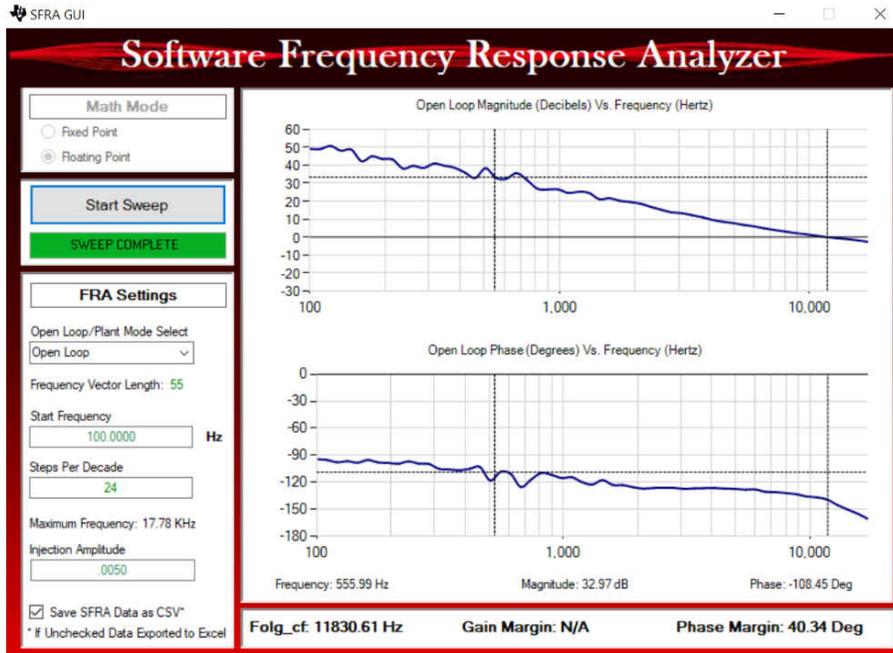


Figure 2-3. HHC Voltage Loop Bode Plot

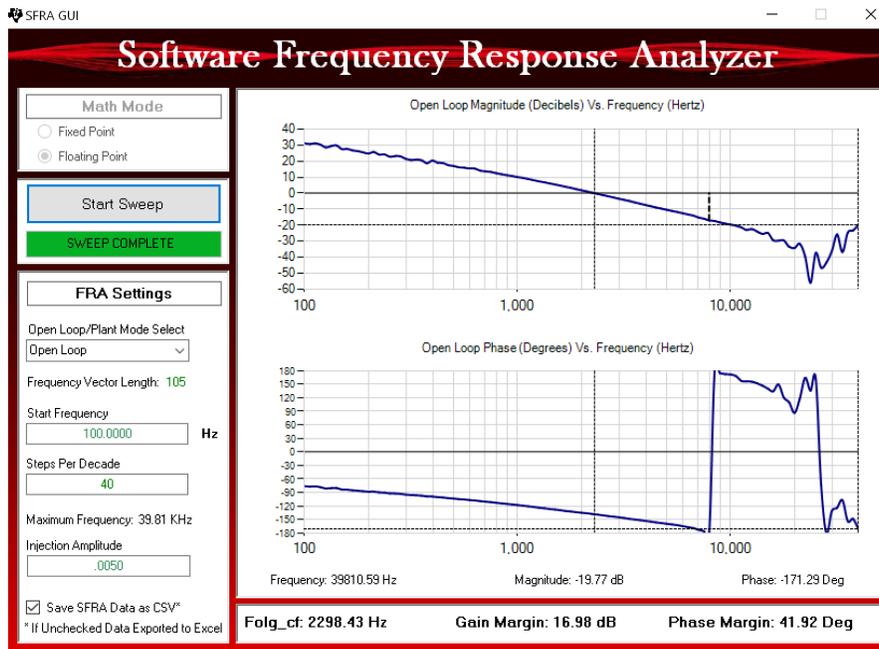


Figure 2-4. VMC Voltage Loop Bode Plot

2.3 Transient Response Test

The following tables present load transient comparisons between HHC and VMC:

Table 2-1. V_{OUT} Deviation Comparison Between HHC and VMC

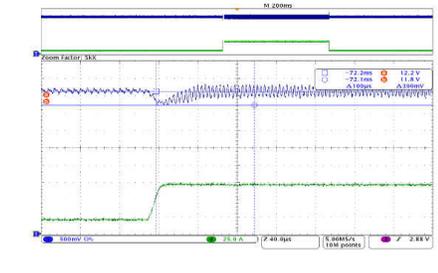
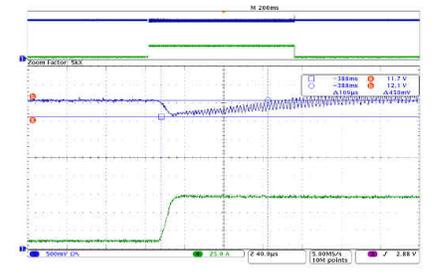
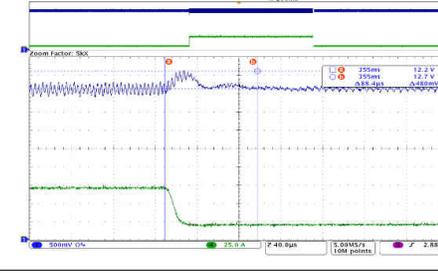
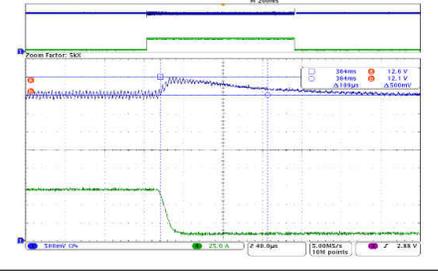
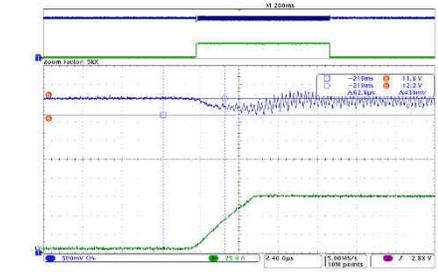
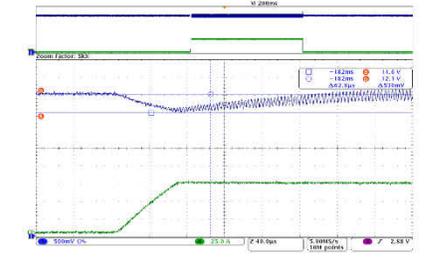
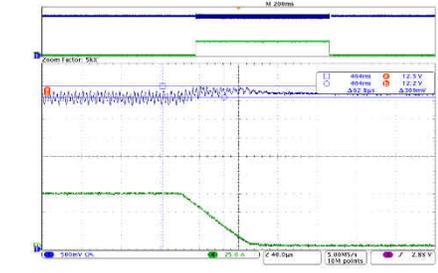
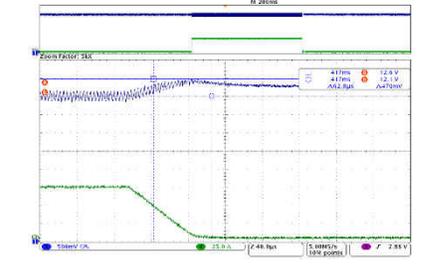
Load Transient Parameters	HHC	VMC	Output Capacitance: $3300 \mu\text{F} \times 2$
25% → 85% Load Transient (4 A/ μs) Transition: 10 μs			HHC: 390 mV vs VMC: 450 mV
85% → 25% Load Transient (4 A/ μs) Transition: 10 μs			HHC: 480 mV vs VMC: 500 mV
1 A → 70 A Load Transient (1 A/ μs) Transition: 60 μs			HHC: 430 mV vs VMC: 530 mV
70 A → 1 A Load Transient (1 A/ μs) Transition: 60 μs			HHC: 300 mV vs VMC: 470 mV

Table 2-2. Settling Time Comparison Between HHC and VMC

Load Transient Parameters	HHC	VMC	Output Capacitance: 3300 $\mu\text{F} \times 2$
25% \rightarrow 85% Load Transient (4 A/ μs) Transition: 10 μs			HHC: 76.8 μs vs VMC: 538 μs
85% \rightarrow 25% Load Transient (4 A/ μs) Transition: 10 μs			HHC: 88.4 μs vs VMC: 404 μs

2.4 References

- Texas Instruments, [1-kW, 80 Plus Titanium, GaN CCM Totem Pole Bridgeless PFC and Half-Bridge LLC reference design guide](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated