

Isolated 10-W PSR DCM Flyback Reference Design



Description

This design introduces a tiny isolated auxiliary power supply used to supply automotive IGBT drive. The three isolated outputs support three gate controls, each output delivers +15 V and -5 V. An additional +10-V output is provided on the primary side. To simplify transformer windings, a virtual ground by ZENER diodes is implemented on the secondary side and well suited for symmetrical loading.


The flyback converter itself supports input voltage cranking as low as 5 V_{min} and load dump up to 42 V_{max}.

Features

- Simple transformer due to virtual ground by ZENER dividers
- Primary side regulation avoids optoisolator
- Three isolated HV outputs plus single LV output, 3-kV isolation voltage
- Wide input voltage range supports cranking to 5 V and load dump 42 V

Applications

- Traction inverter-high voltage

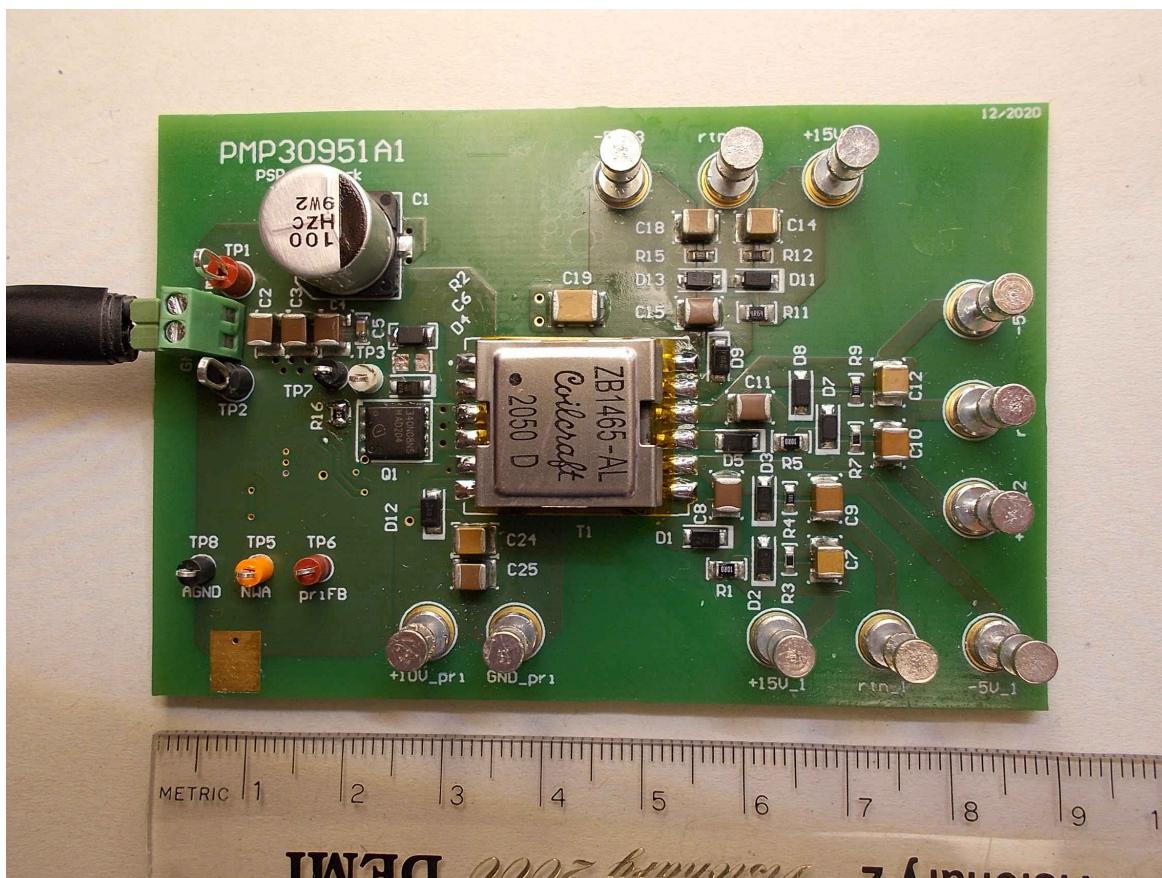

Top Photo

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Parameter	Specifications
Input Voltage Range	8 V to 16 V typical (5 V _{min} , 42 V _{max})
Primary (Non-Isolated) Output Voltage	+10 V at 0.2 A _{max}
Secondary Positive Output Channel 1 and 2	+15 V at 0.075 A _{max}
Secondary Negative Output Channel 1 and 2	-5 V at 0.075 A _{max}
Secondary Positive Output Channel 3	+15 V at 0.15 A _{max}
Secondary Negative Output Channel 3	-5 V at 0.15 A _{max}
Switching Frequency	200 kHz

1.2 Considerations

Keep the following considerations in mind while working with this design:

- Unless otherwise indicated, input voltage was set to 12 V
- Resistors were used as load
- Output currents were set to full load
- Cut the PCG trace to insert diode D101
- Measured switching frequency \Rightarrow 200 kHz
- Undervoltage lockout ON \Rightarrow 7 V
- Undervoltage lockout OFF \Rightarrow 5 V

1.3 Dimensions

The dimensions of the PCB are 88 mm \times 58 mm.

2 Testing and Results

2.1 Efficiency Graphs

The following graph shows efficiency and loss versus percentage of load.

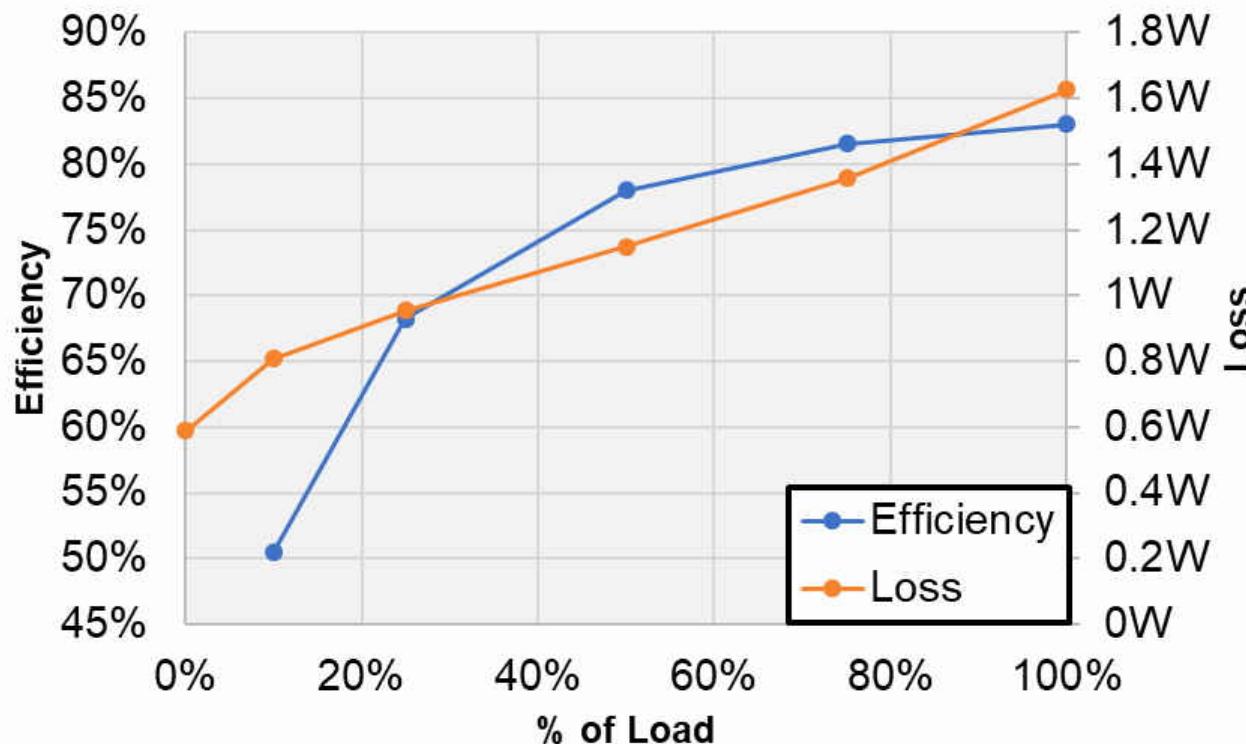


Figure 2-1. Efficiency Graph

2.2 Efficiency Data

Efficiency data for special cases (cross regulation) is shown in the following table.

Table 2-1. Efficiency Data for Special Cases (Cross Regulation)

	Case A	Case B
V_{IN}	12.004	12.018
I_{IN}	0.5626	0.456
V_{OP}	10.122	10.1224
I_{OP}	0.2007	0.2007
U_{OS1+}	15.14	15.16
I_{OS1+}	0.0751	0.0752
U_{OS1-}	4.841	4.847
I_{OS1-}	0.0733	0.0732
U_{OS2+}	15.14	15.75
I_{OS2+}	0.0756	0.008
U_{OS2-}	4.86	5.06
I_{OS2-}	0.0726	0.0076
U_{OS3+}	15.74	15.76
I_{OS3+}	0.0152	0.0152
U_{OS3-}	5.061	5.065
I_{OS3-}	0.0146	0.0147
$P_{IN} = U_{IN} \times I_{IN}$	6.753	5.480
$P_{op} = V_{OP} \times I_{OP}$	2.031	2.032
$PO_{S1+} = (U_{OS1+}) \times (I_{OS1+})$	1.137	1.140
$PO_{S1-} = (U_{OS1-}) \times (I_{OS1-})$	0.355	0.355
$PO_{S2+} = (U_{OS2+}) \times (I_{OS2+})$	1.145	0.126
$PO_{S2-} = (U_{OS2-}) \times (I_{OS2-})$	0.353	0.038
$PO_{S3+} = (U_{OS3+}) \times (I_{OS3+})$	0.239	0.240
$PO_{S3-} = (U_{OS3-}) \times (I_{OS3-})$	0.074	0.074
$P_O = PO_{S1+} + PO_{S1-} + PO_{S2+} + PO_{S2-} + PO_{S3+} + PO_{S3-}$	5.334	4.005
$Eff = P_O / P_{IN}$	0.790	0.731
$Loss = P_{IN} - P_O$	1.420	1.475

Case A \Rightarrow Primary, Secondary 1 and 2 \Rightarrow full load; Secondary 3 \Rightarrow 10%

Case B \Rightarrow Primary, Secondary 1 \Rightarrow full load; Secondary 2 and 3 \Rightarrow 10%

Positive voltage 15 V varies in between 15.14 V to 15.76 V

Negative voltage -5 V varies in between -4.86 V to -5.07 V

2.3 Load Regulation

2.3.1 Primary Output

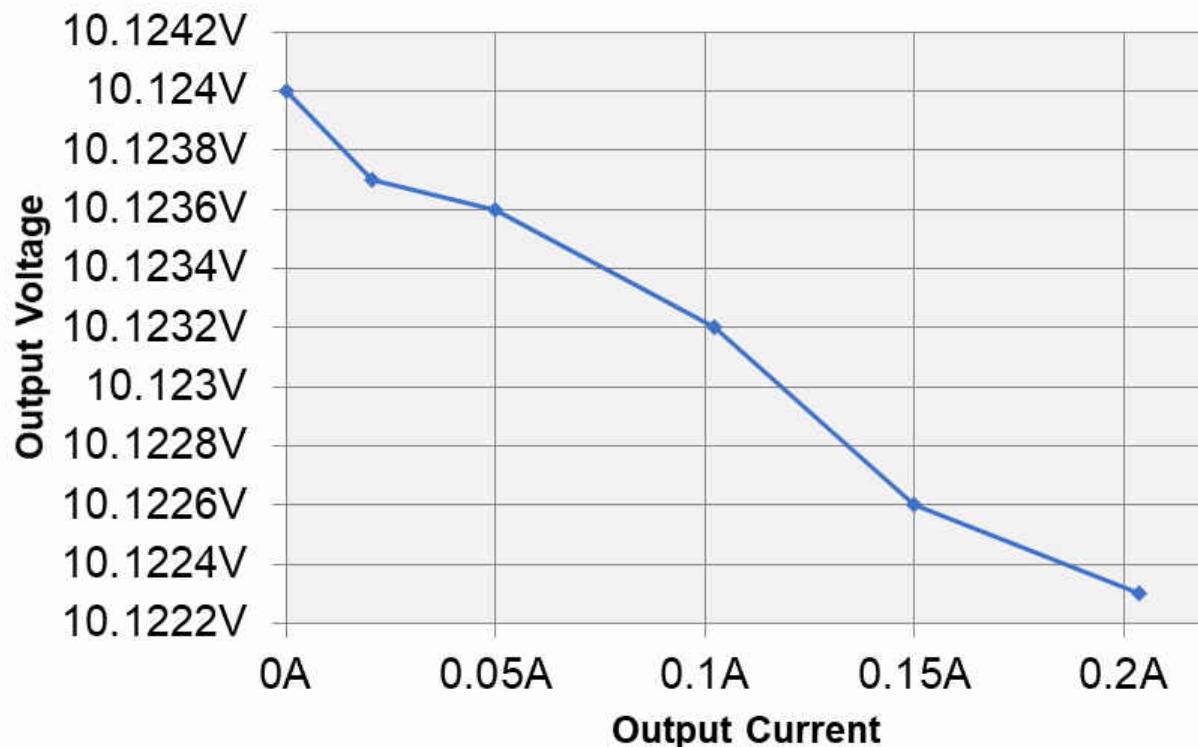


Figure 2-2. Output Voltage vs Output Current (Primary Output)

2.3.2 Secondary Outputs

The following images show the load regulation of the secondary outputs.

2.3.2.1 Positive Outputs

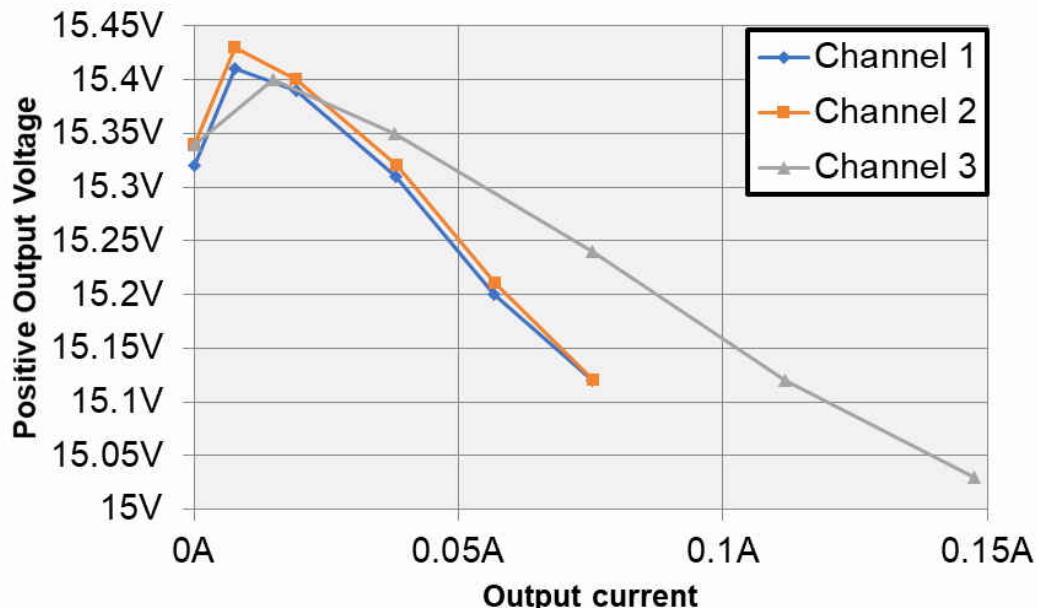


Figure 2-3. Output Voltage vs Output Current (Positive Outputs)

2.3.2.2 Negative Outputs

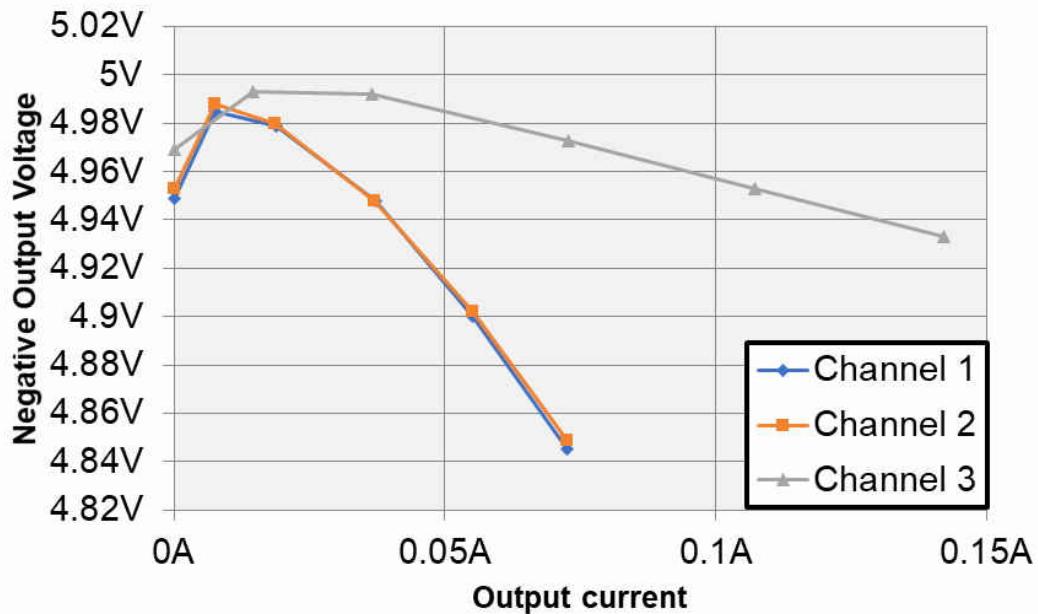


Figure 2-4. Output Voltage vs Output Current (Negative Outputs)

2.4 Line Regulation

2.4.1 Primary Output

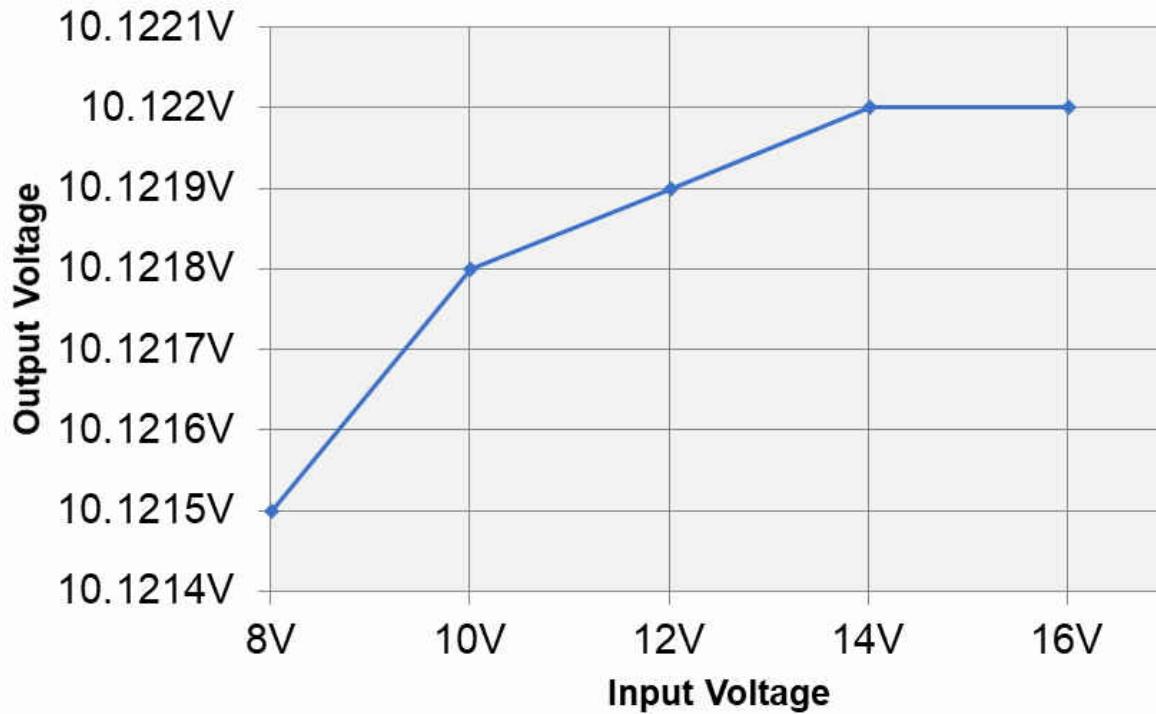


Figure 2-5. Primary Output Voltage vs Input Voltage

2.4.2 Secondary Outputs

The following images show the line regulation of the secondary outputs.

2.4.2.1 Positive Outputs

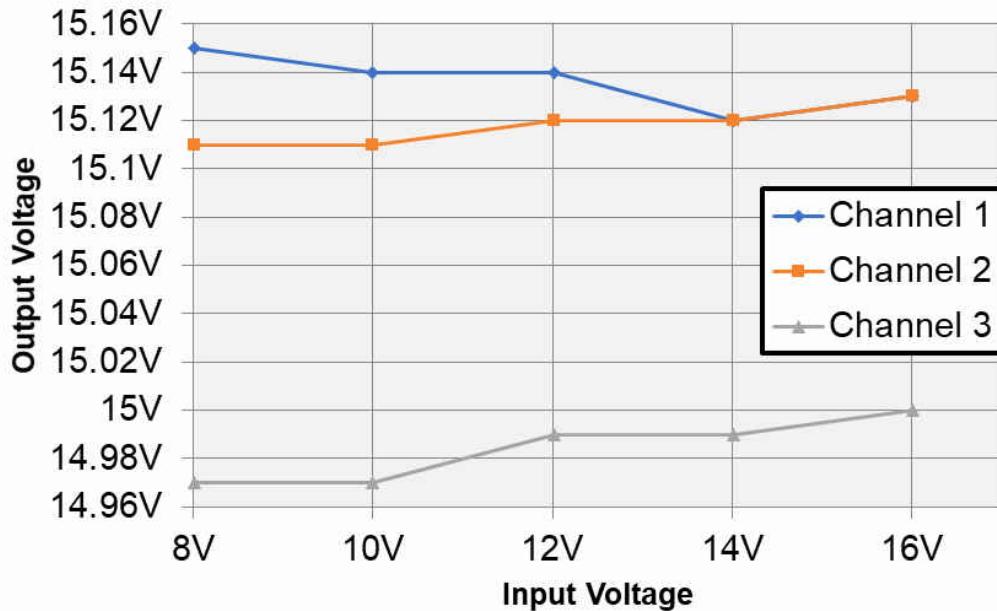


Figure 2-6. Secondary Output Voltages vs Input Voltage (Positive Outputs)

2.4.2.2 Negative Outputs

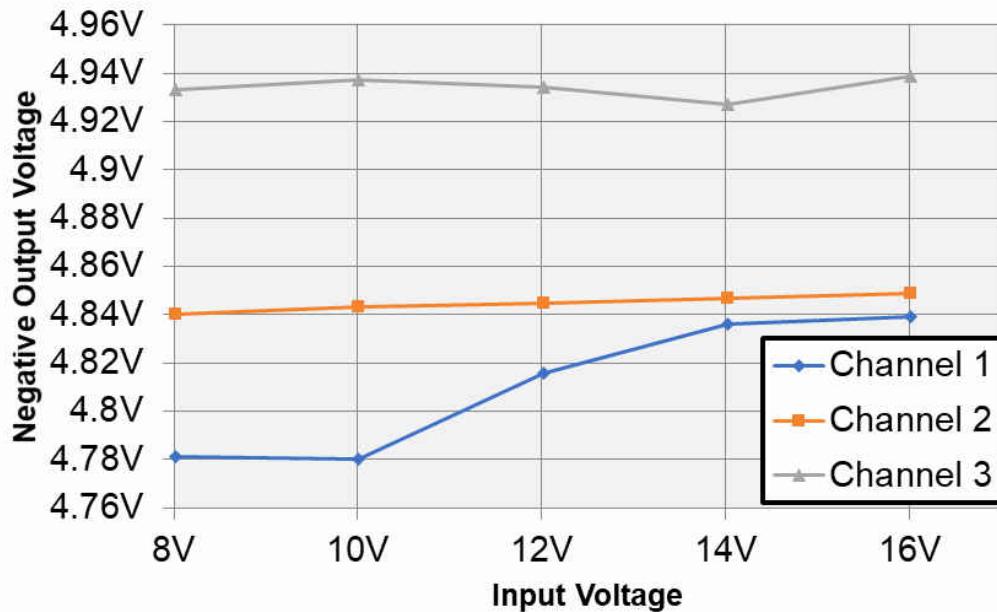


Figure 2-7. Output Voltage vs Input Voltage (Negative Outputs)

2.5 Thermal Images

The thermal image is shown in the following figure. Transformer T1 was painted black.

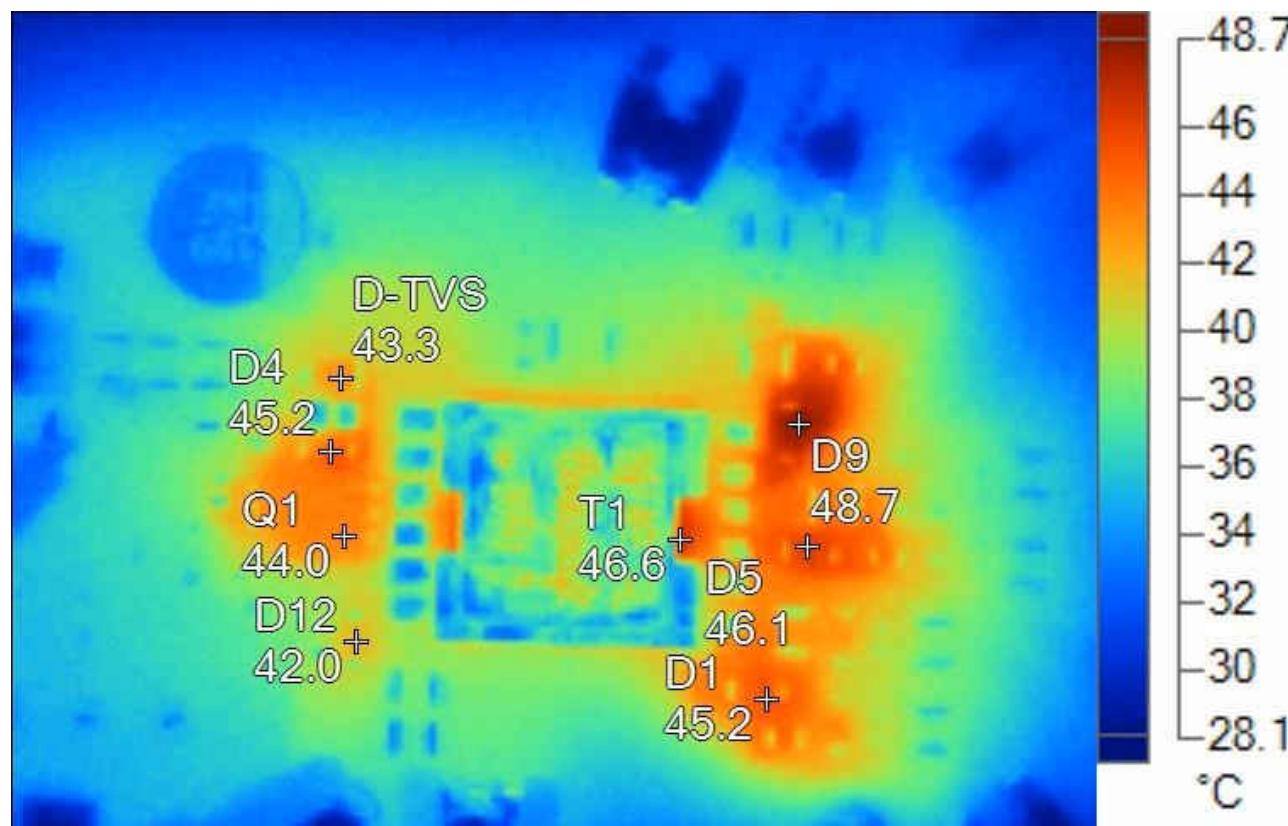


Figure 2-8. Thermal Image, Full Load, Input 12 V at Ambient Temperature 23°C

Name	Temperature
D1	45.2°C
D12	42.0°C
D4	45.2°C
D5	46.1°C
D9	48.7°C
D-TVS	43.3°C
Q1	44.0°C
T1	46.6°C

The maximum temperature rise is below 30 K.

2.6 Bode Plots

The table below summarizes the bode plots in the following figures.

V_{in}	5.5 V	12 V
Bandwidth (kHz)	13	15.6
Phase Margin	84°	83°
Slope (20 dB/decade)	-0.93	-0.98
Gain Margin (dB)	-14.7	-16.4
Slope (20 dB/decade)	-0.92	-1.6
Freq (kHz)	83	83

2.6.1 5.5-V Input Voltage

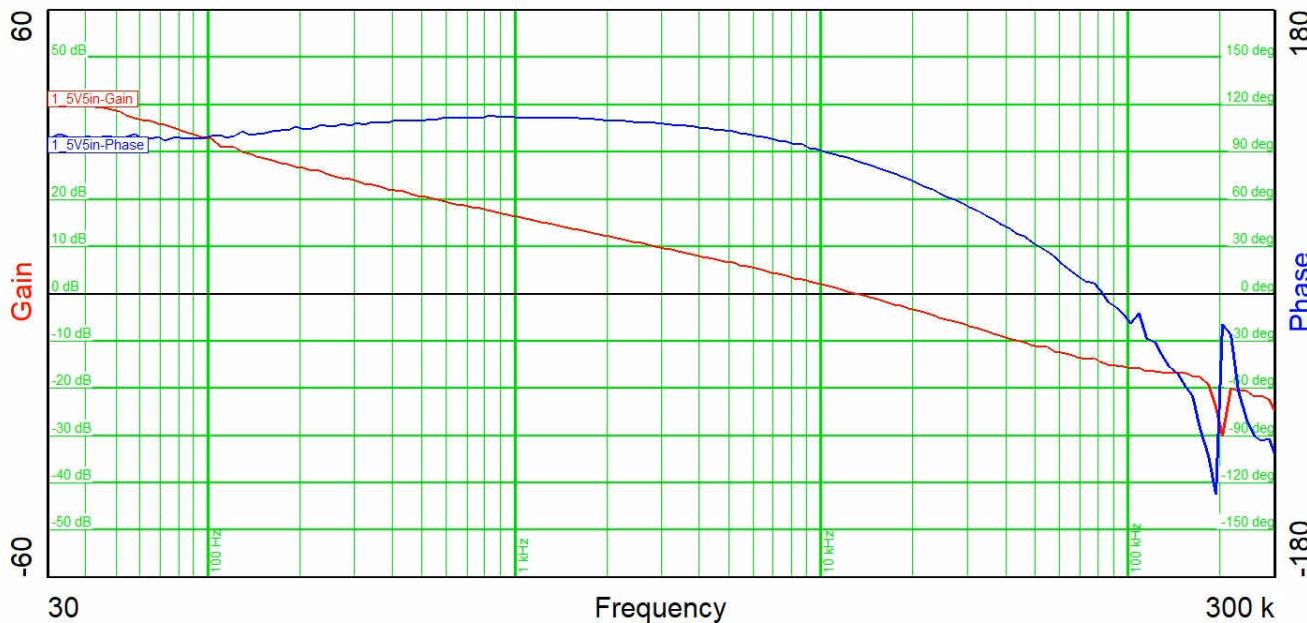


Figure 2-9. Bode Plot at 5.5-V Input Voltage

2.6.2 12-V Input Voltage

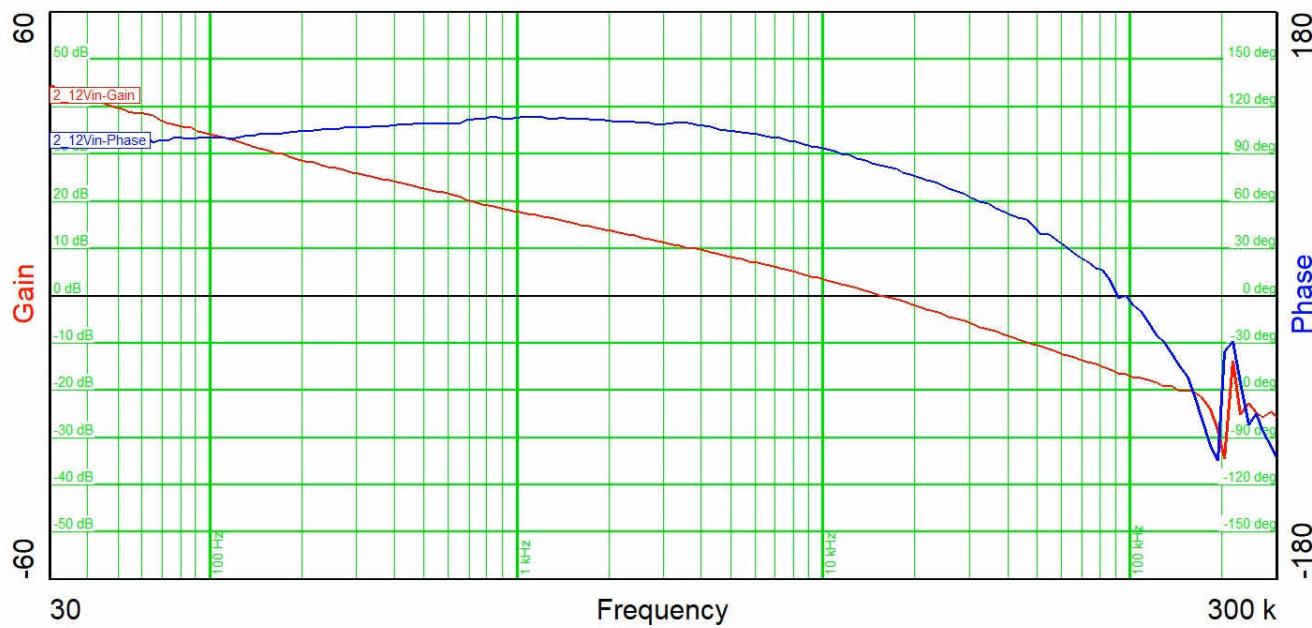


Figure 2-10. Bode Plot at 12-V Input Voltage

3 Waveforms

3.1 Switching

3.1.1 Q1 Drain to GND

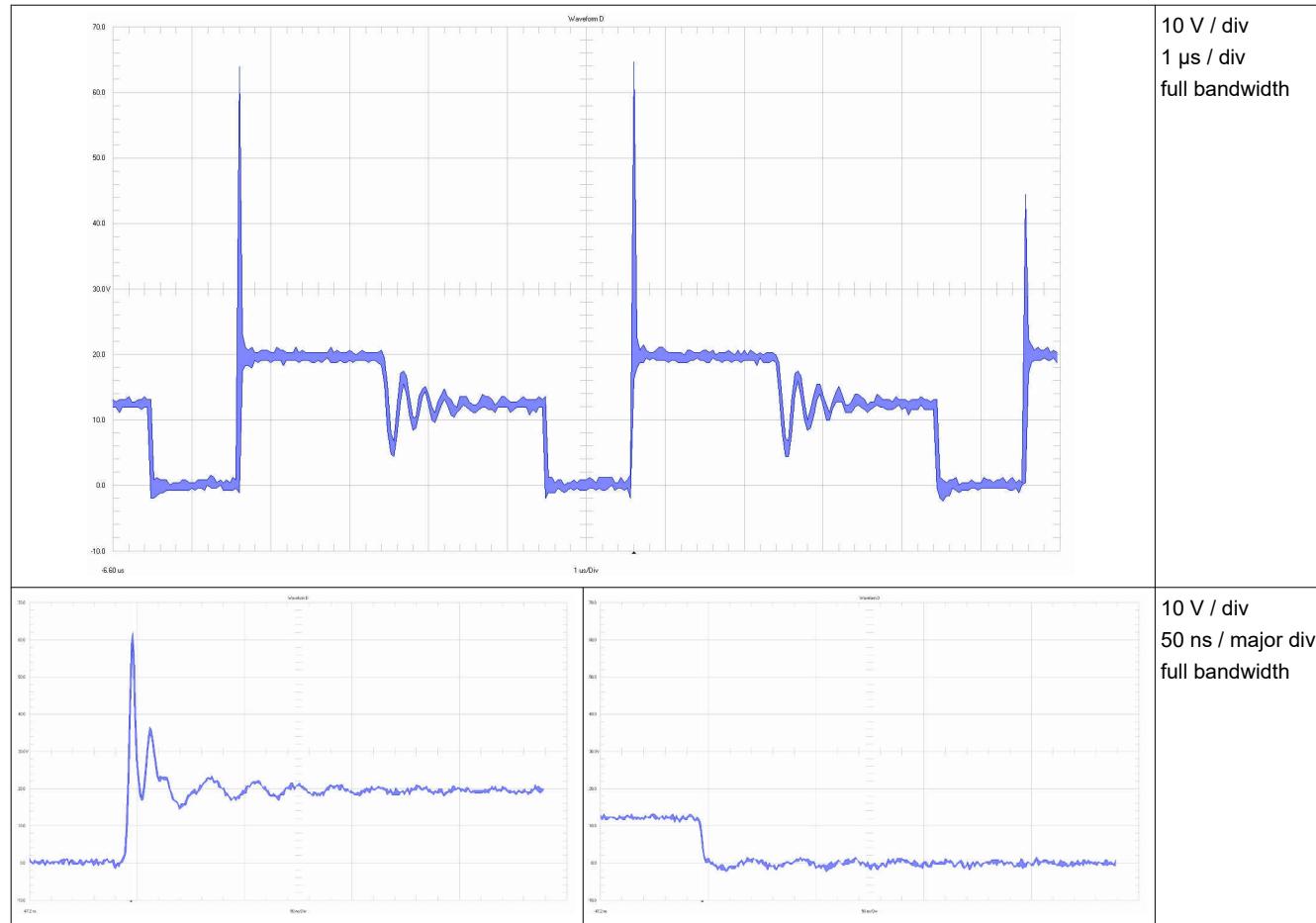


Figure 3-1. Switchnode to GND

3.1.2 Q1 Gate to GND

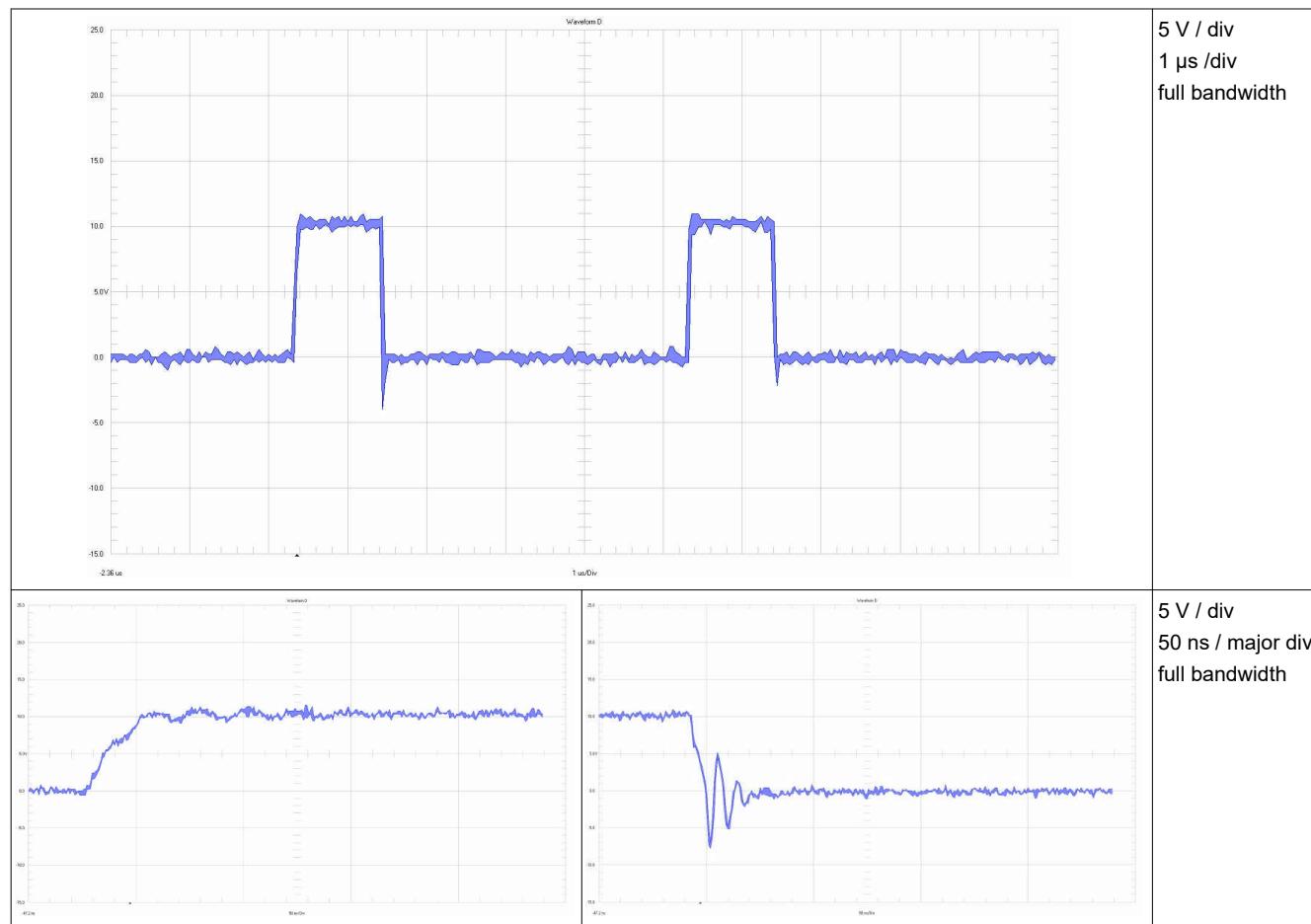


Figure 3-2. Waveform Gate Q1 to GND

3.1.3 Diode D12

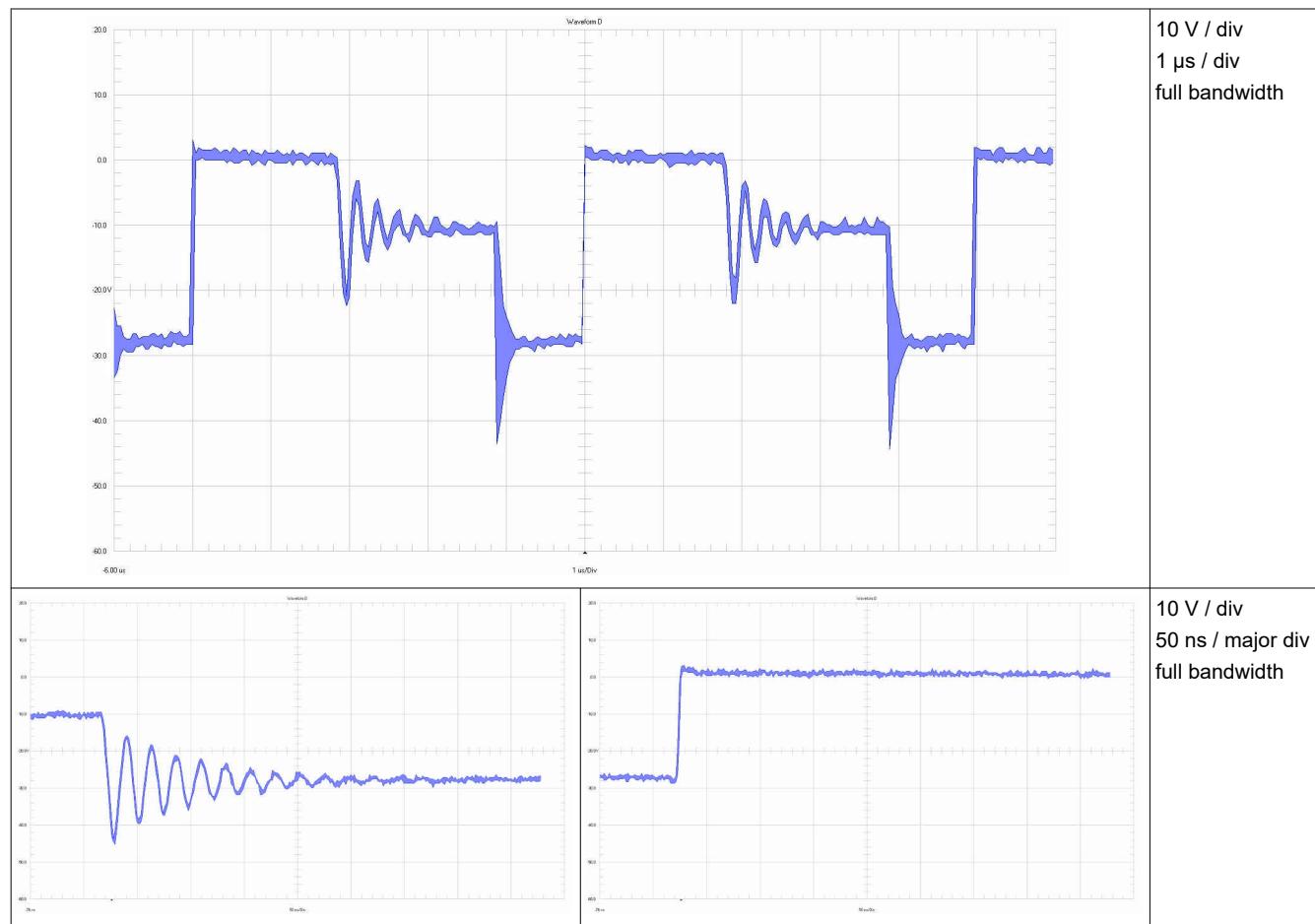


Figure 3-3. Diode D12 to +10 V_{pri}

3.1.4 Diode D9

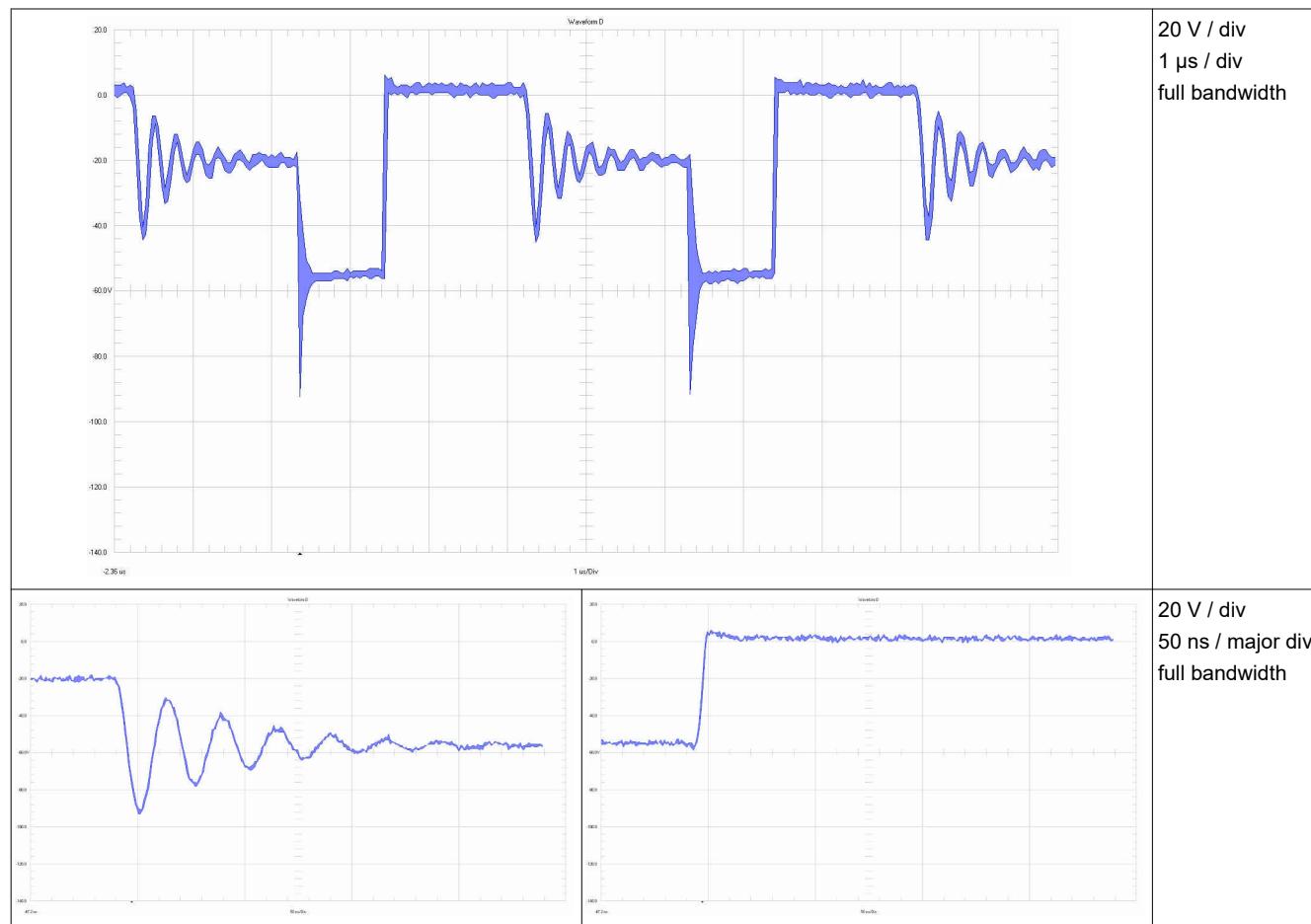


Figure 3-4. Diode D9 to +15V_3

3.2 Output Voltage Ripple

Output voltage ripple is shown in the following figures.

3.2.1 Primary 10 V (Auxiliary)

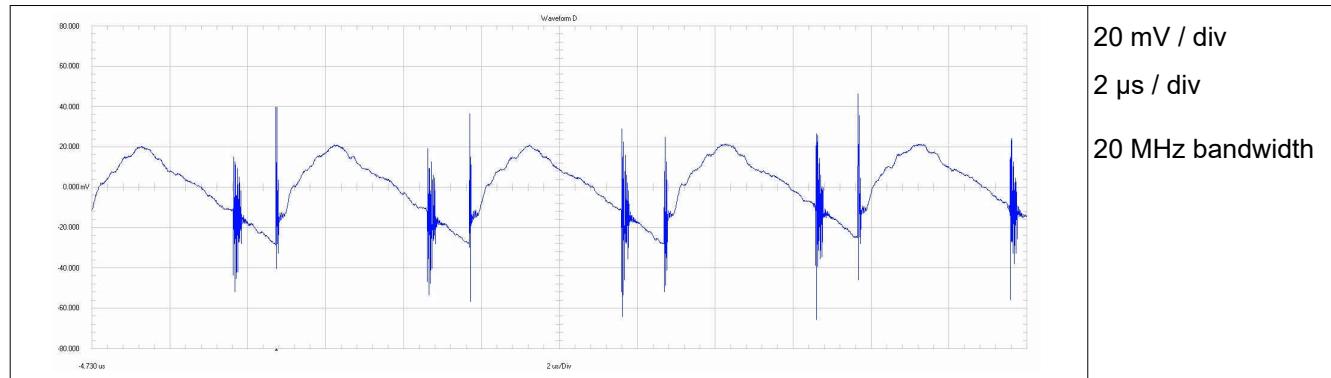


Figure 3-5. +10 V_{aux} Output

3.2.2 Secondary +15 V

The following three waveforms show the output voltage ripple of the three secondary +15-V outputs.

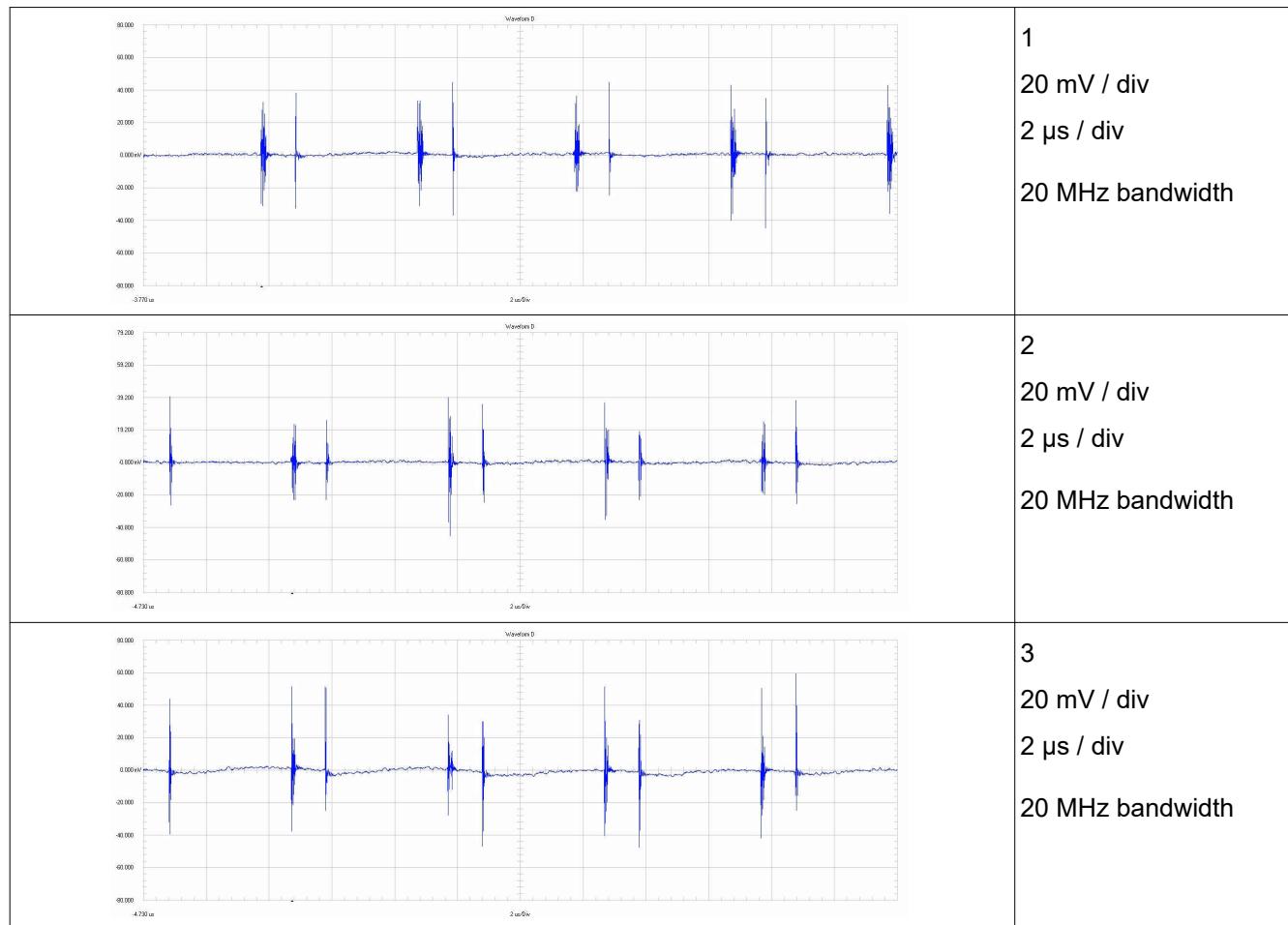


Figure 3-6. +15-V Output

3.2.3 Secondary –5 V

The following three waveforms show the output voltage ripple of the three secondary –5 V outputs.

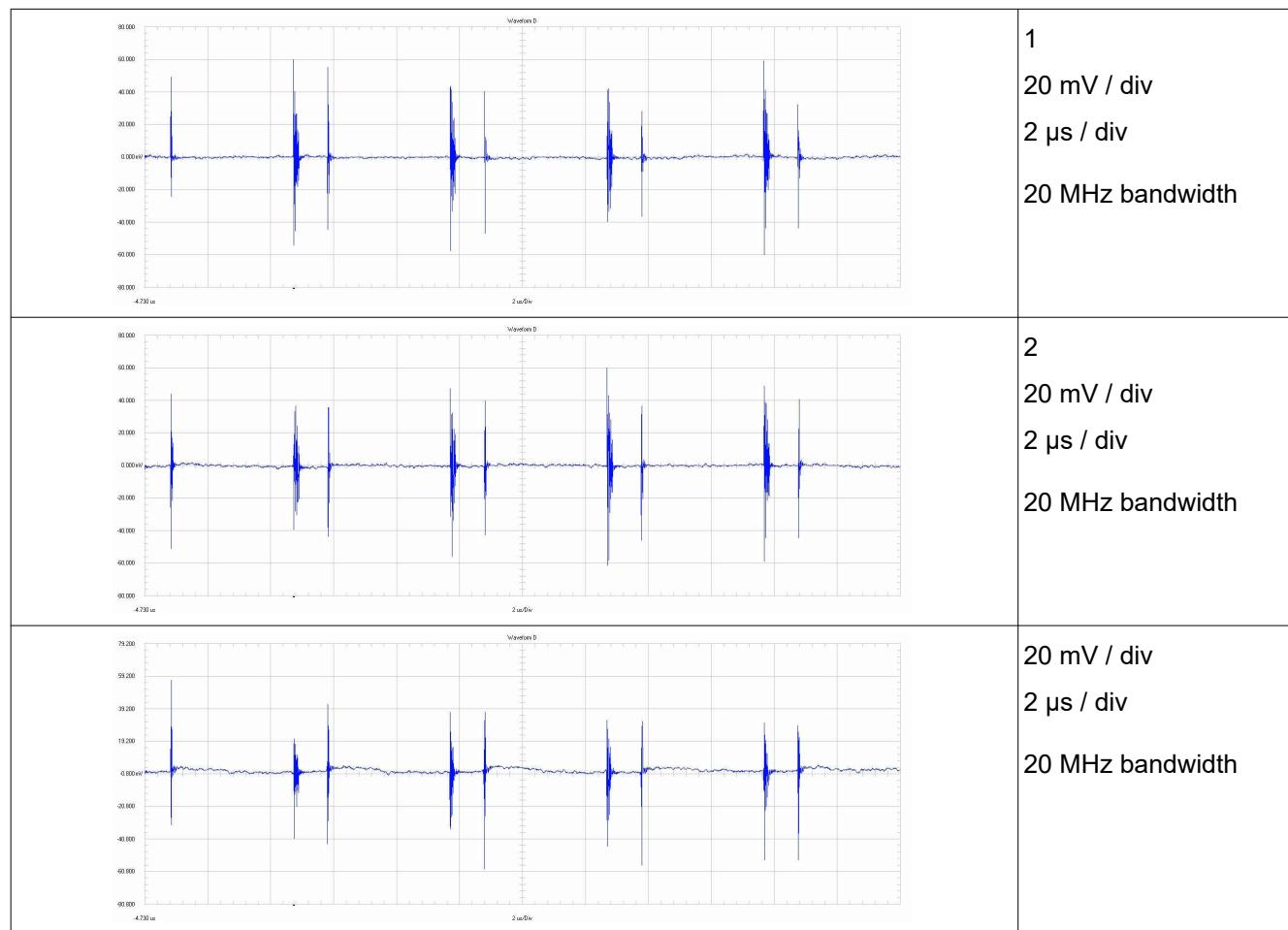


Figure 3-7. –5-V Output

3.3 Input Voltage Ripple

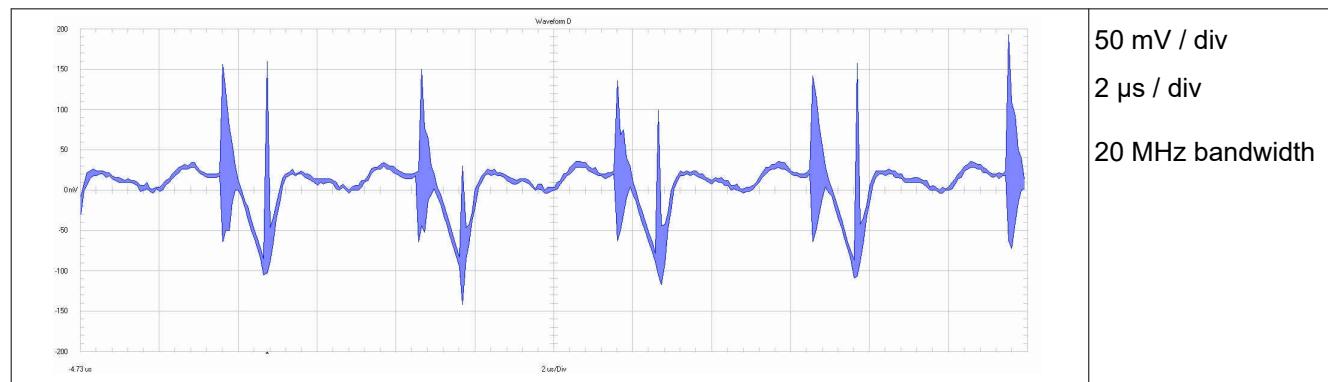


Figure 3-8. Input Voltage Ripple

3.4 Start-Up Sequence

Start-up behavior is shown in the following figure. An oscilloscope with isolated channels was used.

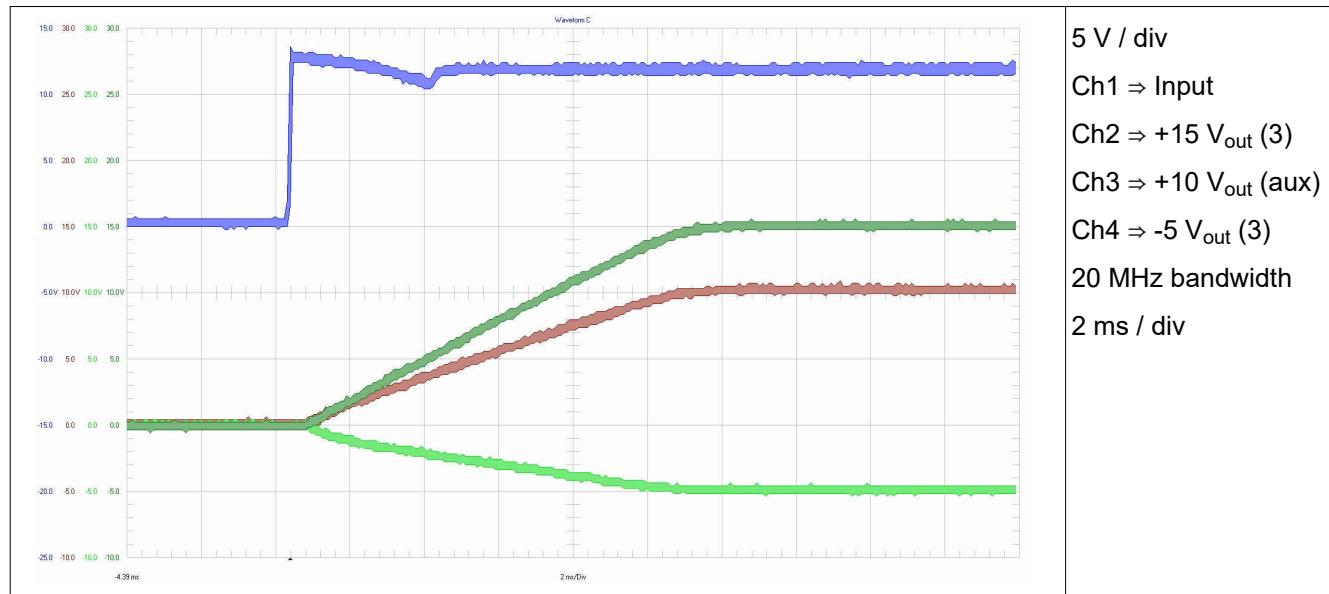


Figure 3-9. Start-up

3.5 Shutdown Sequence

Shutdown behavior is shown in the following figure. An oscilloscope with isolated channels was used.

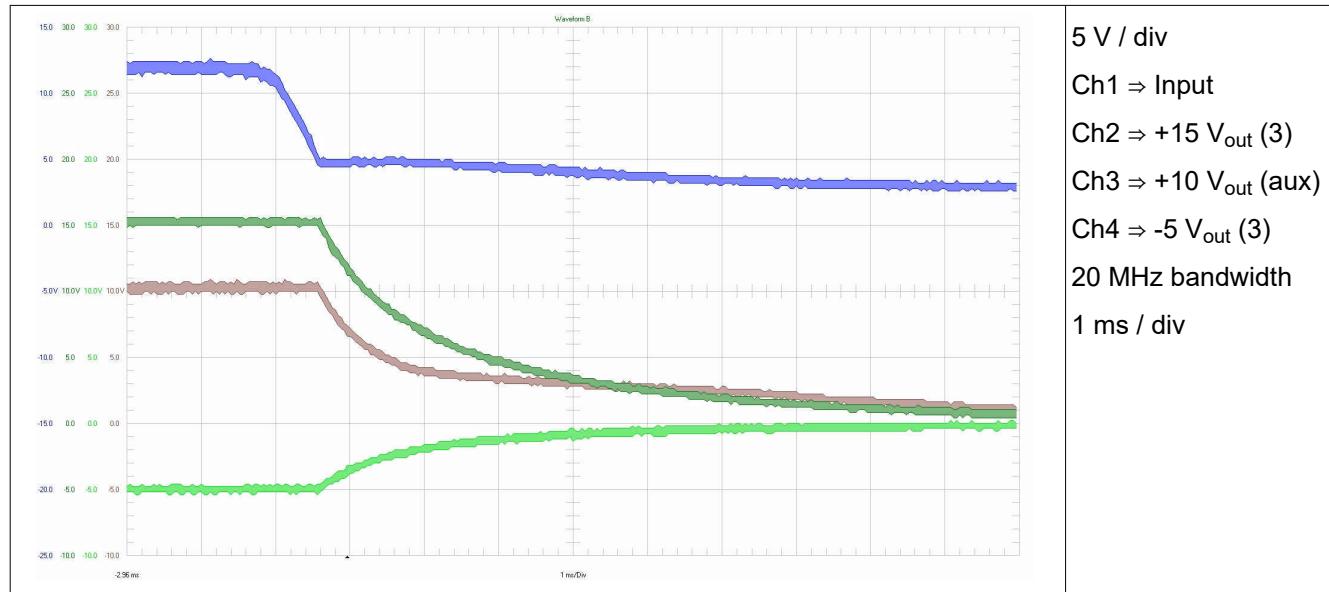


Figure 3-10. Shutdown

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated