

# **Wide $V_{IN}$ PSR Flyback Converter Dual-Output Reference Design**



## **Description**

The primary side regulated flyback provides dual outputs (B: 12 V at 170 mA, A: 18 V at 60 mA). The design has a small form factor with low component count. This design operates over an input voltage range of 8 V to 28 V to deliver two isolated outputs. Operating without an auxiliary winding or optocoupler, the LM5180 provides very tight output voltage regulation. The LM5180 offers several features that provide protection of the regulator during fault conditions.



**Top Photo**

## **Features**

- Primary-side regulation eliminates optocoupler
- Integrated FET minimizes external components
- 8-V to 28-V input voltage range
- 12-V and 18-V output voltages

## **Applications**

- [Process analytics](#)



**Bottom Photo**



**Angled Photo**

## 1 Test Prerequisites

### 1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Parameter	Specifications
Input Voltage Range (DC)	8 V to 36 V
Output Voltage A	18 V
Maximum Output Current A	0.06 A
Output Voltage B	12 V
Maximum Output Current B	0.17 A
IC	LM5180
Topology	Isolated Flyback

### 1.2 Considerations

Unless otherwise mentioned, resistors were used as load and the input voltage was set to 24 V.

### 1.3 Dimensions


The size of the two-layer board is 58.4 mm × 41.9 mm. The copper thickness is 35 µm on each layer.

## 2 Testing and Results

### 2.1 Efficiency and Loss Graph


The measurements in [Figure 2-1](#) and [Figure 2-2](#) were performed with  $R9 = 3.01\text{ k}\Omega$  and  $R10 = 6.49\text{ k}\Omega$  pre-load resistors.

#### 2.1.1 Efficiency

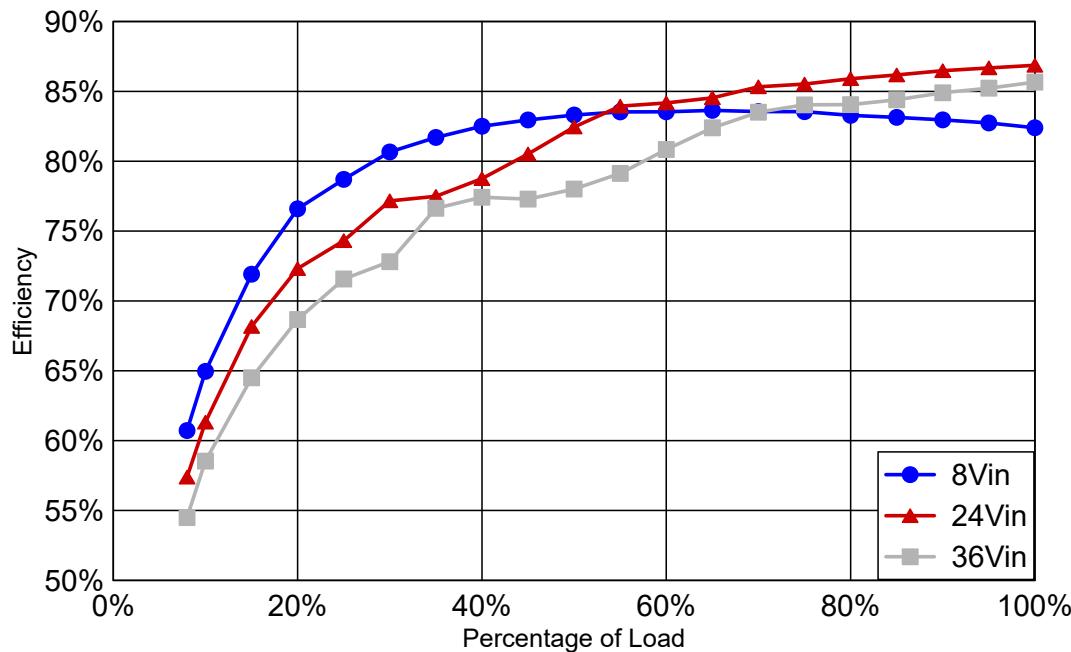

**Figure 2-1. Efficiency vs Percentage of Load**

#### 2.1.2 Loss

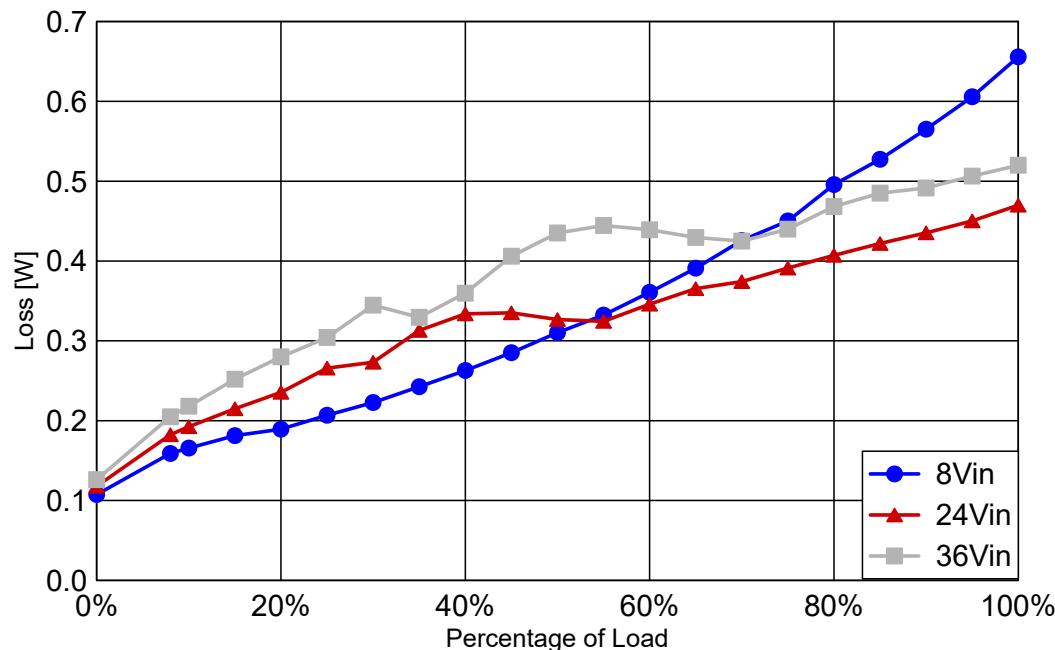


**Figure 2-2. Loss vs Percentage of Load**

## 2.2 Load Regulation


During the measurement for efficiency and loss, the values for load regulation were also obtained.

### 2.2.1 18-V Output Voltage (V<sub>OUT</sub>-A)

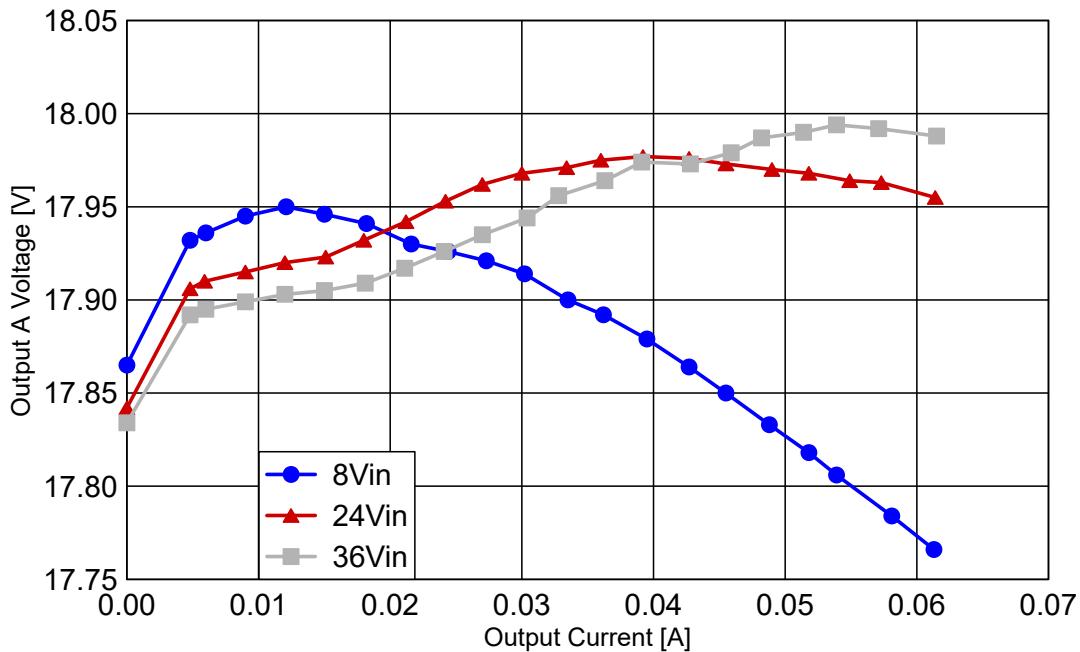

**Figure 2-3. Load Regulation for 18-V Output Voltage**

### 2.2.2 12-V Output Voltage (V<sub>OUT</sub>-B)

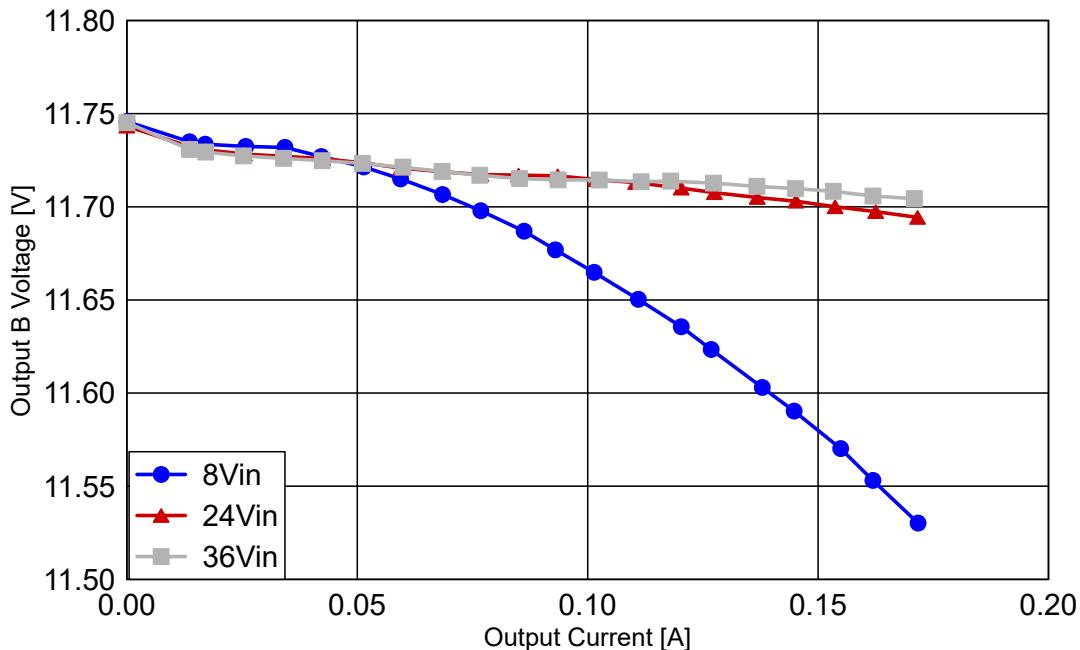


**Figure 2-4. Load Regulation for 12-V Output Voltage**

## 2.3 Line Regulation


The measurements for line regulation were done with the revision B circuit.

### 2.3.1 18-V Output Voltage (V<sub>OUT</sub>-A)

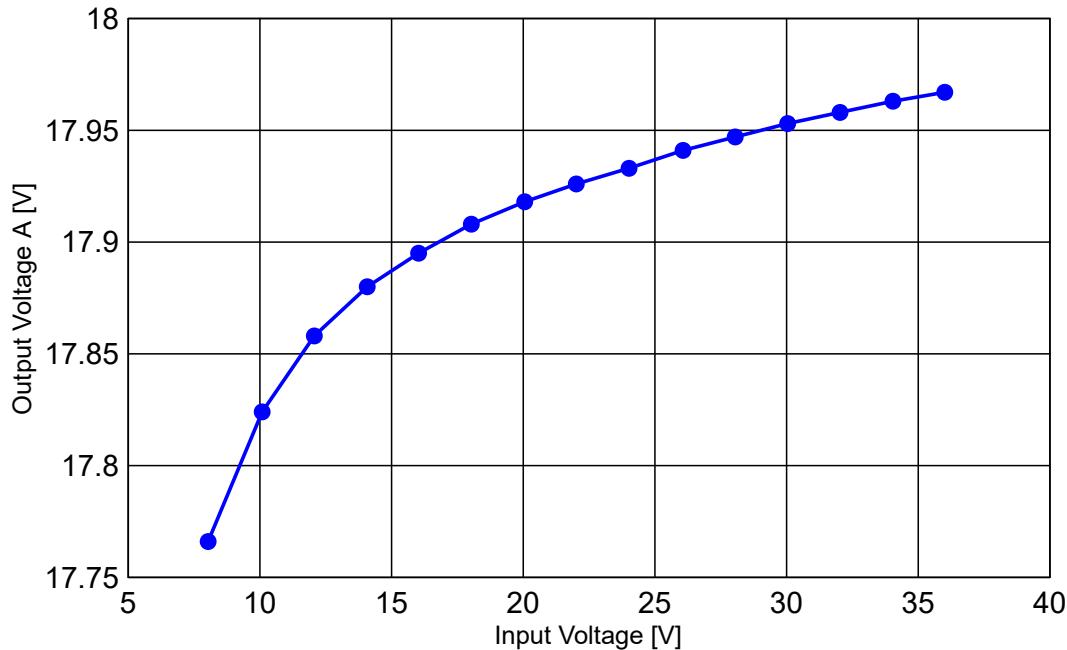

**Figure 2-5. Line Regulation for 18-V Output Voltage**


### 2.3.2 12-V Output Voltage (V<sub>OUT</sub>-B)

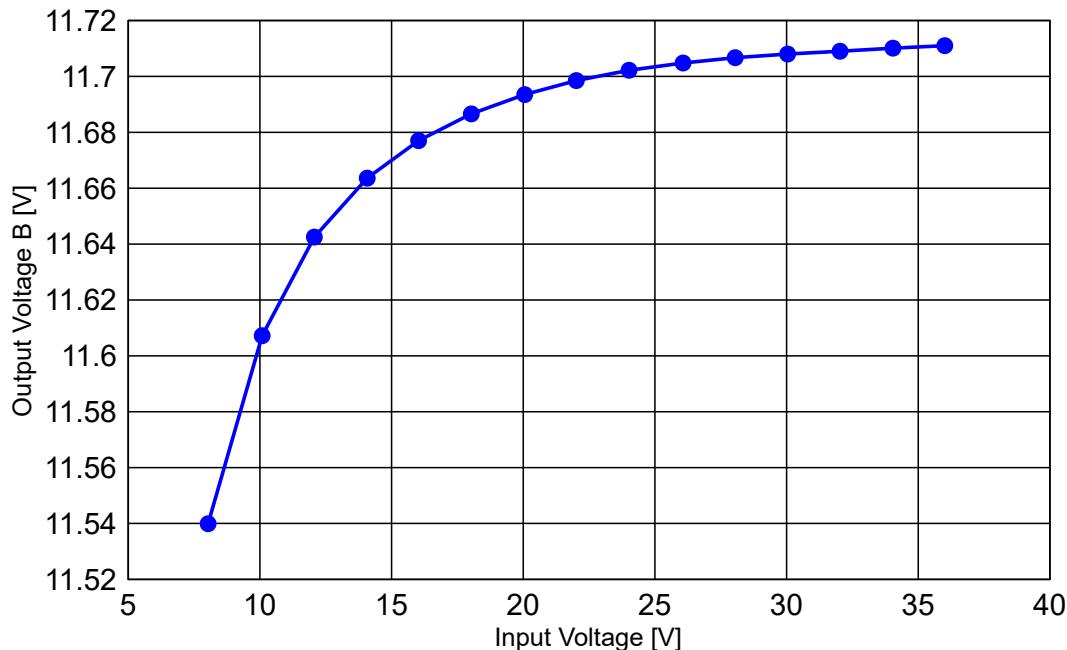

**Figure 2-6. Line Regulation for 12-V Output Voltage**

### 2.3.3 Efficiency and Loss vs Line Variation

The efficiencies were measured with  $R9 = 1.5\text{-k}\Omega$  and  $R10 = 1\text{-k}\Omega$  pre-load resistors.

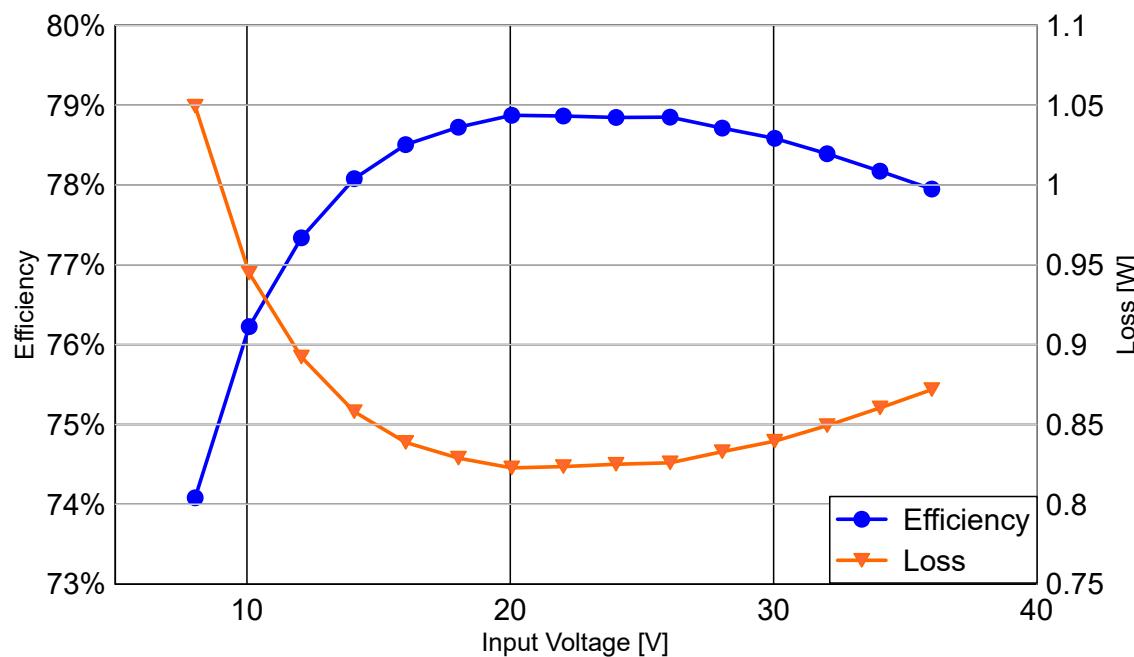

**Figure 2-7. Efficiency and Loss vs Input Voltage**

## 2.4 Cross Regulation

For the measurements in this section, the input voltage was set to 24 V.

### 2.4.1 12-V Output With No Load

#### 2.4.1.1 Effects on the 18-V Output

Figure 2-8 displays:

- (blue curve) 18-V output voltage; during the output current of the 18-V output was varied.
- (red curve) the according voltage values with symmetrically loaded outputs. (See also Figure 2-3).

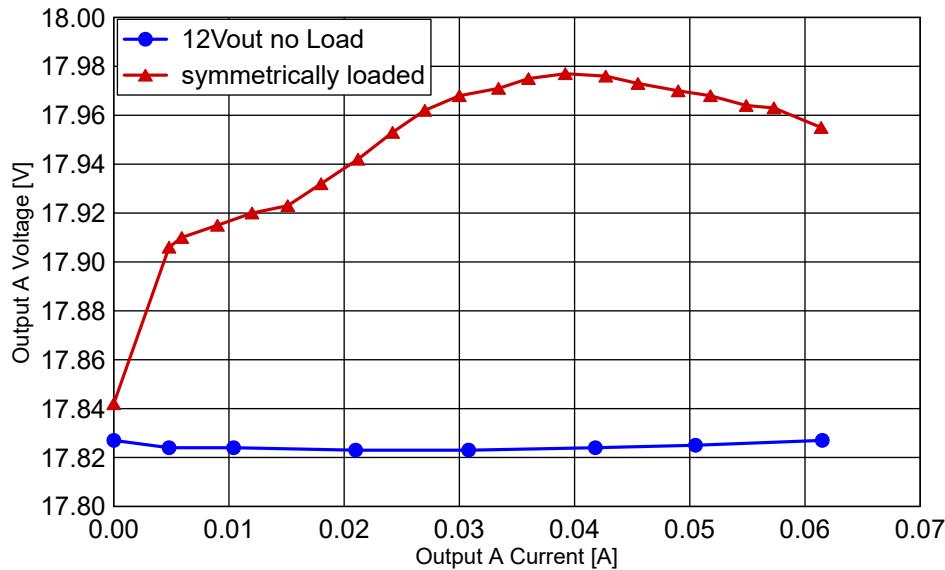


Figure 2-8. 18-V Output Voltage (VOUT-A) vs Output Current A

#### 2.4.1.2 Effects on the 12-V Output

Figure 2-9 displays:

- (blue curve) 12-V output voltage during the output current of the 18-V output was varied.
- (red curve) the according voltage values with symmetrically loaded outputs. (See also Figure 2-4)

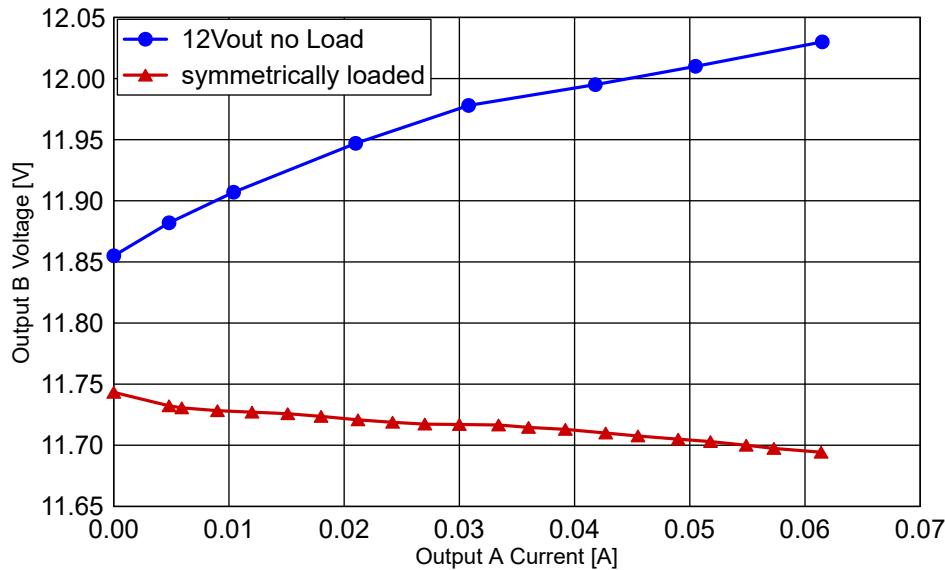


Figure 2-9. 12-V Output Voltage (VOUT-B) vs Output Current A

## 2.4.2 18-V Output With no Load

### 2.4.2.1 Effects on the 12-V Output Voltage

Figure 2-10 displays:

- (blue curve) 12-V output voltage during the output current of the 12-V output was varied.
- (red curve) the according voltage values with symmetrically loaded outputs. (See also Figure 2-4)

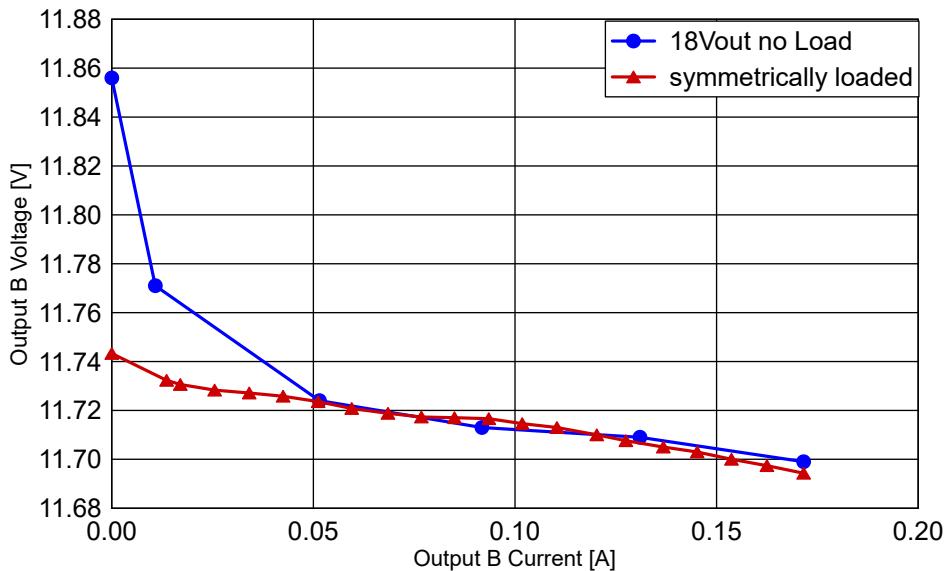


Figure 2-10. 18-V Output Voltage ( $V_{OUT\text{-}A}$ ) vs Output Current B

### 2.4.2.2 Effects on the 18-V Output Voltage

Figure 2-11 displays:

- (blue curve) 12-V output voltage during the output current of the 18-V output was varied.
- (red curve) the according voltage values with symmetrically loaded outputs. (See also Figure 2-3)


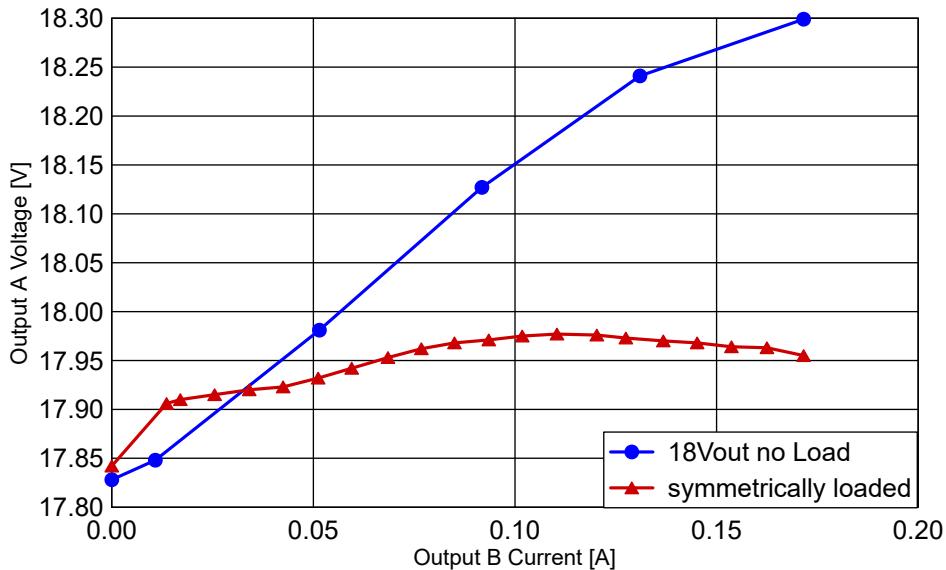


Figure 2-11. Output Voltage B vs Output Current B

## 2.5 Thermal Images

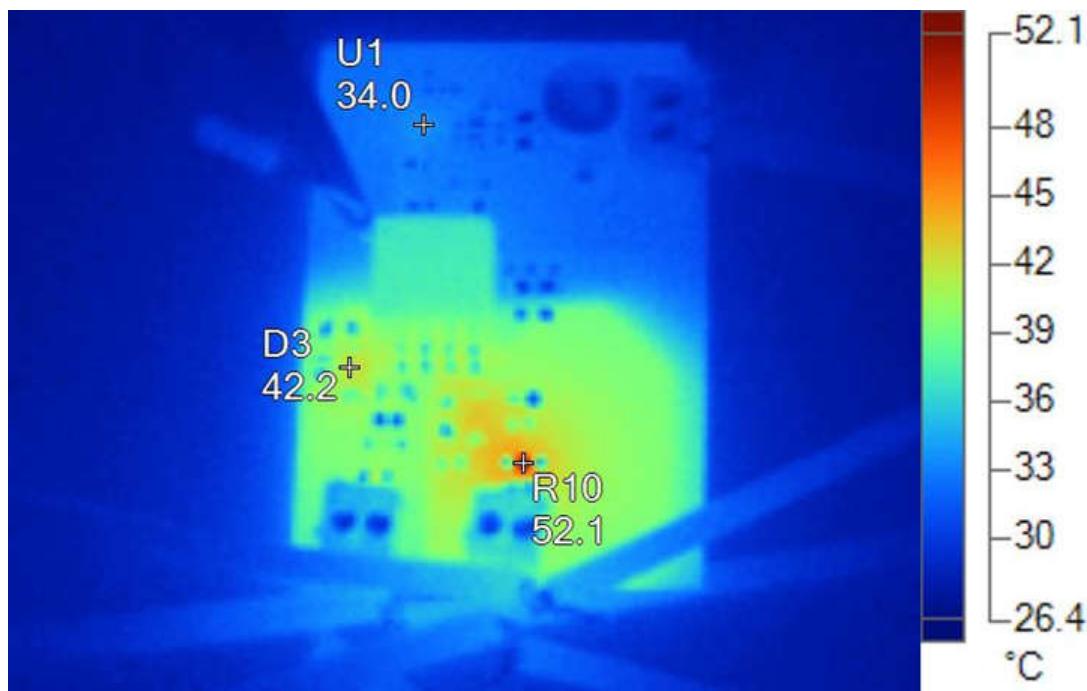

**Figure 2-12. Infrared Image Full Load 24-V Input Voltage**

Name	Temperature
R10	52.1°C
D3	42.2°C
U1	34.0°C


## 3 Waveforms

### 3.1 Switching

#### 3.1.1 Primary Switching Node


##### 3.1.1.1 8-V Input Voltage

###### 3.1.1.1.1 Full Load

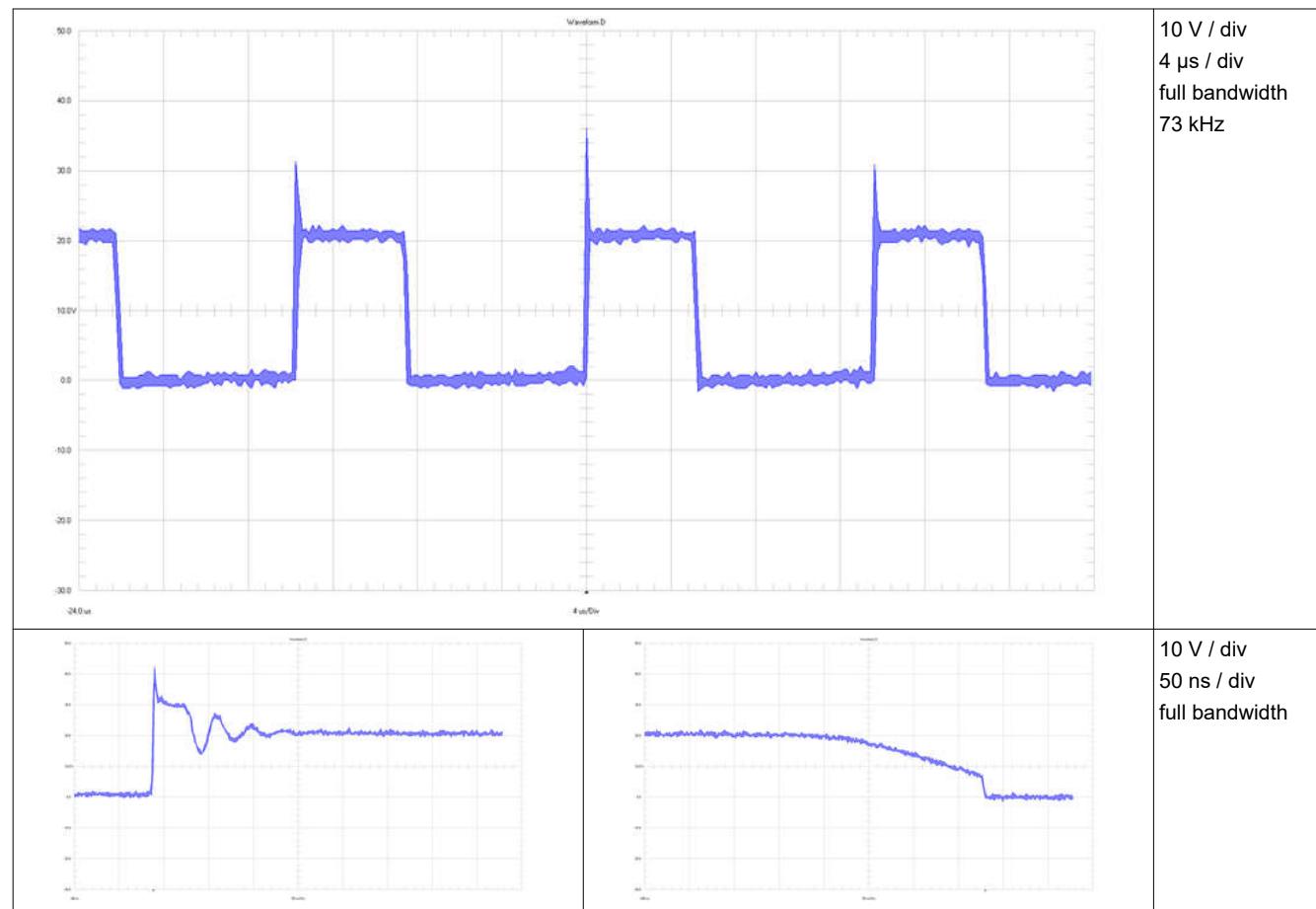

**Figure 3-1. Primary Switch Node, 8  $V_{IN}$ , Full Load**


### 3.1.1.1.2 No Load

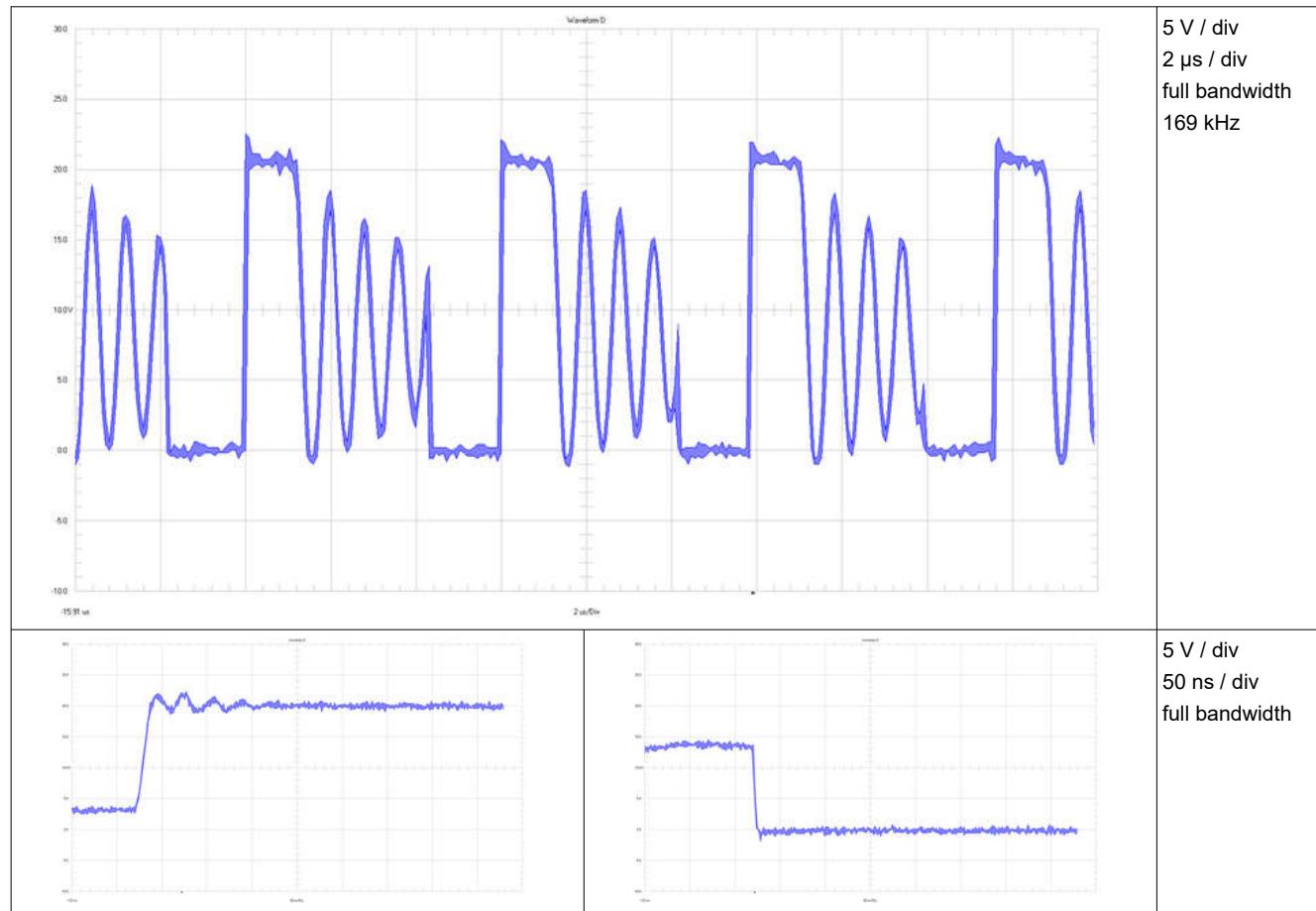

**Figure 3-2. Primary Switch Node, 8  $V_{IN}$ , No Load**


### 3.1.1.2 36-V Input Voltage

#### 3.1.1.2.1 Full Load

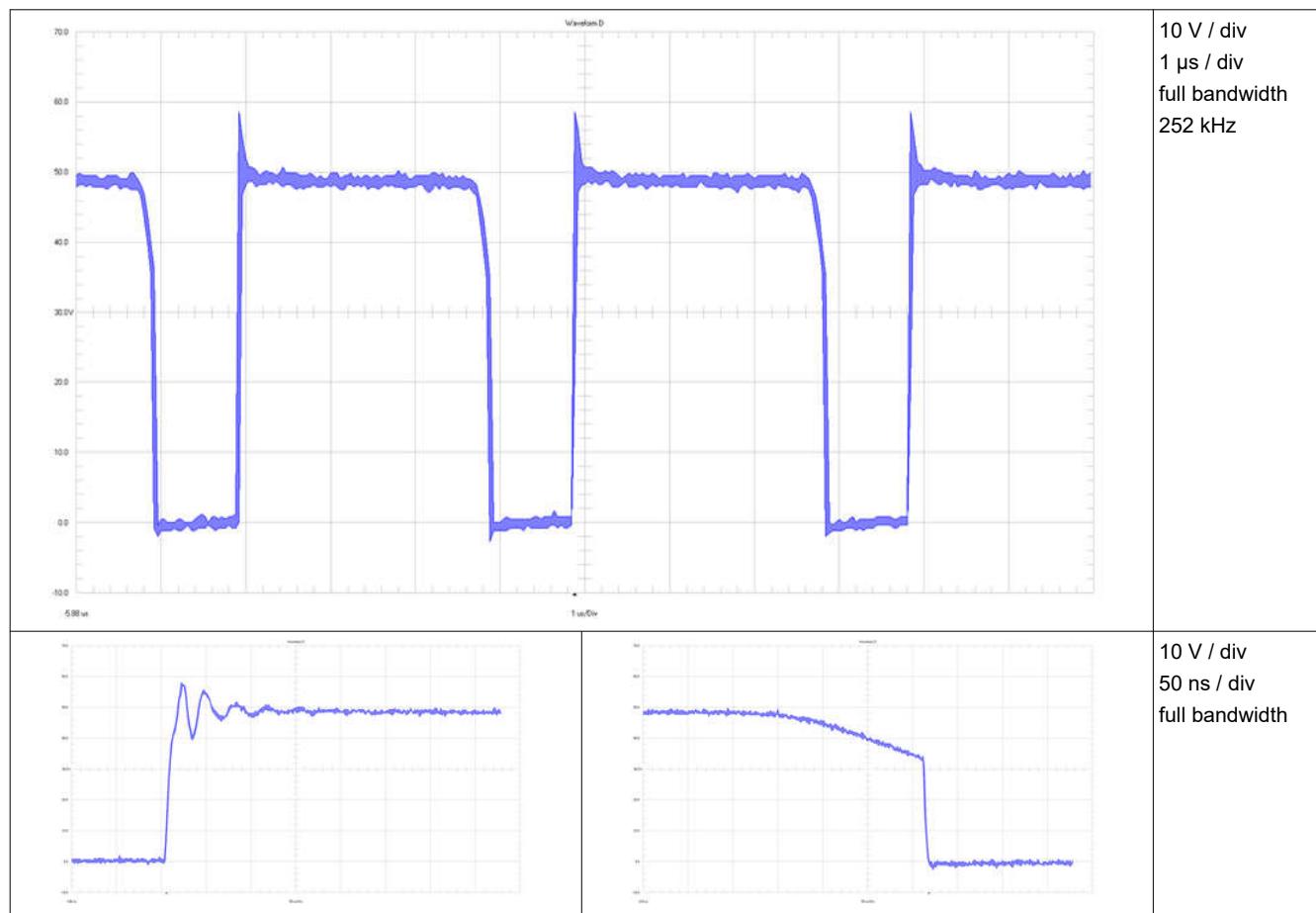

**Figure 3-3. Primary Switch Node, 36  $V_{IN}$ , Full Load**

### 3.1.1.2.2 No Load

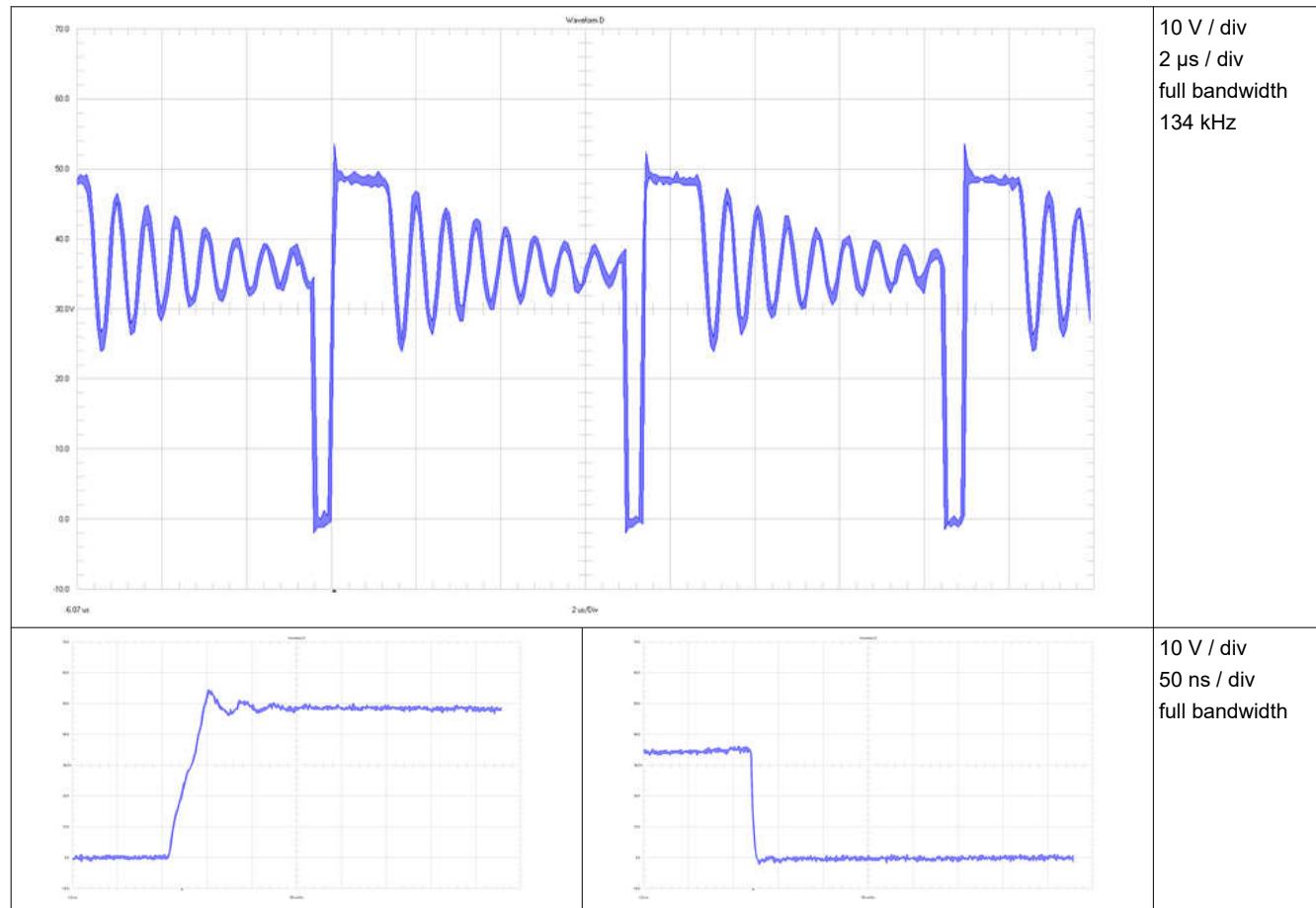


**Figure 3-4. Primary Switch Node, 36  $V_{IN}$ , No Load**

### 3.1.2 Diode D3 Referenced to VOUT-B (12 V)

#### 3.1.2.1 8-V Input Voltage

##### 3.1.2.1.1 Full Load

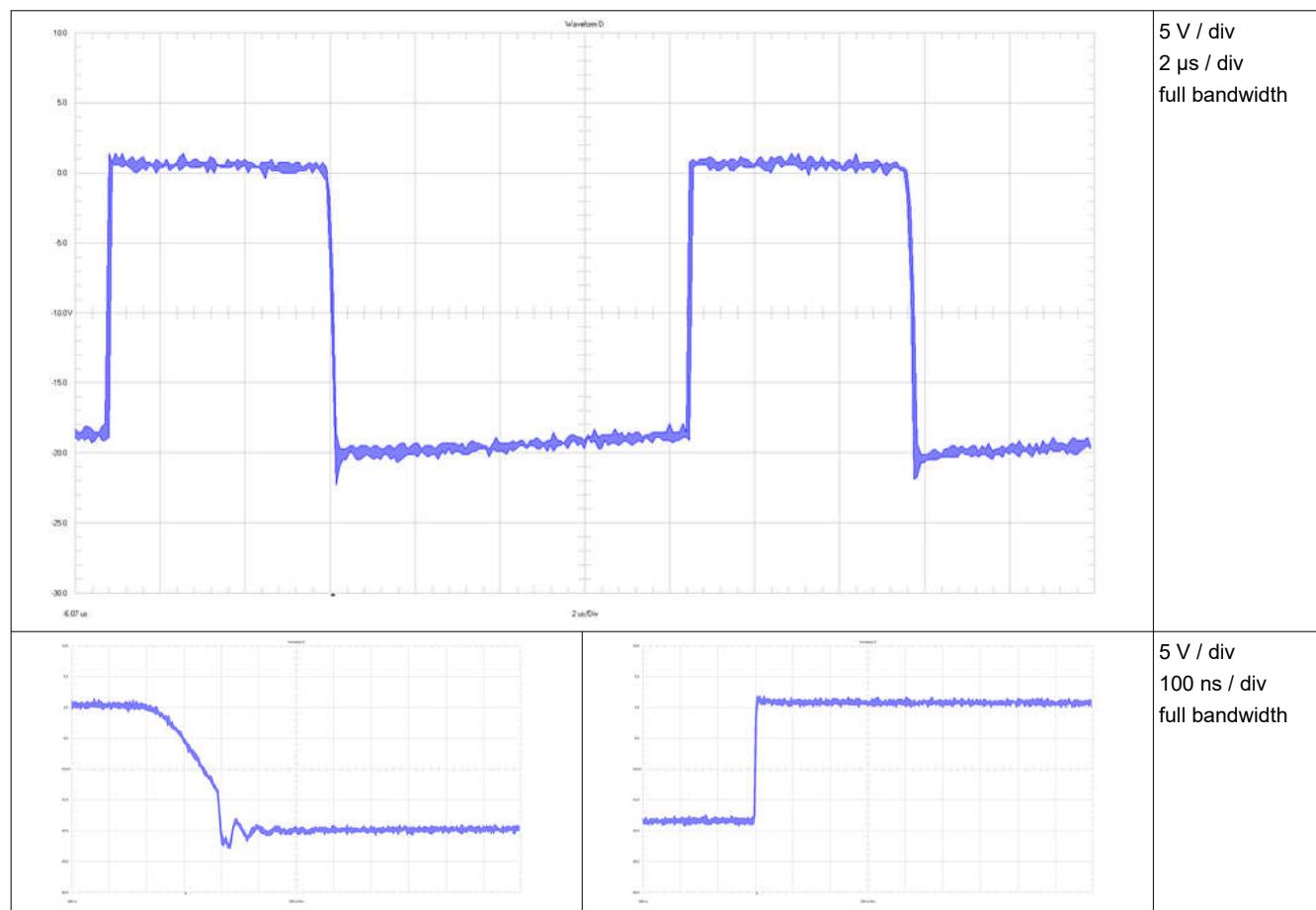

**Figure 3-5. Diode D3, 8  $V_{IN}$ , Full Load**

### 3.1.2.1.2 No Load


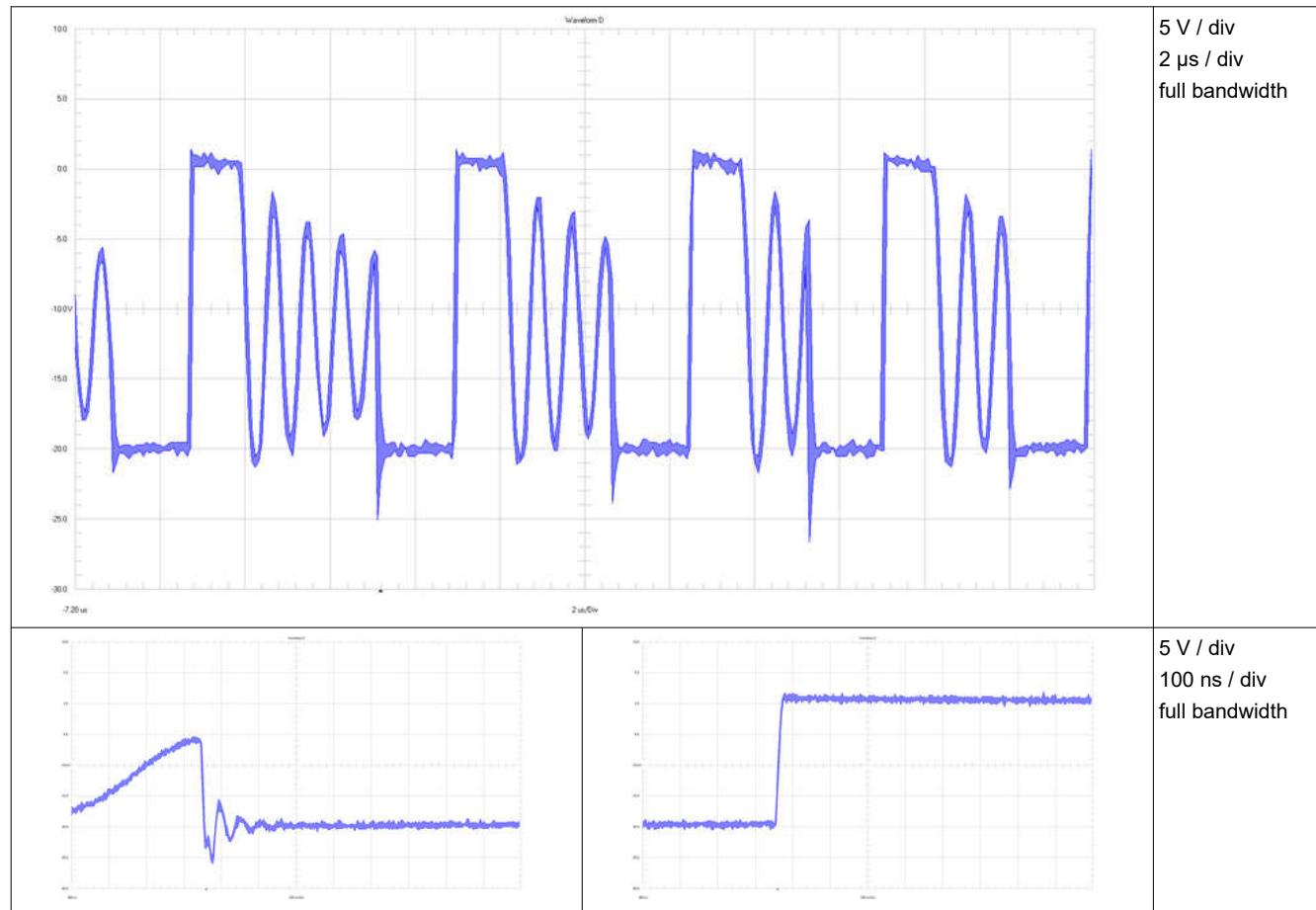


Figure 3-6. Diode D3, 8  $V_{IN}$ , No Load


### 3.1.2.2 36-V Input Voltage

#### 3.1.2.2.1 Full Load

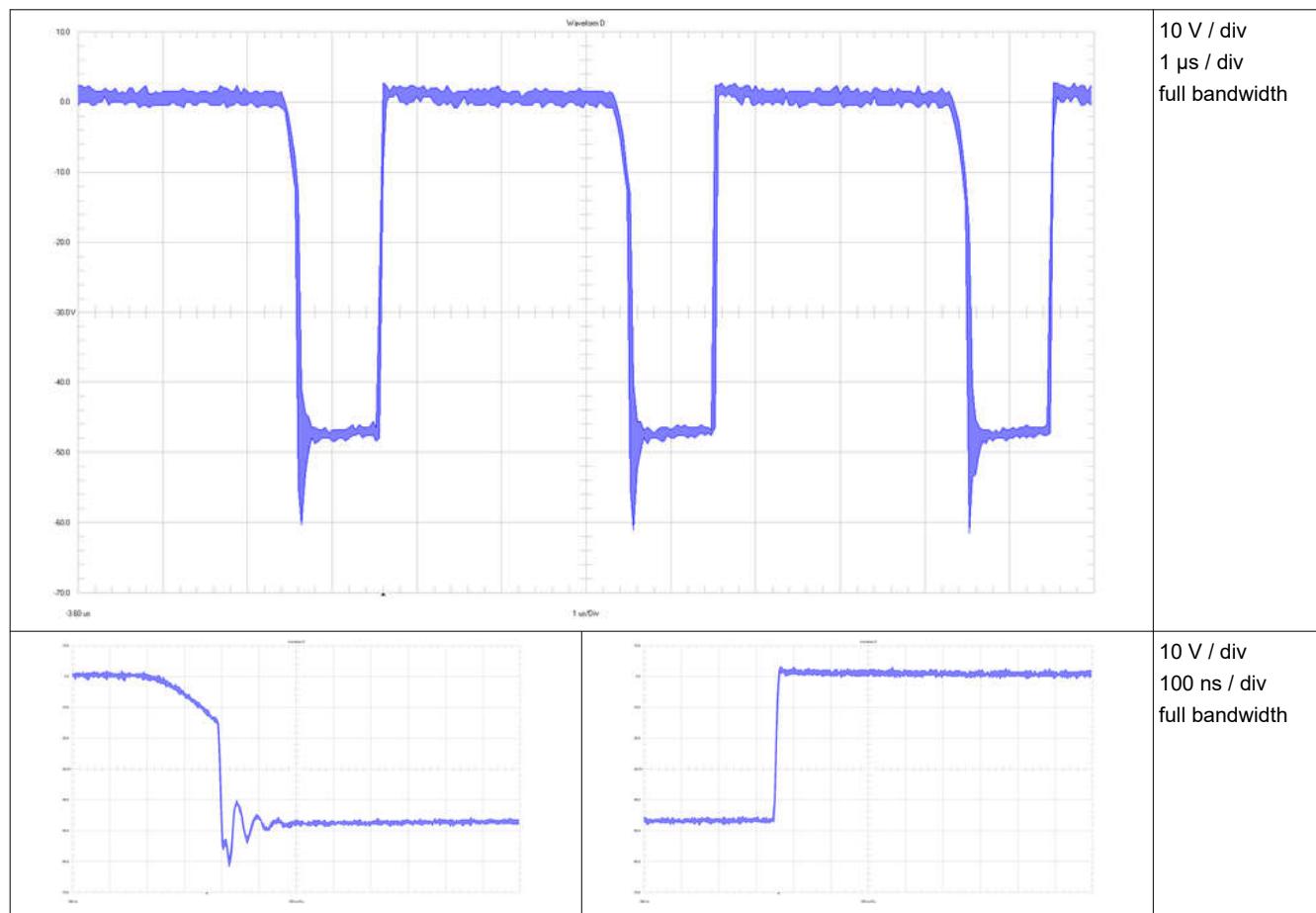

**Figure 3-7. Diode D3, 36  $V_{IN}$ , Full Load**

### 3.1.2.2.2 No Load

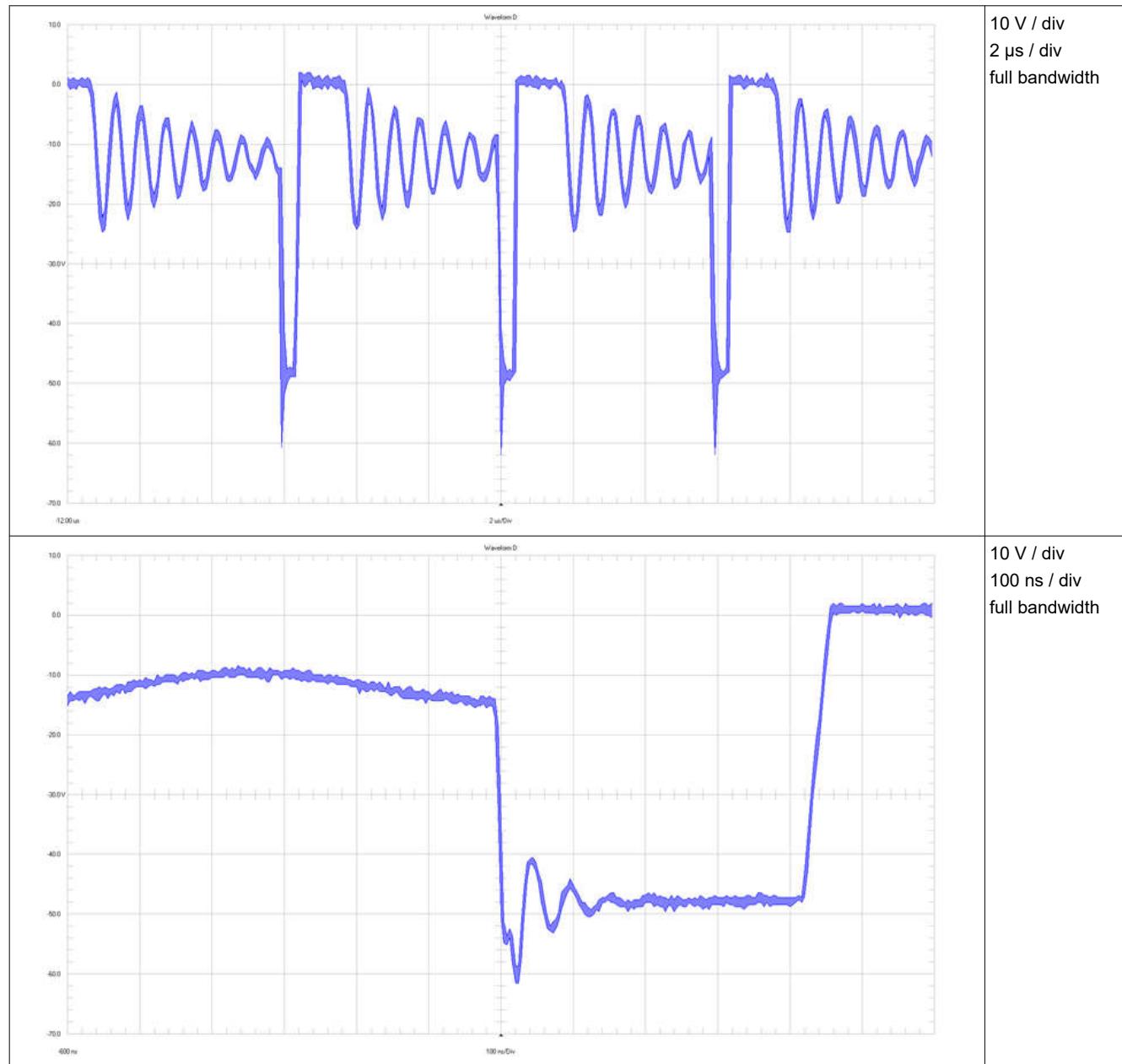


**Figure 3-8. Diode D3, 36  $V_{IN}$ , No Load**

### 3.1.3 Diode D4 Referenced to VOUT-A (18 V)

#### 3.1.3.1 8-V Input Voltage

##### 3.1.3.1.1 Full Load

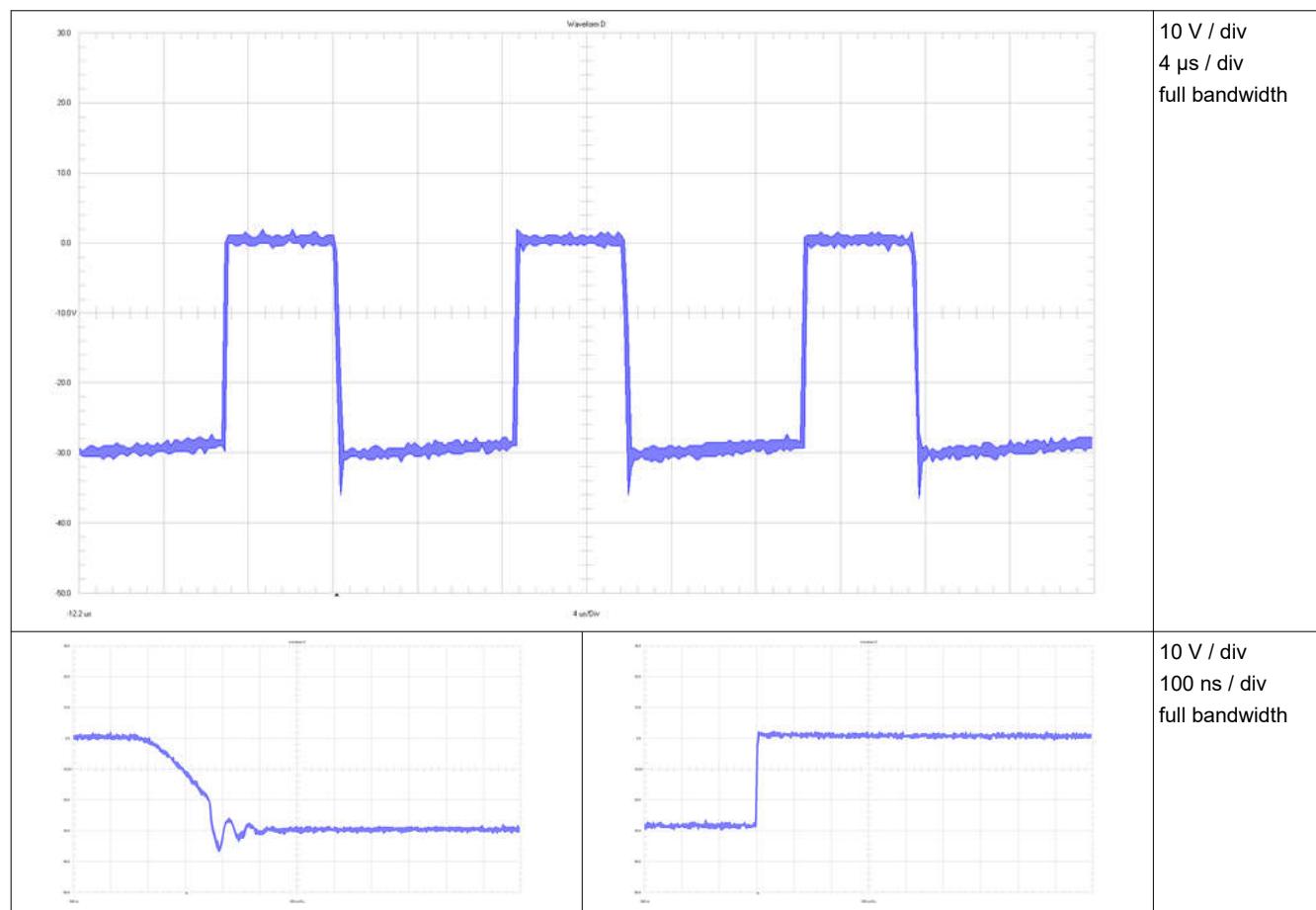

**Figure 3-9. Diode D4, 8  $V_{IN}$ , Full Load**

### 3.1.3.1.2 No Load


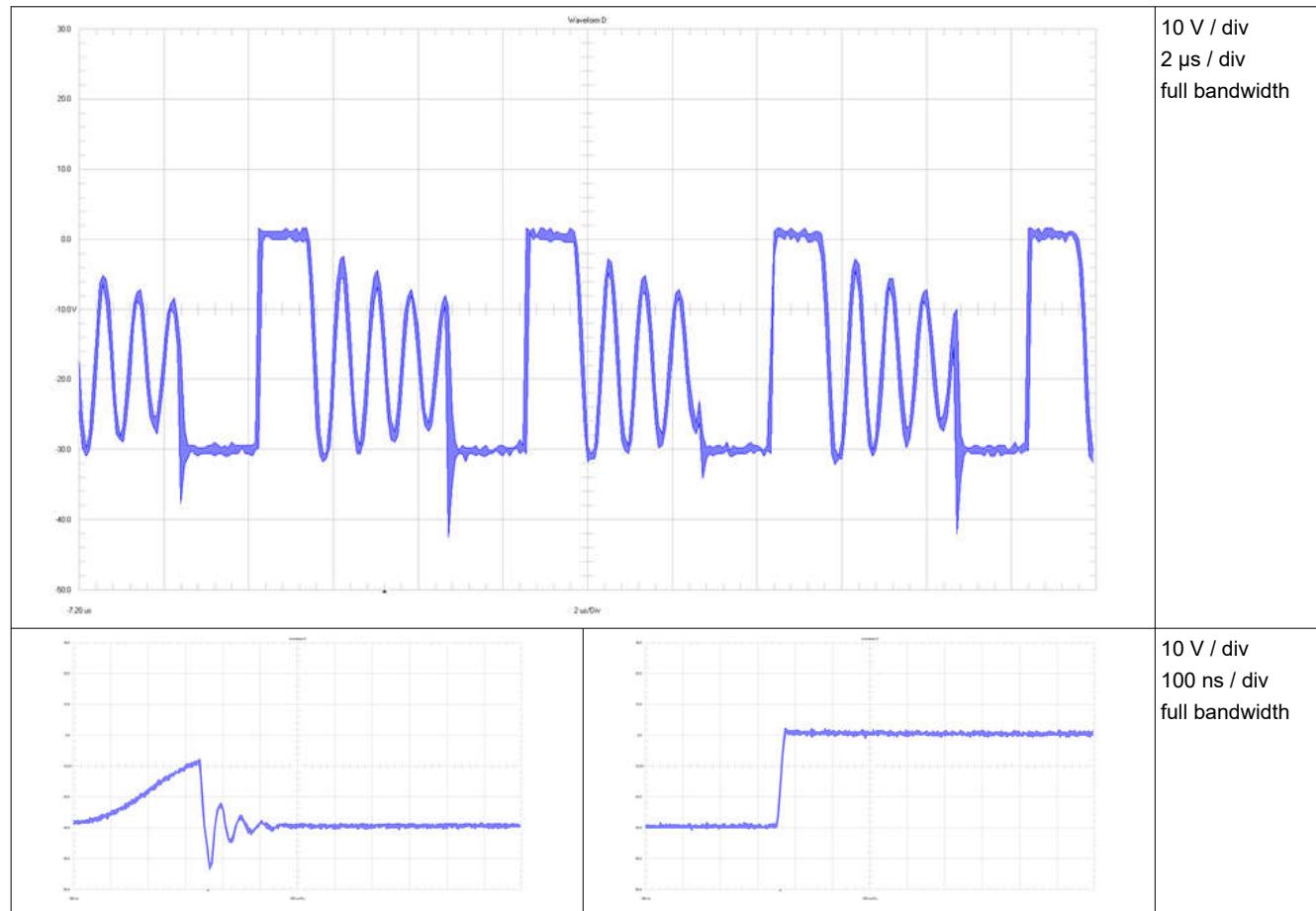


Figure 3-10. Diode D4, 8  $V_{IN}$ , No Load


### 3.1.3.2 36-V Input Voltage

#### 3.1.3.2.1 Full Load

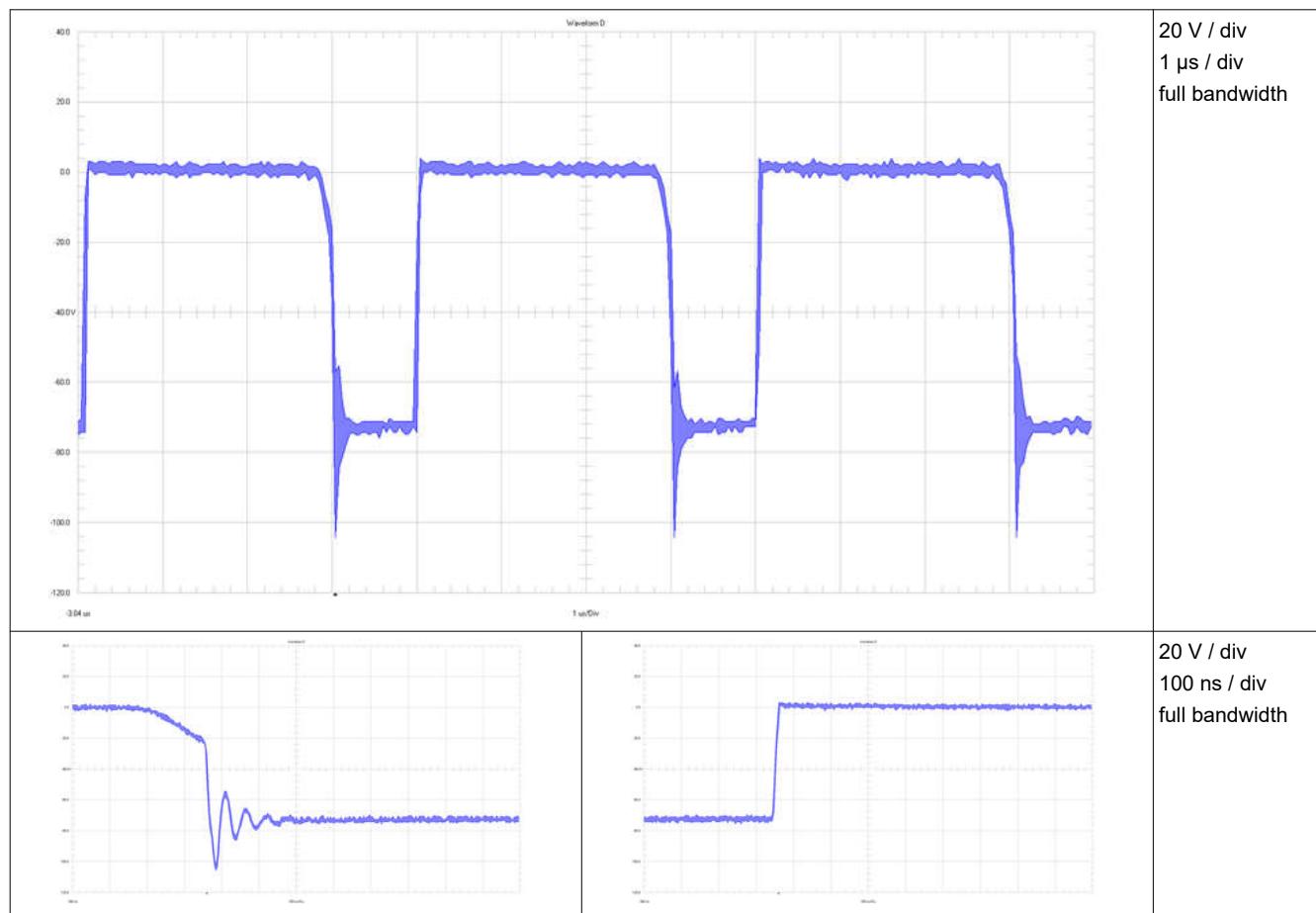


**Figure 3-11. Diode D4, 36  $V_{IN}$ , Full Load**

### 3.1.3.2.2 No Load

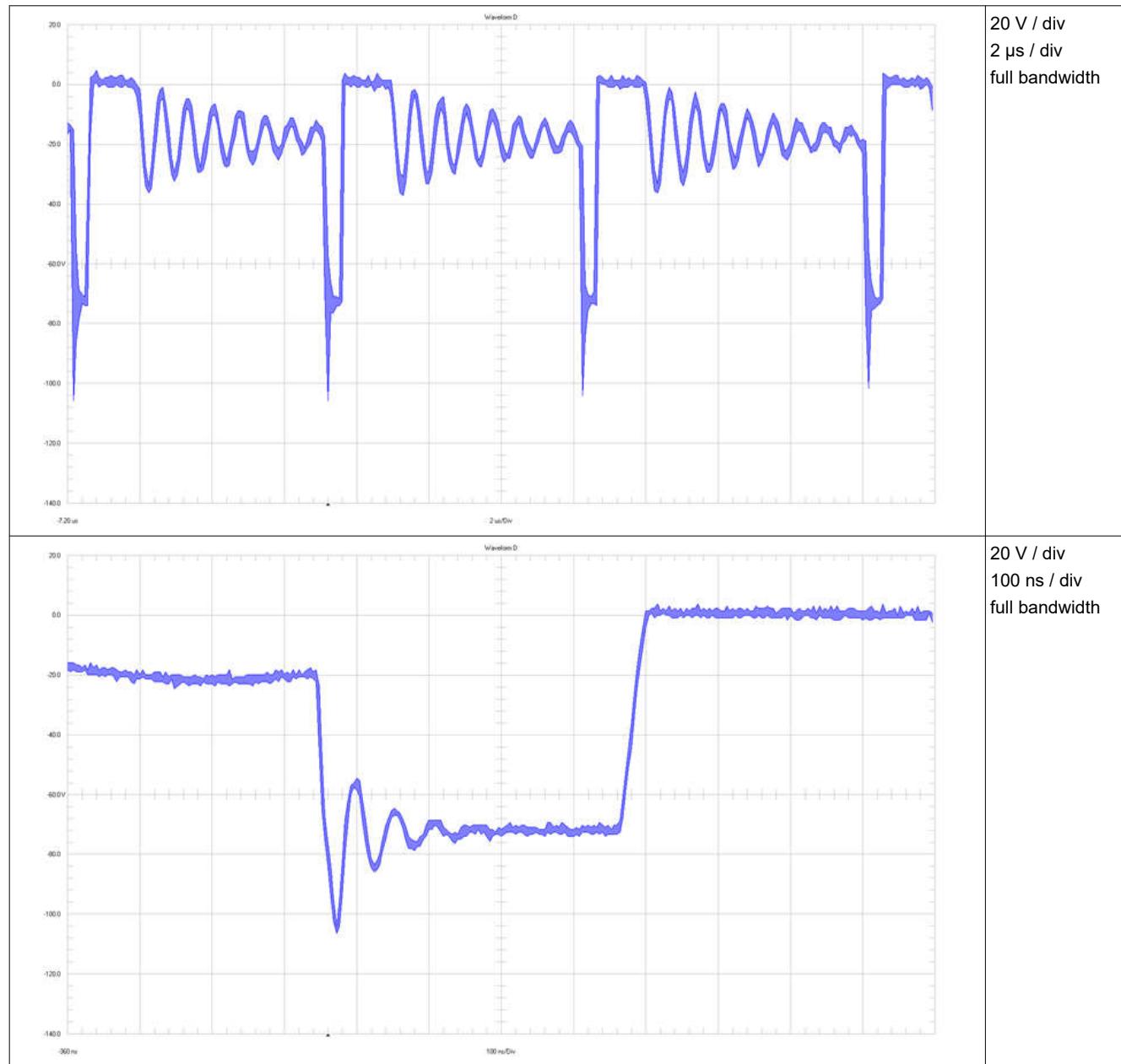

**Figure 3-12. Diode D4, 36  $V_{IN}$ , No Load**

### 3.2 Input Voltage Ripple

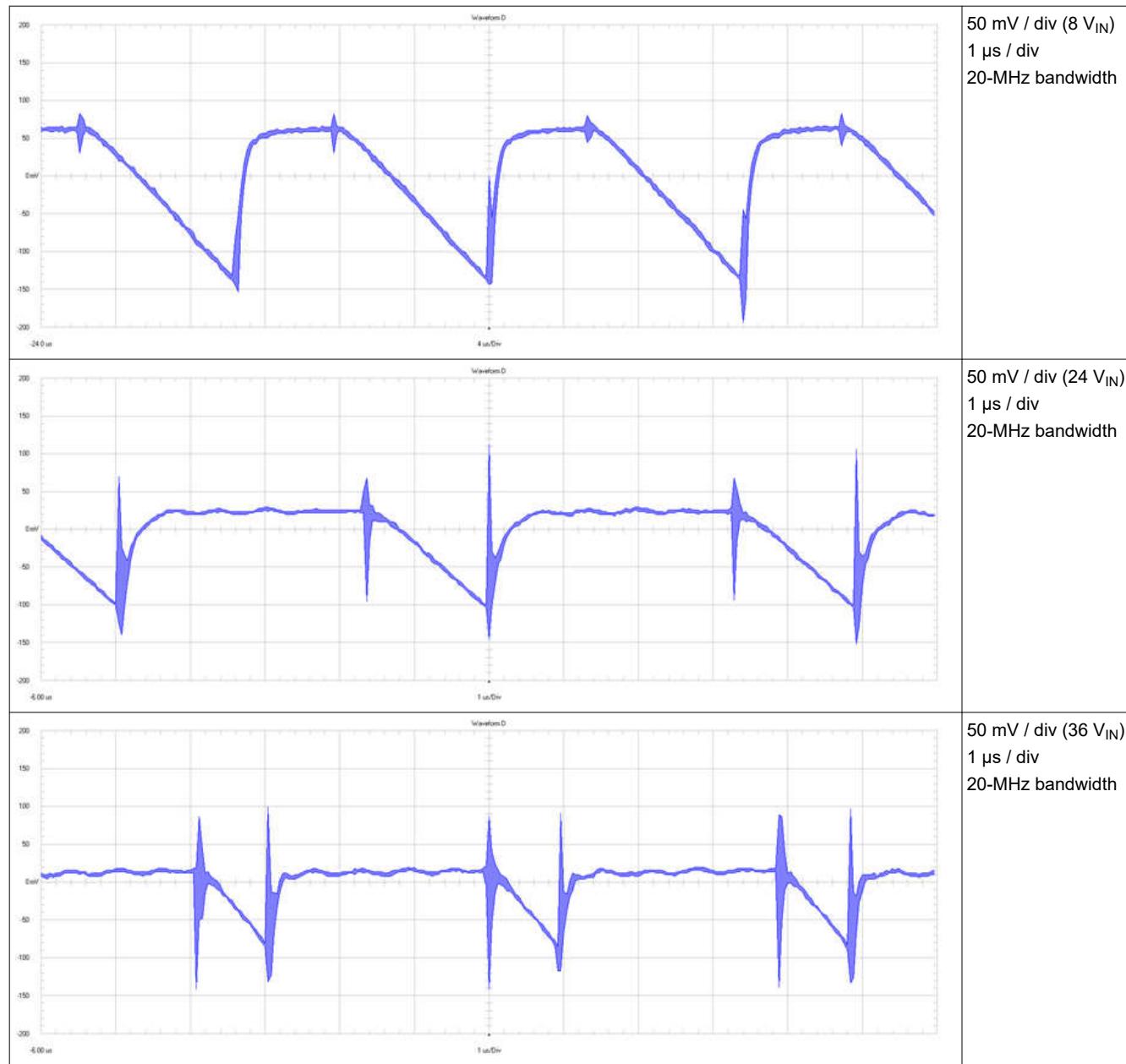


**Figure 3-13. Input Voltage Ripple at Full Load**

### 3.3 Output Voltage Ripple


The input voltage was set to 24 V. Both outputs were fully loaded.

#### 3.3.1 VOUT-A (18 V)

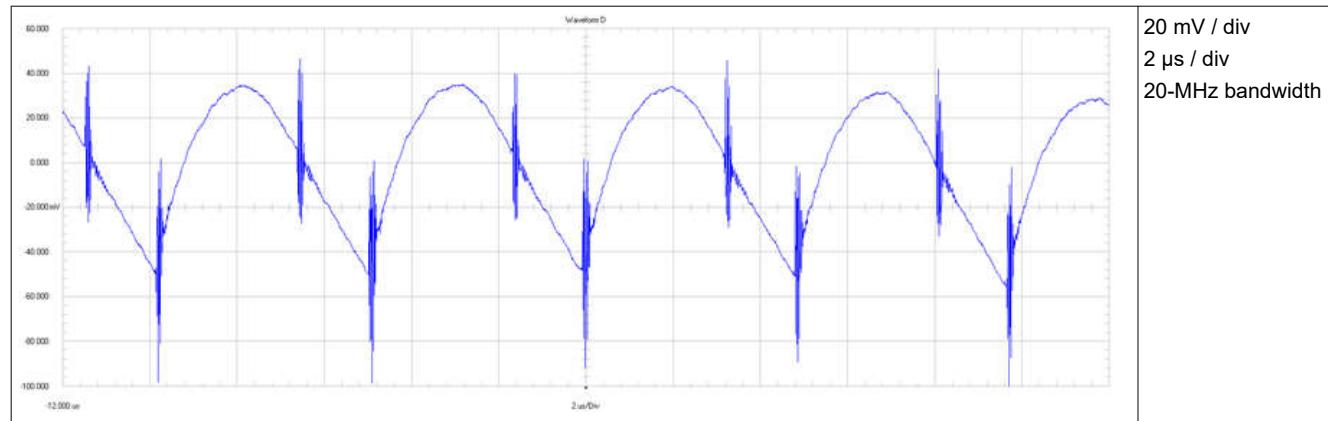

**Figure 3-14. Output Voltage Ripple VOUT-A**

#### 3.3.2 VOUT-B (12 V)

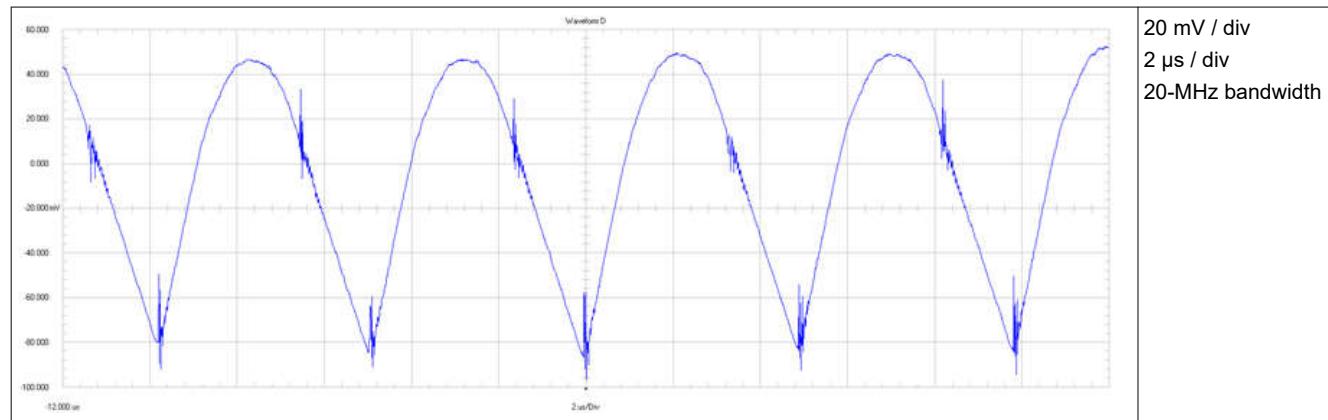

**Figure 3-15. Output Voltage Ripple VOUT-B**

## 3.4 Load Transients

### 3.4.1 Switching on VOUT-A (18 V)

The electronic load switches from 0.03 A to 0.06 A with a frequency of 200 Hz.

#### 3.4.1.1 Effects on VOUT-A

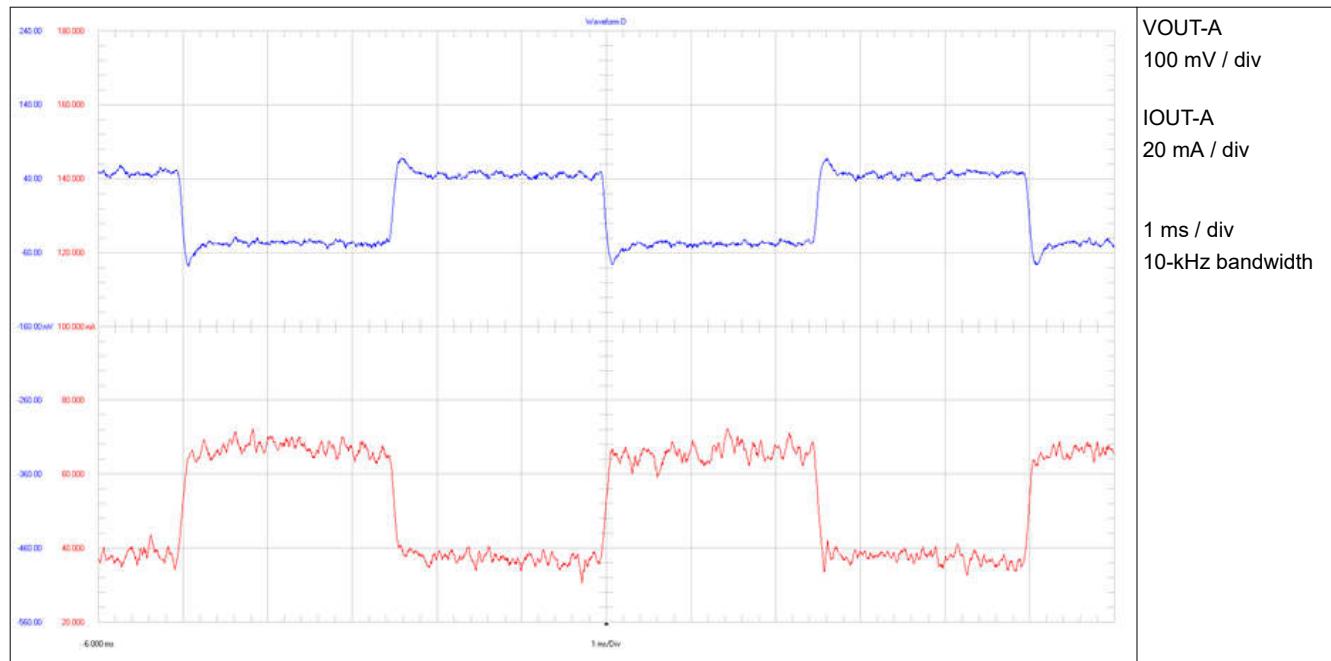


Figure 3-16. Transient on VOUT-A  $\Rightarrow$  VOUT-A

#### 3.4.1.2 Effects on VOUT-B

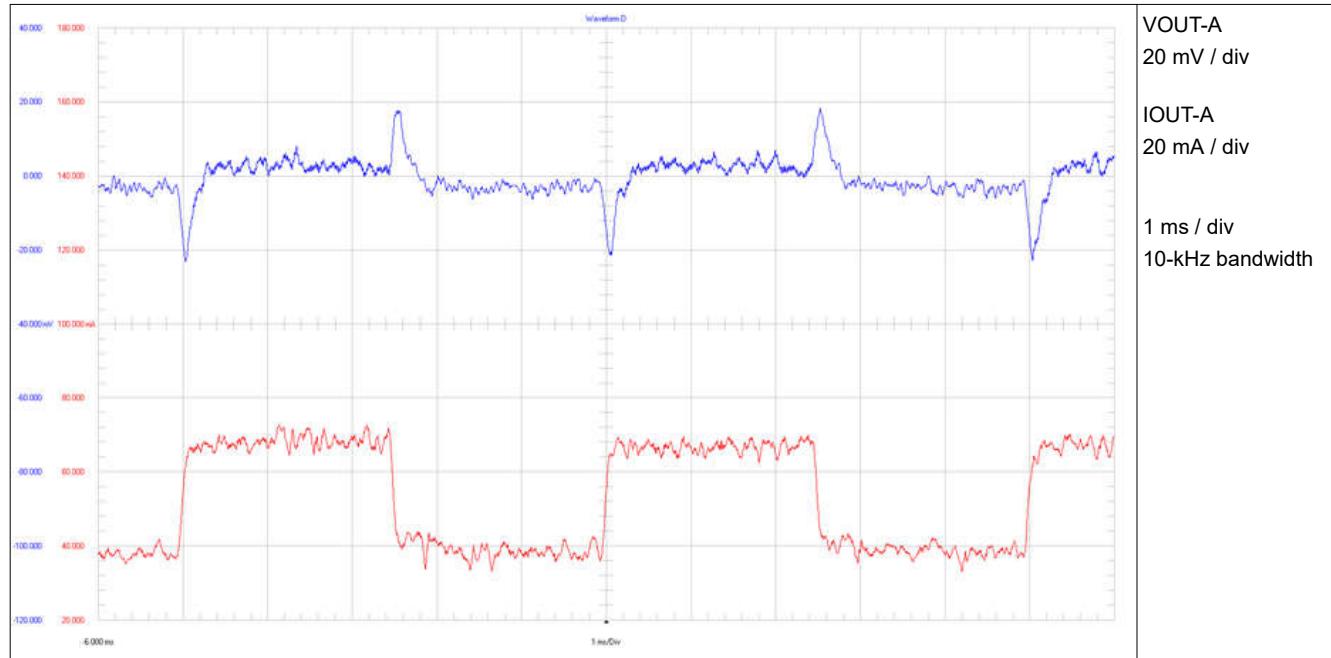


Figure 3-17. Transient on VOUT-A  $\Rightarrow$  VOUT-B

### 3.4.2 Switching on VOUT-B (12 V)

The electronic load switches from 0.05 A to 0.17 A with a frequency of 200 Hz.

#### 3.4.2.1 Effects on VOUT-B

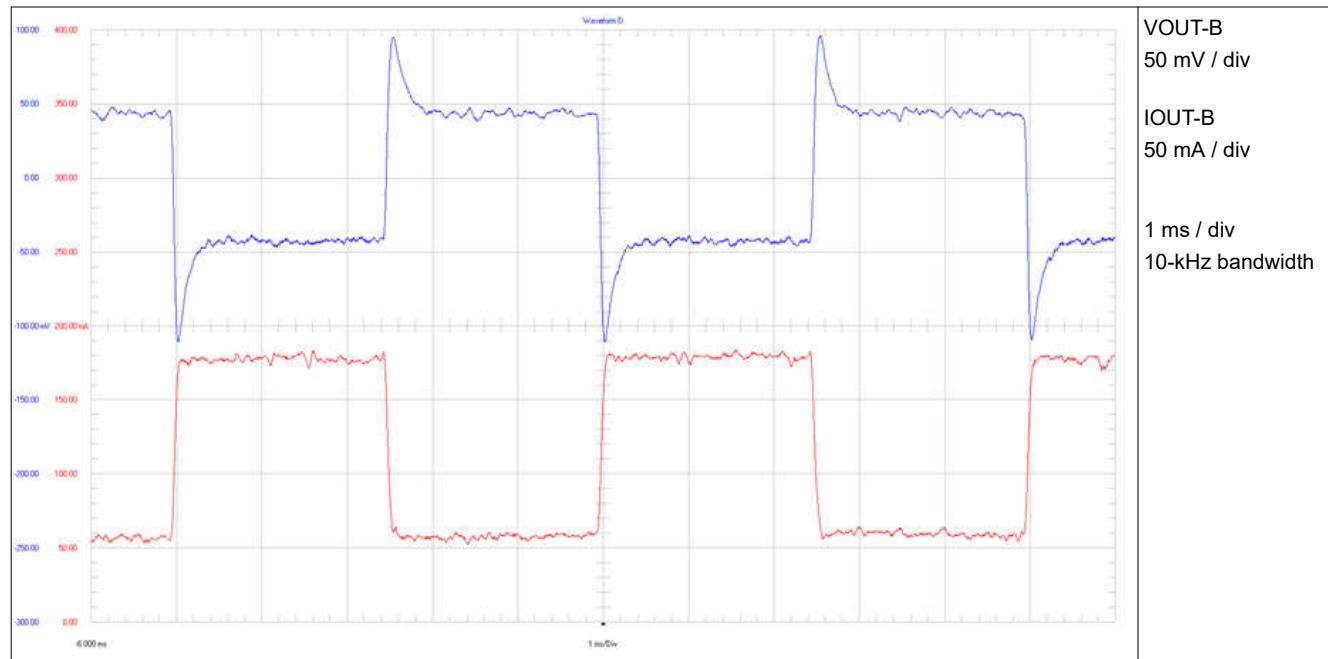


Figure 3-18. Transient on VOUT-B  $\Rightarrow$  VOUT-B

#### 3.4.2.2 Effects on VOUT-A


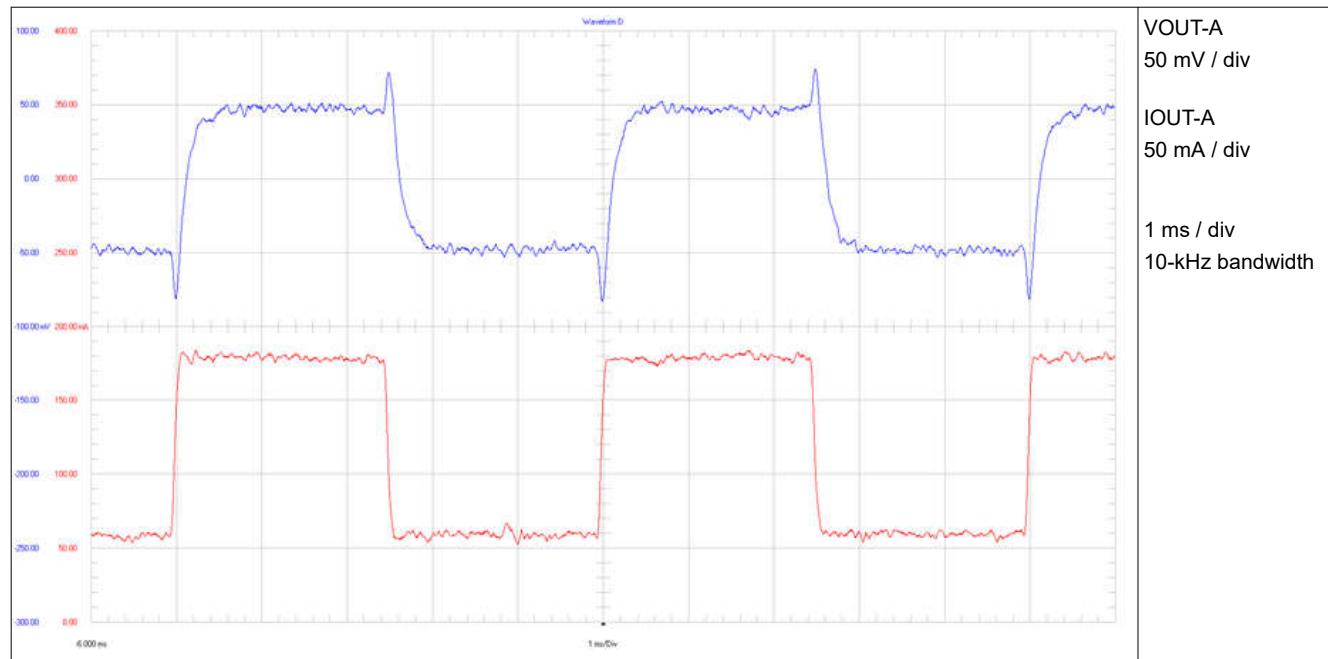


Figure 3-19. Transient on VOUT-B  $\Rightarrow$  VOUT-A


### 3.5 Start-Up Sequence

#### 3.5.1 Full Load

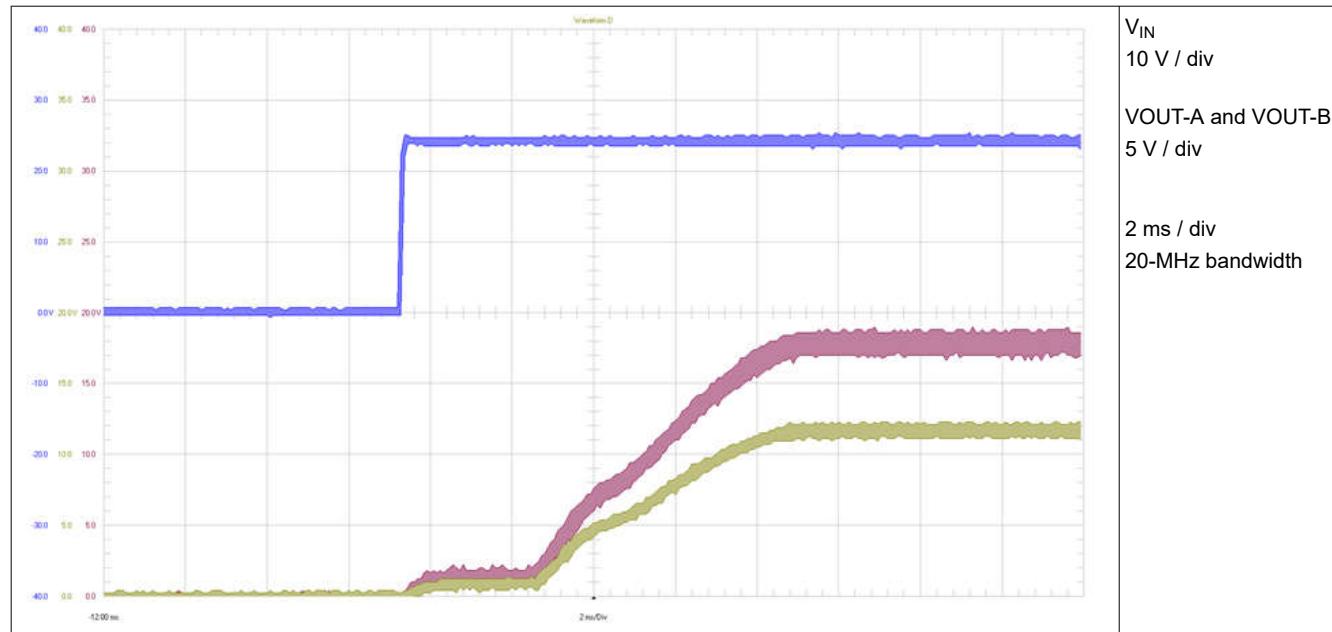


**Figure 3-20. Start-Up With Full Load**

#### 3.5.2 No Load

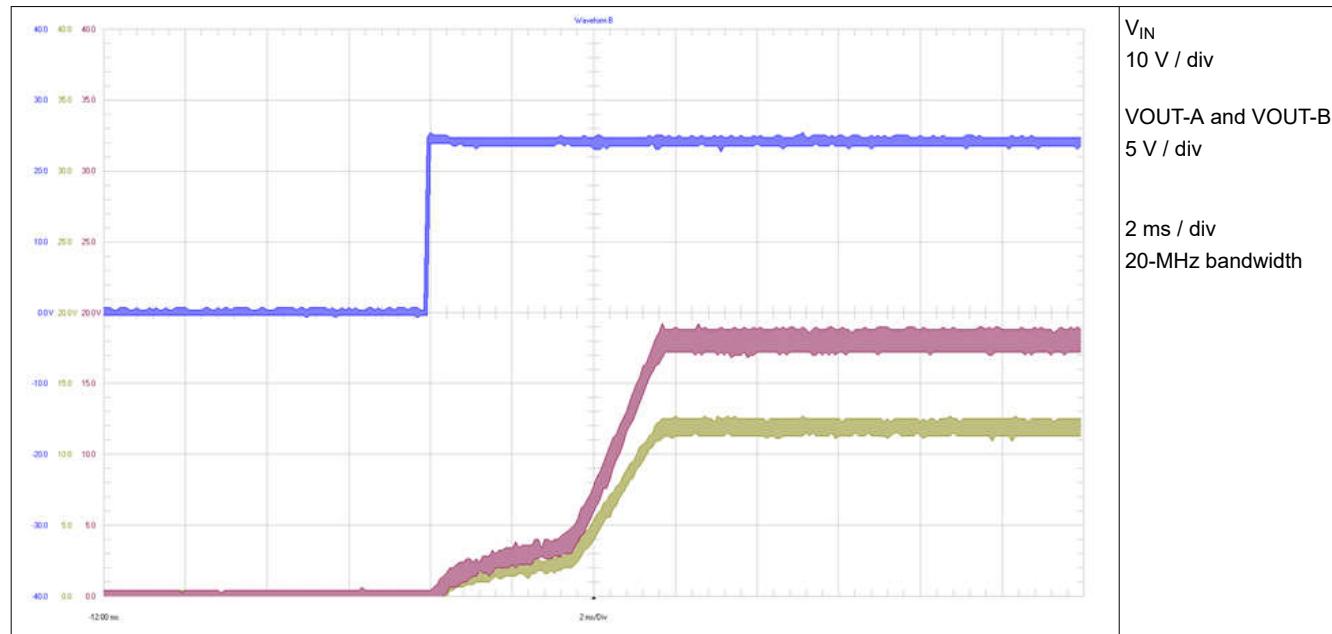

**Figure 3-21. Start-Up With No Load**

### 3.6 Shutdown Sequence

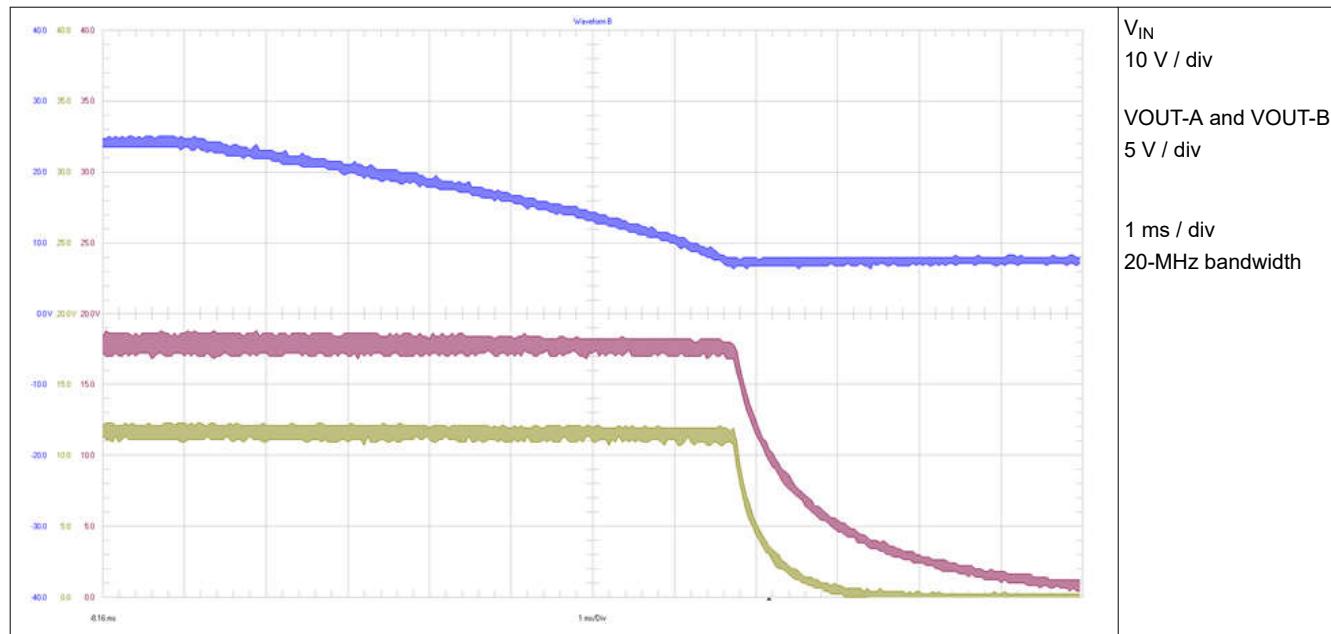

**Figure 3-22. Shutdown With Full Load**

## **IMPORTANT NOTICE AND DISCLAIMER**

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated