

Dual-Phase Buck Converter Reference Design Using GaN FETs for 48V Automotive Applications



Description

This reference design utilizes two LM5148-Q1 single-phase synchronous buck controllers and four LMG3100R017 GaN FETs configured as a dual-phase, interleaved, synchronous buck converter. The converter generates a regulated 5V output capable of delivering a nominal 30A of current to the load, with a peak current capability of 60A, accepting an input voltage of between 24V_{in} to 60V_{in} (48V_{in} nominal). The design is built on a 6-layer PCB with 2oz copper for each of the six layers. The evaluation board measures 5.0in × 3.4in (127.00mm × 86.36mm); however, the actual converter design size measures approximately 53.5mm × 52.0mm. This board is optimized for high efficiency across the entire load current range, which is achieved by configuring the converter to run in Pulse Frequency Modulation (PFM) mode at light loads.

Features


- Small design size
- High efficiency
- Spread-spectrum switching reduces EMI
- Interleaved two-phase operation reduces ripple voltages and RMS currents

Applications

- [Surround view system ECU](#)
- [ADAS domain controller](#)
- [Conditionally automated drive controller](#)



Top of Board

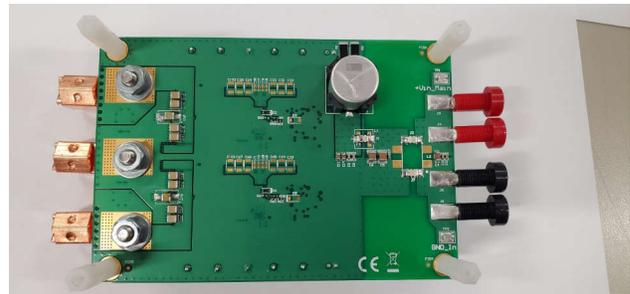

Bottom of Board

1 Test Prerequisites

1.1 Voltage and Current Requirements

Parameter	Specifications
V_{IN}	48V _{DC} Nominal (24V _{IN} minimum; 60V _{IN} maximum)
V_{OUT}	5V _{DC}
I_{OUT}	30A nominal (60A peak)
F_{sw}	300kHz per phase (600kHz effective interleaved)

1.2 Required Equipment

- Power Supply
- Electronic Load
- DMMs
- Oscilloscope

1.3 Considerations

Unless stated otherwise, the tests performed in this test report are taken at the nominal 48V input voltage and 30A load current and the device is configured to PFM mode.

2 Testing and Results

2.1 Efficiency, Power Loss, and Load Regulation Graphs

Figure 2-1 through Figure 2-12 show the buck converter efficiency, power loss, and load regulation, at 24V, 48V, and 60V input voltages.

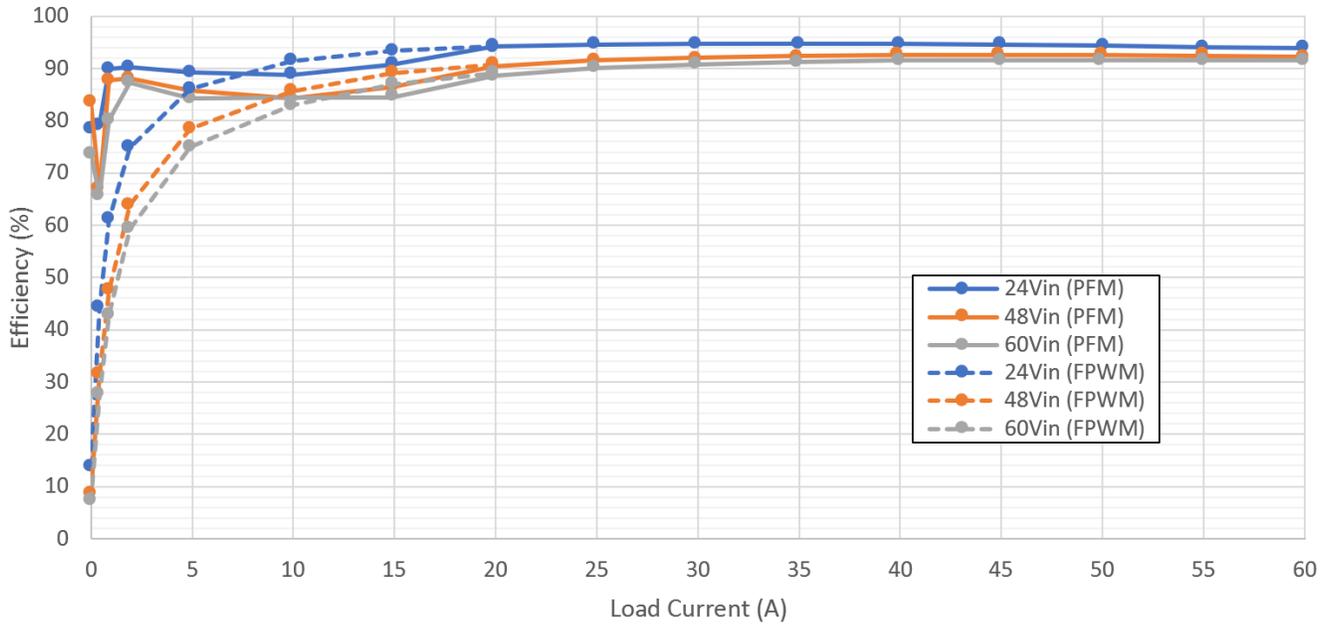


Figure 2-1. Efficiency (0A to 60A)

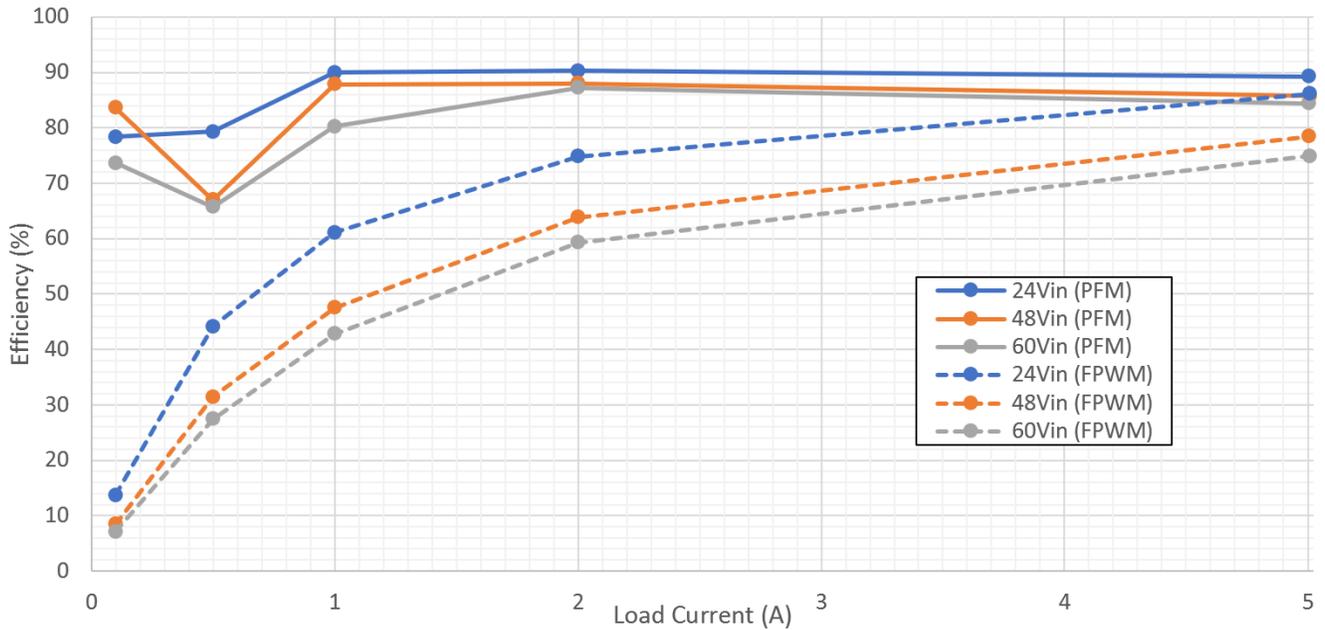


Figure 2-2. Efficiency (0A to 5A)

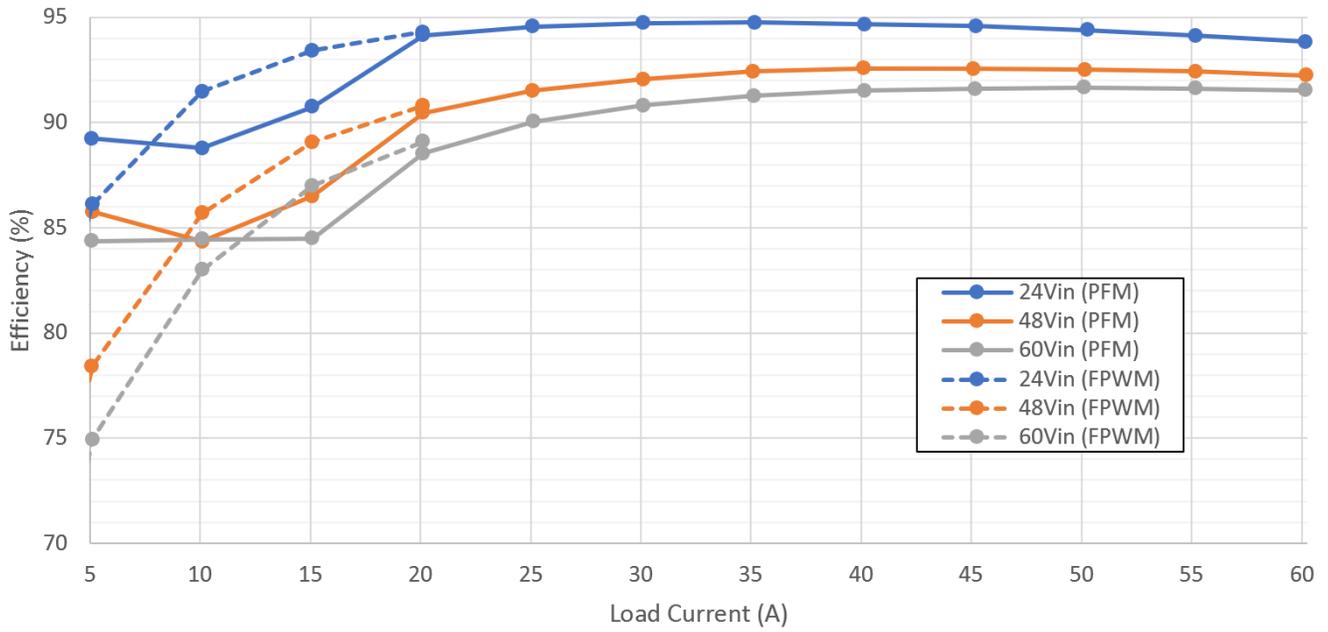


Figure 2-3. Efficiency (5A to 60A)

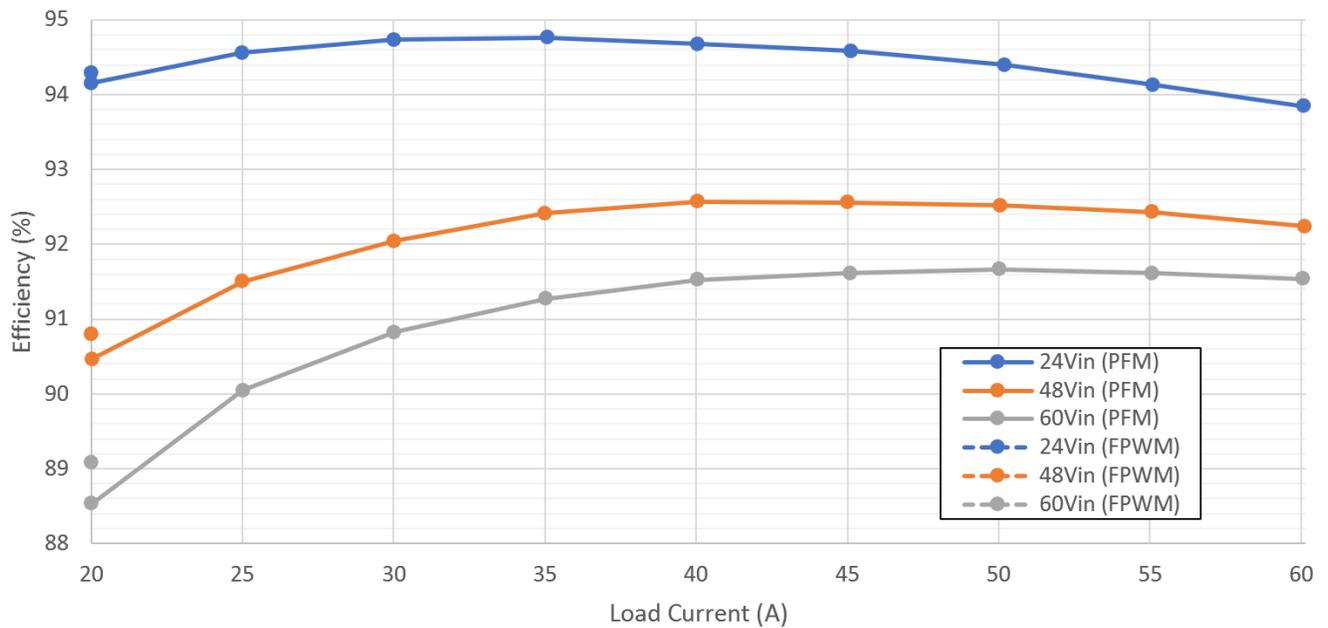


Figure 2-4. Efficiency (20A to 60A)

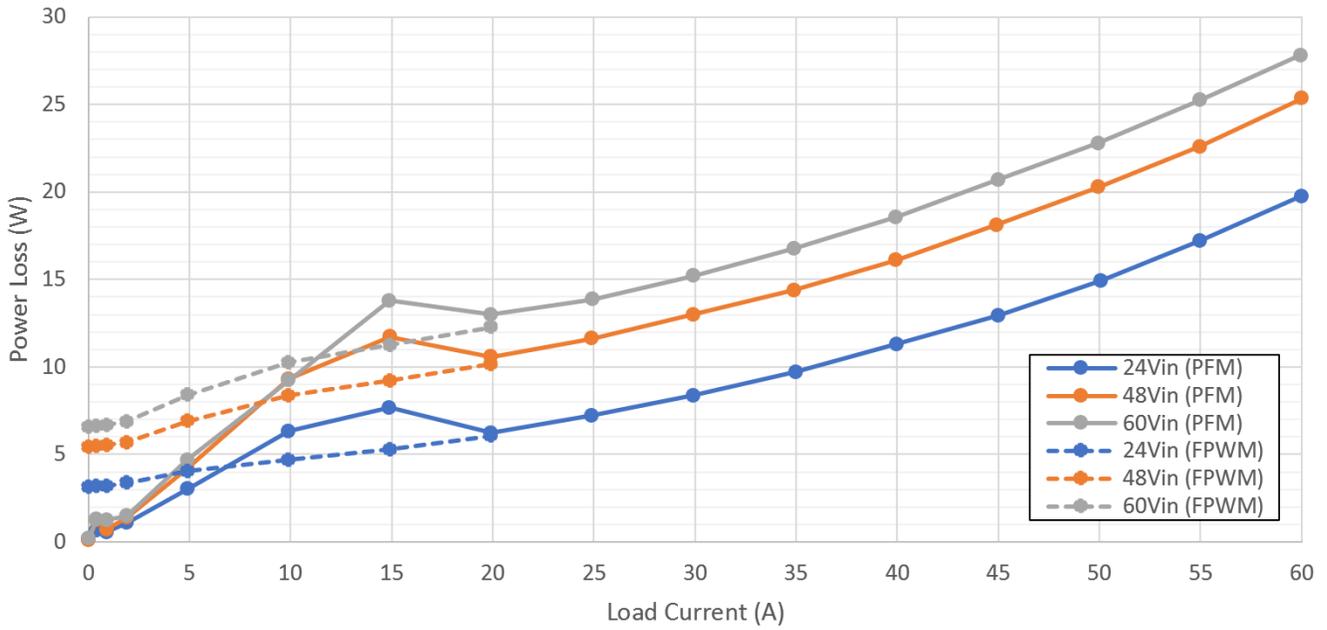


Figure 2-5. Power Loss (0A to 60A Load)

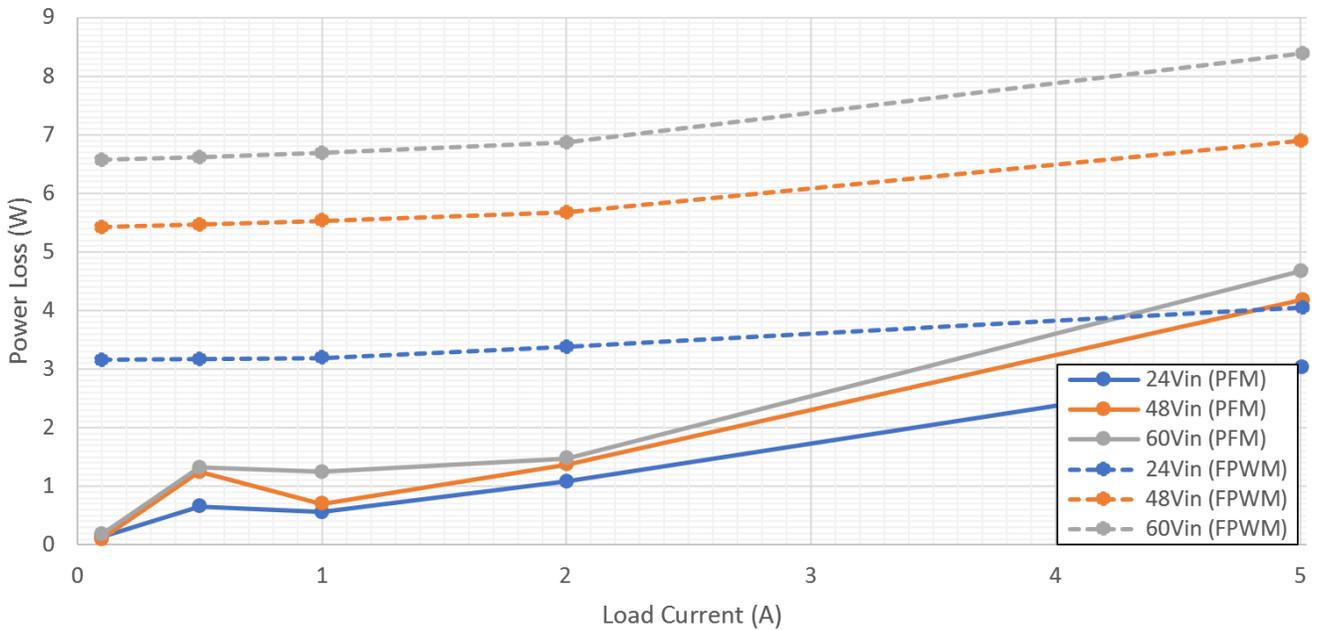


Figure 2-6. Power Loss (0A to 5A Load)

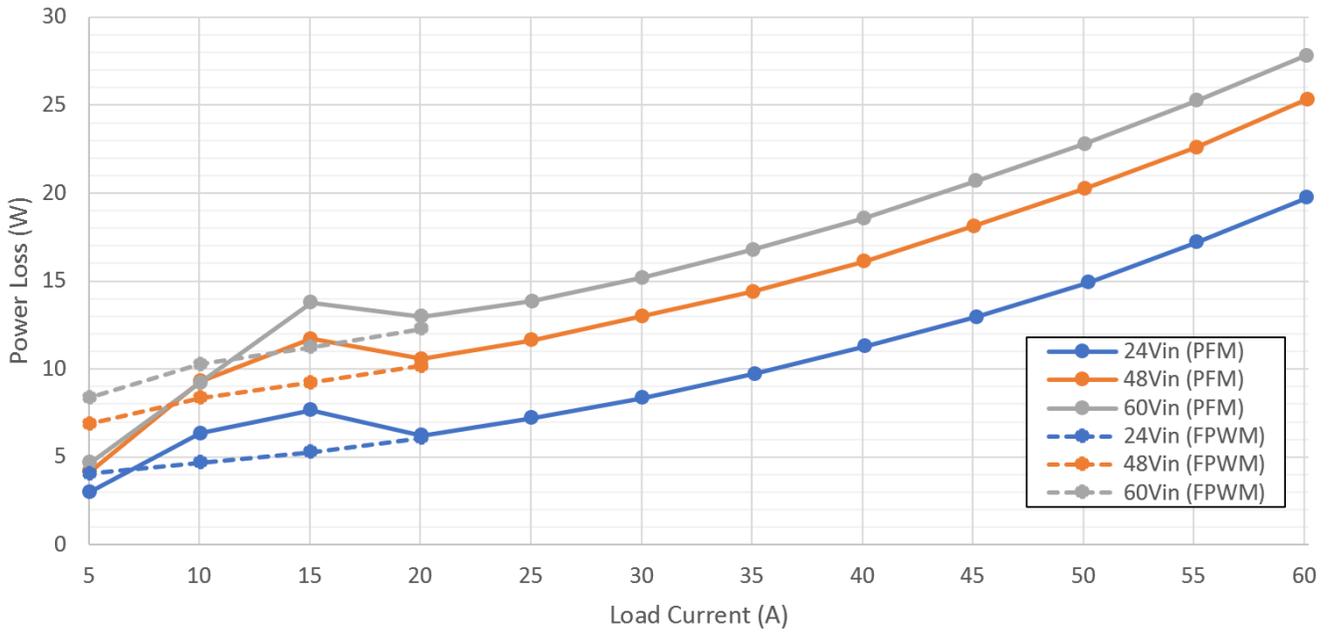


Figure 2-7. Power Loss (5A to 60A Load)

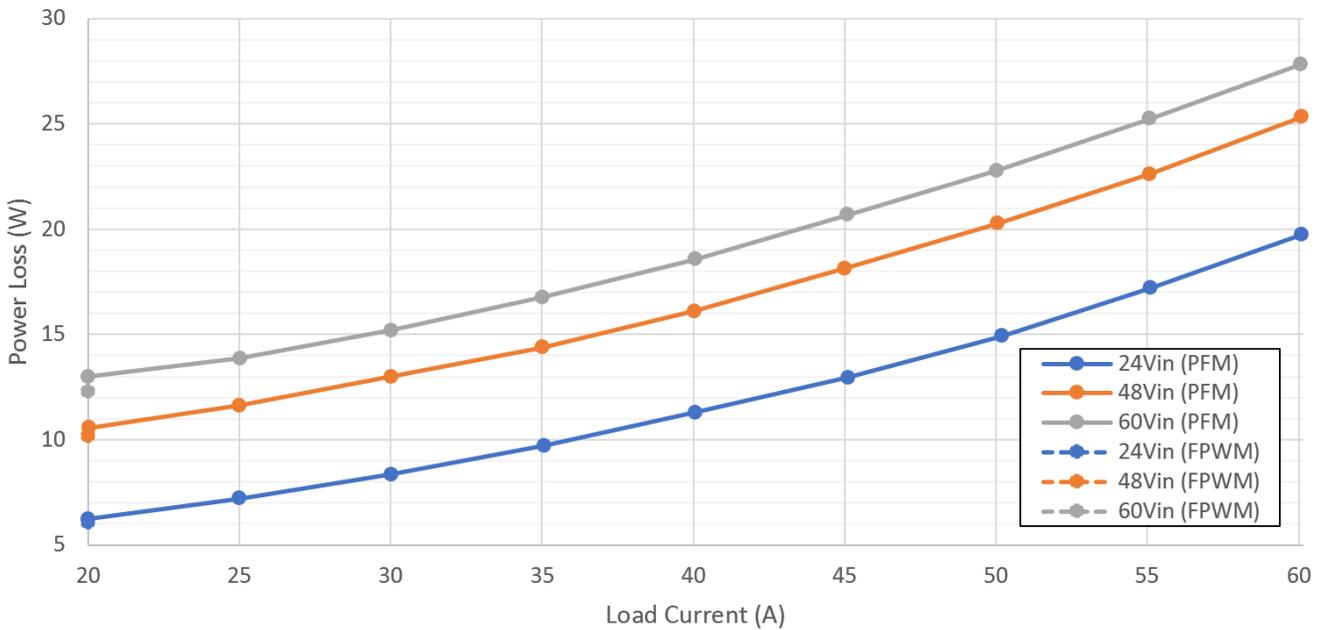


Figure 2-8. Power Loss (20A to 60A Load)

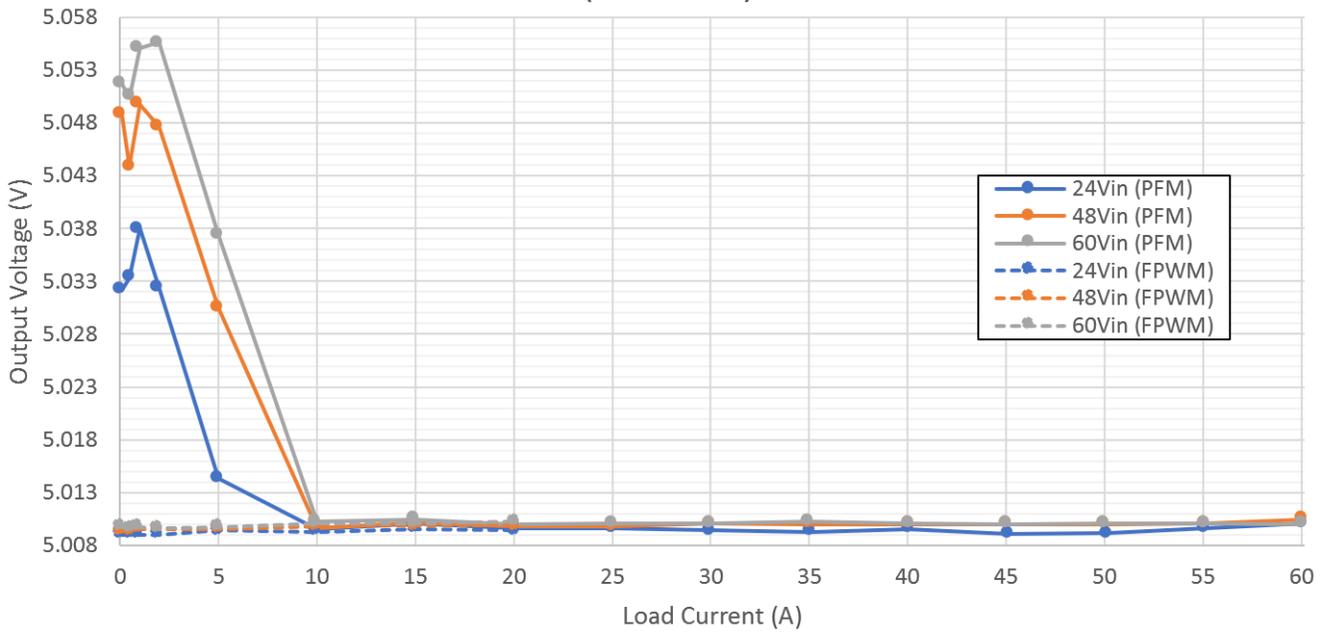


Figure 2-9. Load Regulation (0A to 60A Load)

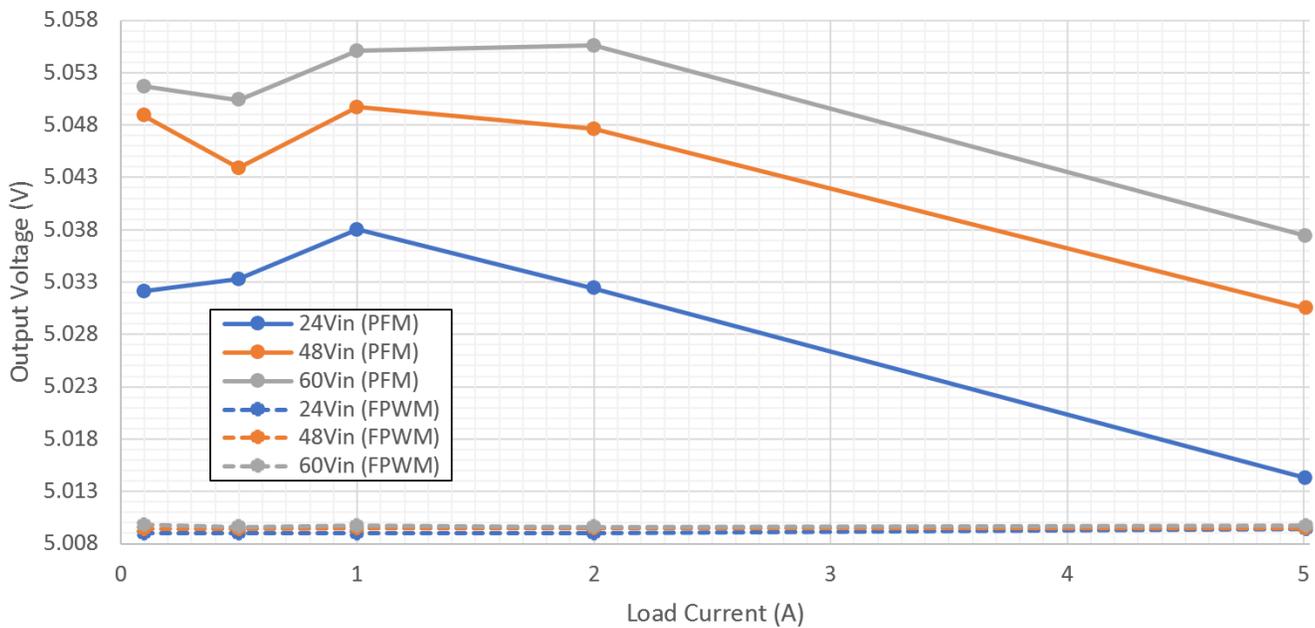


Figure 2-10. Load Regulation (0A to 5A Load)

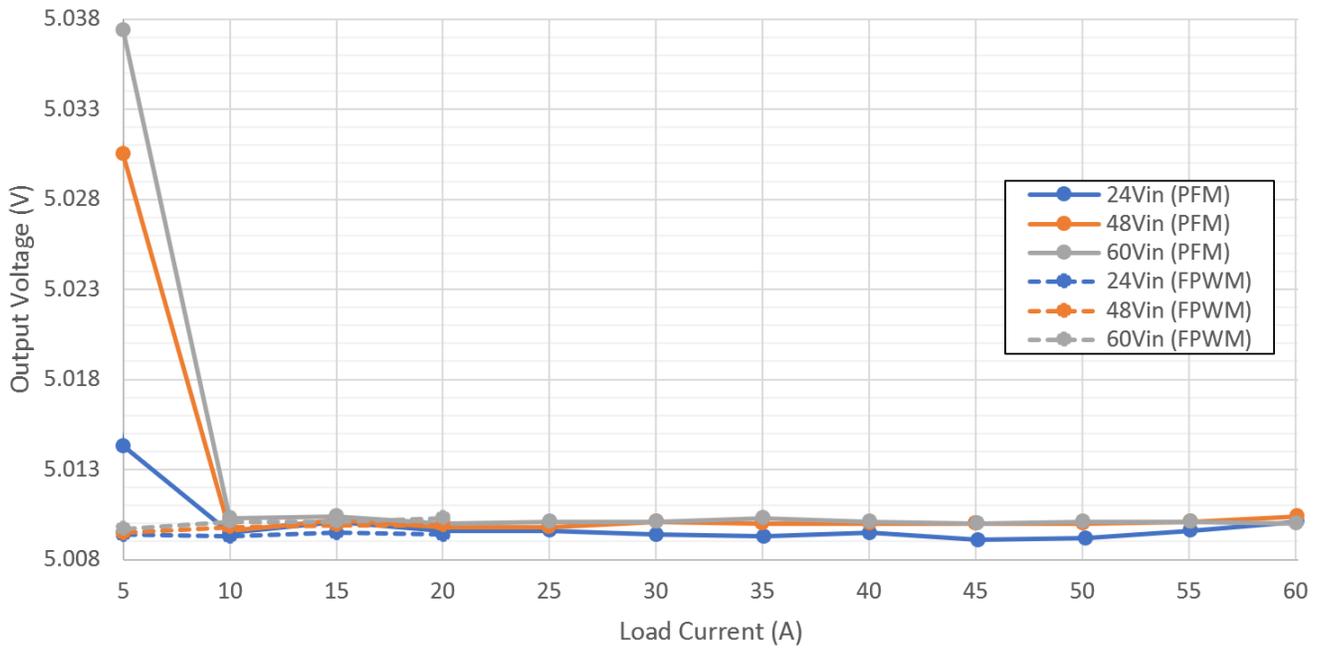


Figure 2-11. Load Regulation (5A to 60A Load)


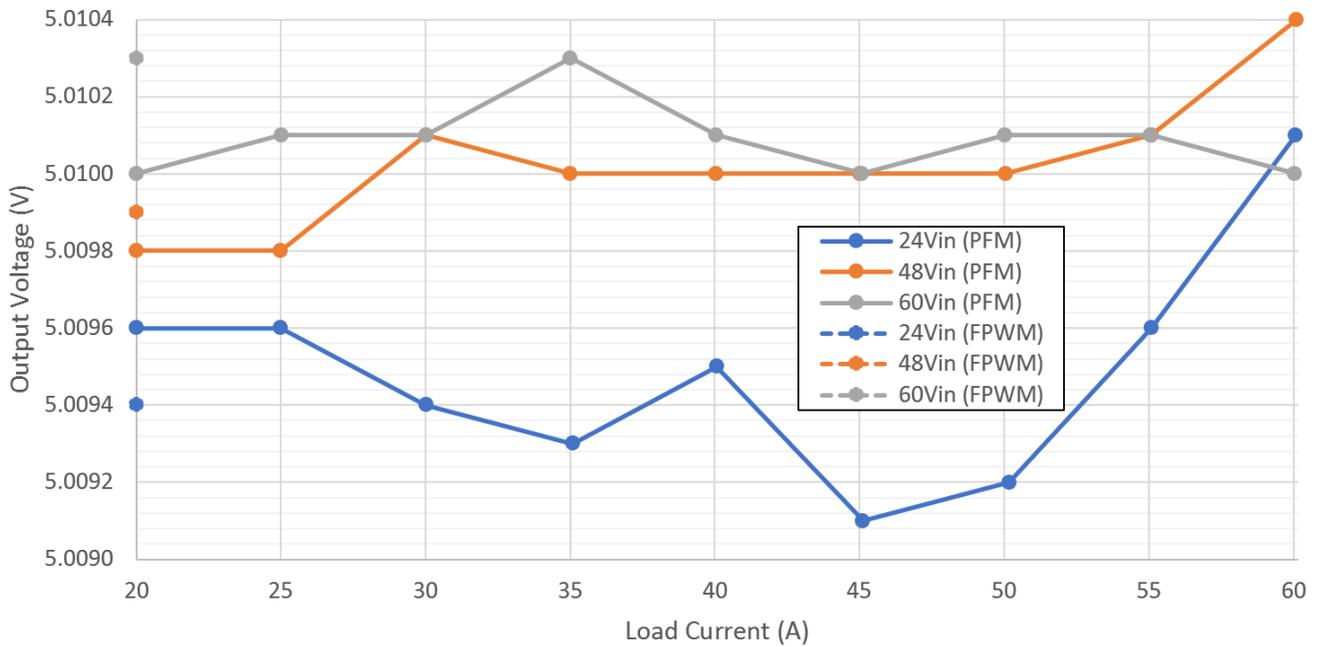


Figure 2-12. Load Regulation (20A to 60A Load)

2.2 Thermal Images

Figure 2-13 shows the buck converter thermal performance operating at 48V input and 30A load. The thermal test was conducted at room temperature with no airflow (natural convection), and the image was captured after thermal equilibrium was reached.

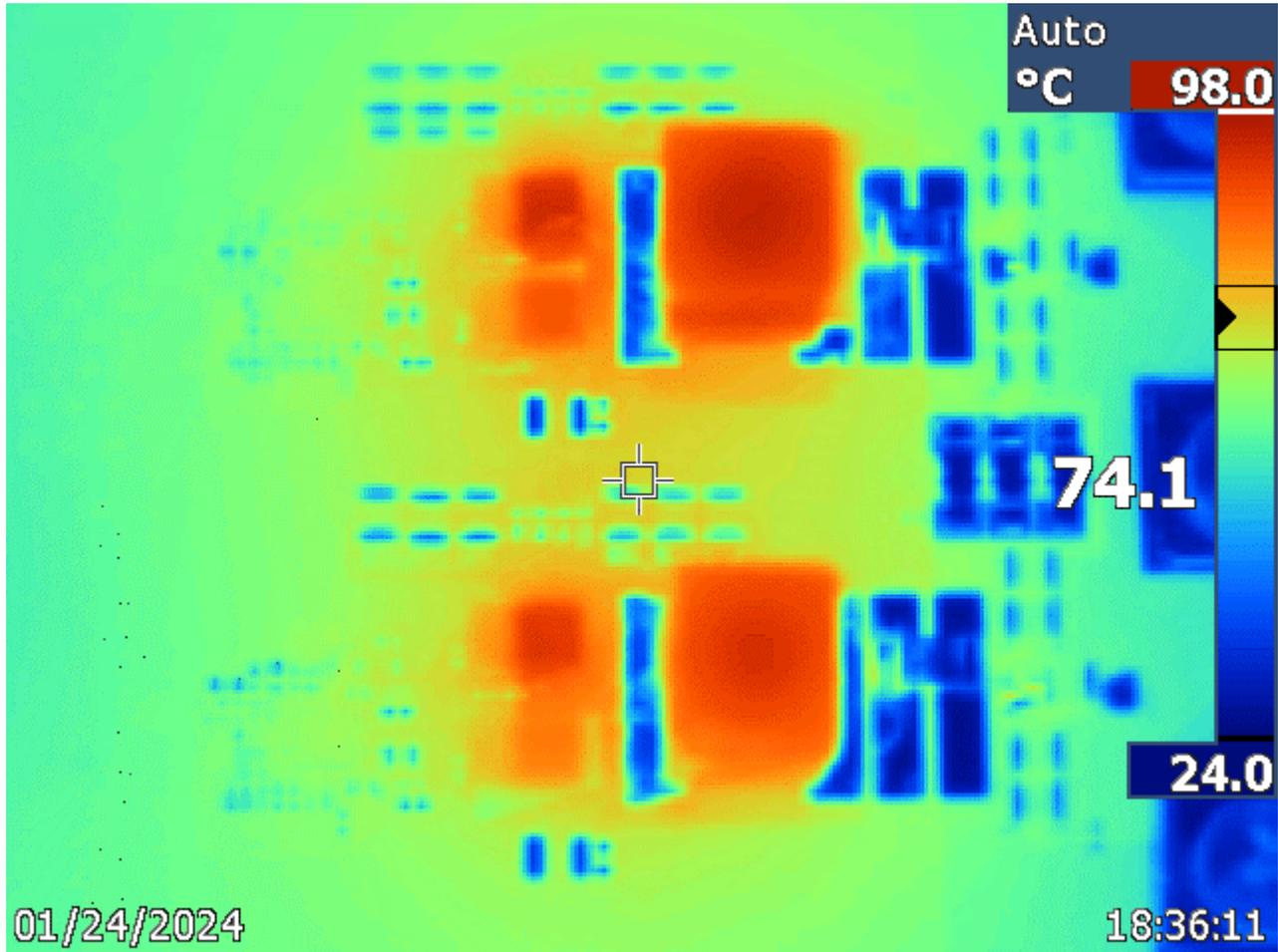

Natural convection (that is, no airflow); ambient at room temperature; thermal equilibrium reached

Figure 2-13. Thermal Image, 48V Input, 5V Output at 30A Load

2.3 Dimensions

Figure 2-14 and Figure 2-15 present the top and bottom photos of the PMP23392 board, respectively. The board dimensions are 5.0in × 3.4in (127.00mm × 86.36mm). Remember that this is an evaluation board and has plenty of unutilized space, for ease of testing. The final design size can be significantly reduced to approximately 53.5mm × 52.0mm (or smaller).

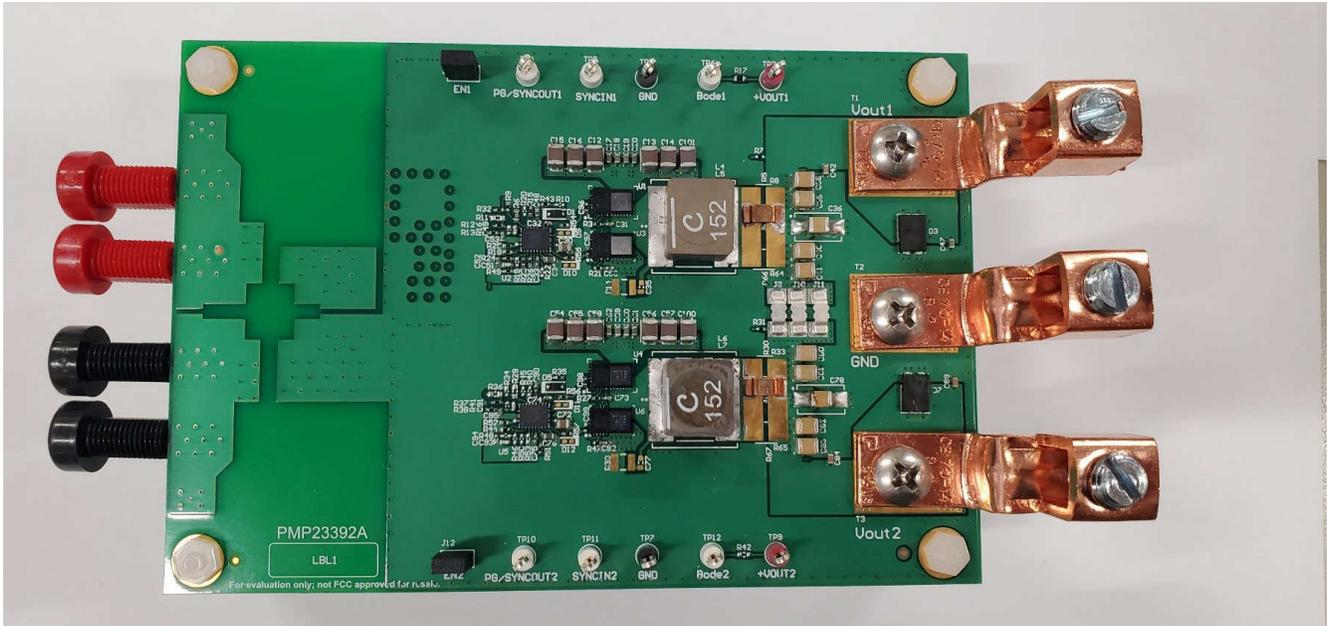


Figure 2-14. Top of PMP23392 Board

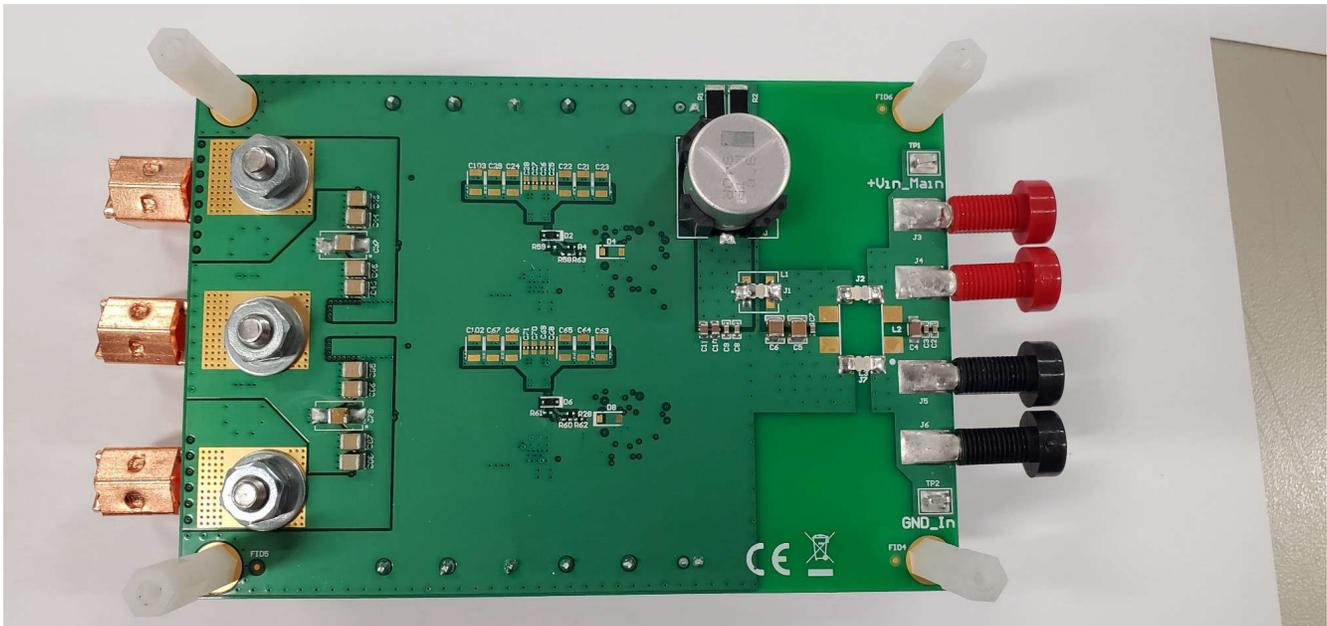


Figure 2-15. Bottom of PMP23392 Board

3 Waveforms

3.1 Switching

Figure 3-1 through Figure 3-9 show the switch node voltages of the buck converter at various operating conditions.



Figure 3-1. Switch Node Voltages, 24V Input, No Load, PFM Mode

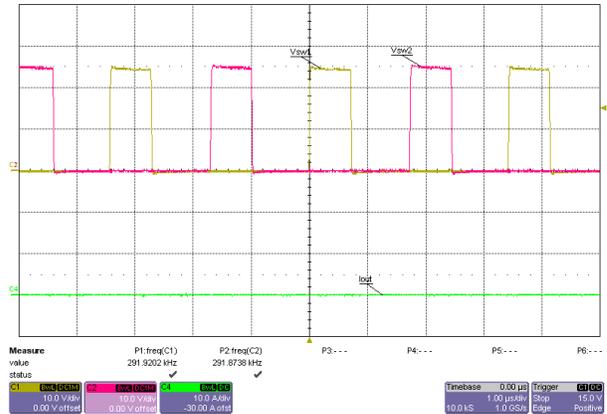


Figure 3-2. Switch Node Voltages, 24V Input, No Load, FPWM Mode

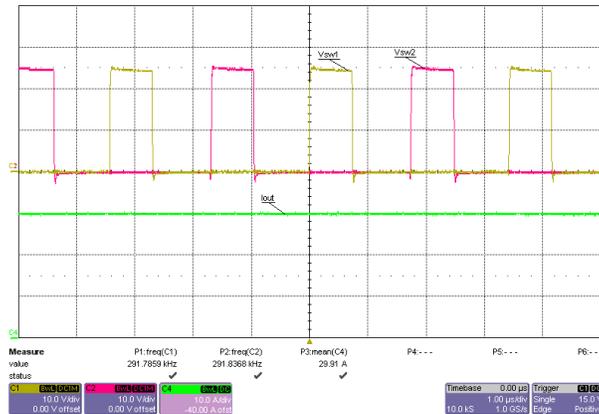


Figure 3-3. Switch Node Voltages, 24V Input, 30A Load

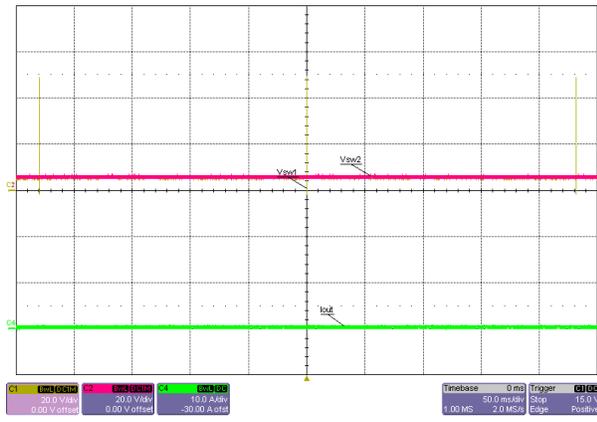


Figure 3-4. Switch Node Voltages, 48V Input, No Load, PFM Mode

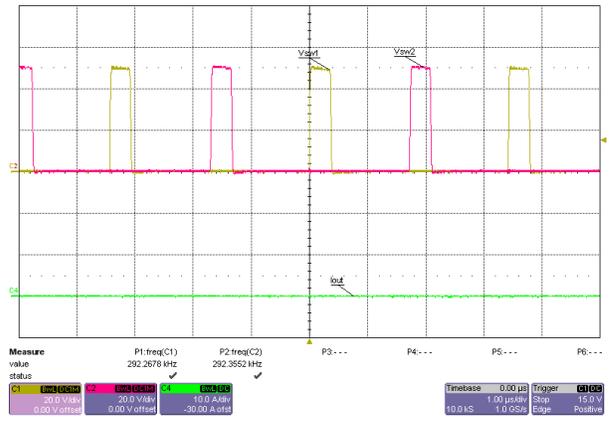


Figure 3-5. Switch Node Voltages, 48V Input, No Load, FPWM Mode

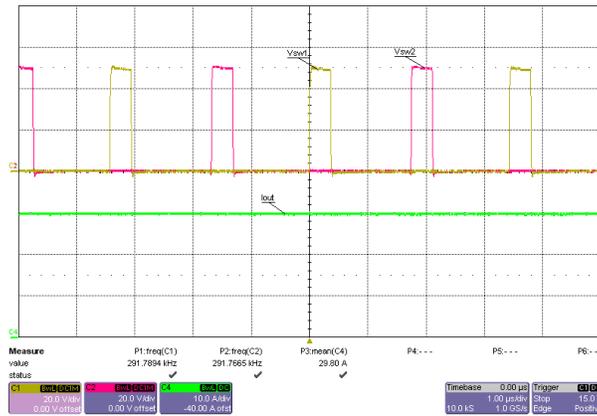


Figure 3-6. Switch Node Voltages, 48V Input, 30A Load

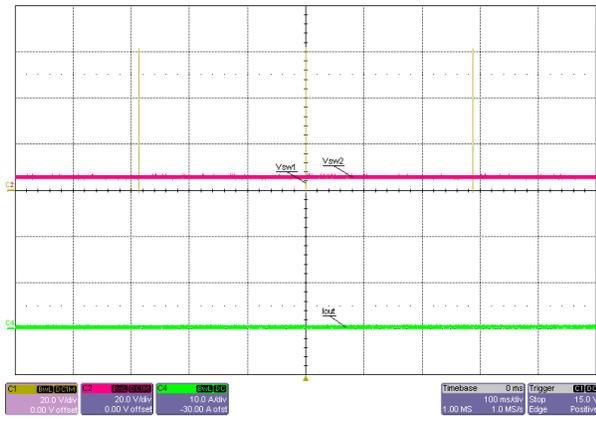


Figure 3-7. Switch Node Voltages, 60V Input, No Load, PFM Mode

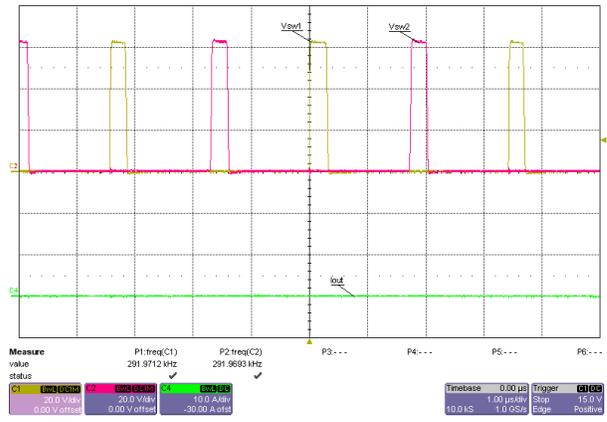


Figure 3-8. Switch Node Voltages, 60V Input, No Load, FPWM Mode

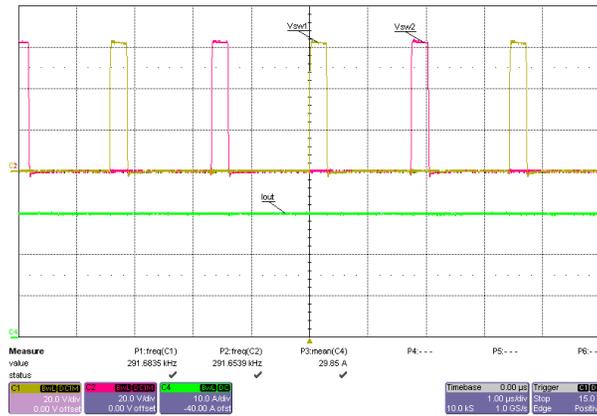


Figure 3-9. Switch Node Voltages, 60V Input, 30A Load

3.2 Output Voltage Ripple

Figure 3-10 through Figure 3-18 show the output voltage ripple at various operating conditions

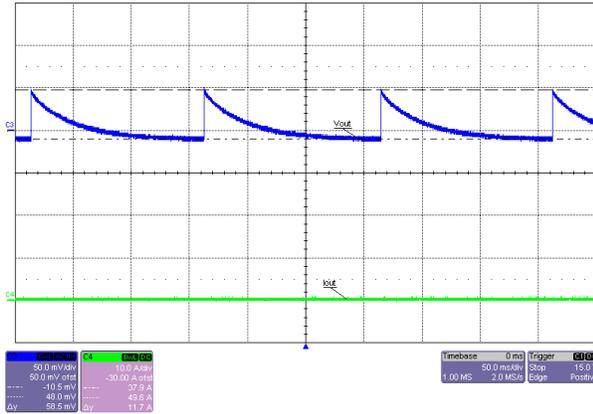


Figure 3-10. Output Voltage Ripple, 24V Input, No Load, PFM Mode

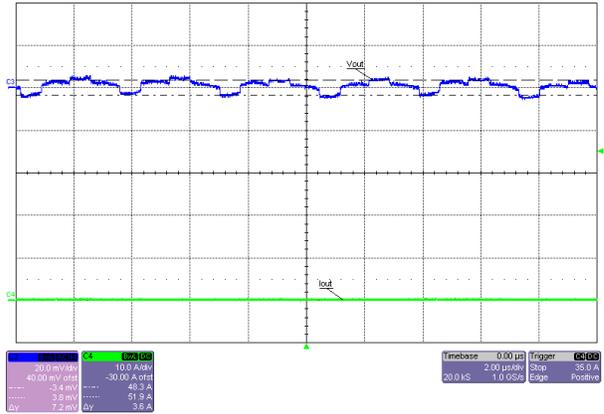


Figure 3-11. Output Voltage Ripple, 24V Input, No Load, FPWM Mode

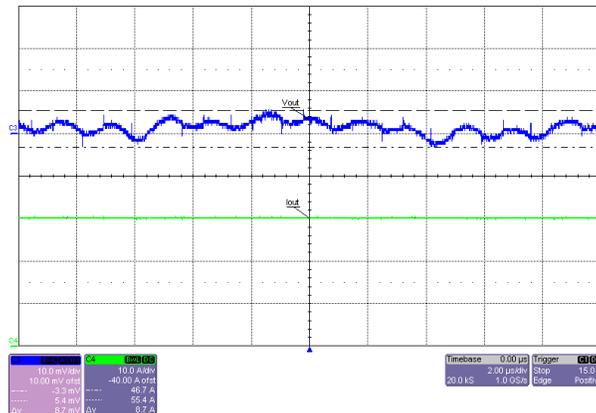


Figure 3-12. Output Voltage Ripple, 24V Input, 30A Load

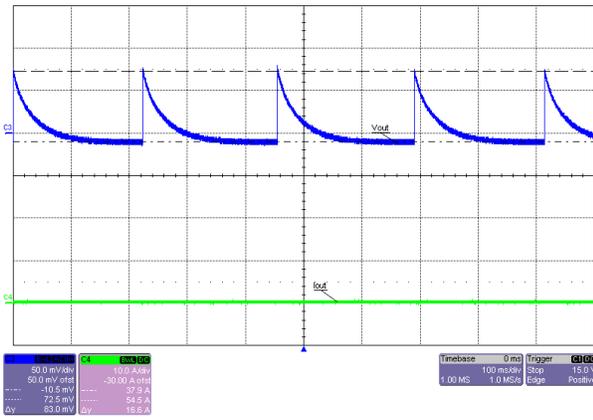


Figure 3-13. Output Voltage Ripple, 48V Input, No Load, PFM Mode

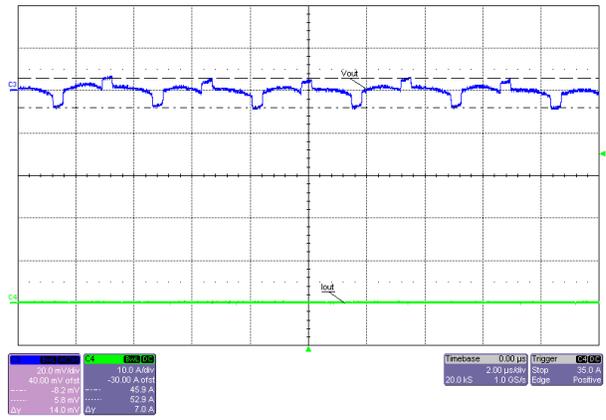


Figure 3-14. Output Voltage Ripple, 48V Input, No Load, FPWM Mode

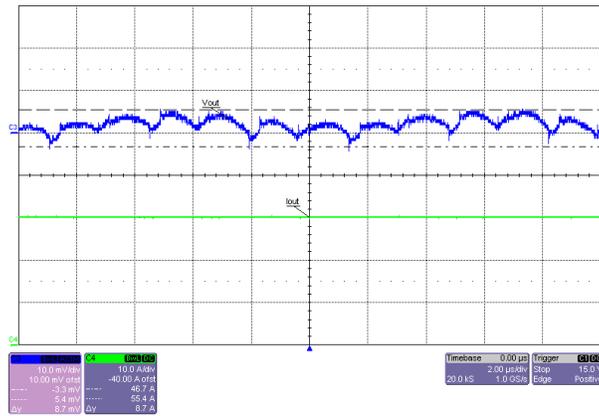


Figure 3-15. Output Voltage Ripple, 48V Input, 30A Load

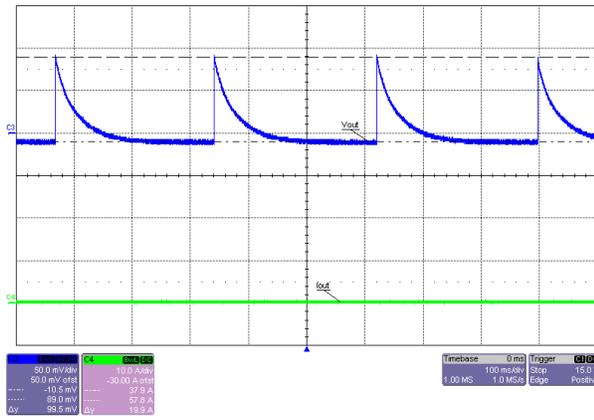


Figure 3-16. Output Voltage Ripple, 60V Input, No Load, PFM Mode

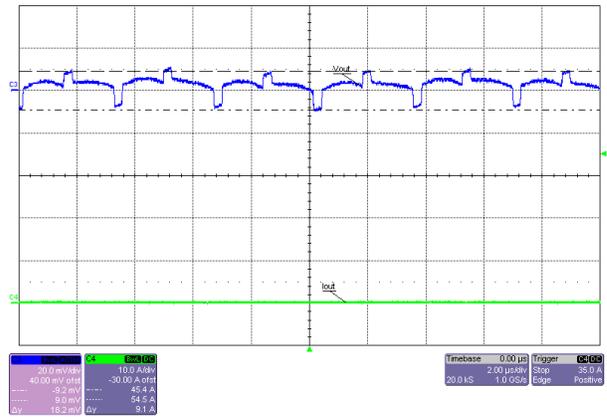


Figure 3-17. Output Voltage Ripple, 60V Input, No Load, FPWM Mode

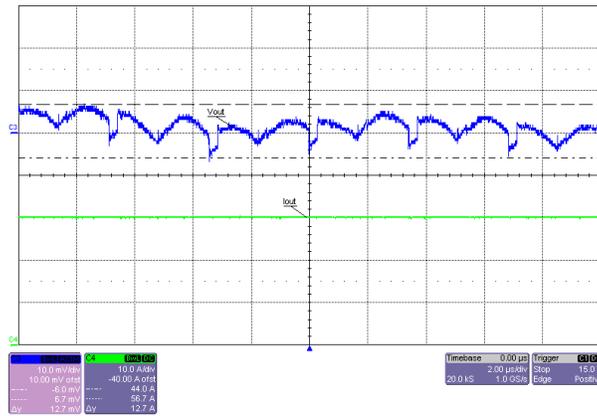


Figure 3-18. Output Voltage Ripple, 60V Input, 30A Load

3.3 Load Transient Response

Figure 3-19 through Figure 3-21 show the load transient waveforms of at various input voltages with the output undergoing a 30A-to-60A load step.

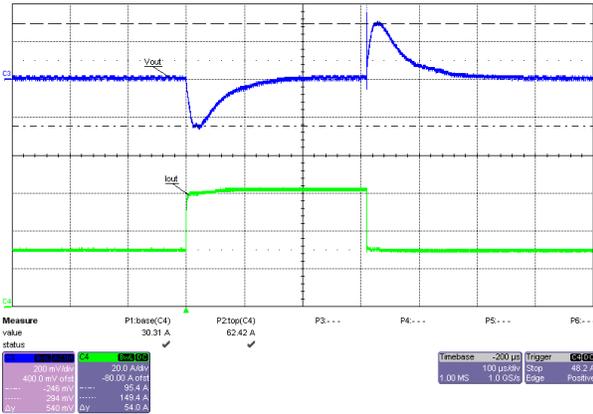


Figure 3-19. Load Transient Response, 24V Input, 30A-to-60A Load Step

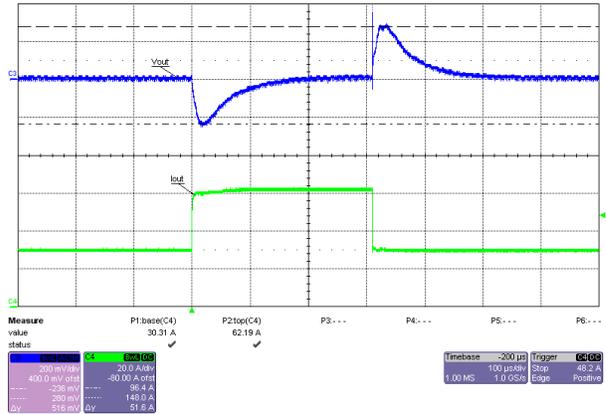


Figure 3-20. Load Transient Response, 48V Input, 30A-to-60A Load Step

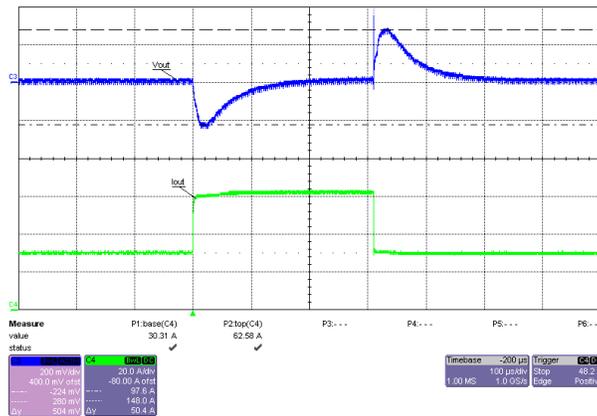


Figure 3-21. Load Transient Response, 60V Input, 30A-to-60A Load Step

3.4 Start-Up

Figure 3-22 through Figure 3-27 show the start-up waveforms of the converter at various operating conditions.

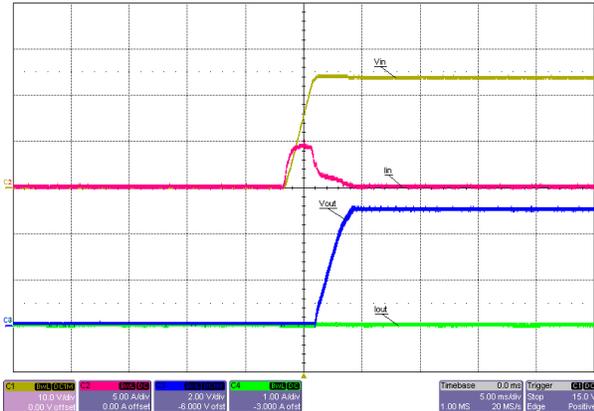


Figure 3-22. Start-Up Into No Load, 24V Input

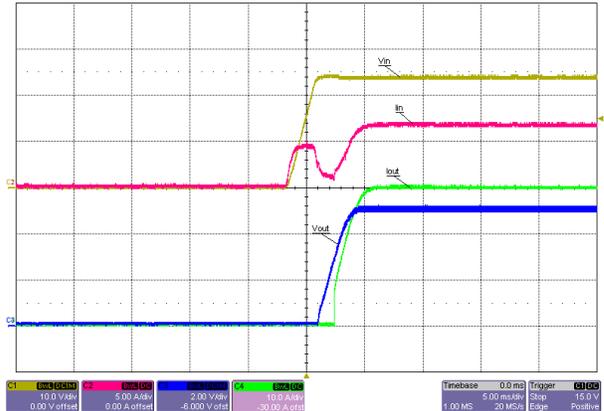


Figure 3-23. Start-Up Into 30A Constant-Resistance Load, 24V Input

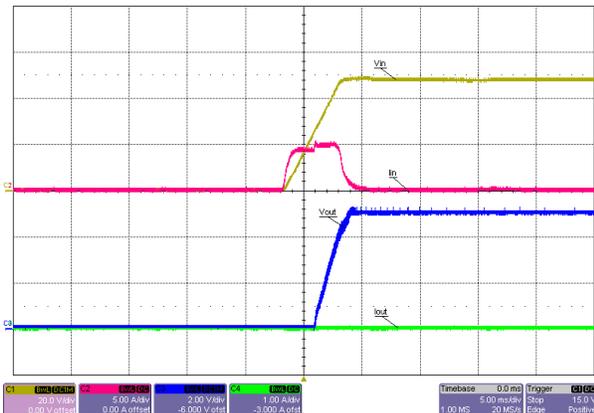


Figure 3-24. Start-Up Into No Load, 48V Input

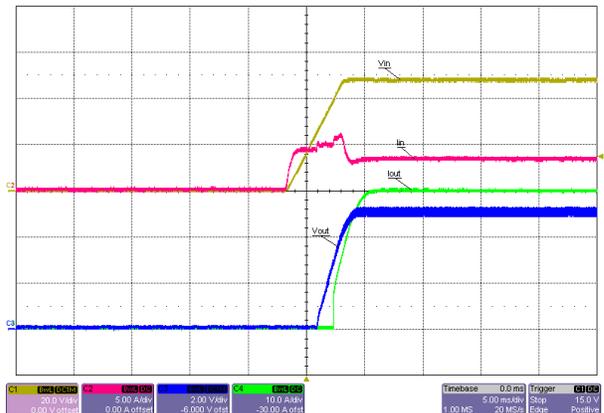


Figure 3-25. Start-Up Into 30A Constant-Resistance Load, 48V Input

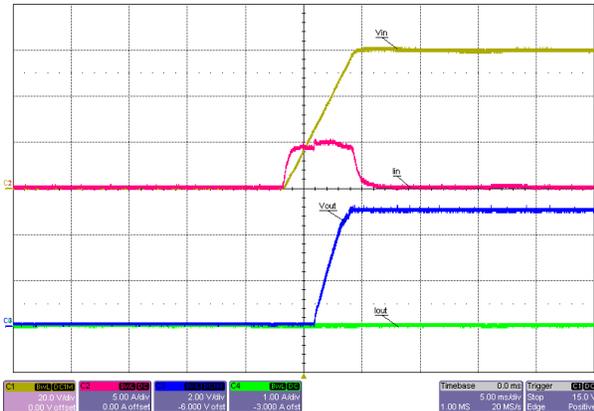


Figure 3-26. Start-Up Into No Load, 60V Input

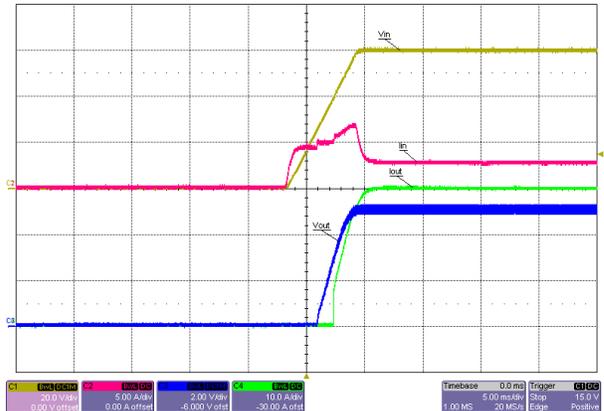


Figure 3-27. Start-Up Into 30A Constant-Resistance Load, 60V Input

3.5 Overcurrent Protection

Figure 3-28 shows the overcurrent protection (OCP) threshold of the buck converter at 48V input voltage.

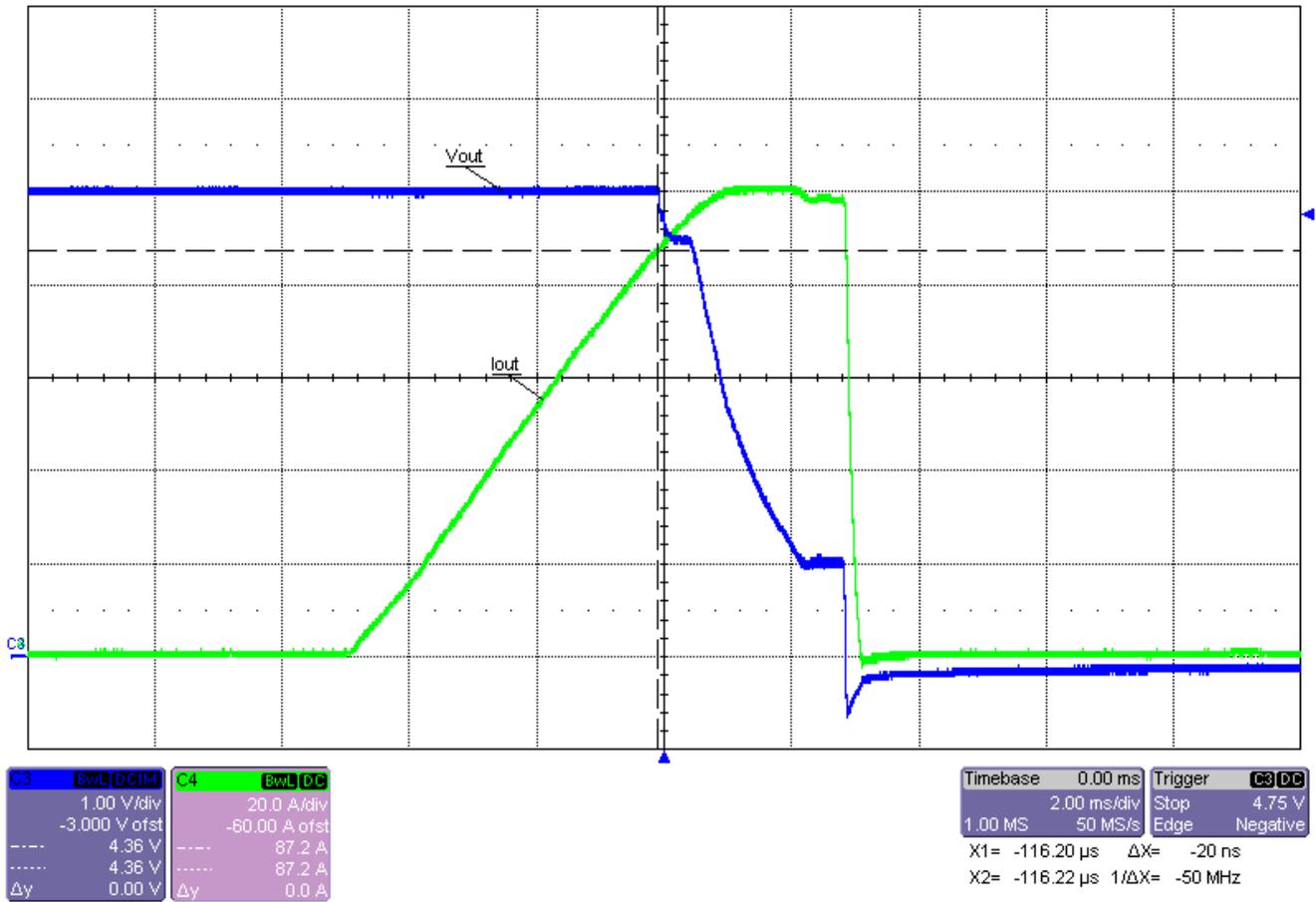


Figure 3-28. Overcurrent Protection at 48V Input

3.6 Efficiency and Power Loss Comparison of Varying Solutions

Figure 3-29 and Figure 3-30 show the difference in efficiency and power loss between Silicon FET and GaN FET designs operating at various switching frequencies. Results shown are taken at 48V input voltage.

The PMP23392 design uses LMG3100R017 GaN FETs switching at 300kHz / phase and XAL1010-152 inductors, exemplifying a small solution size. A variant of the PMP23392 design (using LMG3100R017 GaN FETs) except using ZE2652-AE inductors and switching at 150kHz / phase, exemplifies a high-efficiency solution.

PMP23420, a design equivalent to PMP23392, yet using Silicon FETs, ZE2652-AE inductors, and switching at 150kHz / phase, exemplifies a low-cost solution.

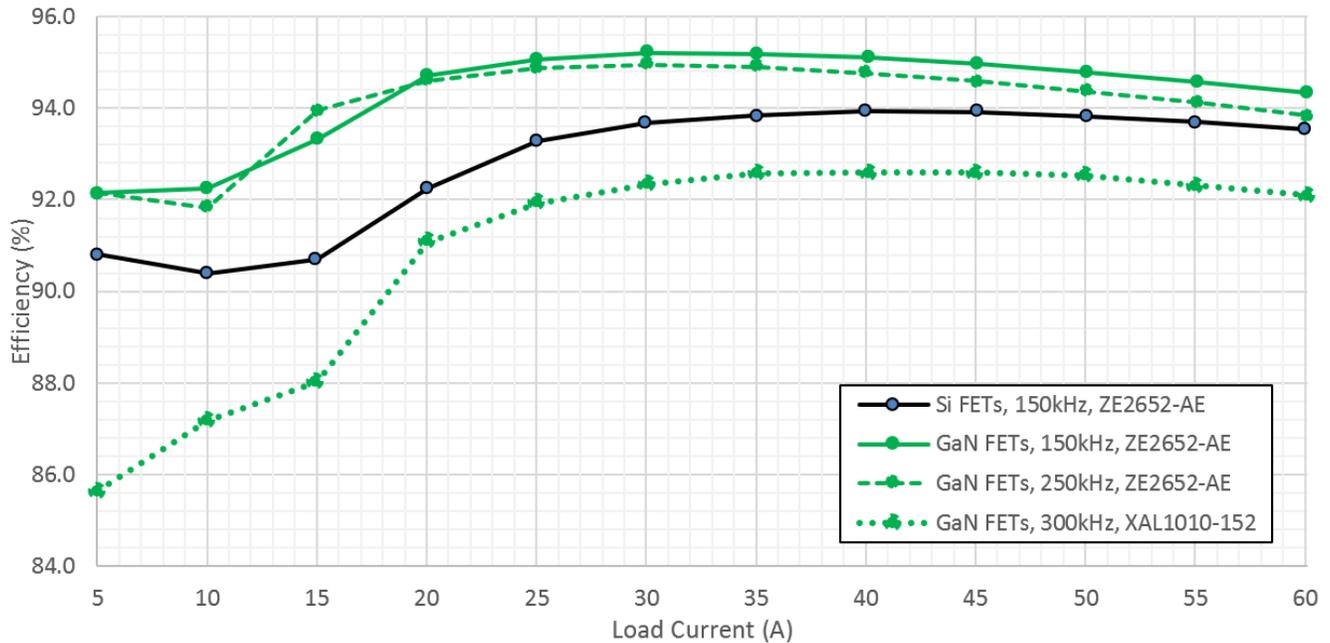


Figure 3-29. Efficiency Comparison Between Silicon and GaN FET Solutions at Varying Switching Frequencies (5A to 60A Load)

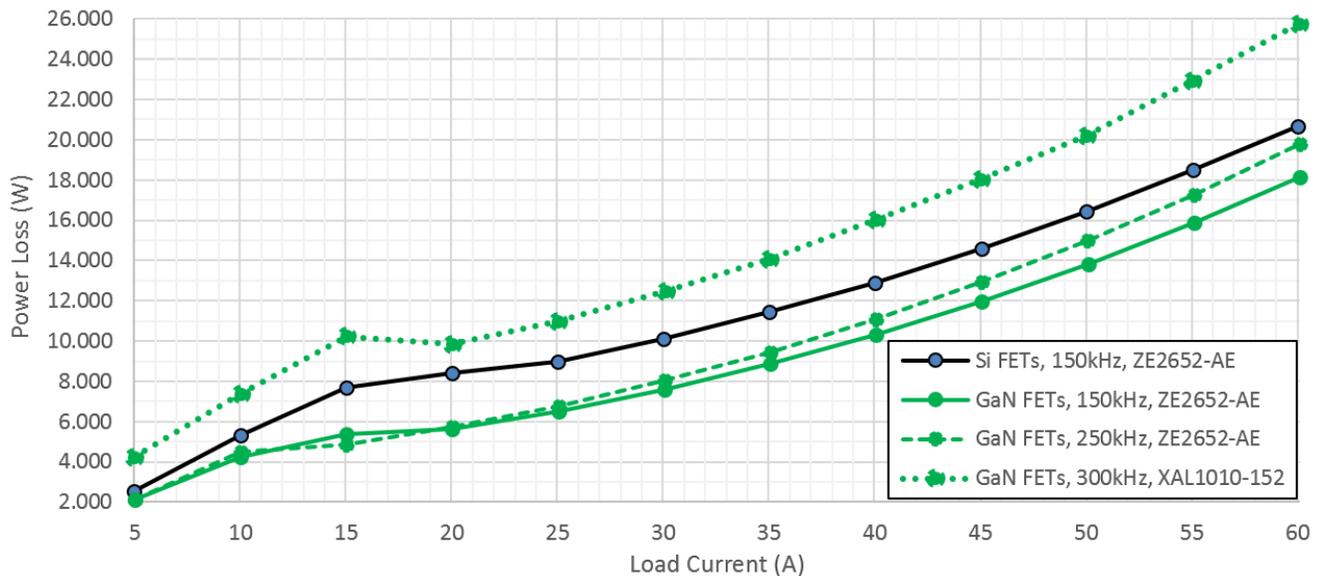


Figure 3-30. Power Loss Comparison Between Silicon and GaN FET Solutions at Varying Switching Frequencies (5A to 60A Load)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated