

7.8W Wide AC Input Non-Isolated High-Side Buck Reference Design



Description

This reference design is an ultra-wide input offline high-side buck power supply that provides a 13V output at a maximum of 0.6A. The input accepts a voltage range of 85V_{AC} to 485V_{AC}. The reference design uses the UCC28750 current-mode flyback controller with optocoupler feedback. The design is developed to be resistant to magnetic fields up to 200mT near the inductor.


Features

- Fixed-frequency operation for full load

- Frequency foldback and burst mode for improved light-load efficiency
- Very wide input voltage range: 85V_{AC} to 485V_{AC}
- Overvoltage and undervoltage lockout
- Output short-circuit (OSC) protection
- Cycle-by-cycle peak overcurrent limit
- High magnetic resistance

Applications

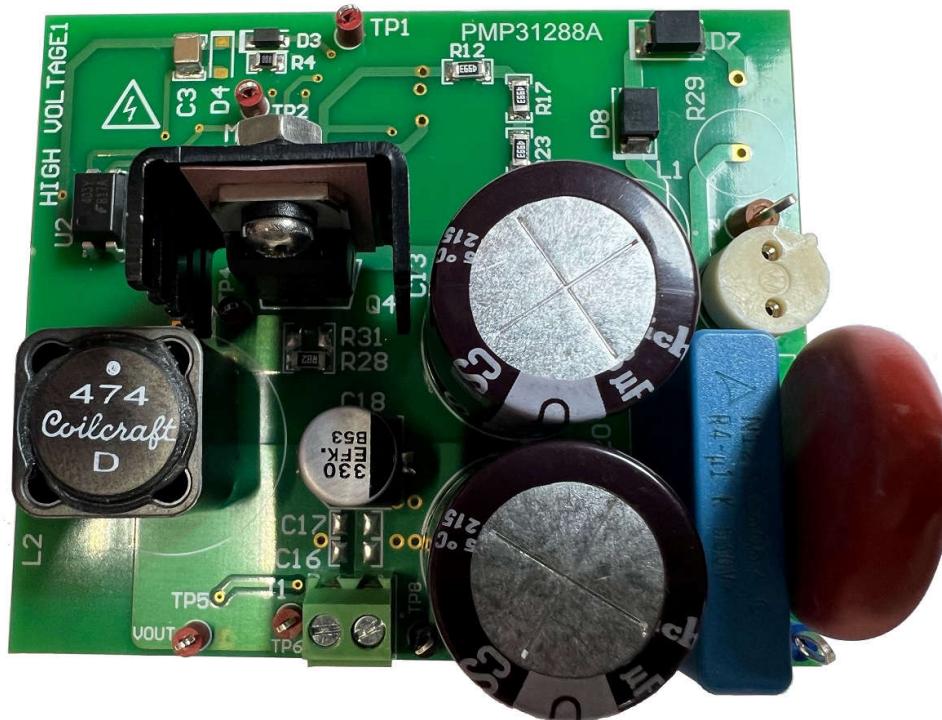- Electricity meter
- AC-input BLDC motor drive
- String inverter



Top of Board

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Parameter	Specifications
Input Voltage Range	80V _{DC} to 623V _{DC}
Output Voltage	13V
Maximum Output Current	0.6A

1.2 Overcurrent Protection

Input Voltage	Maximum Output Current
85V _{DC}	0.82A
325V _{DC}	1.2A
630V _{DC}	1.8A

1.3 Dimensions

The outline of the two-layer board is 73.7mm × 62.2mm.

2 Testing and Results

2.1 Efficiency Graphs

2.1.1 Efficiency vs Output Current

2.1.1.1 325V_{DC} Input Voltage

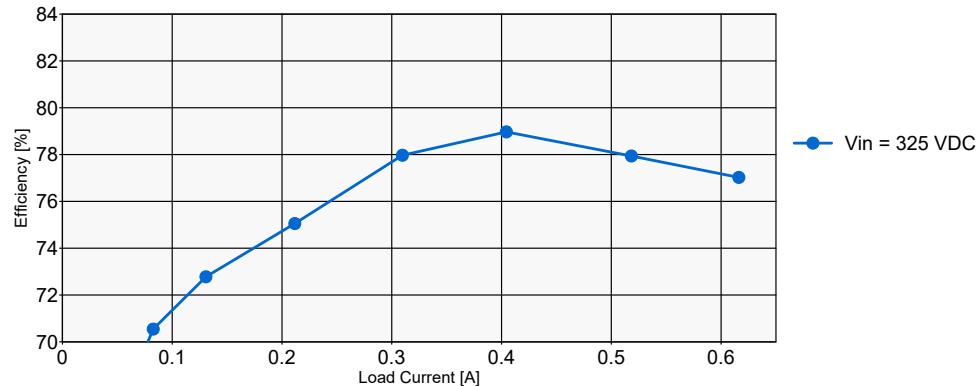


Figure 2-1. Efficiency vs Load Current at 325V_{DC} Input Voltage

2.1.1.2 240V_{AC} Input voltage

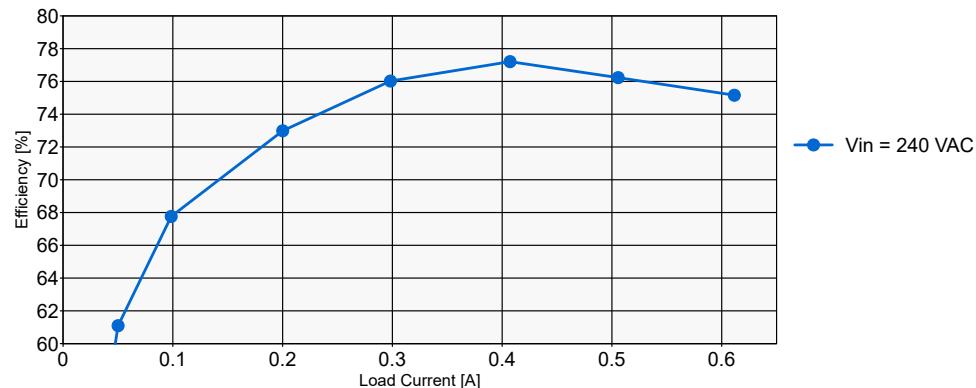


Figure 2-2. Efficiency vs Load Current at 240V_{AC} Input Voltage

2.1.2 Efficiency vs Input Voltage (DC)

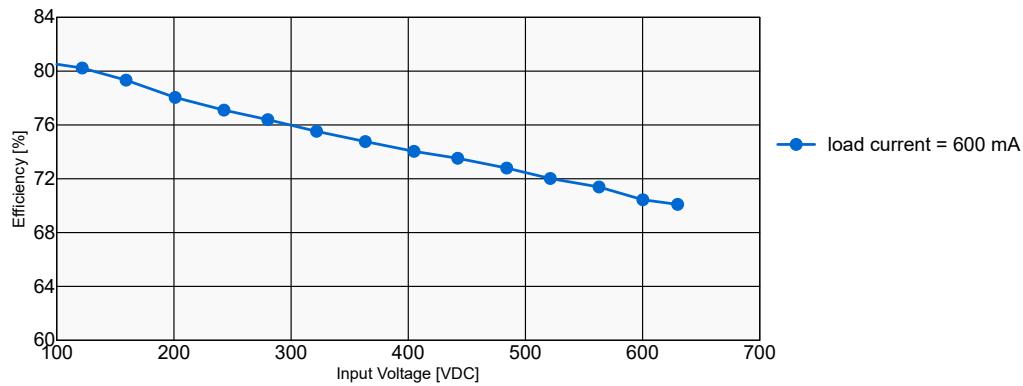


Figure 2-3. Efficiency vs Input Voltage (DC) at 600mA Output Current

2.2 Load Regulation

2.2.1 325V_{DC} Input Voltage

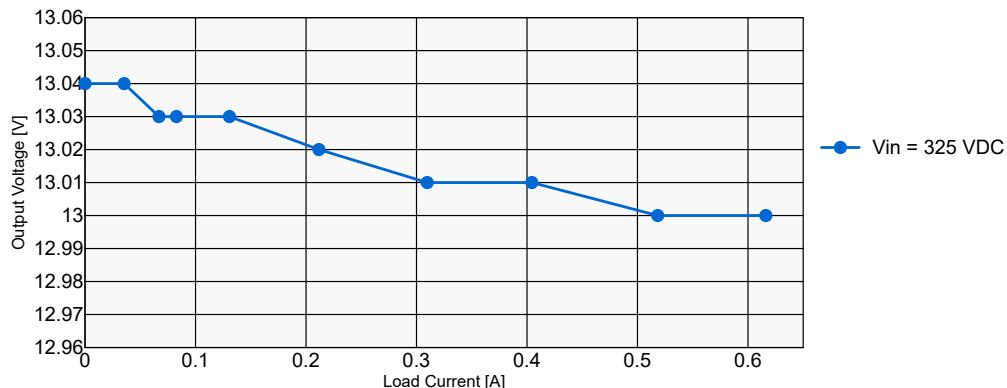


Figure 2-4. Output Voltage vs Load Current at 325V_{DC} Input Voltage

2.2.2 240V_{AC} Input Voltage

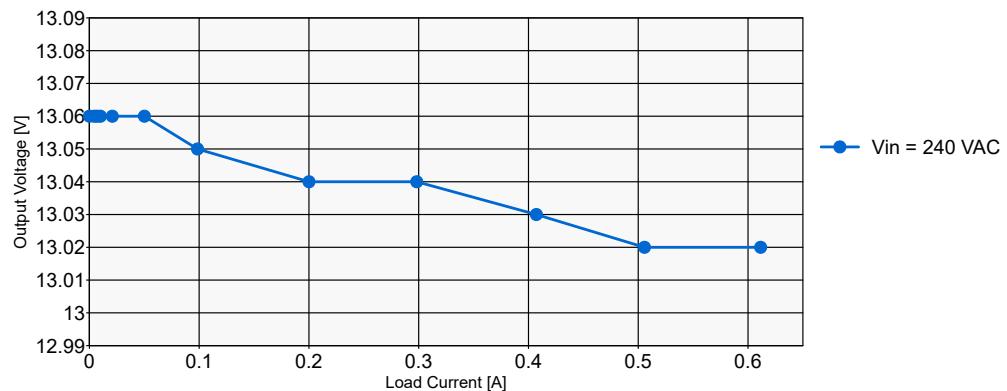


Figure 2-5. Output Voltage vs Load Current at 240V_{AC} Input Voltage

2.3 Line Regulation

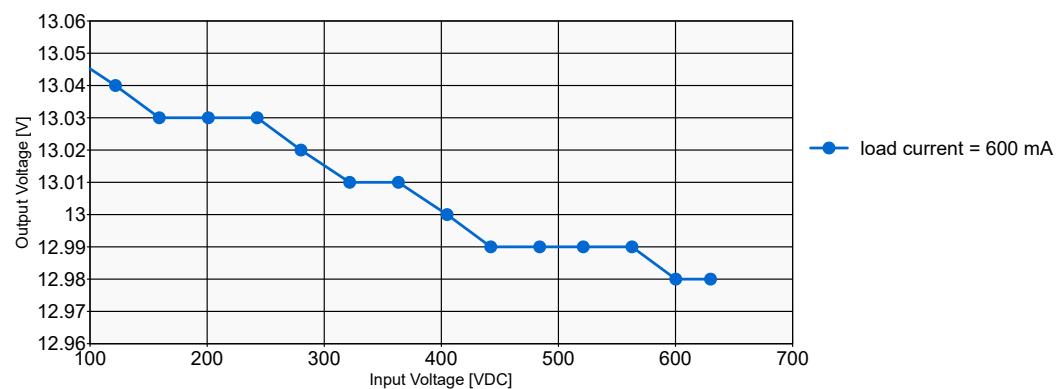


Figure 2-6. Output Voltage (DC) vs Input Voltage at 600mA Load Current

2.4 Thermal Images After 5 Minutes Operation

Input voltage was set to 230V_{AC} and load current was adjusted to 600mA.

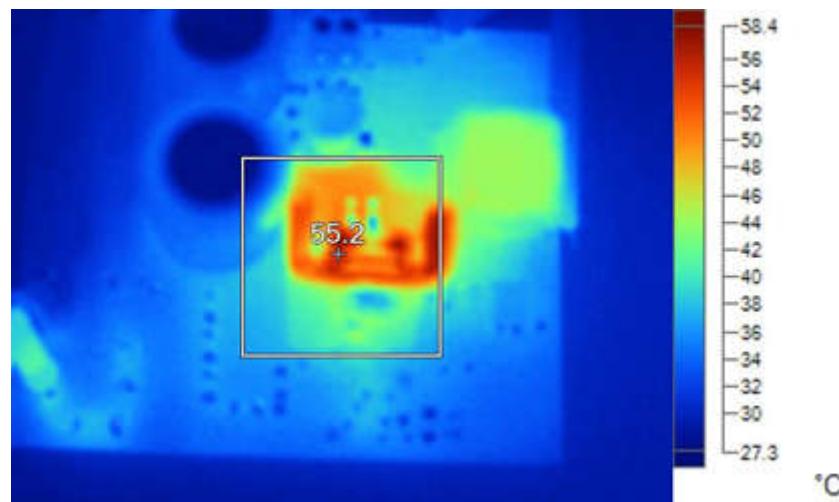


Figure 2-7. Top Side

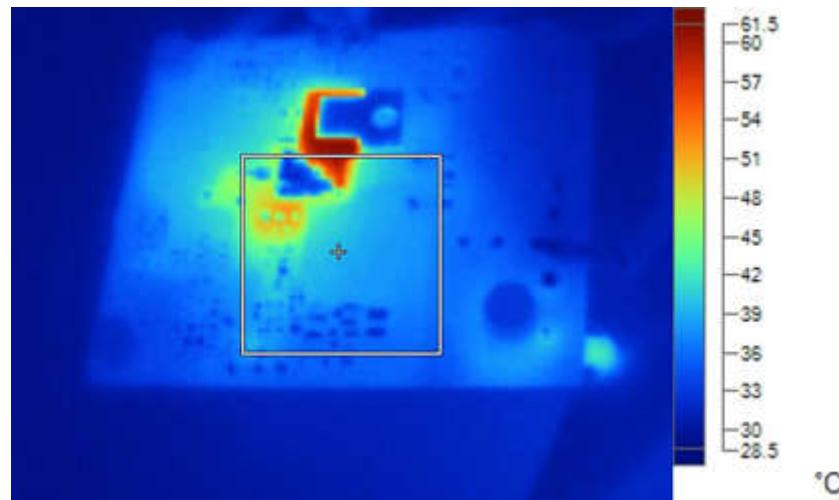


Figure 2-8. Bottom Side

2.5 Bode Plots

Bode plot is shown in the following figure.

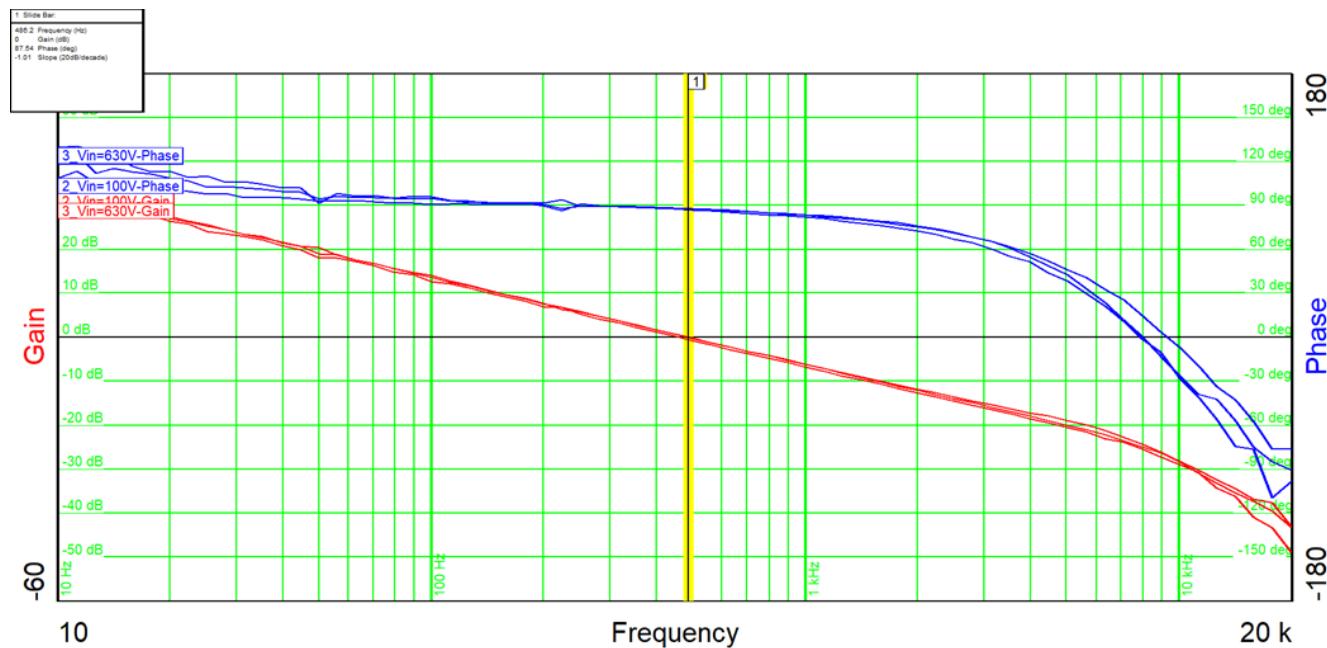


Figure 2-9. Bode Plot

Input voltage = 100V_{DC}

Load current = 0.6A

Phase margin = 87° (deg)

Gain margin > 15dB

Bandwidth = 0.48kHz

Input voltage = 325V_{DC}

Load current = 0.6A

Phase margin = 87° (deg)

Gain margin > 15dB

Bandwidth = 0.49kHz

Input voltage = 630V_{DC}

Load current = 0.6A

Phase margin = 87° (deg)

Gain margin > 15dB

Bandwidth = 0.46kHz

3 Waveforms

3.1 Switch Node Voltage

The load current was adjusted to 600mA.

The waveforms in [Figure 3-1](#) and [Figure 3-2](#) were done without applying an external magnetic field.

The waveforms in [Figure 3-3](#) and [Figure 3-4](#) were gathered by applying an external magnetic field with a distance of 2mm from the inductor of the circuit.

3.1.1.1 Without External Magnet Field

3.1.1.1.1 10 μ s / Division

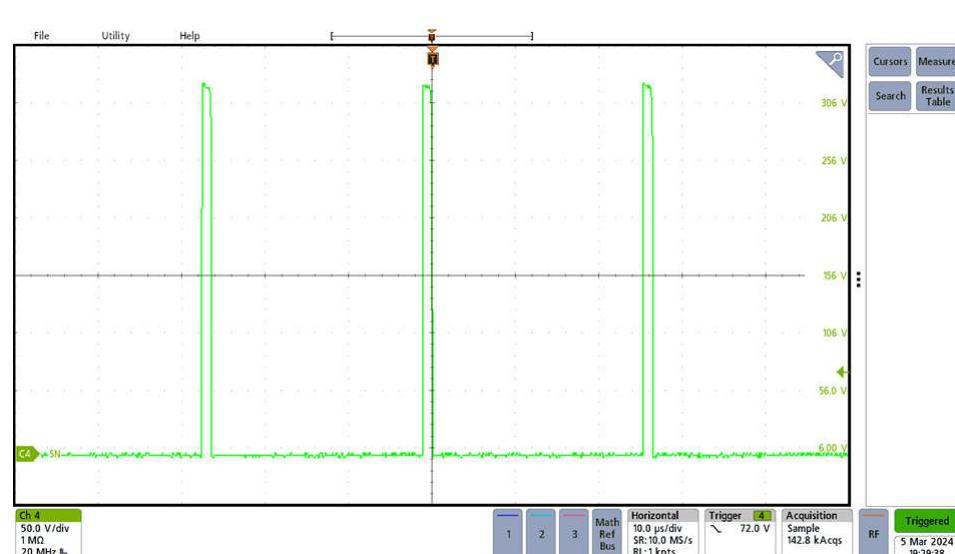


Figure 3-1. 600mA Load Current (10 μ s / div)

3.1.1.1.2 1 μ s / Division

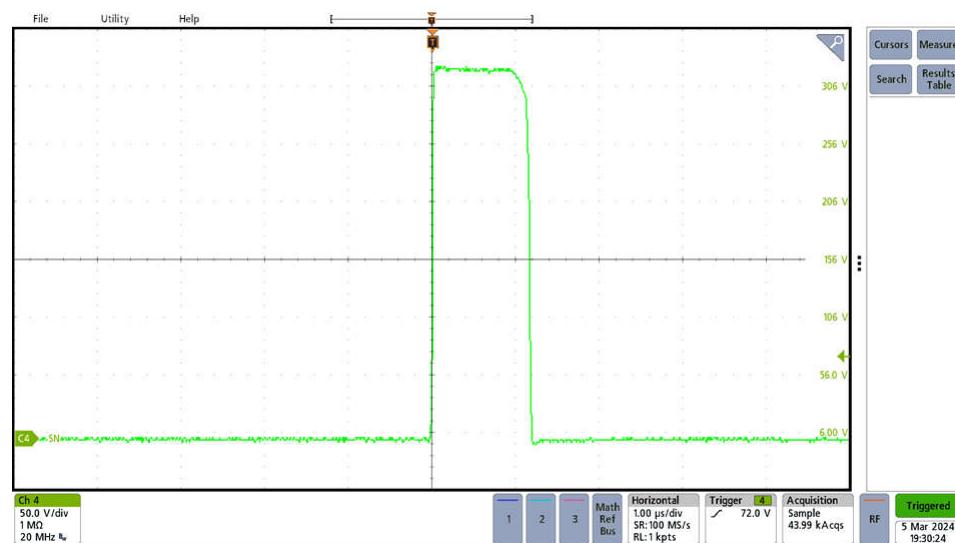


Figure 3-2. 600mA Output Current (1 μ s / div)

3.1.1.2 With an External Magnetic Field

3.1.1.2.1 10 μ s / div

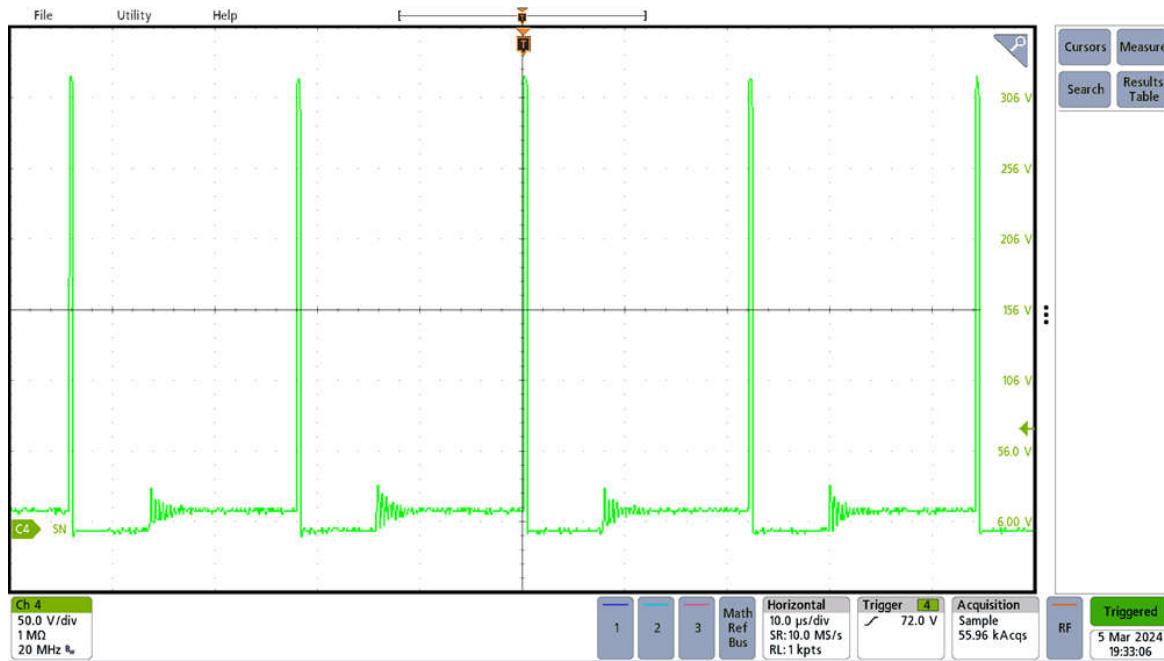


Figure 3-3. 600mA Load Current and External Magnetic Field (10 μ s / div)

3.1.1.2.2 1 μ s / Div

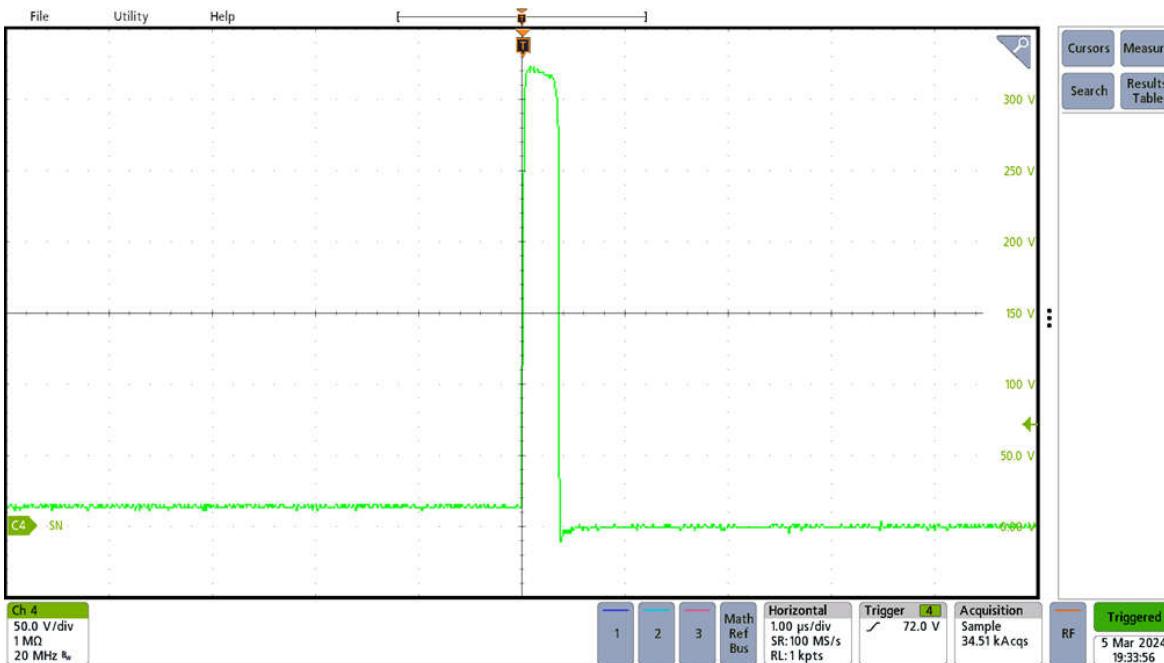


Figure 3-4. 600mA Load Current and External Magnetic Field (1 μ s / div)

3.1.2 630V_{DC} Input Voltage

3.1.2.1 200mA Load Current

3.1.2.1.1 40μs / Division

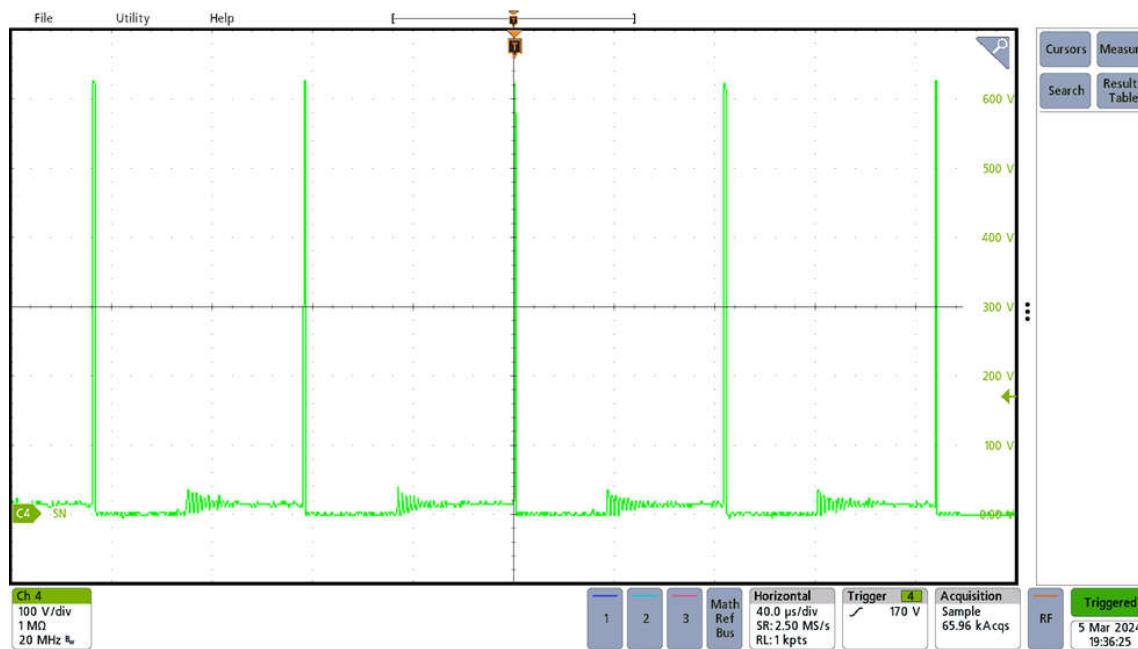


Figure 3-5. 200mA Load Current (40μs / div)

3.1.2.1.2 1μs / Division

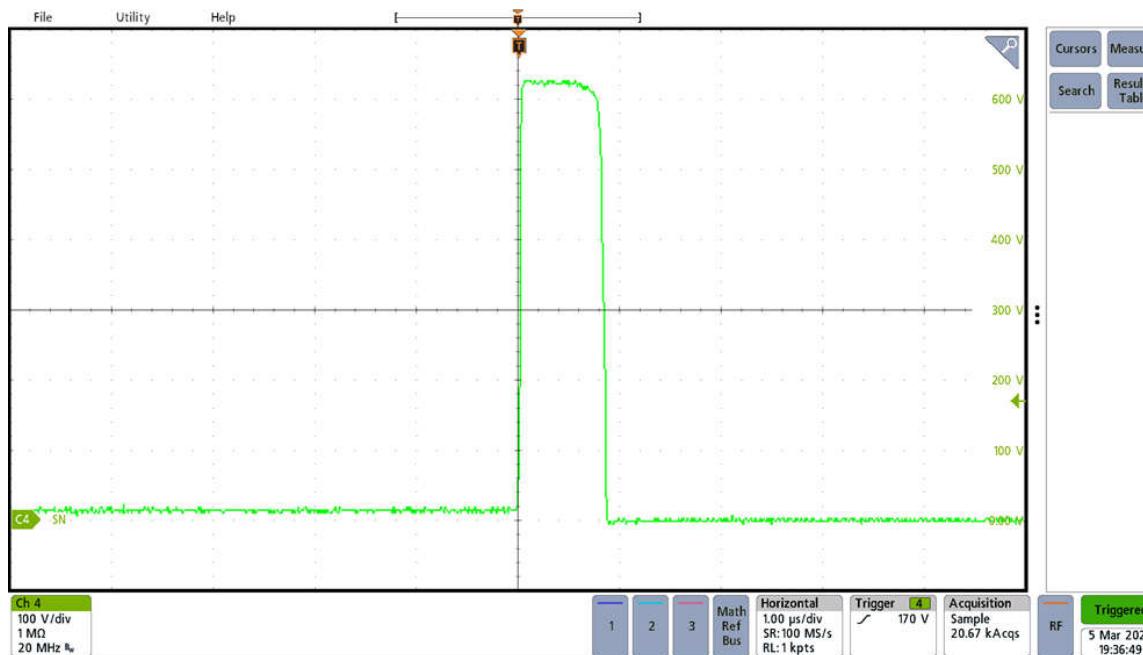


Figure 3-6. 200mA Load Current (1μs / div)

3.1.2.2 600mA Load Current

3.1.2.2.1 10 μ s / Division

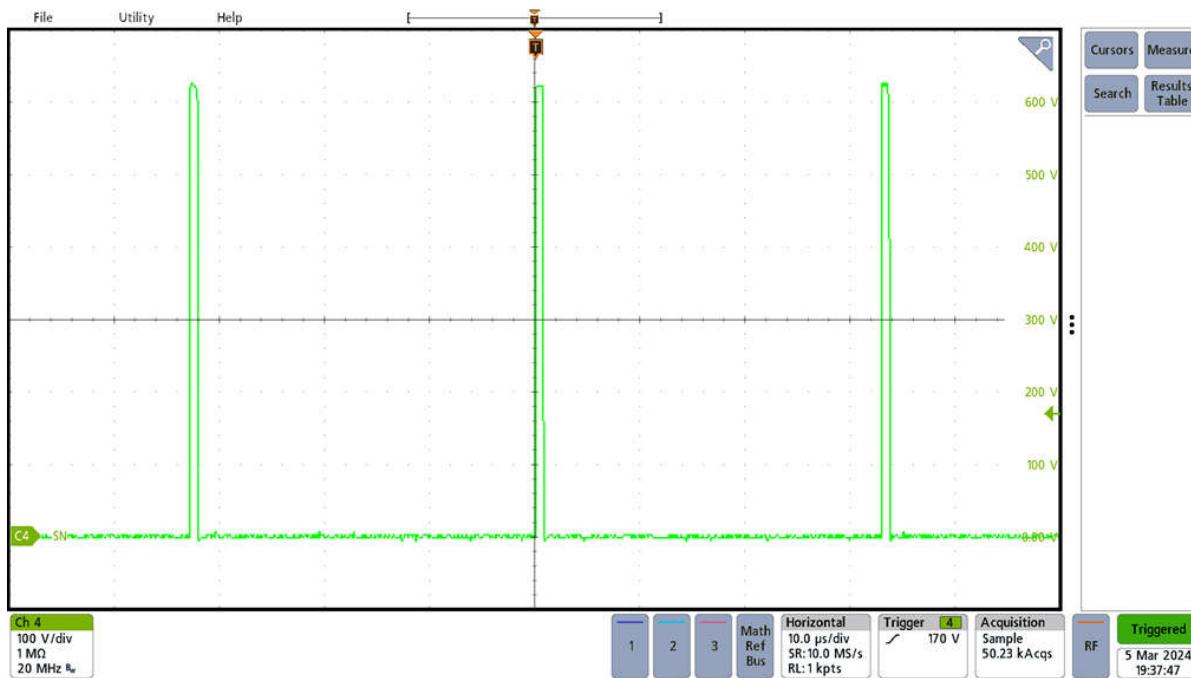


Figure 3-7. 600mA Load Current (10 μ s / div)

3.1.2.2.2 1 μ s / division

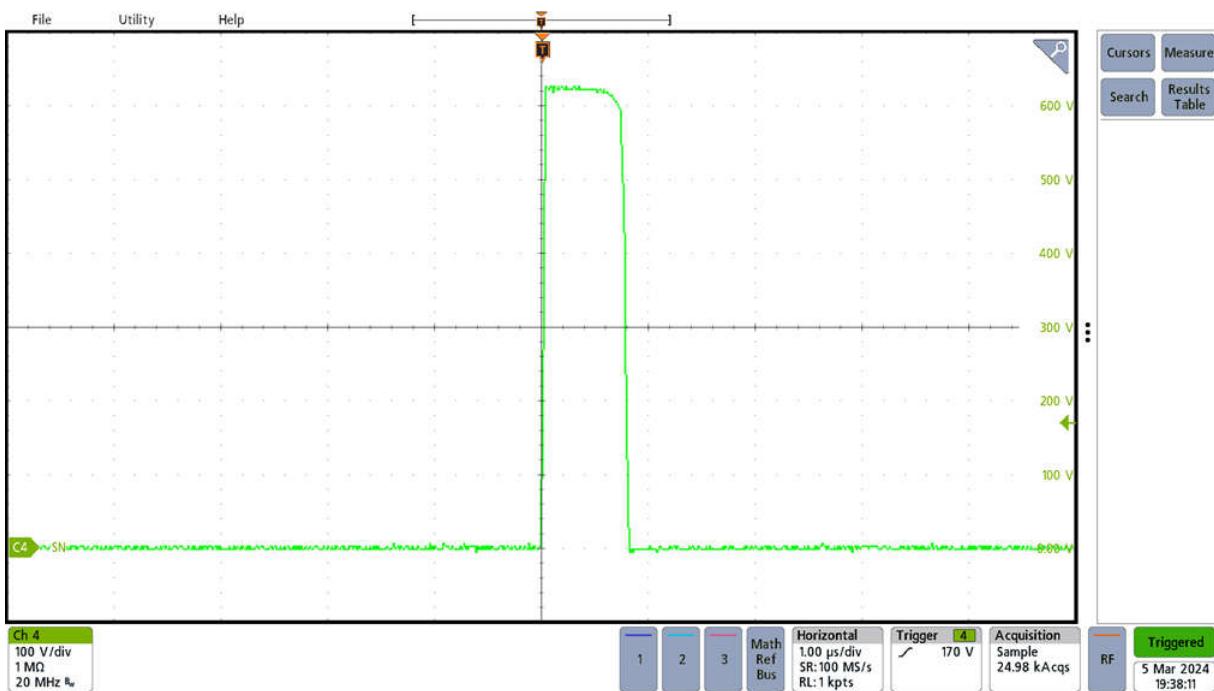


Figure 3-8. 600mA Load Current (1 μ s / div)

3.2 Output Voltage Ripple

3.2.1 325V_{DC} Input Voltage, Full Load

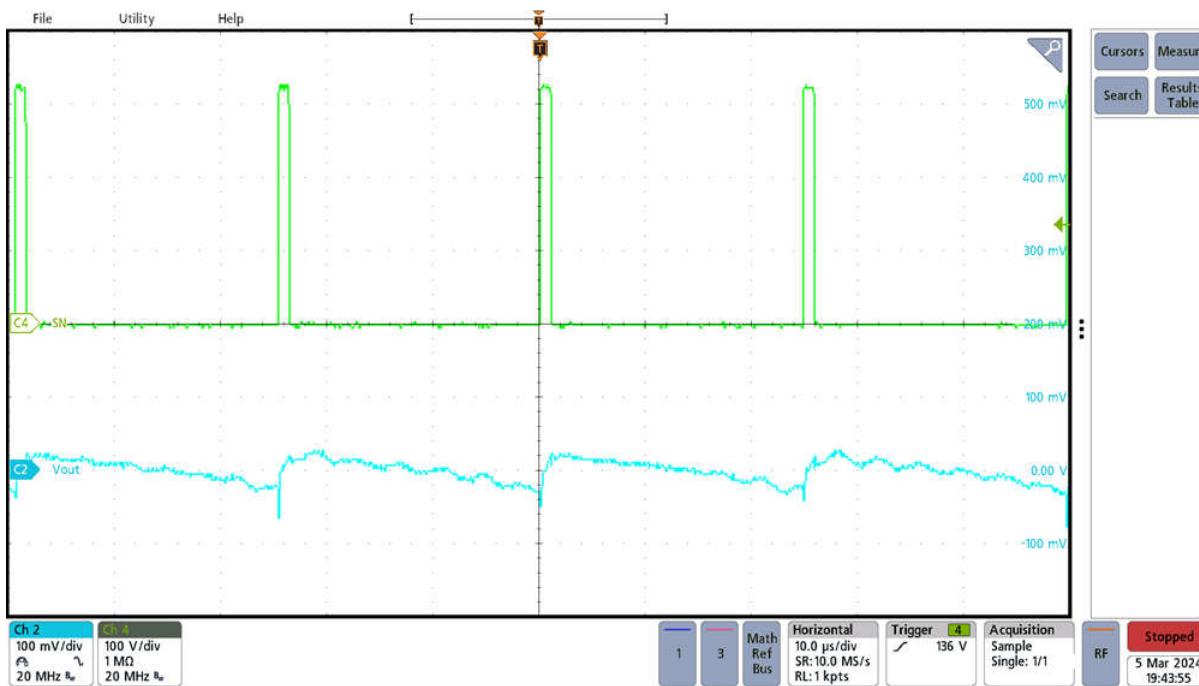


Figure 3-9. Output Voltage Ripple at 325V_{DC} Input Voltage

3.2.2 630V_{DC} Input Voltage, Full Load

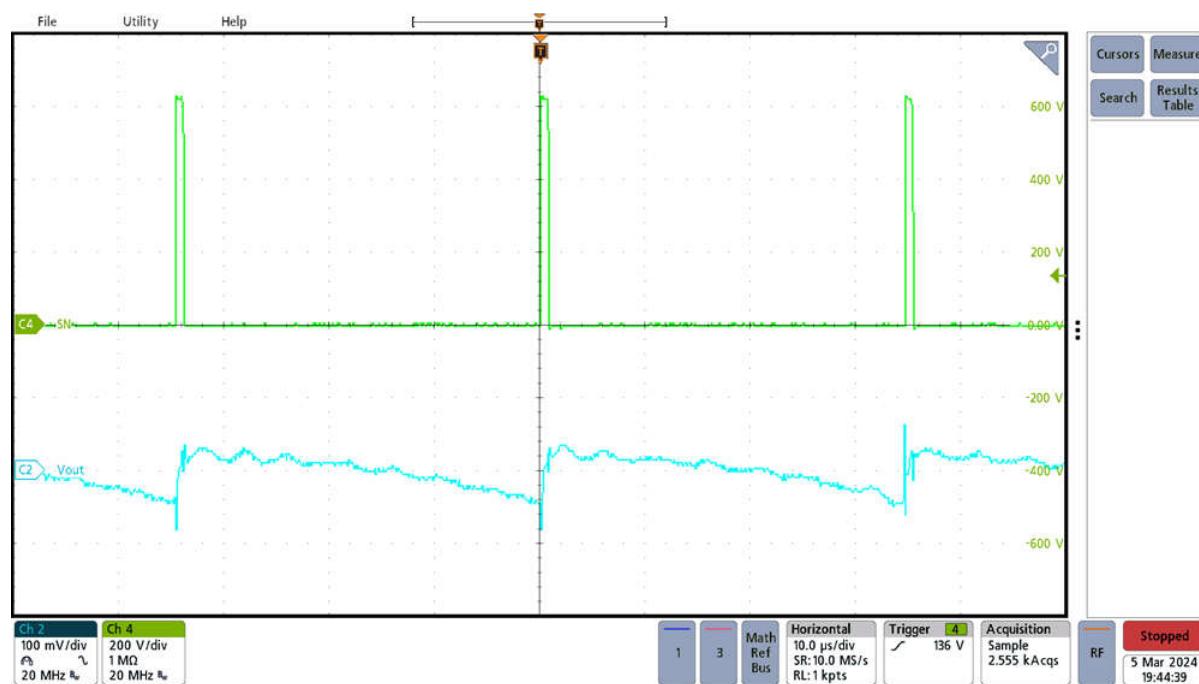


Figure 3-10. Output Voltage Ripple at 630V_{DC} Input Voltage

3.3 Input Voltage Ripple

3.3.1 80V_{AC} Input Voltage, 130mA Load Current

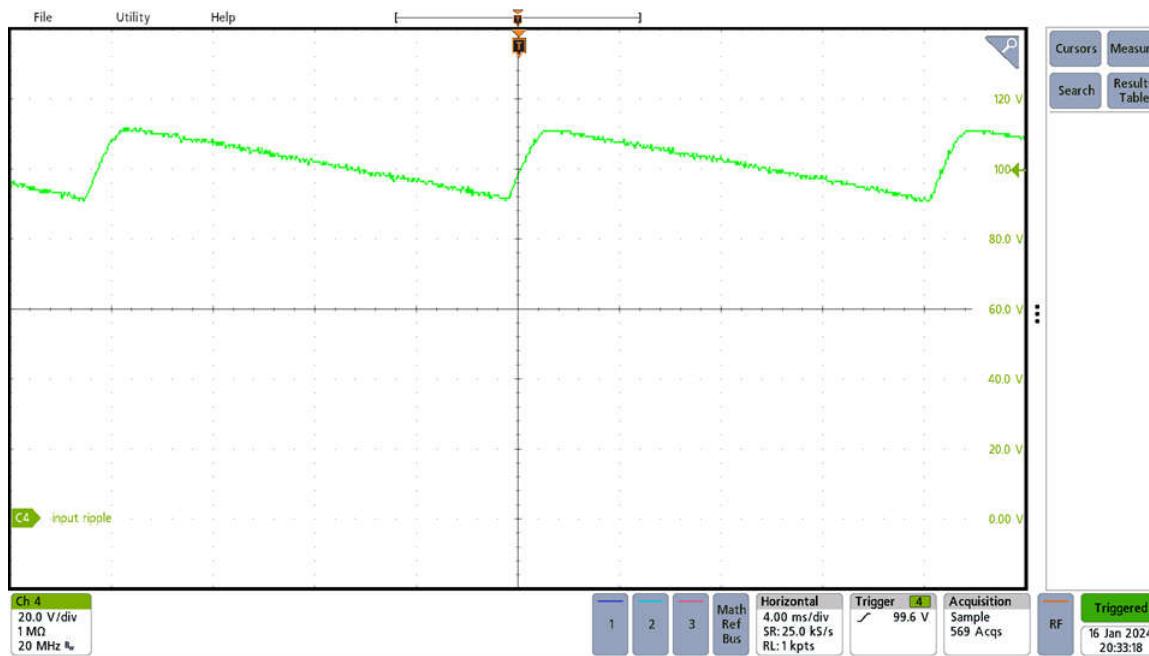


Figure 3-11. 80V_{AC} Input Voltage Ripple at 130mA Load Current

3.3.2 120V_{AC} Input Voltage, 600mA Load Current

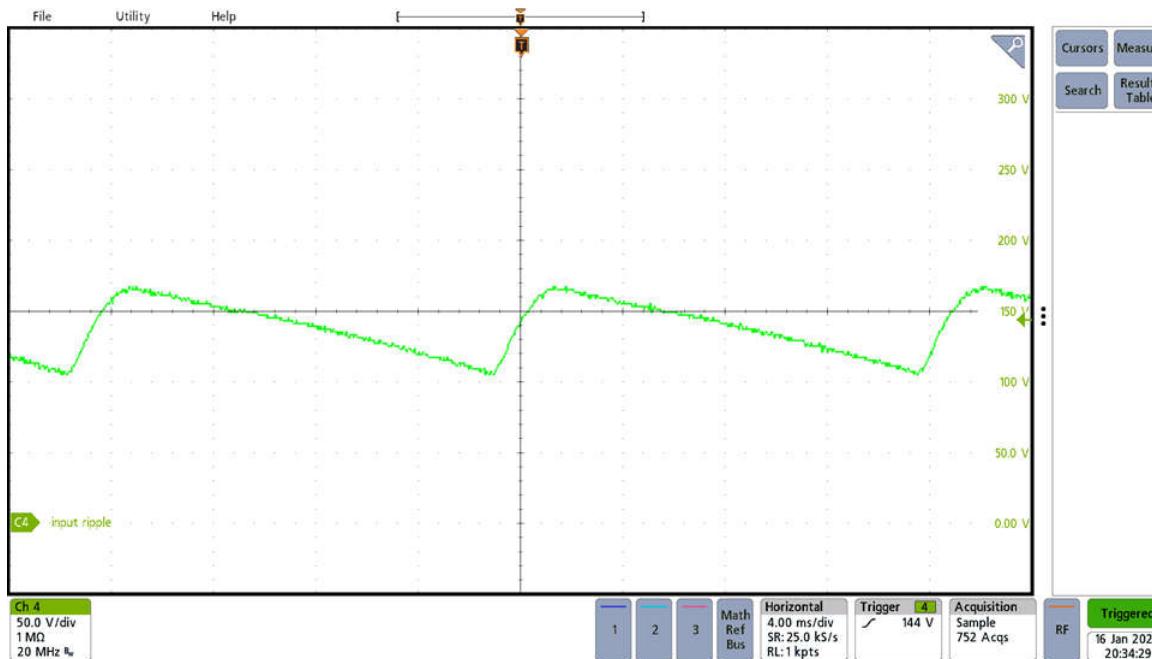


Figure 3-12. 120V_{AC} Input Voltage Ripple at 600mA Load Current

3.4 Load Transients

The electronic load switches between 100mA and 600mA.

3.4.1 110V_{DC} Input Voltage

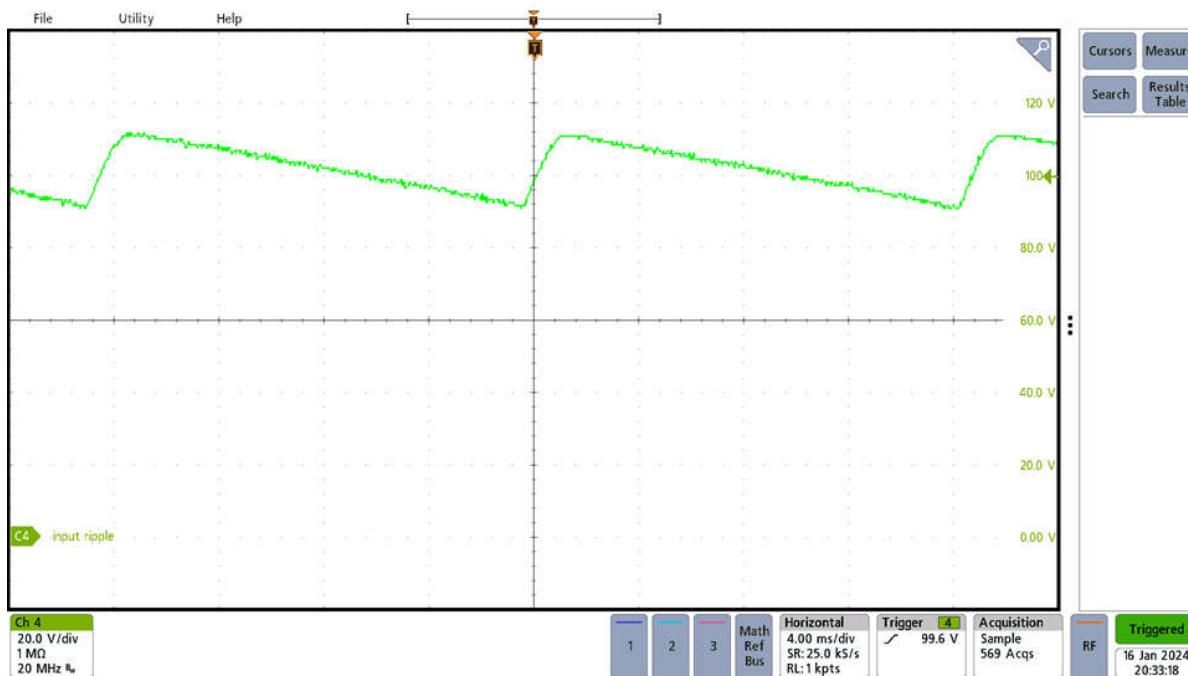


Figure 3-13. 100mA to 600mA Load Step at 110V_{DC} Input Voltage

3.4.2 325V_{DC} Input Voltage

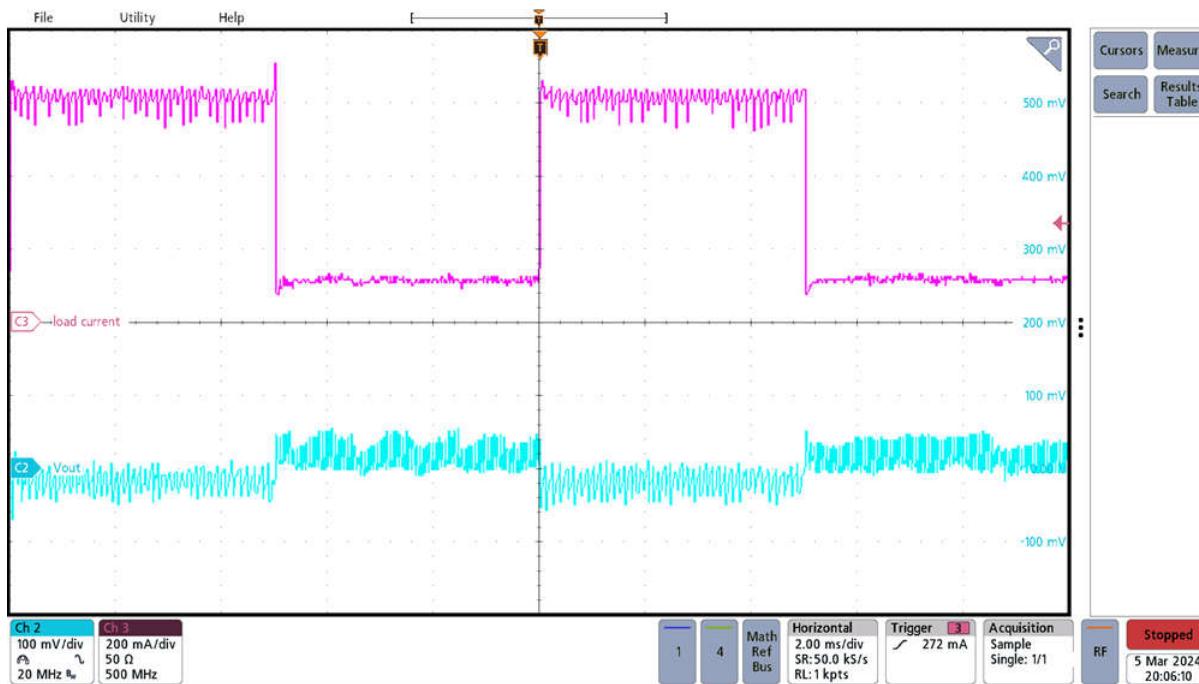


Figure 3-14. 100mA to 600mA Load Step at 325V_{DC} Input Voltage

3.4.3 630V_{DC} Input Voltage

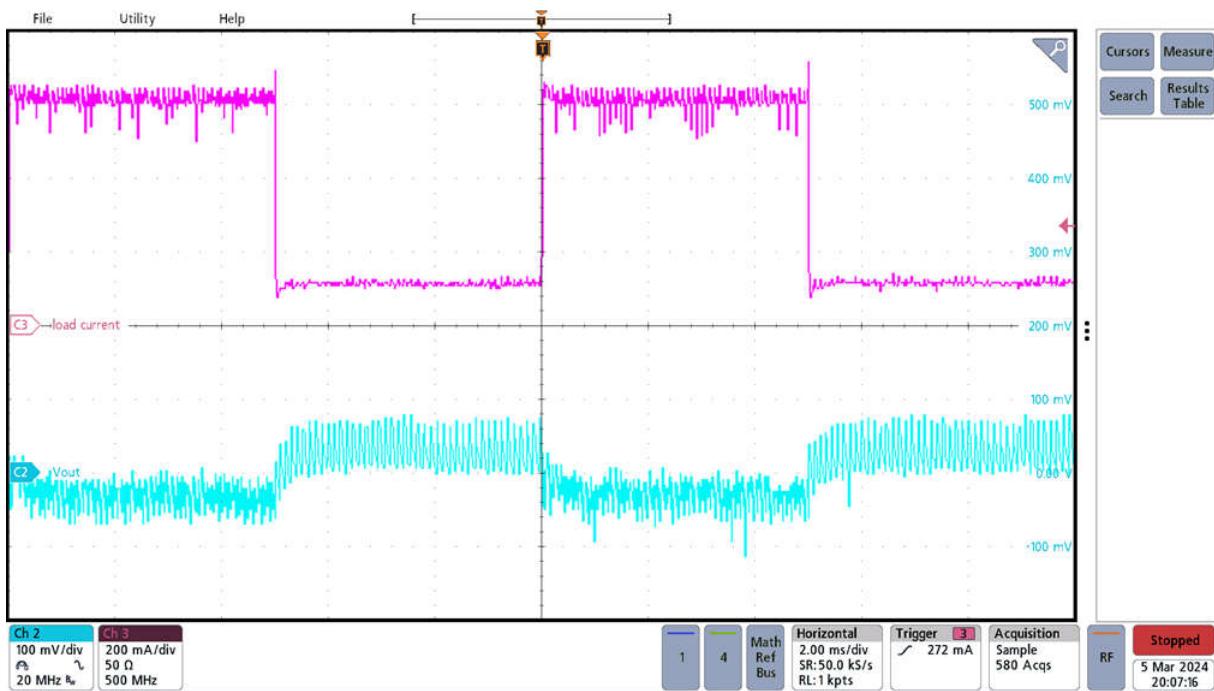


Figure 3-15. 100mA to 600mA Load Step at 630V_{DC} Input Voltage

3.5 Start-Up Sequence

3.5.1 80V_{DC} Input Voltage, 130mA Load Current

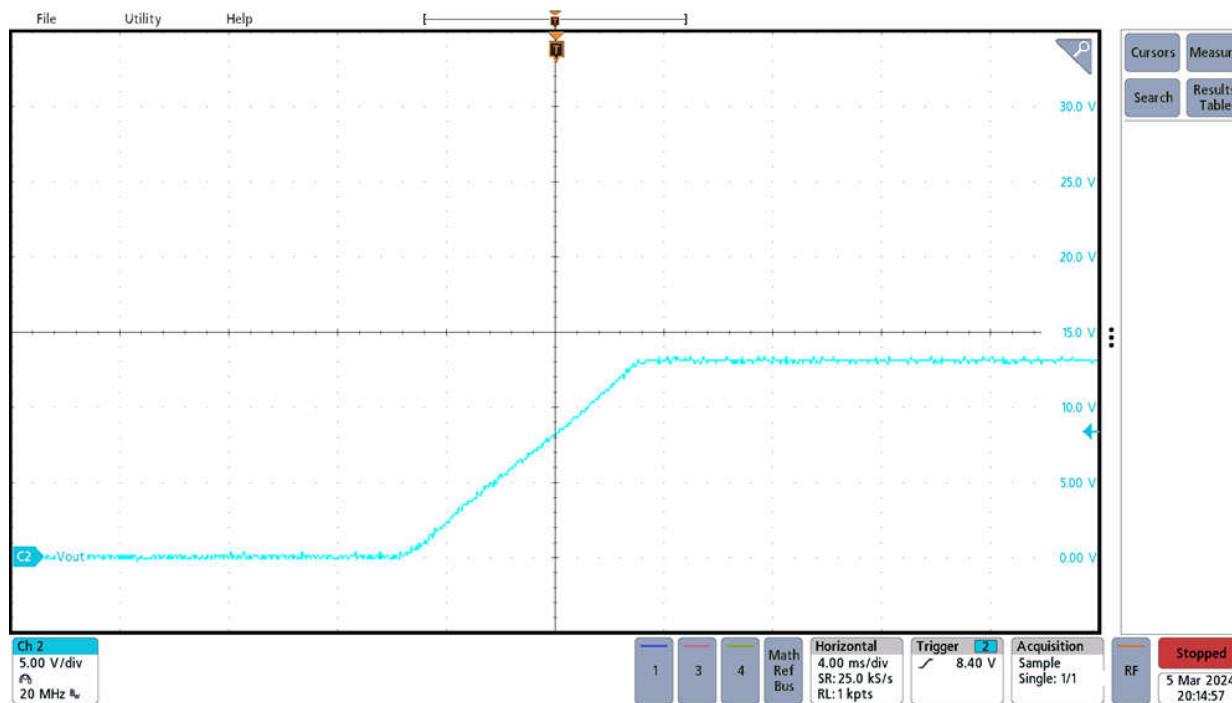


Figure 3-16. Start-Up at 80V_{DC} Input Voltage With 130mA Load Current

3.5.2 155V_{DC} Input Voltage, 600mA Load Current

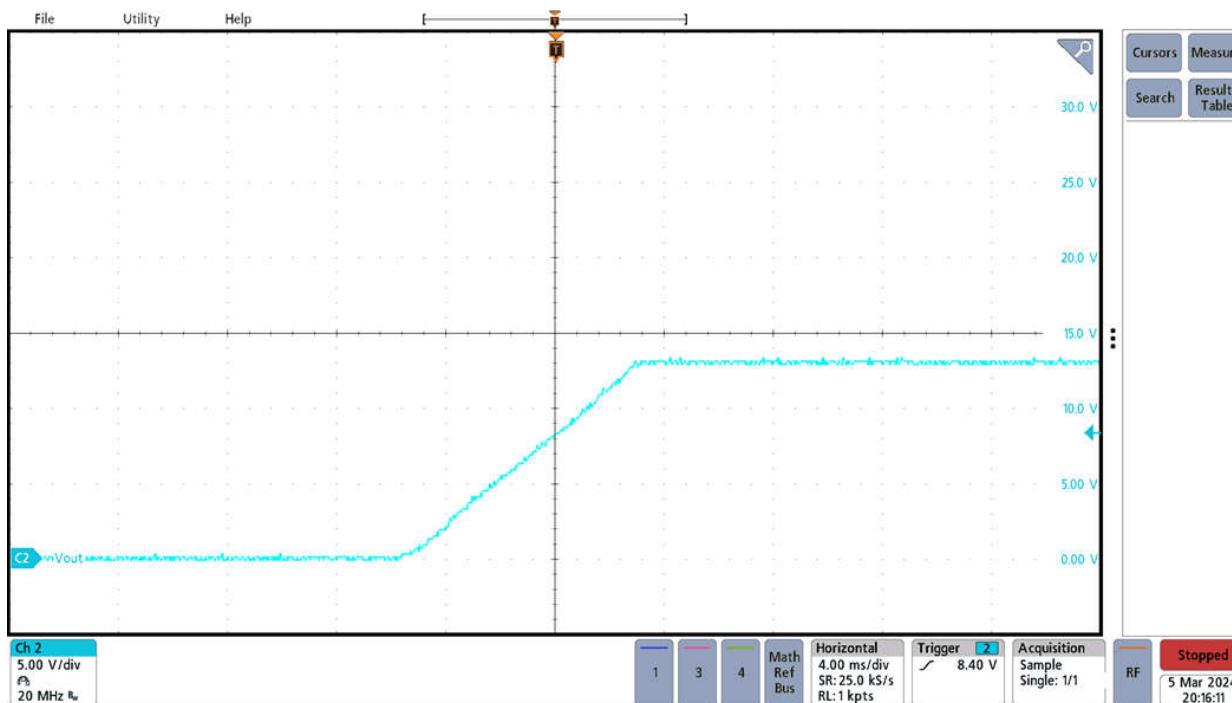


Figure 3-17. Start-Up at 155V_{DC} Input Voltage With 600mA Load Current

3.5.3 630V_{DC} Input Voltage, 600mA Load Current

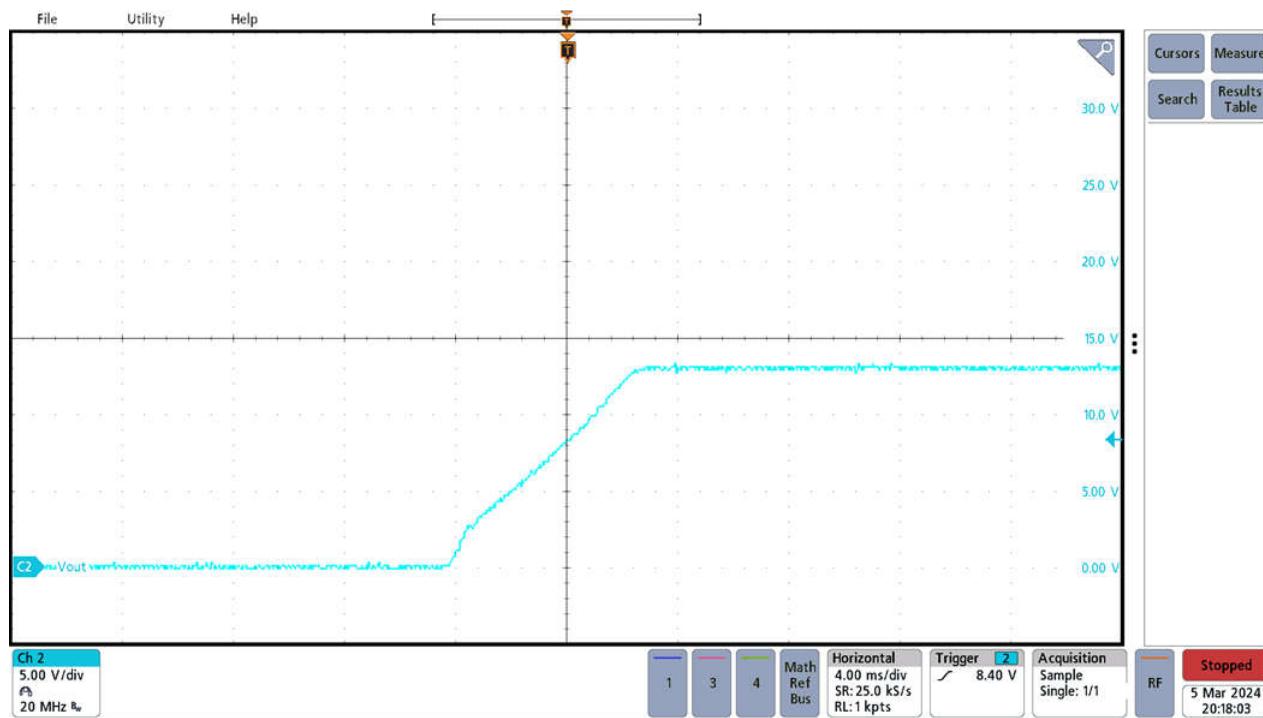


Figure 3-18. Start-Up at 630V_{DC} Input Voltage With 600mA Load Current

3.5.4 325V_{DC} Input Voltage, 600mA Load Current

3.5.4.1 No External Magnetic Field Applied

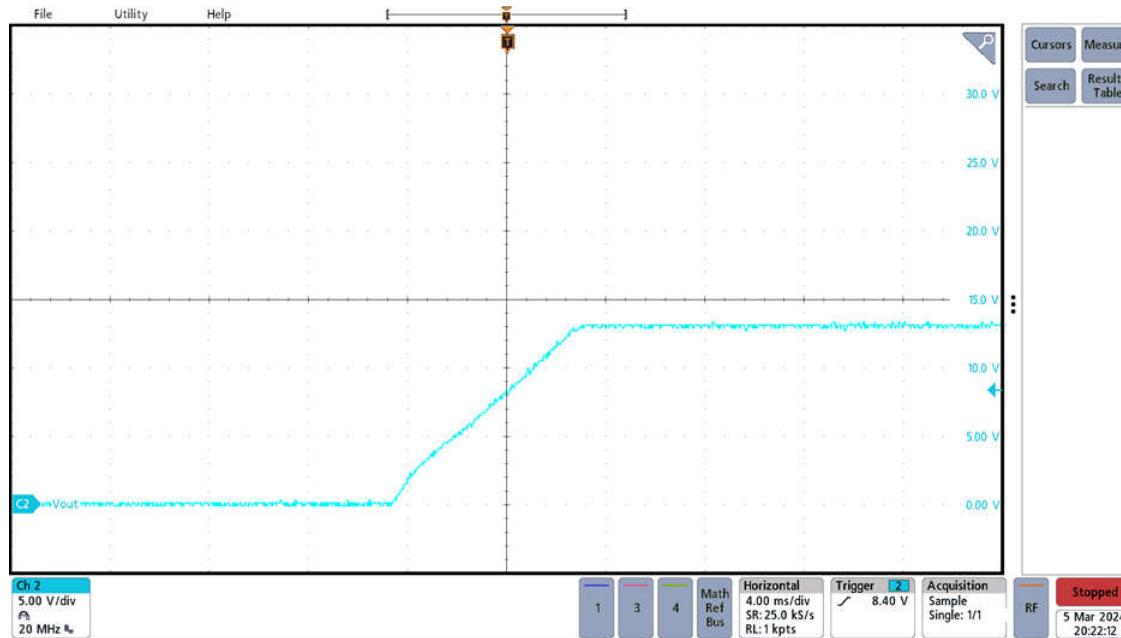


Figure 3-19. Start-Up With 625V_{DC} Input Voltage Without External Magnetic Field

3.5.4.2 With Magnetic Field Applied (2mm Distance Between Magnet and Inductor)

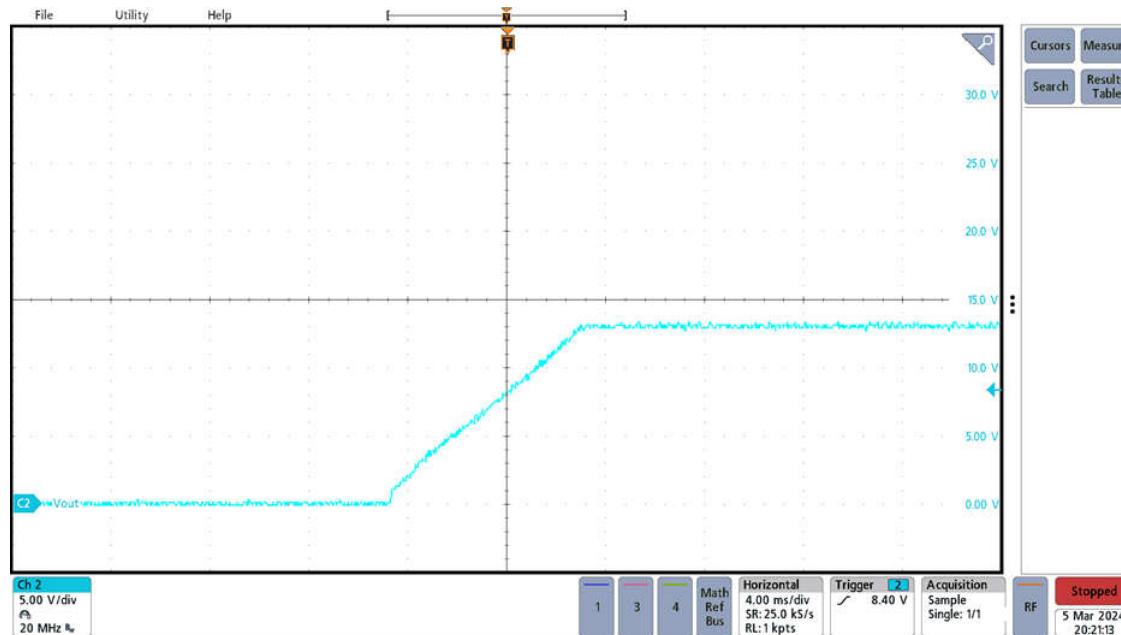


Figure 3-20. Start-Up With 625V_{DC} Input Voltage With External Magnetic Field

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated