
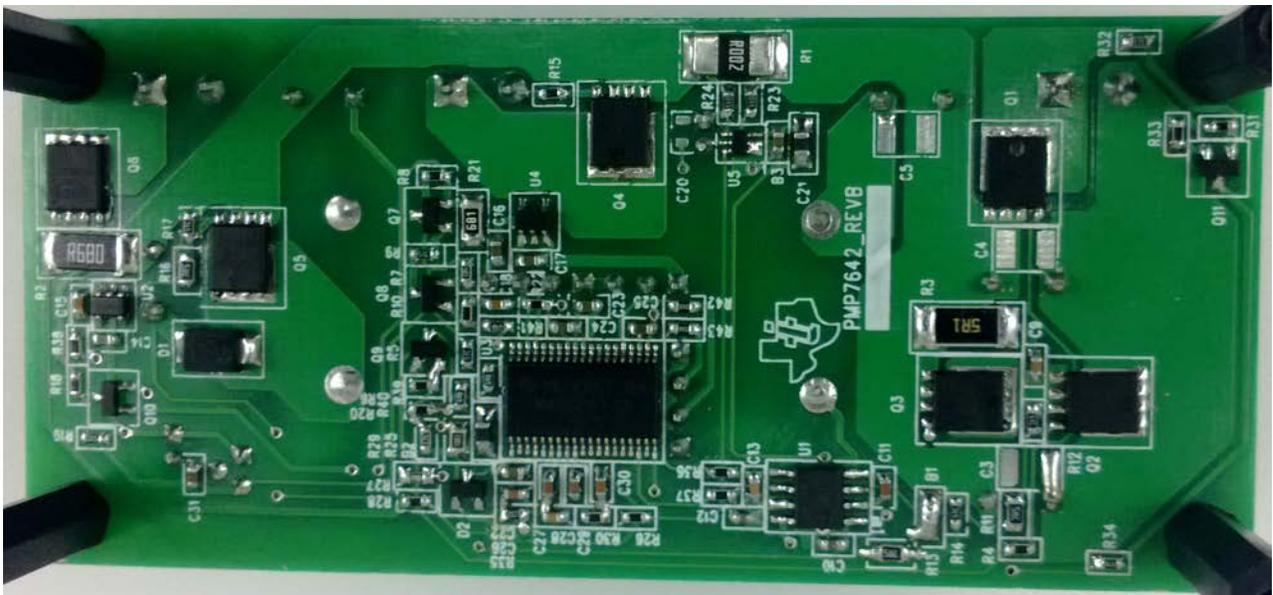


TEST REPORT OF MPPT & LED DRIVER

PMP 7647

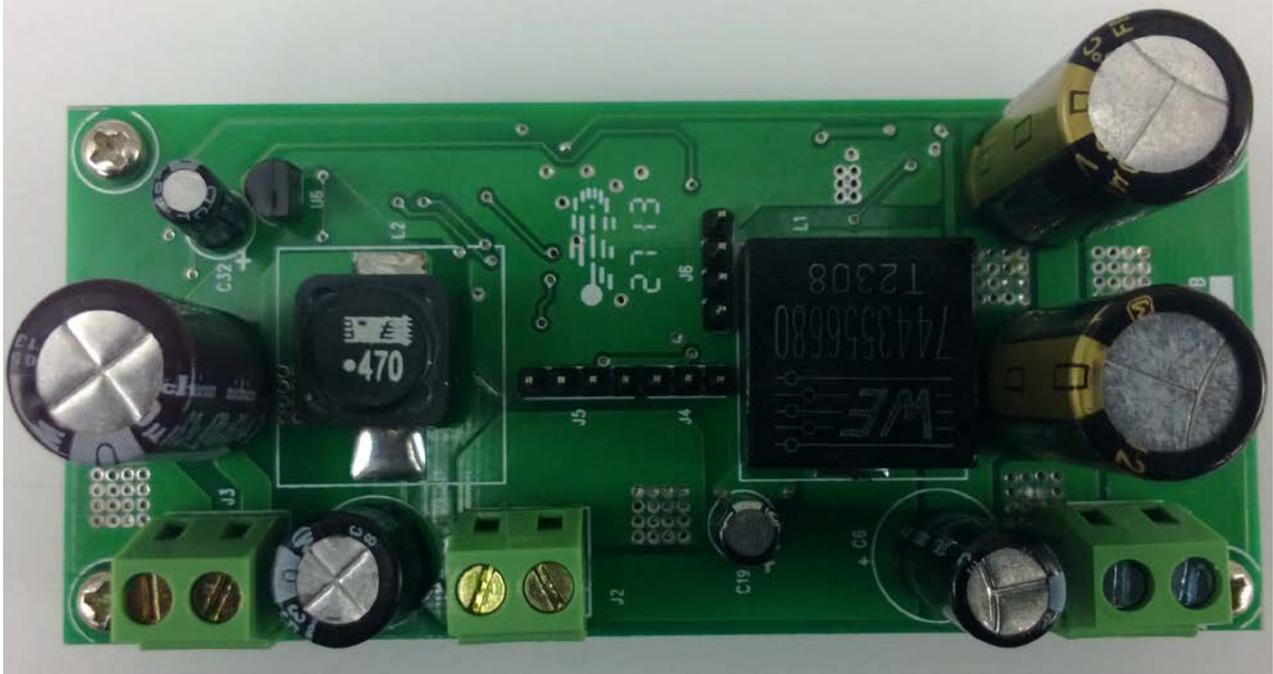

CONTENTS

Contents

| | | |
|-------|---------------------------------|----|
| I. | INTRODUCTION..... | 3 |
| II. | DESCRIPTION..... | 3 |
| III. | BLOCK DIAGRAM..... | 4 |
| IV. | SPECIFICATIONS..... | 5 |
| V. | BOARD LAYOUT..... | 5 |
| VI. | TEST SETUP..... | 6 |
| VII. | TEST DATA..... | 7 |
| a. | MPPT PERFORMANCE..... | 7 |
| b. | LED DRIVER PERFORMANCE..... | 7 |
| c. | MPPT EFFICIENCY PLOT..... | 7 |
| VIII. | WAVEFORMS..... | 8 |
| a. | Switching Node Waveforms..... | 8 |
| b. | Gate waveforms..... | 9 |
| IX. | POWER GAIN WITH MPP..... | 10 |
| a. | Test Set-up..... | 10 |
| b. | Test Results..... | 10 |
| X. | SCHEMATIC..... | 11 |
| a. | Power Stage..... | 11 |
| b. | Controller and Bias Supply..... | 12 |
| XI. | BILL OF MATERIALS..... | 13 |
| XII. | CONCLUSION..... | 13 |
| XIII. | APPENDIX..... | 14 |

I. INTRODUCTION

The following document is a compilation of test results of the PMP7647 reference design, a 12A MPPT solar charge controller & 700mA LED driver. The test results are taken with simulated solar panel input corresponding to 12V panel.

II. DESCRIPTION

The PMP7647 is developed around the MSP430F5132 controller IC. The design is targeted for low power solar charger and LED driver solutions such as solar street lights. This design is capable of charging 12V batteries with up to 10A output current from 12V panels. However, it can be easily adapted to 24V systems by just changing the MOSFETs to 60V rated parts. Also, the design can drive up to 15 LEDs in series with 700mA of current. It is possible to adapt the design for LED currents up to 1.1A with minimum change in hardware.

The MPPT section has a typical electrical efficiency of 97% at full load. This efficiency figure includes the losses in battery reverse protection and panel reverse flow protection MOSFETs, which are part of the design. The high efficiency is the result of the low gate charge MOSFETs from TI used in the design, and also the optimum layout. Another feature is the relatively small sized components used, possible due to the high operating frequency (settable from 100 - 200 KHz). The design has built-in battery charge profile for 12V Lead acid batteries. The design presently uses 'perturb and observe' algorithm for MPP tracking. This gives fast acquisition of MPP operation.


The LED driver section is a boost converter. The electrical efficiency of boost section is about 93% while driving 12 LEDs at 700mA, and is around 91% while driving 6 LEDs at 350mA. The section is protected with load and converter cut-off during overload, short circuit and load open fault situations. There is also provision to dim the output after specified time intervals. Though in a typical application the time intervals are in hours, the board is programmed for one minute intervals of 700mA and 350mA current drive for easy demonstration of the feature. The design is also capable of detection of ambient light based on the panel voltage, and taking appropriate decisions to turn on LEDs, charge battery in MPPT mode or go to standby accordingly. Low battery voltage protection by dimming the LEDs to 10% brightness and subsequently going to low power mode with further reduction in voltage is also implemented. The voltage levels at which these actions are taken can be set by software.

The various parameters of the circuit like battery charge current, load current, load timing pattern, battery under voltage set points etc can be set using a GUI made for the design. This makes customization a lot easier.

The circuit takes only under 4mA of standby current while operating from battery. This is further reduced to under 1mA while the circuit is in battery under voltage cut-off. Software programmable indications are provided in hardware, but are left non-configured.

Surge protection and EMI filtering components are not present on this design, and has to be added depending upon required specification levels.

III. BLOCK DIAGRAM

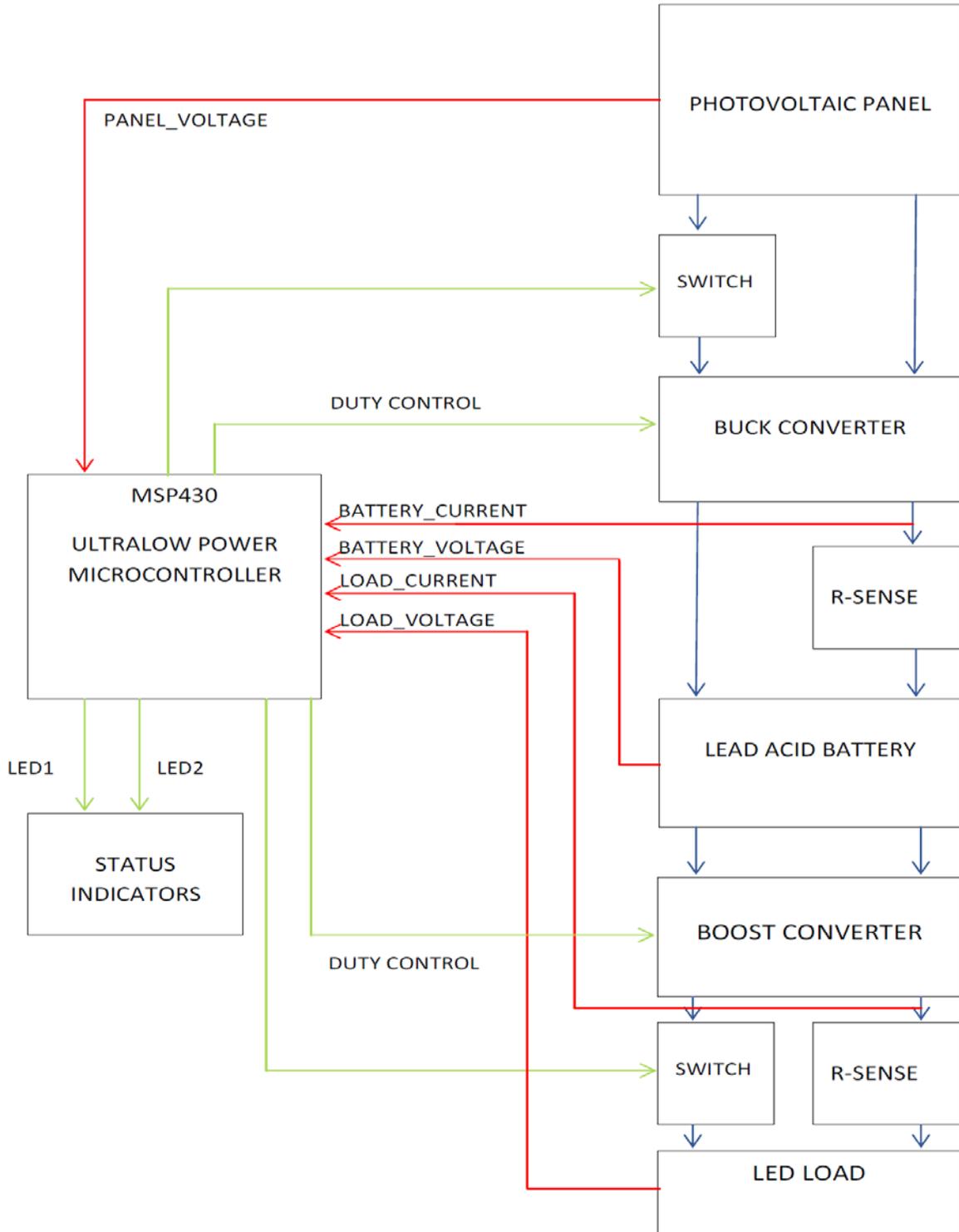

IV. SPECIFICATIONS

Input Voltage Range: 15VDC - 22VDC

Storage: 12V battery



Charging Current: 10A, with current limit set at 12A

Output: 12 LEDs at 700mA

Board Form Factor: 100 mm x 45 mm x 32 mm

Expected efficiency: >95% for MPPT charger, and >90% for LED driver

V. BOARD LAYOUT

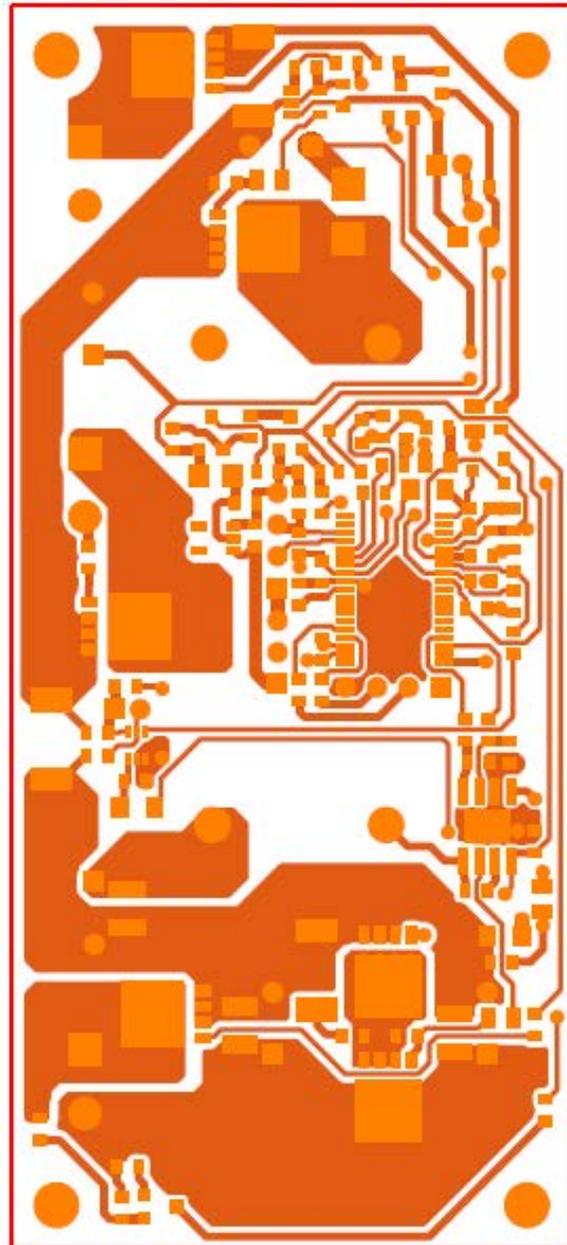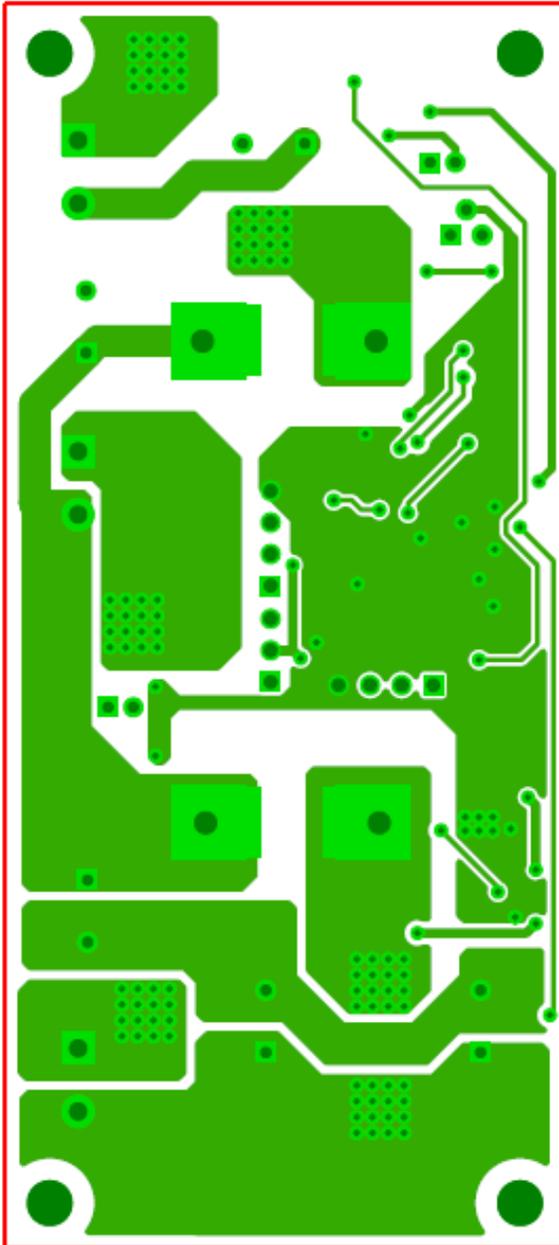

VI. TEST SETUP

Input conditions:

Panel input: 15VDC to 22VDC

Set current limit to the short circuit current of panel when DC source is used instead of panel

Storage:

12V battery

Output:

12 LED array


Equipment Used:

1. Current limited DC source simulating solar panel
2. Digital Oscilloscope
3. Multimeters
4. LED load/LED simulator

Procedure:

1. Connect appropriate battery to the battery terminals of the PMP7647 reference board, maintaining correct polarity.
2. Connect panel or current limited DC source to panel terminals, maintaining correct polarity.
3. Set the output voltage of DC source to slightly above the MPP voltage of the panel being simulated (if DC source is used instead of panel) and turn on.
4. Observe for gradual build-up of battery charge current.
5. Connect LED array to the load terminals with proper polarity.
6. Turn off the panel input to observe gradual build-up of LED current.

Connection Diagram:

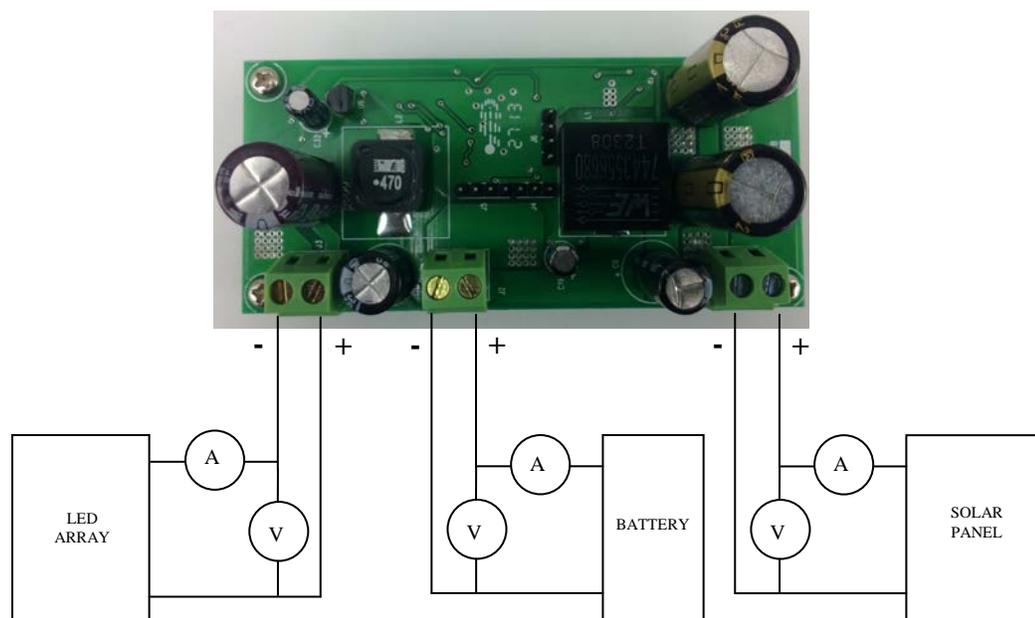

VII. TEST DATA


a. MPPT PERFORMANCE

| Vi (V) | Ii (A) | Vo (V) | Io (A) | Pi (W) | Po (W) | Efficiency |
|--------|--------|--------|--------|--------|--------|------------|
| 17.04 | 0.44 | 13.04 | 0.50 | 7.43 | 6.56 | 88.29 |
| 17.38 | 0.81 | 13.11 | 1.01 | 14.13 | 13.18 | 93.25 |
| 17.18 | 2.01 | 13.33 | 2.50 | 34.53 | 33.33 | 96.51 |
| 16.87 | 4.17 | 13.68 | 5.00 | 70.28 | 68.41 | 97.34 |
| 17.01 | 6.35 | 14.03 | 7.50 | 108.00 | 105.23 | 97.43 |
| 16.62 | 8.93 | 14.39 | 10.02 | 148.42 | 144.19 | 97.15 |

b. LED DRIVER PERFORMANCE

| Vi (V) | Ii (A) | Vo (V) | Io (A) | Pi (W) | Po (W) | Efficiency |
|--------|--------|--------|--------|--------|--------|------------|
| 11.23 | 2.775 | 41.23 | 0.702 | 31.16 | 28.94 | 92.88 |
| 12.15 | 0.708 | 21.55 | 0.365 | 8.60 | 7.87 | 91.44 |


c. MPPT EFFICIENCY PLOT

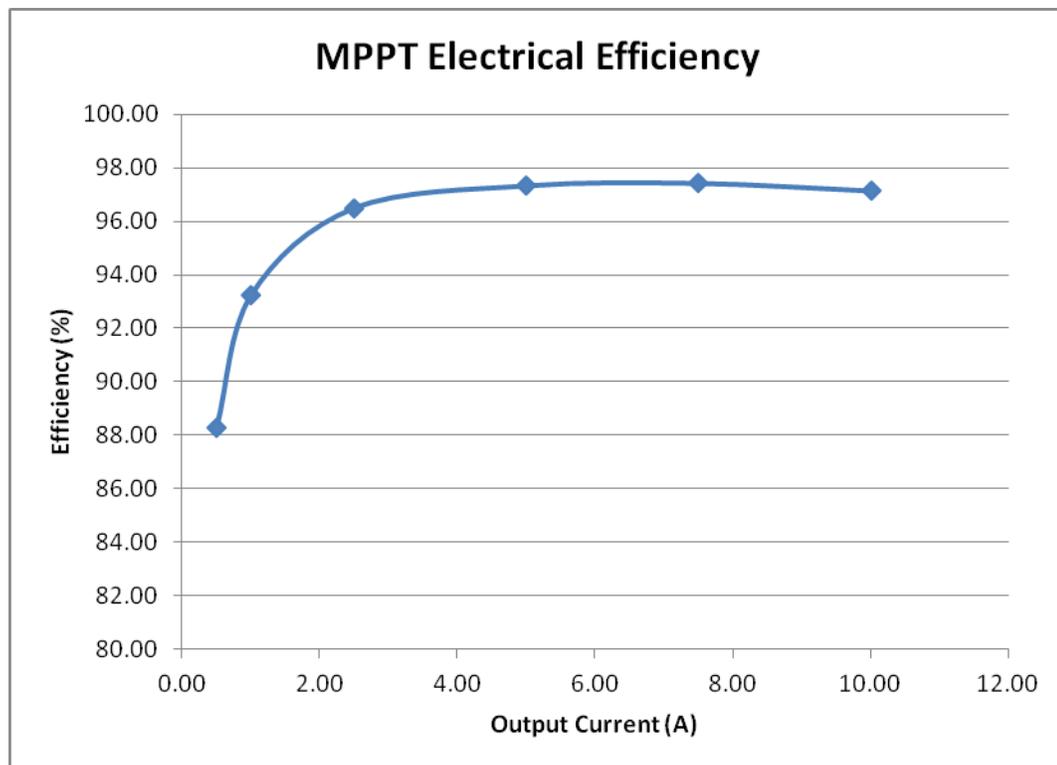


VIII. WAVEFORMS

a. Switching Node Waveforms

MPPT switch node at 10A charging current

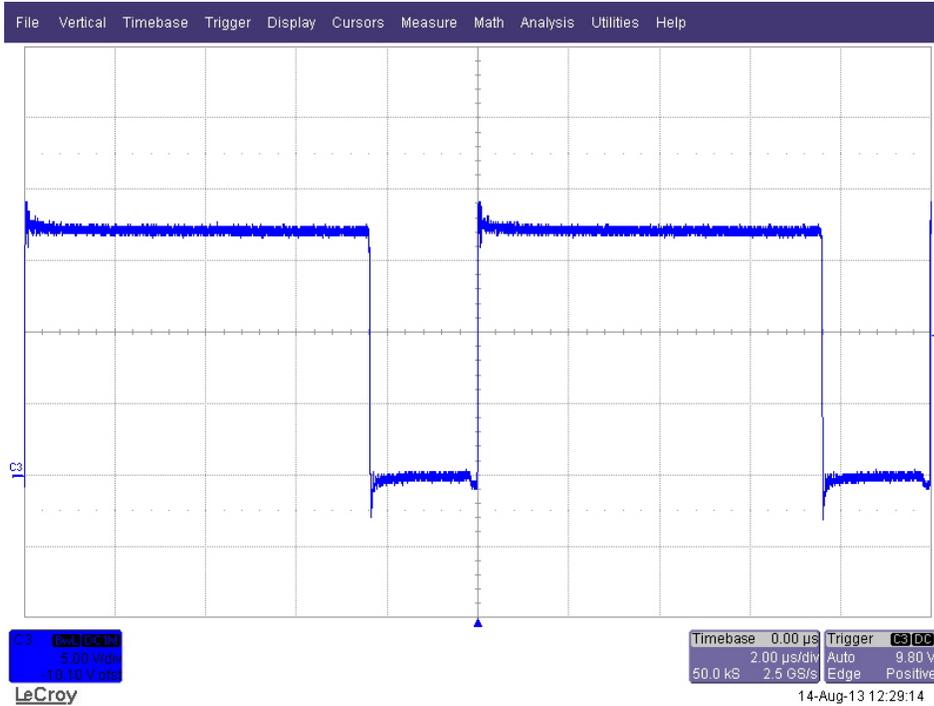


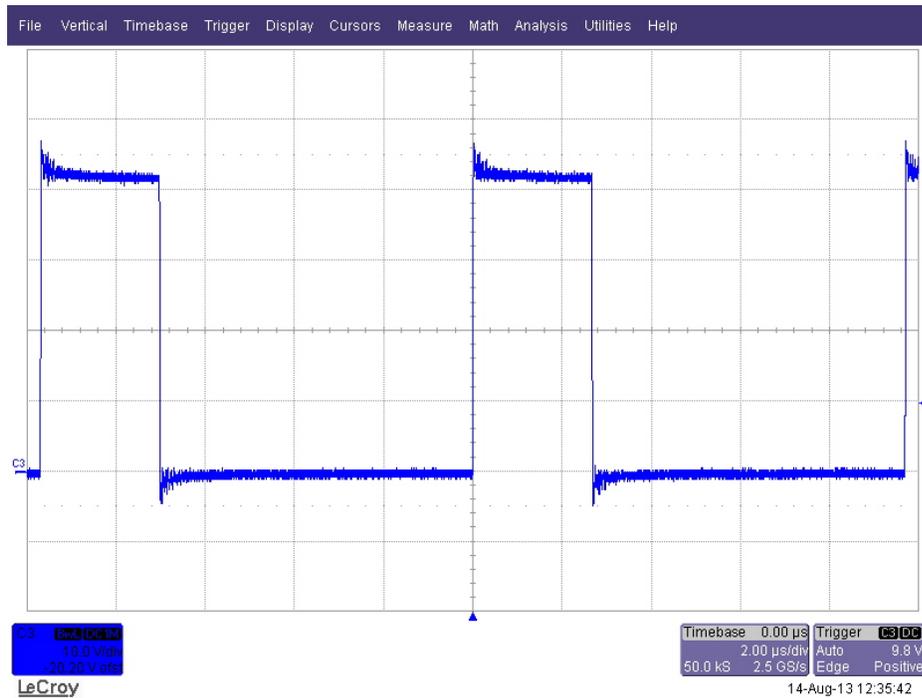Boost converter switch node at 12LED, 700mA load




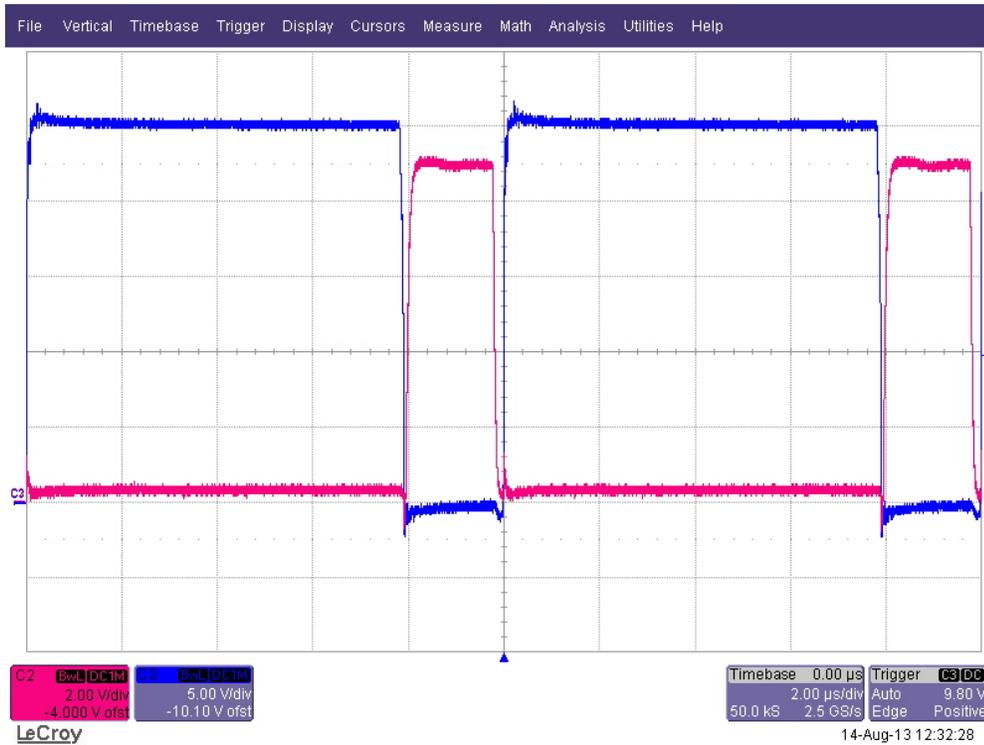b. Gate waveforms

MPPT gate waveforms at 10A load show dead-time implementation




Expanded view

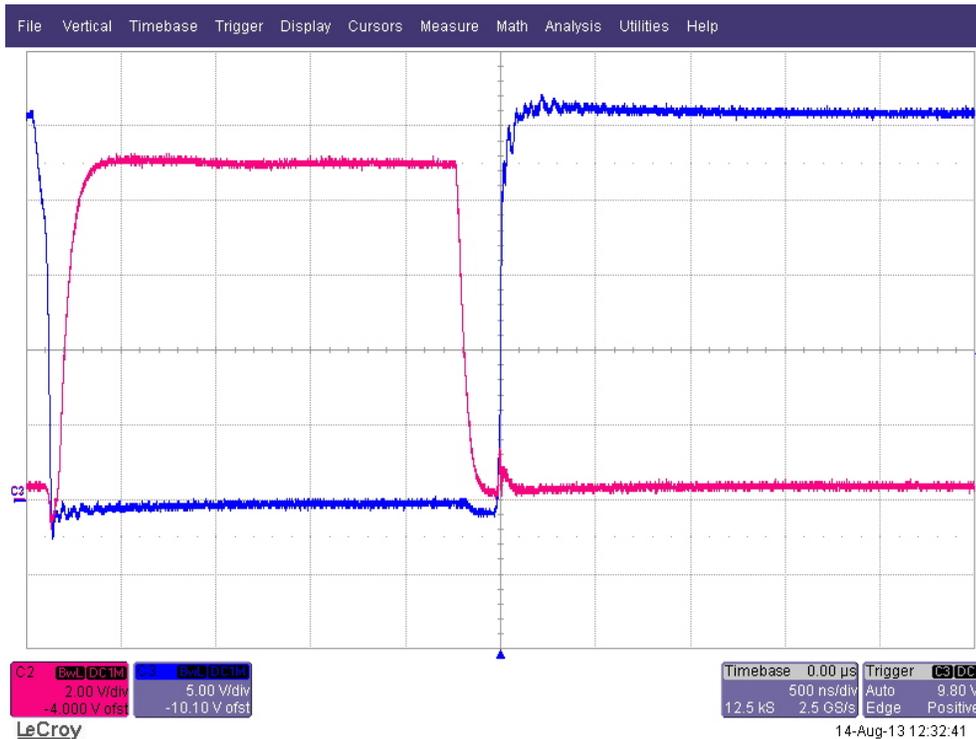

IX. POWER GAIN WITH MPP

a. Test Set-up

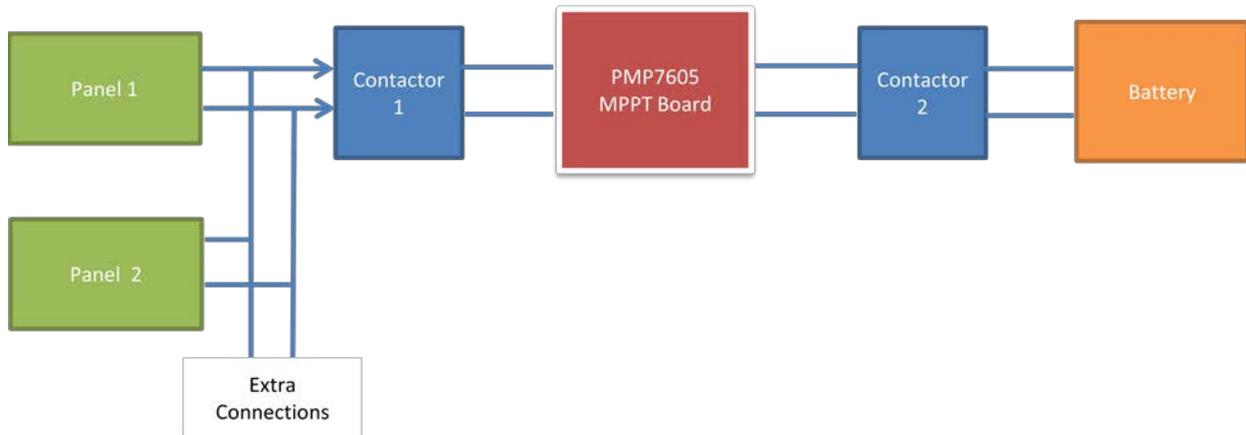


This test was done with an earlier similar design PMP7605. Setup Explains the Power flow from Panel to Battery during MPPT Operation. To connect Panel directly to battery, both contactors were opened and Extra connections were connected directly onto the battery.

b. Test Results


| 12 V System | | | |
|---|-------------------------------------|-------------------------|---------------|
| Battery Voltage = 11.96 | | | |
| Two Panels connected | | | |
| Readings Taken approximately every 5-7 mins (@ 3.15 pm) Cloudy Conditions | | | |
| Sr No | Charging Currents (A) | | Improvement % |
| | Panel directly connected to Battery | Charging via MPPT Board | |
| 1 | 1.794 | 2.08 | 15.94 |
| 2 | 1.28 | 1.443 | 12.73 |
| 3 | 0.55 | 0.6 | 9.09 |
| 4 | 1.15 | 1.3 | 13.04 |
| 5 | 1.21 | 1.35 | 11.57 |
| 6 | 2.13 | 2.5 | 17.37 |

X. SCHEMATIC

a. Power Stage

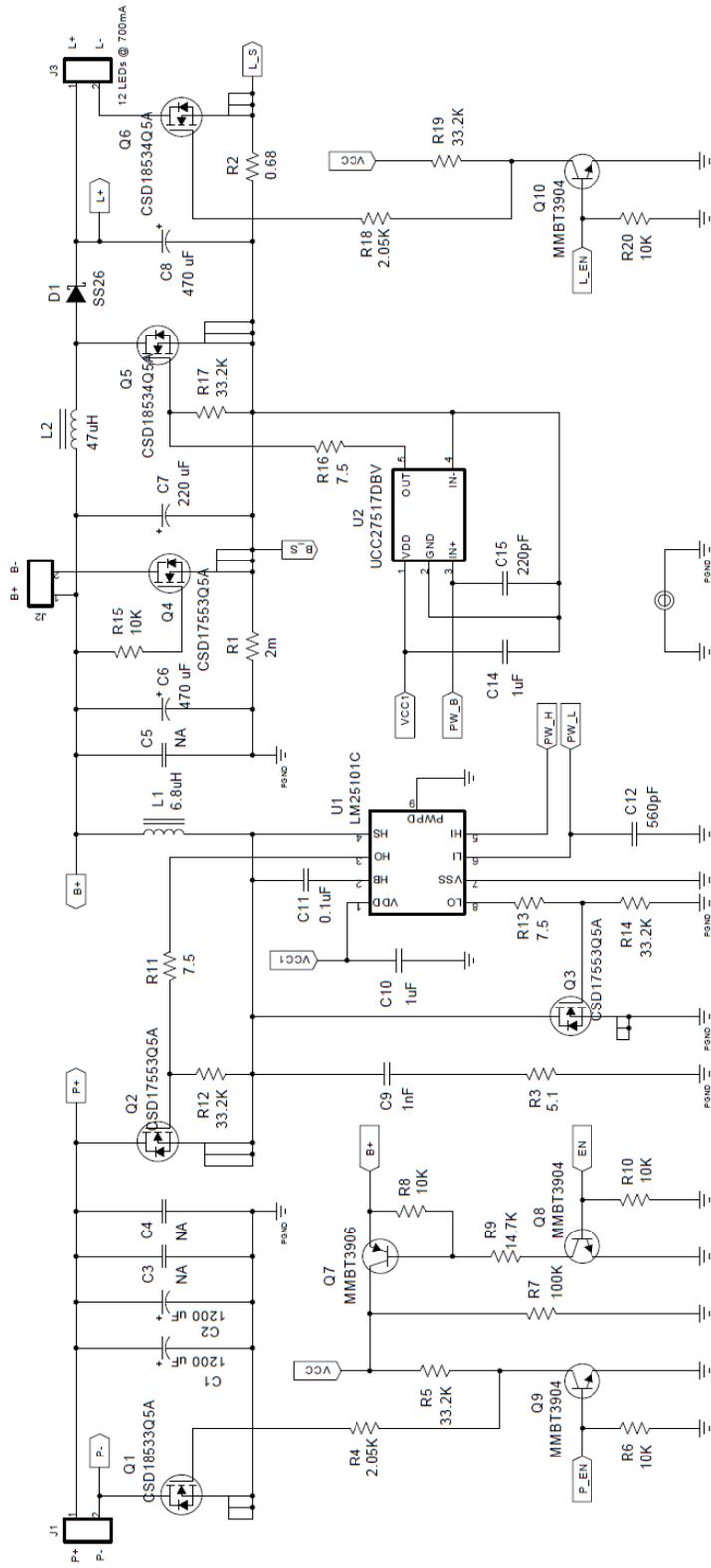

b. Controller and Bias Supply

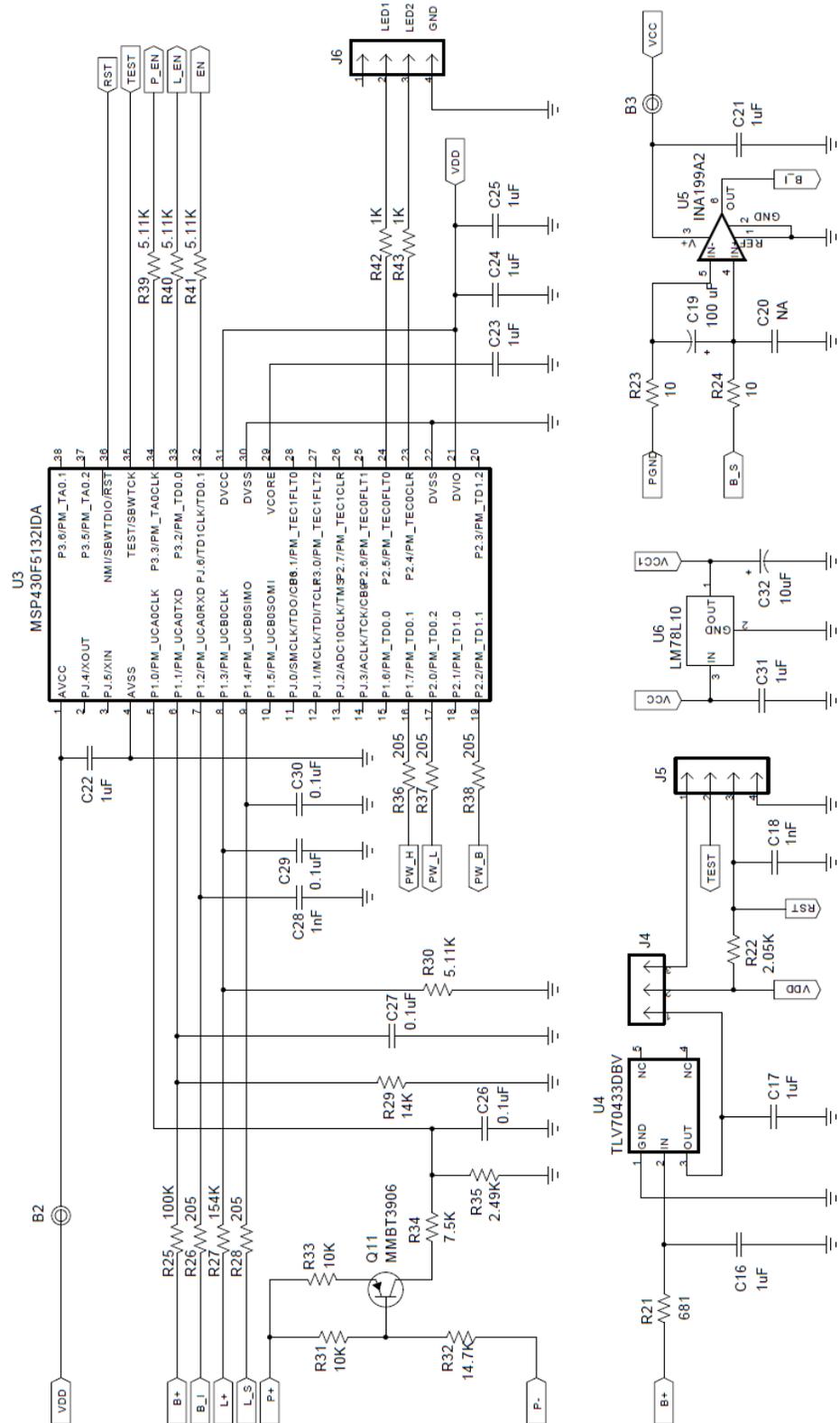

XI. BILL OF MATERIALS

| PMP7647 BOM Revision C | | | | | | | |
|------------------------|-----|--|----------------|---|-------------------|------------------|------------------|
| Item | Qty | Reference | Value | Description | Part Number | Manufacturer | Size |
| 1 | 2 | B2, B3 | | Bead, Ferrite, 500mA, 600ohms | 7427920415 | Würth Elektronik | 805 |
| 2 | 2 | C1, C2 | 1200 uF | Capacitor, Aluminium Electrolytic, Low ESR, 35V | EEU-FM1V122L | Panasonic | 12.5 x 30 mm |
| 3 | 1 | C6 | 470 uF | Capacitor, Aluminium Electrolytic, Low ESR, 35V | EEU-FR1V471L | Panasonic | 8 x 22 mm |
| 2 | 1 | C7 | 220 uF | Capacitor, Aluminium Electrolytic, Low ESR, 35V | UHE1V221MPD6 | Nichicon | 10 x 12.5 mm |
| 3 | 1 | C8 | 470 uF | Capacitor, Aluminium Electrolytic, Low ESR, 63V | UPW1J471MHD | Nichicon | 12.5 x 25 mm |
| 4 | 3 | C9, C18, C28 | 1nF | Capacitor, Ceramic, 50V, X7R, 10% | Std | Std | 603 |
| 5 | 10 | C10, C14, C16, C17, C21, C22, C23, C24, C25, C31 | 1uF | Capacitor, Ceramic, 25V, X7R, 10% | TMK107B7105KA-T | Taiyo-Yuden | 603 |
| 6 | 5 | C30 | 0.1uF | Capacitor, Ceramic, 50V, X7R, 10% | Std | Std | 603 |
| 7 | 1 | C12 | 560pF | Capacitor, Ceramic, 50V, NPO, 1% | Std | Std | 603 |
| 8 | 1 | C15 | 220pF | Capacitor, Ceramic, 50V, NPO, 1% | Std | Std | 603 |
| 9 | 1 | C19 | 100 uF | Capacitor, Aluminium, 10V, 20% | EEU-EB1A101 | Panasonic | 5 x 11 mm |
| 10 | 1 | C32 | 10uF | Capacitor, Aluminium, 10V, 20% | 50YXM10MEFC5X11 | Rubycon | 5 x 11 mm |
| 11 | 1 | D1 | SS26 | Diode, Schottky, 2A, 60V | SS26-TP | MCC Semi | SMA |
| 12 | 3 | J1, J2, J3 | OSTTC022162 | Terminal Block, 2-pin, 15-A, 5.1mm | OSTTC022162 | OST | 0.40 x 0.35 inch |
| 13 | 1 | J4 | PEC36SAAN | Header, Male 3-pin, 100mil spacing, (36-pin strip) | PEC36SAAN | Sullins | 0.100 inch x 3 |
| 14 | 2 | J5, J6 | PEC36SAAN | Header, Male 4-pin, 100mil spacing, (36-pin strip) | PEC36SAAN | Sullins | 0.100 inch x 4 |
| 15 | 1 | L1 | 6.8uH | Inductor, SMT, 18.5-A, 4.1-milliohm | 7443556680 | Würth Elektronik | 18 x 18 x 9 mm |
| 16 | 1 | L2 | 47uH | Inductor, SMT, 3.6-A, 60-milliohm | 7447709470 | Würth Elektronik | 12 x 12 x 10 mm |
| 17 | 1 | Q1 | CSD18533Q5A | MOSFET, N-Chan, 60V, 103A, 5.9 mOhm | CSD18533Q5A | TI | QFN-8 POWER |
| 18 | 2 | Q5, Q6 | CSD18534Q5A | MOSFET, N-Chan, 60V, 50A, 9.8 mOhm | CSD18534Q5A | TI | QFN-8 POWER |
| 19 | 3 | Q2, Q3, Q4 | CSD17553Q5A | MOSFET, N-Chan, 30V, 23.5A, 2.7 mOhm | CSD17553Q5A | TI | QFN-8 POWER |
| 20 | 2 | Q7, Q11 | MMBT3906 | Trans, PNP, 40-V, 200-mA, 225-mW | MMBT3906LT1G | On Semi | SOT23 |
| 21 | 3 | Q8, Q9, Q10 | MMBT3904 | Trans, NPN, 40-V, 200-mA, 225-mW | MMBT3904LT1G | On Semi | SOT23 |
| 22 | 1 | R1 | 2m | Resistor, 2 milliOhm, 3W, 1% | LRMAP2512-R002FT4 | TT/Welwyn | 2512 |
| 23 | 1 | R2 | 0.68 | Resistor, 0.68 Ohm, 2W, 1% | CSRN2512FKR680 | Stackpole | 2512 |
| 24 | 1 | R3 | 5.1 | Resistor, 5.1Ohm, 1W, 5% | Std | Std | 2512 |
| 25 | 3 | R4, R18, R22 | 2.05K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 26 | 5 | R5, R12, R14, R17, R19 | 33.2K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 27 | 7 | R6, R8, R10, R15, R20, R31, R33 | 10K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 28 | 1 | R7 | 100K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 29 | 3 | R11, R13, R16 | 7.5 | Resistor, Chip, 1/10W, 5% | Std | Std | 805 |
| 30 | 1 | R21 | 681 | Resistor, Chip, 1/4 watt, ± 5% | Std | Std | 1206 |
| 31 | 2 | R23, R24 | 10 | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 32 | 1 | R25 | 100K | Resistor, Chip, 1/10W, 1% | Std | Std | 805 |
| 33 | 5 | R26, R28, R36, R37, R38 | 205 | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 34 | 1 | R27 | 154K | Resistor, Chip, 1/10W, 1% | Std | Std | 805 |
| 35 | 1 | R29 | 14K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 36 | 2 | R9, R32 | 14.7K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 37 | 1 | R34 | 7.5K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 38 | 1 | R35 | 2.49K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 39 | 4 | R30, R39, R40, R41 | 5.11K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 40 | 2 | R42, R43 | 1K | Resistor, Chip, 1/16W, 1% | Std | Std | 603 |
| 41 | 1 | U1 | LM25101C | 1A 80V Half-Bridge Gate Driver | LM25101CMAX | TI | SO8 |
| 42 | 1 | U2 | UCC27517DBV | IC, 4A Single Channel High-Speed Low-Side Gate Drivers | UCC27517DBV | TI | SOT23-5 |
| 43 | 1 | U3 | MSP430F5132IDA | IC, Mixed Signal Microcontroller | MSP430F5132IDA | TI | MSOP-38 |
| 44 | 1 | U4 | TLV70433DBV | IC, 24-V Input, 150 mA, Utralow IQ LDO Regulator | TLV70433DBV | TI | SOT-23 |
| 45 | 1 | U5 | INA199A2 | IC, Current shunt monitor, Bi-Directional Zero-Drift Series | INA199A2DCK | TI | SC-70 |
| 46 | 1 | U6 | uA78L10A | IC, 3 Pin 100mA Fixed 10V Positive Voltage Regulator | UA78L10ACLPR | TI | TO-92 |

XII. CONCLUSION

The board is tested for the given specifications and found to meet them. Further optimization of software can be done depending on specific system requirements.

XIII. APPENDIX

EVALUATION BOARD/KIT/MODULE (EVM) WARNINGS, RESTRICTIONS AND DISCLAIMER

For Feasibility Evaluation Only, in Laboratory/Development Environments. The EVM is not a complete product. It is intended solely for use for preliminary feasibility evaluation in laboratory / development environments by technically qualified electronics experts who are familiar with the dangers and application risks associated with handling electrical / mechanical components, systems and subsystems. It should not be used as all or part of a production unit.

Your Sole Responsibility and Risk. You acknowledge, represent and agree that:

1. You have unique knowledge concerning Federal, State and local regulatory requirements (including but not limited to Food and Drug Administration regulations, if applicable) which relate to your products and which relate to your use (and/or that of your employees, affiliates, contractors or designees) of the EVM for evaluation, testing and other purposes.
2. You have full and exclusive responsibility to assure the safety and compliance of your products with all such laws and other applicable regulatory requirements, and also to assure the safety of any activities to be conducted by you and/or your employees, affiliates, contractors or designees, using the EVM. Further, you are responsible to assure that any interfaces (electronic and/or mechanical) between the EVM and any human body are designed with suitable isolation and means to safely limit accessible leakage currents to minimize the risk of electrical shock hazard.
3. Since the EVM is not a completed product, it may not meet all applicable regulatory and safety compliance standards (such as UL, CSA, VDE, CE, RoHS and WEEE) which may normally be associated with similar items. You assume full responsibility to determine and/or assure compliance with any such standards and related certifications as may be applicable. You will employ reasonable safeguards to ensure that your use of the EVM will not result in any property damage, injury or death, even if the EVM should fail to perform as described or expected.

Certain Instructions. Exceeding the specified EVM ratings (including but not limited to input and output voltage, current, power, and environmental ranges) may cause property damage, personal injury or death. If there are questions concerning these ratings please contact a TI field representative prior to connecting interface electronics including input power and intended loads. Any loads applied outside of the specified output range may result in unintended and/or inaccurate operation and/or possible permanent damage to the EVM and/or interface electronics. Please consult the EVM User's Guide prior to connecting any load to the EVM output. If there is uncertainty as to the load specification, please contact a TI field representative. During normal operation, some circuit components may have case temperatures greater than 60°C as long as the input and output ranges are maintained at nominal ambient operating temperature. These components include but are not limited to linear regulators, switching transistors, pass transistors, and current sense resistors which can be identified using the EVM schematic located in the EVM User's Guide. When placing measurement probes near these devices during normal operation, please be aware that these devices may be very warm to the touch.

Agreement to Defend, Indemnify and Hold Harmless. You agree to defend, indemnify and hold TI, its licensors and their representatives harmless from and against any and all claims, damages, losses, expenses, costs and liabilities (collectively, "Claims") arising out of or in connection with any use of the EVM that is not in accordance with the terms of this agreement. This obligation shall apply whether Claims arise under the law of tort or contract or any other legal theory, and even if the EVM fails to perform as described or expected.

Safety-Critical or Life-Critical Applications. If you intend to evaluate TI components for possible use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, such as devices which are classified as FDA Class III or similar classification, then you must specifically notify TI of such intent and enter into a separate Assurance and Indemnity Agreement.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated