

TI Designs – Precision: Verified Design

Low-Power Reference and Bipolar Voltage Conditioning Circuit Reference Design for Low-Power ADCs



TI Designs – Precision

TI Designs – Precision are analog solutions created by TI's analog experts. Verified Designs offer the theory, component selection, simulation, complete PCB schematic & layout, bill of materials, and measured performance of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed

Circuit Description

This low-power reference and conditioning circuit attenuates and level-shifts a bipolar input voltage within the proper input range of a single-supply low-power 16-Bit $\Delta\Sigma$ ADC such as the one inside the MSP430 or other similar single-supply ADCs. Precision reference circuits are used to level-shift the input signal, provide the ADC reference voltage and to create a well-regulated supply voltage for the low-power analog circuitry. A low-power zero-drift op amp circuit is used to attenuate and level-shift the input signal.



Design Resources

[Design Archive](#)
[TINA-TI™](#)
[REF3330](#)
[REF3312](#)
[OPA317](#)

All Design files
 SPICE Simulator
 Product Folder
 Product Folder
 Product Folder



  [Ask The Analog Experts](#)
[WEBENCH® Design Center](#)
[TI Designs – Precision Library](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments
 WEBENCH is a registered trademark of Texas Instruments

1 Design Summary

The design requirements are as follows:

- Supply Voltage: +3.3 V
- Maximum Input Voltage: +/- 6 V
- Specified Input Voltage: +/- 5 V
- ADC Reference Voltage: 1.25 V

The goal for this design is to accurately condition a ± 5 V bipolar input voltage into a voltage suitable for conversion by a low-voltage ADC with a 1.25 V reference voltage, V_{REF} , and an input voltage range of $V_{REF}/2$. The circuit should function with reduced performance over a wider input range of at least ± 6 V to allow for easier protection of over-voltage conditions. The specific design goals and performance metrics are summarized in Table 1. Figure 1 depicts the measured transfer function and accuracy results.

Table 1. Comparison of Design Goals, Simulation, and Measured Performance for ± 5 V Input

	Goal	Simulated	Measured
Calibrated Error (%FSR)	0.001	N/A	0.0005
Unadjusted Error (%FSR)	0.15	0.0439	0.0138
Operational Current Consumption (μ A)	100	93.07	89.54
60 Hz Rejection (dB)	> 60	60	62

 


Figure 1: Measured Transfer Function Over the Full ± 6 V Input Range

 


Figure 2: Calibrated Error Voltage

2 Theory of Operation

Figure 3 depicts a simplified schematic for this design showing the MSP430 ADC inputs and full input conditioning circuitry. The ADC is configured for a bipolar measurement where final conversion result will be the differential voltage, V_{DIFF} , between the voltage at the positive and negative ADC inputs, V_{A1+} and V_{A1-} . The bipolar, GND referenced input signal must be level-shifted and attenuated by the op amp such that the output is biased to $V_{REF}/2$ and has a differential voltage that is within the $\pm V_{REF}/2$ input range of the ADC. The transfer function for the op-amp circuit simplifies to Equation 1 if the conditions in Equations 2 and 3 are met. The full transfer function for the input circuitry is shown in Appendix B.1 for reference. The V_{A1-} voltage is based on the resistor divider formed by R_6 and R_7 and will be set to $V_{REF}/2$ by setting R_6 equal to R_7 as shown in Equation 4.

 


Figure 3: Simplified Circuit schematic

$$V_{A1+} = \left(\frac{R_3}{R_2 + R_3} \right) V_{REF} + \left(\frac{R_2 \parallel R_3}{R_1} \right) V_{IN} \quad (1)$$

Given

$$R_4 = R_1 \quad (2)$$

and

$$R_5 = R_2 \parallel R_3 \quad (3)$$

$$V_{A1-} = \left(\frac{R_7}{R_6 + R_7} \right) V_{REF} = \frac{V_{REF}}{2} \quad (4)$$

2.1 Op Amp Level-Shift Design

The ratio of R_2 , R_3 , and the V_{REF} voltage will determine the voltage on the output of the op amp when the differential input is 0 V. The components will be selected such that V_{OUT} is equal to $V_{REF}/2$ voltage when V_{IN} is equal to 0 V as shown in Equations 5 – 7.

$$V_{A1+} = \frac{V_{REF}}{2} = \left(\frac{R_3}{R_2 + R_3} \right) V_{REF} \quad (5)$$

Given

$$V_{in} = 0 \text{ V} \quad (6)$$

and

$$R_2 = R_3 \quad (7)$$

The value of R_5 can be solved for by setting R_3 equal to R_2 in Equation 3 as shown in Equation 8.

$$R_5 = \left(\frac{R_2 * R_2}{R_2 + R_2} \right) = \frac{R_2^2}{2 * R_2} = \frac{R_2}{2} \quad (8)$$

2.2 Differential Input Attenuator Design

V_{DIFF} is the difference between the two inputs as shown in Equation 9.

$$V_{DIFF} = (V_{A1+}) - (V_{A1-}) = \left(\frac{R_3}{R_2 + R_3} \right) V_{REF} + \left(\frac{R_2 \parallel R_3}{R_1} \right) V_{IN} - \frac{V_{REF}}{2} \quad (9)$$

When the ratio of R_3 and R_2 equals the ratio of R_7 and R_6 , Equation 9 simplifies to Equation 11.

If

$$\left(\frac{R_3}{R_2 + R_3} \right) V_{REF} = \left(\frac{R_7}{R_6 + R_7} \right) V_{REF} = \frac{1}{2} V_{REF} \quad (10)$$

then

$$V_{DIFF} = \left(\frac{R_2 \parallel R_3}{R_1} \right) V_{IN} \quad (11)$$

The ratio of R_1 , R_2 , and R_3 can be determined by setting V_{A1+} equal to the maximum V_{DIFF} voltage for a full-scale positive and/or negative input voltage V_{IN_MAX} as shown in Equation 12.

$$V_{A1+} = V_{DIFF_MAX} = \left(\frac{R_2 \parallel R_3}{R_1} \right) V_{IN_MAX} \quad (12)$$

Since R_2 equals R_3 , Equation 12 simplifies to $R_2/2$ resulting in Equation 13.

$$V_{DIFF_MAX} = \left(\frac{R_2}{2 * R_1} \right) V_{IN_MAX} \quad (13)$$

2.3 Input Filtering

Both inputs feature first-order low-pass anti-aliasing filters that limit the bandwidth and noise of the input signals applied to the ADC. The A1+ filter is formed by R_8 and C_1 and the equation for the -3dB cutoff frequency is shown in Equation 14.

$$f_{-3dB_A1+} = \frac{1}{2 * \pi * R_8 * C_1} \quad (14)$$

The A1- input filter is formed by C_2 and the parallel combination of the R_6 and R_7 resistors as shown in Equation 15.

$$f_{-3dB_A1-} = \frac{1}{2 * \pi * \left(\frac{R_6}{2}\right) * C_2} \quad (15)$$

3 Component Selection

3.1 Voltage References

The REF33xx series of precision low-power voltage references was selected for this design to pair well with the low power consumption of the MSP430 while achieving the target accuracy goals. The 16-bit converter in the MSP430F2013 accepts an external reference voltage from 1 V to 1.5 V with a typical reference input of 1.25 V as shown in Figure 4.

SD16_A, External Reference Input (MSP430F20x3)

over recommended ranges of supply voltage and operating free-air temperature (unless otherwise noted)

PARAMETER	TEST CONDITIONS	V _{CC}	MIN	TYP	MAX	UNIT
V _{REF(I)} Input voltage range	SD16REFON = 0	3 V	1	1.25	1.5	V
I _{REF(I)} Input current	SD16REFON = 0	3 V			50	nA

Figure 4: MSP430F2013 SD16_A External Voltage Reference Specifications

The REF3312 was selected to provide the desired 1.25 V reference voltage for the MSP430 ADC. The accuracy of the REF3312 output, shown in Figure 5, will directly affect the accuracy of the entire system and needs to be less than the desired unadjusted error goals. The REF3312 maximum $\pm 0.15\%$ initial accuracy specification is equal to the unadjusted error design goal of 0.15% indicating that most of the error budget in this design needs to be devoted to the reference accuracy.

PARAMETER	CONDITIONS	REF33xx			UNITS	
		MIN	TYP	MAX		
REF3312 (1.25V)						
OUTPUT VOLTAGE						
Initial Accuracy	V _{OUT}	V _{IN} = 5V		1.25		V
			-0.15		+0.15	%
NOISE						
Output Voltage Noise		f = 0.1Hz to 10Hz		35		μV_{PP}

Figure 5: REF3312 Output Accuracy Specifications

The +3.3 V system supply voltage that powers the MSP430 may also supply other devices and therefore may have regulation and noise issues. The REF3330 was selected to create an accurate and stable +3.0 V output that was used by the op amp, REF3312, and other low-power analog circuitry. The REF33xx series has a drop-output voltage of V_{OUT}+200 mV so as long as the input supply remains above +3.2 V the REF3330 will produce a regulated +3.0 V output. The output current for the REF33xx series is specified at +/-5 mA as shown in Figure 6 which is sufficient for REF3312 and a low-power op amp.

 


Figure 6: REF33xx Output Voltage vs. Load Current

3.2 Op Amp

The OPA317 was selected because of the low offset voltage, low offset voltage drift, CMRR, and low power consumption. The important dc specifications for the OPA317 can be seen in Figure 7. The maximum offset of 100 μV will account for only 0.001% of the full-scale signal and the low-drift will reduce temperature drift effects. Therefore, as previously mentioned, most of the error in this design will be from the reference accuracy and passive component tolerances.

ELECTRICAL CHARACTERISTICS: $V_S = +1.8 \text{ V to } +5.5 \text{ V}$

At $T_A = +25^\circ\text{C}$, $R_L = 10 \text{ k}\Omega$ connected to midsupply, $V_{CM} = V_{OUT} = \text{midsupply}$, unless otherwise noted.

PARAMETER	TEST CONDITIONS	OPA317, OPA2317, OPA4317			UNIT
		MIN	TYP	MAX	
OFFSET VOLTAGE					
V_{OS}	Input offset voltage	$V_S = +5 \text{ V}$ $T_A = -40^\circ\text{C to } +125^\circ\text{C}, V_S = +5 \text{ V}$			μV
dV_{OS}/dT	vs temperature	$T_A = -40^\circ\text{C to } +125^\circ\text{C}$			$\mu\text{V}/^\circ\text{C}$
PSRR	vs power supply	$T_A = -40^\circ\text{C to } +125^\circ\text{C}, V_S = +1.8 \text{ V to } +5.5 \text{ V}$			$\mu\text{V}/\text{V}$
INPUT VOLTAGE RANGE					
V_{CM}	Common-mode voltage range	$(V-) - 0.1$ $(V+) + 0.1$			V
CMRR	Common-mode rejection ratio	$T_A = -40^\circ\text{C to } +125^\circ\text{C}$ $(V-) - 0.1 \text{ V} < V_{CM} < (V+) + 0.1 \text{ V}$			95 108 dB
		OPA4317, $T_A = -40^\circ\text{C to } +125^\circ\text{C}$ $(V-) - 0.1 \text{ V} < V_{CM} < (V+) + 0.1 \text{ V}, V_S = 5.5 \text{ V}$			95 108 dB
POWER SUPPLY					
V_S	Specified voltage range	1.8 5.5			V
I_Q	Quiescent current per amplifier	$T_A = -40^\circ\text{C to } +125^\circ\text{C}, I_O = 0$			21 35 μA
	Turn-on time	$V_S = +5 \text{ V}$			100 μs

Figure 7: OPA317 dc Specifications

3.3 Input Attenuation and Level Shifting

For this design, the bipolar $\pm 5 \text{ V}$ input must be attenuated and level shifted so the differential voltage is within the input range of $\pm V_{REF}/2$, or $\pm 0.625 \text{ V}$. The accuracy of the op amp output and ADC input may degrade near the supply rails and V_{REF} voltage so the output will be designed to produce a 0.125 V to 1.125 V output, or $\pm 0.5 \text{ V}$ for a $\pm 5 \text{ V}$ input. Scaling the output this way also increases the allowable input range to $\pm 6 \text{ V}$ and allows for some under/over-scale voltage measurement and protection.

Equation 13 can be solved to scale the ± 5 V input to a ± 0.5 V differential voltage as shown in Equations 16 - 18. R_1 and R_4 will dominate the input impedance for this design and were therefore selected to be 100 k Ω . Higher values can be selected to increase the input impedance at the expense of input noise.

$$R_1 = R_4 = 100 \text{ k}\Omega \quad (16)$$

$$0.5 \text{ V} = \left(\frac{R_2}{2 * 100 \text{ k}\Omega} \right) * 5 \text{ V} \quad (17)$$

$$R_2 = R_3 = 20 \text{ k}\Omega \quad (18)$$

With the value for R_2 and R_3 selected, the value for R_5 can be calculated as shown in Equation 19.

$$R_5 = \frac{R_2}{2} = 10 \text{ k}\Omega \quad (19)$$

In order for V_{A1-} to equal to $V_{REF}/2$, R_6 needs to equal R_7 . The two resistors will be selected to be 47 k Ω to conserve power without creating an impedance too weak to drive the ADC input.

$$R_6 = R_7 = 47 \text{ k}\Omega \quad (20)$$

3.4 Input Filtering

The MSP430 ADC was configured to run from the 1.1 MHz SMCLK with an over-sampling rate (OSR) of 256 yielding a sample rate of roughly 4.3 kHz. The input filter cutoff frequency was set to 1 kHz to limit the input signal bandwidth as shown in Equation 21 and 22. R_8 was selected to be 1 k Ω to provide isolation from the capacitive load of the low-pass filter thereby reducing stability concerns.

$$f_{-3dB_A1+} = 1\text{kHz} = \frac{1}{2 * \pi * R_8 * C_1} \quad (21)$$

$$C_1 = \frac{1}{2 * \pi * 1\text{k}\Omega * 1\text{kHz}} = 159 \text{ nF} \quad (22)$$

C_1 was reduced to 150nF so it could be a standard value.

The A1- input of the $\Delta\Sigma$ converter is not buffered and therefore requires a large capacitor to supply the charge for the internal sampling capacitor. A 47 μF capacitor was selected resulting in the cutoff frequency shown in Equation 23. Applications that can't tolerate such a low frequency cutoff, and therefore long start-up time, should buffer the A1- input with another OPA317 to properly drive the ADC input with a lower input capacitor.

$$f_{-3dB_A1-} = \frac{1}{2 * \pi * \left(\frac{R_6}{2} \right) * C_2} = 0.144 \text{ Hz} \quad (23)$$

3.5 Passive Component Tolerances and Materials

Resistors R_1 , R_2 , R_3 , R_4 , R_5 , R_6 , and R_7 directly affect the accuracy of the circuit. To meet the unadjusted accuracy goals of 0.2%, the resistors were chosen to be 0.1%. As described in Reference 1, selecting 0.1% resistors for the construction of the difference amplifier circuit should provide a common-mode rejection (CMRR) of at least 60 dB.

Signal path capacitors should be C0G/NP0 dielectric material to minimize the signal distortion as well as prevent piezo-electric effects that are present with other ceramic capacitor dielectrics.

4 Simulation

The TINA-TI™ simulation circuit for this design can be seen in Figure 8. The dc transfer function results with the component values selected in Section 3 are shown in Figure 9.

 


Figure 8: TINA-TI™ – Circuit Schematic

 


Figure 9: DC Transfer Function Results

A more accurate representation of the circuit results can be obtained by performing a Monte-Carlo analysis on the circuit with the correct component tolerances. Figure 10 displays the histogram for the results with a +5V input and the other results can be found in Appendix B. Table 2 contains the results obtained by creating a histogram of the Monte-Carlo output voltage results obtained from a -5 V, 0 V, and +5 V input.

 


Figure 10: Circuit Output Variation with a Full-Scale +5 V dc Input

Table 2. Histogram Results of the Monte-Carlo Data

Statistic	Units	Input Voltage (V)		
		-5	0	+5
Mean Value	mV	125.0224	625.0206	1125.0190
Standard Deviation	μV	134.6068	82.5096	140.0637
Nominal Value	mV	125.0104	625.0111	1125.0124

Using the mean (μ) and standard deviation (σ) from the Monte-Carlo simulation to represent the final production circuit results, a six sigma (-3σ to 3σ) or 99.7% prediction of full-scale error (%FSR) is calculated using Equation 24.

$$\text{Percent Error (\%FSR)} = \frac{(\mu \pm 3\sigma) - V_{\text{OUT_EXPECTED}}}{V_{\text{OUT_FULL_SCALE}}} \times 100 \quad (24)$$

The maximum simulated error at the positive full-scale input of +5 V is $\pm 0.0439\%$ as shown in Equation 25. The maximum simulated error at the negative full-scale input of -5V is $\pm 0.0426\%$.

$$\text{Percent Error (\%FSR)} = \frac{(1125.0190 \pm (3 * 0.1400637)) - 1125}{1000} \times 100 = 0.0439 \% \quad (25)$$

Performing a Monte-Carlo ac transfer simulation with the input terminals shorted together provides an accurate representation of the CMRR performance of the circuit. As shown in Figure 11, the low frequency results are dominated by the matching of the 0.1% passive components. The curves in Figure 11 have been adjusted for the gain of the circuit and show at least 60dB of CMRR for signal frequencies up to 5 kHz.

 


Figure 11: Circuit CMRR Variation over Frequency from Resistor Tolerance

4.1 Simulated Results Summary

The simulated performance is compared to the performance goals set in Section 0 in Table 3.

Table 3: Simulated Performance Result Summary

	Goal	Simulated
Calibrated Error (%FSR)	0.001	N/A
Unadjusted Error (%FSR)	0.15	0.0439
Operational Current Consumption (μ A)	100	93.07
60 Hz Rejection (dB)	> 60	60

5 PCB Design

The PCB schematic and bill of materials can be found in Appendix A.

5.1 PCB Layout

For optimal performance of this design follow standard PCB layout guidelines, including proper decoupling close to all integrated circuits and adequate power and ground connections with large copper pours. The size of the PCB and connectors were selected to connect directly to the MSP430 LaunchPad.

 


Figure 12: Altium PCB Layout

6 Verification & Measured Performance

This section focuses only on the performance of the reference and input circuitry. It does not take the MSP430 ADC performance into consideration. Complete data with the MPS430F2013 ADC can be found in Appendix B.3.

6.1 DC Performance

The measured dc performance and calculated error of the circuit can be seen in Figure 13 and Figure 14 respectively. By applying a 2-point gain and offset calibration over the specified $\pm 5\text{V}$ input range the calibrated error can be seen in Figure 15. The uncalibrated results show errors of $138\ \mu\text{V}$ or $0.0138\ \%\text{FSR}$. The calibrated results with a simple 2-point calibration show errors under $5\ \mu\text{V}$ or $0.0005\ \%\text{FSR}$ in the specified input range of $\pm 5\ \text{V}$. Methods for 2-point calibration are explained in Reference 2.

 


Figure 13. Measured DC Transfer Function with $\pm 6\text{V}$ Input

 


Figure 14. Measured Output Error with $\pm 6\text{V}$ Input

 


Figure 15. Calibrated Output Error with ±6V Input

6.2 AC Performance

The AC transfer function for the attenuation and level-shifting circuit can be seen in Figure 16.

 


Figure 16. Measured ac Transfer Function

The low-frequency ac CMRR performance was measured to be 62 dB as shown in Figure 17.

 


Figure 17. Measured ac CMRR Results

6.3 Measured Results Summary

Table 4. Comparison of Design Goals, Simulation, and Measured Performance

	Goal	Simulated	Measured
Calibrated Error (%FSR)	0.001	N/A	0.0005
Unadjusted Error (%FSR)	0.15	0.0439	0.0138
Operational Current Consumption (μA)	100	93.07	89.54
60 Hz Rejection (dB)	> 60	60	62

7 Modifications

The gain and reference levels of this circuit can be adjusted using the equations in Section 2. Table 5 lists other low-power amplifiers with different performance specifications that may have advantages in other circuits. Other similar $\Delta\Sigma$ ADCs may require a buffer for the V_{A1} for proper conversion results. Higher sampling rate $\Delta\Sigma$ ADCs and SAR ADC topologies will likely require higher bandwidth amplifiers to properly drive the inputs.

Table 5. Alternate Low-Power Op Amps

Op Amp	Supply Voltage (V)	Quiescent Current Typ/Max (μA)	V_{os} Typ/Max (μV)	V_{os} Drift ($\mu\text{V}/^\circ\text{C}$)	CMRR Typ/Max (dB)	Gain-Bandwidth (kHz)
OPA317	1.8 – 5.5	21 / 35	20 / 100	0.05	95 / 108	300
OPA330	1.8 – 5.5	21 / 35	8 / 50	0.02	100 / 115	350
OPA333	1.8 – 5.5	17 / 25	2 / 10	0.02	106 / 130	350
OPA369	1.8 – 5.5	0.8 / 1.2	250 / 750	0.4	90 / 100	12
OPA379	1.8 – 5.5	2.9 / 5.5	400 / 1500	0.4	62 / 100	90
LPV511	2.7 - 12	0.88 / 1.2	200 / 3000	0.3	77 / 100	27

8 About the Author

Collin Wells is an applications engineer in the Precision Linear group at Texas Instruments where he supports industrial products and applications. Collin received his BSEE from the University of Texas, Dallas.

Janet Sun is an analog field application engineer in Beijing, China supporting industrial and other performance analog customers. She completed work on this system as well as several others during a 6-month rotation working with the precision amplifier team in Dallas.

9 Acknowledgements & References

1. *Pete Semig, Common-Mode Rejection, Presentation 2012.*
2. *Mock, Mike, 0-1A, Single-Supply, Low-Side, Current Sensing Solution, [TIDU040](#)*

Appendix A.

A.1 Electrical Schematic

 


Figure A-1: Electrical Schematic

A.2 Bill of Materials

TEXAS INSTRUMENTS

Bill of Materials

Ti Designs Precision - TIP0154 - Low-Power Reference and Bi-Polar Voltage Conditioning for 16-Bit ADC

Item #	Quantity	Designator	Value	Description	Manufacturer	Part Number
1	1	C1	0.15uF	CAP, CERM, 0.15uF, 16V, +/-10%, X7R, 0603	MuRata	GRM188R71C154KA01C
2	1	C2	47uF	CAP, CERM, 47uF, 6.3V, +/-20%, X5R, 0603	MuRata	GRM188R60J476M
3	3	C3, C4, C5	1uF	CAP, CERM, 1uF, 16V, +/-10%, X7R, 0603	TDK	C1608X7R1C105K
4	1	C6	10uF	CAP, CERM, 10uF, 16V, +/-20%, X7R, 1206	TDK	C3216X7R1C106M
5	1	C7	1000pF	CAP CER 1000PF 50V 20% X7R 0603	Johanson Dielectrics Inc	500X14W102MV4T
6	1	C8	0.1uF	CAP, CERM, 0.1uF, 50V, +/-10%, X7R, 0603	MuRata	GRM188R71H104KA93D
7	1	D1		DIODE TVS ARRAY 15V SOD323	Bourns	CDSOD323-T15SC
8	2	J1, J2		CONN HEADER 10POS SOCKET 2.54MM	Würth Electronics	61301011821
9	1	J3		Terminal Block, 6A, 3.5mm Pitch, 2-Pos, TH	On-Shore Technology	ED555/2DS
10	5	R1, R4, R9	100k	RES, 100k ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603100KFKEA
11	2	R2, R3	20.0k	RES, 20.0k ohm, 0.1%, 0.1W, 0603	Susumu Co Ltd	RG1608P-203-B-T5
12	1	R5	10.0k	RES, 10.0k ohm, 0.1%, 0.1W, 0603	Susumu Co Ltd	RG1608P-103-B-T5
13	1	R6, R7	47.0k	RES, 47.0k ohm, 0.1%, 0.1W, 0603	Susumu Co Ltd	RG1608P-473-B-T5
14	1	R8	1.00k	RES, 1.00k ohm, 0.1%, 0.1W, 0603	Yageo America	RT0603BRD071KL
15	1	SW1		SWITCH TACTILE SPST-NO 0.05A 32V	C&K Components	KSC222J LFS
16	4	TP1, TP2, TP3, TP4		Test Point, Miniature, Black, TH	Keystone	5001
17	1	U1		IC, 30 ppm/C, 3.9 uA 3.0V-Voltage Reference	Texas Instruments	REF3330AIDCKT
18	1	U2		IC, 30 ppm/C, 3.9 uA 1.25V-Voltage Reference	Texas Instruments	REF3312AIDCKR
19	1	U3		IC OPAMP GP 300KHZ RRO SC70-5	Texas Instruments	OPA317IDCKR

Figure A-2: Bill of Materials

Appendix B.

B.1 Complete Transfer Function

The complete transfer function for the circuit topology featured in this design is shown in the equation below:

$$V_{OUT} = \left(\frac{R_2 * R_5 * R_3 + R_1 * R_5 * R_3}{R_3 * R_4 * R_1 + R_5 * R_4 * R_1 + R_5 * R_3 * R_1} \right) V_{REF} + \left(\frac{R_2 * R_5 * R_4 + R_1 * R_5 * R_4}{R_3 * R_4 * R_1 + R_5 * R_4 * R_1 + R_5 * R_3 * R_1} \right) V_{IN}$$

B.2 Simulated Monte-Carlo Results

 


Figure 18: Histogram Transfer Function Results

 


Figure 19: Circuit Output Variation with a Negative Full-Scale +5 V dc Input

 


Figure 20: Circuit Output Variation with a 0 V dc Input

 


Figure 21: Circuit Output Variation with a Positive Full-Scale +5 V dc Input

B.3 MSP430F2013 SD_16 Measured Results

The measured output code results using the MSP430F2013 SD_16 $\Delta\Sigma$ ADC are shown in Figure 22. The error codes and calibrated error codes are shown in Figure 23 and Figure 24, respectively. The uncalibrated error codes results in approximately 2.86 mV of error or 0.286 %FSR, while the calibrated results reduce the error to approximately 172 μ V or 0.017 %FSR.

 


Figure 22: MSP430F2013 Output Code vs. Input Voltage

 


Figure 23: Un-calibrated Error Codes vs. Input Voltage

 


Figure 24: Calibrated Error Codes vs. Input Voltage

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.