

TIDA-00331- "Precision Power Limiting Solution"

1. System Description:

This solution limits the power delivered to a maximum of 15W to ensure IEC60730 compliance in Human-Machine-Interaction (HMI) ports, making it very easy for the end equipment to meet safety regulations.

This design uses TI's TPS25921AD to monitor the voltage and current flowing through the connected system and controls the power output within 2%. Along with the power limit function, TPS25921AD also protects against over voltage, under voltage, inrush current and short circuits.

2. System Operation

Figure 1 shows a very simple and cost effective way to limit the power delivered to the downstream load. This concept uses TI's TPS25921 and supplies power to the connected output load in such a way that load power never exceeded 15W to meet IEC60730 compliance requirements. The operation of the circuit is as follows.

For the given load condition, higher input will produce more power at the load and that may be more than 15W if the load current is not reduced.

The maximum current limit of the device can be set up to 1.5A by R_{ILIM} resistor. A small circuit wired around Q1 with R3, R4 and R5 is utilized to reduce the current whenever output power exceeds more than 15W. The Q1 remains inactive until V_{out} is less than 10V and can deliver up to 15W load. The Q1 plays a role to reduce the effective resistance at ILIM pin by diverting some current from ILIM pin through R5 and Q1 as the V_{out} starts increasing higher than 10V. This reduces impedance at ILIM, altering current limit setting and now current limit will be lower than 1.5A for the increased input voltage.

The R3, R4 and R5 are selected in such a way that allows Q1 keep altering the TPS25921 current limit dynamically as V_{out} increases.

For example if V_{in} or V_{out} is 12V, the Q1 will program 1.25A current limit and for 16V output, the current limit will be altered to 1.066A in order to maintain the output power not exceeding 15W.

TIDA-00331- "Precision Power Limiting Solution"

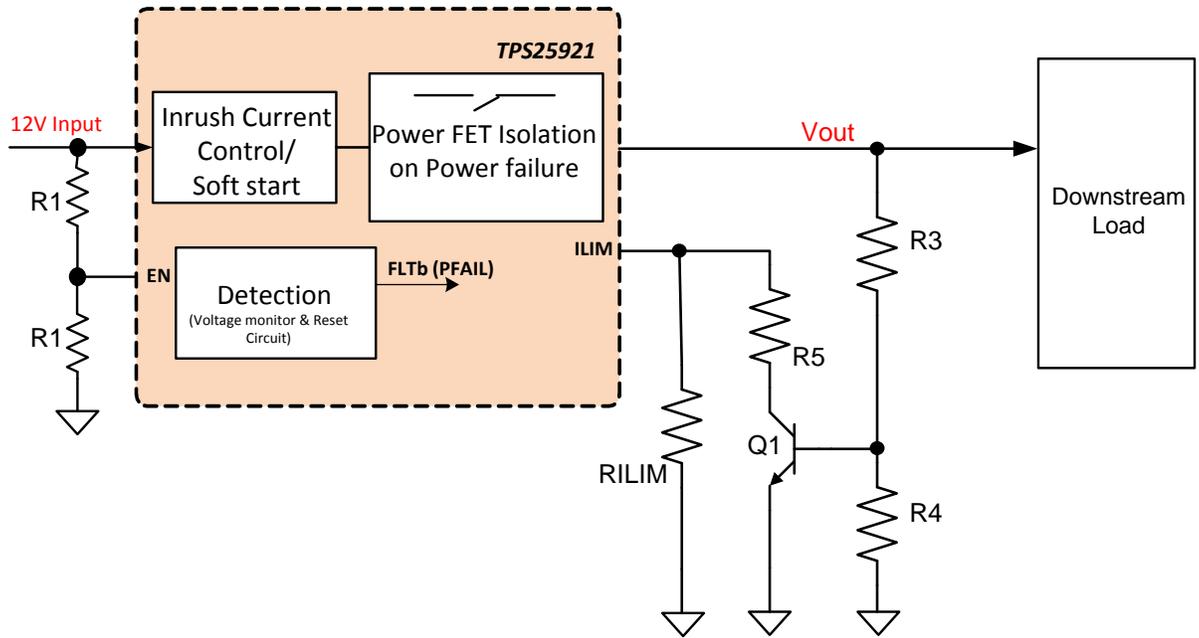


Figure 1: Block Diagram Precision Power Limiting Solution

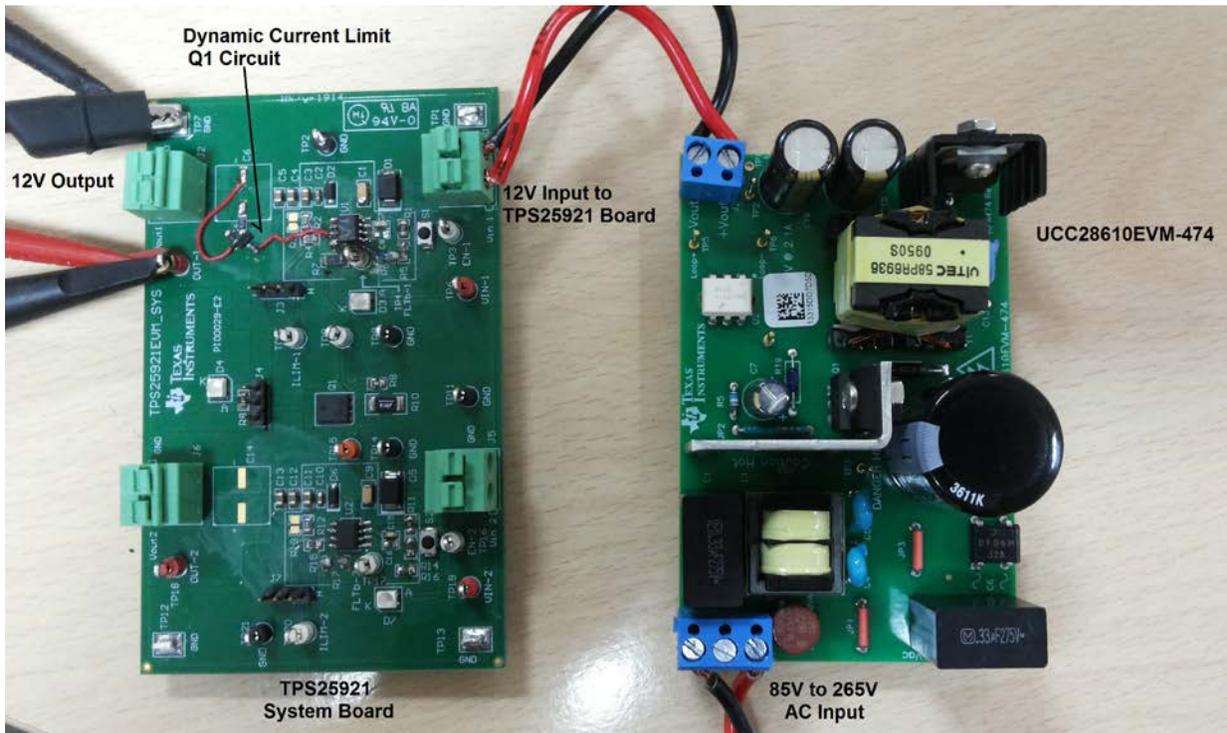


Figure 2 Test Set-up made by using TPS25921 System Board and UCC28610 EVM

3. Test Results

Test setup Precision Power Limiting Solution

- Vin from AC/DC converter (UCC28610EVM-474) = 12V@2.5A
- Output Voltage from TPS25921 system board = 12V
- TPS25921 EVM current limit set by RILIM= 1.5A
- Output Load Variation- 1A to 1.5A
- Additional power supply used for the test – 0-20V,10A

Scope label Information

- VIN- Input supply voltage to TPS25921 system board.
- IN= Iout = Load current
- Vout – Load voltage
- Pout – Power delivered to the load with varying load current or volatge

Test Result 1:

The input voltage is set to 12V and load current (Iout) is varied from 1A to 1.25A, the figure 3 show the dymanic adjustment of the current limit to limit output power when load current is incread beyond 1.25A and load power is limited to 15W.The device enters retry-mode when it reaches the adjusted power limit.

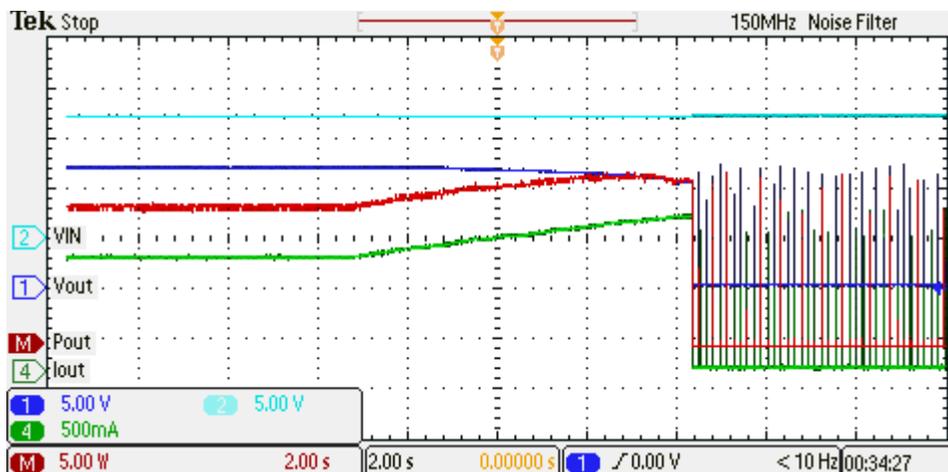


Figure 3: Load Power is limited to 15W for VIN= 12V, Iout varied from 1 to beyond 1.25A

Test Result 2:

In this case the input voltage is set to 10V and load current (I_{out}) is varied from 1.0A to 1.5A. Figure 4 shows this design adjusts the current limit and limits the output power at 15W, when load current is increased beyond 1.5A.

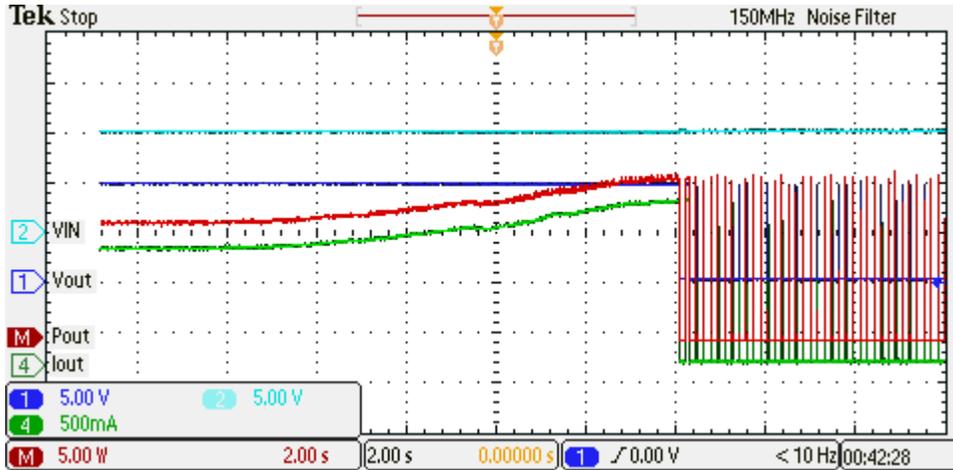


Figure 4: Load Power limited to 15W, for V_{IN} = 10V and I_{out} is increased from 1A to beyond 1.5A

Test Result 3:

In this case, the input voltage is set to 15V and load current (I_{out}) is varied from 0.5A to 1.0A and figure 5 show the dynamic power limiting feature of the solution limits the power at 15W, when load current is increased beyond 1A. This is shown in figure 5.

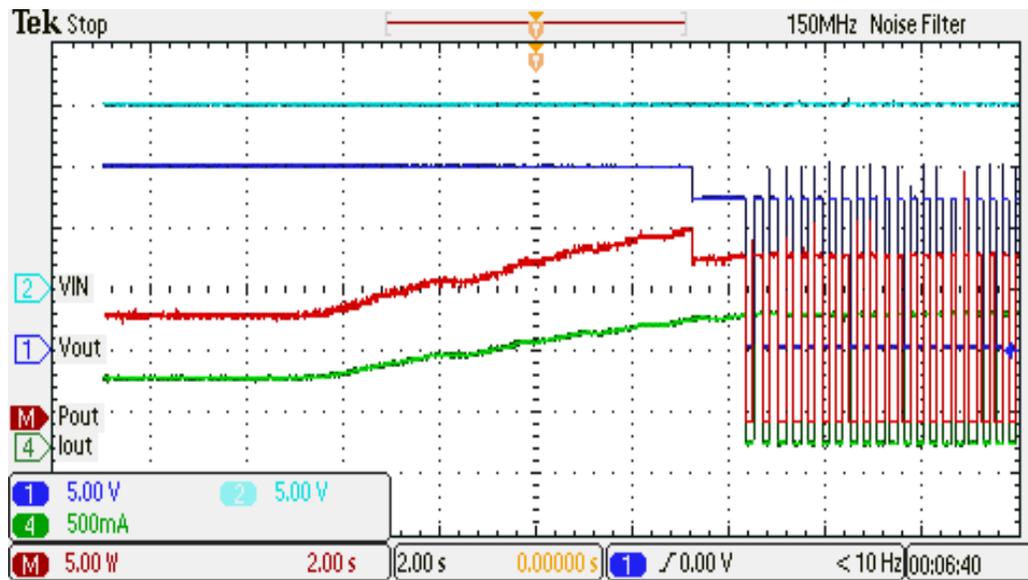


Figure 5: Load Power limits at 15W, for V_{IN} = 15V, I_{out} is increased from 0.5A to beyond 1A

Test Result 4:

Figure 6, shows, Input voltage is varied from 8V to 15V at the constant load ($I_{out} = 1.1A$) and demonstrates that V_{out} start falling when load power goes beyond 15W. This also shows, the current limit is not adjusted until load power exceeding 15W. The device enters retry-mode when it reach the adjusted power limit.

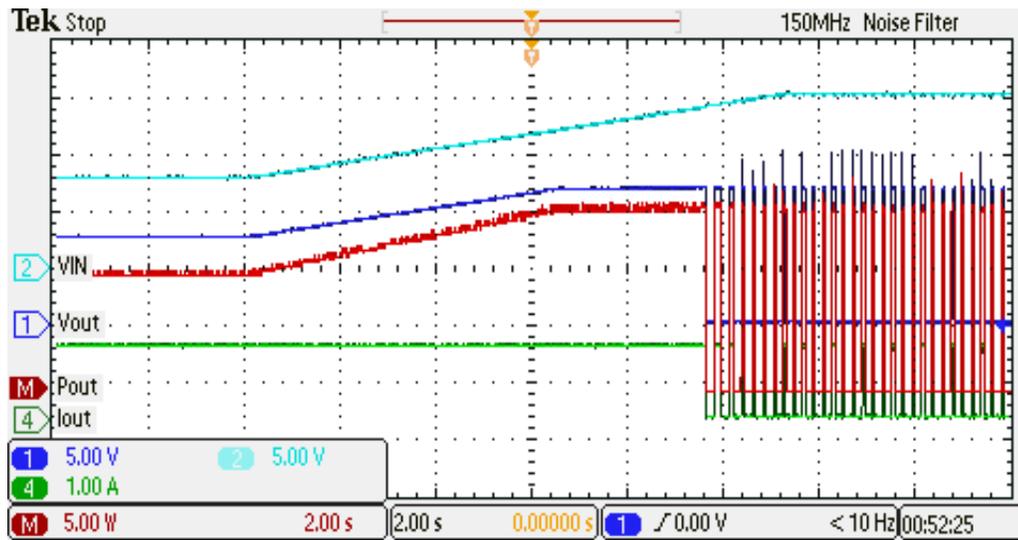


Figure 6 : Load Power limit at 15W, for VIN= 8V to 15V @ 1.1A load

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated