

TI Designs: Verified Design

Reinforced Isolated M-LVDS Transceiver



TI Designs

TI Designs are analog solutions created by TI's analog experts. Verified Designs offer theory, component selection, simulation, complete PCB schematic and layout, bill of materials and measured performance of useful circuits.

Circuit Description

This reference design combines TI's ISO7842 reinforced digital isolator with the SN65MLVD203 transceiver to create a reinforced, isolated, full-duplex, 100 Mbps M-LVDS transceiver node.

An isolated DC-DC converter provides a power supply across the isolation barrier utilizing the push-pull converter principle.


Design Resources

- [Design Archive](#)
- [ISO7842](#)
- [SN65MLVD203](#)
- [SN6501](#)
- [TPS76333](#)

- All Design Files
- Product Folder
- Product Folder
- Product Folder
- Product Folder



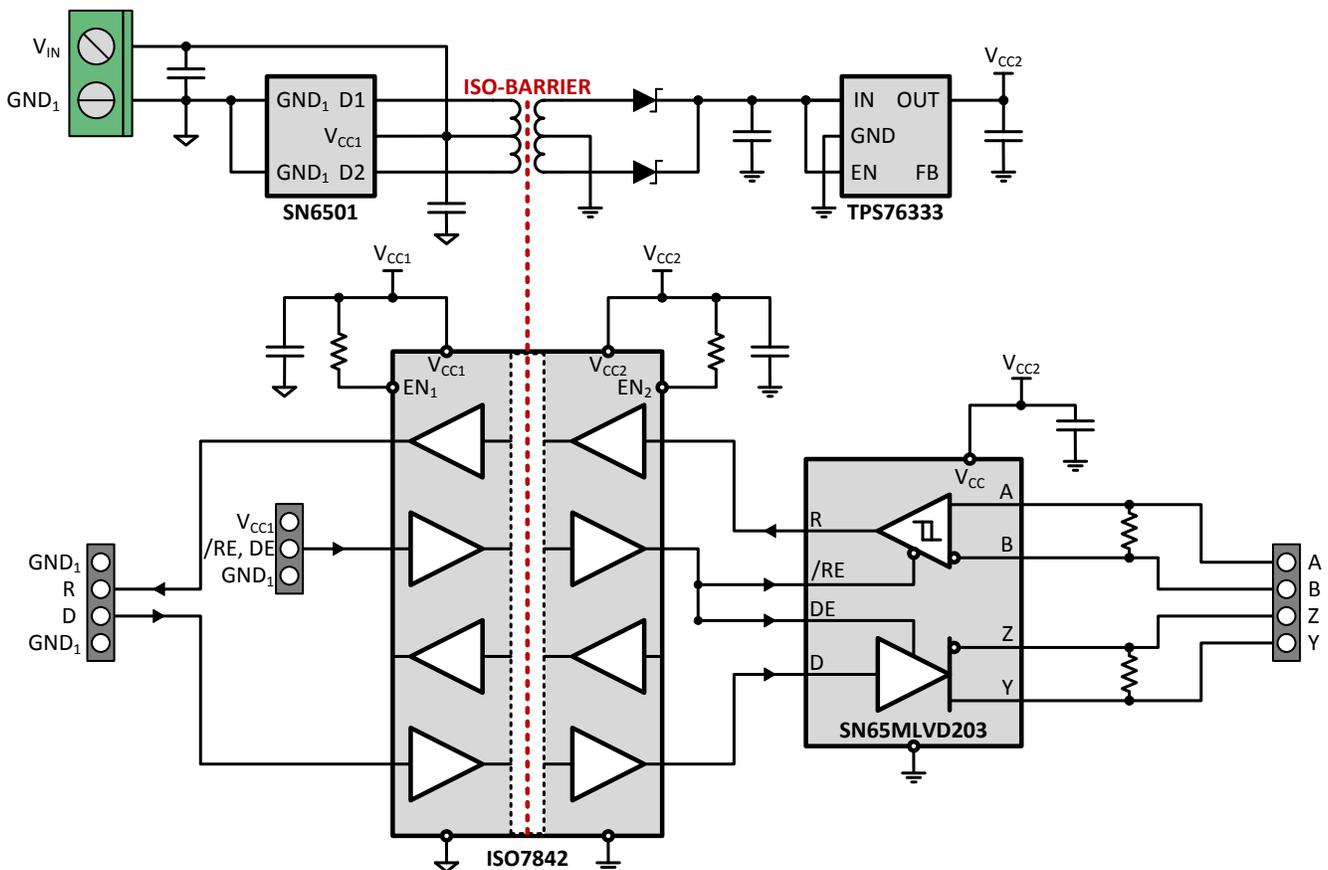[Ask The Analog Experts](#)
WEBENCH® Design Center



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments
WEBENCH is a registered trademark of Texas Instruments

1 Design Summary

1.1 Overview

Isolation is a means of preventing DC and unwanted AC currents between two parts of a system, while allowing signal and power transfer between the two sections. To make systems compact and lower-cost, it is desirable to have only one level of isolation, while providing the required electrical strength, reliability, and shock protection of two levels of basic isolation. This is referred to as *reinforced isolation*.

LVDS is a high speed differential signaling standard that achieves high data rates over long distances at low power. The M-LVDS standard extends LVDS to support multi-point applications.

Modern isolation system architectures are moving toward consolidating multiple low-speed channels into fewer high speed channels in order to reduce the number of isolated channels, and thus reduce cost and conserve board area. CMOS signaling at high data rates has limited reach, large power consumption, and large electromagnetic emissions. Beyond 50 Mbps, LVDS is a suitable choice, and introduces the need for isolated LVDS designs.

An isolated LVDS design combines a high-speed digital isolator for isolation, and an LVDS transceiver for high-speed communication over long distances.

This reference design demonstrates a reinforced isolated M-LVDS transceiver node consisting of TI's ISO7842 reinforced digital isolator and the SN65MLVD203 full-duplex M-LVDS transceiver. An isolated DC-DC converter provides a power supply across the isolation barrier using the SN6501 transformer driver.

1.2 Features

The M-LVDS transceiver node is designed to meet the following specifications:

- Reinforced isolation: $V_{ISO} = 5 \text{ kV}_{RMS}$
- M-LVDS common mode range: -1V to 3.4V
- Data rate up to 100 Mbps

2 Design Considerations

2.1 M-LVDS Transceiver

The SN65MLVD203 is a full-duplex MLVDS optimized for signaling rates up to 200 Mbps. The driver supports multipoint buses presenting as low as 30 Ω , and the driver transition times are controlled to allow for stubs off of the trunk of an MLVDS network.

2.2 Digital Isolator

The control side of the SN65MLVD203 is isolated from the node controller via a four-channel, digital isolator, ISO7841/2, providing isolation with the following specifications:

- $V_{ISO} = 5.7 \text{ kV}_{RMS}$
- $V_{SURGE} = 12.8 \text{ kV}$
- $V_{IOTM} = 8000 \text{ V}_{PK}$
- $V_{IORM}/V_{IOWM} = 1.5 \text{ kV}_{RMS}/2121 \text{ V}_{PK}$

This isolator utilizes capacitive isolation with silicon dioxide (SiO₂) as dielectric. Digital capacitive isolators are industry's most reliable and most precise, low-power isolators.

The ISO7841 is ideal for half- and full-duplex transceivers which require independent control lines for the driver and receiver enable inputs. Alternatively, the driver and receiver enable pins may be controlled with a single signal, allowing the fourth channel of the ISO7841 or ISO7842 to transmit additional data. This design includes multiple 0 Ω resistors to accommodate both the ISO7841 and ISO7842.

2.3 Power Supply

The isolated DC-DC power supply converter utilizes the push-pull converter principle. The transformer driver SN6501 drives an isolated transformer with center-tap. The transformer output is rectified by two Schottky diodes (D1, D2) and capacitor (C3). The subsequent low dropout regulator, TPS76333, provides a regulated 3.3V output for up to 150mA output current. For best stability and lowest ripple, a low-ESR, 4.7μF ceramic capacitor (C4) buffers the regulator output.

3 Measurement

3.1 Data Transmission

For point-to-point applications, only one transceiver must be isolated to provide reinforced isolation. Using one non-isolated transceiver reduces the total jitter of the signal path.

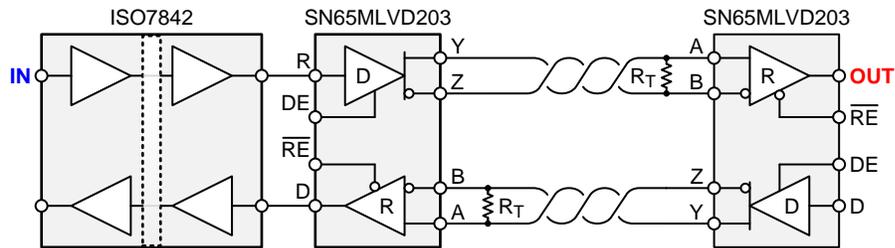


Figure 1: Point-to-point eye diagram measurement

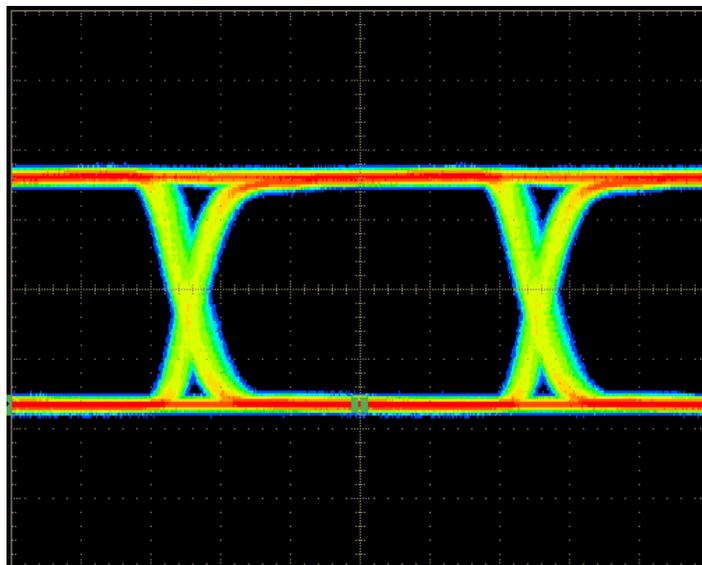


Figure 2: Eye diagram – 100Mbps

For multipoint applications, each transceiver must be isolated from the bus. Total jitter, therefore, consists of a driver, a receiver, and two isolator channels.

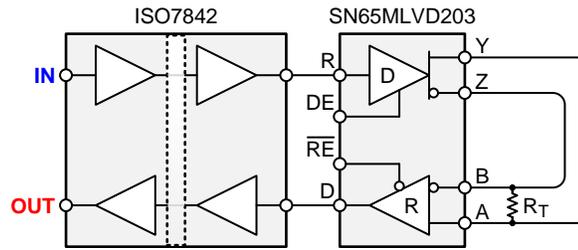


Figure 3: Multipoint eye diagram measurement

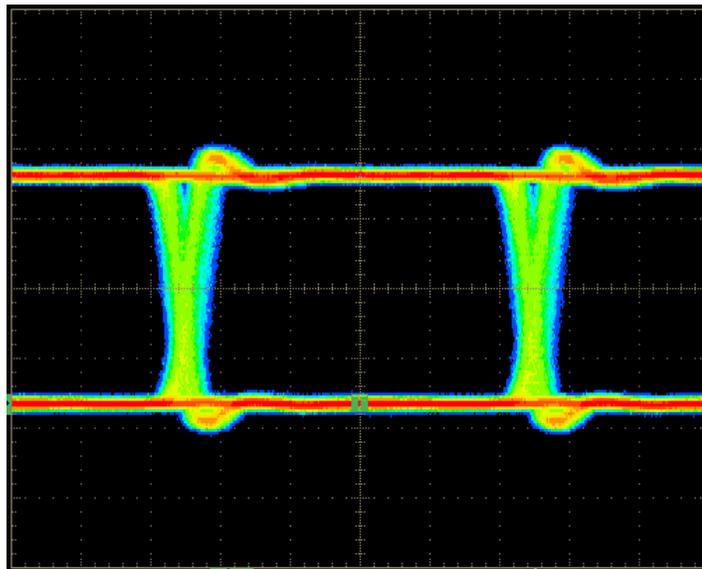


Figure 4: Eye diagram – 100Mbps

4 PCB Design

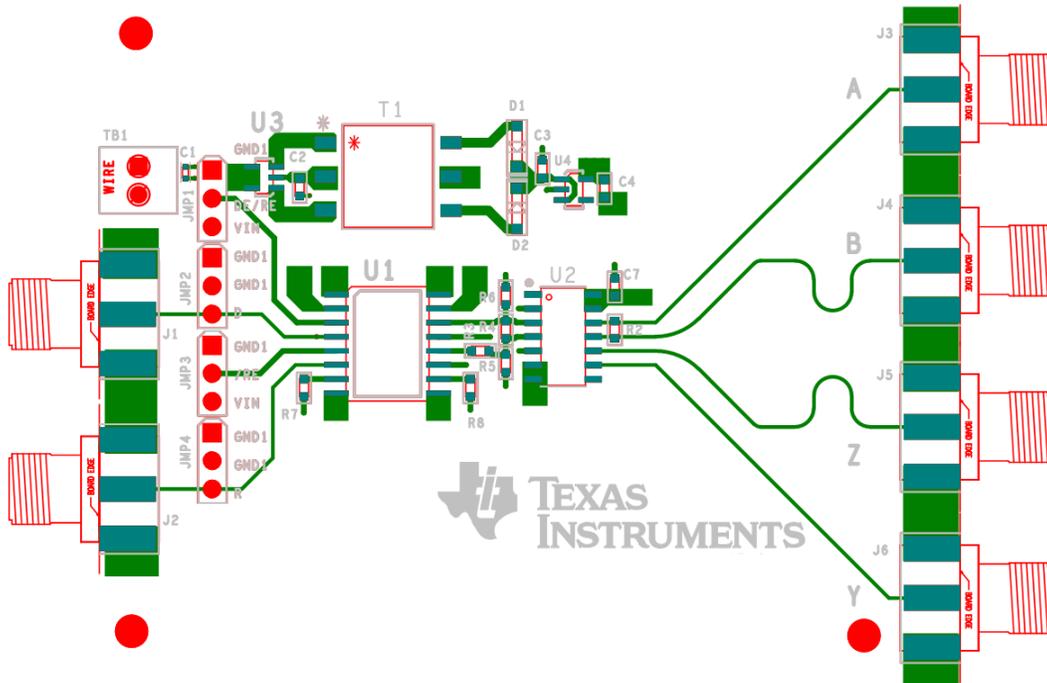


Figure 6: PCB layout top

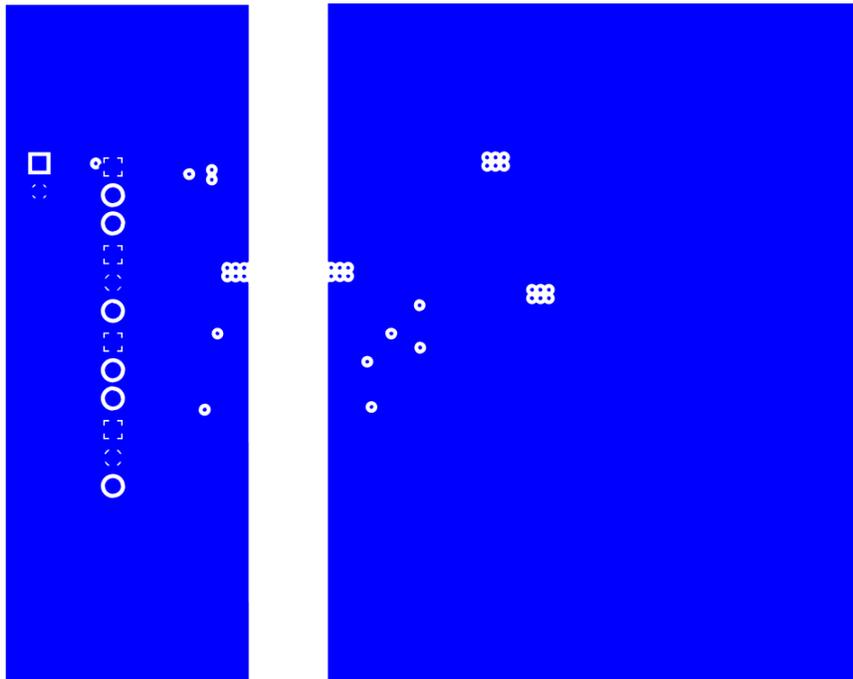


Figure 7: PCB layout ground

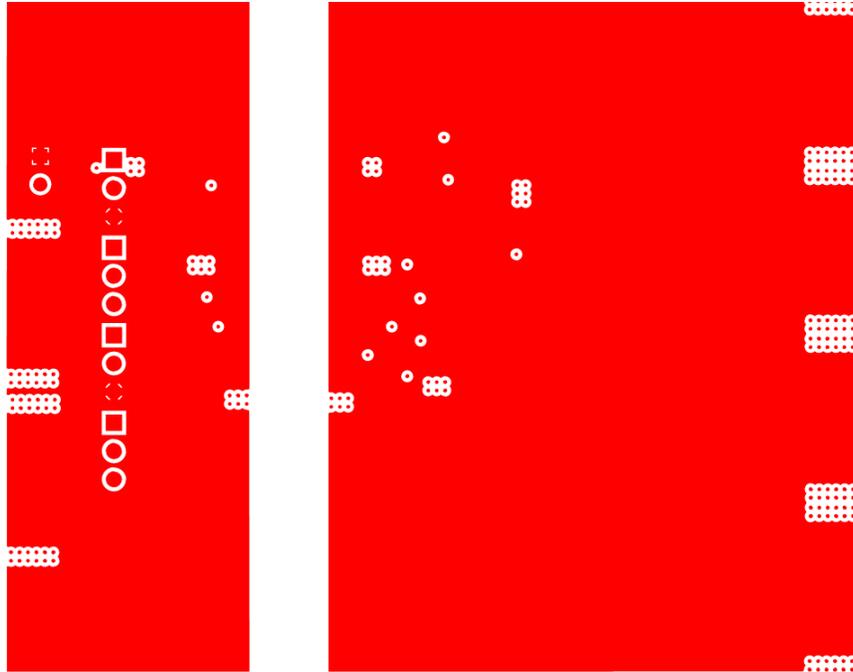


Figure 8: PCB layout power

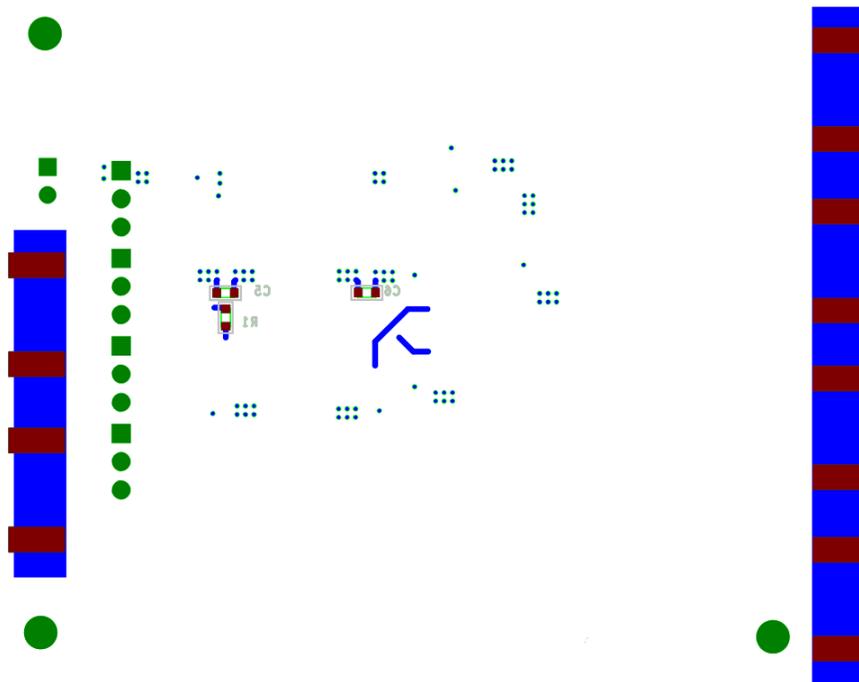


Figure 9: PCB layout bottom

5 References

1. *LVDS Owner's Manual*, [SNLA187](#)
2. *Introduction to M-LVDS (TIA/EIA-899)*, Peffers 2013, [SLLA108A](#)

6 Appendix

6.1 Schematic

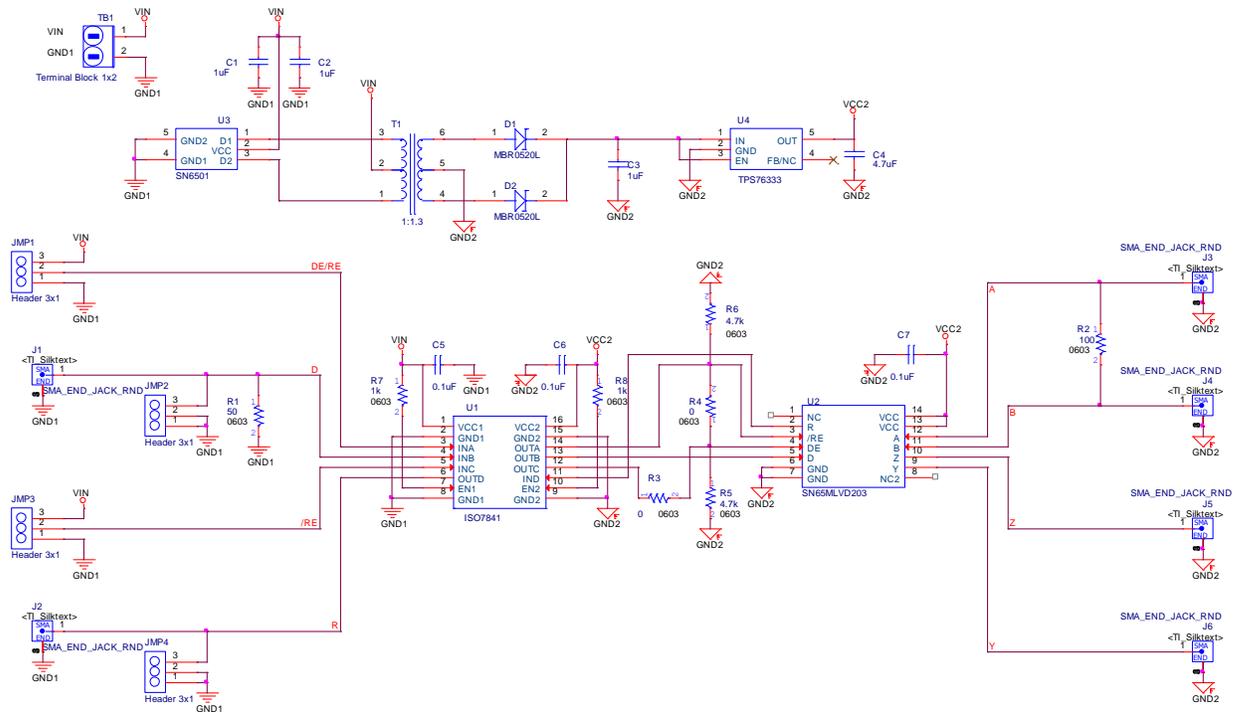


Figure 10: Reinforced isolated MLVDS transceiver

6.2 Bill of Materials

Table 1: Isolated auto-polarity RS-485 transceiver Bill of Materials

Item	Quantity	Reference	Part	Footprint	Manufacturer	Manufacturer Part Number
1	1	C1	1uF	0402	Taiyo Yuden	LMK105BJ105KV-F
2	2	C2, C3	1uF	0603	TDK	C1608X7R1C105K
3	1	C4	4.7uF	0603	TDK	C1608X5R0J475K
4	2	C5, C6, C7	0.1uF	0603		
5	2	D1, D2	MBR0520L	SOD-123	ON-Semi	MBR0520LT1G
6	6	J1, J2, J3, J4, J5, J6	SMA_END_JACK_RND		Johnson Components	142-0701-801
7	4	JMP1, JMP2, JMP3, JMP4	Header 3x1			
8	1	R1	50	0603		
9	1	R2	100	0603		
10	1	R3	DNI	0603		
11	1	R4	0	0603		
12	2	R5, R6	4.7k	0603		
13	2	R7, R8	1k	0603		
14	1	T1	1:1.3	SMT	Würth Electronics	750313638
15	1	TB1	Terminal Block 1x2			
16	1	U1	ISO7842	16DW	Texas Instruments	ISO7842DW
17	1	U2	SN65MLVD203	SOIC-14	Texas Instruments	SN65MLVD203DR
18	1	U3	SN6501	SOT-23	Texas Instruments	SN6501DBVR
19	1	U4	TPS76333	SOT-23	Texas Instruments	TPS76333DBVR

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.