

PMP10600 Test Report

Contents

- 1) Diagram
- 2) Board Photos
- 3) Startup
- 4) Efficiency
- 5) Load Regulation
- 6) Output Ripple Voltage (Full Load)
- 7) Load Transients
- 8) Thermal Images

Figures

1) Block Diagram

Zynq 5w


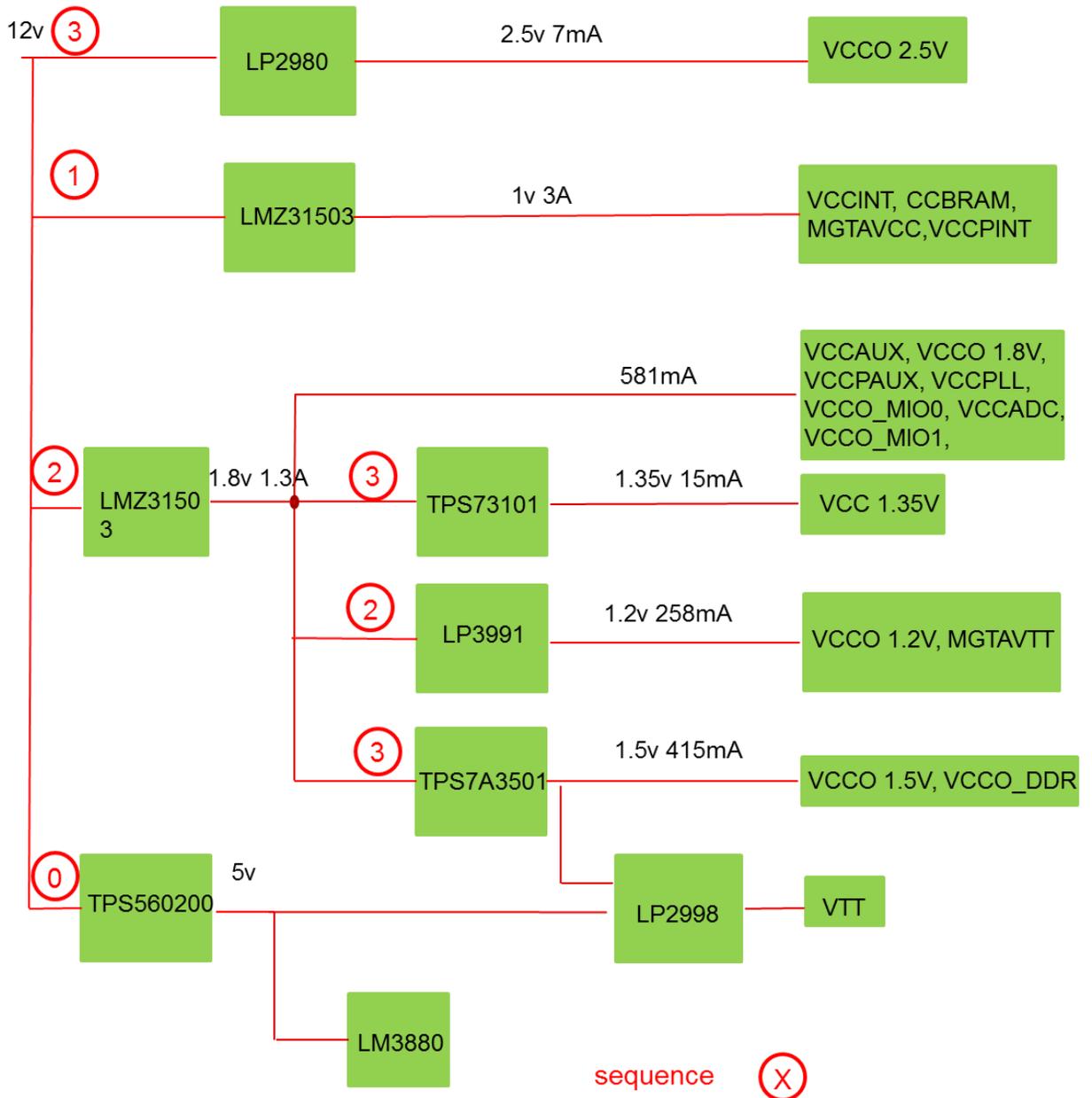


Figure 1. Block Diagram


3) Startup Waveforms

one LM3880 is used for power sequencing as shown in figures 4, 5,

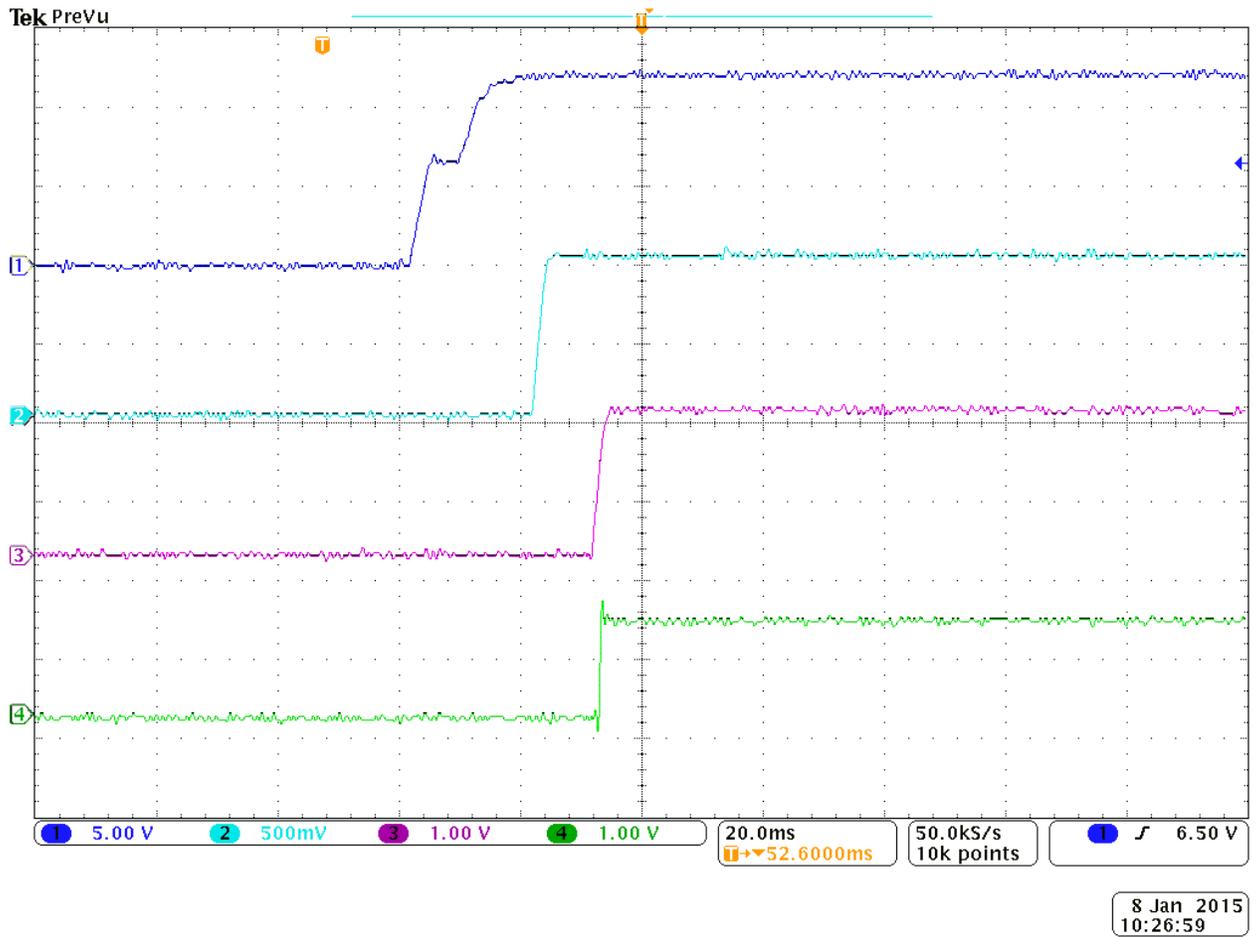

Ch.1: VIN
 Ch.2: VCCINT
 Ch.3: VCCAUX
 Ch.4: VCCO 1.2V

Figure 4. Startup Waveform

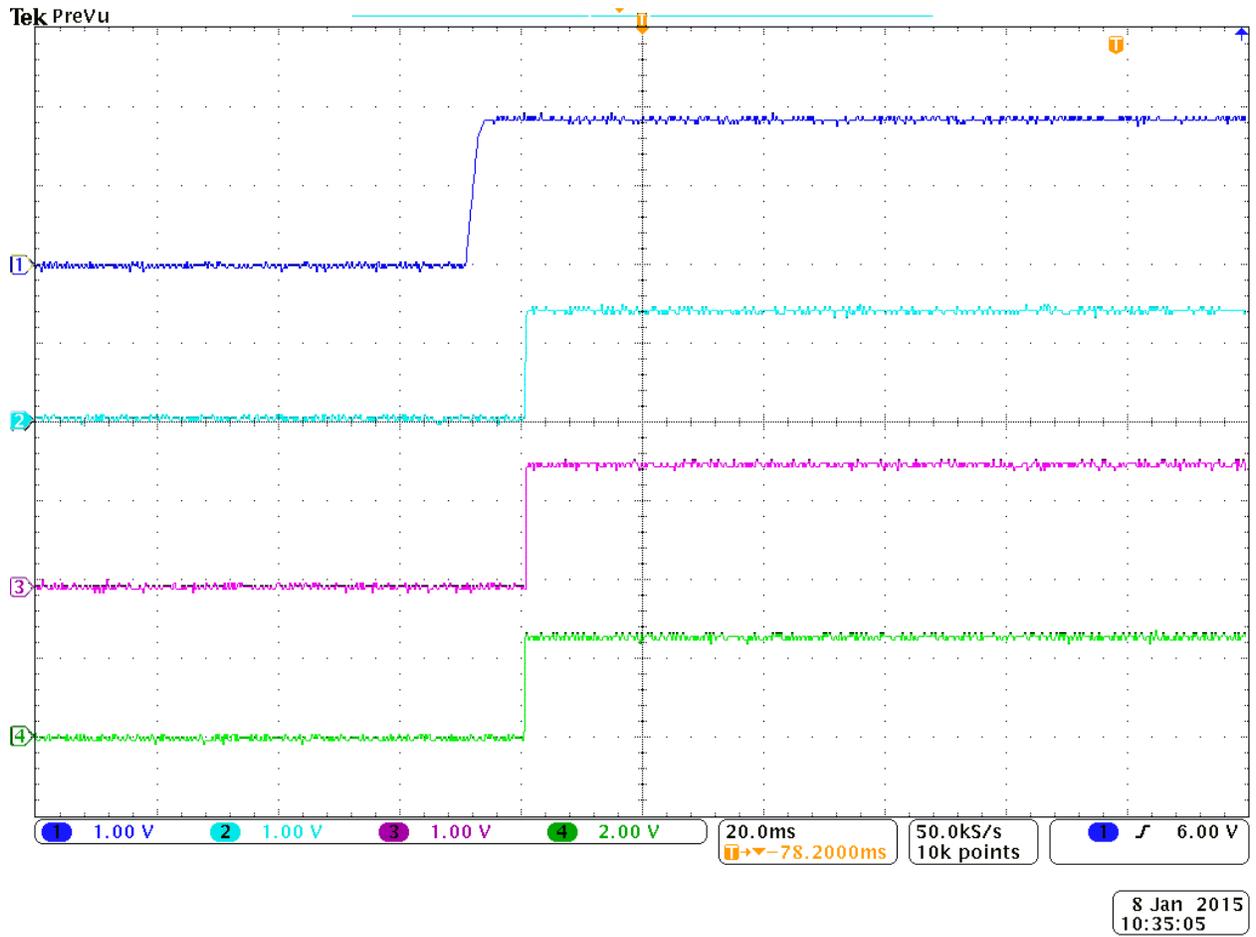

- Ch.1: VCCAUX
- Ch.2: VCC 1.35V
- Ch.3: VCCO 1.5V
- Ch.4: VCCO 2.5V

Figure 5. Startup Waveform

4) Efficiency

The efficiency of the converters is shown in the figures below. The input voltage is set to 12V.

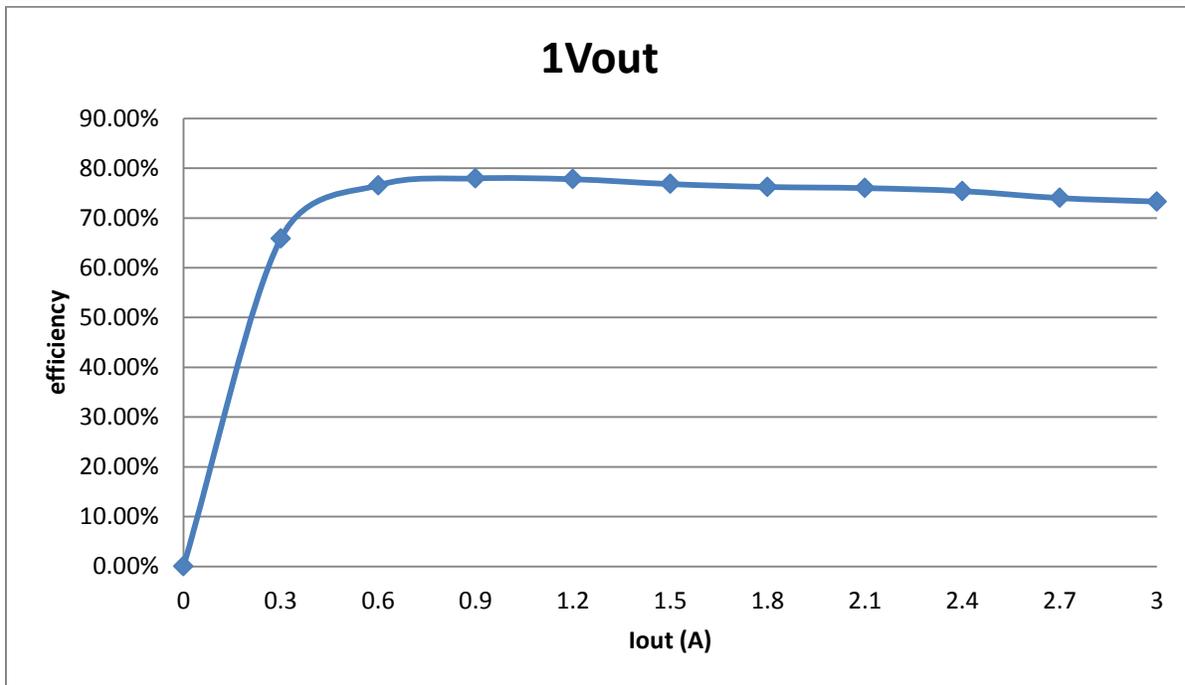


Figure 6. VIN = 12V, VCCINT Efficiency

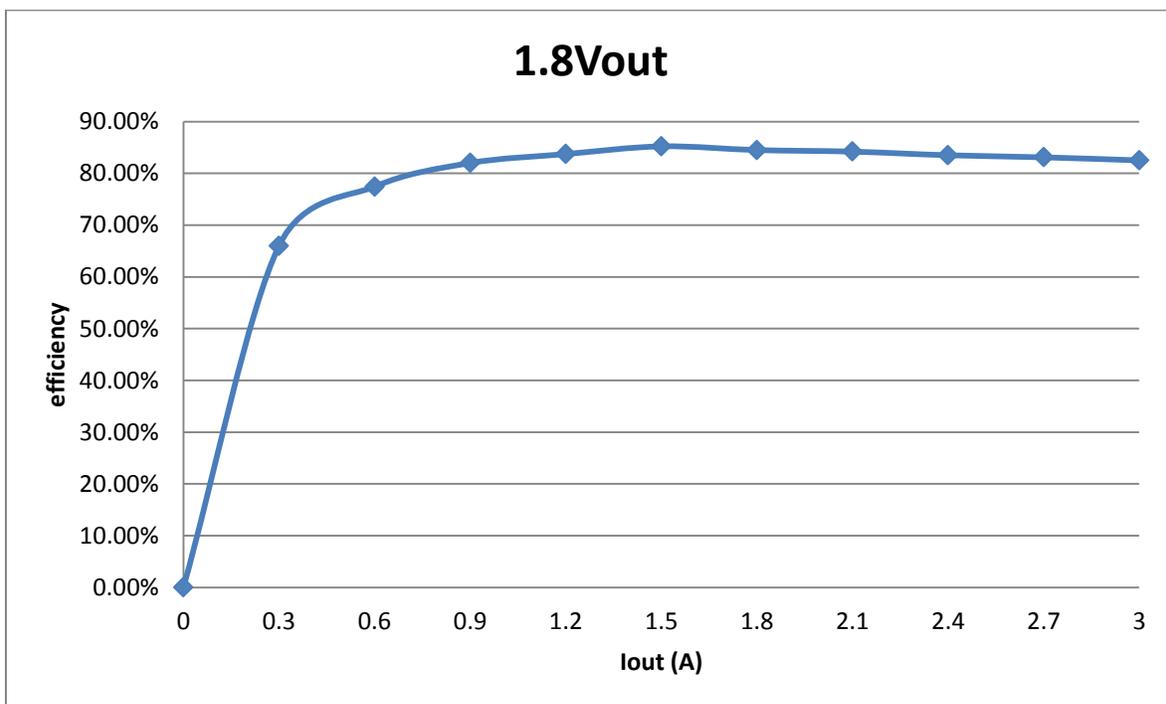


Figure 7. VIN = 12V, VCCAUX Efficiency

5) Load Regulation

The images below show the output load regulation. The input voltage is 12V.

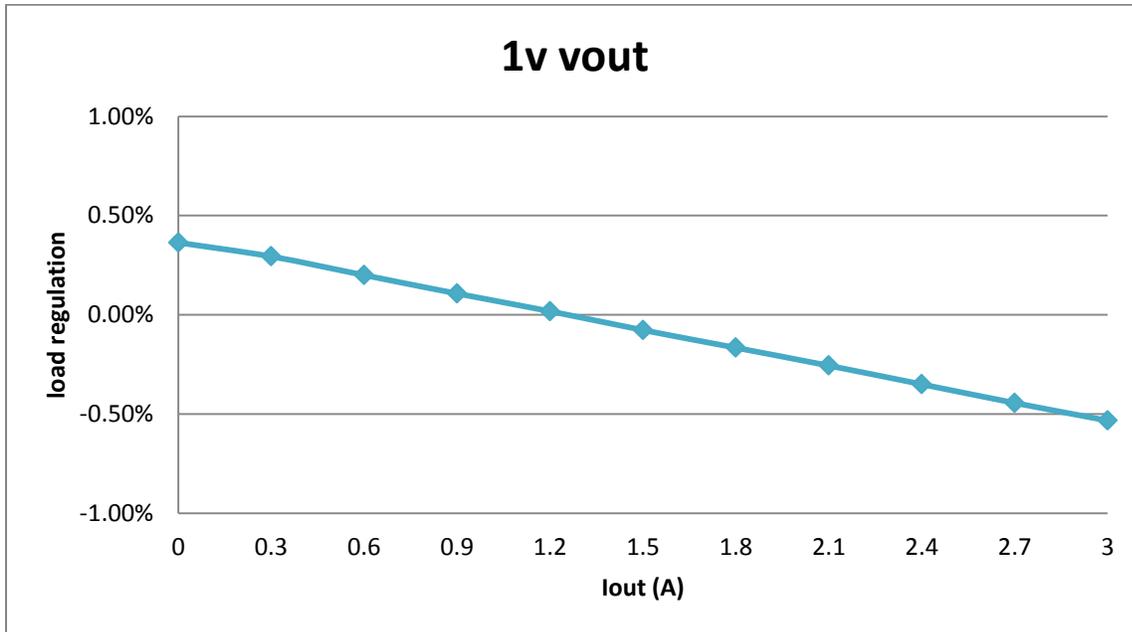


Figure 8. VIN = 12V, VCCINT Load Regulation

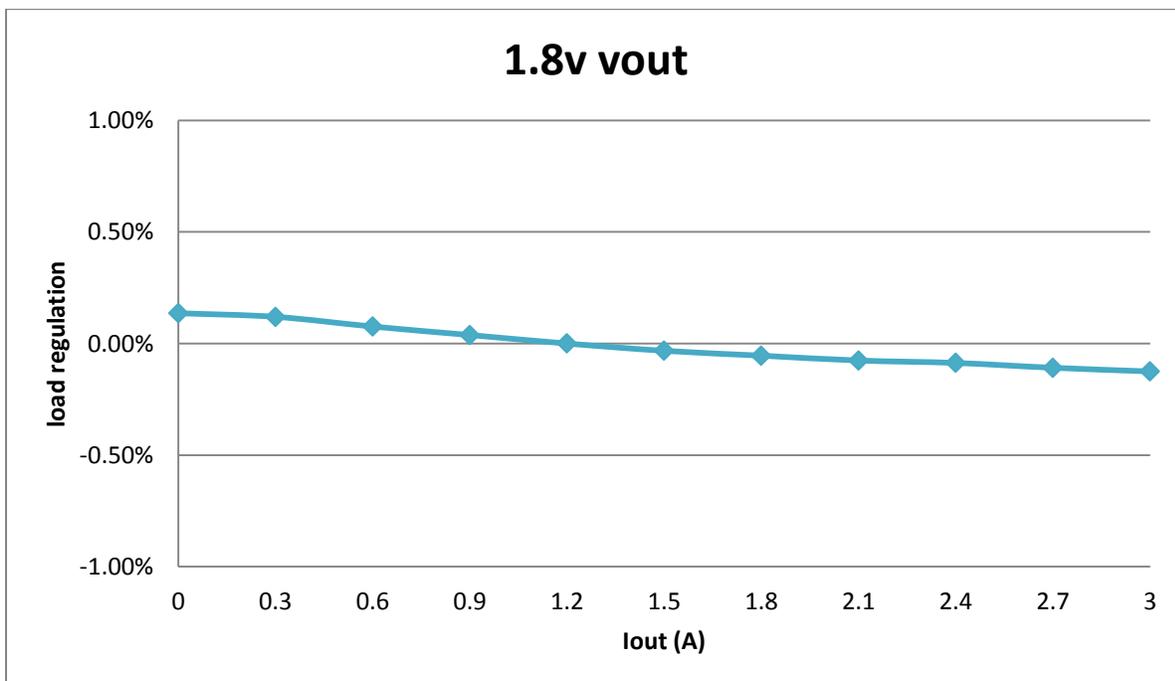


Figure 9. VIN = 12V, VCCAUX Load Regulation

6) Output Voltage Ripple

The images below shows the output voltage ripple when load is fully applied. The input voltage is 12V.

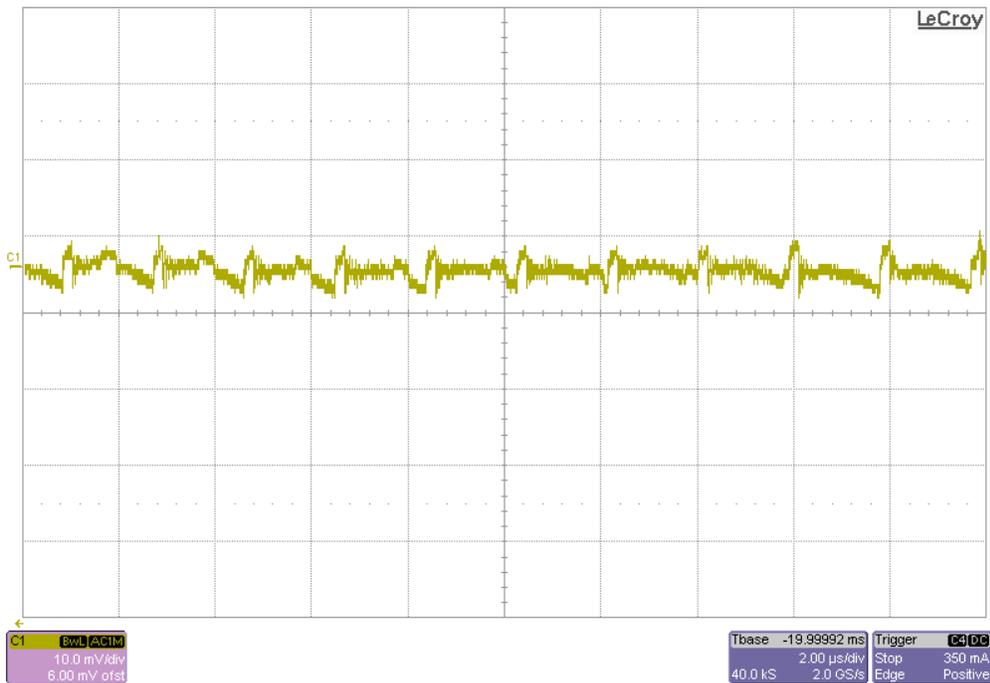


Figure 10. VIN = 12V, VCCINT Output Ripple @ IOOUT = 3A

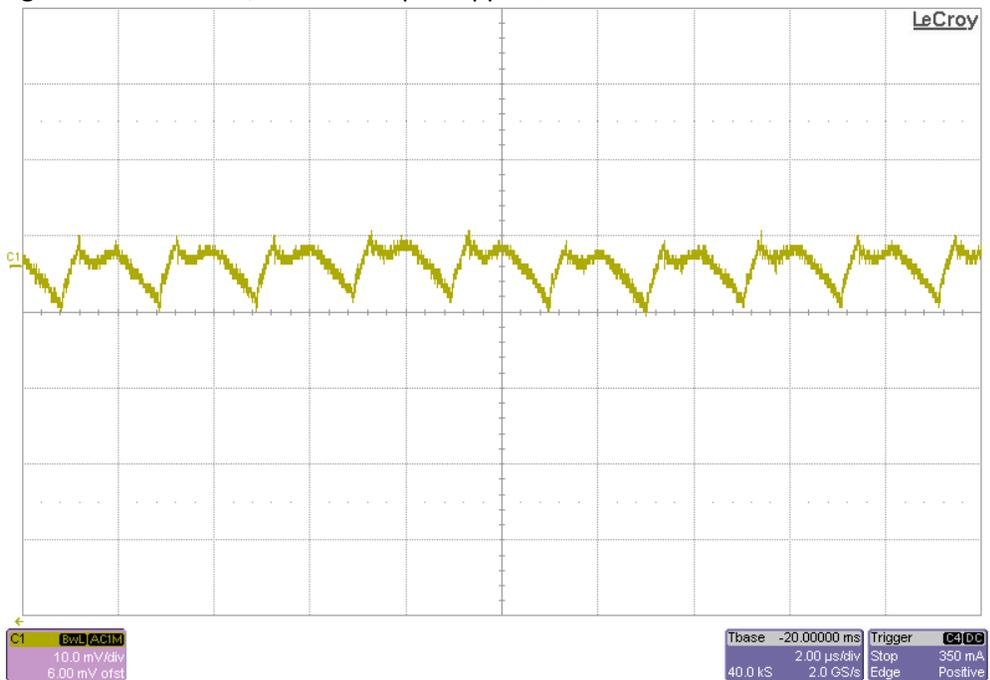


Figure 11. VIN = 12V, VCCAUX Output Ripple @ IOOUT = 3A

7) Load Transients

The transient response of the converters is shown below. The input voltage is 12V. The output current is pulsed from 0 to 50% load.

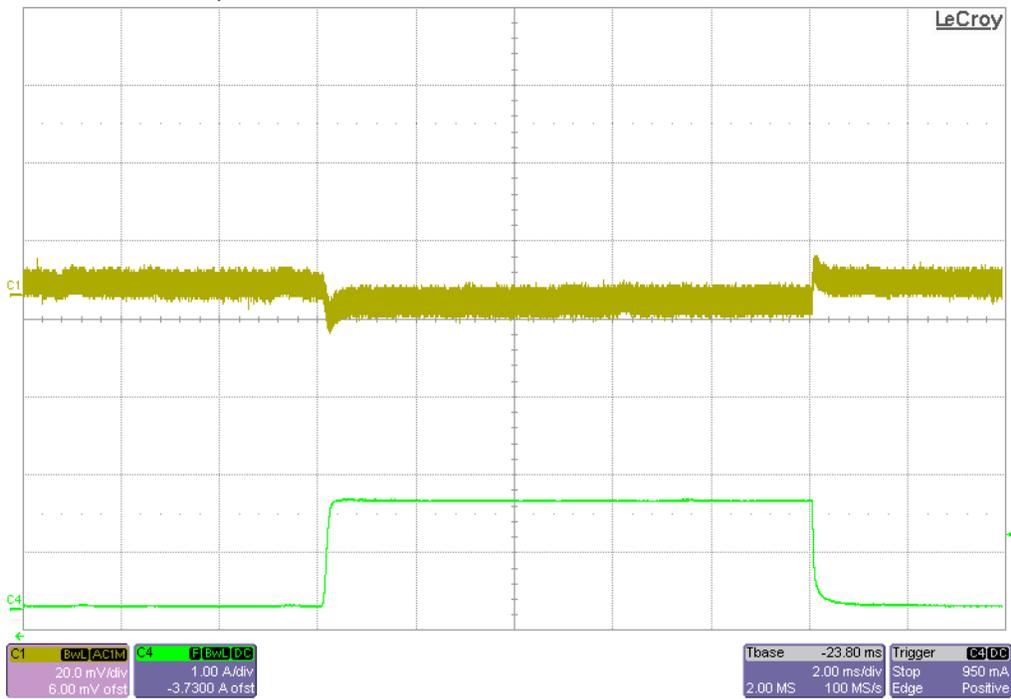


Figure 12. VIN = 12V, VCCINT Load Transient slew rate=1A/us

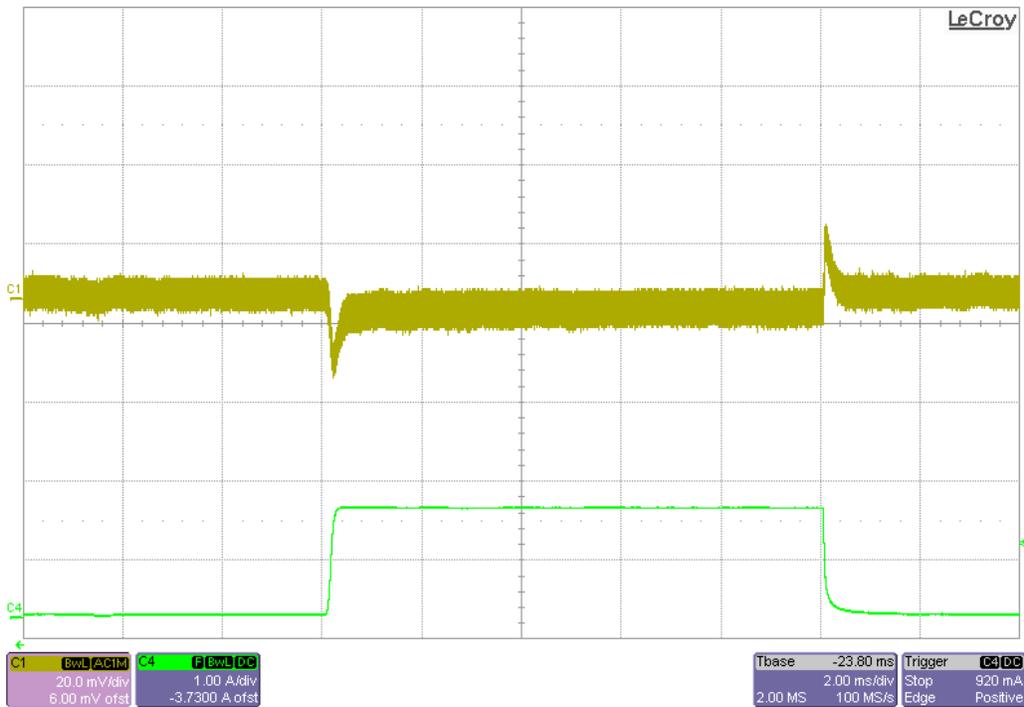


Figure 13. VIN = 12V, VCCAUX Load Transient

8) Thermal Image

Thermal images at full load of each device are shown below, the remaining rails are not drawing any current during these tests. The input voltage is 12V.

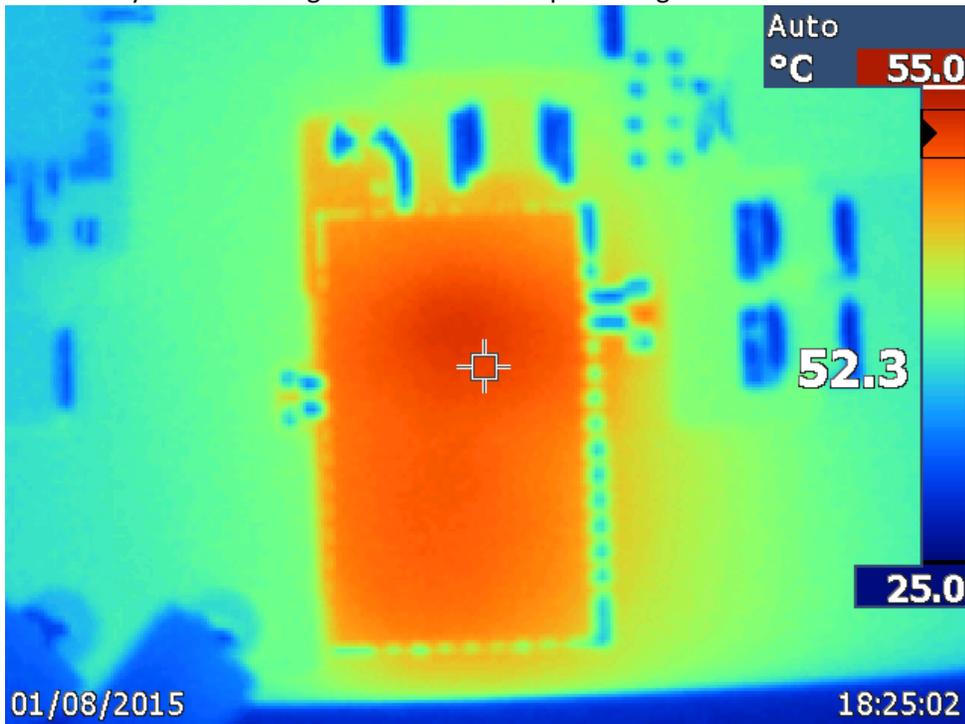


Figure 14. VIN = 12V, VCCINT Thermal Image @ Full Load

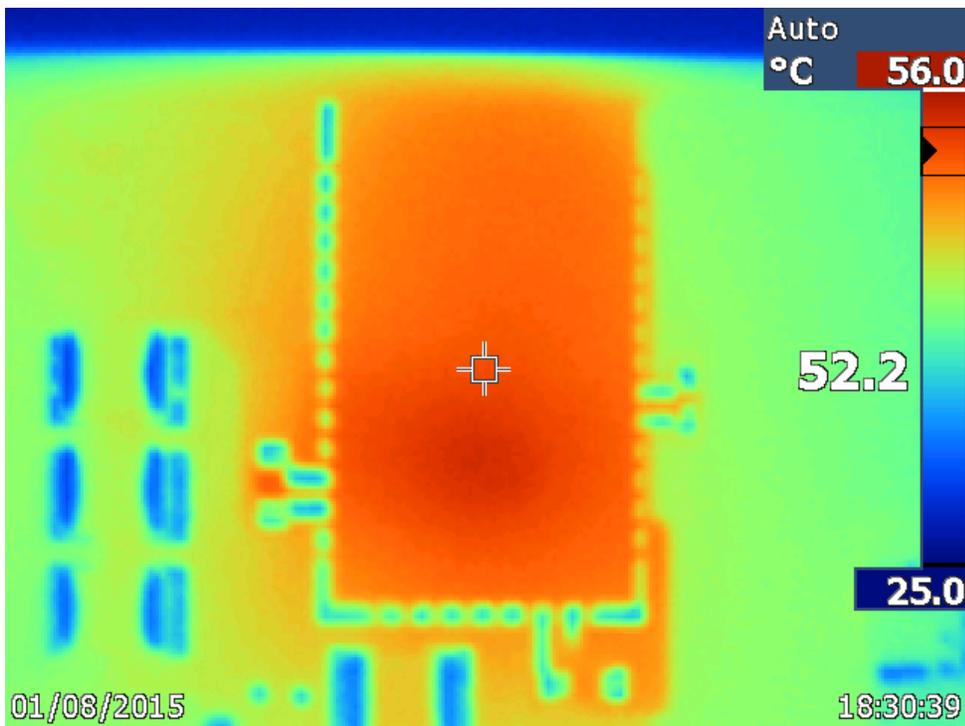


Figure 15. VIN = 12V, VCCAUX Thermal Image @ Full Load

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated