TI Designs

16-Bit 1-Gsps Digitizer Reference Design With AC and DC Coupled Variable Gain Amplifier



TI Designs

TI Designs provide the foundation that you need including methodology, testing and design files to quickly evaluate and customize the system. TI Designs help *you* accelerate your time to market.

Design Resources

TSW54J60EVM Product Folder

ADS54J60EVM Product Folder


LMH6401EVM Product Folder

TSW54J60 Design Package EVM Design Package

LMH6401 Design Package EVM Design Package



ASK Our E2E Experts

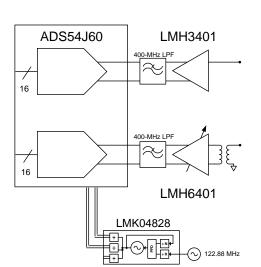

Design Features

- Flexible Transformer Coupled Analog Input on the LMH6401 Path to Allow for a Variety of Source and Frequencies
- Options for AC or DC Coupling, Single-Ended or Differential Inputs
- Easy to Use Software GUI to Configure the ADS54J60, LMH6401 and LMK04828 for a Variety of Configurations Through a USB Interface
- Quickly Evaluate ADC Performance Through High-Speed Data Converter Pro Software
- Simple Connections to TSW14J56EVM Capture Card

Featured Applications

- · Radar and Antenna Arrays
- Broadband Wireless
- Cable CMTS, DOCSIS 3.1 Receivers
- Software Defined Radio (SDR)
- Digitizers



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

All trademarks are the property of their respective owners.



Circuit Description www.ti.com

1 Circuit Description

This reference design discusses the use and performance of the digital variable-gain high-speed amplifier, the LMH6401 to drive the high-speed analog-to-digital converter (ADC), the ADS54J60 device. Different options for common-mode voltages, power supplies, and interfaces are discussed and measured, including AC-coupling and DC-coupling, to meet the requirements for a variety of applications.

This type of circuit may be used in software defined radio, military communications, test equipment, cable headend receiver, radar receiver and digitizer applications.



www.ti.com Introduction

2 Introduction

This reference design, the TSW54J60EVM, serves as a comprehensive summary of the performance and trade-offs when driving an ADC with high-speed amplifiers. A printed-circuit board was developed in order to test different setups in AC and DC coupled applications. This board consists of an ADS54J60 device, which is a dual-channel, 16-Bit, 1-GSPS ADC, and two high-speed fully-differential amplifiers: the LMH3401 (Fixed gain) and the LMH6401 (Digital variable gain). This board uses the LMH6401 amplifier to drive one channel of the ADC and a LMH3401 to drive the other channel. The board includes a jitter-cleaning clock generator (LMK04828), USB interface to allow operation with TI's High Speed Data Converter Pro GUI, and TI power solution LDO's and switchers. The JESD204B standard interface allows the EVM to be used with TI's TSW14J56EVM capture board or other JESD204B compatible platforms for data analysis.

The LMH6401 is a wideband, digitally-controlled, variable-gain amplifier (DVGA) designed for dc to radio frequency (RF), intermediate frequency (IF) and high-speed time-domain applications. The device is an ideal analog-to-digital converter (ADC) driver for dc- or ac-coupled applications that require an automatic gain control (AGC). The device supports both single- and split- supply operation for driving an ADC. A common- mode reference input pin is provided to align the amplifier output common-mode with the ADC input requirements.

The LMH6401 gain ranges from 26dB to -6dB in 1dB steps achieving a 32dB dynamic range. To reduce gain errors from one gain setting to the other, it is important to note that the change in input impedance or input return loss of the amplifier across gain steps should be minimal. The LMH6401 exhibits constant input impedance across gain settings making it suitable for wide-band automatic gain control (AGC) applications.

This document includes the general considerations when driving an ADC with an amplifier, such as common-mode voltages, power supplies, AC-coupling and DC-coupling, and filter interfaces. This document also includes a discussion of the measured performance of the LMH6401 and ADS54J60 interface. This includes IMD3 measurements as well as SNR and SFDR. This TIDesign will only focus on the LMH6401 channel driving the ADS54J60. Another TIDesign will feature the LMH3401 channel driving the ADS54J60. See the TSW54J60EVM User's Guide, SLAU649A, for more information regarding operation and testing of this EVM.

3 General Considerations

3.1 AC-Coupled Configuration

AC-coupling is the configuration that TI recommends if the application does not require processing of signals close to DC. The TSW54J60 uses a 1:2 (Zo = $50-\Omega$) transformer to convert single-ended input signals to 100 Ω differential signal for the LMH6401 device. This is required since the amplifier can only be used with differential inputs. A typical application would use a differential amplifier output to drive this device. For more information regarding this type of application, refer to TI Designs document TIDA-00654, titled "Cascaded LMH5401 and LMH6401 Reference Design". The board default configuration is AC-coupled, as shown in Figure 1. Note that the impedance seen on each input pin must be balanced with no DC offset voltage. Figure 1 shows the LMH6401 AC-coupled configuration.

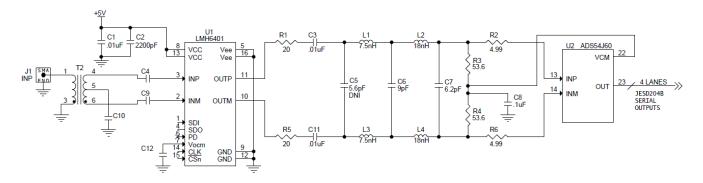


Figure 1. LMH6401 AC-Coupled Configuration



General Considerations www.ti.com

The output of the amplifier goes through a 370MHz low pass filter before connecting to the ADC. The specifications of the filter and data captured plots are shown later in this document. In AC-coupled configuration, the output common mode (CM) voltage of the amplifier output is isolated from the input CM of the ADC through the 0.01µF coupling capacitors. As a result, the output common control (VOCM) pin for the LMH6401 can be left floating or disconnected from the VCM pin of the ADS54J60. The LMH6401 output CM voltage defaults to mid-supply (2.5V in this case) if the VOCM pin is left floating. The amplifier and ADC interface has the best linearity performance when the output CM voltage of the amplifier is close to the mid-supply.

3.2 DC-Coupled Configuration

The LMH6401 path driving the ADS54J60 can be either dc- or ac-coupled at the inputs. The LMH6401 device provides excellent performance as a digitally-controlled fully differential amplifier down to DC. Figure 2 shows a typical DC-coupled configuration where a LMH6401 device is used to produce a balanced differential output signal for the ADS54J60 input.

In general, transformers are used to provide single-to-differential conversion, but these transformers are inherently band-pass in nature and cannot be used for DC-coupled applications. As a result, a common solution is to use a high speed amplifier in order to enable DC-coupling without affecting ADC performance at higher frequencies. Amplifiers offer a flexible and cost-effective solution when the application requires gain, a flat pass-band with low ripple, DC-level shifts, or a DC-coupled signal path.

In order to dc-couple the LMH6401 input path, care must be taken to ensure the common-mode voltage is set within the input common-mode range of the LMH6401. Please refer to the Electrical Characteristics table in the LMH6401 datasheet to set the input common-mode voltage within the device range. Since the LMH6401 is a fully differential amplifier, the path inputs must be driven differentially. For single-ended input source dc-coupled applications, care must be taken to select an appropriate fully-differential (such as the LMH3401 or LMH5401) that can convert single-ended signals into differential signals with minimal distortion.

When interfacing an amplifier to the ADC in dc-coupled application, it is required to match the output CM voltage of the amplifier close to the input CM voltage of the ADC. Best performance is achieved when the ADC input pins are at the same voltage as the ADC VCM pin or (INPADC + INMADC)/2 equals VCMADC. Interfacing the LMH6401 to the ADS54J60 is made easier by an option provided in the amplifier to control the output common-mode voltage using the VOCM pin of the amplifier. The LMH6401 device performance is optimal when the output common-mode voltage is within ±0.5 V of mid-supply and performance degrades outside the range when the output swing approaches clipping levels. For the ADS54J60, the input CM voltage to be maintained is close to 2.0V as specified in the ADC datasheet. The ADC input CM voltage of 2.0V makes it easier for the LMH6401 to be run on a single +5V supply and use the VOCM pin to set the output CM voltage to 2.0 V, since it is within ±0.5 V of mid-supply.

See the *TSW54J60EVM User's Guide*, section 5.2.1 of (<u>SLAU649A</u>), for more information regarding testing with this mode of operation.

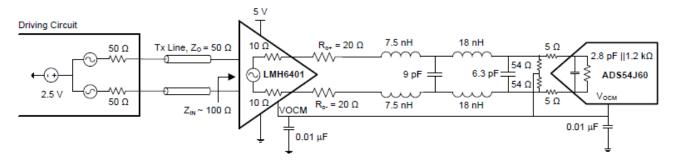


Figure 2. Interfacing LMH6401 With the ADS54J60 in the DC-Coupled Configuration



4 Common Mode Considerations

To achieve the best performance while DC-coupling an amplifier and an ADC interface, match the output CM voltage of the amplifier to the input CM voltage of the ADC. For DC-coupled applications, the LMH6401 provides an option to control the output common-mode voltage using the VOCM pin. Device performance is optimal when the output common-mode voltage is within ± 0.5 V of mid-supply and performance degrades outside the range when the output swing approaches clipping levels. The LMH6401 can achieve a maximum output swing of 6 VPPD with the output common-mode voltage centered at mid-supply. Note that by default, the output common-mode voltage is set to mid-supply before the two 10- Ω , on-chip resistor. On a single-supply operation when DC-coupling the device outputs to an ADC using common-mode level-shifting resistors, the output common-mode voltage and resistor values being calculated must include the two internal 10- Ω resistors in the equation.

Figure 3 shows where a resistor network can be used to perform the common-mode level shift. This resistor network consists of the amplifier series output resistors and pullup or pulldown resistors to a reference voltage. This resistor network introduces signal attenuation that may prevent the use of the full-scale input range of the ADC. ADCs with an input common-mode closer to the typical 2.5-V output common-mode of the LMH6401 are easier to dc-couple, and require little or no level shifting

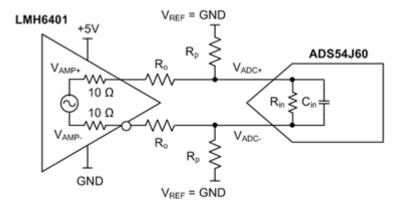


Figure 3. Resistor Network to DC Level-Shift

When operating the LMH6401 on split supplies and DC-coupling the outputs, TI recommends matching the output common-mode voltage of the LMH6401 with the input common-mode voltage of the ADC. A simple design procedure is to select the supply voltages (VS+ and VS-) such that the default output common-mode voltage being set is equal to the input common-mode voltage of the ADC.


To minimize the design complexity on the TSW54J60EVM, the LMH6401 uses a single supply (5VDC) instead of split-supplies which would be centered close to an output CM voltage of 2.5-V. This is done because the input CM voltage of the ADS54J60 is within the ±0.5 V of the LMH6401 mid-supply on a single 5-V supply.

5 Filter Design

The TSW54J60EVM follows the LMH6401 with a 370MHz 4th order Chebyshev Low Pass Filter (LPF) filter to remove out-of-band noise and harmonics aliasing into the first Nyquist zone of the ADS54J60. The filter has been designed for less than 2dB pass-band ripple with cut-off frequency at 370MHz, and stop-band attenuation of 30dB at 1GHz. The circuit is appropriately biased to match the ADC common-mode level by connecting the VCM output to the common mode termination. Figure 4 shows the filter simulated response is shown in, and Figure 5shows he measured performance of this filter.



Filter Design www.ti.com

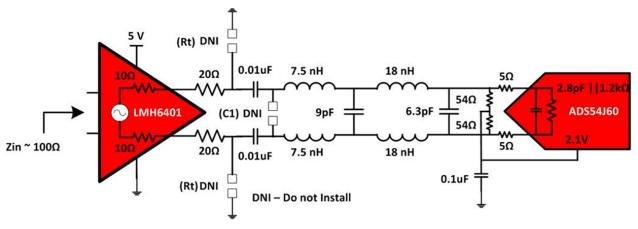

Eqn Sdd21 = 0.5*[S(2,1) + S(4,3) - S(4,1) - S(2,3)]

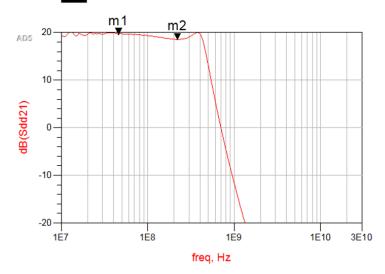


Figure 4. 370 MHz Low-Pass Filter and Simulation Response



www.ti.com Filter Design


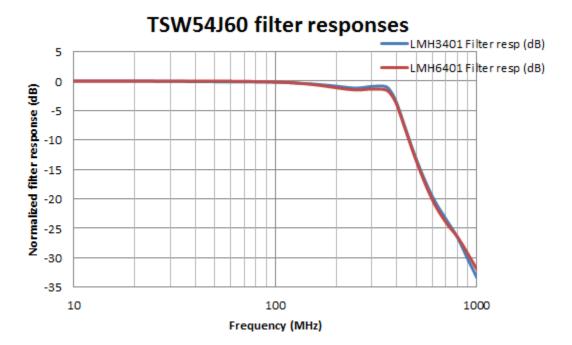


Figure 5. 370 MHz Low-Pass Filter Measured Responses

The LMH6401, as with most RF amplifiers, has two 10- Ω , on-chip resistors on each output leg to provide isolation from board parasitic at the output pins. When designing a filter between the amplifier and the interfacing circuitry (ADC), the filter source impedance must be calculated by taking into account the two 10- Ω , on-chip resistors. Table 1 shows the calculated external source impedance values (R_{O+} and R_{O-}) required for various matched filter loads (RL). An important note is that the filter design between the LMH6401 and the ADC is not limited to a matched filter, and source impedance values (R_{O+} and R_{O-}) can be reduced to achieve higher swing at the filter outputs. Achieving lower loss in the filter source impedance resistors or higher swing at the filter outputs is often desirable because the amplifier must reduce the output swing to maintain the same full-scale input at the ADC and, thus, better linearity performance.

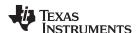

The 370-MHz, un-matched, low-pass filter between the LMH6401 and ADS54J60 is illustrated in Figure 4, with (R_{O+} and R_{O-}) set to 20 Ω and RL set to 100 Ω . Since the ADC input impedance (RL) is set to 100 Ω and the termination resistors including the two on-chip 10- Ω resistors on LMH6401 output is 60 Ω , the termination loss (or insertion loss) between the LMH6401 and ADS54J60 is close to 4-dB (or 2-dB). The termination loss is calculated by the voltage division between the ADC input and the termination resistors at the amplifier output.

$$VIN_{ADC}(diff) = Loss \times VOUT_{AMP}(diff)$$
(1)

For the LMH6401 and ADS54J60 interface, use:

Loss(dB) =
$$20 \times log10 \left(\frac{R_L}{R_L + R_{0+} + R_{0-} + 20} \right)$$
 (2)

Table 1 shows the load component values.

Table 1. Load Component Values

| LOAD (R _L) | R _{O+} AND R ₀₋ FOR A MATCHED TERMINATION | TOTAL LOAD RESISTANCE AT AMPLIFIER OUTPUT | TERMINATION LOSS |
|------------------------|--|--|------------------|
| 50 Ω | 15 Ω | 100 Ω | 6 dB |
| 100 Ω | 40 Ω | 200 Ω | 6 dB |
| 200 Ω | 90 Ω | 400 Ω | 6 dB |
| 400 Ω | 190 Ω | 800 Ω | 6 dB |
| 1 kΩ | 490 Ω | 2000 Ω | 6 dB |

6 Power Supply Consideration

The LMH6401 device can operate with either a single or dual supply, and with either DC coupling or AC coupling. The advantage of AC-coupling over DC-coupling is to offer more freedom of choice in regard to power supply. The main concern with DC coupling is ensuring that the input common-mode voltage does not violate the device operating conditions. By AC-coupling the input of the driver, the input self-biases at the level set by the output CM (V_{CM}) pin which ensures optimal operation.

If a single supply is used, AC-coupling the amplifier when driving an ADC is easier in relation to common-mode settings. The TSW54J60EVM uses a 5-V single supply configuration for both the LMH6401 and LMH3401 amplifiers.

If DC-coupling must be used with a single supply, the common-mode output of the driver must operate at VS+/2 (in this case, 2.5 V) and then DC level shifting must be used to match the common mode of the ADC. The appropriate common mode is set by using a voltage divider as described in the Section 4 section. The drawback is this method results in a loss of signal power because the amplifier must drive a larger voltage to overcome the attenuation of the voltage divider, which results in degraded performance.

The input common-mode voltage (V_{ICM}) of the DC-coupled driver input must also be considered. While the output common-mode voltage (V_{OCM}) is set at V_{CM} , V_{ICM} can have a small delta compared to V_{OCM} based on the internal feedback resistors. This delta can generate a flow-back current that wastes power in the feedback resistors. Also, based on the signal source, the delta can cause issues in some applications that may require a buffer amplifier before the fully-differential amplifier.



7 Loop Filter Component Selection

The TRF3765 requires an external loop filter for proper operation. The loop filter design is critical for achieving low closed-loop phase noise. For this design the synthesizer is operating in Fractional-N mode with a PFD (phase frequency detector) frequency of TBD. The charge pump current is set to 1.95 mA to minimize noise. The loop filter component values are given in Table 2, and are referenced to designators in .

If the application uses a split supply, an advantageous approach is to use a non-symmetric supply operation. For example, non-symmetric supply operation with a DC-coupled application driving an ADC that requires an input common mode of 2.0 V. Using +4.5 V and -0.5 V supplies will allow to set the amplifier output CM to 2.0 V.

The following summarizes the AC-coupling and DC-coupling differences between a single-supply operation and a split-supply operation.

Single Supply Operation (5 V):

AC-coupling:

- The CM is biased at 2.5 V at the output of the amplifier.
- Easily adapts to any required ADC input CM.
- Filter design between the amplifier and ADC interface is easier because the DC level shifting is not required.

DC-coupling:

The input CM of the amplifier may differ from the output CM, which leads to current leakages.

Split-supply Operation:

AC-coupling:

- The CM is biased at the output of the amplifier.
- Easily adapts to any required ADC input CM.

DC-coupling:

- Best solution if the supply is set to match the required input CM of the ADC.
- Voltage divider is not required, which leads to an easier interface configuration.
- Increases the number of supplies, which increases board space and cost.

Table 2. TRF3765 Loop Filter Components

| Fpfd (MHz) | C1 | C2 | R5 | C3 | R6 |
|------------|-------|--------|------|--------|--------|
| 1.6 | 47 pF | 560 pF | 10 K | 4.7 pF | 4.99 K |

If a modification to the PFD frequency or operational mode is required, then the loop filter may need to be modified. The Loop_Filter-CALC program available on the TI website is a great resource in determining the proper loop filter component values.



Results www.ti.com

8 Results

The measured results below were made using a TSW54J60 connected to a TSW14J56EVM and the HSDC Pro GUI. Two signal generators, band pass filters, and 3dB attenuators were used along with a power combiner for the two tests. Data was collected using frequencies ranging from 70MHz to 250MHz and LMH6401 Gain settings from 2dB to 26dB (max gain). Figure 6 shows show captured data in two formats. The two tones were separated by 1MHz. Table 3 lists the two tone test results across several frequency and gain settings. Figure 6 shows the two tone test results across several frequency and gain settings.

Table 3. Two Tone Test Results Across Several Frequency and Gain Settings Table

| GAIN (dB) | 70 M | 125 M | 150 M | 220 M | 250 M |
|--------------|-------|-------|-------|-------|--------|
| 2 | -77.5 | -85.3 | -76.2 | -74.4 | -68.06 |
| 6 | -79/4 | -77.9 | -79 | -75.3 | -69.42 |
| 11 | -79.9 | -77.9 | -80.5 | -75.9 | -69.77 |
| 15 | -81 | -79.4 | -82.9 | -77.6 | -71.33 |
| 18 | -81.1 | -78.9 | -81.9 | -76.1 | -70.32 |
| 22 | -82.6 | -79.1 | -81.8 | -77.3 | -71.98 |
| 26 | -81.5 | -79.1 | -79.5 | -76.5 | -70.05 |

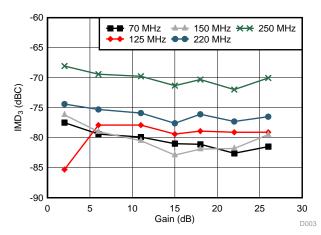


Figure 6. Two Tone Test Results Across Several Frequency and Gain Settings



www.ti.com Results

Figure 7 is a screen shot from HSDC Pro GUI of a two tone test using (169.5 MHz and 170.5 MHz) with a LMH6401 gain setting of 16 dB.

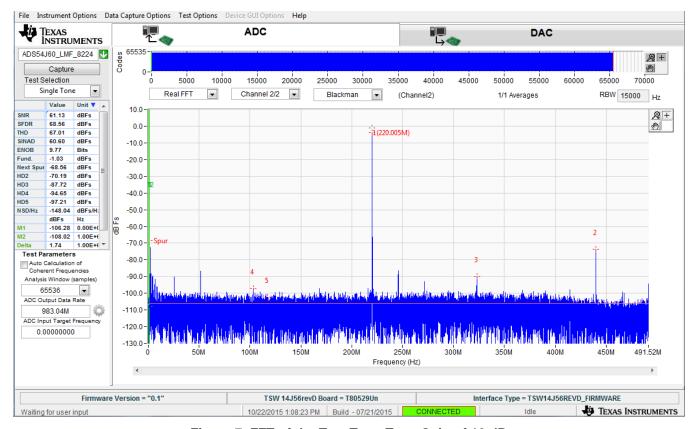


Figure 7. FFT of the Two Tone Test, Gain of 16 dB



Results www.ti.com

The following three figures show a 220MHz single tone captured using different LMH6401 Gain settings. This setup used a signal generator, a band pass filter, and 6dB attenuator between the filter and SMA connector INBP (J3) to provide a robust 50- Ω source impedance. Figure 8 shows a 220MHz IF, AC-Coupled, LMH6401 Gain = 26dB (max).

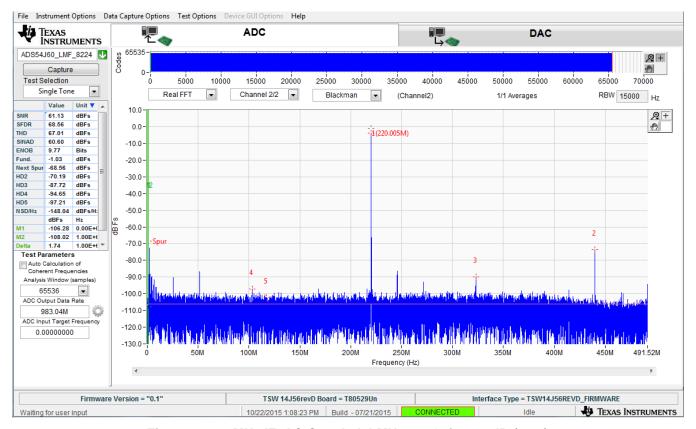


Figure 8. 220 MHz IF, AC-Coupled, LMH6401 Gain = 26dB (max)



www.ti.com Results



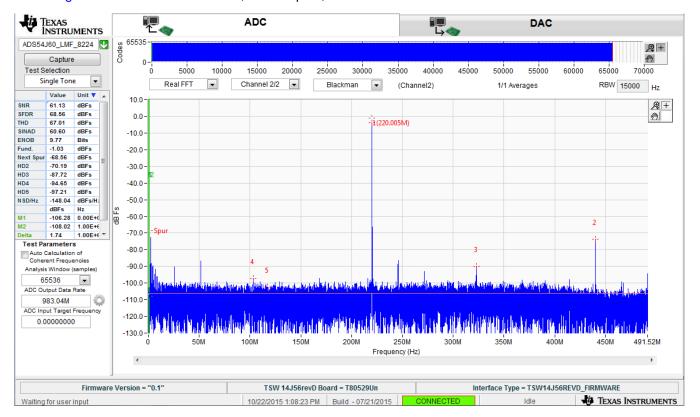


Figure 9. 220 MHz IF, AC-Coupled, LMH6401 Gain = 21dB



Results www.ti.com

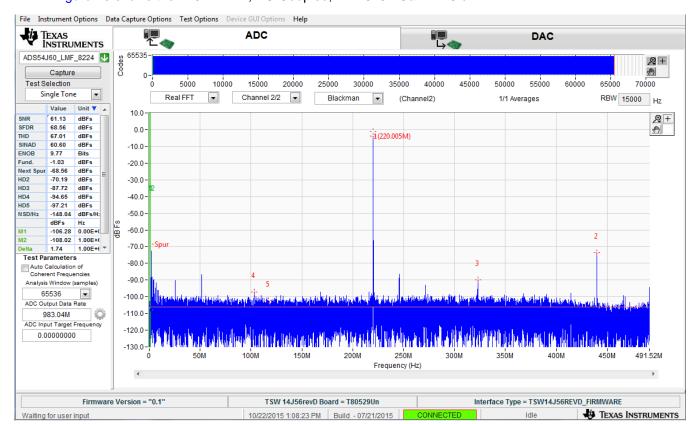


Figure 10 shows the 220 MHz IF, AC-Coupled, LMH6401 Gain = 16 dB.

Figure 10. 220 MHz IF, AC-Coupled, LMH6401 Gain = 16 dB

The measured results show that the LMH6401 device is a good solution to drive a high-speed ADC such as the ADS54J60 device for high speed, wide input voltage range digitizer applications. The LMH6401 device can be set in either DC-coupled or AC-coupled configuration. An important consideration is proper common-mode biasing. One difficulty with the DC-coupling case is the need to provide the optimal common-mode voltage at the amplifier output pins and the ADC input pins. Another challenge with DC coupling is the need to level shifted the DC source to the amplifier's input common mode voltage.

In terms of SNR and SFDR, the performance can be improved if time is spent to optimize the interface circuit and filtering, likely further than what is shown in this document. One way of improving the SFDR performance is by designing the output filter with lower termination resistor values at the amplifier output and keeping the same ADC input impedance. Such an output filter design lowers the amplifier output swing for the same full-scale input at the ADC and would result in lower SFDR. The limitation in terms of SFDR performance is the second harmonic coming from the LMH6401 device when driven by a transformer. The HD2 performance can be improved by using a high performance balun such as a Marki BAL-0010 in front of the amplifier to do the conversion from single-ended to differential, however this can only be used when AC coupling is allowed. An additional high speed differential amplifier could also be used in front of the LMH6401, such as a LMH5401 to provide DC level shifting and single-ended to differential conversion.



www.ti.com Design Files

9 Design Files

9.1 Bill of Materials

Table 4 lists the bill of materials.

Table 4. Bill of Materials

| ITEM | QTY | PART REFERENCE | VALUE | PCB FOOTPRINT | MANUFACTUR ER NAME | MANUFACTU RER PART NUMBER | NOTE |
|------|-----|---|---------|------------------|--------------------------|------------------------------------|-----------------------|
| 1 | 4 | C1, C3, C14, C16 | .01 uF | 0306 | Murata | LLL185R71E1 03MA01L | |
| 2 | 4 | C2, C4, C15, C17 | 2200 pF | 0306 | Murata | LLL185R71H2 22MA01L | |
| 3 | 14 | C5, C10, C13, C18, C24, C27, C101, C104, C197, C198, C200–C203 | .01 uF | 0402 | Murata | GRM155R71H 103JA88D | |
| 4 | 0 | C6, C19 | 5.6 pF | 0402 | AVX Corp | MK02275R6B AT2A_DNI | DNI |
| 5 | 2 | C7, C20 | 9 pF | 0402 | Murata | GJM1555C1H 9R0CB01D | |
| 6 | 2 | C5, C10, C13, C18, C24, C27, C101, C104, C197, C198, C200–C203 | 6.2 pF | 0402 | Murata | GJM1555C1H 6R2CB01D | |
| 7 | 32 | C6, C19 | .1 uF | 0402 | Murata | GRM155R71C 104KA88D | |
| 8 | 2 | C7, C20 | 9 pF | TANT_A | AVX | TPSA106K010 R0900 | Low ESR or equivalent |
| 9 | 38 | C8, C21 | .1 uF | 0201 | Murata | GRM033R61A 104KE15D | |
| 10 | 16 | C9, C12, C23, C26, C35, C65, C73–C75, C79–C84, C86–C91, C93, C95, C97, C117–C119, C122–C124, C132, C133 | .01 pF | 0603 | AVX | 06035C103JA T2A | |
| 11 | 0 | C11, C25 | .68 pF | 0402 | Murata | GRM155R71C 104KA88D_DN I | |
| 12 | 2 | C28–C34, C36–C62, C66, C67, C70, C71 | 47 pF | 0201 | TDK | C0603X5R1A1 03K030BA | |
| 13 | 1 | C63, C147-C149, C158-C160, C171-C173, C182-C184,C193-C19 | 3900 pF | 0402 | Murata | GRM155F50J6 84ZE01D | |
| 14 | 3 | C64, C72 | 100 pF | 0402 | Murata | GRM1555C1H 470FA01D | DNI |
| 15 | 1 | C68, C69 | 10 uF | 0402 | Murata | GRM155R71H 392KA01D | |
| 16 | 2 | C76 | 2200 pF | 0402 | AVX Corp | 06031A101GA T2A | |
| 17 | 4 | C77, C120, C121 | 10 pF | 0603 | TDK | C1608X5R1C1 06M080AB | |
| 18 | 1 | C78 | 1 uF | 0402 | Murata | GRM155R71E 222KA01D | |



Design Files www.ti.com

Table 4. Bill of Materials (continued)

| ITEM | QTY | PART REFERENCE | VALUE | PCB FOOTPRINT | MANUFACTUR ER NAME | MANUFACTU RER PART NUMBER | NOTE |
|------|-----|---|--|---------------------------------------|--------------------------|------------------------------------|-----------------------|
| 19 | 1 | C85, C92 | 10 pF | 0402 | Murata | GRM1555C1H 100JA01D | |
| 20 | 9 | C99, C102, C105, C108, C112–C116 | 1 uF | 0402 | TDK | C1005X5R1C1 05K050BC | |
| 21 | 4 | C100, C103, C129, C136 | 10 uF | 3528 | Kemet | T520B106M01 6ATE100 | Low ESR or equivalent |
| 22 | 0 | C106, C107, C109- C111 | .01 uF | 0402 | Murata | GRM155R71H 103JA88D_DN I | DNI |
| 23 | 1 | C125 | 47 uF | TANT_B | AVX | TPSB476K010 R0250 | |
| 24 | 16 | C126, C140, C145, C150, C151, C156, C161, C164, C169, C174, C175, C180, C185, C186, C191, C196 | 10 uF | 0805 | Murata | GRM21BR61E 106KA73L | |
| 25 | 4 | C128, C135, C139, C163 | 22 uF | 0603 | TDK Corp | C1608X5R0J2 26M080AC | |
| 26 | 7 | C130, C137, C141, C152, C165, C176, C187 | 0.1 uF | 0603 | AVX | 0603YC104KA T2A | |
| 27 | 2 | C131, C199 | 1000 pF | 0603 | Kemet | C0603C102K3 RACTU | |
| 28 | 10 | C142, C146, C153, C157, C166, C170, C177, C181, C188, C192 | 1 uF | 0603 | TDK | C1608X7R1E1 05K080AB | |
| 29 | 5 | C143 C154 C167 C178 C189 | 47 uF | 1206 | Murata | GRM31CR61A 476ME15L | |
| 30 | 5 | C144, C155, C168, C179, C190 | 33 uF | TANT_B | AVX | TPSB336K016 R0350 | |
| 31 | 4 | D1-D4 | LED Green | LED_1206 | Lite On | LTST- C150KGKT | DNI |
| 32 | 0 | F1 | FUSE 10 A 63 V FAST | 1206 | TE Connectivity | 1206SFF200F/ 63-2_DNI | |
| 33 | 16 | FB1-11, FB13-FB17 | 120 Ω at 100 MHz | 1206 | Murata | BLM31PG121 SN1L | |
| 34 | 1 | FB12 | 1 k Ω at 100 MHz | 1806 | Murata | BLM41PG102 SN1L | |
| 35 | 2 | FLT1, FLT2 | FILTER LC HIGH FREQ, .2 uF | 1806_BEAD_NF M41P | Murata | NFM41PC204 F1H3L | |
| 36 | 5 | J1-5 | CONN, SMA, JACK, 50 Ω, EDGE MNT | SMA_SMEL_DU AL_PSF- S01_250x215 | Johnson Components | 142-0711-821 | |
| 37 | 1 | J6 | CONN, SMA, JACK, 50 Ω , THVT | SMA_THVT_312 x312 | Johnson Components | 142-0701-201 | |
| 38 | 1 | J7 | CON, SMVT, HS, FIELD ARRAY, 400POS, MALE | SMA_THVT_312 x312 | Samtec | SEAM-40- 02.0-S-10-2-A- K-TR | |
| 39 | 1 | J8 | CONN, USB MINI AB, SMT | CON_SMRT_US BMNE20_F | Wurth ELektronik | 651305142821 | |
| 40 | 1 | J9 | CONN, JACK, PWR, MINI, R/A, TH | CON_RAPC722_ JACK_THVT_3 | Switchcraft | RAPC722X | |



www.ti.com Design Files

Table 4. Bill of Materials (continued)

| | Table 4. Bill of Materials (Continued) | | | | | | | | | |
|------|--|---|--|---------------------------|--------------------------|------------------------------------|------|--|--|--|
| ITEM | QTY | PART REFERENCE | VALUE | PCB FOOTPRINT | MANUFACTUR ER NAME | MANUFACTU RER PART NUMBER | NOTE | | | |
| 41 | 2 | JP1. JP2 | HDR, THVT, 2POS, .100 | HDR_THVT_1x2 _100_M | Samtec | HTSW-102-07- G-S | | | | |
| 42 | 4 | L1. L3, L5, L7 | 7.5 nH | ind_0603 | Coilcraft | 0603CS- 7N5XGEU | | | | |
| 43 | 4 | L2 L4 L6 L8 | 18 nH | ind_0603 | Coilcraft | 0603CS- 18NXGEU | | | | |
| 44 | 1 | L9 | 1.5 uH | 2016 | Toyo | 1286AS-H- 1R5M | | | | |
| 45 | 2 | MT1, MT2 | STANDOFF, FEMALE, 4-40 X 1 3/16", AL | MFG125_PLATE D | Raf | 1648-440-AL | | | | |
| 46 | 0 | PP1 | PROBE POINT | PROBE_POINT_ 30PAD | N/A | N/A | | | | |
| 47 | 1 | Q1 | CSD17313Q2 | mosfet_8_2mmx2 mm_0p65 | Texas Instruments | CSD17313Q2 | | | | |
| 48 | 4 | R2, R14, R17, R25 | 4.99 | 0402 | Vishay Dale | CRCW04024R 99FKED | | | | |
| 49 | 0 | R3, R10 | 129 | 0402 | Panasonic | ERJ- 2RKF1270X_D NI | DNI | | | |
| 50 | 0 | R4, R15, R19, R26 | A/R | 0402 | DNI | DNI | DNI | | | |
| 51 | 4 | R5, R9, R20, R23 | 53.6 | 0402 | Panasonic | ERA- 2AEB53R6X | | | | |
| 52 | 9 | R7, R21, R38, R39, R41, R64, R67, R119, R125 | 0 | 0402 | Panasonic | ERJ- 2GE0R00X | | | | |
| 53 | 0 | R11 | 365 | 0402 | Panasonic | ERJ- 2RKF3650X_D NI | DNI | | | |
| 54 | 6 | R12, R18, R22, R42, R49, R51 | 49.9 | 0402 | Panasonic | ERJ- 2RKF49R9X | | | | |
| 55 | 4 | R16, R24, R29, R33 | 20 | 0402 | Panasonic | ERJ- 2RKF20R0X | | | | |
| 56 | 5 | R27, R28, R30, R31, R74 | 1 k | 0402 | Panasonic | ERJ- 2RKF1001X | | | | |
| 57 | 2 | R32, R34 | 100 | 0201 | Panasonic | ERJ- 1GEF1000C | | | | |
| 58 | 1 | R36 | 240 | 0402 | Panasonic | ERJ- 2GEJ621X | | | | |
| 59 | 1 | R37 | 0 | 0402 | Panasonic | ERJ- 2GEJ393X | | | | |
| 60 | 0 | R40 | 100 | 0402 | Panasonic | ERJ- 2RKF1000X_D NI | DNI | | | |
| 61 | 4 | R43, R44, R46, R47 | 750 | 0402 | Panasonic | ERJ- 2RKF2400X | | | | |
| 62 | 0 | R45, R54, R55, R57, R120-R124, R126, R131, R132 | 2.1 k | 0402 | Panasonic | ERJ- 2GE0R00X_D NI | DNI | | | |
| 63 | 2 | R48, R58 | 100 | 0402 | Panasonic | ERJ- 2RKF1000X | | | | |
| 64 | 3 | R50, R52, R53 | 750 | 0603 | Vishay Dale | CRCW060375 0RFKEA | | | | |
| 65 | 1 | R56 | 2.1 k | 0402 | Panasonic | ERJ- 2RKF2101X | | | | |



Design Files www.ti.com

Table 4. Bill of Materials (continued)

| ITEM | QTY | PART REFERENCE | VALUE | PCB FOOTPRINT | MANUFACTUR ER NAME | MANUFACTU RER PART NUMBER | NOTE |
|------|-----|--|-------------------------------------|--|--------------------------|------------------------------------|-----------|
| 66 | 1 | R59 | 48.7 k | 0402 | Panasonic | ERJ- 2RKF4871X | |
| 67 | 3 | R60-R62 | 4.75 k | 0402 | Panasonic | ERJ- 2RKF4751X | |
| 68 | 0 | R63, R82, R84, R85, R89, R91, R92, R99, R102, R104, R106, R109, R111, R113–R115, R117, R118 | 0 | 0603 | Panasonic | ERJ- 3GEY0R00V_ DNI | DNI |
| 69 | 3 | R65 R69 R70 | 22.1 | 0402 | Panasonic | ERJ- 2RKF22R1X | |
| 70 | 14 | R68, R83, R86, R87, R90, R93, R94, R100, R101, R103, R107, R108, R110, R116 | 0 | 0603 | Panasonic | ERJ- 3GEY0R00V | |
| 71 | 1 | R76 | 1.05 M | 0603 | Vishay Dale | CRCW06031M 05FKEA | |
| 72 | 1 | R77 | 200 k | 0603 | Panasonic | ERJ- 3EKF2003V | |
| 73 | 5 | R78, R88, R95, R105, R112 | 47.5 k | 0603 | Panasonic | ERJ- 3EKF4752V | |
| 74 | 1 | R80 | 590 k | 0603 | Panasonic | ERJ- 3EKF5903V | |
| 75 | 2 | R81, R98 | 162 k | 0603 | Panasonic | ERJ- 3EKF1623V | |
| 76 | 1 | R96 | 301 k | 0603 | Panasonic | ERJ- 3EKF3013V | |
| 77 | 0 | SJP1 | JUMPER_L_0603 _SMT | JUMPER_SMD_L _0603 | DNI | DNI | |
| 78 | 0 | SJP2 | SOLDER JUMPER, 0603 | JUMPER_SMT_1 x2_0603 | DNI | DNI | Shunt 1–2 |
| 79 | 0 | SJP3 | JUMPER_L_0603 _SMT | JUMPER_SMD_L _0603 | DNI | DNI | Shunt 2-3 |
| 80 | 1 | SW1 | SWITCH, SMT, PUSHBUTTON, SPST | SW_SMVT_SPS T_EVQPJX_2 | Panasonic | EVQ-PNF04M | |
| 81 | 1 | T1 | JTX-2-10T+ | XFMR_6_310X28 0_100 | Mini-Circuits | JTX-2-10T+ | |
| 82 | 1 | T2 | JTX-2-10T+ | XFMR_6_310X28 0_100 | Mini-Circuits | JTX-2-10T+ | |
| 83 | 9 | TP1, TP7–TP10, TP13–TP16 | Red | TESTPOINT_62D RILL_THM | Keystone | 5000 | |
| 84 | 7 | TP2-TP6, TP11, TP12 | Black | TESTPOINT_62D RILL_THM | Keystone | 5001 | |
| 85 | 1 | U1 | LMH3401 | QFN_14_98x98_ 0P50MM | Texas Instruments | LMH3401IRMS | |
| 86 | 1 | U2 | LMH6401 | UQFN_16_118x1 18_0P5mm_RMZ | Texas Instruments | LMH6401IRMZ | |
| 87 | 1 | U3 | ADS54J60 | QFN_72_10MMX 10MM_0P50MM_ PWRPAD | Texas Instruments | ADS54J40IRG C | |
| 88 | 1 | U4 | LMK04828 | QFN_64_360X36 0_0P50MM_PWR PAD | Texas Instruments | LMK04828BIS Q/NOPB | |



www.ti.com Design Files

Table 4. Bill of Materials (continued)

| ITEM | QTY | PART REFERENCE | VALUE | PCB FOOTPRINT | MANUFACTUR ER NAME | MANUFACTU RER PART NUMBER | NOTE |
|------|-----|-------------------|---------------------------------|------------------------------------|--------------------------|------------------------------------|--------------------|
| 89 | 1 | U5 | SN65LVDS4 | QFN_10_81X61_ RSE | Texas Instruments | SN65LVDS4R SET | |
| 90 | 2 | U6, U8 | TXB0104 | VQFN_14_138x1 38_0P50_RGY | Texas Instruments | TXB0104RGY R | |
| 91 | 1 | U7 | FT245RL | SSOP_28_413x2 20_26 | FTDI Chip | FT245RL- REEL | |
| 92 | 1 | U9 | TPS63050 | DSBGA_12_1P5 6MMx1P16MM_Y FF | Texas Instruments | TPS63050YFF | |
| 93 | 2 | U10 | TPS2400 | DBV5 | Texas Instruments | TPS2400DBVT | |
| 94 | 2 | U11, U15 | TPS82085 | uSIL_8_3MMx2p 8MM_0p65mm | Texas Instruments | TPS82085SIL | |
| 95 | 5 | U12–U14, U16, U17 | TPS7A8300 | VQFN_20_138x1 38_0P50_RGR | Texas Instruments | TPS7A8300R GR | |
| 96 | 1 | Y1 | 122.88 MHz | VCXO_6_CUSTO M | Crystek | CVHD-950- 122.880 | |
| 97 | 1 | | BARE BOARD, TSW54J60 | | TTM | TSW54J60 REV B | |
| 98 | 2 | | SCREW, 4-40 X 3/4", PHIL, SS | | Building Fasteners | PMSSS 440 0075 PH | Screw for standoff |
| 99 | 2 | SEE NOTE 3 | SHUNT- JUMPER-0603 | | Panasonic | ERJ- 3GEY0R00V | Shunt for jumper |

9.2 Software Files

To download the software files, see the design files at TSW54J60EVM

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design. TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have *not* been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.