

Automotive 1.3-MP Low-Cost Camera Module Reference Design With YUV422, PMIC, FPD-Link III, and POC



Description

This camera module reference design addresses the need for small low-cost cameras in automotive driver assistance systems (ADAS) by combining a 1.3-megapixel imager with integrated image signal processor (ISP) with a 12-bit, 100-MHz TI FPD-Link III serializer. Additionally, it provides a power-management integrated circuit (PMIC) power supply for both devices in an ultra-small form factor. This design includes a high-speed serial interface to connect a remote automotive camera module to a display or machine vision processing system with a coaxial cable transmitting both data and power. The FPD-Link III SerDes technology used in this reference design enables the transmission of raw or processed video data, bidirectional control signals, and power over coax (POC) using a single cable.

Resources


TIDA-050050	Design Folder
TPS650330-Q1	Product Folder
DS90UB933-Q1	Product Folder

Features

- Space-optimized design with integrated power supply that fits on a single 18 mm × 18 mm PCB
- Integrated TPS650320-Q1 power supply includes three step-down converters and LDO to enable high efficiency and low noise supply generation
- P2P compatible power supplies to enable functional safety applications
- Enables camera applications up to 1 MP/60 fps using DS90UB933-Q1
- 1.3-MP OX01F10 image sensor from Omnivision providing HDR YUV422, RGB888, RAW
- Single Rosenberger Fakra coaxial connector for digital video, power, control, and diagnostics

Applications

 - [Camera module without processing](#)
- [Rear camera](#)
- [Surround view system ECU](#)



1 System Description

Many automotive applications require small form factors with reduced circuit area that enable compact and modular systems. As a result, most cameras along with electronic components must meet this minimal area constraint when designing ADAS camera applications. This reference design addresses these needs by including a 1-megapixel imager, 1.9 Gbps serializer, and a single Power Management IC, and all components contained within an area of an 18-mm × 18-mm circuit board. The only connection required by the system is a single 50-Ω coaxial cable.

A combined signal containing the DC power, the FPD-Link front and back channels enter the board through the FAKRA coax connector. The filter in [Figure 1-1](#) blocks all of the high-speed content of the signal (without significant attenuation) while allowing the DC (power) portion of the signal to pass through inductor L5.

 


Figure 1-1. FPD-Link III Signal Path

The DC portion is connected to the buck 1 input of the TPS650320-Q1 Power Management IC. This voltage powers buck 2 and buck 3 of the device, which are responsible for creating the supply rails to the imager and serializer. The LDO input pin is supplied 3.8 V, which is responsible for providing a low-noise, 3.3-V analog supply to the imager. Buck 3 outputs the imager-dedicated 1.1-V and buck 2 generates a universal 1.8-V digital supply that is shared by both the imager and serializer. The high-frequency portion of the signal is connected directly to the serializer. This is the path that the video data and the control back channel takes between the serializer and deserializer.

The output of the imager is connected through a parallel digital video port (DVP) interface to the serializer. The serializer transmits this video data over a single LVDS pair to the deserializer located on the other end of the coax cable.

Additionally, on the same coax cable, there is a separate low-latency, bidirectional control channel that provides the additional function of transmitting control information from an I²C port. This control channel is independent of the video blanking period. It is used by the system microprocessor to configure and control the imager.

1.1 Key System Specifications

Table 1-1. Key System Specifications

PARAMETER	COMMENTS	MIN	TYP	MAX	UNIT	
V _{IN}	Supply voltage	Power over coax (POC)	4.5	9	18.3	V
P _{TOTAL}	Total power consumption	V _{POC} = 12 V	—	0.6	1	W
A _{PCB}	PCB Area		—	—	18 x 18	mm ²

2 System Overview

2.1 Block Diagram

 


Figure 2-1. Camera Block Diagram

2.2 Design Considerations

The following subsections discuss the considerations behind the design of each subsection of the system.

2.2.1 PCB and Form Factor

This reference design is not intended to fit any particular form factor; however, the goal of the design is to showcase a solution with minimal PCB area and compact design. The area of the board roughly equates to a dimension of 18 mm × 18 mm. The area near the board edge in [Figure 2-2](#) is reserved for attaching the optics housing that holds the lens.

 


Figure 2-2. 3-D PCB Top Layer

 


Figure 2-3. 3-D PCB Bottom Layer

2.2.2 Power Supply Design

2.2.2.1 POC Filter

One of the most critical portions of a design that uses POC is the filter circuitry. The goal is twofold:

1. Deliver a clean DC supply to the input of the switching regulators.
2. Protect the FPD-Link communication channels from noise-coupled backwards from the rest of the system.

The DS90UB933-Q1 and DS90UB954-Q1 SerDes devices used in this system communicate over two carrier frequencies, 1 GHz at full speed ("forward channel") and a lower frequency of 2.5 MHz ("back channel") determined by the deserializer device. The filter must attenuate this rather large band spanning both carriers, hoping to pass only DC.

For the POC design, to enable the forward channel and back channel to pass uninterrupted over the coax, an impedance of 1 k Ω across the 1-MHz to 1-GHz bandwidth is required. Use two inductors: a 4.7- μ H inductor for high-frequency forward channel filtering, and a 100- μ H inductor for low-frequency back-channel filtering. For more details, see the [Sending Power Over Coax in DS90UB913A Designs](#) application report. In addition, a 1-k Ω resistor is placed in parallel with both of these inductors. A 1-k Ω ferrite bead is also placed in series for extra filtering at the forward channel data rate.

Lastly, in regards to filtering, ensuring that the FPD-Link signal is uninterrupted is just as important as providing a clean, noise-free DC supply to the system. To achieve this, AC coupling capacitors shown by the 0.1 μ F and 0.047 μ F are chosen to ensure the high-speed AC data signals are passed through but that the DC is blocked from getting on the data lines.

 


Figure 2-4. Power Over Coax

2.2.2.2 Power Supply Considerations

Because this reference design is targeted at automotive applications, there are several considerations that limit design choices. Additionally, the following list of system-level specifications helped shape the final overall design:

- The total solution size must be minimized to meet the size requirement of this design, which is equivalent to 18 mm \times 18 mm. This means choosing parts that integrate FETs, diodes, compensation networks, and feedback resistor dividers to eliminate the need for external circuitry.
- To avoid interference with the AM radio band, all switching frequencies must be greater than 1700 kHz or lower than 540 kHz. Lower switching frequencies are less desirable in this case because they require large inductors and can still produce harmonics in the AM band. For this reason, this reference design looks at higher frequency switchers.
- All devices must be AEC Q100 (-Q1) rated.

Before parts are chosen, the input voltage range, required voltage rails, and required current per rail must be known. In this case, the input voltage is a pre-regulated 9-V supply coming in over the coaxial cable. This system has only two main devices, the imager and serializer, which are responsible for power consumption during operation. [Table 2-1](#) shows the requirements of the supplies:

Table 2-1. System Power Budget

PARAMETER	VOLTAGE (V)	CURRENT (mA)	POWER (mW)
DS90UB933			
VDD	1.8	98	176
OX01F10			
VDD-D	1.1	170	187
VDD-IO	1.8	21	38
VDD-A	3.3	33	109
Oscillator			
VDD	1.8	3	5
Total			
VDD-D	1.1	170	187
VDD-IO	1.8	122	220
VDD-A	3.3	33	109

The 9-V supply over the coaxial cable is first stepped down to 3.8 V, which then supplies the rest of the system on the camera module. In this design, the 1.8-V rail supplies both the DS90UB933 supply, and the interface supply of the OX01F10 imager. The OX01F10 3.3-V analog rail requires 33 mA, the DS90UB933 serializer 1.8-V rail requires 98 mA, and the OX01F10 digital 1.1-V rail requires 170 mA.

Assuming 85% efficiency to simplify calculations with the previous values, it is calculated that the 3.8-V supply will require 160 mA to successfully power the 1.1-V, 1.8-V, and 3.3-V rails. Because the input and output voltages, output current requirements, and total wattage consumption are known, calculate the input current using [Equation 1](#):

$$P_{IN} = V_{IN} \times I_{IN} = \frac{P_{OUT}}{\eta_{SYSTEM}} = \frac{\frac{P_{OUT2}}{\eta_2} + \frac{P_{OUT3}}{\eta_3} + \frac{P_{LDO}}{\eta_{LDO}}}{\eta_1} \quad (1)$$

$$\therefore I_{IN} = \frac{\frac{187 \text{ mW}}{85\%} + \frac{220 \text{ mW}}{85\%} + \frac{109 \text{ mW}}{87\%}}{9 \text{ V} \times 85\%} = 79.0 \text{ mA}$$

This information provides a strong foundation in the selection of power topologies and inductive passives that are explained in later sections.

Due to the requirement of Q100, it is mandatory that the switching frequency is rated outside of the AM band and must satisfy the voltage and current requirements derived previously. As the input voltage is a regulated voltage that will always be greater than any of the power rails produced, the power topologies selected should either be step-down converters (bucks) or LDOs. Bucks are generally included in supplies where switching noise is not a significant concern, and power savings is the largest care about. Conversely, LDOs can be incorporated in establishing low-noise analog supplies that reduce inherent noise and are more robust against EMI interactions; however, this is at the expense of larger current consumption.

In this design, a single Power Management IC is responsible for powering the supply rails. This device, the TPS650320-Q1, was chosen as it incorporates three step-down converters (BUCKS) and an LDO in a single 4.0-mm x 4.0-mm VQFN package. The current requirements of the design also played an important role in the selection of the device, as the secondary BUCKS are capable of providing 600 mA, while the LDO is capable of supplying a maximum current output of 300 mA. BUCK1 steps down the 9-V POC input to 3.8 V. The 3.8-V rail then supplies power to BUCK2, BUCK3, and the LDO input. BUCK 2 provides the interface and digital supply for both the OX01F10 imager and DS90UB933 serializer, while the LDO output creates a clean, low-noise supply for the 3.3-V analog supply for the OX01F10.

2.2.2.2.1 Choosing External Components

For simplicity, the efficiency of the buck regulators is assumed to be 85% for these operating conditions, and the efficiency of the LDO is given by [Equation 2](#).

$$\eta_{LDO} = \frac{V_{OUT}}{V_{IN}} \tag{2}$$

System and Buck 1 currents calculated assuming 85% switching regulator efficiency are given in [Equation 1](#).

[Table 2-2](#) shows the load capability of each regulator compared to the requirements of the camera module. The TPS650320-Q1 device is capable of supplying the system power with plenty of margin to account for variations between typical and maximum current variation.

Table 2-2. Regulator Load Capability

REGULATOR	OUTPUT VOLTAGE (V)	MAX CURRENT (mA)	REQUIRED CURRENT (mA)
Buck 1	3.8	800	160
Buck 2	1.8	600	122
Buck 3	1.1	600	170
LDO	3.3	300	33

After determining that the TPS650320-Q1 device is suitable based on the power requirements, the external components can be chosen quickly based on the data sheet recommendations, simplifying the design process. These recommendations are shown in [Figure 2-5](#) and [Equation 1](#).

 


Figure 2-5. TPS650320-Q1 Typical Application Circuit

Table 2-3. TPS650330-Q1 Recommended Components

COMPONENT	DESCRIPTION	VALUE	UNIT
C _{VSYS,VSYS_S}	VSYS and VSYS_S decoupling	10	μF
C _{PVIN_B1}	Buck 1 input capacitor	10	μF
L _{SW_B1}	Buck 1 inductor	2.2	μH
C _{OUT_B1}	Buck 1 output capacitor	10	μF
C _{PVIN_B2}	Buck 2 input capacitor	10	μF
L _{SW_B2}	Buck 2 inductor	1.0	μH
C _{OUT_B2}	Buck 2 output capacitor	10	μF
C _{PVIN_B3}	Buck 3 input capacitor	10	μF
L _{SW_B3}	Buck 3 inductor	1.0	μH
C _{OUT_B3}	Buck 3 output capacitor	10	μF
C _{PVIN_LDO}	LDO input capacitor	1.0	μF
C _{OUT_LDO}	LDO output capacitor	2.2	μF

The high, fixed PWM 2.3-MHz switching frequency enables the use of small inductors with a fast transient response. A value of 2.2 μH is typically recommended for the BUCK1 channel output. This value helps to minimize the inductor ripple current.

With the inductance value chosen, the design now needs an inductor with a proper saturation current. This is the combination of the steady-state supply current as well as the inductor ripple current. The current rating needs to be sufficiently high but minimized as much as possible to reduce the physical size of the inductor. Calculate inductor ripple with [Equation 3](#):

$$\Delta I_{L(\max)} = V_{\text{OUT}} \times \left(\frac{1 - \frac{V_{\text{OUT}}}{V_{\text{IN}(\max)}}}{L_{(\min)} \times f_{\text{SW}}} \right) \quad (3)$$

where:

- $I_{L(\max)}$ is the maximum inductor current
- ΔI_L is the peak-to-peak inductor ripple current
- $L_{(\min)}$ is the minimum effective inductor value
- f_{SW} is the actual PWM switching frequency

The parameters for this reference design using the TPS650330-Q1 are:

- $V_{\text{OUT}} = 3.3 \text{ V}$
- $V_{\text{IN}(\max)} = 18.3 \text{ V}$
- $L_{(\min)} = 2.2 \text{ μH}$
- $f_{\text{SW}} = 2.3 \text{ MHz}$

These parameters yield an inductor current of $\Delta I_L = 535 \text{ mA}$. The maximum current draw of the system through this regulator is 327 mA. The minimum saturation current is calculated as:

$$L_{\text{SAT}} \geq I_{\text{OUT}(\text{MAX})} + \frac{\Delta I_{L(\text{MAX})}}{2} = 327 \text{ mA} + \frac{535 \text{ mA}}{2} = 594 \text{ mA} \quad (4)$$

The TPS650330-Q1 device on this design uses a Murata® LQM2MPN2R2NG0, which has a rated current of 1.2 A and a DC resistance maximum of 138 mΩ. Additionally, this device has an operating temperature from –55°C to 125°C and comes in a very small 2-mm × 1.6-mm package.

2.2.2.2.2 Choosing the Buck 1 Inductor

With an inductance value of 2.2 μH selected, the minimum inductor saturation current must be derived to choose an appropriate inductor for the design. This is the combination of the steady-state supply current as well as the inductor ripple current. To ensure flexibility of the power and serializer base board to higher power image sensors, the inductor is chosen based on each maximum rated output current of the regulator. [Equation 5](#) calculates inductor ripple current:

$$\Delta I_{L(\text{max})} = V_{\text{OUT}} \times \left(\frac{1 - \frac{V_{\text{OUT}}}{V_{\text{IN}(\text{max})}}}{L_{(\text{min})} \times f_{\text{sw}}} \right) \quad (5)$$

where

- $\Delta I_{L(\text{max})}$ is the maximum peak-to-peak inductor ripple current
- $L_{(\text{min})}$ is the minimum effective inductor value
- f_{sw} is the actual PWM switching frequency

The parameters for Buck 1 of this reference design are:

- $V_{\text{OUT}} = 3.8 \text{ V}$
- $V_{\text{IN}(\text{max})} = 18.3 \text{ V}$
- $L_{(\text{min})} = 2.2 \mu\text{H}$
- $f_{\text{sw}} = 2.3 \text{ MHz}$

These parameters yield an inductor ripple current of $\Delta I_L = 595 \text{ mA}$. Assuming a maximum load current of 800 mA, use [Equation 6](#) to calculate a minimum saturation current of 1100 mA.

$$L_{\text{SAT}} \geq I_{\text{OUT, (MAX)}} + \frac{\Delta I_{L(\text{MAX})}}{2} \quad (6)$$

The TPS650330-Q1 device on this design uses a TDK® TFM201610ALMA2R2MTAA, which has a rated current of 2 A and a DC resistance maximum of 152 m Ω . Additionally, this inductor has an operating temperature from -55°C to 150°C in a very small 2.0-mm \times 1.6-mm package.

2.2.2.2.3 Choosing the Buck 2 and Buck 3 Inductors

Buck 2 and Buck 3 have a recommended inductor value of 1.0 μH . When selecting a component, it is important to verify the DC resistance and saturation current. The DC resistance of the inductance influences the efficiency of the converter directly – lower DC resistance is directly proportional to efficiency. The saturation requirement of the inductor is determined by combining the steady-state supply current and the inductor ripple current. The current rating needs to be sufficiently high but minimized as much as possible to reduce the physical size of the inductor. Calculate the inductor ripple current using [Equation 5](#).

The parameters for the Buck 2 1.8-V rail include:

- $V_{\text{OUT}} = 1.8 \text{ V}$
- $V_{\text{IN}(\text{max})} = 3.8 \text{ V}$
- $L_{(\text{min})} = 1.0 \mu\text{H}$
- $f_{\text{sw}} = 2.3 \text{ MHz}$

These parameters yield an inductor ripple current of $\Delta I_L = 412 \text{ mA}$. Assuming a maximum load current of 600 mA, [Equation 6](#) can be used to calculate a minimum saturation current of 810 mA.

The parameters for the Buck 3 1.2-V rail include:

- $V_{\text{OUT}} = 1.2 \text{ V}$
- $V_{\text{IN}(\text{max})} = 3.8 \text{ V}$
- $L_{(\text{min})} = 1.0 \mu\text{H}$
- $f_{\text{sw}} = 2.3 \text{ MHz}$

These parameters yield an inductor ripple current of $\Delta I_L = 357 \text{ mA}$. Assuming a maximum load current of 600 mA, [Equation 6](#) can be used to calculate a minimum saturation current of 780 mA.

Buck 2 and Buck 3 of this design use the TDK® TFM201610ALMA1R0MTAA, which has a current rating of 3.1 A and a DC resistance of 60 mΩ. Additionally, this inductor has an operating temperature of –55°C to 150°C in a very small 2.0-mm × 1.6-mm package.

2.2.2.3 Functional Safety

The TPS650320-Q1 device has integrated supervisors in addition to temperature and current monitoring. The device is also pin-compatible with the TPS650331-Q1, TPS650332-Q1, and TPS650333-Q1, with only a single component change of the Buck 1 inductor to 1.5 μH. Each of the TPS650331-Q1, TPS650332-Q1, and TPS650333-Q1 devices provides additional safety features as an ASIL-B safety elements out of context (SEooC), allowing the scalability of this design to camera applications with more stringent safety requirements.

2.3 Highlighted Products

This reference design uses the following TI products:

- DS90UB933-Q1: is the serializer portion of a chipset that offers an FPD-Link III interface with a high-speed forward channel and a bidirectional control channel for data transmission over a single coaxial cable or differential pair. This chipset incorporates differential signaling on both the high-speed forward channel and bidirectional control channel data paths. The serializer-deserializer pair is targeted for connections between imagers and video processors in an electronic control unit (ECU).
- TPS650320-Q1: an automotive qualified, four-channel PMIC optimized for camera applications. The device integrates three buck converters and one LDO, along with overvoltage protection and undervoltage supervisors on each voltage rail. A high, fixed PWM 2.3-MHz switching frequency enables the use of small inductors with a fast transient response. The low-noise, high-PSRR LDO provides an output voltage option for sensitive analog circuits. A wide range of output voltage and sequencing settings, along with other operational settings, are programmable for compatibility with a variety of imagers without the need for any additional components.

2.3.1 OX01F10 Imager

The OmniVision® OX01F10 is a diagonal 6.67-mm, 1/3.55" color CMOS image sensor with 1.36 effective mega-pixels. The sensor supports AD 10-bit, MIPI 2-lane, DVP, YUV422, RGB888, BT656, and RAW10 up to RAW24 HDR output. Other included features follow:

- Supports 1340 × 1020 resolution (1.3-MP) and any cropped size image sizes
- Integrated ISP with AEC, AGC, AWB, lens correction, defective pixel correction, HDR combination, tone mapping, and black level correction
- 50- and 60-Hz flicker cancellation
- Requires three voltage rails (3.3 V, 1.8 V, and 1.1 V)
- Can be configured using an I²C-compatible two-wire serial interface

2.3.2 DS90UB933-Q1

Using a serializer to combine 10-bit video with a bidirectional control signal onto one coax or twisted pair greatly simplifies system complexity, cost, and cabling requirements. The parallel video input of the DS90UB933-Q1 mates well with the 10-bit parallel video output of the OV10640 imager. Once combined with the filters for the POC, video, I2C, diagnostics, and power can all be transmitted up to 15 m on a single, inexpensive coax cable. For more information on the cable itself, see the [Cable Requirements for the DS90UB913A and DS90UB914A](#) application report.

2.3.3 TPS650320-Q1

The TPS650320-Q1 device is a highly-integrated power management IC for automotive camera modules. This device combines three step down converters and one low-dropout (LDO) regulator. The BUCK1 step-down converter has an input voltage range up to 18.3 V for connections to Power over Coax (POC). All converters operate in a forced fixed-frequency PWM mode. The LDO can supply 300 mA and operate with an input voltage range from 3.0 V to 5.5 V. The step-down converters and the LDO have separate voltage inputs that enable maximum design and sequencing flexibility. Additionally, an integrated advanced Spread-Spectrum Clock (SSC) enables robust EMI performance. A small form-factor, added rail supervision features, and programmability make this device a very attractive candidate for designs that need to be expedited or scaled for future applications.

2.4 System Design Theory

The main design challenges to consider for automotive cameras are size, ease of use, and thermal efficiency. Automotive cameras are often placed in remote regions of the vehicle where area is limited, requiring an overall compact solution. Because of this, the system is designed around having the lowest number of components with a fully-integrated PMIC power solution. The ease of use and design flexibility offered by a PMIC solution is also critical to enable a single platform design and reduce development time as ADAS applications continue to grow. The DS90UB933-Q1 and TPS650320-Q1 additionally both provide compatibility with a wide range of imagers. The choice of a two-board solution highlights this capability, as the power and serializer base board can be reused with different imager boards depending on the camera application. Lastly, the small size and remote placement of these cameras increases their susceptibility to heat. A power-efficient system is crucial to preserve the image quality in these conditions. The TPS650320-Q1 device is optimized for efficiency with a three-buck and one-LDO regulator topology, enabling the support of medium- and high-quality imagers without sacrificing thermal performance. Due to the impact of thermals on the system performance, it is important to calculate total system efficiency as part of the design process. From the Buck 1 output power in [Table 2-2](#), the TPS650320-Q1 efficiency is about 80%. Using this value, [Equation 3](#) calculates a system input power of about 760 mW. [Equation 7](#) can then be used with the output power of Buck 2, Buck 3, and the LDO to calculate the overall system efficiency.

$$\eta_{SYSTEM} = P_{OUT} / P_{IN} = (P_{OUT,2} + P_{OUT,3} + P_{OUT,LDO}) / P_{IN,1} = 68\% \quad (7)$$

3 Hardware, Testing Requirements, and Test Results

3.1 Hardware Requirements

This reference design needs only one connection to a system with a compatible deserializer over the FAKRA connector as shown in [Figure 3-1](#).



Figure 3-1. Getting Started With the Board

3.1.1 Hardware Setup

[Figure 3-2](#) shows the setup to test the camera module reference design. This design includes an OX01F10 image sensor, which connects to the DS90UB933-Q1 serializer over CSI-2 and I²C interfaces. The DS90UB933-Q1 serializer then connects through POC to a DS90UB954-Q1 deserializer. Note that for test setup, only one channel is used from the DS90UB954-Q1 device. The Analog LaunchPad™ GUI writes all the back channel I²C setting configurations for the IMX390, DS90UB933-Q1, and DS90UB954-Q1 devices.

 


Figure 3-2. Block Diagram of Test Setup

3.1.2 FPD-Link III I²C Initialization

With the setup in [Figure 3-2](#) connected, the DS90UB954-Q1 EVM is supplied 12-V input power, which is regulated to 9-V with an onboard LDO and delivered through POC to power the TIDA-050050 camera module. Once all rails are established, all devices (OX01F10, DS90UB933-Q1, and DS90UB954-Q1) receive power. Then, the I²C writes for initialization can begin. Note that the following writes are only showing one channel camera and may not be the mode wanted for specific multi-camera mode. The Analog LaunchPad compatible Python[®] script to initialize the DS90UB954-Q1 deserializer and DS90UB933-Q1 serializer are as follows:

```
# Set up Port1
board.WriteI2C(UB954, 0x4C, 0x12)

# Set up Back Channel Config (0x58)
board.WriteI2C(UB954, 0x58, 0x58)

# Set up SER Alias ID
board.WriteI2C(UB954, 0x5C, UB933)

# Set up Slave/Camera ID
board.WriteI2C(UB954, 0x5D, SensorID)

# Set up Slave/Camera Alias ID
board.WriteI2C(UB954, 0x65, Sensor)

# Set GPIO2 output high, where GPIO2 = XSHUTDOWN
board.WriteI2C(UB933, 0x0D, 0x95)
```

3.1.3 OX01F10 Initialization

Once the FPD-Link III setup is done for the DS90UB933-Q1 and DS90UB954-Q1 devices, the I²C initialization can now be done on the OX01F10. For these writes, see the OX01F10 data sheet for register settings. There are many register settings listed to configure both the imager and ISP, but as long as the DS90UB933-Q1 and DS90UB954-Q1 FPD-Link III parts are configured, the I²C back channel allows for the OX01F10 to be accessed at address 0x6C. For this testing, the OX01F10 is configured for YUV422 DVP output at 1340 × 1020 resolution.

3.2 Test Setup

For the following tests to verify power supply and I²C communication, the camera is connected to the DS90UB954-Q1 EVM.

 


Figure 3-3. Block Diagram of Characterization Test Setup

3.2.1 Power Supplies Start Up

To verify the power supply sequencing and start-up behavior, each voltage rail output from the TPS650320-Q1 device is measured after applying power over coax to the system.

In this design, the PDB reset signal of the DS90UB933-Q1 device is connected directly to the nRSTOUT pin of the TPS650320-Q1 device. With the integrated sequencing capabilities of the PMIC, this ensures that the PDB reset line goes high after the 1.8-V supply is stable, eliminating the need for an external RC network.

3.2.2 Setup for Verifying I²C Communications


Back-channel I²C communications are verified with the DS90UB954-Q1 compatible GUI, Analog LaunchPad. The GUI is available for download [here](#).

3.3 Test Results

The following sections show the test data from verifying the functionality of the camera design.

3.3.1 Power Supplies Start-Up

Figure 3-4 shows the start-up behavior for the 3.8-V, 1.8-V, 1.1-V, and 3.3-V rails.

 


(Channel 1): 3.3-V supply; (Channel 2): 2.9-V supply; (Channel 3): 1.2-V supply; (Channel 4): 1.8-V supply

Figure 3-4. Point-of-Load Power Supply Start-Up

3.3.2 Power Supply Start-Up—1.8-V Rail and PDB

To properly initialize, the PDB pin of the serializer remains low until all power supplies stabilize to their final voltages. Figure 3-5 shows the power supply start up. Note that the PDB pin is directly connected to $\overline{\text{RSTOUT}}$ of the TPS650320-Q1 device and allows proper PDB synchronization after all rails are established.

 

(Channel 1): PDB; (Channel 2): 2.9-V supply; (Channel 3): 1.2-V supply; (Channel 4): 1.8-V supply

Figure 3-5. Serializer Power-Up Sequence

3.3.3 Power Supply Voltage Ripple

To achieve a quality output video stream, the output voltage ripple on the OX01F10 and DS90UB933-Q1 supplies must be low so that it does not affect the integrity of the high-speed data and internal PLL clocks. Measurements for 3.8-V, 3.3-V, 1.8-V, and 1.1-V rails are shown in Figure 3-6, Figure 3-7, and Figure 3-8, respectively. The rails that impact imager performance are the 3.3-V and 1.1-V rails as they are responsible for providing a clean analog rail and digital supply. The 3.8-V rail powers the entire system and also has excellent ripple performance of 0.4%. As measured, the 3.3-V and 1.1-V rails have a ripple performance of 0.1% and 0.7%, respectively. The 1.8-V rail is significant to the serializer, because it supplies the VDD and VDD_PLL rails. The 1.8-V rail has great voltage ripple performance at 0.5%. The voltage ripple on all rails is low enough for video output to be successfully transmitted.

 


Figure 3-6. Output Voltage Ripple - 3.8 V

 


Figure 3-7. Output Voltage Ripple - 3.3 V

 


Figure 3-8. Output Voltage Ripple - 1.8 V

 


Figure 3-9. Output Voltage Ripple - 1.1 V

3.3.4 Power Supply Load Currents

The last measurements to take in regard to the power supplies on the camera module are the load currents for the system supply, and the load currents on the OX01F10 imager. These measurements verify total power consumption of the camera module as well as the load current for each individual rail on the OX01F10 imager. For the following test data, each rail is drawing the specific load current outlined for the serializer and imager. All load current measurements are taken while a video output stream is present.

Table 3-1 displays the currents measured through each supply voltage in this reference design. The 9-V load current is the total input load for the camera module and measures at 85 mA. The total power consumption corresponds to an overall system efficiency of 67%, close to the 68% value derived in Section 2.4.

Table 3-1. Measured Supply Currents

VOLTAGE RAIL	MEASURED CURRENT
9.0 V	85 mA
3.8 V	153 mA
3.3 V	31 mA
1.8 V	130 mA
1.1 V	151 mA

3.3.5 I²C Communications

I²C communication between the DS90UB954-Q1 EVM and OX01F10 imager over the FPD-Link III back channel can be confirmed with the Analog LaunchPad GUI. Figure 3-10 and Figure 3-11 show the established link with the serializer on RX port 1, and the corresponding register map.

 


Figure 3-10. Analog LaunchPad™ Link Confirmation

 


Figure 3-11. Serializer Remote Registers

Read and writes to the imager, at slave alias address 0x6C (7-bit), are confirmed with the built-in Python scripting window of the Analog LaunchPad. Register 0x3035 reads data 0x6C, which is the expected default value for the register.

 


Figure 3-12. Back-Channel I2C Communication

4 Design and Documentation Support

4.1 Design Files

4.1.1 Schematics

To download the schematics, see the design files at [TIDA-050050](#).

4.1.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-050050](#).

4.1.3 PCB Layout Recommendations

4.1.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-050050](#).

4.1.3.2 PMIC Layout Recommendations

The PMIC portion of the layout requires careful consideration to minimize both PCB area and noise. As EMI is a critical concern in automotive systems, the TPS650330-Q1 device includes a spread spectrum feature to reduce conducted and radiated emissions, allowing more flexibility with placement and layout for space-constrained applications. However, it is still recommended to follow as many best practices as possible. This includes minimizing the area traveled by switching currents between buck regulator input capacitor, inductor, and output capacitor with tight component placement and minimal return path to the PMIC thermal pad. [Figure 4-1](#) shows an example of this for buck 2.

For the LDO, separation of input and output capacitor ground planes will reduce noise coupling from the switching rails to the sensitive 3.3-V analog rail. To further reduce noise coupling, the dedicated AGND pin of the PMIC is connected to the ground plane on an internal layer with a via, rather than directly to the noisier thermal pad on the top layer.

 


Figure 4-1. PCB Layout With POC Routing

4.1.3.3 Serializer Layout Recommendations

Decoupling capacitors must be located very close to the supply pin on the serializer. Again, this requires consideration of the path of the supply current and the return current. Keeping the loop area of this connection small reduces the parasitic inductance associated with the connection of the capacitor. Due to space constraints, ideal placement is not always possible. For decoupling capacitors placed on the opposite layer of the serializer, minimize the return path to the serializer thermal pad. Place smaller value capacitors that provide higher frequency decoupling closest to the device.

For this application, a single-ended impedance of 50 Ω is required for the coax interconnect. Anti-pads are implemented in the ground plane under critical components such as the DOUT AC coupling capacitors to minimize impedance mismatch. Keep the coax connection to the serializer short. [Figure 4-1](#) shows the routing of the high-speed serial line, highlighted by the yellow line. The total length of the yellow line is about $\frac{1}{2}$ inch.

Lastly, minimize crosstalk between high-speed data lines by ensuring the high-speed data routing on adjacent layers do not overlap. If they must overlap due to space constraints, place a ground layer between the two

routing layers as a buffer. Keep high speed trace vias to a minimum. The vias must ideally be two or fewer to reduce stubs that cause reflections.

4.1.3.4 Imager Layout Recommendations

High-speed data routing must follow the same guidelines previously outlined for the serializer layout. Similarly, place the decoupling capacitors as close as possible to the supply pins, with smaller capacitors taking priority in terms of distance to the pin. Minimize the parasitic resistance and inductance to the ground plane with vias and wide traces. For some imagers, a separate analog ground (AGND) plane is recommended to reduce image noise. Connect imager AGND pins, AVDD decoupling capacitors, and the LDO output capacitor to this AGND plane, and connect the plane back to the main ground at a single point.

4.1.3.5 PCB Layer Stackup Recommendations

Figure 4-2 shows the 8-layer stackup used for the PMIC and serializer board. Two signal layers are required due to the complex routing requirements introduced by the small size requirements of the PCB that must include I2C, logic IOs, clock, and control signals between the PMIC, serializer, and imager. The separation of the outer layers is selected to ensure a characteristic impedance of 50 Ω, ±10%

In this design, high current components are placed on both the top layer and the bottom layer, so Layer 2 and Layer 7 in the stackup are dedicated ground planes to minimize high current return paths. A separate AGND plane is also included on Layer 7 for the imager.

Layer Name	Type	Material	Thickness (mil)	Dielectric Material	Dielectric Constant	Pullback (mil)	Orientation	Coverlay Expansion
Top Overlay	Overlay							
Top Solder	Solder Mask/...	Surface Mat...	0.4	Solder Resist	3.5			0
1 Top Layer	Signal	Copper	2.1				Top	
Dielectric 1	Dielectric	Core	6	FR-4 High Tg	4.2			
2 GND 1	Signal	Copper	1.4				Not Allowed	
Dielectric 2	Dielectric	Core	6	FR-4 High Tg	4.2			
3 Signal 1	Signal	Copper	1.4				Not Allowed	
Dielectric 3	Dielectric	Prepreg	6	FR-4 High Tg	4.2			
4 Signal 2	Signal	Copper	1.4				Not Allowed	
Dielectric 4	Dielectric	Core	12.6	FR-4 High Tg	4.2			
5 Power	Signal	Copper	1.4				Not Allowed	
Dielectric 5	Dielectric	Core	6	FR-4 High Tg	4.2			
6 Signal 3	Signal	Copper	1.4				Not Allowed	
Dielectric 6	Dielectric	Core	6	FR-4 High Tg	4.2			
7 GND 2	Signal	Copper	1.4				Not Allowed	
Dielectric 7	Dielectric	Core	6	FR-4 High Tg	4.2			
8 Bottom Layer	Signal	Copper	2.1				Bottom	
Bottom Solder	Solder Mask/...	Surface Mat...	0.4	Solder Resist	3.5			0
Bottom Over...	Overlay							

Total Thickness: 62mil

Figure 4-2. Layer Stackup

4.1.4 Altium Project

To download the Altium project files, see the design files at [TIDA-050050](#).

4.1.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-050050](#).

5 Tools and Software

Tools

[Concise Description](#)

Description

Software

[Concise Description](#)

Description

6 Documentation Support

1. Texas Instruments, [TPS650320-Q1 EVM](#) user's guide
2. Texas Instruments, [DS90UB95x-Q1EVM Deserializer](#) user's guide
3. Texas Instruments, [DS90UB933-Q1 FPD-Link III Serializer for 1-MP/60-fps Cameras 10/12 Bits, 100 MHz](#) data sheet
4. Texas Instruments, [Sending Power Over Coax in DS90UB913A Designs](#) application report
5. Texas Instruments, [Camera PMIC Spin Selection Guide](#) application report

7 Support Resources

[TI E2E™ support forums](#) are an engineer's go-to source for fast, verified answers and design help — straight from the experts. Search existing answers or ask your own question to get the quick design help you need.

Linked content is provided "AS IS" by the respective contributors. They do not constitute TI specifications and do not necessarily reflect TI's views; see TI's [Terms of Use](#).

8 Trademarks

TI E2E™ and LaunchPad™, and are trademarks of Texas Instruments.

Murata® is a registered trademark of Murata Manufacturing Co., Ltd..

TDK® is a registered trademark of TDK Electronics AG.

OmniVision® is a registered trademark of Omnivision Technologies Inc..

Python® is a registered trademark of Python Software Foundation.

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated