

# TI Designs: TIDA-01234

## 24-W Boost and Boost-to-Battery Reference Design for Automotive LED Lighting



### Description

This reference design is a 24-W, high-efficiency (94%), low-cost, asynchronous boost design for automotive LED applications based on the LM3481-Q1.

### Resources

[TIDA-01234](#)

Design Folder

[LM3481-Q1](#)

Product Folder

[INA213-Q1](#)

Product Folder



[ASK Our E2E Experts](#)


### Features

- 24-W Automotive LED Driver Solution
- Input: 6 to 18 V, Output: 24 V at 1 A for Boost and  $V_{IN} + 12 V$  at 1 A for Boost to Battery
- 94% System Efficiency at Full Load at 12  $V_{IN}$  for Boost
- 88.9% System Efficiency at Full Load at 12  $V_{IN}$  for Boost to Battery
- Switching Frequency: 350 kHz
- 0- to 1-A Full Range Analog Dimming
- Open Circuit Protection
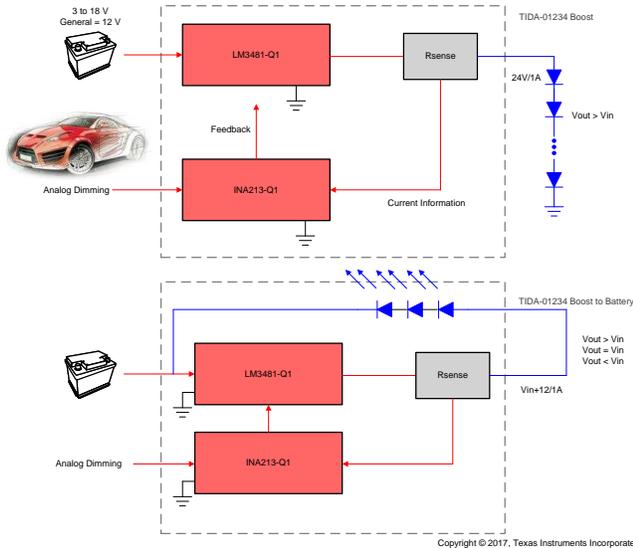
### Applications

- SMPS for Automotive LED Lighting

TIDA-01234  
24W Boost and Boost-to-Battery Reference Design for Automotive LED Lighting



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 1 System Description

This reference design is a 24-W, high-efficiency, low-cost, asynchronous boost design for automotive LED applications based on the LM3481-Q1. This design applies to automotive high brightness lighting such as headlights, tail lights, and interior LED lighting systems. The design also support analog LED brightness control and output open protection.

The design is divided into two major configurations:

1. Boost configuration:
  - Wide input range from 6 to 18  $V_{IN}$
  - Can drive multiple strings of six to seven LEDs at 1-A constant current
  - High efficiency (94%), low cost
2. Boost-to-battery configuration:
  - Wide input range from 6 to 18  $V_{IN}$
  - Input voltage can either be higher, lower, or equal to required LED strings voltage
  - High efficiency (89%), low cost

### 1.1 Key System Specifications


**Table 1. Key System Specifications**

PARAMETER	SPECIFICATIONS
$V_{IN}$ minimum	6-V DC
$V_{IN}$ maximum	18-V DC
$V_{OUT}$	16 to 24 V (boost only), 8 to 12 V (boost-to-battery)
LED drive current (maximum)	1 A
Approximate switching frequency	350 kHz
LED dimming	0 to 1 A with no flickering

## 2 System Overview

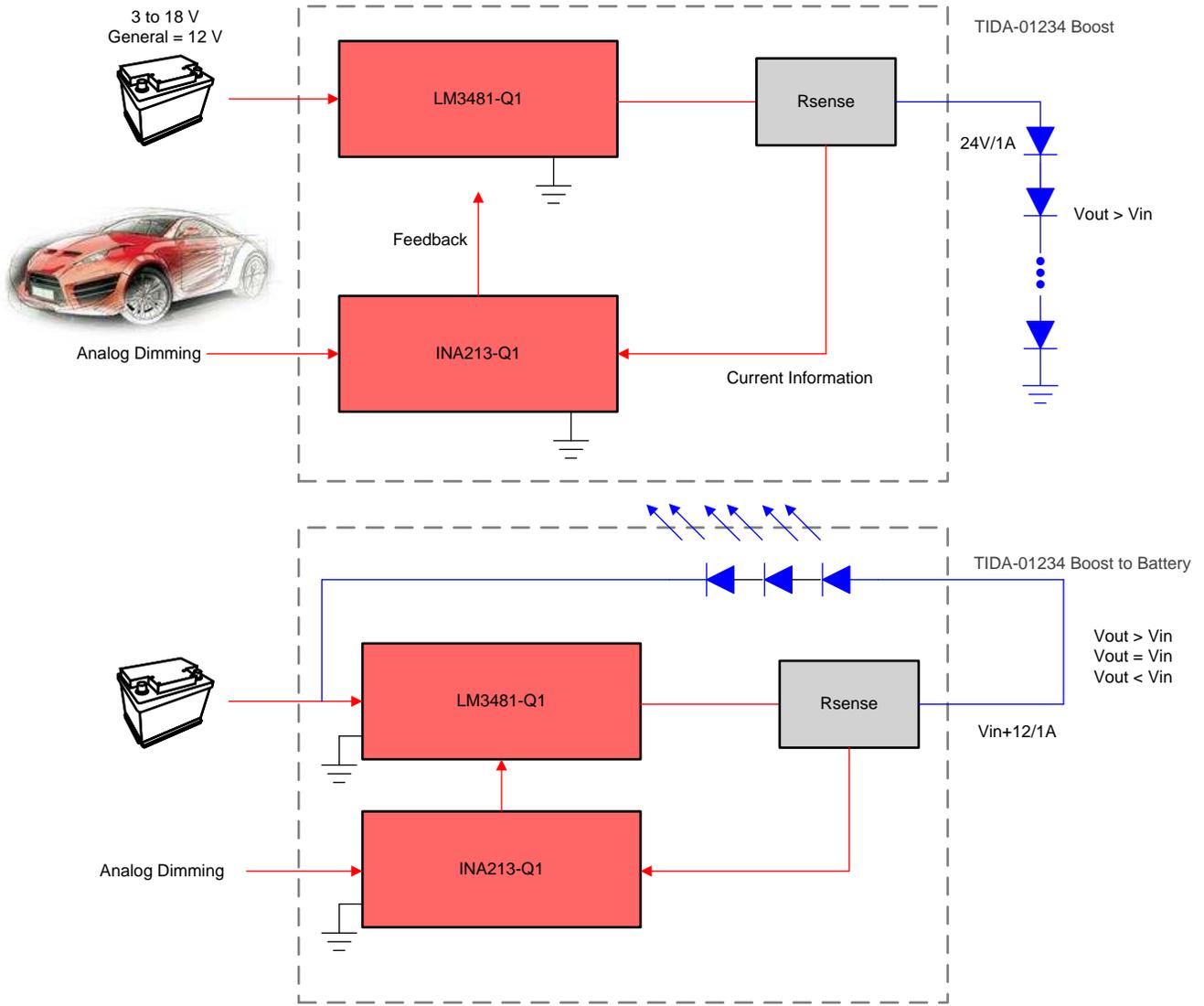
### 2.1 Block Diagram

TIDA-01234  
24W Boost and Boost-to-Battery Reference Design for Automotive LED Lighting



Copyright © 2017, Texas Instruments Incorporated

Figure 1. TIDA-01234 Block Diagram

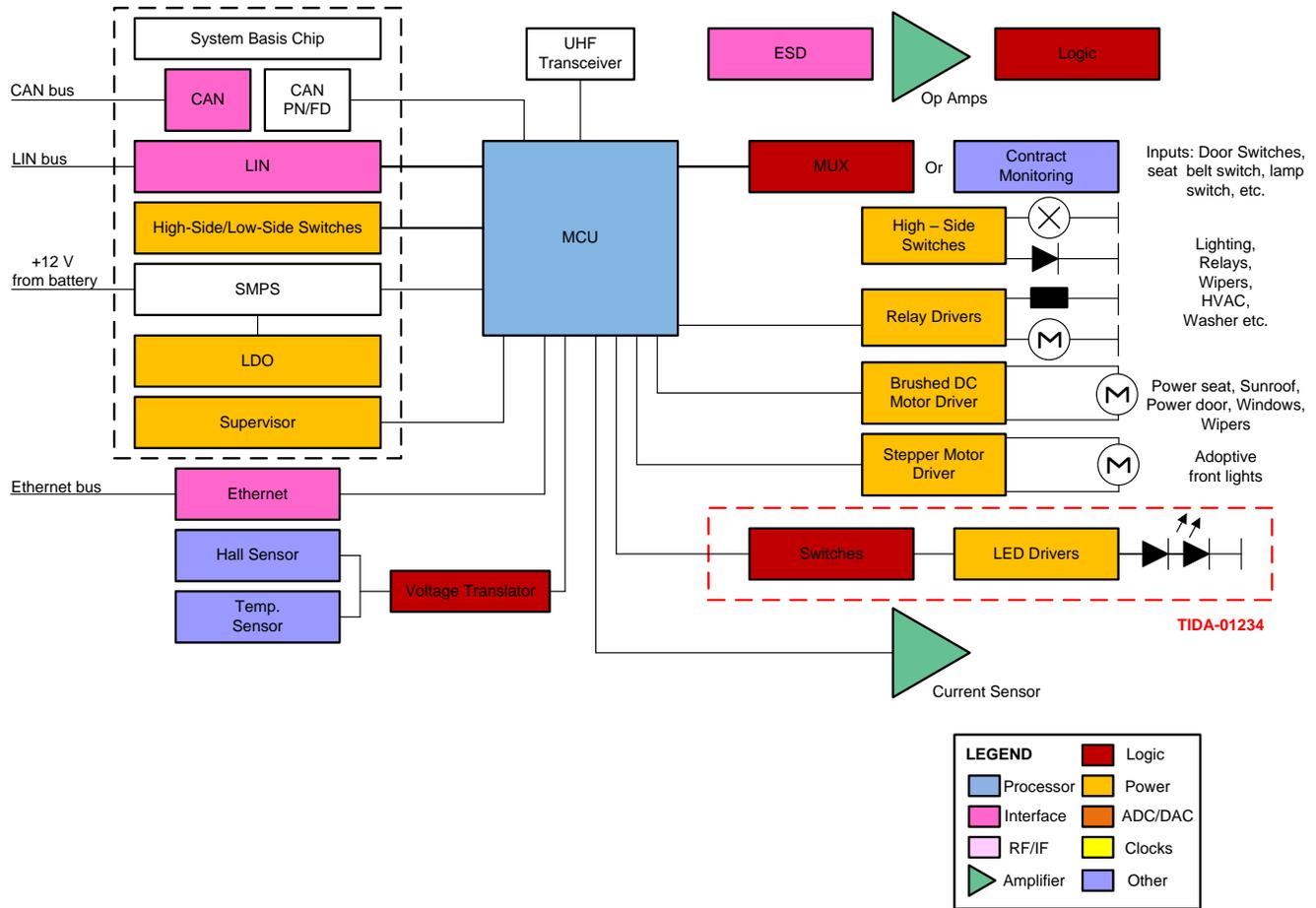

Copyright © 2017, Texas Instruments Incorporated

Figure 2. Automotive LED Lighting Example Highlighting TIDA-01234

## 2.2 Highlighted Products

The following TI products are used in this reference design.

### 2.2.1 LM3481-Q1

- AEC-Q100 grade 1 qualified temperature:  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  operating junction temperature
- Wide supply voltage range: 2.97 to 48 V
- 100-kHz to 1-MHz adjustable and synchronizable clock frequency
- Pulse skipping at light loads
- Adjustable undervoltage lockout (UVLO) with hysteresis
- Internal soft-start

### 2.2.2 INA213-Q1

- AEC-Q100 grade 1 qualified temperature:  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  operating junction temperature
- Wide common-mode range:  $-0.3$  to 26 V
- Offset voltage:  $\pm 100\ \mu\text{V}$  (maximum; enables shunt drops of 10-mV full-scale)
- Accuracy:
  - $\pm 1\%$  gain error (maximum over temperature)
  - $0.5\text{-}\mu\text{V}/^{\circ}\text{C}$  offset drift (maximum)
  - $10\text{-ppm}/^{\circ}\text{C}$  gain drift (maximum)
- Quiescent current: 100  $\mu\text{A}$  (maximum)
- SC70 package

## 2.3 System Design Theory

### 2.3.1 Boost Description

Generally, the output voltage can be programmed using a resistor divider and feedback pins. The output current depends on the load requirement. But for an LED application, constant current is necessary to keep a specific lightness. This design used current sensing to achieve constant current by the boost controller LM3481-Q1.

To keep constant current flowing through LED, there is a current sense resistor,  $R_{SHUNT}$ , at the output of the controller to sense how much current flows through it. This reference design uses a 50-m $\Omega$  current sense resistor to generate 50 mV of crossing voltage. This crossing voltage will be amplified by the INA213-Q1, which provides a gain = 50 V/V. Using an external voltage injected into the current sense amplifier reference at J1 allows for analog dimming of the LEDs at the output by changing the output current, as shown in Equation 1:

$$V_{FB} = \left[ (I_{OUT} \times R_{SHUNT}) + V_{REF} \right] \times \frac{R3}{R3 + R4} \tag{1}$$

where:

- $V_{FB}$  is 1.275 V
- $R_{SHUNT}$  is 50 m $\Omega$
- R3 equal to R4 are 10 k $\Omega$

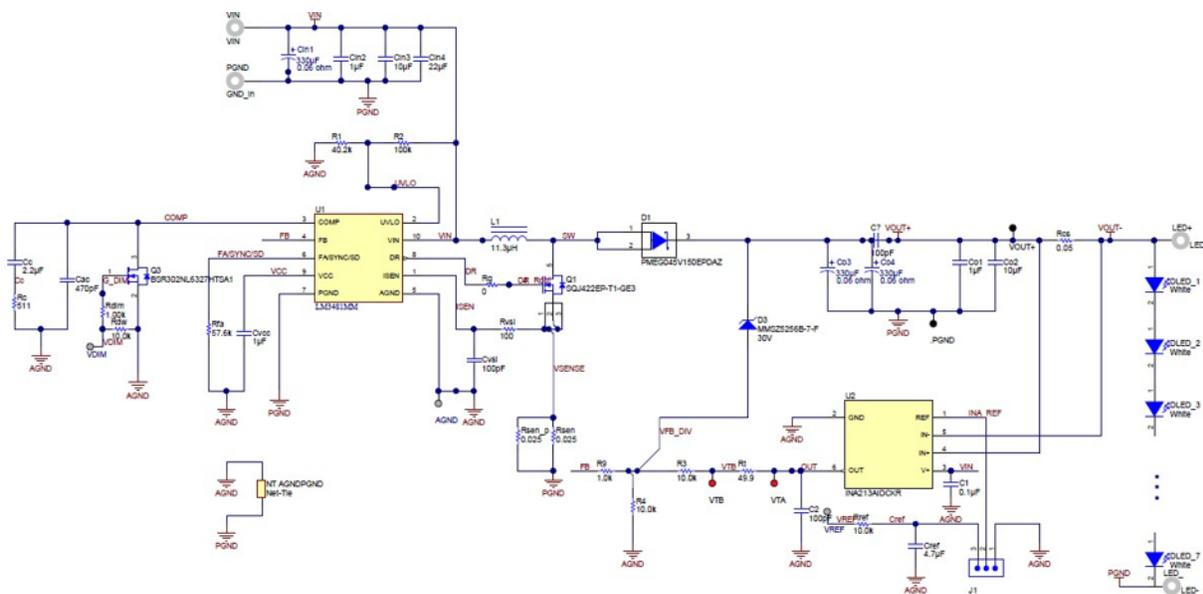


Figure 3. Boost Configuration and LM3481 Schematic

If the output LED burns out or is open at the output circuit, the output voltage will continuously rise. The TIDA-01234 design provides output open circuit protection. For the boost configuration, a Zener diode connected between  $V_{OUT}$  and VFB\_DIV, clamping the output voltage at the Zener voltage  $V_z$  plus the output voltage of the current sense amplifier.

### 2.3.2 Boost-to-Battery Description

In order to generate constant current with an output voltage closed to the input voltage, the designer must use a buck-boost or a SEPIC structure, which is complex and costly. By connecting the cathode of LED strings to the input instead of the GND, the TIDA-01234 can also be modified to boost-to-battery configuration. In this configuration, input voltage can either be higher, lower, or equal to the required LED strings voltage.

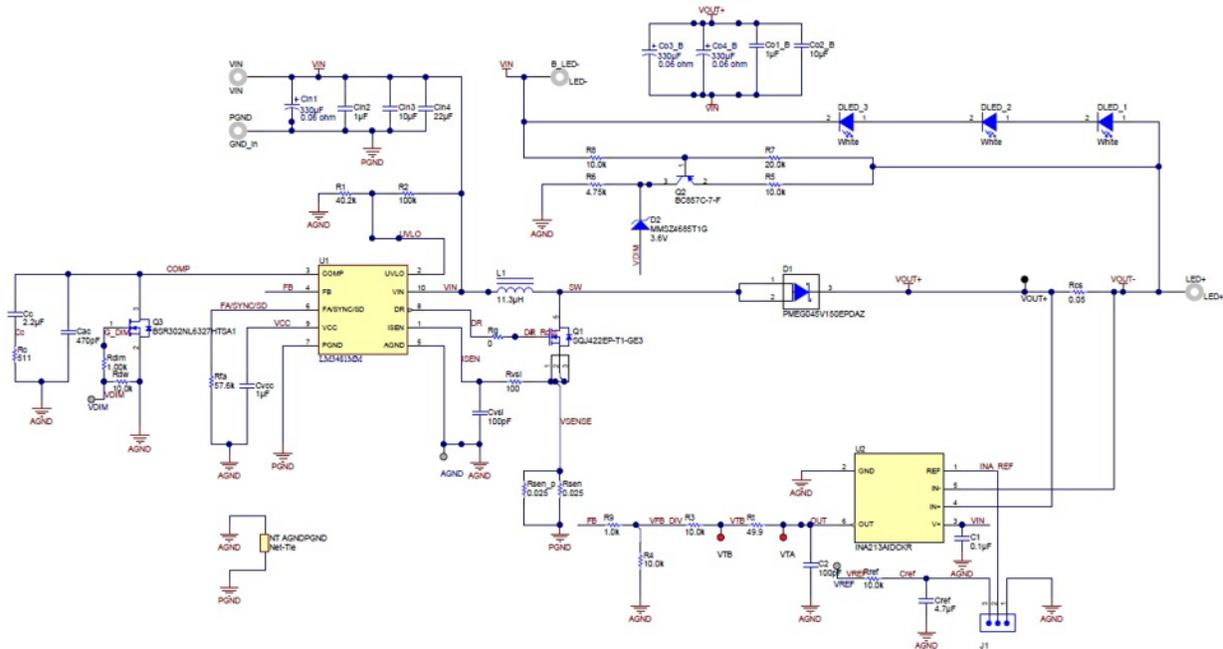


Figure 4. Boost-to-Battery Configuration and LM3481 Schematic

For boost-to-battery, the TIDA-01234 provides another solution for open circuit protection by using transistor Q2 combined with R5, R6, R7, R8, and D2 to detect differential voltage between output voltage and input voltage. When the differential voltage rises up to  $V_{OV}$ , where  $V_{OV}$  is overvoltage at the output, Zener diode D2 will turn on and pull the comp pin voltage down by Q3. As a result, the output voltage will stay low until the load is connected.

For design calculations and layout examples, see the devices' respective datasheets:

- *LM3481-Q1 High-Efficiency Controller for Boost, SEPIC and Flyback DC-DC Converters* ([SNVS346](#))
- *INA21x-Q1 Automotive-Grade, Voltage Output, Low- or High-Side Measurement, Bidirectional, Zero-Drift Series, Current-Shunt Monitors* ([SBOS475](#))

### 3 Testing and Results

#### 3.1 Boost Configuration Test Results

##### 3.1.1 Thermal Data

The infrared thermal image shown in [Figure 5](#) was taken at a steady state with 12 V<sub>IN</sub> and full load of a 1-A load current (current sense comparator reference set to 0 V) for boost configuration.

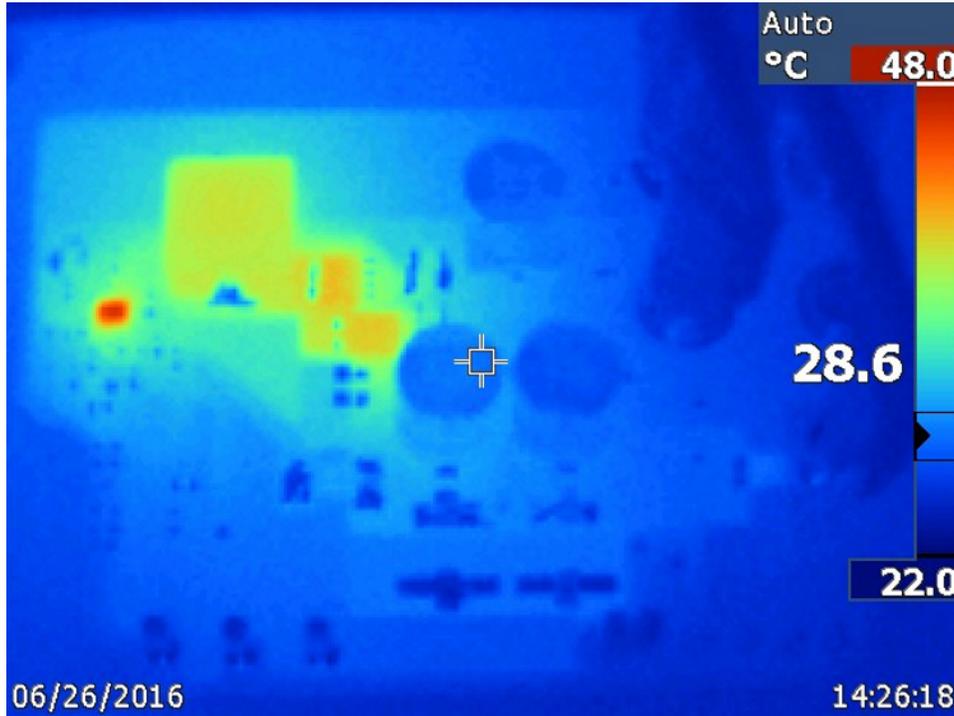


Figure 5. Thermal Image of Boost Configuration

##### 3.1.2 Efficiency Data

###### 3.1.2.1 Efficiency Chart

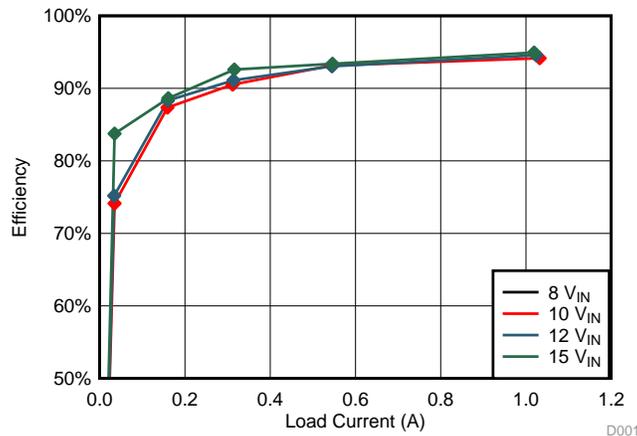


Figure 6. Boost Efficiency versus Load Current at Various Input Voltages

**3.1.2.2 Efficiency Data**
**Table 2. Boost Efficiency Table at 6 V<sub>IN</sub>**

REF (V)	V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	EFF (%)
0	6.004	4.278	23.67	1.009	92.98394
1.0	6.006	2.082	22.20	0.524	93.02897
1.8	6.002	0.835	20.67	0.218	89.91135
2.2	6.000	0.291	19.56	0.075	84.02062
2.5	6.000	0.002	11.63	0	0

**Table 3. Boost Efficiency Table at 10 V<sub>IN</sub>**

REF (V)	V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	EFF (%)
0	10.005	2.564	24.11	1.010	94.92563
1.0	10.006	1.251	22.17	0.525	92.98378
1.8	10.005	0.500	20.71	0.219	90.66447
2.2	10.008	0.181	19.59	0.076	82.19060
2.5	10.000	0.002	12.53	0	0

**Table 4. Boost Efficiency Table at 12 V<sub>IN</sub>**

REF (V)	V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	EFF (%)
0	12.006	2.140	24.02	1.010	94.42397
1.0	12.009	1.043	22.18	0.526	93.14427
1.8	12.002	0.423	20.74	0.219	89.46618
2.2	12.000	0.153	19.62	0.076	81.21569
2.5	12.000	0.002	11.96	0	0

**Table 5. Boost Efficiency Table at 15 V<sub>IN</sub>**

REF (V)	V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	EFF (%)
0	15.01	1.687	23.77	1.010	94.81014
1.0	15.005	0.833	22.19	0.526	93.38176
1.8	15.000	0.339	20.76	0.220	89.81711
2.2	15.004	0.114	19.64	0.076	87.26562
2.5	15.000	0.002	14.96	0	0

### 3.1.3 Boost Configuration Waveforms

#### 3.1.3.1 Switching and Output Current

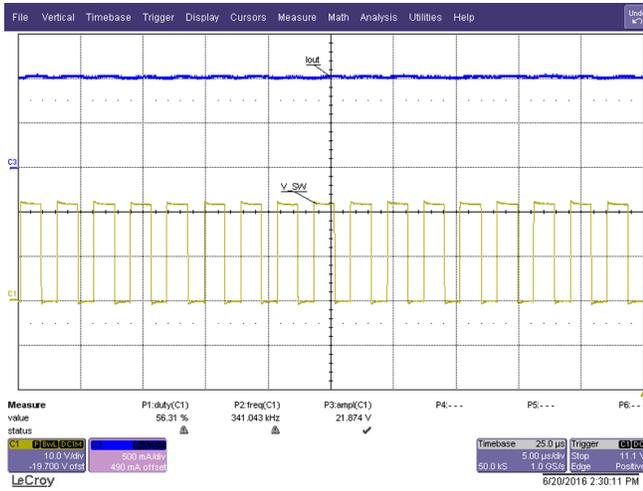


Figure 7. 12-V<sub>IN</sub> and 0-V Reference on Current Sense Comparator Provides Maximum Output Current

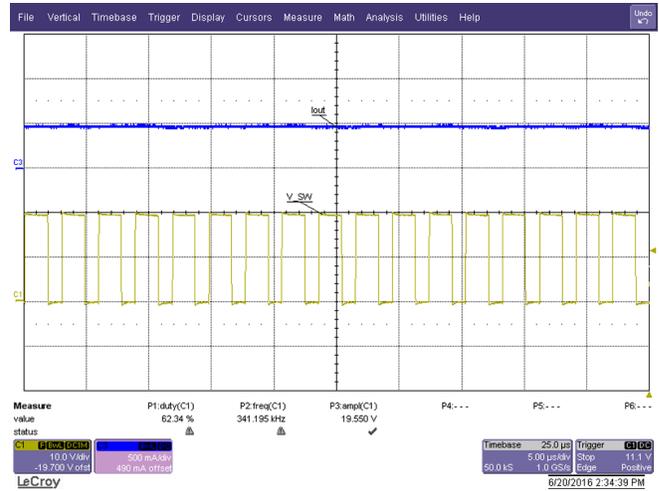


Figure 8. 12 V<sub>IN</sub> and 1.2-V Reference on Current Sense Comparator Provides Maximum Output Current


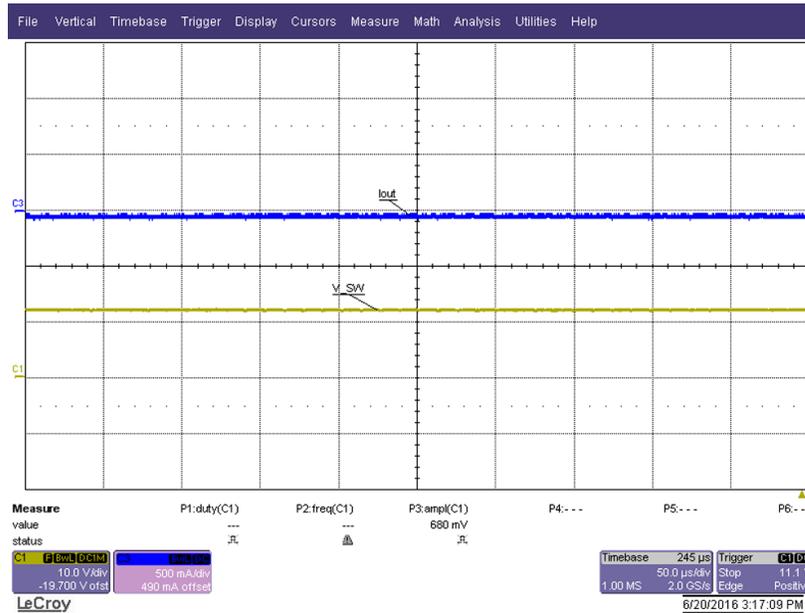



Figure 9. 12 V<sub>IN</sub> and 2.5-V Reference on Current Sense Comparator Provides Maximum Output Current

NOTE: Ch1 (yellow trace): Switch node voltage, Ch2 (pink trace): Output current


### 3.1.3.2 System Startup Waveforms

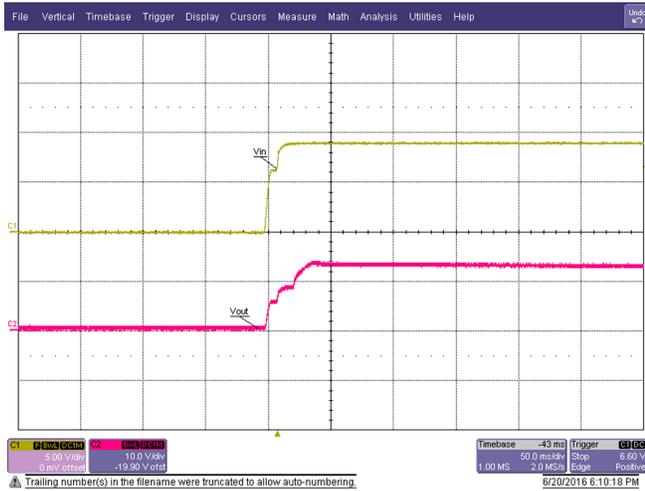


**Figure 10. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 2.5 V) at 9  $V_{IN}$**

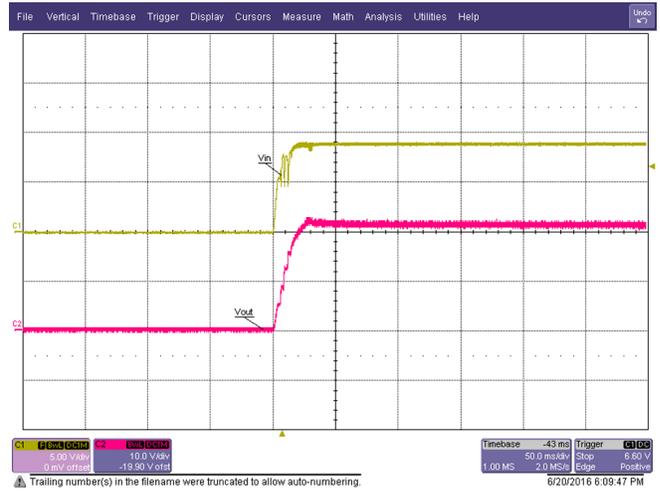

**Figure 11. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 0 V) at 9  $V_{IN}$**

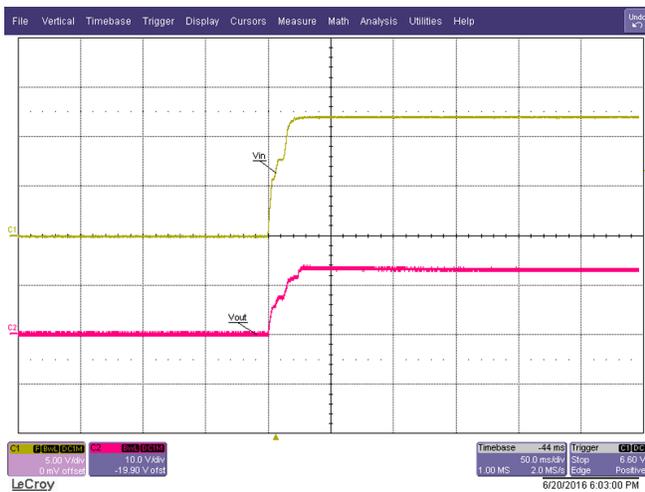

**Figure 12. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 2.5 V) at 12  $V_{IN}$**

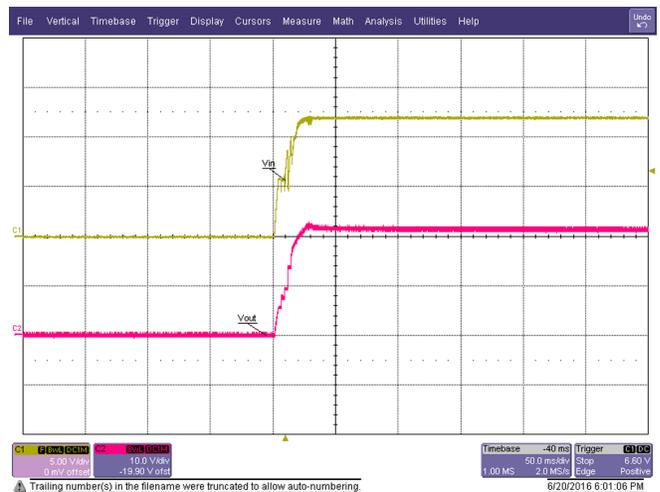

**Figure 13. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 0 V) at 12  $V_{IN}$**

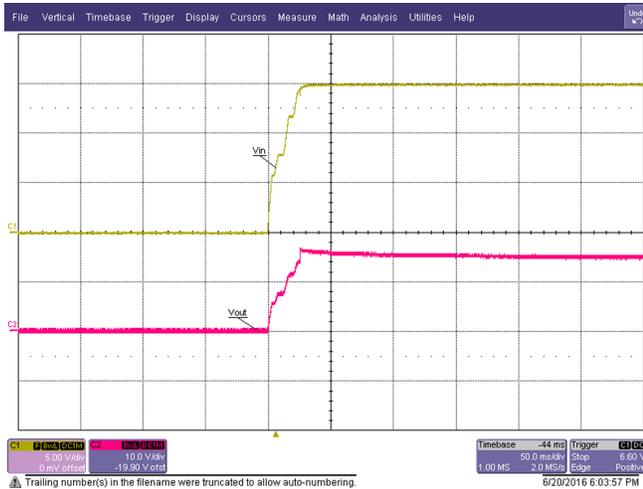


Figure 14. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 2.5 V) at 15 V<sub>IN</sub>

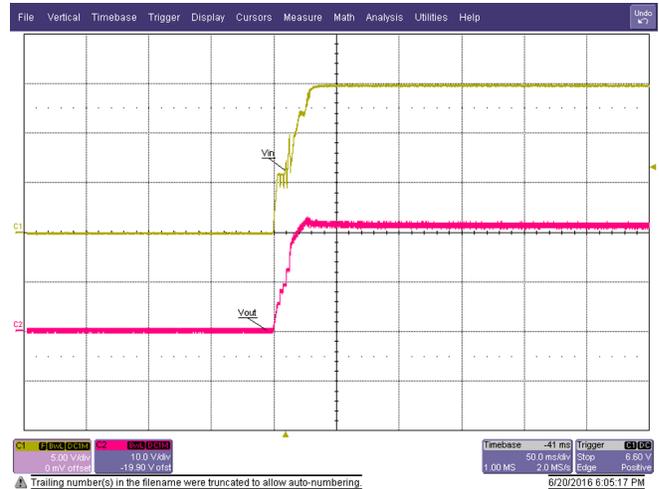


Figure 15. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 0 V) at 15 V<sub>IN</sub>

NOTE: Ch1 (yellow trace): V<sub>IN</sub>, Ch2 (pink trace): V<sub>OUT</sub>

### 3.1.4 Analog Dimming


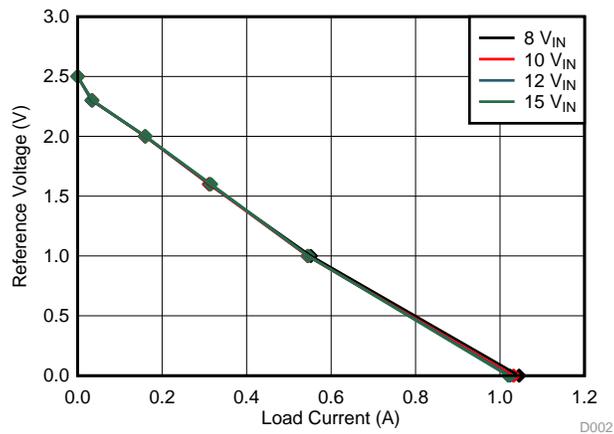



Figure 16. Reference Voltage for Current Sense Comparator versus Load Current

NOTE: Figure 16 shows the current regulation for the boost configuration.

### 3.1.5 Loop Response

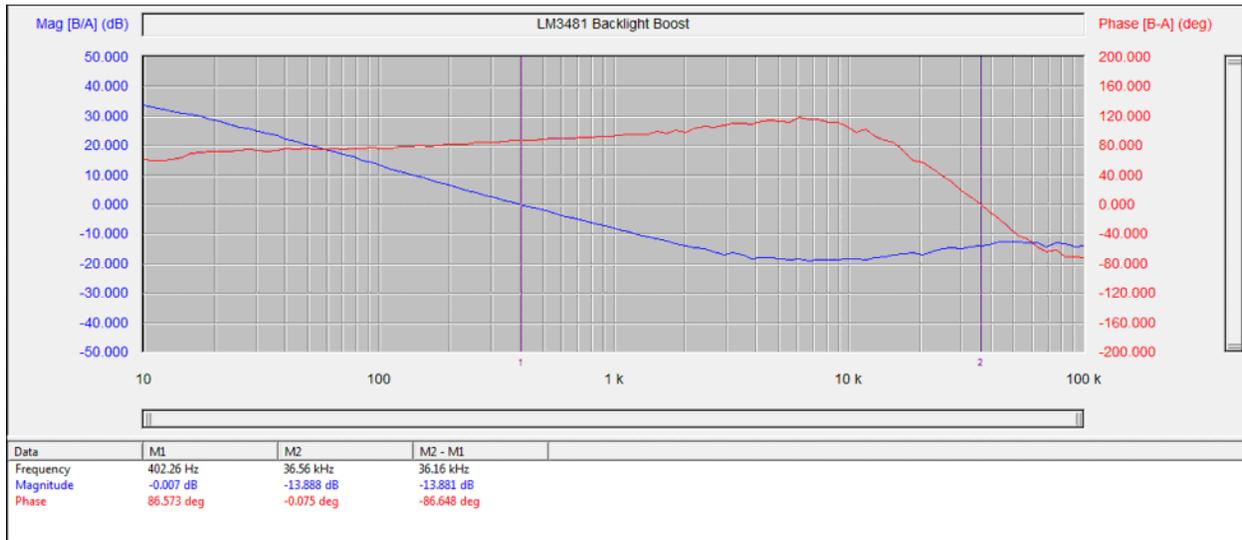

**Figure 17. 6-V<sub>IN</sub> Loop Response Showing a Stable System With Gain Margin: 13.8 dB and Phase Margin: 86.5°**

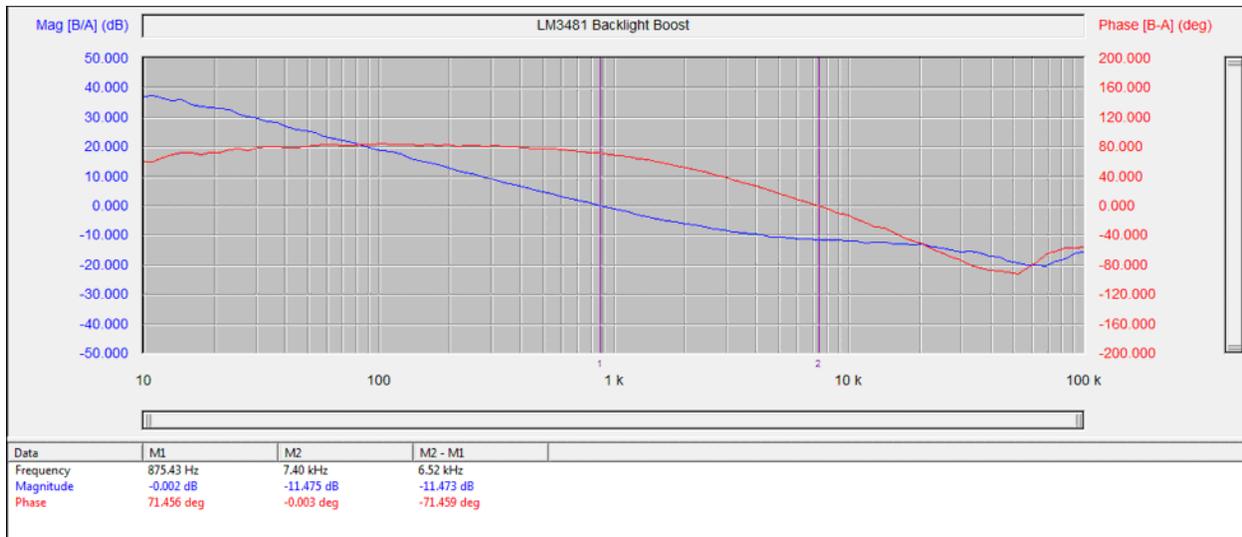

**Figure 18. 12-V<sub>IN</sub> Loop Response Showing a Stable System With Gain Margin: 11.4 dB and Phase Margin: 71.4°**

### 3.2 Boost-to-Battery Configuration Test Results

#### 3.2.1 Thermal Data

The infrared thermal image shown in Figure 19 was taken at steady state with 12 V<sub>IN</sub> and full load of a 1-A load current (current sense comparator reference set to 0 V) for boost-to-battery configuration.

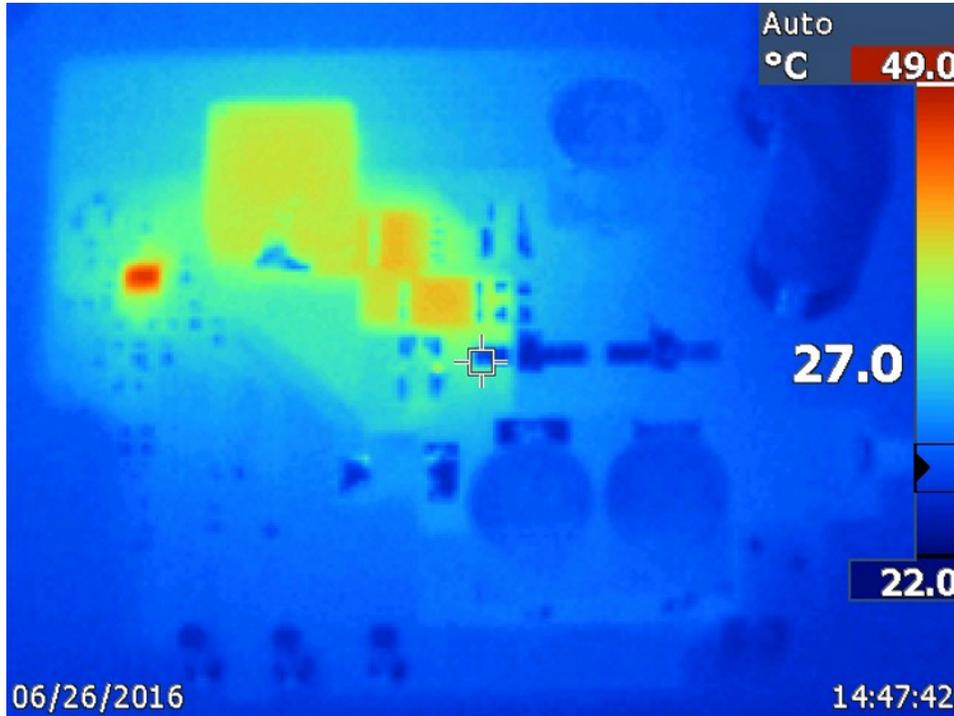


Figure 19. Thermal Image of Boost-to-Battery

#### 3.2.2 Efficiency Data

##### 3.2.2.1 Efficiency Chart

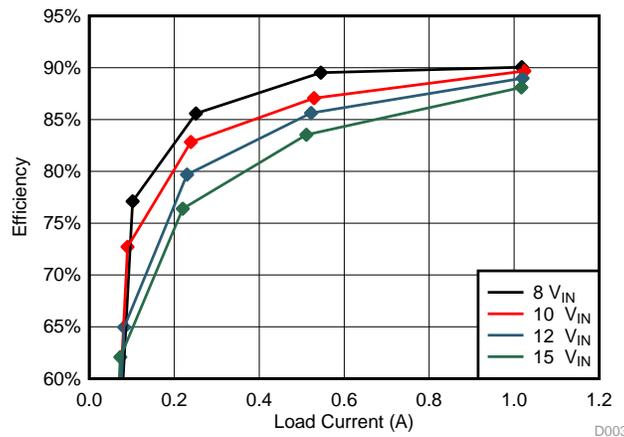


Figure 20. Boost-to-Battery Efficiency versus Load Current at Various Input Voltages

**3.2.2.2 Efficiency Data**
**Table 6. Boost-to Battery Efficiency Table at 6 V<sub>IN</sub>**

REF (V)	V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	EFF (%)
0	6.000	1.918	10.18	1.018	90.05249
1.0	6.000	0.970	9.56	0.545	89.52234
1.8	6.006	0.438	8.97	0.251	85.58679
2.2	6.002	0.188	8.53	0.102	77.10728
2.5	6.000	0.002	0	0	0

**Table 7. Boost-to Battery Efficiency Table at 10 V<sub>IN</sub>**

REF (V)	V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	EFF (%)
0	10.002	1.161	10.17	1.024	89.68129
1.0	10.004	0.577	9.50	0.529	87.06223
1.8	10.009	0.258	8.95	0.239	82.83436
2.2	10.008	0.105	8.49	0.090	72.71326
2.5	10.000	0.002	0	0	0

**Table 8. Boost-to Battery Efficiency Table at 12 V<sub>IN</sub>**

REF (V)	V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	EFF (%)
0	12.006	0.970	10.16	1.020	88.98643
1.0	12.002	0.482	9.49	0.522	85.63199
1.8	12.002	0.215	8.94	0.230	79.68439
2.2	12.000	0.089	8.46	0.082	64.95506
2.5	12.000	0.002	0	0	0

**Table 9. Boost-to Battery Efficiency Table at 15 V<sub>IN</sub>**

REF (V)	V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	EFF (%)
0	15.002	0.781	10.15	1.017	88.10221
1.0	15.001	0.387	9.49	0.511	83.53259
1.8	15.006	0.171	8.91	0.220	76.39050
2.2	15.003	0.066	8.42	0.073	62.07445
2.5	15.000	0.002	0	0	0

### 3.2.3 Boost-to-Battery Configuration Waveforms

#### 3.2.3.1 Switching and Output Current

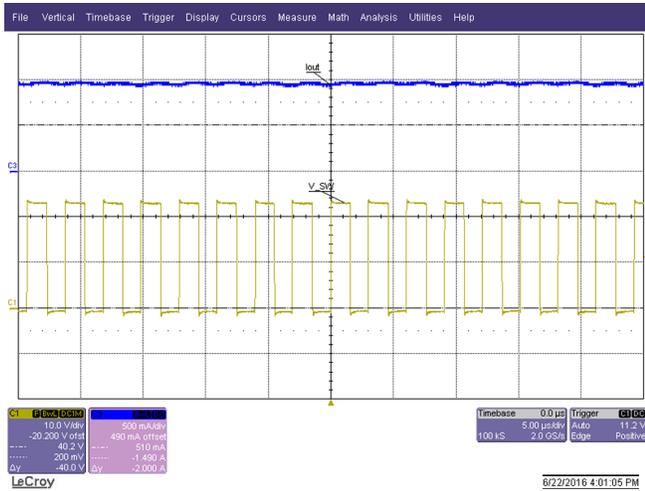


Figure 21. 12-V<sub>IN</sub> and 0-V Reference on Current Sense Comparator Provides Maximum Output Current

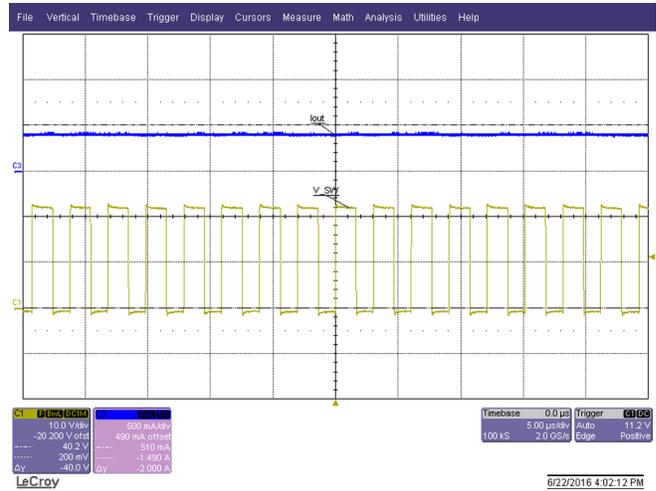


Figure 22. 12-V<sub>IN</sub> and 0-V Reference on Current Sense Comparator Provides Maximum Output Current


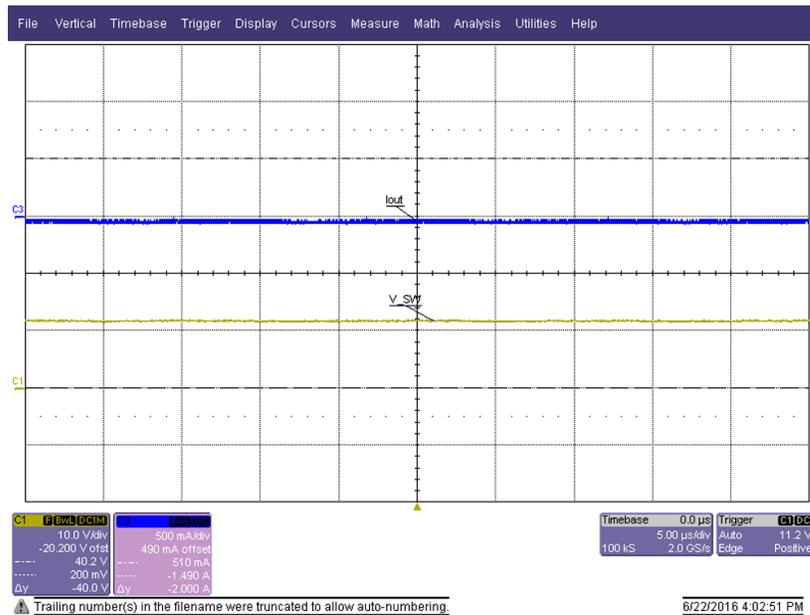



Figure 23. 12-V<sub>IN</sub> and 2.5-V Reference on Current Sense Comparator Provides Maximum Output Current

NOTE: Ch1 (yellow trace): Switch node voltage, Ch2 (pink trace): Output current


### 3.2.3.2 System Startup Waveforms

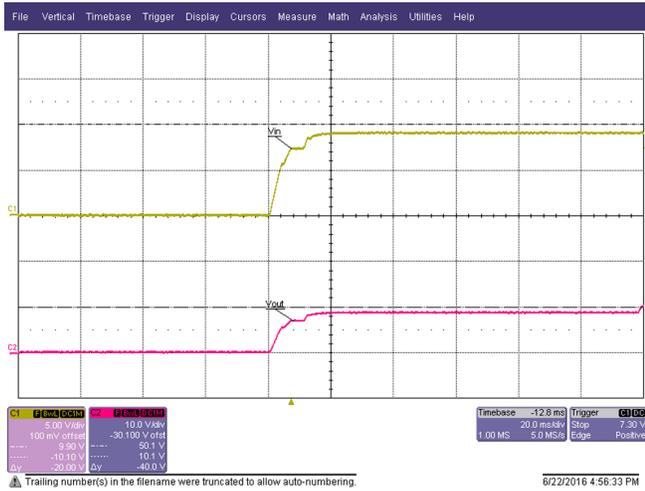


**Figure 24. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 2.5 V) at 9 V<sub>IN</sub>**

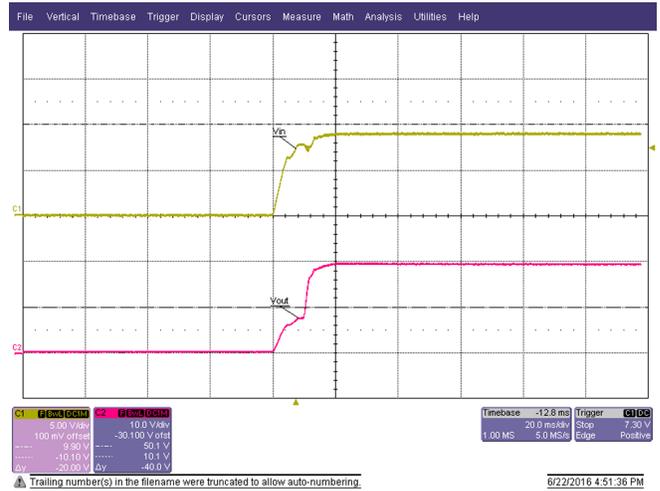

**Figure 25. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 0 V) at 9 V<sub>IN</sub>**

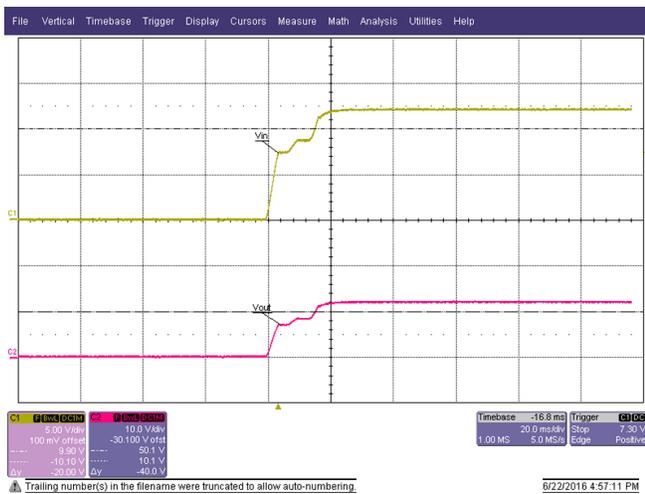

**Figure 26. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 2.5 V) at 12 V<sub>IN</sub>**

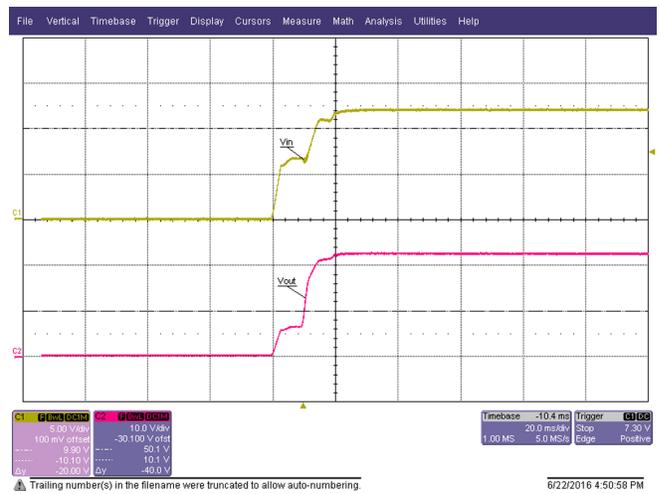

**Figure 27. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 0 V) at 12 V<sub>IN</sub>**

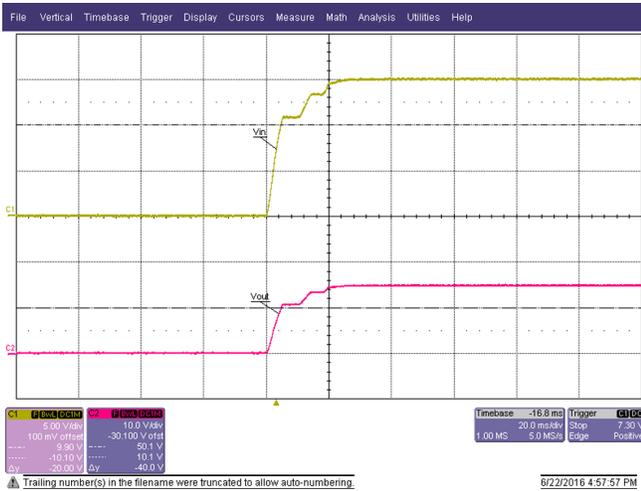


Figure 28. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 2.5 V) at 15 V<sub>IN</sub>

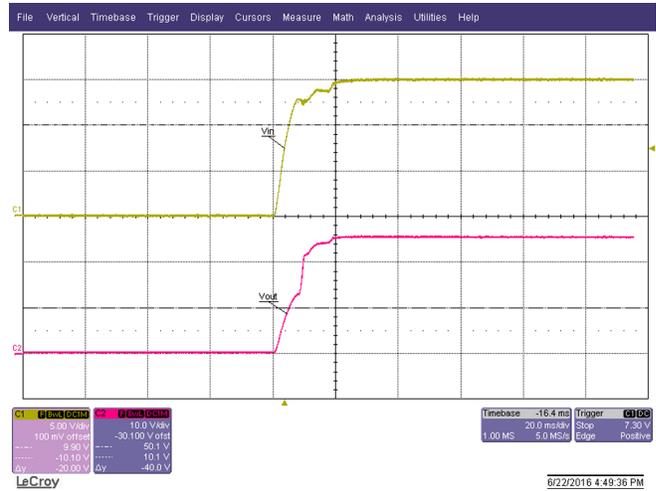


Figure 29. Startup Into No Load (Current Sense Comparator Reference Voltage Set to 0 V) at 15 V<sub>IN</sub>

NOTE: Ch1 (yellow trace): V<sub>IN</sub>, Ch2 (pink trace): V<sub>OUT</sub>

### 3.2.4 Analog Dimming

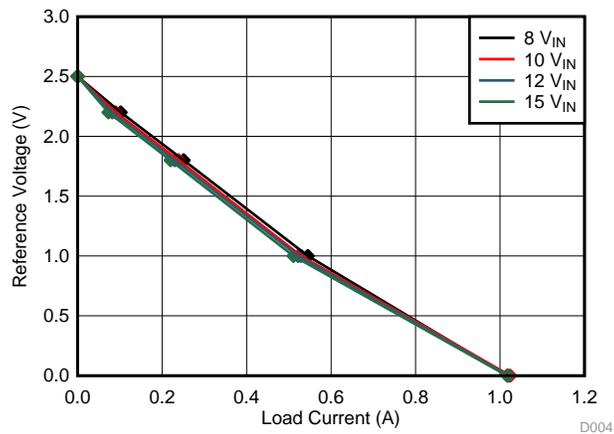


Figure 30. Reference Voltage for Current Sense Comparator versus Load Current

NOTE: Figure 30 shows the current regulation for the boost configuration.

### 3.2.5 Open Circuit Protection



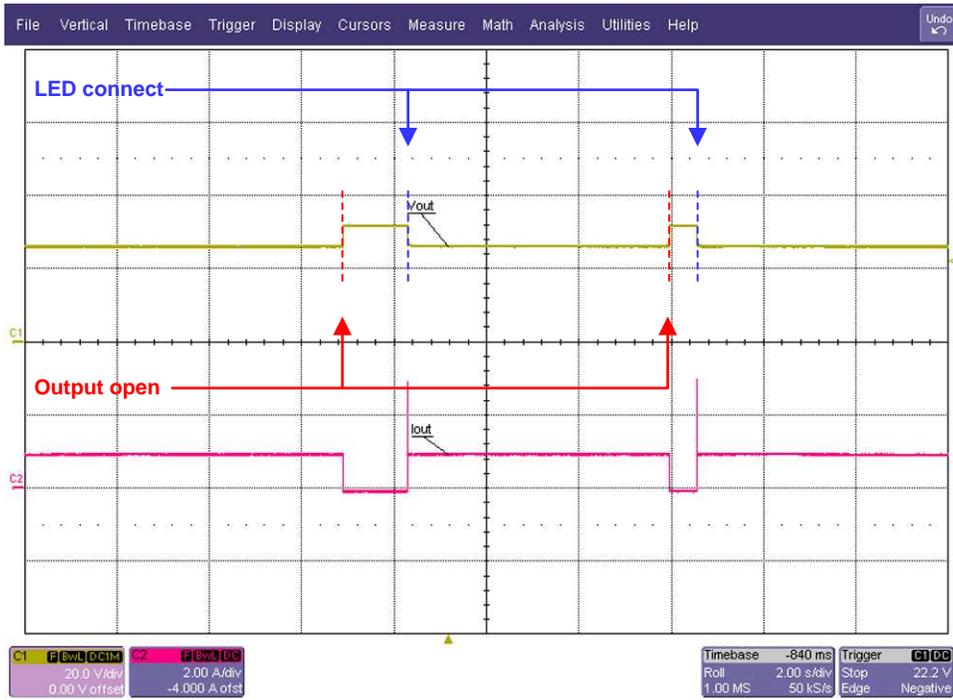


Figure 31. Boost-to-Battery Open Circuit Protection

### 3.2.6 Loop Response

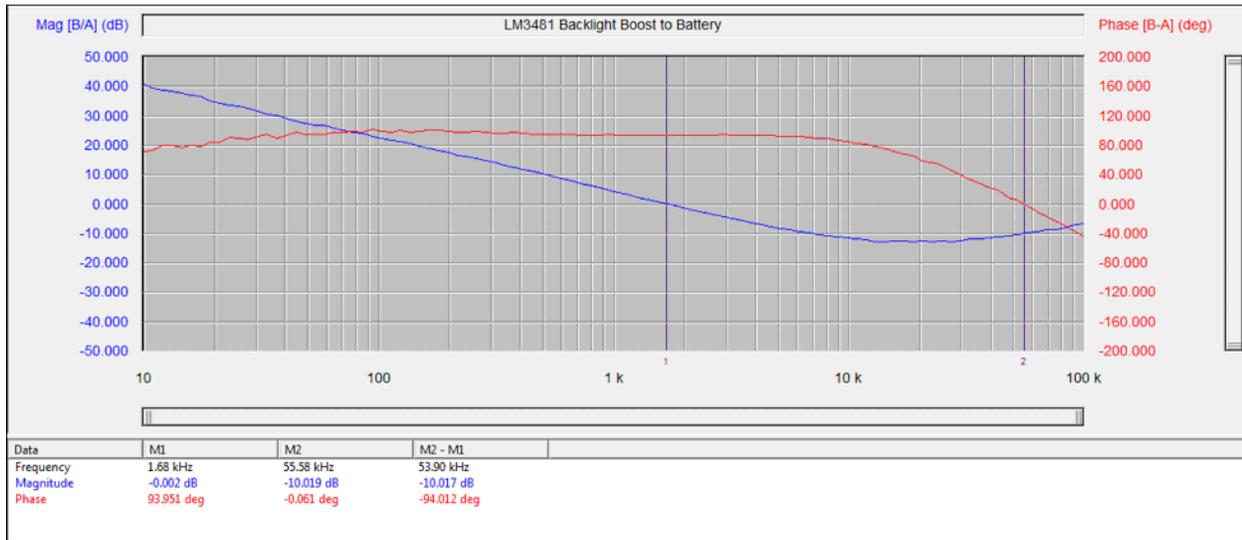

**Figure 32. 6-V<sub>IN</sub> Loop Response Showing a Stable System With Gain Margin: 10.0 dB and Phase Margin: 93.95°**

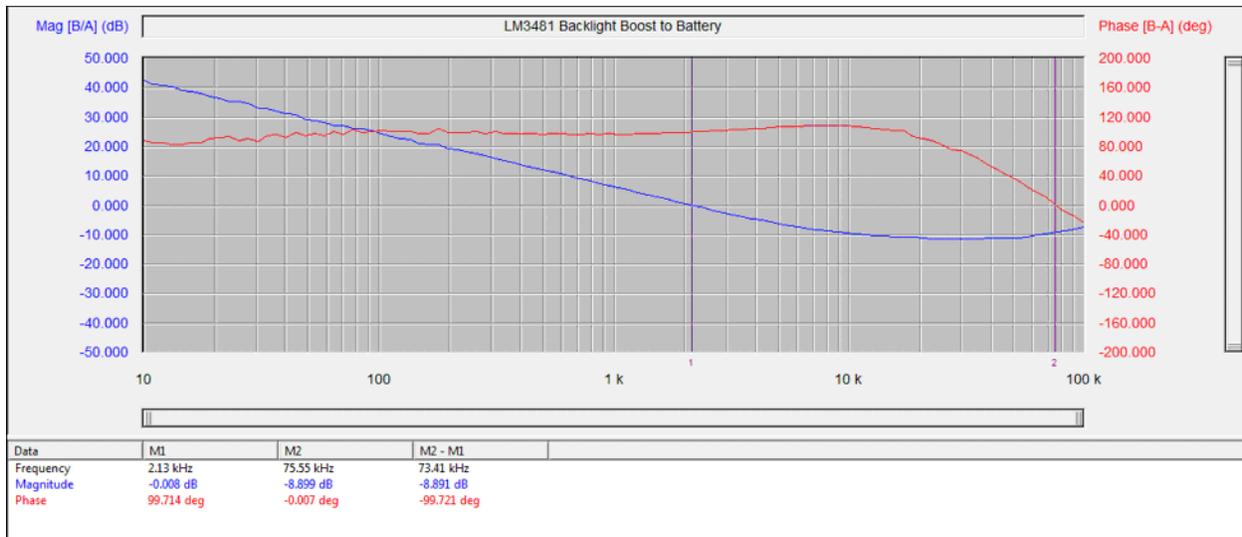

**Figure 33. 12-V<sub>IN</sub> Loop Response Showing a Stable System With Gain Margin: 8.9 dB and Phase Margin: 99.7°**

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-01234](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01234](#).

### 4.3 PCB Layout Recommendations

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01234](#).

### 4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01234](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01234](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01234](#).

## 5 Software Files

To download the software files, see the design files at [TIDA-01234](#).

## 6 Related Documentation

This reference design did not use any related documentation.

### 6.1 Trademarks

All trademarks are the property of their respective owners.

## 7 About the Author

**SHAQUILLE CHEN** is a field application engineer at Texas Instruments where he is responsible for major account in Taiwan. Shaquille earned his master of technology (M.Tech) from the National Taiwan University of Science and Technology in Taipei.

---

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from Original (August 2016) to A Revision</b>	<b>Page</b>
• Changed from preview draft to fit current design guide template .....	1

---

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated