
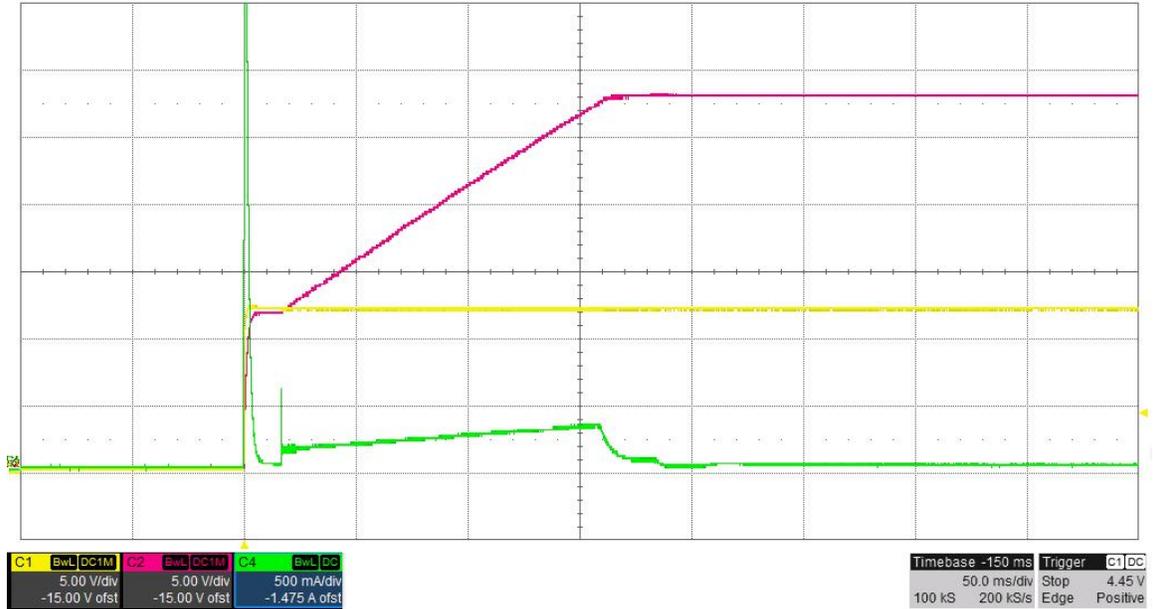


1 Startup

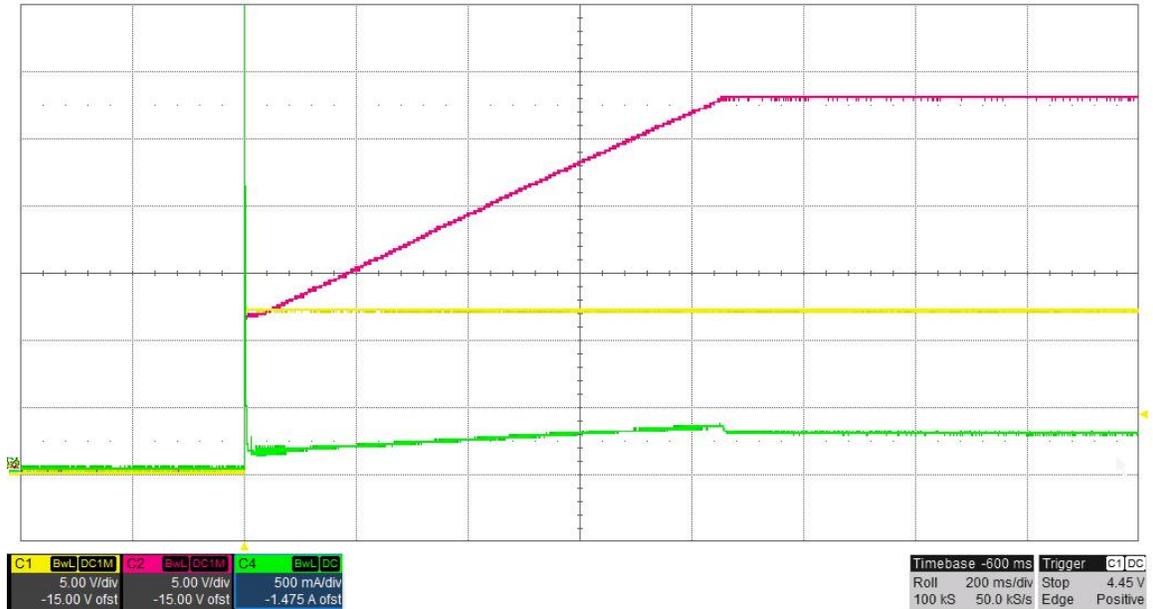The photo below shows the output voltage startup waveform after the application of 12V in with the 28V output loaded to 0A. The input current is shown in green. (5V/DIV, 500mA/DIV, 50ms/DIV)




The photo below shows the output voltage startup waveform after the application of 12V in with the 28V output loaded to 0.10A. The input current is shown in green. (5V/DIV, 500mA/DIV, 50ms/DIV)




2 Efficiency

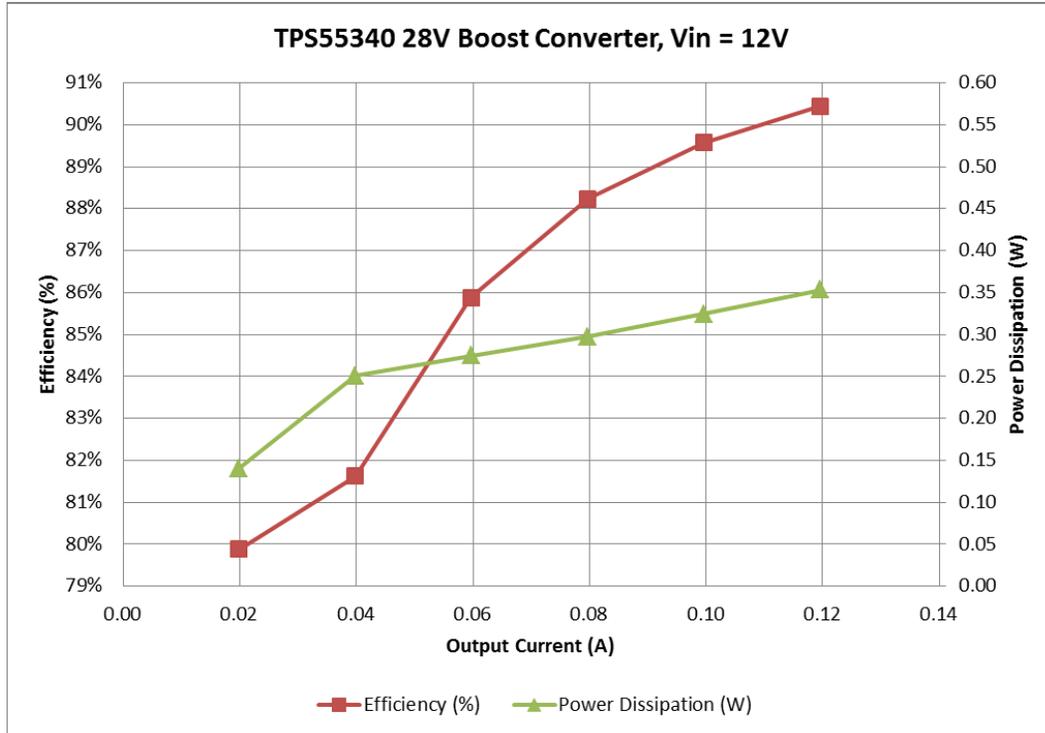The TPS55340 28V@0.12A boost converter efficiency is shown in the figure below. The converter is operating in voltage regulation mode.




3 Output Ripple Voltage

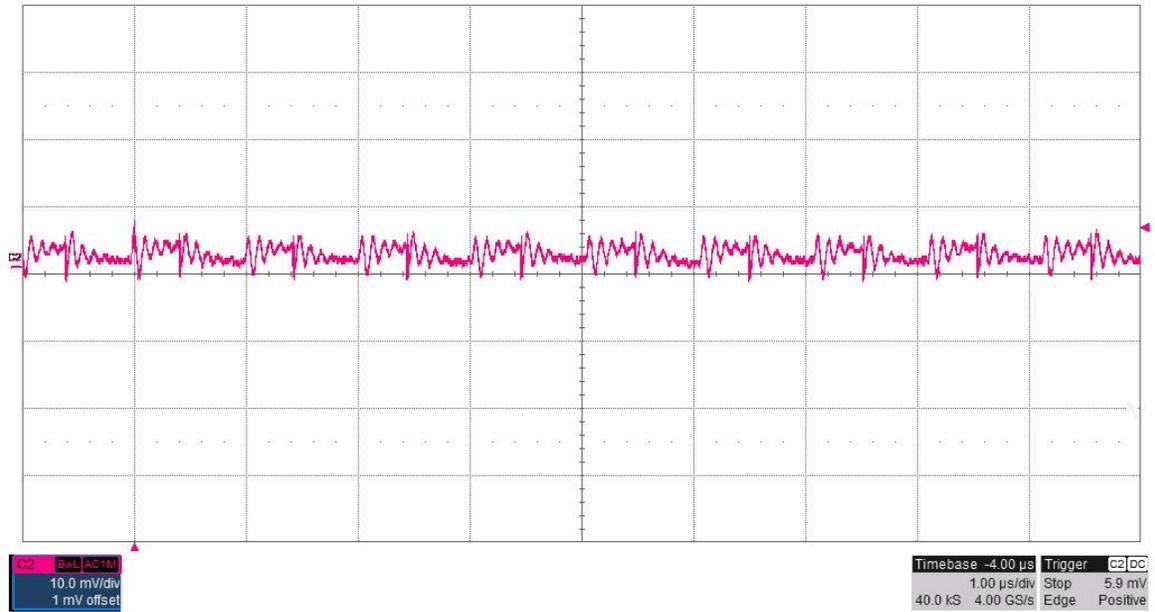The output ripple voltage is shown in the figure below. The image was taken with the 28V output loaded to 0.12A and the input voltage set to 12V. (10mV/DIV, 1uS/DIV)




4 Load Transients

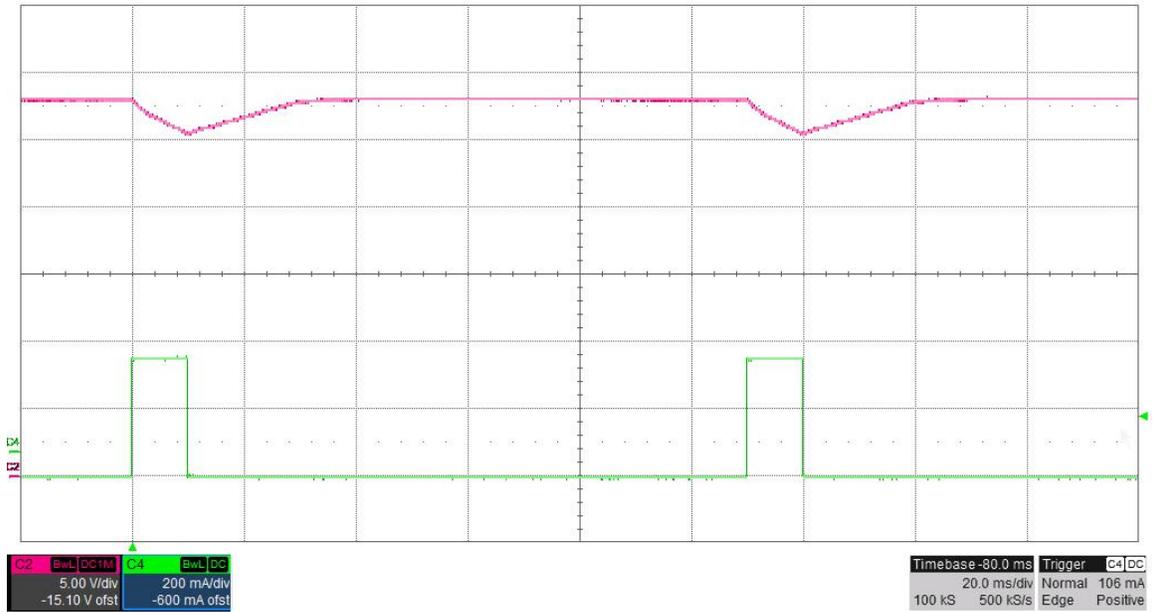
The photo below shows the output voltage when the load current is stepped between 0A and 0.35A.
 $V_{in} = 12V$. (5V/DIV, 200mA/DIV, 20mS/DIV)



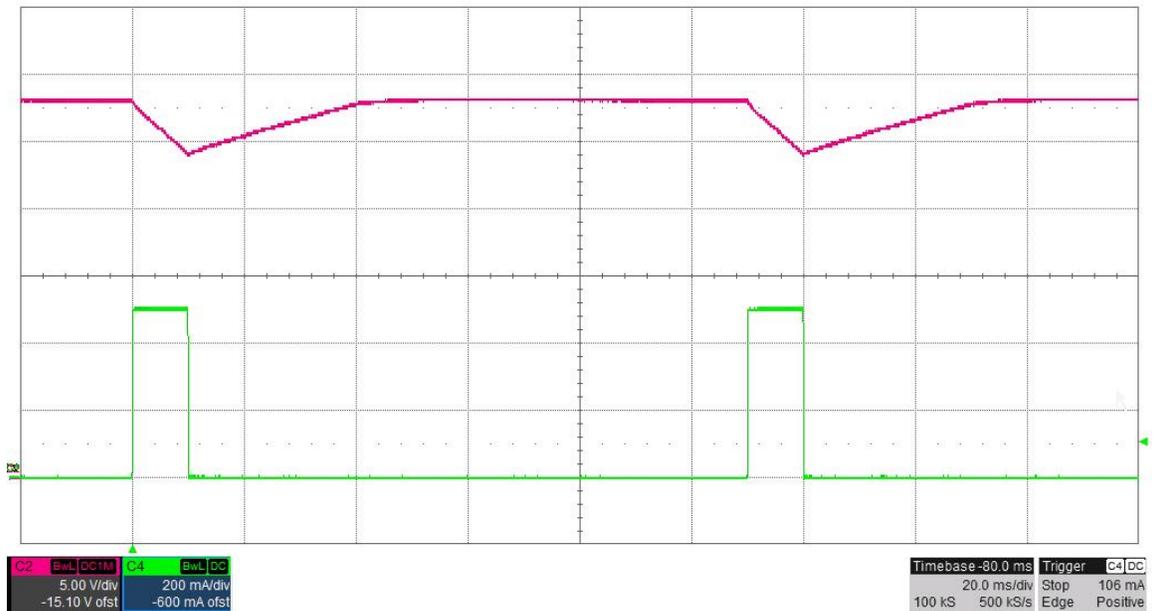
The photo below shows the output voltage when the load current is stepped between 0A and 0.5A.
 $V_{in} = 12V$. (5V/DIV, 200mA/DIV, 20mS/DIV)



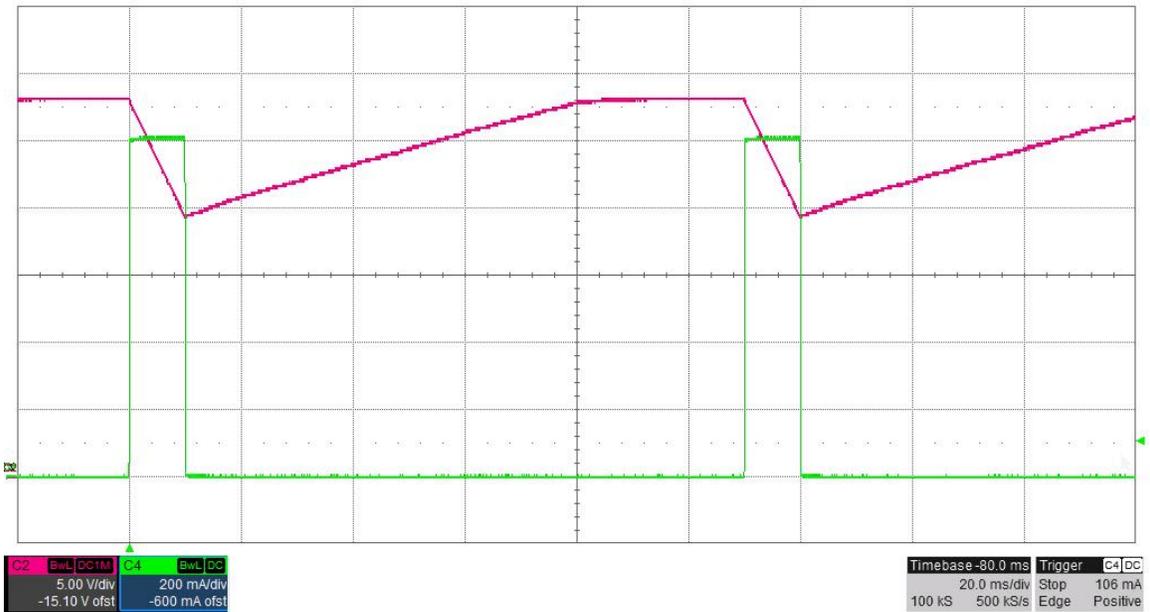
The photo below shows the output voltage when the load current is stepped between 0A and 1A.
 $V_{in} = 12V$. (5V/DIV, 200mA/DIV, 20mS/DIV)



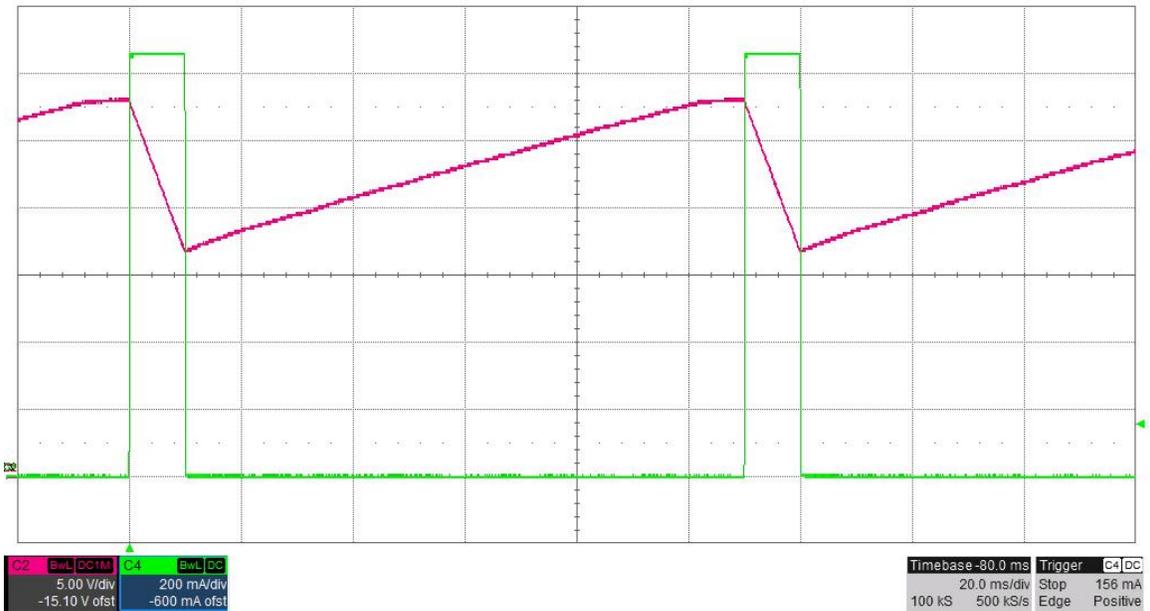The photo below shows the output voltage when the load current is stepped between 0A and 1.25A.
 $V_{in} = 12V$. (5V/DIV, 200mA/DIV, 20mS/DIV)




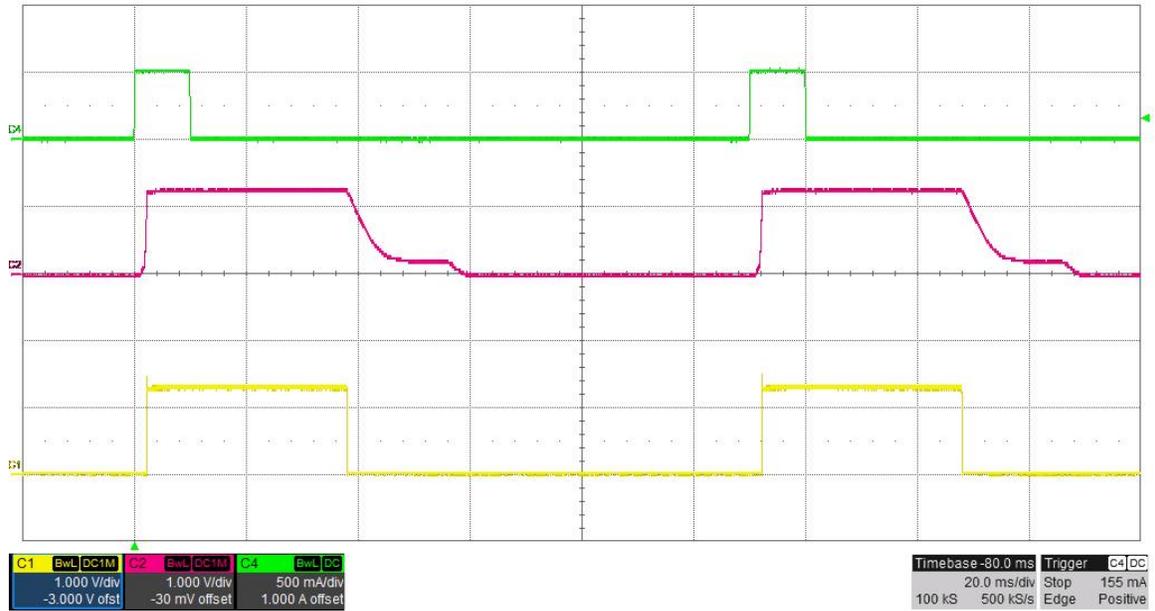The photo below shows the output voltage when the load current is stepped between 0A and 0.35A. $V_{in} = 12V$. Ch2 is the voltage at R2 (output of INA139). Ch1 is the voltage at diode D2 Anode. The current loop is in control when V_{out} is less than 28V. (1V/DIV, 500mA/DIV, 20mS/DIV)




5 Switch Node Waveforms

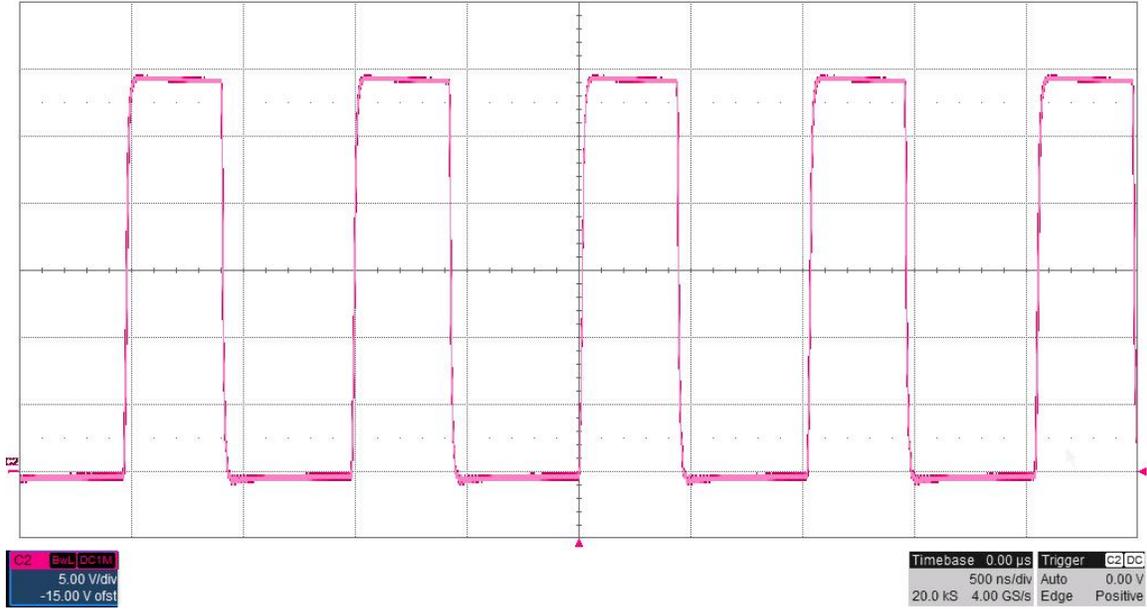The photo below shows the switch node voltage (SW pin). The input voltage is 12V and the 28V output is loaded to 0.12A. (5V/DIV, 500nS/DIV)



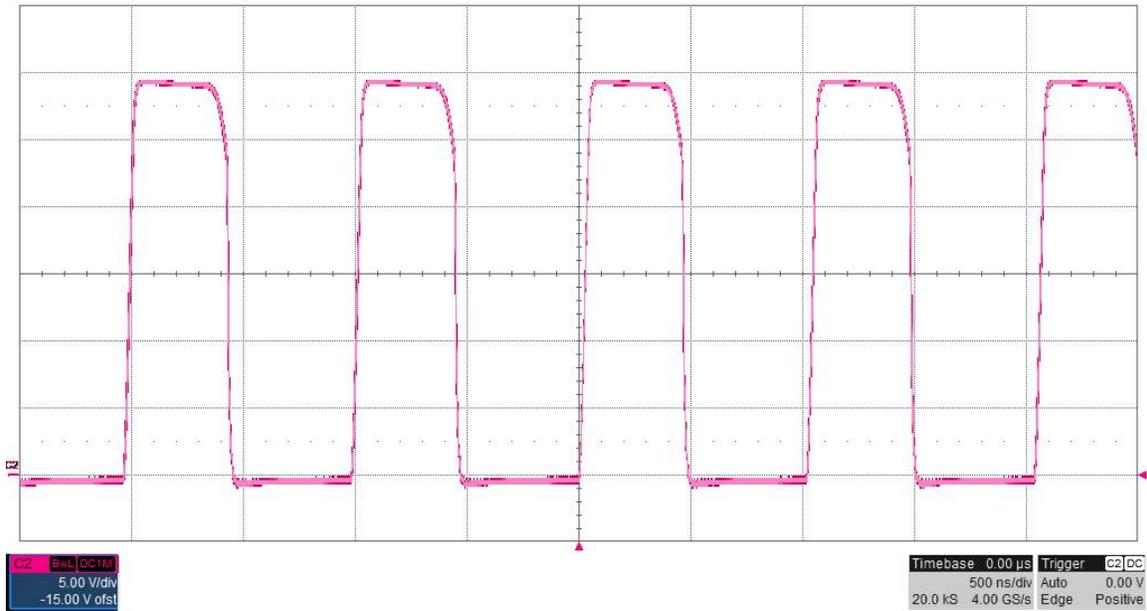The photo below shows the switch node voltage (SW pin). The input voltage is 12V and the 28V output is loaded to 0.025A. The converter is operating in discontinuous conduction mode. (5V/DIV, 500nS/DIV)



The photo below shows the switch node voltage (SW pin). The input voltage is 12V and the 28V output is loaded to 0A. The converter is operating in discontinuous conduction mode. (5V/DIV, 500ns/DIV)




6 Control Loop Gain / Stability

The plot below shows the boost converter's loop gain and phase margin when the 28V output is loaded to 0.13A. The converter is regulating the output **current** with $V_{out} \sim 25V$.

$V_{in} = 12V$

Band Width = 16.3KHz

Phase Margin = 79 degrees

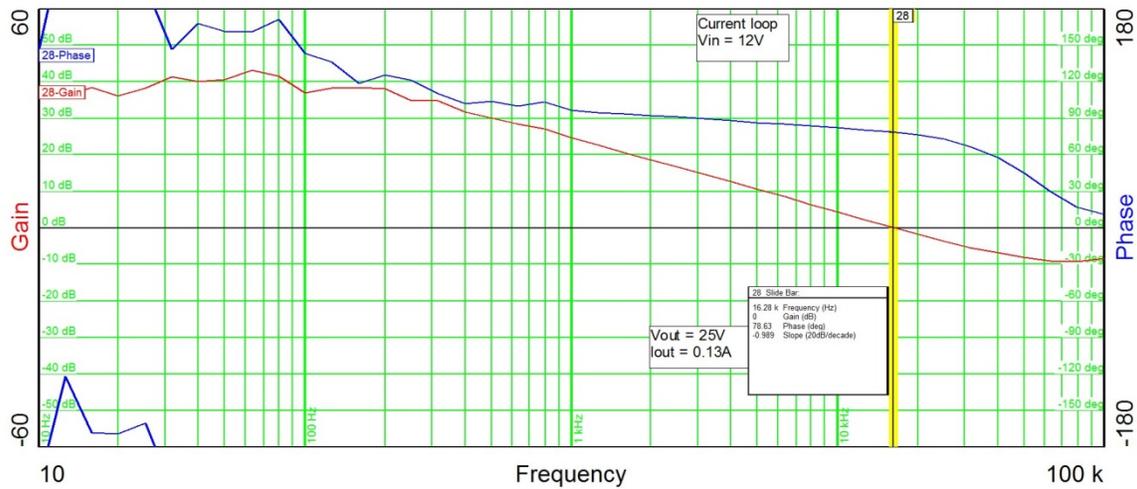

The plot below shows the boost converter's loop gain and phase margin when the 28V output is loaded to 0.05A and 0.10A. The converter is regulating the output **voltage**.

$V_{in} = 12V$ ($I_{out} = 50mA$)


Band Width = 377Hz

Phase Margin = 125 degrees

$V_{in} = 12V$ ($I_{out} = 100mA$)


Band Width = 815Hz

Phase Margin = 129 degrees

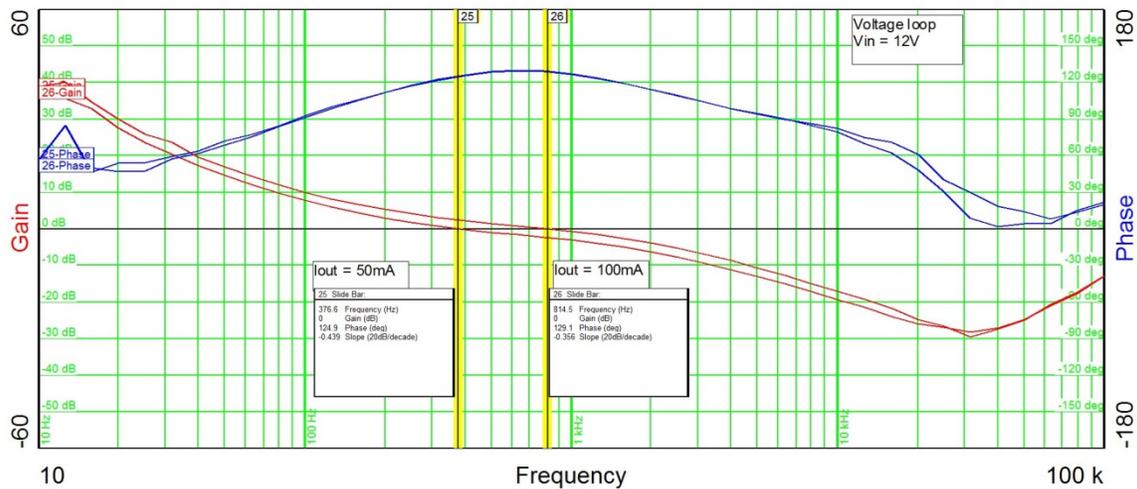


7 Photo

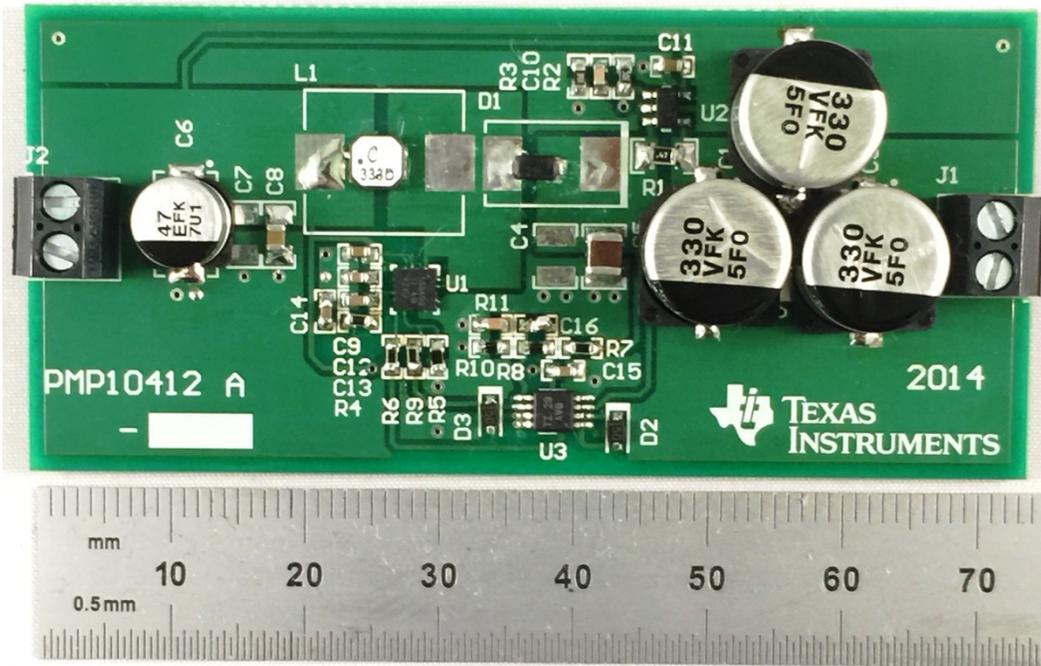The photo below shows the PMP11228 REVB assy built on the PMP10412 REVA PWB.



8 Thermal Image

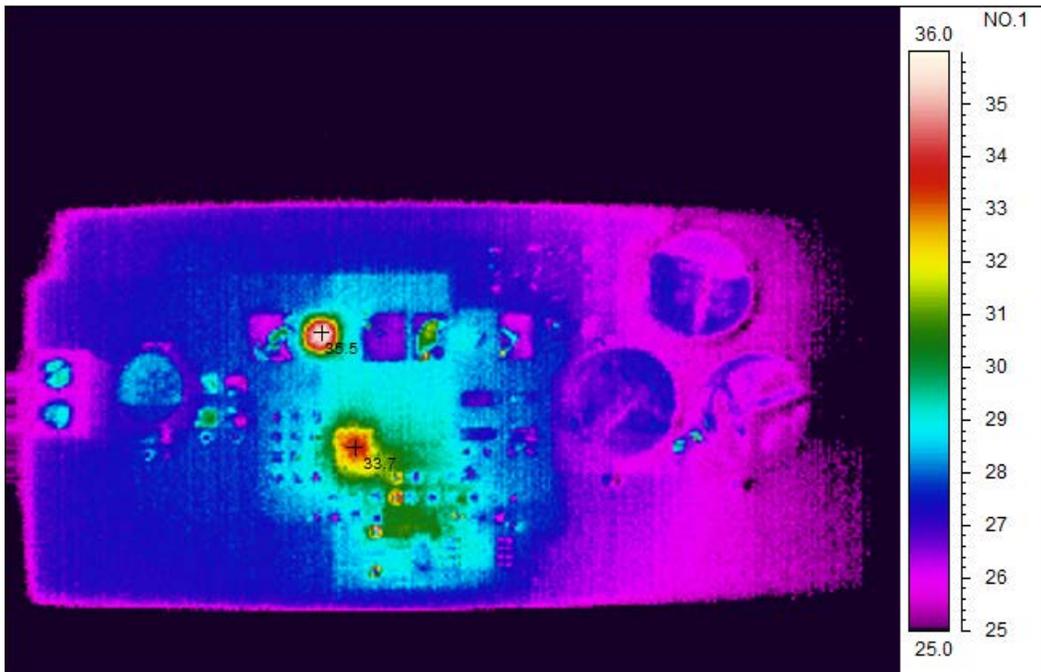The thermal image below shows sustained operation while at a 12V input and 0.12A output, with no airflow.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated