

# TI Designs

## Portable Audio Amplifier With Auto Audio Control 1S1P BMS Reference Design



### Description

This TI Design is a high performance, 10-W (5 W per speaker) portable audio amplifier that includes everything needed to implement a battery management solution (BMS) for a portable audio amplifier (including a charger, fuel (gas) gauge, and protection for a 1S1P 18650 2400-mAh Lithium battery) for a Class D Audio Amplifier. Get extended operating time by using efficient power regulators, a Class D amplifier, and proper battery management.

### Resources

<a href="#">TIDA-01182</a>	Design Folder
<a href="#">bq25896</a>	Product Folder
<a href="#">bq27426</a>	Product Folder
<a href="#">bq29705</a>	Product Folder
<a href="#">LM3481</a>	Product Folder
<a href="#">MSP430FR5735</a>	Product Folder
<a href="#">TPS78225</a>	Product Folder
<a href="#">TPA3004D2</a>	Product Folder
<a href="#">DAC081C085</a>	Product Folder
<a href="#">PCA9306</a>	Product Folder
<a href="#">CSD16323Q3</a>	Product Folder
<a href="#">CSD17578Q5A</a>	Product Folder

### Features



- High Performance, 10-W (5 W per Speaker) Portable Audio Amplifier
- Includes Everything Needed for a BMS for a Portable Audio Amplifier (Charger, Fuel (Gas) Gauge, and Protection for a 1S1P 18650 Lithium Battery)
- Class D Audio Amplifier 0.01% THD
- High Efficiency Boost Regulator and Ultra-Low-Power LDO Regulator
- Ultra-Low-Power MSP430™ Microcontroller
- Extended Play Time Due to High Efficiency and Proper Battery Management Techniques

### Applications

- Portable Audio Amplifiers
- Portable MP3 and DVD Players



ASK Our E2E Experts

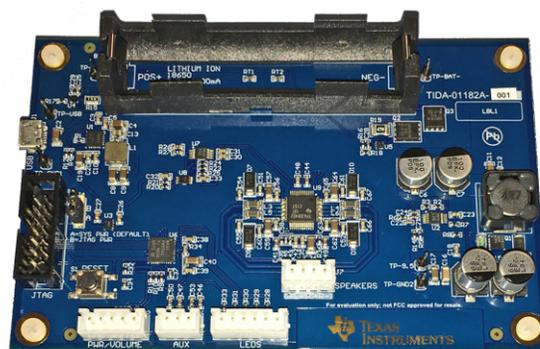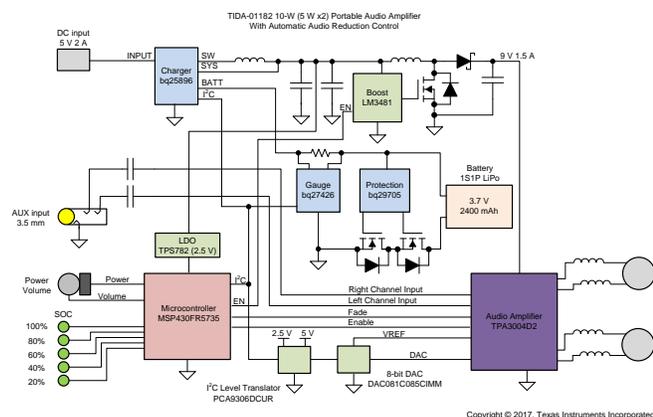

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 1 System Overview

### 1.1 System Description


This is a system core design for any high-performance, 10-W (5 W per speaker) portable audio design that includes everything needed to implement a battery management solution (BMS). This TI Design includes a charger, gauge, and protection for a 1S1P 18650 2400-mAh Lithium battery. This core design can be used in many portable audio designs as a standalone portable audio amplifier or as a portable MP3 player or a portable DVD player. The Class D Audio Amplifier has enough power for almost any design that requires quality, high performance, portability, and long life. This TI Design offers an extended operating time by using efficient power regulators, the Class D amplifier, and proper battery management.

### 1.2 Key System Specifications

**Table 1. Key System Specifications**

PARAMETER	VALUE	UNIT
Minimum input voltage limit for charger	4.5	V <sub>MIN</sub>
Maximum input voltage limit for charger	14	V <sub>MAX</sub>
Battery SOC (at the time of test)	60 to 80	%
Max charge current	2.5	A
Charge termination current	250	mA
Battery voltage with audio amp on (no audio)	3.84	V
Battery current with audio amp on (no audio)	240	mA
Battery voltage with audio amp loaded	3.15	V
Battery current with audio amp loaded	2.93	A
Battery Impedance	235	m
Protection current limit	5.25	A
Boost regulator output voltage—audio amp off	9.6	V
Boost current—audio amp on (no audio)	82	mA
Boost regulator output voltage—audio amp on	9.59	V
Boost regulator output current—audio amp on	750	mA
Boost regulator output voltage under load	9.55	V
Boost regulator maximum load current	1.6	A <sub>MAX</sub>
Boost regulator efficiency	85	%
Boost load regulation	160	mV P-P
Audio amplifier—Load test—Boost regulator output current	1.2	A
Audio amplifier—Load test—Boost regulator input current	2.93	A
Audio amplifier—Peak load test—Boost regulator input current	5	A
Audio amplifier Class D average current, low battery	320	mA
Audio amplifier Class D average current, high battery	230	mA
Power output	10.2	W
Output test the audio amplifier	84	dB
Maximum audio input level	2	V P-P
Total circuit current in low power shutdown mode	0.0007	A
Total circuit idle current	17	mA
Maximum temperature rise in the boost regulator	31	°C
Maximum temperature rise in the charger	38	°C
Maximum temperature rise in the audio amp	34	°C

### 1.3 Block Diagram

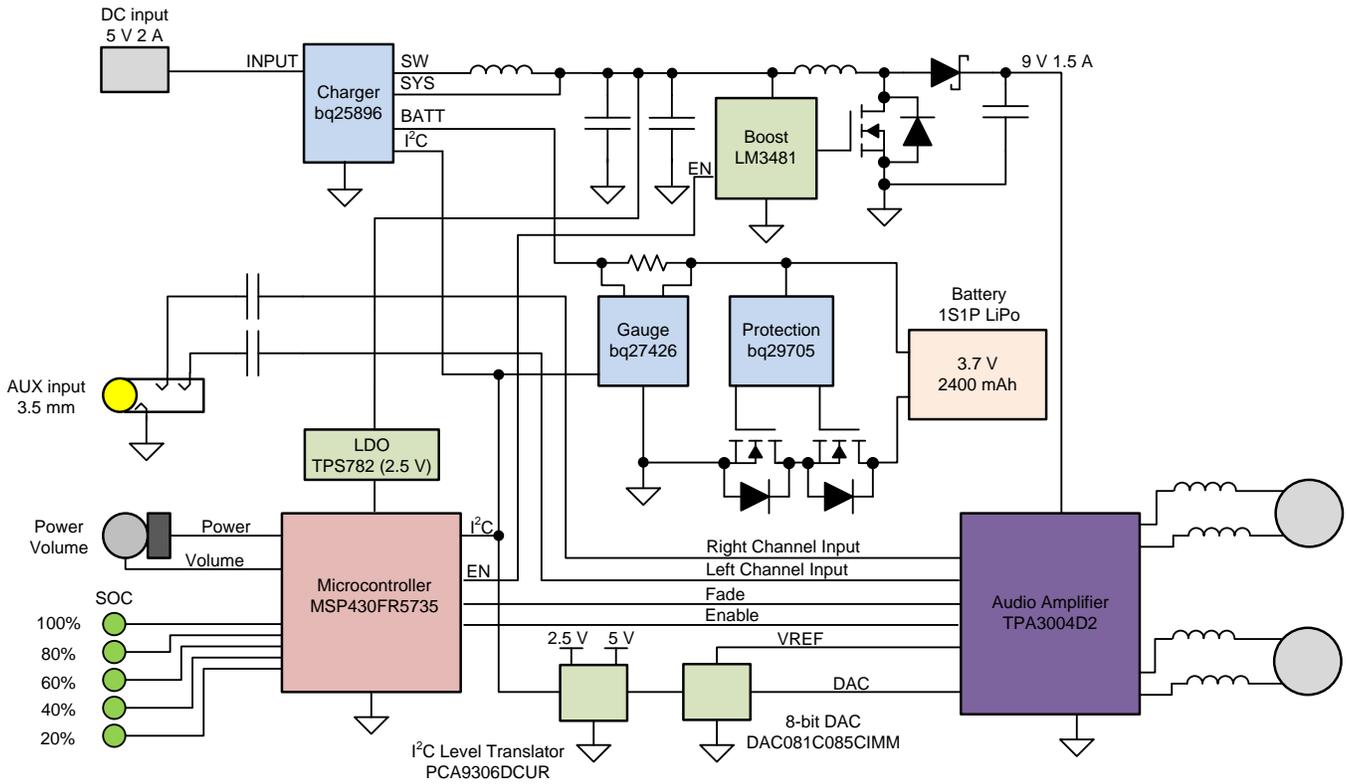


Copyright © 2017, Texas Instruments Incorporated

Figure 1. Block Diagram

## 1.4 Highlighted Products
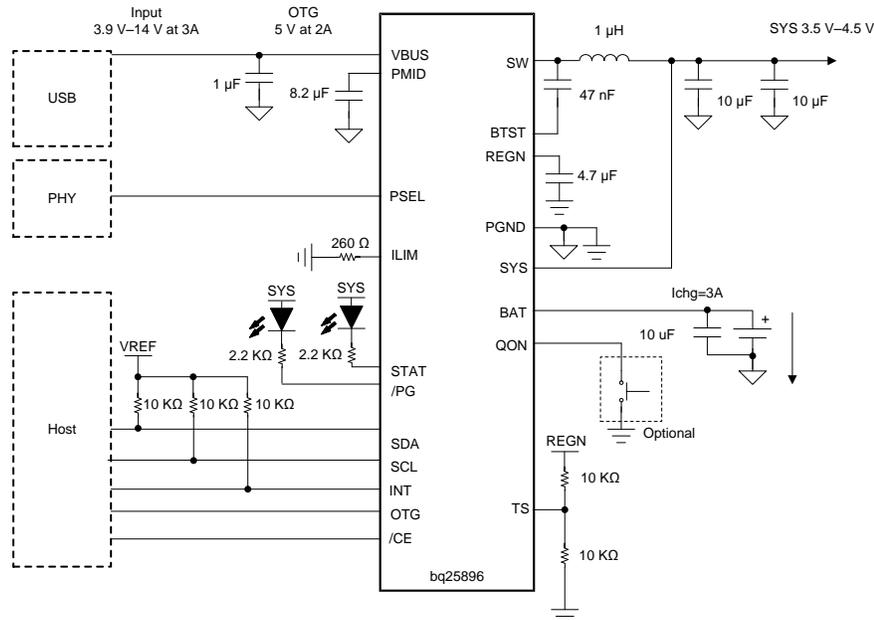
### 1.4.1 bq25896 Charger

The bq25896 is a highly-integrated 3-A switch-mode device for battery charge and system power path management for a single-cell Li-Ion and Li-polymer battery. This device supports high input voltage fast charging. The low impedance power path optimizes switch-mode operation efficiency, reduces battery charging time, and extends battery life during discharging phase. The I<sup>2</sup>C serial interface with charging and system settings makes the device a truly flexible solution.




Copyright © 2016, Texas Instruments Incorporated

Figure 2. bq25896 Typical Application Diagram
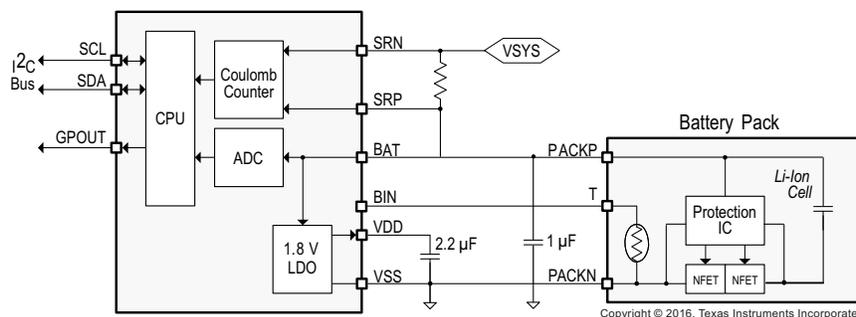
### 1.4.2 bq27426 Gauge

The Texas Instruments bq27426 battery fuel gauge is a single-cell gauge that requires minimal user configuration and system micro-controller firmware development, leading to a quick system bring-up. Three chemistry profiles are pre-programmed to enable minimum user-configuration, and to help manage customer inventory across projects with different battery chemistries. The bq27426 battery fuel gauge has very low sleep power consumption leading to longer battery run time. Configurable interrupts help save system power and free up the host from continuous polling. Accurate temperature sensing is supported via an external thermistor. The bq27426 battery fuel gauge uses the patented Impedance Track™ algorithm for fuel gauging, and provides information such as remaining battery capacity (mAh), state of charge (%), and battery voltage (mV).




Copyright © 2016, Texas Instruments Incorporated

Figure 3. bq27426 Typical Application Diagram


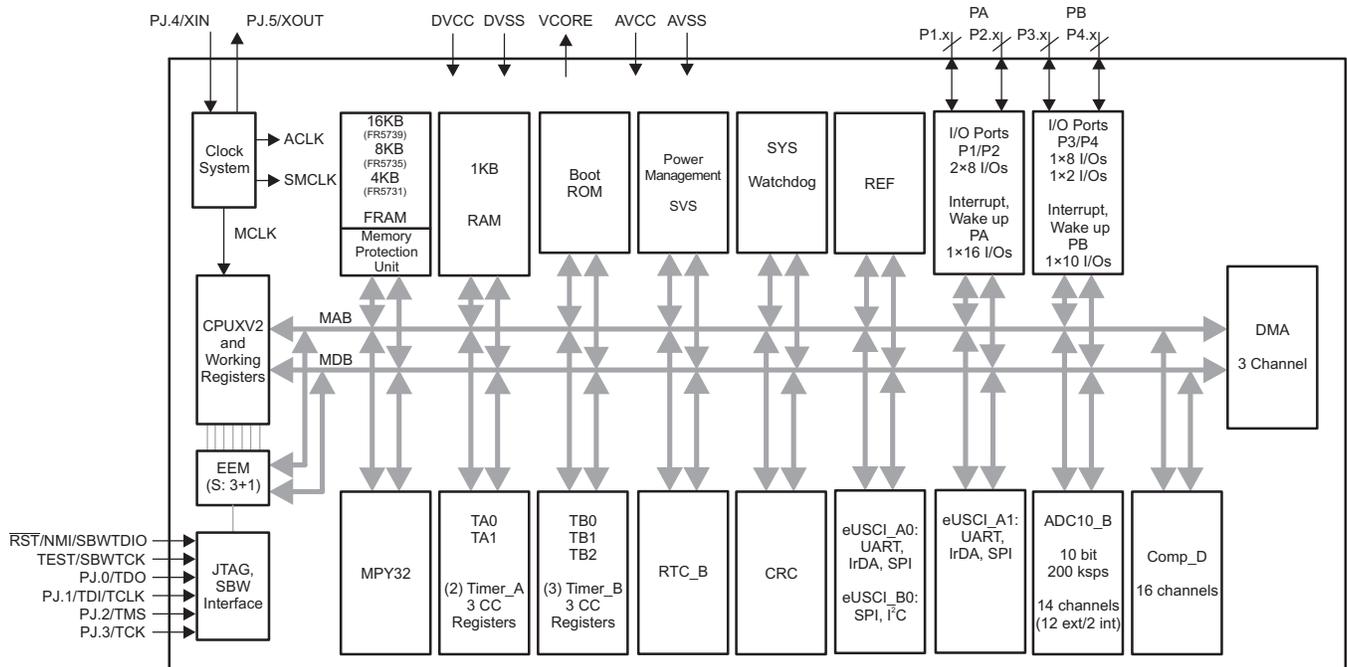
### 1.4.5 MSP430FR5735 Microcontroller

The TI MSP430FR573x family of ultra-low-power microcontrollers consists of multiple devices that feature embedded FRAM nonvolatile memory, ultra-low-power 16-bit MSP430™ CPU, and different peripherals targeted for various applications. The architecture, FRAM, and peripherals, combined with seven low-power modes, are optimized to achieve extended battery life in portable and wireless sensing applications. FRAM is a new nonvolatile memory that combines the speed, flexibility, and endurance of SRAM with the stability and reliability of flash, all at a lower total power consumption. Peripherals include a 10-bit ADC, a 16-channel comparator with voltage reference generation and hysteresis capabilities, three enhanced serial channels capable of I<sup>2</sup>C, SPI, or UART protocols, an internal DMA, a hardware multiplier, an RTC, five 16-bit timers, and digital I/Os.




Copyright © 2016, Texas Instruments Incorporated

Figure 6. MSP430FR5735 Typical Block Diagram
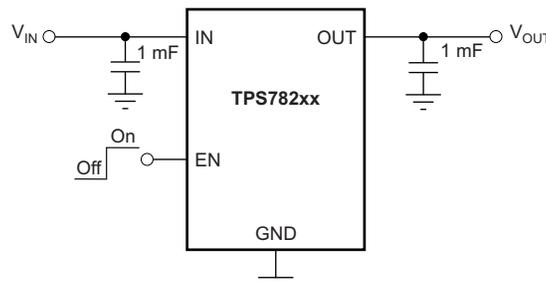
### 1.4.6 TPS78225 LDO Regulator

The TPS782 family of low-dropout regulators (LDOs) offers the benefits of ultra-low-power and miniaturized packaging. This LDO is designed specifically for battery-powered applications where ultra-low quiescent current is a critical parameter. The TPS782 with ultra-low IQ (500 nA) is ideal for microprocessors, microcontrollers, and other battery-powered applications.




Copyright © 2016, Texas Instruments Incorporated

Figure 7. TPS782 Typical Application Diagram


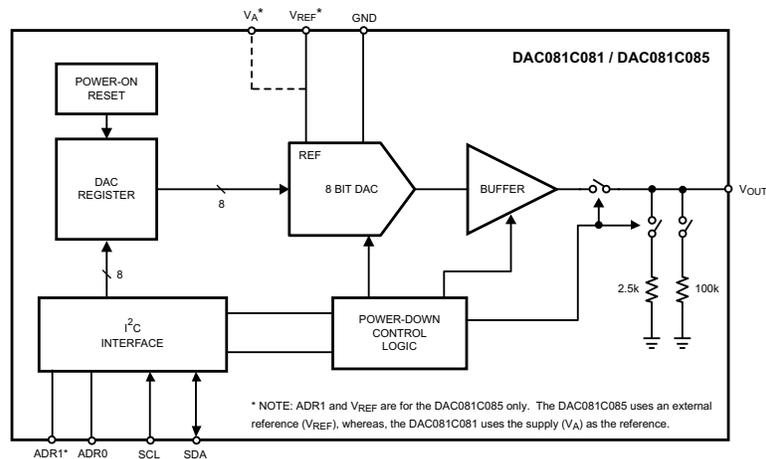
### 1.4.8 DAC081C085 8-Bit DAC

The DAC081C08x device is an 8-bit, single-channel, voltage-output digital-to-analog converter (DAC) that operates from a 2.7- to 5.5-V supply. The output amplifier allows rail-to-rail output swing and has a 4.5- $\mu$ s settling time. The DAC081C081 uses the supply voltage as the reference to provide the widest dynamic output range and typically consumes 132  $\mu$ A while operating at 5 V. It is available in 6-lead SOT and WSON packages and provides three address options (pin selectable). The DAC081C081 and DAC081C085 use a 2-wire, I<sup>2</sup>C-compatible serial interface that operates in all three speed modes, including high-speed mode (3.4 MHz). An external address selection pin allows up to three DAC081C081 or nine DAC081C085 devices per 2-wire bus. Pin-compatible alternatives to the DAC081C081 are available that provide additional address options.




Copyright © 2016, Texas Instruments Incorporated

**Figure 9. DAC081C085 Functional Block Diagram**
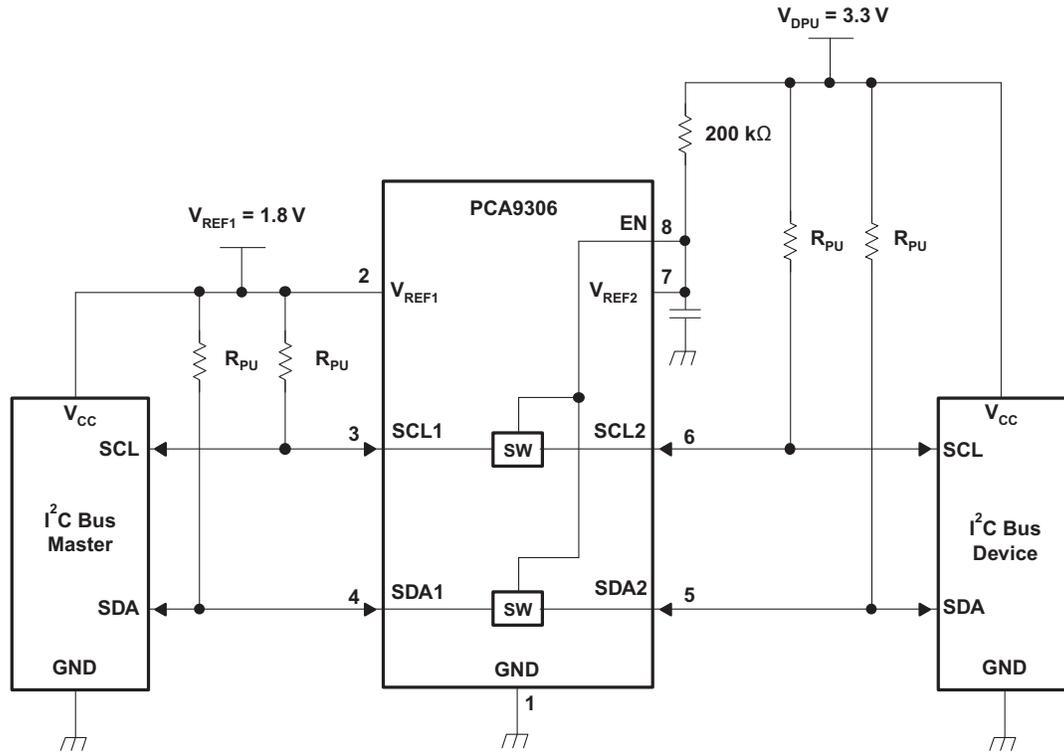
### 1.4.9 PCA9306 Level Translator

The PCA9306 device is a dual bidirectional I<sup>2</sup>C and SMBus voltage-level translator with an enable (EN) input and is operational from 1.2- to 3.3-V VREF1 and 1.8- to 5.5-V VREF2. The PCA9306 device allows bidirectional voltage translations between 1.2 and 5 V without the use of a direction pin. The low ON-state resistance (RON) of the switch allows connections to be made with minimal propagation delay. When EN is high, the translator switch is ON, and the SCL1 and SDA1 I/O are connected to the SCL2 and SDA2 I/O, respectively, allowing bidirectional data flow between ports. When EN is low, the translator switch is off, and a high-impedance state exists between ports.



Copyright © 2016, Texas Instruments Incorporated

Figure 10. PCA9306 Typical Application Diagram

### 1.4.10 CSD16323Q3 MOSFET

This 25-V, 4.4-mΩ, SON 3.3-mm×3.3-mm NexFET™ Power N-Channel MOSFET has been designed to minimize losses in power conversion and optimized for 5-V gate drive applications.

### 1.4.11 CSD17578Q5A MOSFET

This 30-V, 5.9-mΩ, SON 5-mm×6-mm NexFET™ Power N-Channel MOSFET is designed to minimize losses in power conversion applications.

## 2 Getting Started Hardware and Software

### 2.1 Operations

Powering on and off is controlled by the knob in the center of the unit. Rotate to the left until it clicks for off. Rotate to the right to turn on and continue to rotate to the right to increase the volume. This unit never actually turns off or disconnects the power source. Turning this unit off disables the charger, boost regulator and the audio amplifier. The demo unit will enter into a very low power mode monitoring the USB port for power and the on/off switch for changing states. If power is supplied to the micro-USB port the unit will enter into charge mode. The LEDs will ramp from the bottom moving up to the LED that represents the charged state of charge (SOC). When the unit is on and power is supplied to the USB port, the unit will operate using power path technology that will charge the battery and power the unit at the same time.


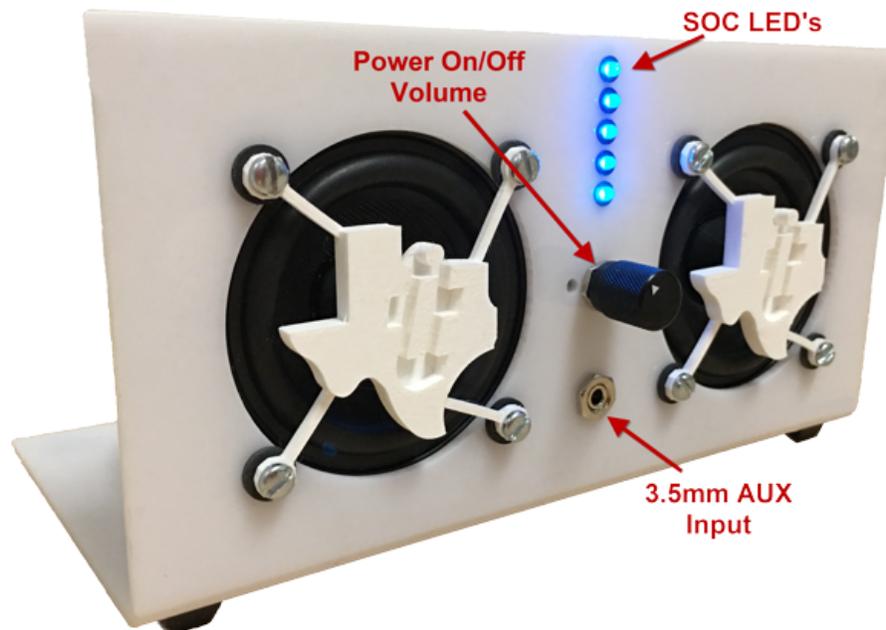


Figure 11. Demo Front View Markup

In the normal operating mode and while not charging, the LEDs will light up showing the SOC of the battery. Each LED represents 20% SOC from 0% to 20%, 20% to 40%, 40% to 60%, 60% to 80%, and 80% and 100%. When the SOC falls below 40% and the battery voltage goes below 3.4-V DC the audio will automatically begin reducing to prevent clipping and distortion as the battery begins a complete discharge. To better understand how this feature works, review [Section 2.2](#). To charge, plug in a micro-USB cable to the input port on the board. This unit will charge at the appropriate rate based on the power that is available for the power source. Any standard USB output will work up to 2.5 A. To play audio, connect a 3.5-mm stereo auxiliary cord to the source and plug the other end into the portable amplifier AUX input. Set the output audio level of the source to max (do not exceed 2 V<sub>p-p</sub>) and control the audio output level with the volume control on the front panel.

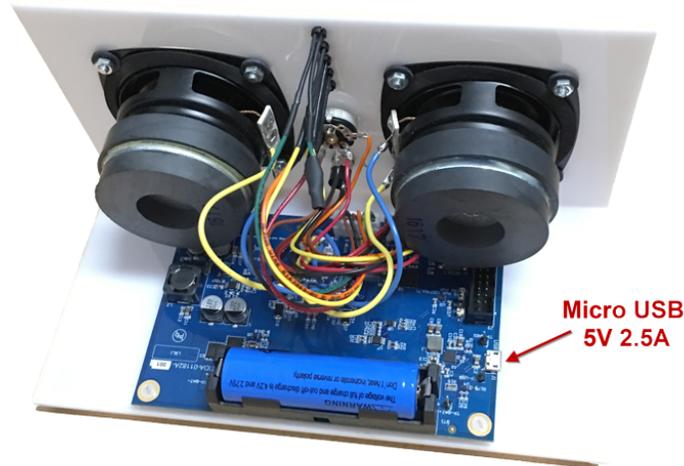

**Figure 12. Demo Rear View Markup**

## 2.2 Programming

The code was written in C using Code Composer Studio™ (CCS) and the MSP430 Driver library.

---

**NOTE:** No actual code will be provided for this TI Design.

---

This design guide provides a flow diagram and explains how the code was written. Some examples of the code are provided for reference only for areas that have been determined to be tricky or difficult. All of the following examples are for reference only. Choosing how to write the code may be different from these examples, but the process will be the same.

### 2.2.1 Using I<sup>2</sup>C To Write Data To The Gauge

The gauge uses 16-bit values internally. I<sup>2</sup>C uses 8-bit values to send and receive bytes. To write a byte to the gauge, separate the data value into a high byte and a low byte, then call the `gauge_write_reg_1byte` (`G_REG_ADDR`, `G_REG_DATA_1`) function as shown in [Figure 13](#). Write the msb byte first, then the lsb byte second. Follow the instructions in the datasheet for details on reading and writing to the gauge. The `gauge_write_reg_1byte`(`G_REG_ADDR`, `G_REG_DATA_1`) function is not part of the driver library but is a standard I<sup>2</sup>C method to send data.

```
// convert design capacity to two 8 bit bytes to be able to transmit the data
uint16_t qmax_msb = (qmax_cell_0 & 0xff00) >> 8;
uint16_t qmax_lsb = (qmax_cell_0 & 0x00ff) ;

gauge_write_reg_1byte(0x40, qmax_msb); // write the qmax msb
gauge_write_reg_1byte(0x41, qmax_lsb); // write the qmax lsb

//*****
// Gauge Comms write address and one byte of data
//*****
// 1 data bytes write register routine for the gauges
void gauge_write_reg_1byte(G_REG_ADDR, G_REG_DATA_1)
{
    // Get the I2C port ready to send data
    init_I2C_TX();
    // specify slave address
    EUSCI_B_I2C_setSlaveAddress(EUSCI_B0_BASE, 0x55);
    // Set to transmit mode
    EUSCI_B_I2C_setMode(EUSCI_B0_BASE, EUSCI_B_I2C_TRANSMIT_MODE);
    // Enable I2C Module to start operations
    EUSCI_B_I2C_enable(EUSCI_B0_BASE);
    // Delay before this transaction
    __delay_cycles(100);
    // sends the first byte of the packet
    EUSCI_B_I2C_masterSendMultiByteStart(EUSCI_B0_BASE, G_REG_ADDR);
    // sends the next byte in the packet
    EUSCI_B_I2C_masterSendMultiByteNext(EUSCI_B0_BASE, G_REG_DATA_1);
    // ends the packet
    EUSCI_B_I2C_masterSendMultiByteStop(EUSCI_B0_BASE);
    __delay_cycles(100);
}
```

**Figure 13. Code Using I<sup>2</sup>C to Write Data to Gauge**

## 2.2.2 Using I<sup>2</sup>C to Read Two Bytes From the Gauge

The same as in writing to the gauge, the data value are 16-bit values for reading as well. So, read the entire data value as two 8-bit values (msb and lsb) from the gauge, combine these values into one 16-bit value, then return the value to the calling code section.

```

// get state of charge
StateOfCharge = gauge_read_16_reg_LSB(0x1C);
//*****
// read two bytes from the gauge and combine them for a 16bit value
//*****
uint16_t gauge_read_16_reg_LSB(G_REG_ADDR) // 2 byte read register routine for the
gauges
{
    uint16_t temp_read;
    uint8_t temp_read_l;
    uint8_t temp_read_h;
// get the I2C port ready to transmit
    init_I2C_TX();
// specify the slave address
    EUSCI_B_I2C_setSlaveAddress(EUSCI_B0_BASE, 0x55);
// Set to transmit mode
    EUSCI_B_I2C_setMode(EUSCI_B0_BASE, EUSCI_B_I2C_TRANSMIT_MODE);
// Enable I2C Module to start operations
    EUSCI_B_I2C_enable(EUSCI_B0_BASE);

    __delay_cycles(100);
// Send single byte data.
    EUSCI_B_I2C_masterSendSingleByte(EUSCI_B0_BASE, G_REG_ADDR);

    __delay_cycles(100);
// get the I2C port ready to receive
    init_I2C_RX();
// specify the slave address
    EUSCI_B_I2C_setSlaveAddress(EUSCI_B0_BASE, 0x55);
// Set to receive mode
    EUSCI_B_I2C_setMode(EUSCI_B0_BASE, EUSCI_B_I2C_RECEIVE_MODE);
// Enable I2C Module to start operations
    EUSCI_B_I2C_enable(EUSCI_B0_BASE);
// Clear the interrupt
    EUSCI_B_I2C_clearInterrupt(EUSCI_B0_BASE, EUSCI_B_I2C_RECEIVE_INTERRUPT0 +
EUSCI_B_I2C_BYTE_COUNTER_INTERRUPT);

    __delay_cycles(100);
// I2C start condition
    temp_read_l = EUSCI_B_I2C_masterReceiveSingleByte(EUSCI_B0_BASE);
// I2C start condition
    temp_read_h = EUSCI_B_I2C_masterReceiveSingleByte(EUSCI_B0_BASE);

    __delay_cycles(100);
// combine the msb and lsb
    temp_read = ((temp_read_h << 8) | temp_read_l);
// return the value
    return(temp_read);
}

```

**Figure 14. Code Using I<sup>2</sup>C to Read Two Bytes From Gauge**

### 2.2.3 Using I<sup>2</sup>C to Write Data to the DAC

The DAC requires that the 8-bit value to set the DAC needs to be inserted into the middle of a 16-bit value. Figure 15 shows a completed example. The MSP430 ADC is a 10-bit value; this value is averaged over several samples to prevent it from bouncing around. The average value is sent to the DAC\_write\_reg (volume\_average) function.

```

// call the DAC write routine and send the averaged volume to the DAC
DAC_write_reg(volume_average);
//*****
// DAC Comms //DAC output value
//*****
void DAC_write_reg(DAC_value)
{
// Get the I2C port ready to send data
init_I2C_TX();
// take the 10bit raw adc value, shift right to make it 8bit. Shift left 4 bits to
create the 16bit I2C value
set_DAC_value = (DAC_value >> 2) << 4;
// msb - convert the new 16bit with/volume into two 8bit bytes to be able to
transmit the data
dac_msb = (set_DAC_value & 0xff00) >> 8;
// lsb
dac_lsb = (set_DAC_value & 0x00ff) ;
// specify the slave address
EUSCI_B_I2C_setSlaveAddress(EUSCI_B0_BASE, DAC_SLAVE_ADDRESS);
// Set to transmit mode
EUSCI_B_I2C_setMode(EUSCI_B0_BASE, EUSCI_B_I2C_TRANSMIT_MODE);
// Enable I2C Module to start operations
EUSCI_B_I2C_enable(EUSCI_B0_BASE);
// Delay before this transaction
__delay_cycles(100);
// begins the packet by sending the slave address
EUSCI_B_I2C_masterSendStart(EUSCI_B0_BASE);
// sends the first byte of the packet
EUSCI_B_I2C_masterSendMultiByteStart(EUSCI_B0_BASE, dac_msb);
// sends the next byte in the packet
EUSCI_B_I2C_masterSendMultiByteNext(EUSCI_B0_BASE, dac_lsb);
// ends the packet
EUSCI_B_I2C_masterSendMultiByteStop(EUSCI_B0_BASE);
}
    
```

**Figure 15. Code Using I<sup>2</sup>C to Write Data to DAC**

## 2.2.4 Reading the Volume Potentiometer and Setting the Auto Volume Control

The first step is to read the voltage drop across the volume potentiometer. This voltage is used to set the audio output level of the Class D amplifier. The raw ADC value from the MSP430 is 10 bits. Average this value, then determine the battery state, and determine what the maximum level the amplifier can be set to in order to prevent clipping and distortion. Then set the DAC level to control the output of the amplifier.

```

//*****
// read the volume setting with the ADC (0-1023bits) (0-3.3V)
//*****
void read_ADC(void)
{
    int i = 0;           // set to 0
    int sum_array = 0;  // set to 0
    int volume_max = 0;

    //Enable and Start the conversion in Single-Channel, Single Conversion Mode
    ADC10_B_startConversion(ADC10_B_BASE, ADC10_B_SINGLECHANNEL);
    __delay_cycles(100); // wait for conversion
    // The latest ADC value as read from the MSP430
    volume_read_new = ADC10_B_getResults(ADC10_B_BASE);
    //FIFO averaging filter for the volume ADC_CH1 -----
    i = 0;           // reset to 0
    sum_array = 0;   // reset the last averaged value to zero to recalculate the
new average value
    // Vdc_1_length = the amount of samples to average across, this number will set the
array length
    // Vdc_1_array = the size of the array that will store the FIFO values for averaging
    for(i = 0; i < Vdc_1_length; i++) // shift the array as a FIFO
    {
        // Makes all the array indexes equal the number after them (Moves all of the values
in the array up one)
        Vdc_1_array[i] = Vdc_1_array[i + 1];
    }
    Vdc_1_array[Vdc_1_length - 1] = volume_read_new; // add the new value to
the end of the array
    for(i = 0; i < Vdc_1_length; i++) // sum the array
    {
        // add all of the array elements each time you add a new element
        sum_array += Vdc_1_array[i];
    }
    // divide the sum of the array to get an average, then divide by 2
    volume_average = ((sum_array / Vdc_1_length)/2);
    // If the battery voltage is below the threshold recalculate to get the auto reduced
value
    if (m_Voltage_1 <= 3400)
    {
        volume_max = (((1023-(3400-m_Voltage_1))-24)/2);
        // if the actual averaged values is greater than the calculated limit use the limit
        if (volume_average >= volume_max)
        {
            volume_average = volume_max;
        }
        // if the actual averaged value is below the calculated limit then use the averaged
value
    }
    // call the DAC write routine and send the averaged volume to the DAC
    DAC_write_reg(volume_average);
    __delay_cycles(10);
}

```

**Figure 16. Code Reading Volume Potentiometer and Setting Auto Volume Control**

2.2.5 Flowchart

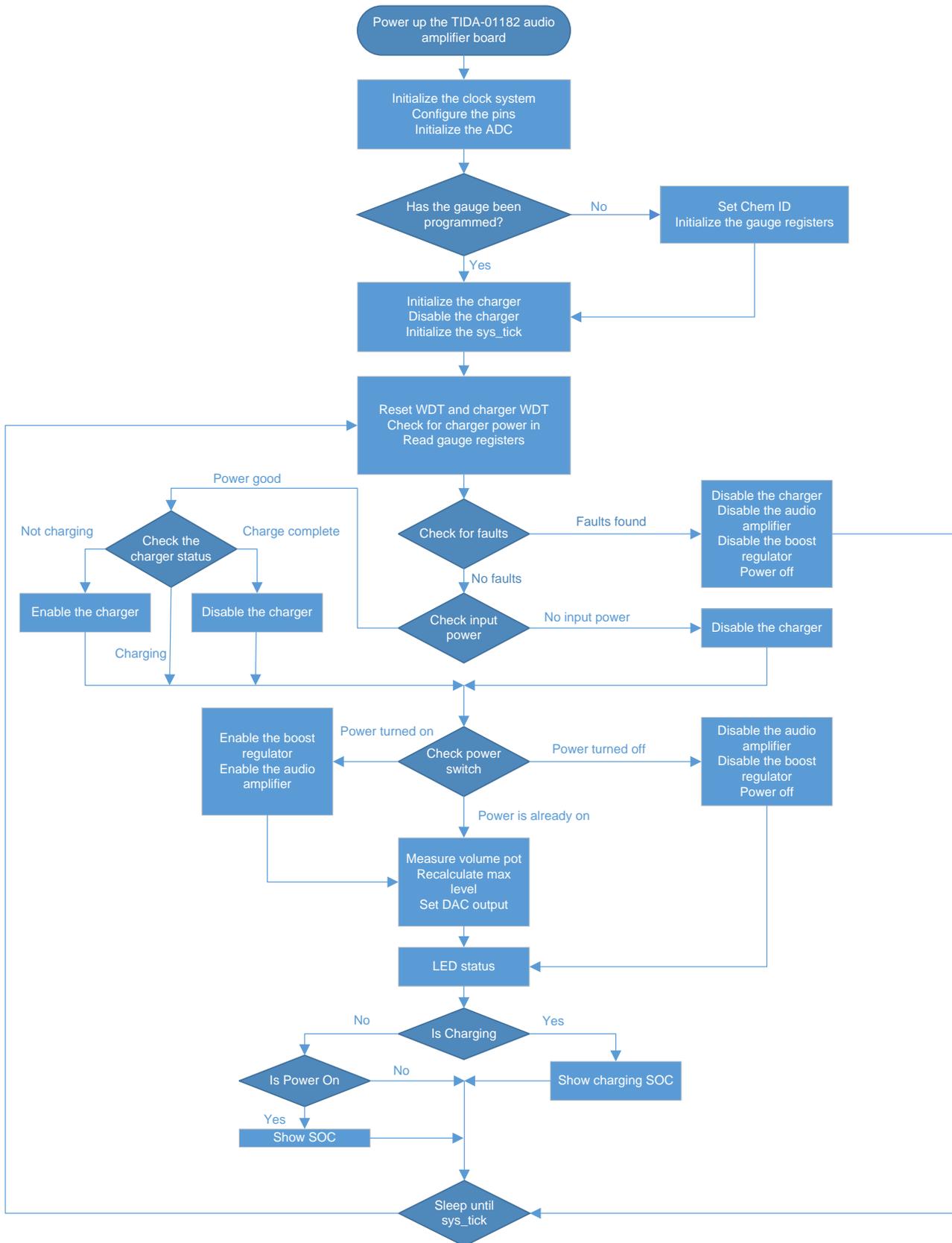


Figure 17. Code Flowchart

### 3 Testing and Results

Figure 18 shows the TIDA-01182 test bench.



**Figure 18. Test Bench**

The test bench setup includes the following:

- Dell® laptop running CCS
- MSP-FET Flash Emulation Tool
- Tektronix® TDS 2024B Oscilloscope
- Fluke™ 189 Multimeter
- Keithley™ 2812 SourceMeter®
- BK Precision 8502 Electronic Load
- Agilent™ E3649A Power Supply
- Flir™ i7 Thermography Camera
- Measurement Computing™ USB-2408 Data Acquisition Module
- LMEM™ MMML100W 8-Ω Load, Resistive Load
- Nady ASM-2 Analog Sound Pressure Level Monitor

Figure 18 is a picture of the basic test bench setup. High-power 8-Ω resistive loads were used on the speaker outputs for most of the testing to minimize the noise during test. Once the power section was verified, the balance of the tests were completed using a battery. The boost, audio amplifier, and power path tests were tested using a battery.

### 3.1 CCS Variable Data

Most of the test results for the gauge and charger were provided by the CCS software while writing the code and debugging the firmware. Create a list of variables to be read from the gauge IC and a set of flag variables to be read from the charger, read the gauge and charger, and then displayed the results in these lists. See Figure 19 for a preview of the list variables that were used while testing the TIDA-01182.

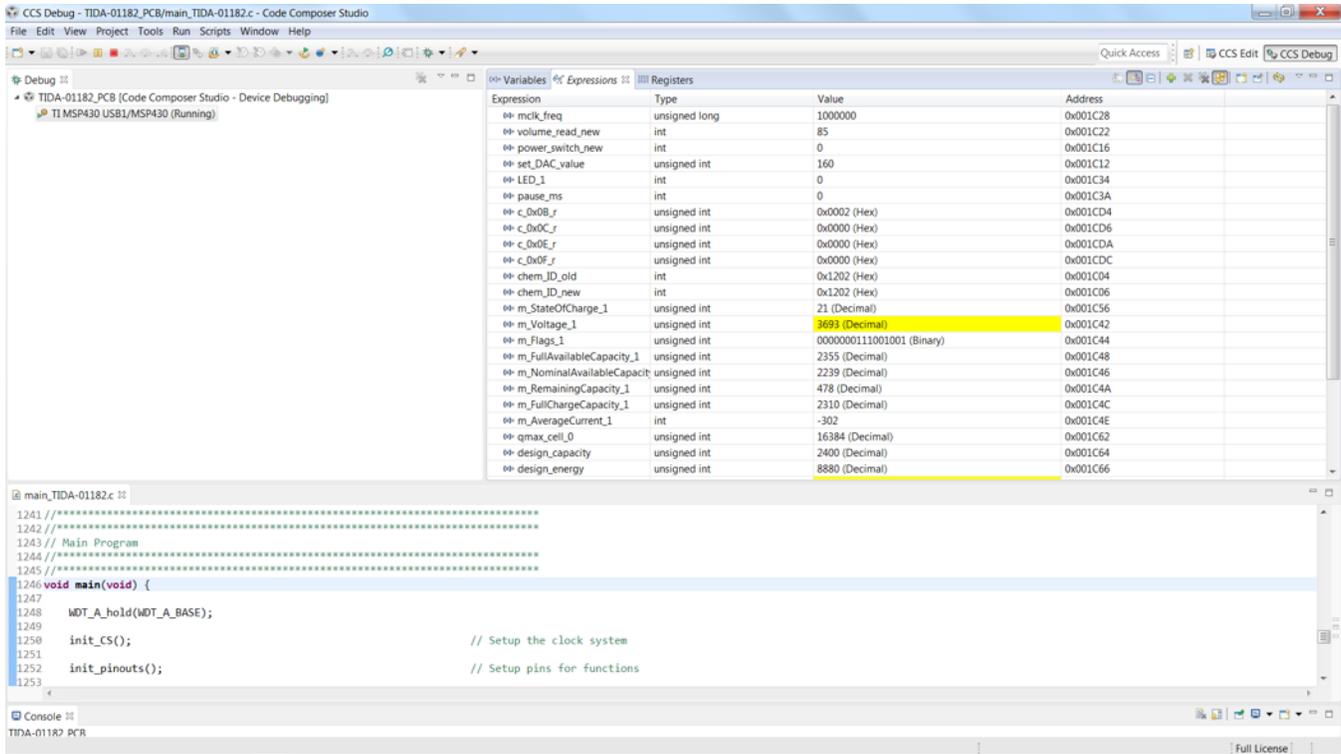


Figure 19. CCS Screenshot Variables

Figure 20 is a picture of the basic debugging test setup used with CCS to write the test code.

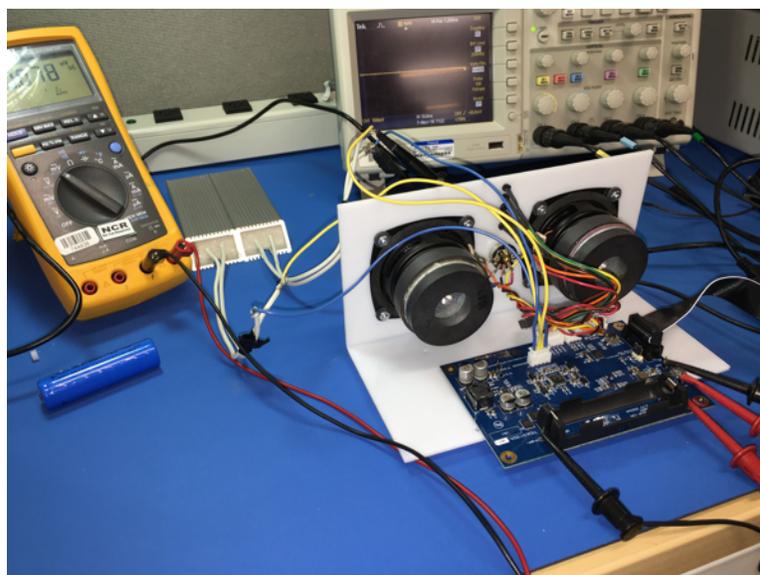


Figure 20. TIDA-01182 Test Bench Debug

### 3.2 Scope Shots

#### 3.2.1 Boost Regulator

The boost regulator output was clean and varied by about  $\pm 4\%$  across several units. In the scope shot in Figure 21, channel 1 in yellow is the boost regulator DC image and channel 2 is the same boost regulator using an AC view to look at the output ripple. The ripple was better than the expected 20 mV, providing a quiet clean audio power source. The peak-to-peak spikes were developed from the current that was sources to the Class D amplifier showing a good load regulation.

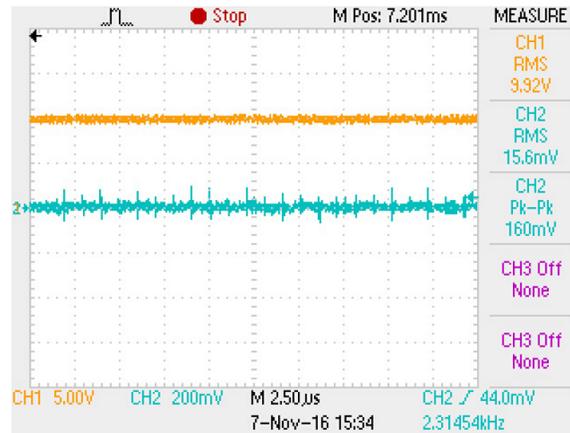


Figure 21. Boost Regulator Output

#### 3.2.2 Class D Output

The output of the Class D amplifier when referenced to ground looks like a 1-MHz square wave. The overshoot spikes are from the inductance of the traces on the PCB and the wires to the load resistors.

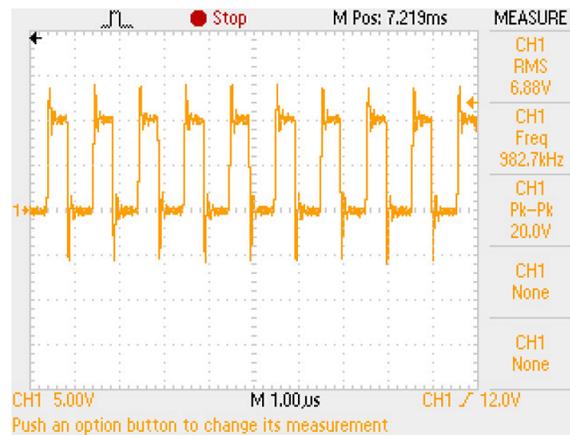


Figure 22. Class D Output Ground Reference

Figure 23 is a view of the Class D amplifier when connected differentially across the speaker. The square wave is gone and only a few high frequency spikes are present. These spikes are from the overshoot and ringing that occurs during the rising and falling edges of the Class D square waves. At 1 MHz these spikes are not audible, but may cause radiated EMI. Pay extra attention to the board layout to minimize radiated EMI.

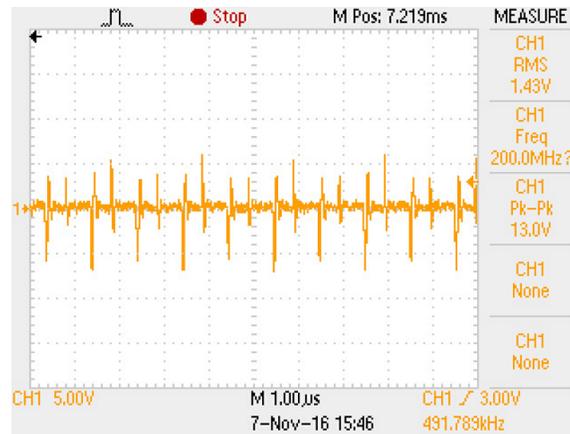


Figure 23. Class D Output Differential


If the traces on the PCB are kept short and the wires to the speakers are kept to a minimum, then the standard ferrite bead and capacitor filters are sufficient to keep the noise to a minimum and prevent unwanted radiated emissions as in Figure 24.



Figure 24. Class D Differential FFT Output

### 3.2.3 Charge Cycle

This charge cycle used a 1-A power supply. The charger opted to charge at 800 mA based on the voltage drop on the output of the wall power supply. The charge time was 1.6 hours to a full charge. The charge voltage for this battery is set to 4.2-V DC. The max charge current is 2.4 A. The charge termination is set to 240 mA and terminated as expected.

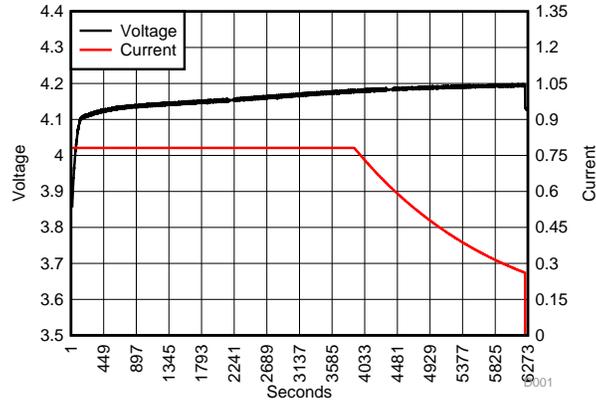

**Figure 25. Charge Cycle Plot**

### 3.2.4 Thermal Results

The charger thermal profile shows good thermal dispersion and a sufficient amount of heat dissipation. While charging at 2.5 A, the charger maintained a well-controlled thermal profile. The extra copper used in the flooded ground planes helps to provide the ability to sink the heat but also to spread the heat evenly throughout the PCB. The extra copper on the top and bottom layers also help to dissipate the heat so it does not build up in the circuit board.

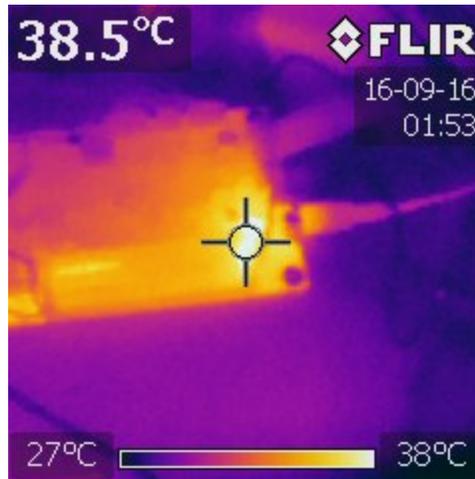


Figure 26. Charger Thermal

The Class D amplifier is very efficient and produces minimal heat in the actual IC. The separation of the power and analog grounds did not create a localized hot spot due to poor thermal dispersion. The boost regulator saw a small amount of localized heating. The ground planes were good at drawing the heat from the IC, thereby preventing thermal stress on the IC. Overall, the thermal dispersion and heat dissipation was very good on all parts of the circuits. There were no excessive heat spots and all circuits operated well within thermal limits.

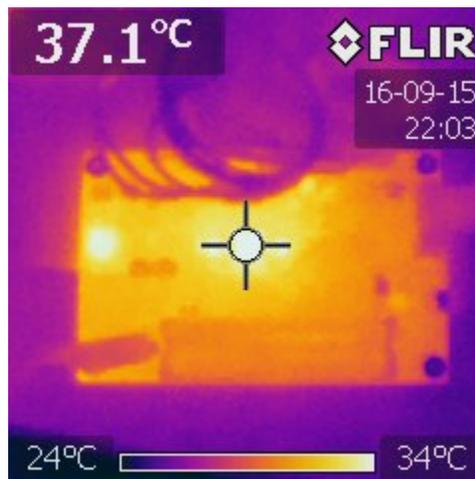


Figure 27. Boost and Class D Thermal

## 4 Design Files


### 4.1 Schematics

To download the schematics, see the design files at [TIDA-01182](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01182](#).

### 4.3 PCB Layout Recommendations

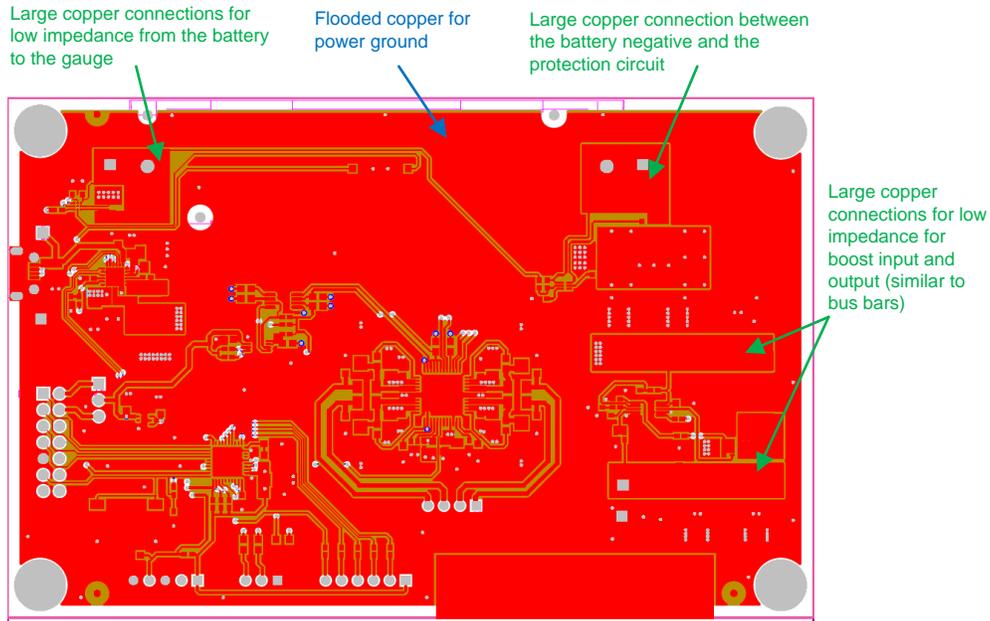

**Figure 28. PCB Top Layer 1 (Component Layer) Layout**



**Figure 29. PCB Inner Layer 2 (Ground Plane Layer) Layout**

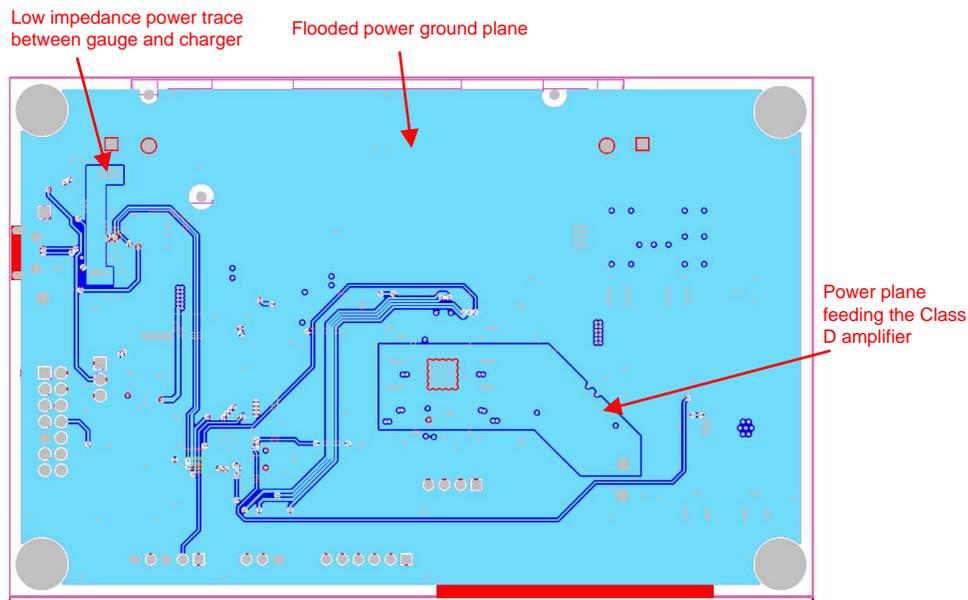


Figure 30. PCB Inner Layer 3 (Power and Ground Plane Layer) Layout

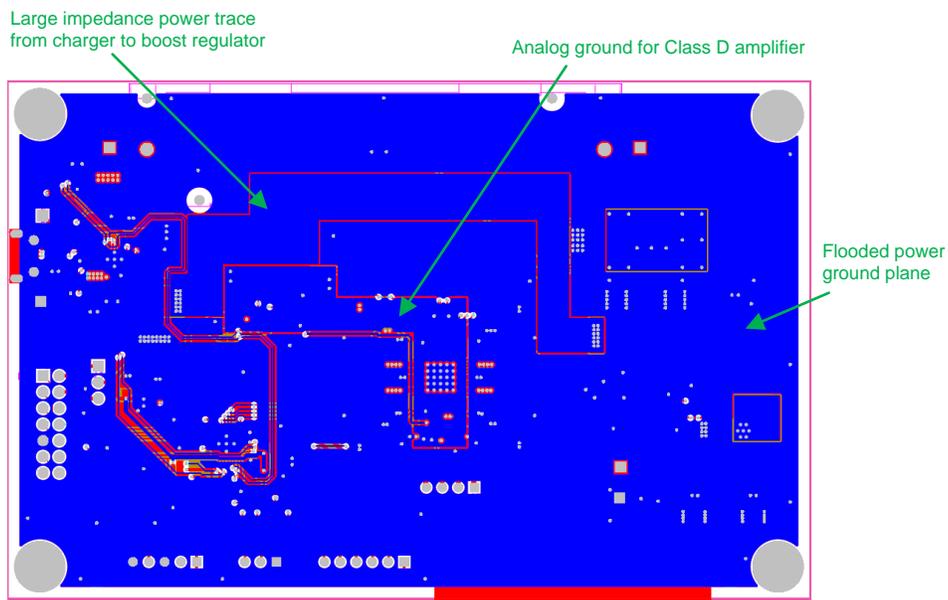


Figure 31. PCB Bottom Layer 4 (Analog Ground and Ground Plane Layer) Layout

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01182](https://www.ti.com/lit/zip/TIDA-01182).

#### 4.4 **Altium Project**

To download the Altium project files, see the design files at [TIDA-01182](#).

#### 4.5 **Gerber Files**

To download the Gerber files, see the design files at [TIDA-01182](#).

#### 4.6 **Assembly Drawings**

To download the assembly drawings, see the design files at [TIDA-01182](#).

### 5 **About the Author**

**GORDON VARNEY** is a Senior Systems and Applications Designer at TI, where he is responsible for developing reference design solutions and demos for the BMS (Battery Management Solutions) Group. Gordon brings to this role his extensive experience in battery management, power, analog, digital, microcontrollers, and energy harvesting. Gordon is an expert in circuit design and board layout as well as programming in several languages. Gordon earned his bachelor of science in electrical engineering (BSEE) from KWU in 1989 and is a member of the Institute of Electrical and Electronics Engineers (IEEE) and the Society of Automotive Engineers (SAE). Gordon is on the Board of Advisors for UTA's Engineering Department and has lectured more than a dozen times at several Colleges and Universities in his 27 years as an engineer.

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated