

TI Designs: TIDA-00892

Isolated RS-485 With Integrated Signal and Power Reference Design



Description

This TI Design provides a compact solution capable of generating isolated DC power while supporting isolated RS-485 communication. The TIDA-00892 consists of a reinforced digital isolator with integrated power combined with an RS-485 transceiver. The solution is designed in such a way as to take up minimal area to achieve this.

Resources

TIDA-00892	Design Folder
ISOW7841	Product Folder
SN65HVD1473	Product Folder




[ASK Our E2E Experts](#)

Features

- Smallest Combination Solution:
 - Equal to ISOW7841 Device Footprint
- Single Power Supply Solution:
 - No Separate Supply Required to Power the Interface-Side Components
- Reduced BOM Cost; Solution Eliminates Requirement For Separate Transformer
- Simpler Design
- Extendable to Other Full-Duplex RS-485 Transceivers:
 - SN65HVD14xx, SN65HVD7x, and SN65HVD3x
- Can Also be Extended to Half-Duplex With Minor Layout Changes

Applications

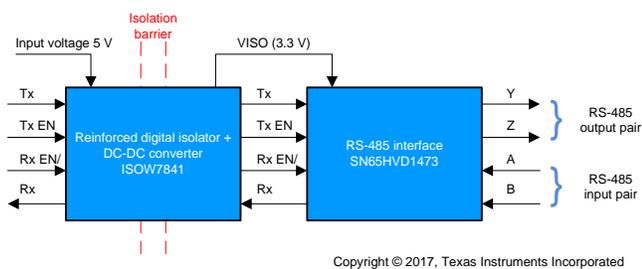- Grid Communication Modules
- Building Automation and HVAC
- Industrial Automation
- Medical Equipment
- Motor Drives



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 System Overview

1.1 Design Theory

1.1.1 Isolation in Data Communication

Most industrial interface systems are areas where noise can seriously affect the integrity of data transfer. A tested method of improving noise performance for any interface circuit is galvanic isolation. Isolating the low-voltage (LV) microcontroller (MCU) side from the high-voltage (HV) interface side has proven to be an effective solution to protect from data corruption and to protect LV side components from seeing HV stresses like electrostatic discharge (ESD), electrical fast transient (EFT), and surge.

Common-mode noise effects and many forms of radiated noise can affect the communication system. Unwanted currents and voltages on a cable bus connecting multiple systems can cause severe problems. These voltages and currents come primarily from two sources: ground loops and electrical line surges. Ground loops occur when a bus or system uses multiple ground paths. Two system grounds connected to the bus and separated by hundreds or thousands of meters may not have the same potential. Because of this potential difference, current flows between these points. This unintended current flow can cause bit errors and damage or destroy components. Electrical surges can be caused by many sources, the result of currents coupled onto cable lines through induction. Long cable lines in industrial environments are especially susceptible to this phenomenon. The operation of electric motors, in particular, causes rapid changes in the ground potential. These changes can generate a current flow through any nearby lines to equalize the ground potential. Other HV stress voltage sources include ESDs, coupled transient noises (EFT) and lightning strikes (surge). These induced surges can result in thousands of volts of potential on the line and manifest themselves as transient current and voltage surges. Thus, a remote node may receive a 5-V switching signal superimposed on a HV level with respect to the local ground. These uncontrolled voltages and currents can corrupt the signal and be catastrophic to the device and system, damaging or destroying the components connected to the bus and resulting in system failure. RS-485 systems that run over long distances and connect multiple systems are especially susceptible to these events.

Isolating the RS-485 system devices from each of the systems connected to the bus prevents ground loops and electrical surges from destroying circuits. Isolation prevents ground loops as each system connected to RS-485 cable bus and each RS-485 circuit has a separate and isolated ground. By referencing each RS-485 circuit only to one ground, ground loops are eliminated. Isolation also allows the RS-485 circuit reference voltage levels to rise and fall with any surges that appear on the cable line. Allowing the circuit voltage reference to move with surges, rather than being clamped to a fixed ground, prevents devices from being damaged or destroyed. To accomplish system isolation, both the RS-485 signal lines and power supplies must be isolated.

1.1.2 RS-485 Communication

Industrial and instrumentation applications (I and I) require transmission of data between multiple systems often over very long distances. The RS-485 bus standard is one of the most widely used physical layer bus designs in I and I applications.

The key features of RS-485 that make it ideal for use in I and I communications applications are:

- Long distance links of up to 4000 feet
- Bidirectional communications possible over a single pair of twisted cables
- Differential transmission increases noise immunity and decreases noise emissions
- Multiple drivers and receivers can be connected on the same bus
- Wide common-mode range allows for differences in ground potential between the driver and receiver

In harsh and noisy environments such as multi-unit residential buildings or industrial settings, an RS-485 bus architecture can be used to implement a low-cost, yet robust communications network. The differential nature of RS-485 signaling makes it less susceptible to external interference. Moreover, the RS-485 specification supports multidrop configurations, thus allowing the connection of multiple meters to a single bus. For instance, RS-485 can be used in an apartment building to transmit data from meters in each apartment to a central unit that aggregates the data from the individual meters, which can then be read through a wireless or PLC link. A similar approach can be used in industrial systems that require multiple cost centers to be metered.

1.2 System Description

The TIDA-00892 reference design combines both data and power isolation along with RS-485 communication interface to provide a robust, low-cost, low footprint solution that customers can directly place on their designs. This TI Design combines a High-Performance Reinforced Digital Isolator with Integrated High-Efficiency, Low Emissions DC-DC Converter (ISOW7841) with a Robust 3.3V Full-Duplex RS-485 Transceiver (SN65HVD1473).

The TIDA-00892 does not require any additional components to generate the isolated power. This makes the solution less than a quarter of the size of all existing solutions using a discrete transformer to generate the required isolated power. This TI Design takes a single power supply input (3 to 5.5 V) and digital signals referred to the input supply level. The board generates an isolated power supply using an integrated DC-DC converter. This isolated supply is used to power the RS-485 transceiver. The input signals are isolated and connected to the transceiver, which converts the digital signals into its RS-485 counterpart.

An electricity grid without adequate communications is simply a power broadcaster. It is through the addition of two-way communications that the power grid is made "smart." Communications enables utilities to achieve three key objectives: intelligent monitoring, security, and load balancing. By using two-way communications, data can be collected from sensors and meters located throughout the grid and transmitted directly to the grid operator's control room. This added communications capability provides enough bandwidth for the control room operator to actively manage the grid. The communications must be reliable, secure, and cost effective. The sheer scale of the electrical grid network makes cost a critical consideration when implementing a communications technology. The communications used in grid infrastructure systems is dominated by RS-485. The TIDA-00892 design can fit in to power the RS-485 bus side and provide a cost-effective, low-footprint solution to this requirement.

PLCs and grid communication systems have been an integral part of factory automation and industrial process control. They use digital and analog I/O modules to interface to sensors, actuators, and other equipment. Analog inputs for the PLC system include temperature sensors and transmitters, current sensors, voltage sensors, and others that can convert a physical quantity to an electrical signal. Digital inputs include push-buttons, proximity switches, photo sensors, pressure switches, and more. These signals need to be either group isolated or per channel isolated. PLCs are expected to work in harsh industrial environments. Hence sensor signals are converted to digital domain and coupled through a digital isolator to control domain. For sensor signal conditioning, power is generated from the backplane side by an isolated DC-DC converter. Fitting in the TIDA-00892 can significantly reduce the required area and bring down the BOM cost by eliminating the requirement for discrete transformers.


Medical equipment need isolation for patient safety. For ECG, multiple leads are connected to the patient. The signal chain must be robust enough to capture very weak signals, digitize and process it, and pass it to the system controller over the isolation barrier. The power for signal processing units is typically generated by onboard isolated DC-DC converters. This power can be replaced directly with the TIDA-00892 to get both communication and power isolation with the RS-485 interface. Also any peripheral connected to this equipment must be isolated from the controller. This solution makes sense to digitally isolate the interface signals and also power up the transceivers.

1.3 Key System Specifications

Table 1. Key System Specifications

FEATURE	SPECIFICATION	VALUE
Input supply	Input voltage	3 to 5 V
Isolated output supply	Output voltage	3.3 V
	Output current	75 mA (3.3 V _{IN}) 130 mA (5 V _{IN})
Communication	Max data rate	20 Mbps (full-duplex communication)
Isolation	Clearance	> 3 mm
	Working voltage	300 V _{RMS}
	CMTI	> 100 kV/μs
EMI or EMC	ESD	6 kV (across barrier)
		16 kV (across RS-485 lines)
	Radiated emissions	CISPR22 (Class A)

1.4 Block Diagram

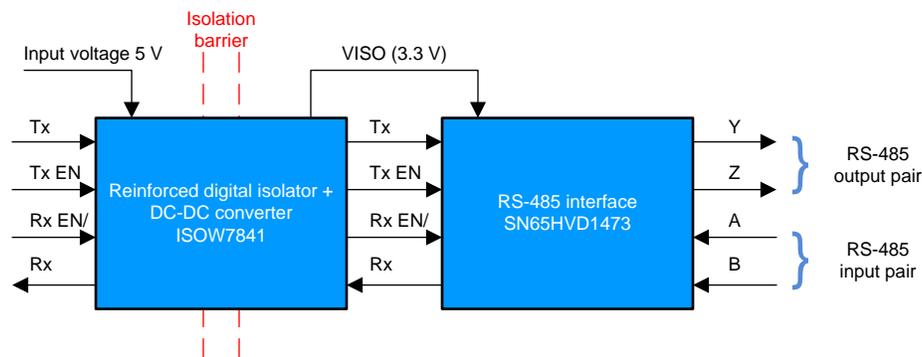

Copyright © 2017, Texas Instruments Incorporated

Figure 1. TIDA-00892 Block Diagram

Figure 1 shows the high-level block diagram of the TIDA-00892. As previously mentioned, this TI Design can be broken down into two main sections: the isolation block (ISOW7841) and the interface block (SN65HVD1473).

The TIDA-00892 works on a single input of 3 to 5.5 V. The integrated power supply can produce an isolated output voltage of 3.3 V (for any input) or 5 V (for VCC1 ≥ 5 V). This can be used to power up the RS-485 interface block. The TIDA-00892 communicates with digital signals on one side and gives the RS-485 lines on the other. The design can be interfaced to an MCU transmitting and receiving data while controlling the TX and RX enable lines. These signals are isolated from the RS-485 lines available for communication to the field side. The SN65HVD1473 RS-485 transceiver and the isolated power supply integrated four channel digital isolator. The side A of the isolator is powered from a 5-V or 3.3-V power supply, the secondary side of the isolator will be powered through the integrated isolated power supply. The integrated power supply can produce two voltage configurations on side B: 5 V or 3.3 V for the 5-V supply on side A and 3.3 V for the 3.3-V supply on side A. The two available voltage configurations enable the same design to be used with other transceivers.

The load in this TI Design is the RS-485 transceiver. The design can interface with the MCU to transmit and receive data and enable transmission and reception. The signals to and from the MCU are isolated from the transceiver. The TIDA-00892 board can be broken down to two main sections: the isolation block and the interface block.

1.5 Highlighted Products

The TIDA-00892 features the following devices from Texas Instruments.

1.5.1 ISOW7841

The ISOW784x is a family of high-performance quad-channel reinforced digital isolators with an integrated high-efficiency power convertor. The integrated DC-DC convertor provides up to 650 mW of isolated power at high efficiency and can be configured for various input and output voltage configurations. These devices eliminate the need for a separate isolated power supply in space-constrained isolated designs. ISOW784x devices provide high electromagnetic immunity and low emissions, while isolating CMOS or LVCMOS digital I/Os. The signal isolation channel has a logic input and output buffer separated by a silicon dioxide (SiO₂) insulation barrier, whereas power isolation uses on-chip transformers separated by a thin film polymer as insulation material. These devices prevent noise currents on a data bus or other circuits from entering the local ground and interfering with or damaging sensitive circuitry. Through innovative chip design and layout techniques, the electromagnetic compatibility of the ISOW784x has been significantly enhanced to ease system level ESD, EFT, surge, and emissions compliance. The high efficiency of the power convertor allows operation at a higher ambient temperature. The ISOW784x family of devices is available in a 16-pin SOIC wide-body (DWE) package.

- Integrated high efficiency DC-DC convertor with on-chip transformer
- Wide input supply range: 3 to 5.5 V
- Regulated 5- or 3.3-V output
- Up to 0.65-W output power
- 130-mA load current (5 to 5 V; 5 to 3.3 V;)
- 75-mA load current (3.3 to 3.3 V)
- Soft start to limit inrush current
- Overload and short circuit protection
- Thermal shutdown
- Signaling rate up to 100 Mbps
- Low prop-delay: 13 ns typical (5-V supply)
- High CMTI: ± 100 kV/ μ s (min)
- Robust electromagnetic compatibility (EMC)
 - System level ESD, EFT, and surge immunity
 - Low radiated emissions
- Safety-related certifications
 - 7071- V_{PK} Reinforced Isolation per DIN V VDE V 0884-10 (VDE V 0884-10): 2006-12
 - 5000- V_{RMS} Isolation for 1 Minute per UL 1577
 - CSA Component Acceptance Notice 5A, IEC 60950-1 and IEC 60601-1 End Equipment Standards
 - CQC Approval per GB4943.1-2011
 - TUV Certification according to EN 60950-1 and EN 61010-1
 - All agency certifications are planned
- Extended temperature range: -40°C to 125°C

1.5.2 SN65HVD1473

The SN65HVD1473 is a full-duplex transceiver that features the highest ESD protection in the RS-485 portfolio, supporting ± 16 -kV IEC61000-4-2 contact discharge and $> \pm 30$ -kV HBM ESD protection. This RS-485 transceiver has a robust 3.3-V driver and receiver and is offered in a standard SOIC package as well as in a small-footprint MSOP package. The large receiver hysteresis of the SN65HVD1473 device provides immunity to conducted differential noise and the wide operating temperature enables reliability in harsh operating environments. This device combines a differential driver and a differential receiver, which operate from a single 3.3-V power supply. Each driver and receiver has a separate input and output pins for full-duplex bus communications designs. These devices all feature a wide common-mode voltage range which makes the devices suitable for multi-point applications over long cable runs.

The SN65HVD1473 device has active-high driver enables and active-low receiver enables. A low, less than 5- μ A standby current can be achieved by disabling both the driver and receiver.

- 1/8 unit-load options available
 - Up to 256 nodes on the bus
- Bus I/O protection
 - $> \pm 30$ -kV HBM protection
 - $> \pm 16$ -kV IEC-61000-4-2 Contact Discharge
 - $> \pm 4$ -kV IEC61000-4-4 Fast Transient Burst
- Extended industrial temperature range:
 - -40°C to 125°C
- Large receiver hysteresis (70 mV) for noise rejection
- Low power consumption
 - < 1.1 -mA quiescent current during operation
 - Low standby supply current: 10 nA typical, < 5 μ A (max)
- Glitch-free power-up and power-down protection for hot-plugging applications
- 5-V tolerant logic inputs compatible with 3.3-V or 5-V controllers

2 Getting Started Hardware

2.1 Board Description

Figure 2 shows the size of the isolated RS-485 with an integrated power solution. The solution space within the board has been marked in red and is slightly bigger than the ISOW7841 IC. The full board measures 31 × 13.3 mm while the actual solution space (marked in red) is 11.9 × 11.2 mm.

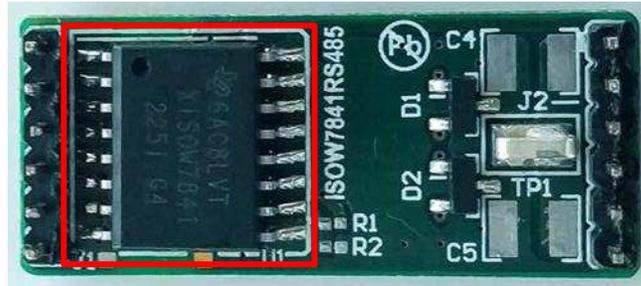


Figure 2. Solution Space

Figure 3 shows the locations of the connectors on the board for interfacing with the solution.

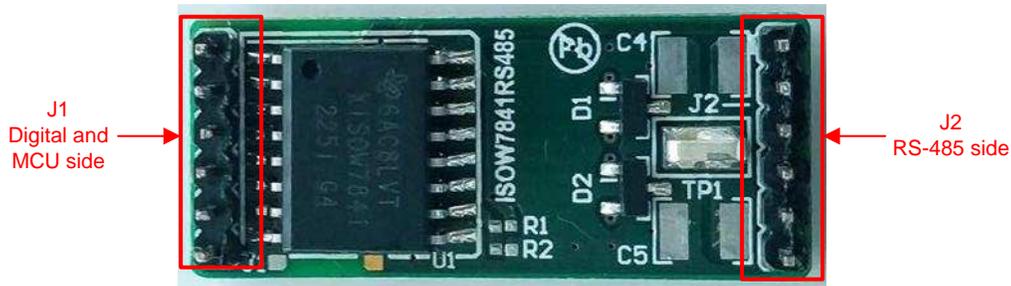


Figure 3. Connectors

2.2 Connectors Description

Table 2. Connectors

CONNECTOR	PIN POSITION	PIN NAME	I/O OR POWER	DESCRIPTION
J1	1	VIN	Power	Input supply (3 to 5.5 V)
	2	Tx	I	Digital driver input
	3	Tx EN	I	Driver enable
	4	Rx EN/	I	Receiver enable
	5	Rx	O	Digital receiver output
	6	GND1	Ground	Input supply ground
J2	1	VISO	Power	Isolated power output
	2,3	Y, Z	O	RS-485 output pair
	5,4	A, B	I	RS-485 input pair
	6	GND2	Ground	Isolated output ground

The design comes pre-populated with two of the TI ICs (ISOW7841 and SN65HVD1473) and a 120- Ω termination resistor on the bus to match the transmission line impedance. VCC1 and GND1 are connected at Pin 1 and Pin 6 of J1, respectively. The digital input can be applied to Pin 2 of J1 and the receiver output can be observed on Pin 5 of J1. On the other side of the board, the differential bus lines A and B (RS-485 input lines) are Pin 5 and Pin 4 respectively on J2, while Y and Z (RS-485 output lines) are connected to Pin 2 and Pin 3 respectively on J2. The boards include male berg heads to allow bus cables to be securely attached.

Connect MCU Tx to Pin 2 of J1 and MCU Rx to Pin 5 of J1. Connect the driver and receiver enable lines from MCU to Pins 3 and 4, respectively. The RS-485 lines, AB and YZ, need to be connected as individual pairs of twisted pair cables. The system can be configured and used for half-duplex or full-duplex communication by providing appropriate transmit and receive enable signal from MCU side.


This TI Design can be extended to other RS-485 transceivers by replacing the existing transceiver on the board and selecting the right voltage configuration. The isolated output voltage configuration can be easily changed by changing the resistor combination of R1 and R2. See [Table 3](#) to understand how to realize the required voltage configuration.

Table 3. Voltage Configurations

INPUT VOLTAGE (V)	OUTPUT VOLTAGE (V)	R1 (Ω)	R2 (Ω)
5.0	5.0	Populate	Do Not Populate
	3.3	Do Not Populate	Populate
3.3	3.3	Do Not Populate	Populate
	5.0	Invalid configuration	Invalid configuration


3 Testing and Results

3.1 Test Setups

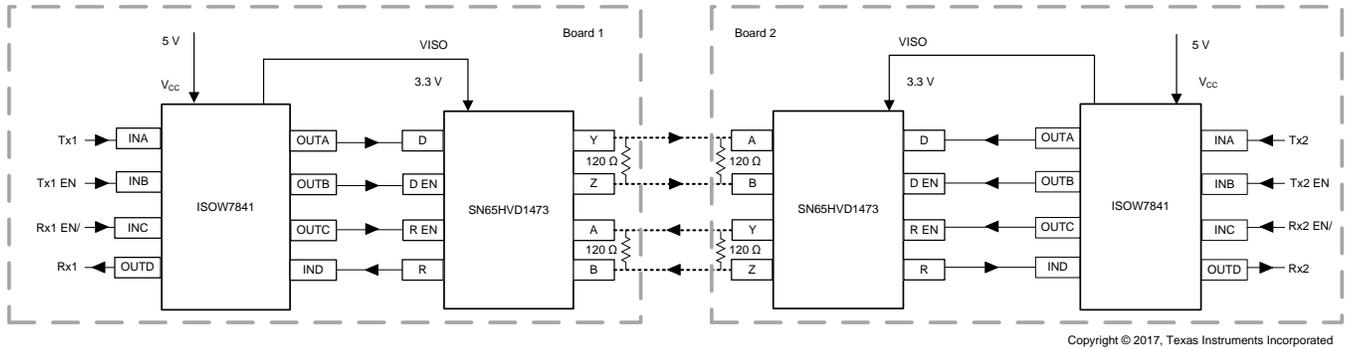

Copyright © 2017, Texas Instruments Incorporated

Figure 4. Full Duplex Communication Test Setup

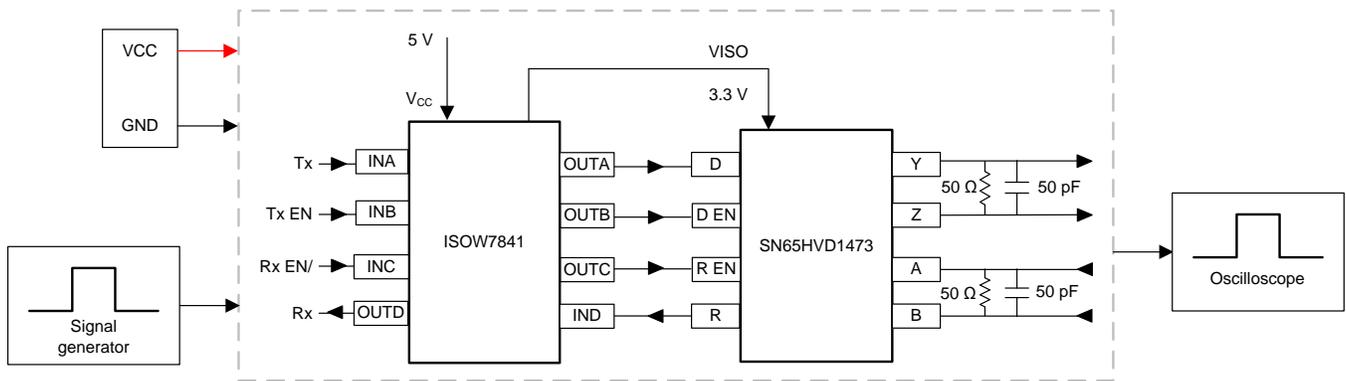

Copyright © 2017, Texas Instruments Incorporated

Figure 5. Typical Test Setup

3.2 Full-Duplex Communication

As shown in [Figure 4](#), two boards are connected to each other, forming a full-duplex system for the test setup. Both the boards are powered with a 5-V supply voltage and VISO is configured for 3.3 V in a full-duplex mode (Tx EN pulled high and Rx EN pulled low).



Figure 6. Full-Duplex Communication

3.3 Propagation Delay

As shown in Figure 5, single board propagation delay from digital side to RS-485 side was measured.

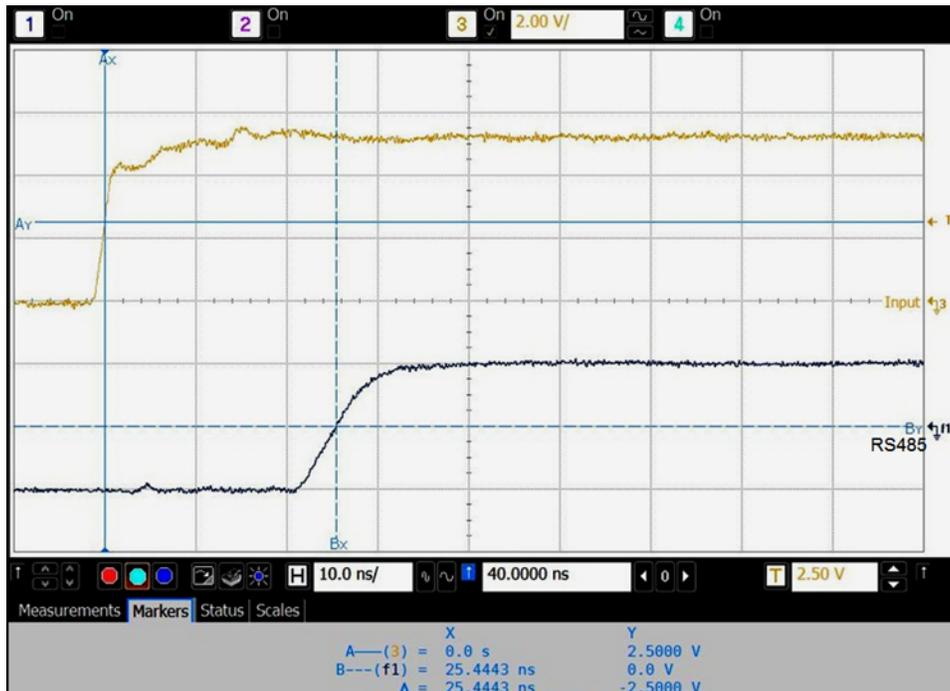


Figure 7. Propagation Delay (Low to High)

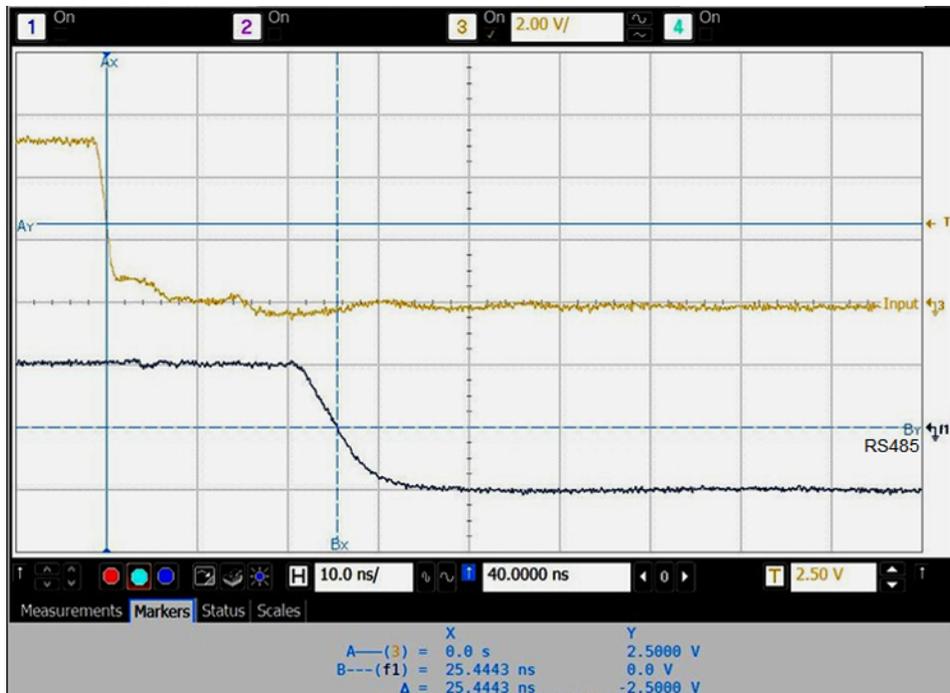


Figure 8. Propagation Delay (High to Low)

3.4 Jitter

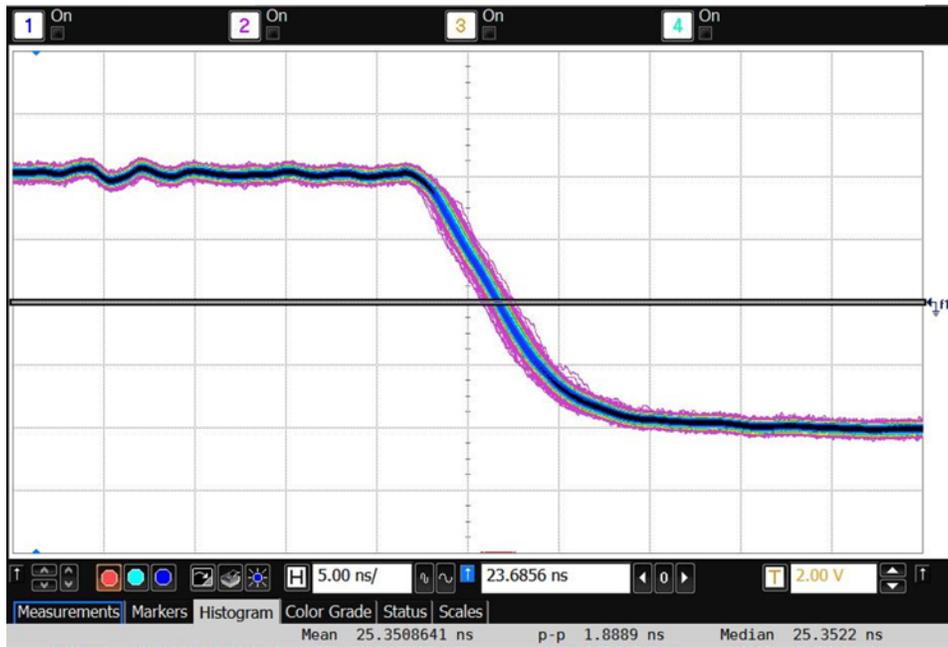


Figure 9. Jitter

3.5 Eye Diagram

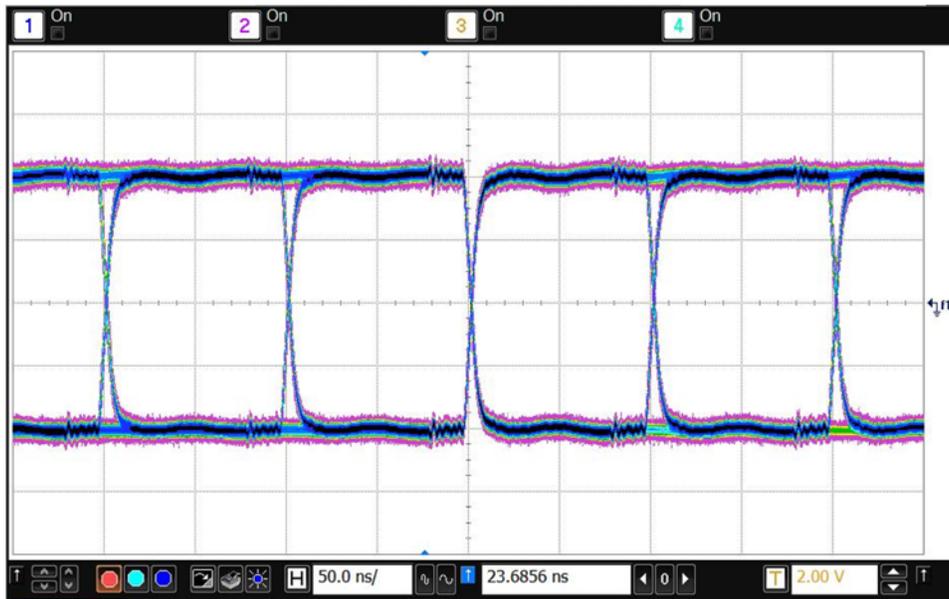


Figure 10. Eye Diagram

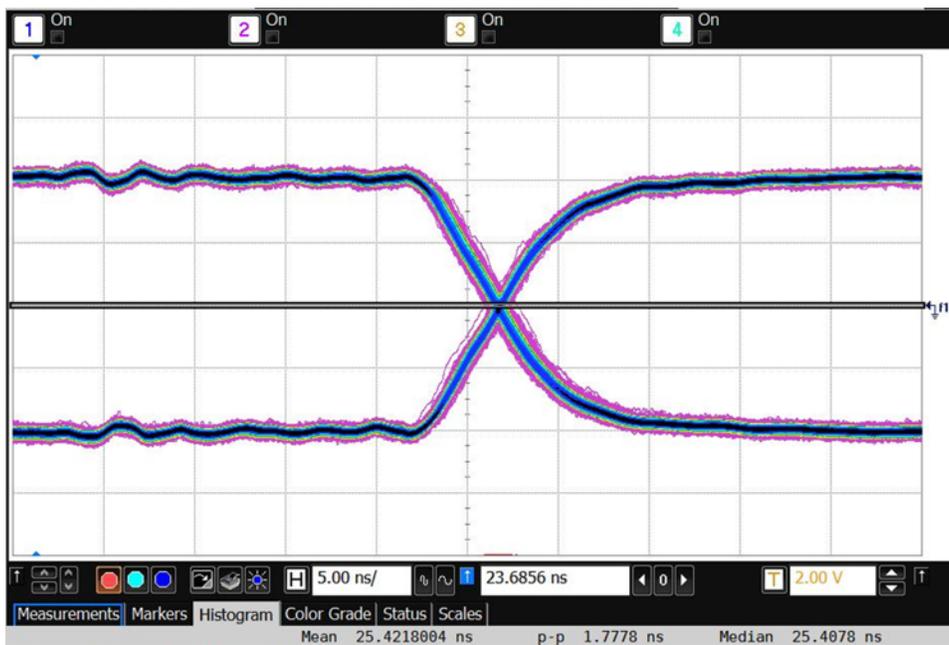


Figure 11. Eye Closure

3.6 Current Consumption

Current consumption of the TIDA-00892 was measured with both the RS-485 receiver and transmitter toggling at different data rates. Termination resistors were populated as per [Figure 5](#).

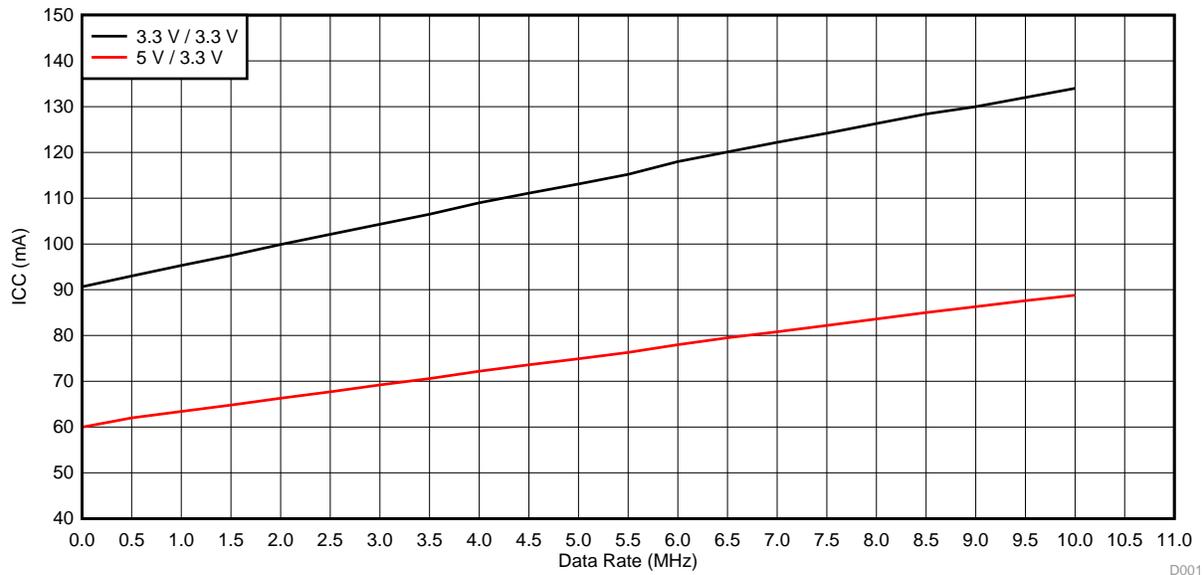


Figure 12. ICC versus Data Rate

3.7 IEC-ESD Performance (IEC-61000-4-2)

Contact discharge IEC-ESD testing was performed on the TIDA-00892 using a pointed contact discharge tip. The board was subjected to mainly two kinds of ESD strikes. In the "Across barrier" row, the interface side was struck with the reference ground or power earth connected at the MCU side ground (GND1). Similarly for the "Same side" row, the interface lines were struck with the reference ground or power earth connected to the interface side ground (GND2). [Table 4](#) shows the IEC-ESD test results. Each of the stressed pins were subjected to 10 strikes of each polarity of the corresponding stress voltage.

Table 4. IEC-ESD Results

NATURE OF STRIKE	STRIKE POINT	STRESS VOLTAGE	RESULT
Across barrier	VISO	±6 kV	Pass
	Y	±6 kV	Pass
	Z	±6 kV	Pass
	A	±6 kV	Pass
	B	±6 kV	Pass
	GND2	±6 kV	Pass
Same side	Y	±16 kV	Pass
	Z	±16 kV	Pass
	A	±16 kV	Pass
	B	±16 kV	Pass

3.8 Radiated Emissions (CISPR 22)

The emissions measurements were done according to CISPR 22 standard in a certified facility. Figure 13 shows the emissions measurement for the TIDA-00892 design when the communication lines were being operated under a static high condition.

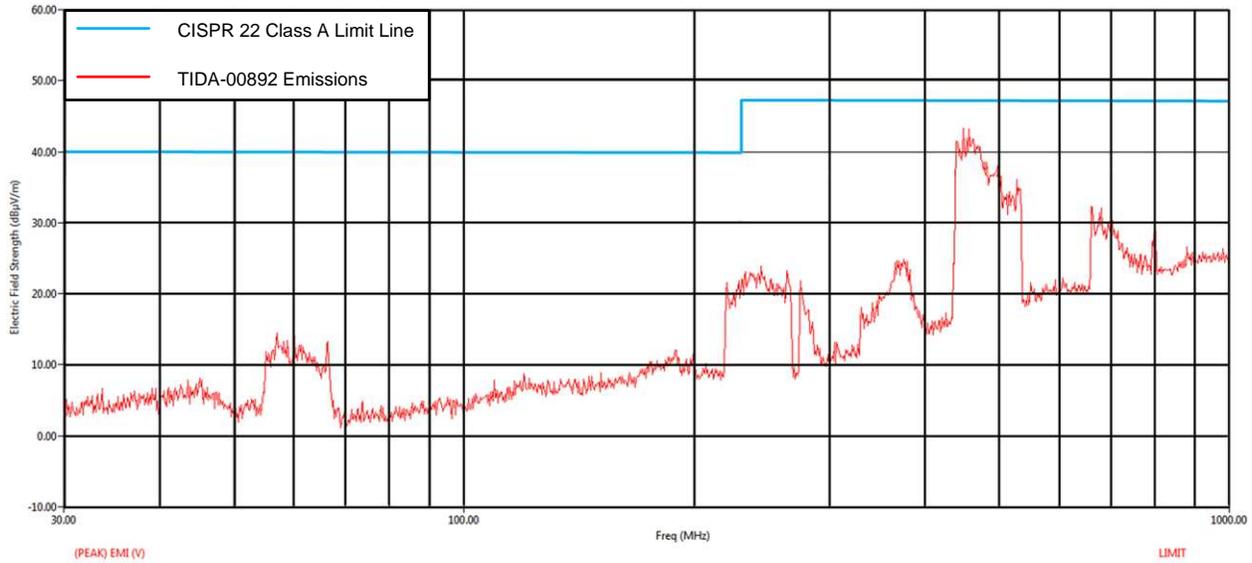


Figure 13. Radiated Emissions (CISPR 22)

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-00892](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-00892](#).

4.3 PCB Layout Recommendations

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-00892](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-00892](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-00892](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-00892](#).

5 Related Documentation

1. Texas Instruments, [ISOW784x High-Performance, 5000-VRMS Reinforced Quad-Channel Digital Isolators With Integrated High-Efficiency, Low-Emissions DC-DC Converter](#), ISOW784x Datasheet (SLLSEY2)
2. Texas Instruments, [SN65HVD147x 3.3-V Full-Duplex RS-485 Transceivers With \$\pm 16\$ -kV IEC ESD](#), SN65HVD147x Datasheet (SLLSEJ8)
3. Texas Instruments, [Isolated RS-232 With Integrated Signal and Power Reference Design](#), TIDA-01230 Design Guide (TIDUCT3)

5.1 Trademarks

All trademarks are the property of their respective owners.

6 About the Authors

ANAND REGHUNATHAN is an applications engineer at Texas Instruments, where he is responsible for defining new high-performance products and providing application support on existing products for industrial and automotive markets, specifically for isolation products. Anand brings to the role an experience in EMC testing for both isolation and interface products. Anand earned his bachelor of technology (B.Tech) in electronics and communications engineering from College of Engineering, Trivandrum, India.

NEERAJ BHARDWAJ is an applications engineer at Texas Instruments, where he is responsible for defining new high-performance analog products and application support on existing products for industrial and automotive markets. He has a high level of experience in motor drive systems and high-voltage systems with an emphasis in safety applications, standards, test and characterization of mixed signal processors, and EMC cognizant systems design. In his previous role, he led the Systems and Applications team in the Safety and Security Microcontroller Group in TI. He mentors teams on competitive robotics. He has over 20 years of experience in the industry and has worked for TI since 2005. He has a B.E. degree in electrical engineering specialized in high voltage and power electronics from the Government Engineering College Jabalpur and a M.Tech. degree in aerospace engineering specialized in control and guidance from the Indian Institute of Technology Bombay.

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Original (March 2017) to A Revision	Page
• Changed interface name in TIDA-00892 block diagram	1

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated