

TI Designs

High-Precision Reference Design for Buffering a DAC Signal



Description

This reference design features the industry's first zero-crossover and zero-drift amplifier (OPA388) to buffer the analog output of a digital-to-analog converter (DAC). It demonstrates the importance of the zero-crossover and zero-drift feature and how they can minimize the integral nonlinearity (INL) of the system as well as make use of the full-scale range of the DAC (DAC8830).

Resources

TIDA-01402	Design Folder
OPA388	Product Folder
DAC8830	Product Folder
REF5050	Product Folder

Features


- 16-Bit Resolution Digital Input Output Driver
- 2.7- to 5.5-V Single-Supply Operation
- High Accuracy, INL < 0.5 LSB
- Fast SPI, up to 50 MHz
- Industry-Standard Pin Configuration
- OPA388 Zero-Crossover, Zero-Drift Amplifier

Applications

- Field Transmitter
- Data Acquisition
- [Wireless Infrastructure](#)
- [Test and Measurement](#)



[ASK Our E2E Experts](#)

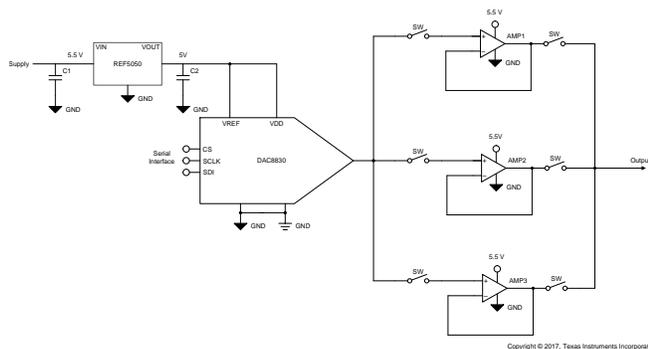

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 System Overview

1.1 System Description


This TI reference design features a precision voltage-output digital-to-analog converter (DAC) that provides excellent linearity and a buffered output with different precision operational amplifiers. This TI Design demonstrates the importance of having an op amp with zero-crossover and zero-drift to minimize the integral nonlinearity (INL) of the system, giving a precision analog output. The design provides a solution of linearization throughout the full scale range of the DAC using a zero-crossover, zero-drift device as the buffered output. This design guide addresses component selection, design theory, and test results of the TIDA-01402 reference design. The following subsections describe the various devices within this reference design system and highlight the characteristics most critical in implementing the corresponding functions.

1.2 Key System Specifications

Table 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Resolution	16-bit resolution
Output range	0 V _{REF}
Linearity error	INL < 0.5 LSB
DNL	0.5 LSB
Gain drift	0.1 ppm/°C
Zero-crossover	140-dB CMRR True RRIO

1.3 Block Diagram

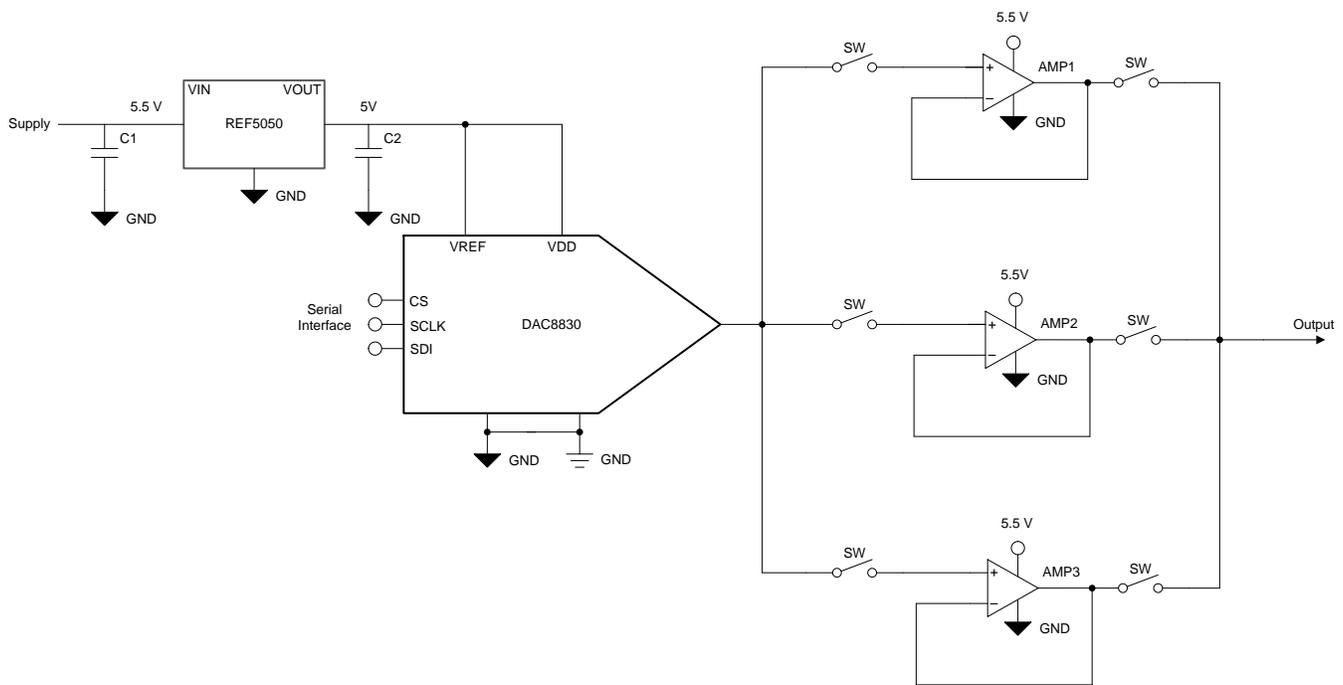

Copyright © 2017, Texas Instruments Incorporated

Figure 1. TIDA-01402 Block Diagram

1.4 Highlighted Products


The TIDA-01402 reference design features the following devices:

- OPA388 (Section 1.4.1): Precision, Zero-Drift, Zero-Crossover, True RRIO Operational Amplifier
- DAC8830 (Section 1.4.3): 16-Bit, Single-Channel, Ultra-Low-Power, Voltage Output DAC
- REF5050 (Section 1.4.4): 3 $\mu\text{Vpp/V}$ Noise, 3 ppm/ $^{\circ}\text{C}$ Drift Precision Voltage Reference

For more information on each of these devices, see their respective product folders at TI.com.

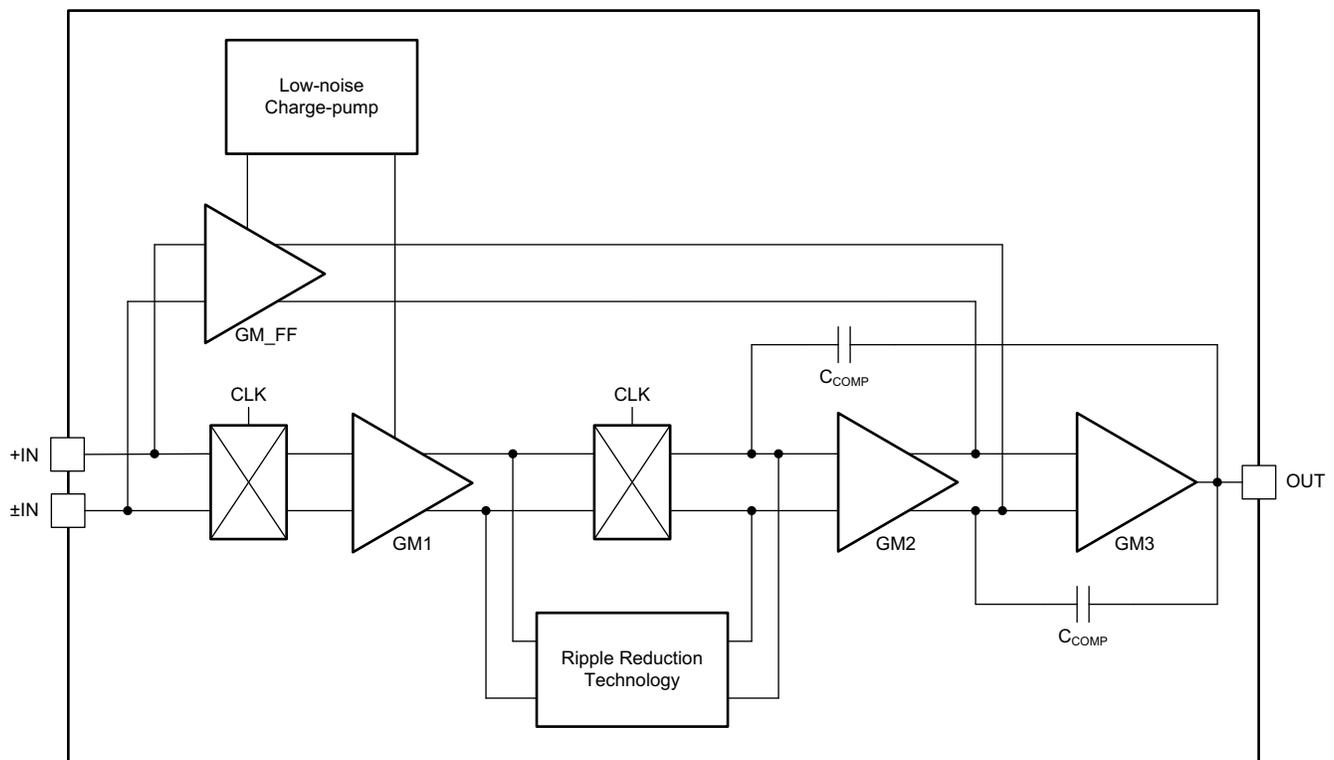1.4.1 OPA388

The OPAx388 is a family of ultra-low-noise, zero-drift, zero-crossover, rail-to-rail input and output op amp. These devices operate from 1.8 to 5.5 V, excellent AC performance, and only 0.25 μV of offset and 0.005 $\mu\text{V}/^{\circ}\text{C}$ of drift over temperature. The OPAx388 is ideal for driving high-precision, analog-to-digital converters (ADCs) or buffering the output of high-resolution, DACs, as well as a wide range of general purpose applications.




Copyright © 2016, Texas Instruments Incorporated

Figure 2. OPA388 Functional Block Diagram

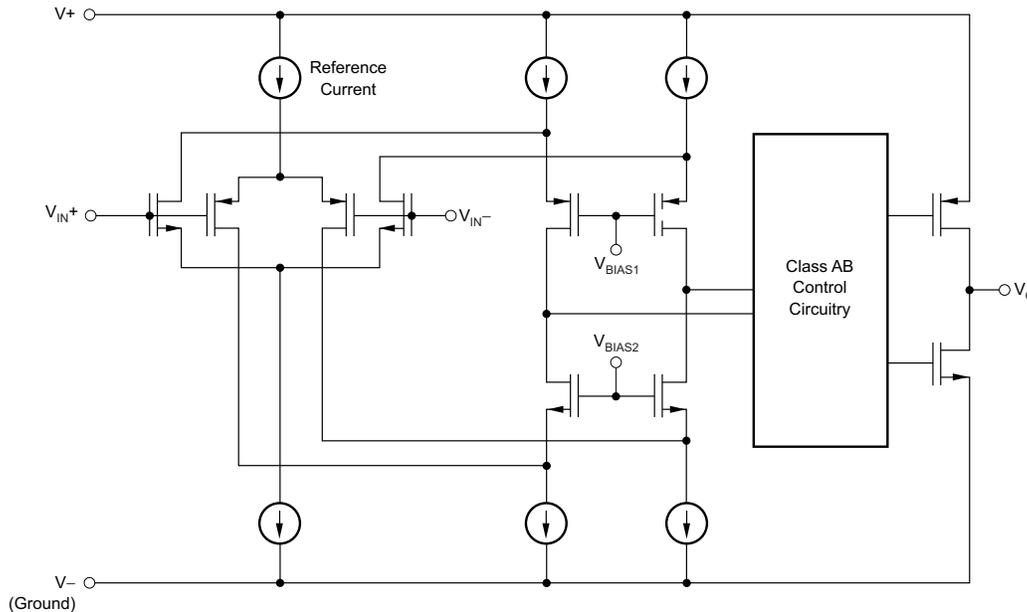1.4.2 OPA340

The OPA340 device operates on a single supply as low as 2.5 V with an input common-mode voltage range that extends 500 mV below ground and 500 mV above the positive supply. Output voltage swing is to within 1 mV of the supply rails with a 100-kΩ load. These devices offer excellent dynamic response ($BW = 5.5 \text{ MHz}$, $SR = 6 \text{ V}/\mu\text{s}$), yet the quiescent current is only 750 A. The devices class AB output stage is capable of driving 600-Ω loads series and extends 500 mV beyond the supply. Rail-to-rail input and output swing significantly increases dynamic range, especially in low-supply applications.




Copyright © 2016, Texas Instruments Incorporated

Figure 3. OPA340 Functional Block Diagram

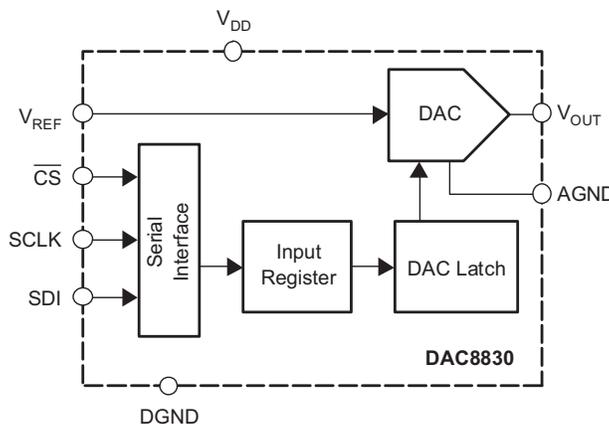1.4.3 DAC8830

The DAC8830 is a single, 16-bit, serial-input, voltage-output DACs operating from a single 3- to 5-V power supply. This device provide excellent linearity (1 LSB INL), low glitch, low noise, and fast settling ($1.0 \mu\text{s}$ to 1/2 LSB of full-scale output) over the specified temperature range of -40°C to 85°C . The output is unbuffered, which reduces the power consumption and the error introduced by the buffer. The DAC8830 output is 0 V to V_{REF} .




Copyright © 2017, Texas Instruments Incorporated

Figure 4. DAC8830 Functional Block Diagram

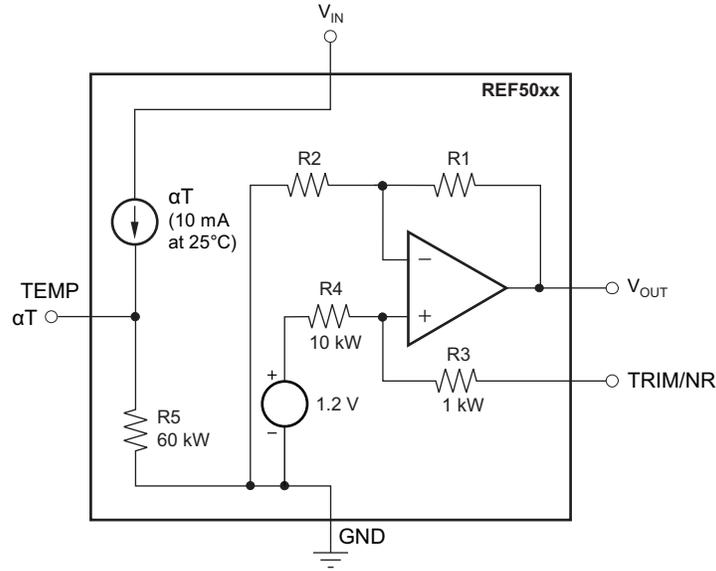1.4.4 REF5050

The REF5050 is a low-noise, low-drift, very high precision voltage reference. This reference is capable of both sinking and sourcing current, and has excellent line and load regulation. Excellent temperature drift (3 ppm/°C) and high accuracy (0.05%) are achieved using proprietary design techniques. These features, combined with very low noise, make the REF5050 ideal for use in high-precision data acquisition systems.



Copyright © 2017, Texas Instruments Incorporated

Figure 5. REF5050 Functional Block Diagram

1.5 Design Theory

INL is the maximum deviation between the ideal output of a DAC and the actual output level after offset and gain error have been calibrated out of the measurement. This specification is important for measuring error in a DAC. For applications that require extremely high precision, INL is the most valuable specification to consider. This is because there is no way to externally compensate INL like one can offset, gain, and zero-code errors. This means for high-precision applications picking a DAC with high linearity such as the DAC8830 is vital as well as the amplifier chosen for the buffered output. The datasheet of the DAC8830 recommends an operational amplifier with low-offset to eliminate the need of offset trims. With a 16-bit DAC and 5-V reference, the LSB voltage is 76 μV.


Input bias current should also be low because the bias current multiplied by the DAC output impedance (approximately 6.25 kΩ) adds to the zero-code error. Rail-to-rail input and output performance are required. For fast settling, the slew rate of the op amp should not impede the settling time of the DAC. Output impedance of the DAC is constant and code-independent, but in order to minimize gain errors the input impedance of the output amplifier should be as high as possible. The amplifier should also have a 3-dB bandwidth of 1 MHz or greater. The amplifier adds another time constant to the system, thus increasing the settling time of the output. A higher 3-dB amplifier bandwidth results in a shorter effective settling time of the combined DAC and amplifier. The OPA388 and OPA340 both meet these requirements as shown in Table 2; however, the OPA340 will effect the INL because it has a crossover region due the two-input differential pairs needed to achieve rail-to-rail input. The OPA388 is a zero-crossover part that uses a charge-pump topology resulting in no crossover region that would effect the INL.

Table 2. Specification Comparison of OPA388 and OPA340

DEVICE	V _{OS} TYPICAL (μV)	INPUT BIAS CURRENT TYPICAL (pA)	RAIL-TO-RAIL	SLEW RATE (V/μS)	UNITY GAIN BANDWIDTH (MHz)
OPA388	±0.25	±30	RRIO	5	10
OPA340	±150	±0.2	RRIO	6	5.5

The internal structure of a traditional rail-to-rail CMOS op amp consists of two differential transistor pairs. In operation, the op amp switches from one pair to the other. This error induced transition region is called the crossover region. Devices with zero-crossover technology eliminate this input offset crossover region. The zero-crossover feature eliminates this input offset transition region that traditional rail-to-rail CMOS op amps have. Eliminating this region provides a highly linear common-mode voltage (V_{CM}) range, assuring maximum linearity and lowest distortion for buffering DAC outputs.

As previously stated, a traditional rail-to-rail input CMOS architecture has two differential pairs. **Figure 6** highlights both circled in red and blue. The differential pair consisting of two PMOS transistors is circled in blue and operates for common-mode input voltages from V_{EE} to $V_{CC}-1.8V$. The other differential pair consisting of two NMOS transistors is circled in red and operates for common-mode input voltages ranging from $V_{CC}-1.8V$ to V_{CC} .

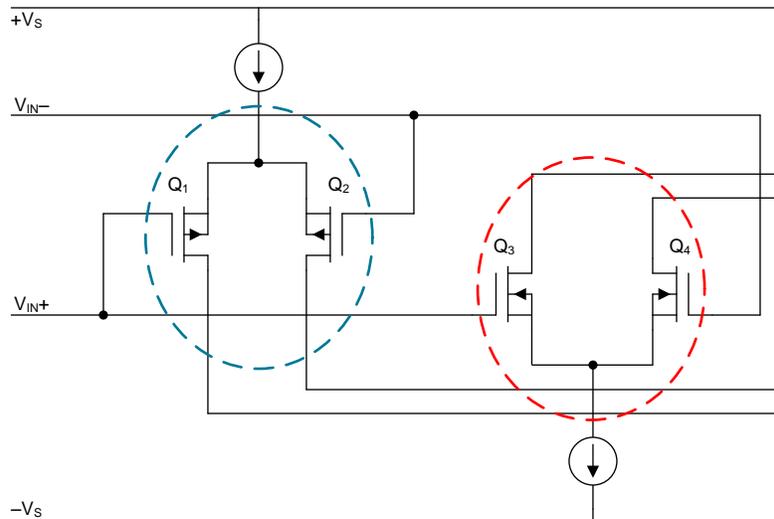


Copyright © 2017, Texas Instruments Incorporated

Figure 6. Simplified Traditional Rail-to-Rail Input Topology

These two input transistor pairs will have independent and uncorrelated input offset voltages. This means the PMOS pair and the NMOS pair will intrinsically have different input offset voltage values. During the transition from one PMOS pair to the NMOS pair, and vice versa, there is a crossover region at 1.8 V below the positive rail where both inputs are conducting. Within this region, the DC input offset voltage can change, which may cause a shift in the amplifiers AC parameters. This is input crossover distortion where the non-linearity introduces a common-mode dependent offset and harmonic distortion. Using the TINA-TI™ SPICE tool (available at <http://www.ti.com/tool/tina-ti>), this offset error can be simulated.

Figure 7 shows a buffer, non-inverting configuration with a typical rail-to-rail input CMOS amplifier. In non-inverting configurations, the common-mode signal is equal to the input signal.

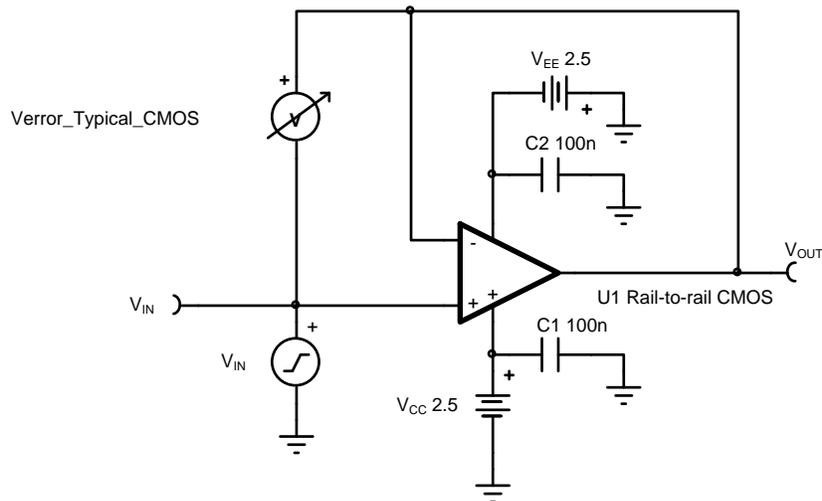

Copyright © 2017, Texas Instruments Incorporated

Figure 7. TINA-TI Schematic for measuring V_{ERROR} of Traditional Rail-to-Rail CMOS Amplifier

Figure 8 shows the simulated results of applying a -2.4 - to 2.4 -V DC transfer sweep on a buffer configuration. The graph clearly shows $V_{error_Typical_CMOS}$ abruptly shift when the common-mode voltage is within the crossover region. This crossover distortion varies on different devices with this input architecture. As with any error source, consider the error budget and decide if this error can be tolerated. If this error source is beyond the error budget, an alternative device is needed that has the zero-crossover feature.


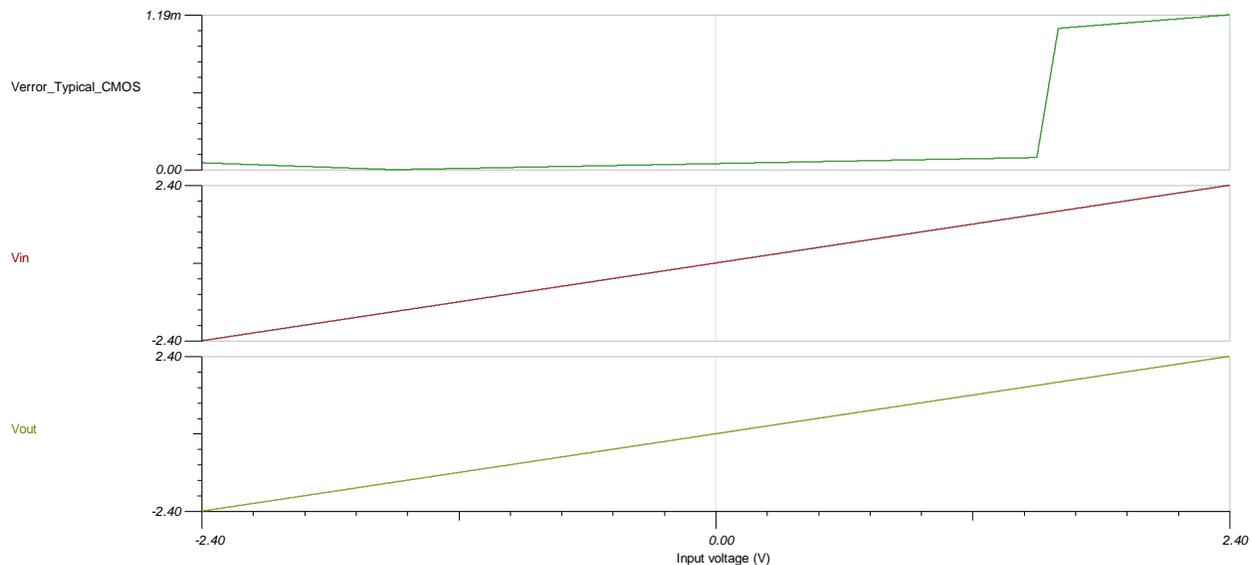


Figure 8. TINA-TI Simulation Results for Measuring Traditional Rail-to-Rail CMOS Op Amp V_{ERROR}


Zero-crossover topology uses a charge pump to achieve voltages beyond the input rail with a single differential transistor pair. This use of a single stage ensures a linear output without distortion over the entire common-mode range. Devices such as the OPA388 include an internal charge pump that powers the amplifier input stage with an internal supply rail that is higher than the external power supply. The internal supply rail allows a single differential pair to operate and to be linear across the entire input common-mode voltage range, as shown in [Figure 9](#).

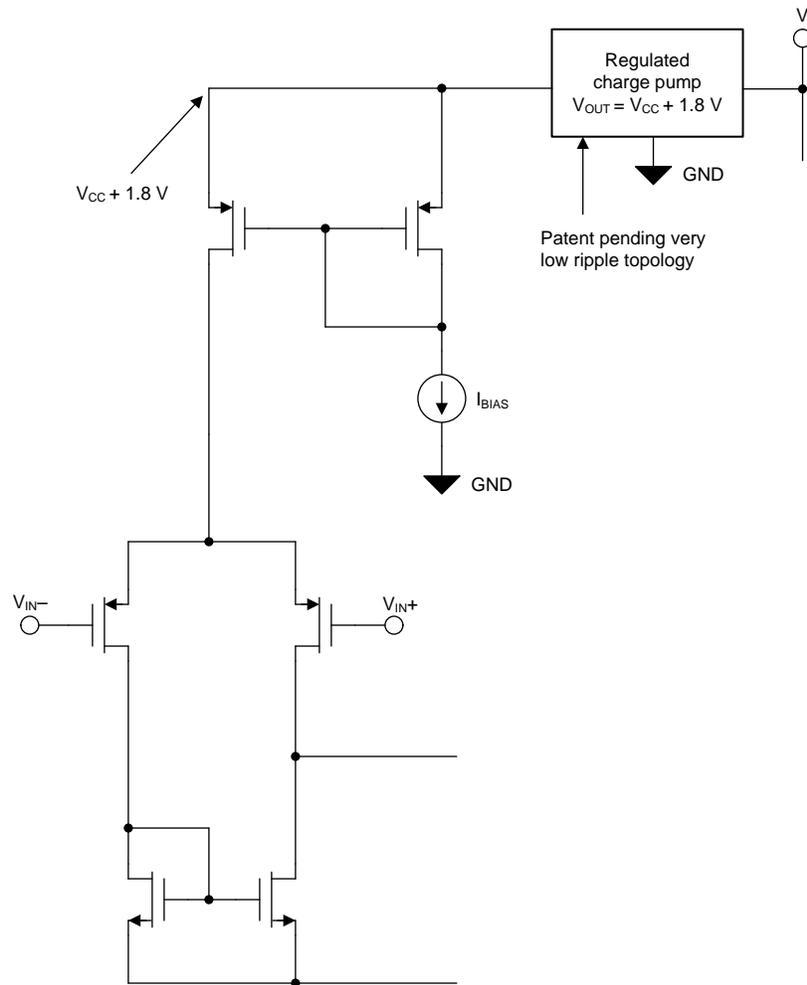

Copyright © 2017, Texas Instruments Incorporated

Figure 9. Zero-Crossover Charge-Pump Topology

Figure 10 shows a simplified representation of the charge pump used in zero-crossover devices. In this case, the charge pump boosts the supply voltage up by 1.8 V while still maintaining a low power budget. This is enough to overcome the 1.8-V drop from the positive rail on the PMOS transistor input pair. One concern that often accompanies charge pump circuits is the noise generated from the use of a switching capacitor to achieve a voltage boost. However, in the case of the OPA388, the amount of noise generated by the charge pump's ripple design is lower than the noise floor, and thus unnoticeable. Using the TINA-TI SPICE tool, Figure 10 shows a buffer configuration with the zero-crossover OPA388. As stated in the previous section, this non-inverting configuration was chosen because the common-mode signal is equal to the input signal.

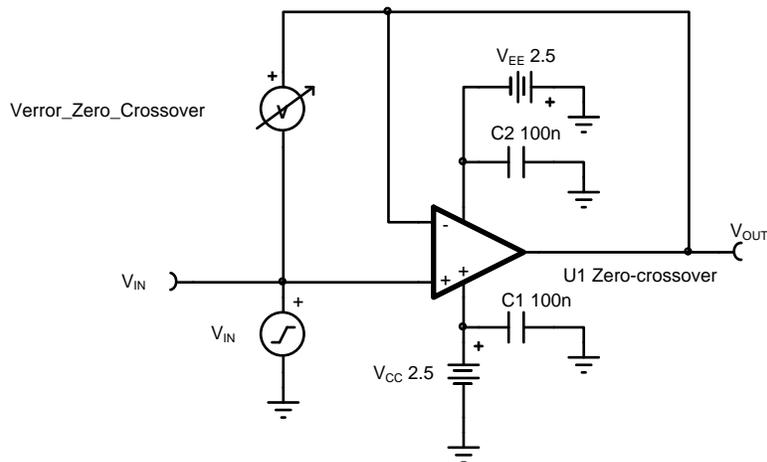

Copyright © 2017, Texas Instruments Incorporated

Figure 10. TINA-TI Schematic for Measuring V_{ERROR} of Zero-Crossover Amplifier

Figure 11 shows the simulated results of applying a -2.4 - to 2.4 -V DC transfer sweep on a buffer configuration. The `Verror_Zero_Crossover` trace in Figure 11 no longer shows an abrupt shift with input common-mode change because there is no crossover region.

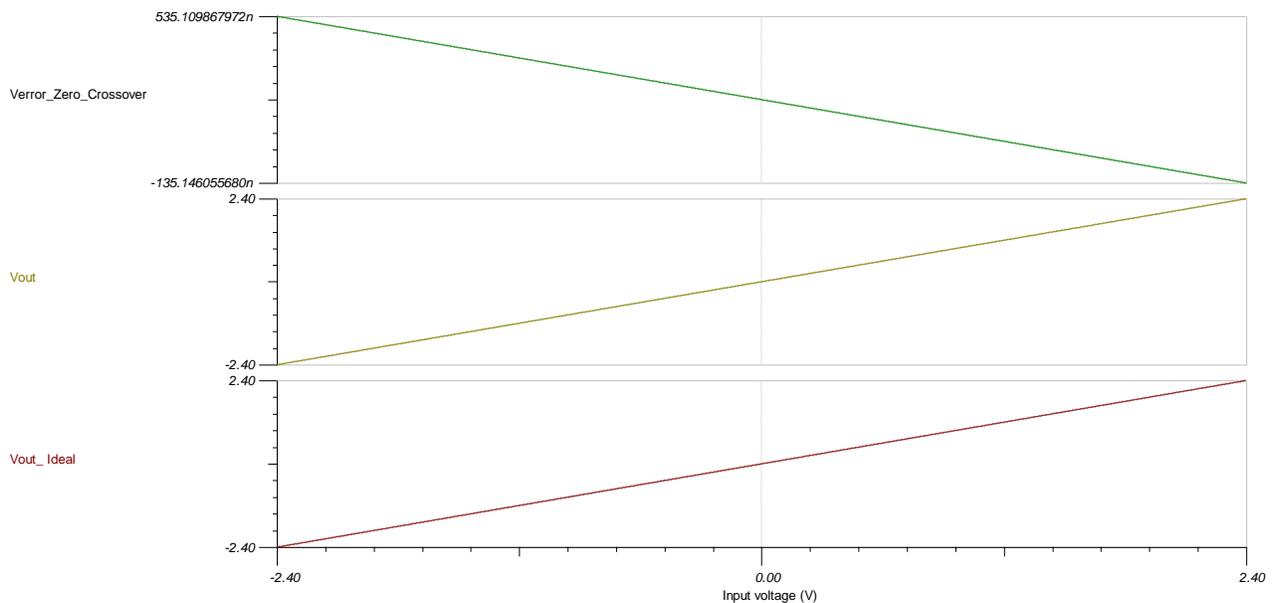


Figure 11. TINA-TI Simulation Results for Measuring Zero-Crossover Op Amp V_{ERROR}

The OPA388 and a typical CMOS amplifier were used in identical, unity-gain buffering configurations (see [Figure 12](#)). These amplifiers were both fed a pure sine wave with an amplitude of 2 V (4 V_{P-P}). The outputs of these circuits were captured in the FFT spectrum. [Figure 12](#) illustrate the output voltage spectrum for the OPA388 and a typical CMOS rail-to-rail amplifier, respectively. The output of the OPA388 has very few spurs and harmonics when compared to the typical rail-to-rail CMOS amplifier. This is the effect of eliminating the crossover region with zero-crossover technology.

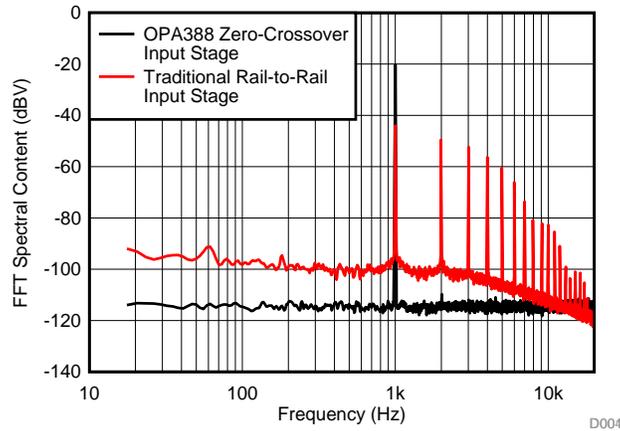


Figure 12. Buffer FFT Spectrum Comparison

2 Getting Started Hardware

2.1 Hardware

This section provides an overview of the TI Design hardware and instructions on setting up and using this board.

This hardware features a 16-bit resolution DAC, precision low-noise voltage reference, and three channels to select between different op amps as a buffered output.

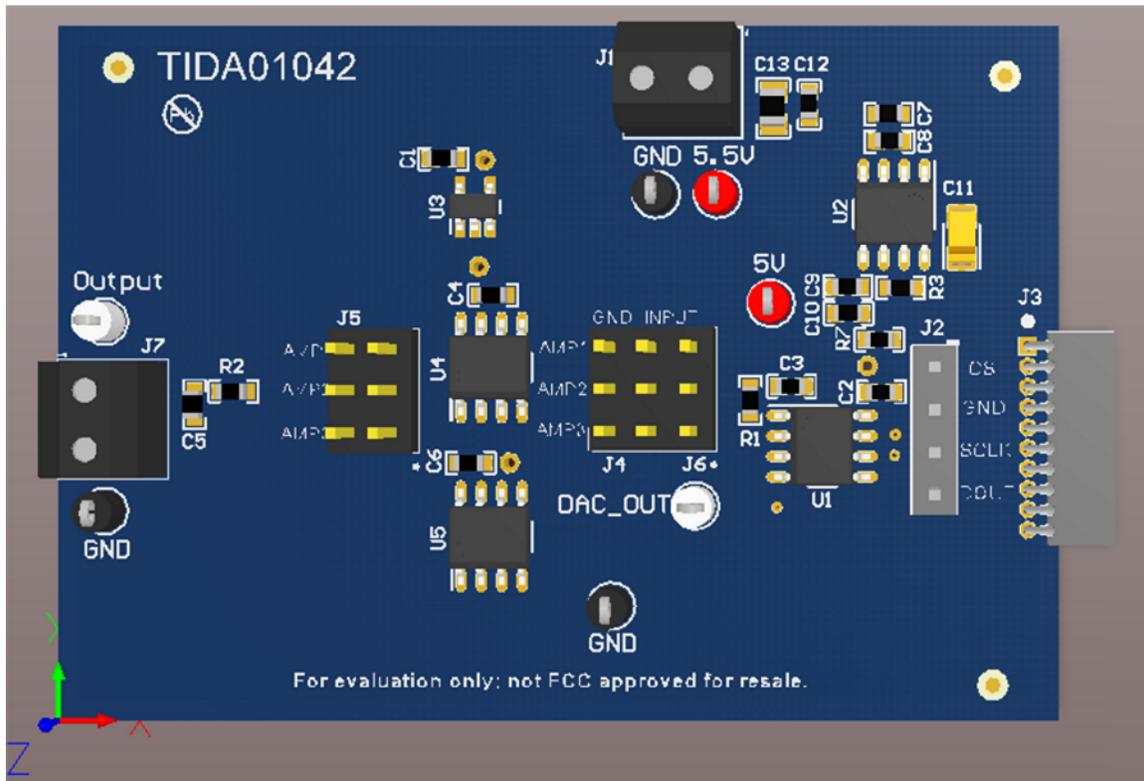


Figure 13. 3D Model Top View of TI Reference Design Board

The board is supplied through connector J1 with a 5.5-V supply. The analog section is directly powered by a 5.5-V DC supply, the digital section has a dedicated 5-V supply on the board provided by the REF5050.

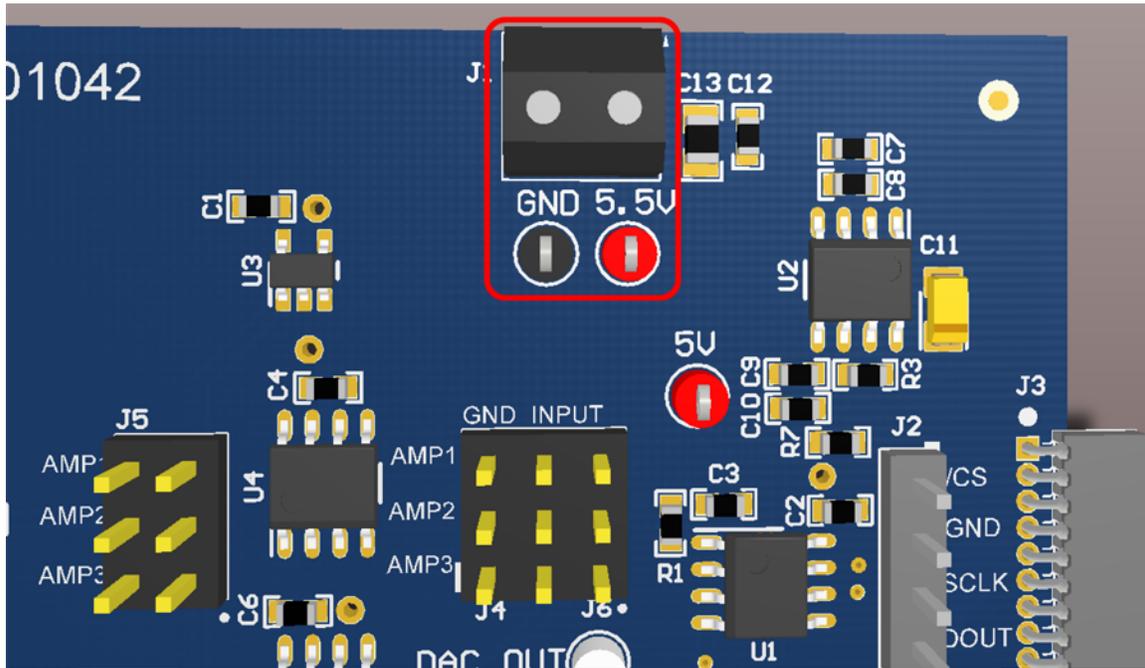


Figure 14. Terminal J1 for 5.5-V DC Supply

Connector J3 is used for the serial peripheral interface (SPI) to send digital values to DAC8830. The dot near the J3 designator on the board indicates pin 1.


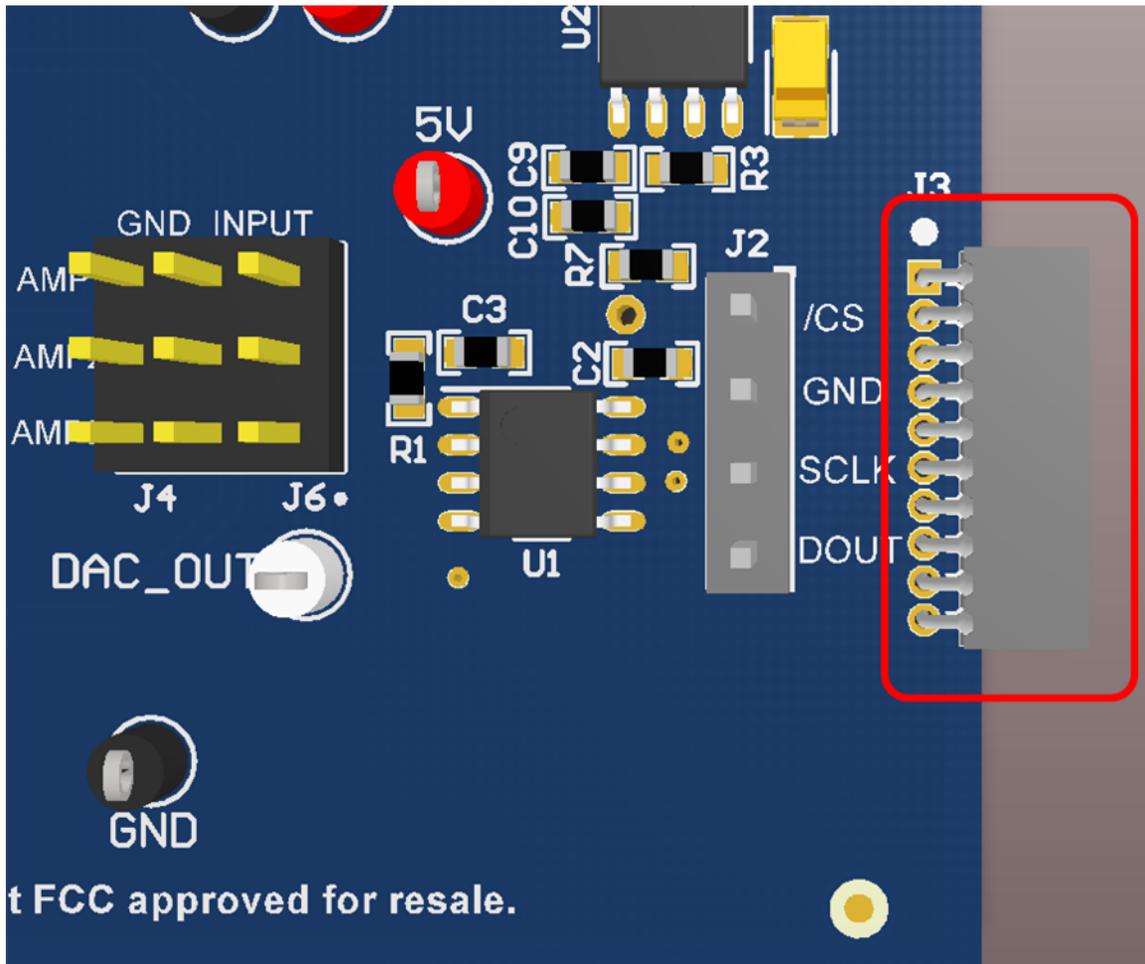


Figure 15. SPI Female Connector J3

Figure 16 shows schematic designation of the following pins needed for SPI: CS, GND, SCLK, and DOUT.

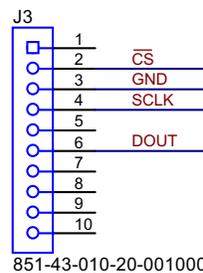

851-43-010-20-001000

Copyright © 2017, Texas Instruments Incorporated

Figure 16. SPI Connector J3 Pin Designation

Connector J2 can be used to measuring the SPI signals for debugging.

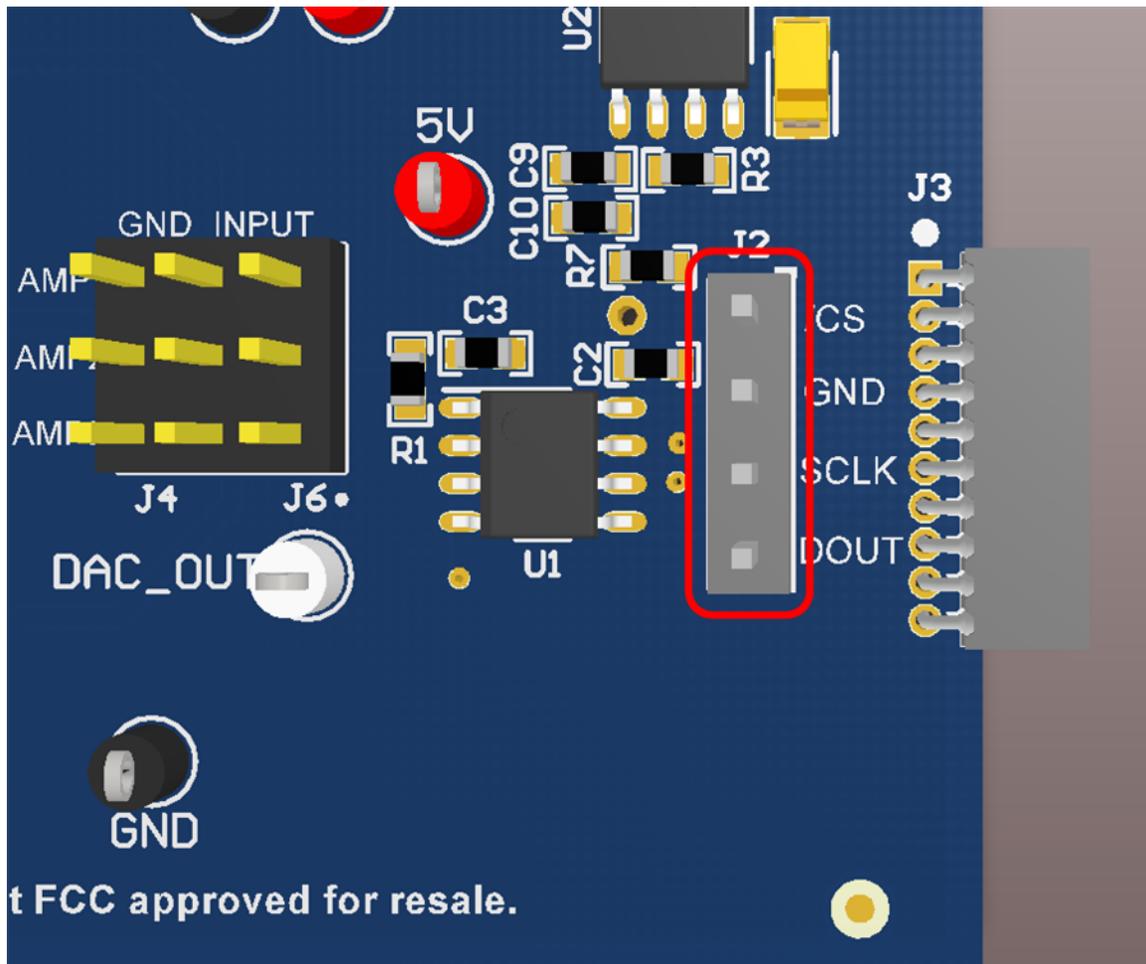


Figure 17. J2 SPI Probing Pins

Connector J7 is the output of the chosen operational amplifier to buffer the DAC output.

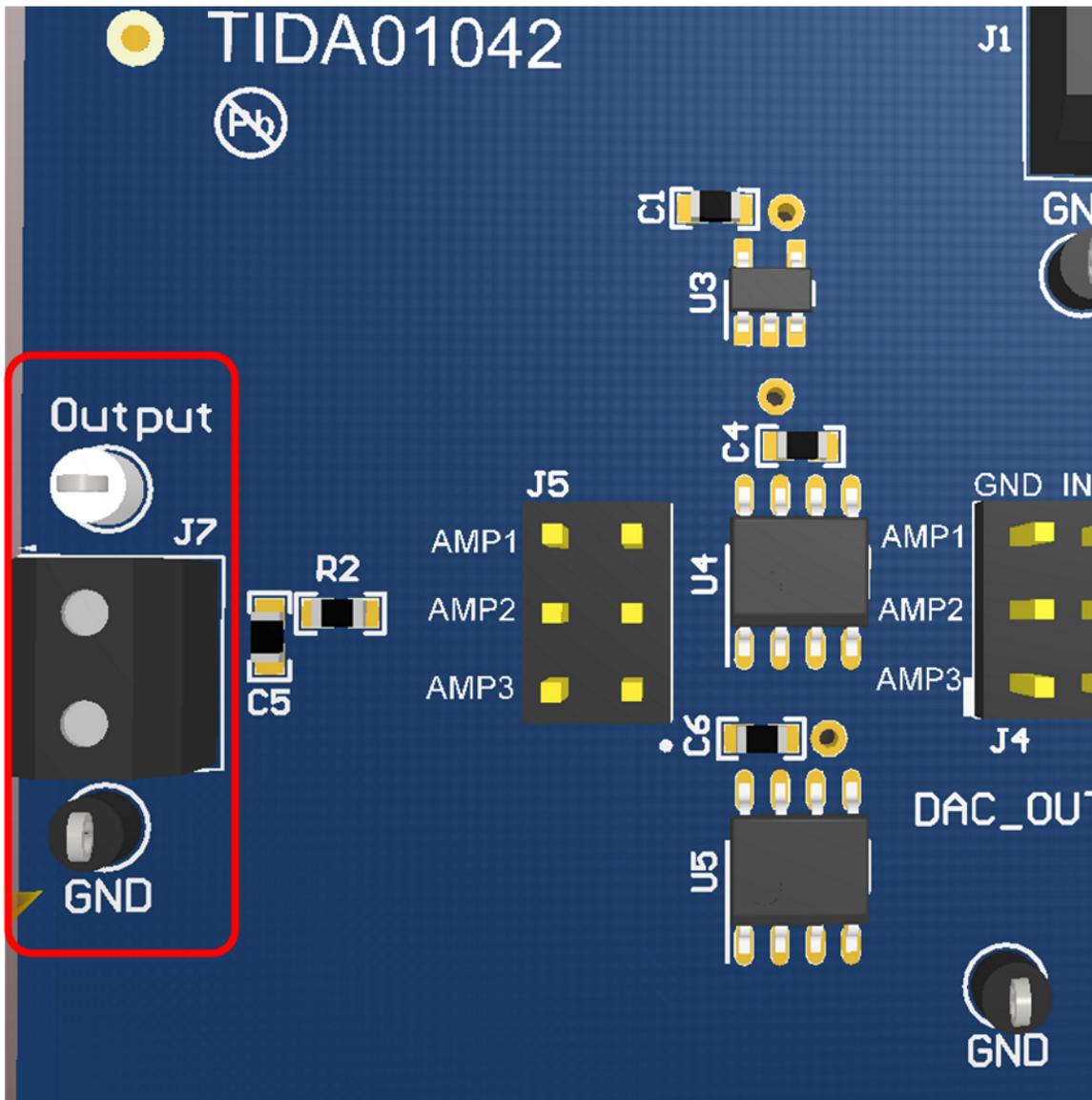


Figure 18. Terminal J7 Buffer Amplifier Output

Connector J4 and J6 are jumper headers. This header will connect the output of the DAC to one of the op amps and ground the input of the unused amplifiers.

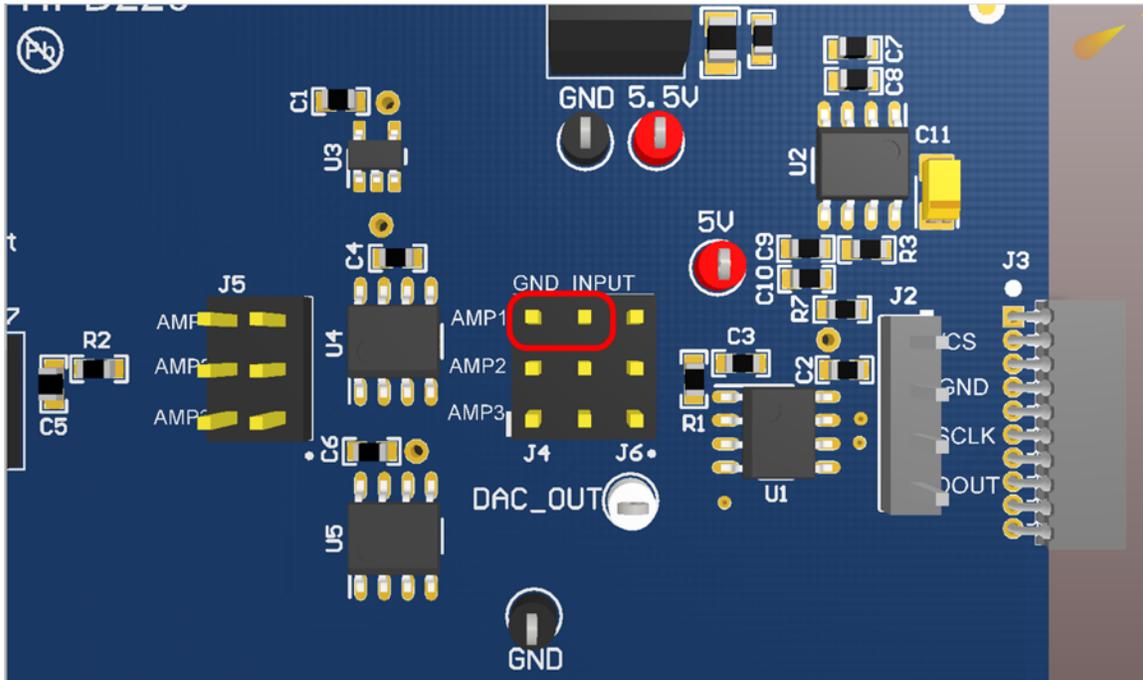


Figure 19. Header Connector for Ground Unused Amplifier Input

Figure 20 shows the position the jumper has to be to connect the DAC to the AMP1.

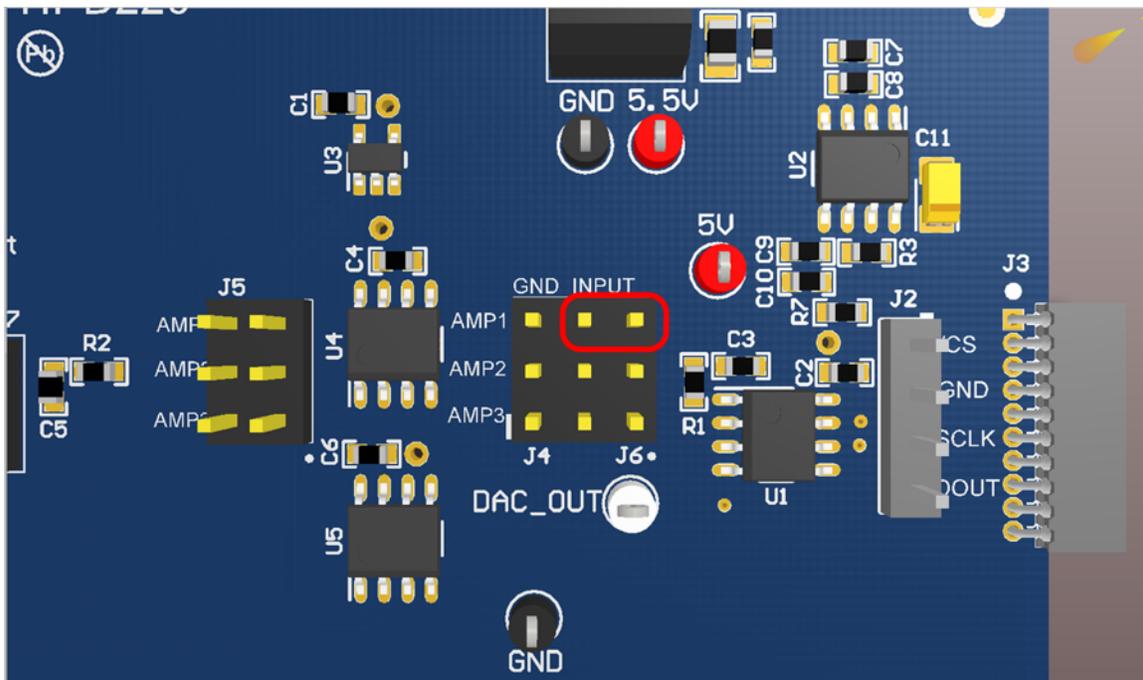


Figure 20. Header Connector for Connecting Amplifier's Input to DAC Output

Figure 21 shows the position the jumper has to be to ground AMP1 and AMP3.

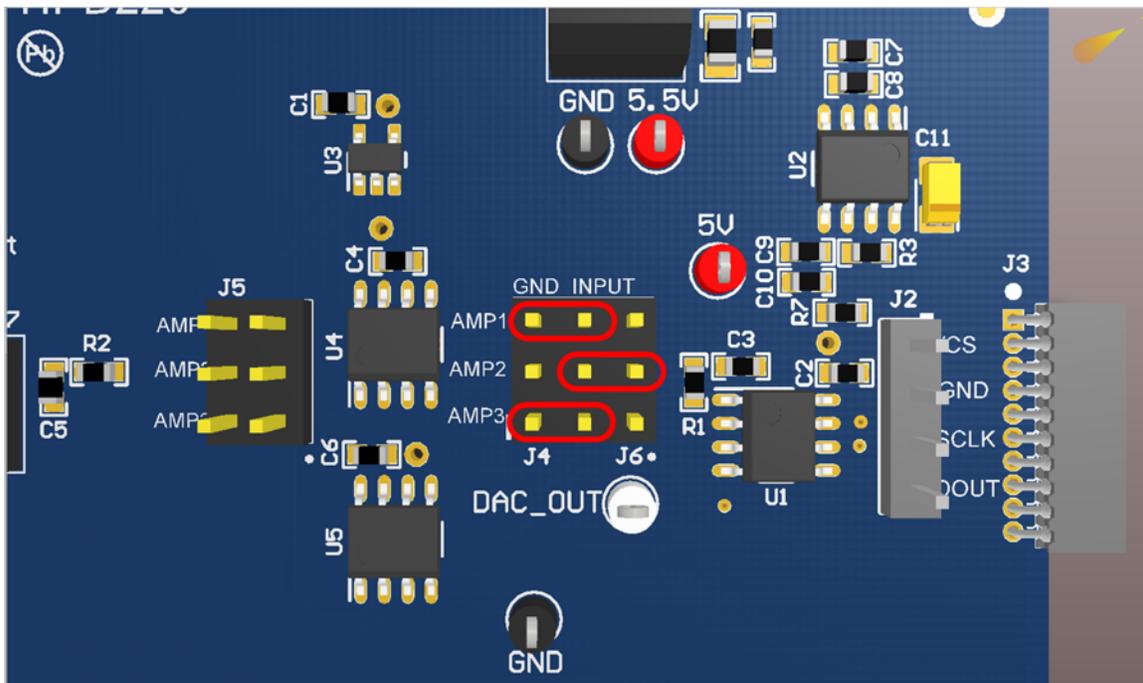


Figure 21. Jumper Position to Ground AMP1 and AMP3 Input and Connect AMP2 to DAC8830

Connector J5 is a jumper header. This header will connect the output of the op amp to connector J7 for measurement probing. As shown in Figure 22, one jumper is only need to connect the amplifier of interest; the other two amplifiers must be left open (no jumper).

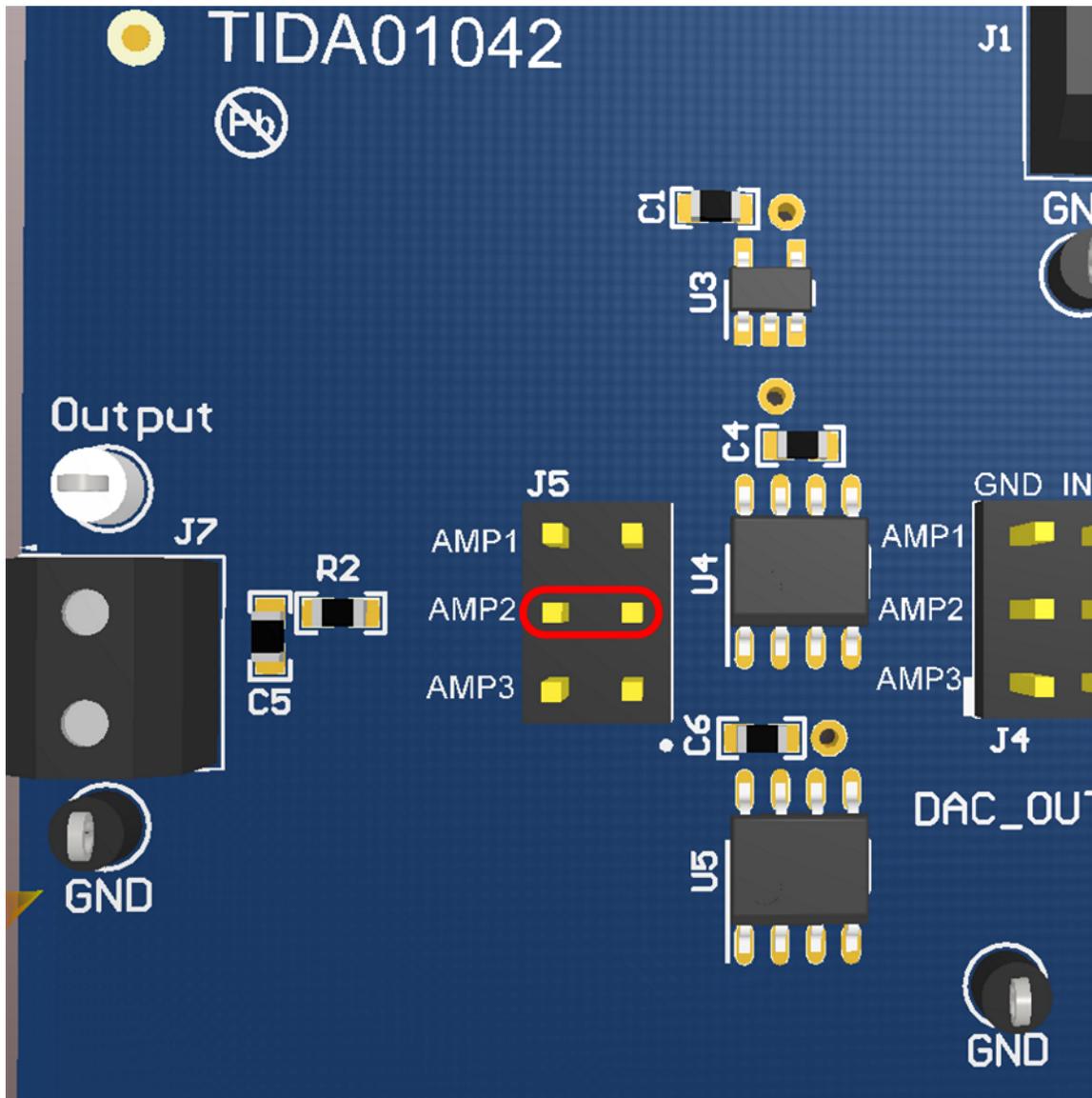


Figure 22. Header Connector J5 Connection to Terminal Block J7

3 Testing and Results

This TI Design linearity test was performed using an Analogic AN3200 DC Voltage Calibrator, an Agilent 3458A digital multimeter, NI USB-8452, and a PC running the LabVIEW™ software. The board was tested for all codes of the device and was allowed to settle for 1ms before the meter is read. This process is repeated for all codes to generate the measurements for INL results for different op amp buffered outputs. The results of the DAC INL characterization test is shown in Figure 27 as well as an output buffer comparison between the OPA388 and OPA340 in Figure 28.

3.1 Test Setup

The TI Design INL test was performed using an Analogic AN3200 DC Voltage Calibrator shown in Figure 23, which provided 5.5 V of power to the board.



Figure 23. Analogic AN3200 DC Voltage Calibrator

The Agilent 3458A digital multimeter shown in Figure 24 is connected to the output to measure the voltage associated with the binary value sent to the DAC.



Figure 24. Agilent 3458A digital multimeter

The NI USB-8452 is an interface used for connecting to the TI Design board and communicate through SPI.



Figure 25. NI USB-8452 Interface Board

The PC running the LabVIEW software to increment the code and collect the measured data. [Figure 26](#) shows the overall test setup for measuring INL.

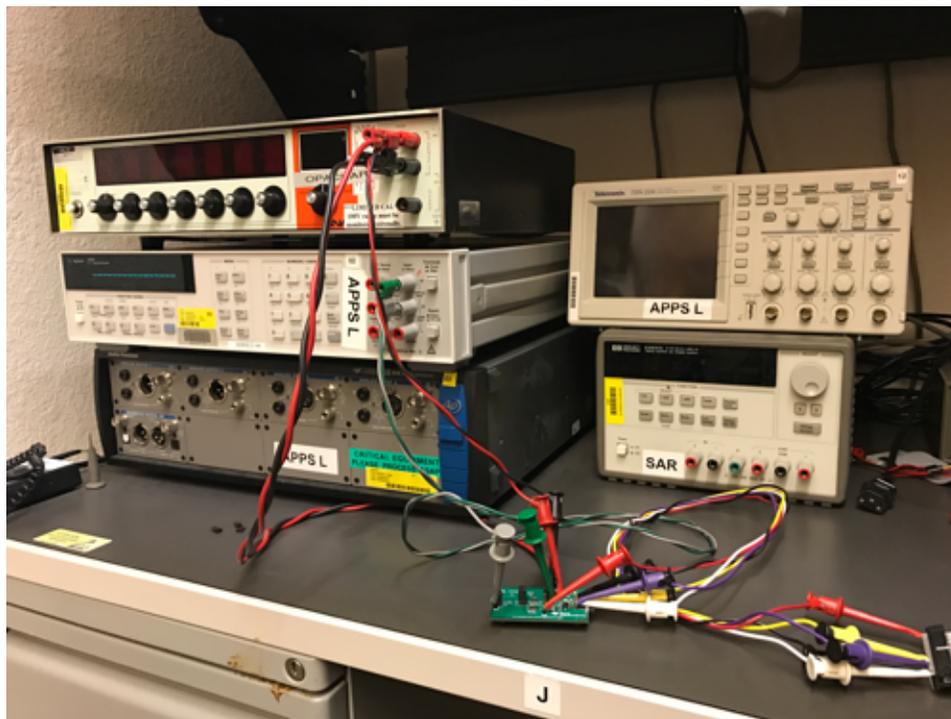


Figure 26. Test Setup for Measuring INL

3.2 Test Results

The results of the DAC INL characterization test is shown in Figure 27 as well as an output buffer comparison between the OPA388 and OPA340 in Figure 28.

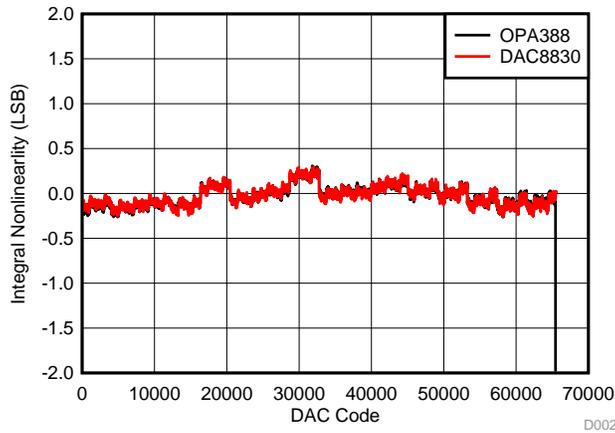


Figure 27. INL Measurement of DAC8830 Only versus OPA388

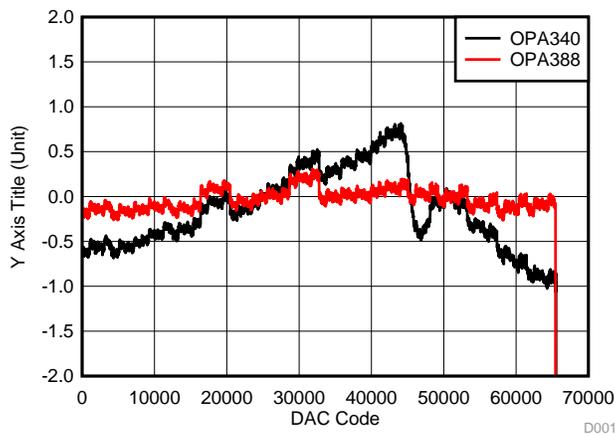


Figure 28. INL Measurement of OPA388 versus OPA340

These results show that a zero-crossover device such as the OPA388 shows almost no deviation from the DAC INL. This means the OPA388 minimally effects the linearity of the DAC. On the other hand, the OPA340 shows a major shift of greater than 1 LSB in the INL within the op amp's crossover region.

4 Design Files

4.1 Schematics

To download the schematics, see the design files at [TIDA-01402](#).

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01402](#).

4.3 PCB Layout Recommendations

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01402](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01402](#).

4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01402](#).

4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01402](#).

5 Related Documentation

1. Texas Instruments, [Zero-crossover Amplifiers: Features and Benefits](#), Zero-crossover Technote (SBOA181)
2. Texas Instruments, [Zero-drift Amplifiers: Features and Benefits](#), Zero-drift Technote (SBOA182)

5.1 Trademarks

TINA-TI is a trademark of Texas Instruments.

LabVIEW is a trademark of ni.

All other trademarks are the property of their respective owners.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated