

TI Designs: TIDA-01412

Power Supply Reference Design for Automotive Microcontroller in Gateway and Body Control Module



Description

This discrete power supply reference design demonstrates a complete power solution for the Freescale™ MPC5748G Microcontroller. This simple solution uses only five DC/DC converters and offers a more flexible, scalable, and cost-effective solution than a power management integrated circuit (PMIC). This design supports numerous automotive applications, such as gateway and central body control modules.

Resources

TIDA-01412	Design Folder
TPS6213013A-Q1	Product Folder
TPS62130A-Q1	Product Folder
TPS62133A-Q1	Product Folder
LM53603-Q1	Product Folder
TPS40210-Q1	Product Folder

Features



- Supports 2.7-V to 16-V, 32-V Peak Input Voltage
- Flexibility in Terms of Load and Scalability for Future Generations of Microcontrollers
- Less Than 1% Accuracy on LV Core Supply of MCU
- Efficiency Up to 80%
- Requires Only Five DC/DCs for Cost-Effective and Simple Power Solution
- AEC-Q100 Qualified

Applications

- [Body Control Module \(BCM\)](#)
- [Automotive Gateway](#)



[ASK Our E2E Experts](#)

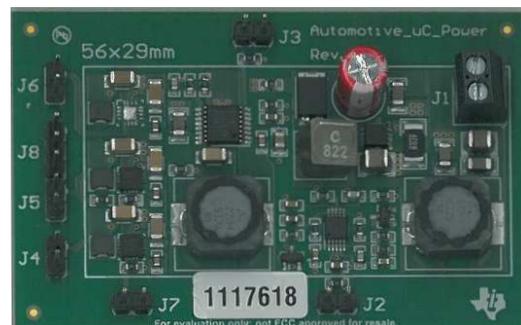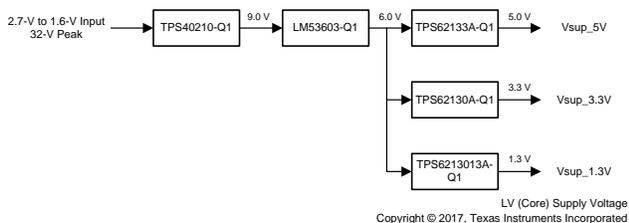

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 System Description

The MPC5748G Microcontroller (MCU) is used in a wide variety of automotive applications, such as high-end gateway, combined body controller and gateway, central body, vehicle body controllers, smart junction box, and front module applications. These applications require a small, highly-efficient power supply. Compared to a PMIC solution, this power solution is more flexible in terms of load requirements for different end applications. Additionally, it has the advantage of being easily scalable to future generations of the MCU. The MPC5748G device has multiple supply pins for the core, input and output (I/O), flash, and analog supplies. This reference design provides a power solution to supply all of these components in different power configurations of the MCU. The design has three output rails: 1.3 V ($V_{sup_1.3V}$), 5 V (V_{sup_5V}), and 3.3 V ($V_{sup_3.3V}$).

- $V_{sup_1.3V}$ is used to supply the core logic (V_{DD_LV}).
- V_{sup_5V} can be used to supply the I/O pins ($V_{DD_HV_A}$, $V_{DD_HV_B}$, and $V_{DD_HV_C}$) and analog pins ($V_{DD_HV_ADC0}$, $V_{DD_HV_ADC1}$, and $V_{DD_HV_ADC1_REF}$), which are also called analog-to-digital converter (ADC) pins depending on the power configuration of the MCU.
- $V_{sup_3.3V}$ can be used to supply the I/O pins ($V_{DD_HV_A}$, $V_{DD_HV_B}$, and $V_{DD_HV_C}$), the flash ($V_{DD_HV_FLA}$), and analog pins ($V_{DD_HV_ADC0}$, $V_{DD_HV_ADC1}$, $V_{DD_HV_ADC1_REF}$, and $V_{IN1_CMP_REF}$), depending on the power configuration of the MCU.

For more details on how to choose the power configuration for each pin, see [MPC5748G Data Sheet](#) and [MPC5748G Hardware Design Guidelines](#).

This reference design provides a tested and documented power solution that is suitable for the MPC5748G MCU. The solution achieves high efficiency by using integrated DC/DC converters and no low dropout (LDO) linear regulators. High efficiency results in a low self-temperature rise and higher reliability.

1.1 Key System Specifications

Table 1. Key System Specifications

PARAMETERS		SPECIFICATIONS	DETAILS
Input voltage range		2.7-V to 16-V, 32-V peak input voltage	—
OUTPUTS PROVIDED			
V_{sup_5V}	Voltage setpoint	5.0 V	Section 4.1
	Ripple	< 25 mV	
	Transient response	< 3%	
	Load regulation	< 1.5%	
$V_{sup_3.3V}$	Voltage setpoint	3.3 V	Section 4.2
	Ripple	< 25 mV	
	Transient response	< 3%	
	Load regulation	< 1.5%	
$V_{sup_1.3V}$	Voltage setpoint	1.3 V	Section 4.3
	Ripple	< 20 mV	
	Transient response	< 3%	
	Load regulation	< 1 %	

MPC5748G power requirements:

- $V_{DD_HV_ADC0}$: 3.3-V / 5.0-V ADC supply voltage
- $V_{DD_HV_ADC1}$: 3.3-V / 5.0-V ADC supply voltage
- $V_{DD_HV_ADC1_REF}$: 3.3-V / 5.0-V ADC1 high reference voltage
- $V_{DD_HV_A}$: 3.3-V / 5.0-V input/output supply voltage
- $V_{DD_HV_B}$: 3.3-V / 5.0-V input/output supply voltage
- $V_{DD_HV_C}$: 3.3-V / 5.0-V input/output supply voltage
- $V_{DD_HV_FLA}$: 3.3-V flash supply voltage (generated internally)
- V_{DD_LV} : 1.3-V internal core supply voltage

The I/O and HV ADCx supply voltages can be either in the 5-V range or in the 3.3-V range. When operating in the 3.3-V range, the HV flash supply voltage ($V_{DD_HV_FLA}$) must be externally supplied using a 3.3-V source. The 3.3-V flash supply is internally generated when the device operates in the 5-V range. The I/O voltages are all independent supplies that can be set to 3.3 V or 5 V. The core supply voltage (V_{DD_LV}) is set to a fixed voltage of 1.3 V. For more details, see [MPC5748G Data Sheet](#).

2 System Overview

2.1 Block Diagram

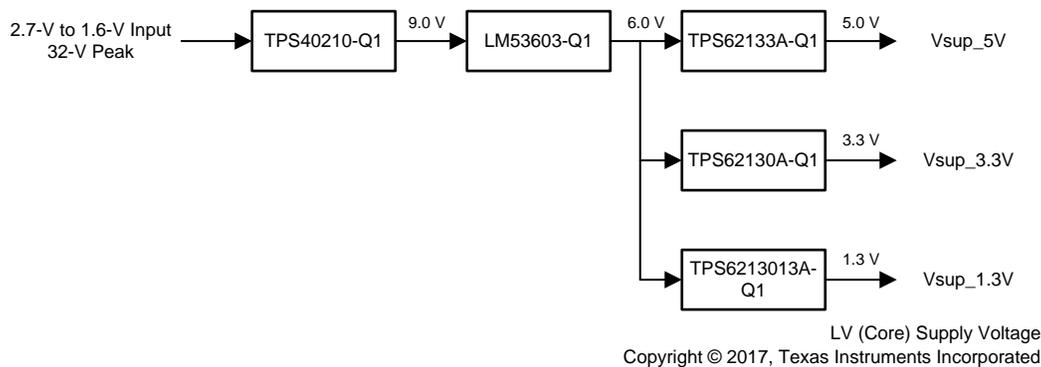


Figure 1. Block Diagram

2.2 Highlighted Products

2.2.1 TPS6213XA-Q1

The [TPS6213XA-Q1](#) devices are easy-to-use, synchronous, step-down DC/DC converters optimized for applications with high power density. A high switching frequency of typically 2.5 MHz allows the use of small inductors and provides fast transient response, as well as high output-voltage accuracy through the use of the DCS-Control™ topology (Direct Control with Seamless Transition into Power Save Mode). With a wide operating input-voltage range of 3 V to 17 V, the devices are ideally suited for systems that draw power from intermediate bus power rails. The devices support up to a 3-A continuous output current at output voltages between 0.9 V and 6 V (with 100% duty cycle mode). The output-voltage start-up ramp is controlled by the soft-start pin, which allows operation as either a standalone power supply or in tracking configurations. Power sequencing is also possible by configuring the enable and open-drain power-good pins. In power save mode, the devices show quiescent current of approximately 17 μ A from V_{IN} . Power save mode, which is entered automatically and seamlessly if the load is small, maintains high efficiency over the entire load range. In shutdown mode, the devices are turned off and shutdown current consumption is less than 2 μ A. The devices are packaged in a 16-pin VQFN package measuring 3 mm \times 3 mm.

The TPS6213013A-Q1 has a higher precision and provides a precise supply to the core rail of the MCU.

Table 2. Device Comparison Table

PART NUMBER	OUTPUT VOLTAGE	PACKAGE MARKING
TPS62130A-Q1	Adjustable	PA6IQ
TPS62133A-Q1	5 V	PA6JQ
TPS6213013A-Q1	1.3 V	13013Q

2.2.2 TPS40210-Q1

The [TPS40210-Q1](#) is a wide-input voltage (4.5 V to 52 V), nonsynchronous boost controller. This controller is suitable for topologies that require a grounded source N-channel field-effect transistor (FET) including boost, flyback, single-ended primary-inductor converter (SEPIC), and various light-emitting-diode (LED) driver applications. The device features include programmable soft-start, overcurrent protection with automatic retry, and programmable oscillator frequency. Current mode control provides improved transient response and simplified loop compensation.

2.2.3 LM53603-Q1

The [LM53603-Q1](#) buck regulator is specifically designed for automotive applications, providing an output voltage of 5 V or 3.3 V (with ADJ option) at 3 A or 2 A, from an input voltage of up to 36 V. Advanced high-speed circuitry allows the device to regulate from an input of up to 20 V, while providing an output of 5 V at a switching frequency of 2.1 MHz. The innovative architecture allows the device to regulate a 3.3-V output from an input voltage of only 3.5 V. All aspects of this product are optimized for the automotive customer. An input voltage range up to 36 V, with transient tolerance up to 42 V, eases input surge protection design. An open-drain reset output, with filtering and delay, provides an accurate indication of system status. This feature negates the requirement for an additional supervisory component, saving cost and board space. Seamless transition between PWM and PFM modes, along with a no-load operating current of only 24 μ A, ensures high efficiency and superior transient response at all loads.

2.3 System Design Theory

The power requirements of the microcontroller are a function of the specific functionality used in a given application. In most cases, the current drawn and the accuracy needed by each rail is not known precisely during the design phase. Only gross estimates are available when the power supply is designed.

Therefore the TIDA-01412 reference design uses DC/DC converters to provide flexibility to the designer and scalability for future generations of the microcontroller. Additionally, this design has the advantage of providing high-precision voltage rails compared to the PMIC solution.

This reference design uses five DC/DC converters and provides three output rails to generate appropriate supply voltages for the MCU. Because of the large input range from 2.7 to 16 V, the TPS40210-Q1 was chosen to get a constant voltage of 9 V. The TPS40210-Q1 is capable of a wide input operating voltage range, and is qualified for automotive applications. The voltage is further decreased with a synchronous 2.1-MHz step down converter (LM53603-Q1) to 6 V. The TPS6213x-Q1 step down converters are then used to obtain the suitable I/O and high-voltage (HV) ADC supply voltage of 5 V or 3.3 V and the core supply voltage of 1.3 V. Due to the high switching frequency of the TPS6213x, small inductors can be used and the design can be kept small and efficient. In this design, the TPS6213x-Q1 DC/DC converter provides a precise output regulation; the TPS6213013A-Q1 provides an output load regulation accuracy less than 1% for the low-voltage (LV) core supply.

3 Getting Started Hardware

To test this reference design, apply an input voltage between 2.7 V and 16 V to the J1 input connector. Then, set the enable pins of connector J8 to ON by using a jumper. All DC/DC converters will start working; check the expected output-voltages at the appropriate connectors. J4 should provide a 5-V output, J5 the 3.3-V output, and J6 the 1.3-V output-voltage. To test the design sufficiently, apply certain loads to observe the behavior of the output voltage.

4 Testing and Results

This section includes the relevant test results to power the MPC5748G MCU. Unless otherwise noted, all testing was conducted at room temperature with 14 V for V_{IN} simulating the main supply from the car battery.

Conducted tests:

- Efficiency
- Load regulation
- Load transient
- Output ripple

4.1 V_{sup_5V}

Measurements were performed on the 5-V rail (J4). A load of 300 mA was continuously applied at J6 ($V_{sup_1.3V}$) to measure a real case behavior of the circuit. Table 3 lists the test conditions.

Table 3. Test Conditions

VOLTAGE RAIL	OUTPUT VOLTAGE	LOAD
V_{sup_5V}	5 V	—
$V_{sup_3.3V}$	3.3 V	0 mA
$V_{sup_1.3V}$	1.3 V	300 mA

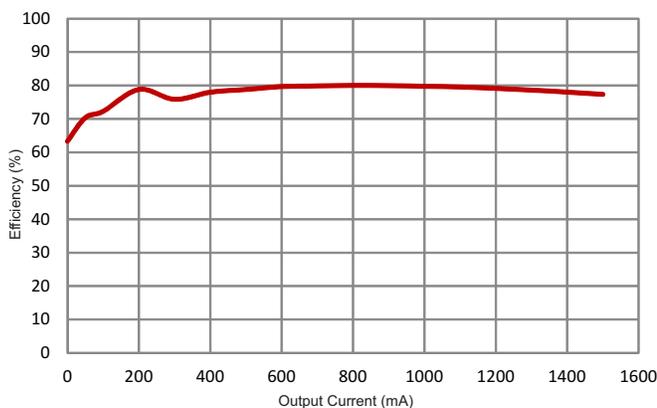


Figure 2. V_{sup_5V} Efficiency (14 V_{IN} , Measured at J4)

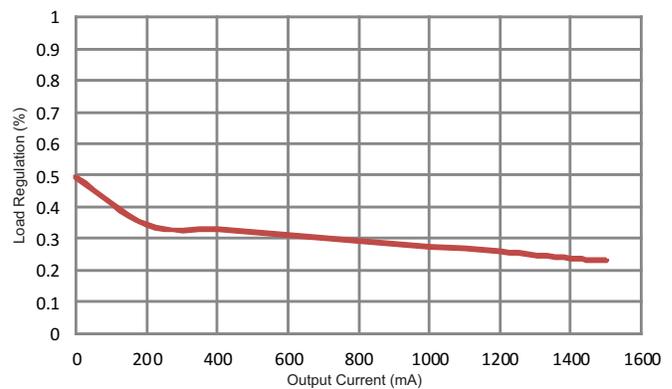


Figure 3. V_{sup_5V} Load Regulation (14 V_{IN} , Measured at J4)

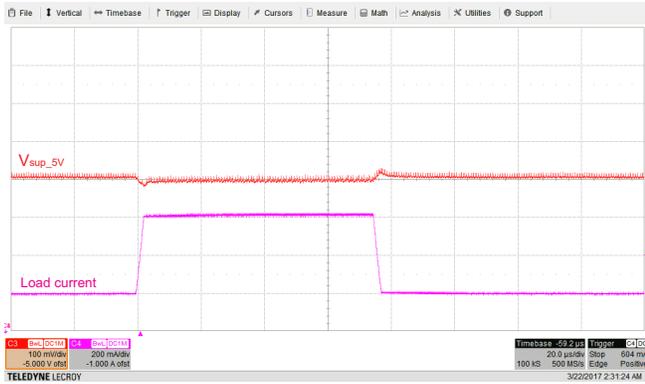


Figure 4. V_{sup_5V} Transient Response ($14 V_{IN}$, 400-mA to 800-mA Load Step, Measured at J4)

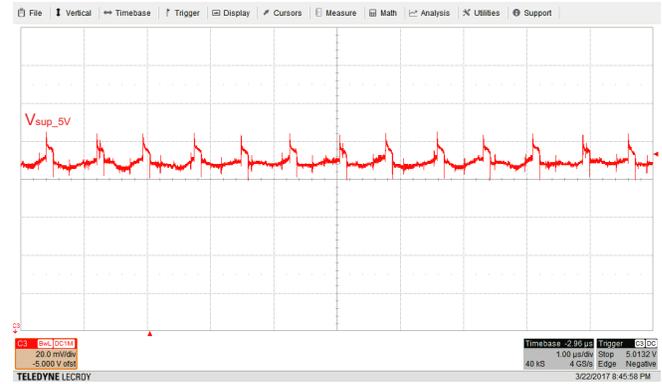


Figure 5. V_{sup_5V} Ripple ($14 V_{IN}$, 500-mA load at V_{sup_5V} , 300-mA load at $V_{sup_1.3V}$, Measured at J4)

4.2 $V_{sup_3.3V}$

The same measurements were performed on the 3.3-V rail (J5). A load of 300 mA was continuously applied at J6 ($V_{sup_1.3V}$) to measure a real case behavior of the circuit.

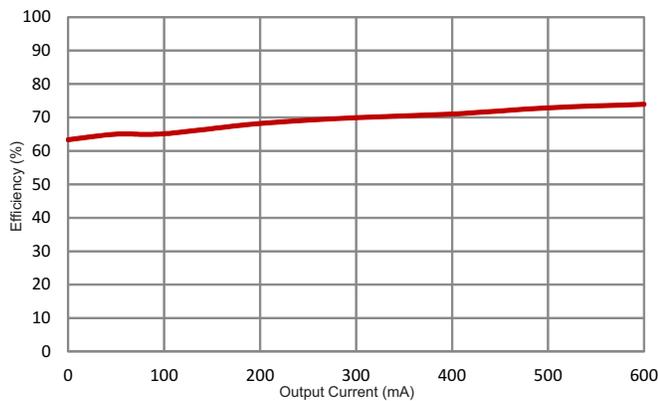


Figure 6. $V_{sup_3.3V}$ Efficiency ($14 V_{IN}$, Measured at J5)

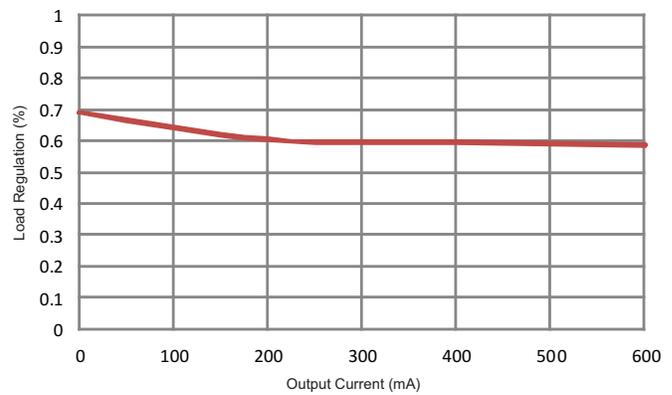


Figure 7. $V_{sup_3.3V}$ Load Regulation ($14 V_{IN}$, Measured at J5)

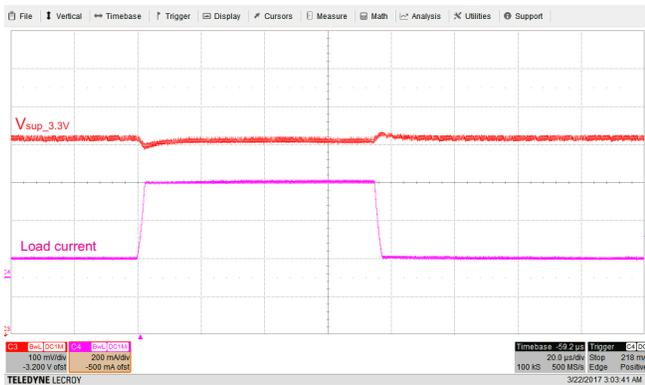


Figure 8. $V_{sup_3.3V}$ Transient Response ($14 V_{IN}$, 100-mA to 500-mA Load Step, Measured at J5)

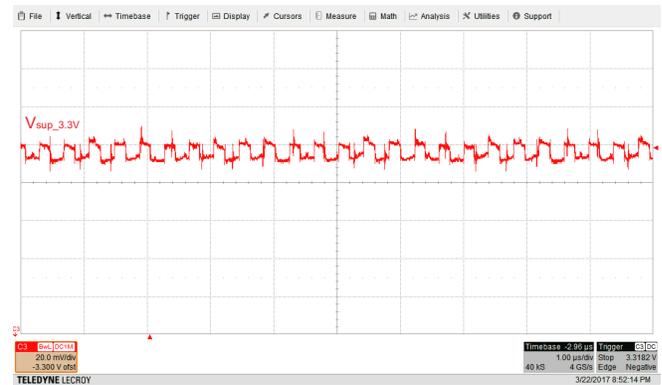


Figure 9. $V_{sup_3.3V}$ Ripple ($14 V_{IN}$, 500-mA load on $V_{sup_3.3V}$, 300-mA load on $V_{sup_1.3V}$, Measured at J5)

4.3 $V_{sup_1.3V}$

The same measurements were performed for the 1.3-V rail (J6). A load of 500 mA was continuously applied at J5 ($V_{sup_3.3V}$) to measure a real case behavior of the circuit.

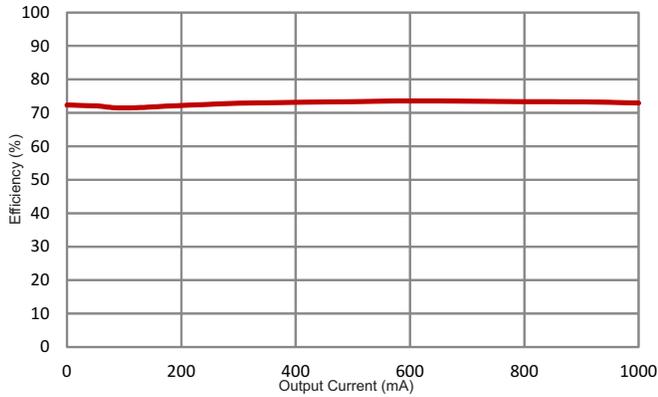


Figure 10. $V_{sup_1.3V}$ Efficiency (14 V_{IN} , Measured at J6)

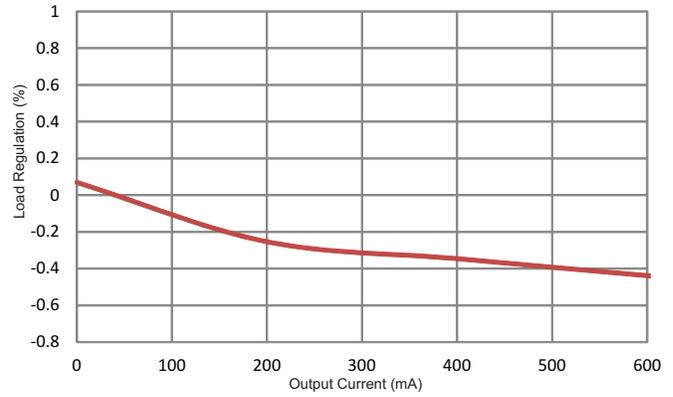


Figure 11. $V_{sup_1.3V}$ Load Regulation (14 V_{IN} , Measured at J6)



Figure 12. $V_{sup_1.3V}$ Transient Response (14 V_{IN} , 400- to 800-mA Load Step, Measured at J6)

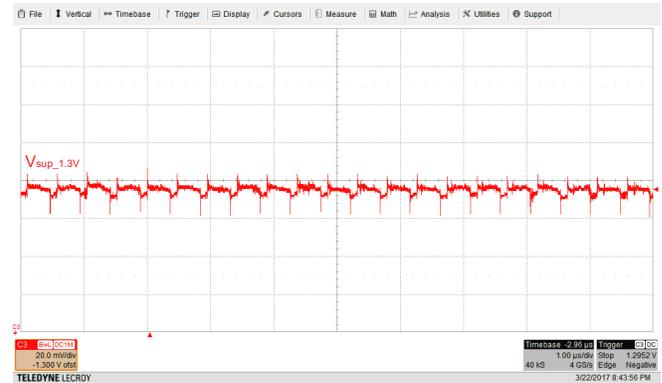


Figure 13. $V_{sup_1.3V}$ Ripple (14 V_{IN} , 500-mA load on $V_{sup_1.3V}$, 500-mA load on V_{sup_5V} , Measured at J6)

5 Design Files

5.1 Schematics

To download the schematics, see the design files at [TIDA-01412](#).

5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01412](#).

5.3 PCB Layout Recommendations

5.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01412](#).

5.4 Gerber Files

To download the Gerber files, see the design files at [TIDA-01412](#).

5.5 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01412](#).

6 Related Documentation

1. Texas Instruments, [TPS6213xA-Q1 3-V to 17-V 3-A Step-Down Converter with DCS-Control™](#)
2. Texas Instruments, [TPS4021x-Q1 4.5-V to 52-V Input, Current-Mode Boost Controllers](#)
3. Texas Instruments, [LM53603-Q1 \(3 A\), LM53602-Q1 \(2 A\) 3.5 V to 36 V Wide-V_{IN} Synchronous 2.1 MHz Step- Down Converters for Automotive Applications](#)
4. NXP Semiconductors, [MPC5748G One Pager](#)
5. NXP Semiconductors, [MPC5748G Data Sheet](#)
6. NXP Semiconductors, [MPC5748G Hardware Design Guidelines](#)

6.1 Trademarks

DCS-Control is a trademark of Texas Instruments.
Freescale is a trademark of Freescale Semiconductor, Inc..
All other trademarks are the property of their respective owners.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated