

## TI Designs: TIDA-01418

# Reference Design for Automotive High-Voltage, High-Power Motor Drive for HVAC A/C Compressor



### Description

This brushless DC (BLDC) motor design offers a solution for controlling an automotive HVAC A/C compressor by using the UCC27712-Q1 high- and low-side gate driver followed by discrete insulated-gate bipolar transistor (IGBT) half bridges. This reference design uses TI's C2000 Piccolo F2805x microcontroller and the InstaSPIN™-FOC sensorless motor control solution. This solution enables identification of motor parameters, automatic tuning of the current loop, and high-performance sensorless operation including start-up under heavy load and ultra-low speed control. InstaSPIN is leveraged in this TI design to increase the dynamic range of the compressor so that the compressor can run at lower speed (500 rpm) at full torque. This means EV battery savings when the HVAC is running. Designers can enable InstaSPIN using special libraries in the read-only memory (ROM) of Piccolo™ microcontrollers (MCUs) and provides expert tools to designers of sensorless (velocity and torque) motor control applications.

### Resources

<a href="#">TIDA-01418</a>	Design Folder
<a href="#">UCC27712-Q1</a>	Product Folder
<a href="#">LM5160-Q1</a>	Product Folder
<a href="#">TPS7B6733-Q1</a>	Product Folder
<a href="#">TPS7B6750-Q1</a>	Product Folder
<a href="#">TCAN1042HGV-Q1</a>	Product Folder
<a href="#">ISO7733-Q1</a>	Product Folder
<a href="#">TMS320F28052F</a>	Product Folder
<a href="#">SN74LVC2G74-Q1</a>	Product Folder
<a href="#">SN74LVC541A-Q1</a>	Product Folder
<a href="#">LMT87-Q1</a>	Product Folder
<a href="#">OPA365-Q1</a>	Product Folder
<a href="#">TLV314-Q1</a>	Product Folder
<a href="#">LMV393-Q1</a>	Product Folder

### Features


- Low-Voltage Side Survives Voltages up to 45 V, Withstands Reverse Battery Conditions, and Withstands Load Dump Conditions (12-V System)
- Incorporates Protection Against Overcurrent and False Turnon Using
  - Active Miller Clamp
  - Overcurrent Detecting Circuit
- Isolated CAN-Communication Interface
- Non-Isolated, Low-Cost, High- and Low-Side Gate Drivers With 2.5-A Peak Output
- Isolated Power Supply
- Compact Layout
- Components Selected for Automotive Temperature and Quality
- InstaSPIN, Sensorless Torque Control Algorithm

### Applications

- [Automotive HVAC Compressor HEV/EV](#)



[ASK Our E2E™ Experts](#)

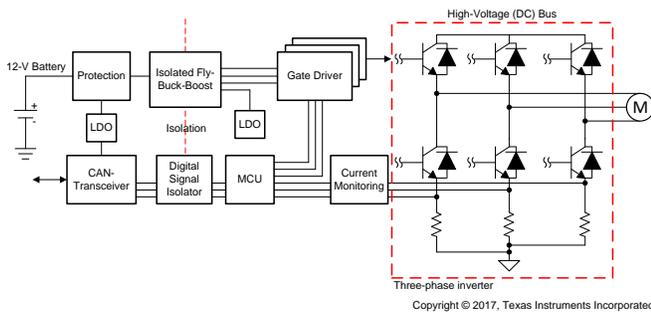

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 1 System Description

One of the core features of hybrid electric vehicles (HEVs) is the idle-stop or stop-start system. When an HEV vehicle starts to idle at a traffic light, the system shuts down the engine. This shutdown indicates that no power is available to drive the A/C compressor. To solve this issue, most hybrid and all electric vehicles (EVs) have an electric drive for the compressor. An electric motor is built in the compressor and is driven by an inverter, which the high-voltage battery of the vehicle supplies. The IGBTs in the inverter carry high currents, which is why such applications typically use a lot of isolated components (gate driver, analog-to-digital converter (ADC)) that add delay in the switching circuit and make the solution more expensive. Another cost factor is the rotation detection of the motor, which the designer can accomplish within some circuits by implementing a resolver or through the use of a couple of Hall sensors.

The TIDA-01418 is a three-phase inverter drive which is based on a discrete IGBT for driving brushless DC (BLDC) motors in automotive A/C compressors using sensorless torque control.

The TIDA-01418 system consists of an:

- Isolated power supply
- Isolated communication interface (CAN)
- Non-isolated IGBT gate driver circuit
- Non-isolated current monitoring and overcurrent detecting circuit
- TMS320F28052 microcontroller

The main goal when creating this reference design was to reduce the number of isolated components, add a few safety features in the hardware (overcurrent detection), and maintain a small and compact design.

### 1.1 Key System Specifications

Table 1. Key System Specifications

PARAMETER	SPECIFICATIONS	
DC bus input voltage	Max 450 V	
Supply voltage (12-V battery)	6.5 V to 18 V	
Gate driver supply voltage	16 V	
Rated power capacity	4 kW (max load current 12 A)	
Non-isolated IGBT gate driver	Supply voltage	10 V to 20 V
	Current sink and source	2.5 A/1.75 A
	Turnon propagation delay	100 ns to 160 ns
	Turnoff propagation delay	100 ns to 160 ns

**Table 1. Key System Specifications (continued)**

PARAMETER	SPECIFICATIONS	
Controller	TMS320F28052	
Digital signal isolation	ISO7731 reinforced	
Power supply specification for MCU and digital logic	3.3 V $\pm$ 2%	
Feedbacks	DC bus voltage, IGBT temperature, motor phase voltage, and motor phase current	
Protections	12-V battery side	Reverse polarity
		Transient voltage
		ESD
	High-voltage side	DC bus undervoltage and overvoltage <sup>(1)</sup>
		Overcurrent <sup>(2)</sup>
		Overtemperature (IGBT) <sup>(3)</sup>

<sup>(1)</sup> Software protection


<sup>(2)</sup> Hardware circuit (overcurrent protection) also realized in software

<sup>(3)</sup> Software protection

## 2 System Overview
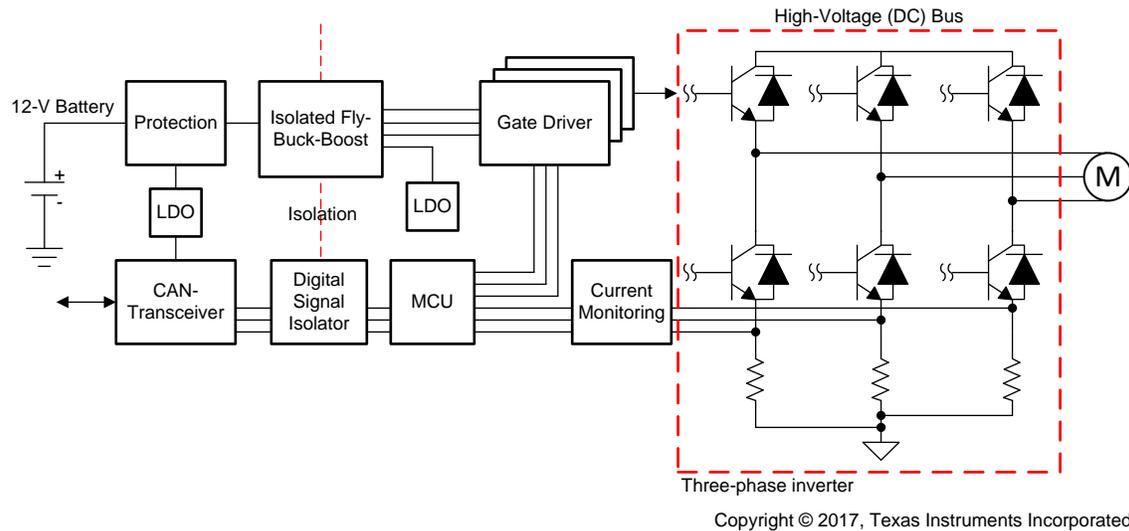
### 2.1 Block Diagram

AC compressors typically use three-phase BLDC motors that are built in the compressor, driven by an inverter, and supplied by the high-voltage battery of the vehicle. Figure 1 shows the block diagram of the three-phase inverter with an isolated power supply and isolated interface between the MCU and CAN transceiver.



Copyright © 2017, Texas Instruments Incorporated

**Figure 1. TIDA-01418 Block Diagram**

The whole system is represented in ten blocks:

- Low-voltage side (12-V battery)
  - Protection: Protects circuit against reverse battery and load dump condition
  - Low dropout regulator (LDO): Supplies the CAN transceiver with 5 V
  - CAN transceiver: Communication interface
- High-voltage side
  - Microcontroller (MCU): TI's C2000™ family of MCUs with InstaSPIN algorithm controls the motor torque, performs all other calculations, and manages communication through the CAN transceiver
  - Current monitoring: Circuit monitors the current in each phase of the inverter and detects the overcurrent condition
  - IGBTs: Delivers the current for the three-phase motor
  - Gate drivers: Controlled by the MCU; each gate driver is capable of driving the gates of the high- and low-side IGBTs
  - LDO: Supplies the MCU and all other logic components on the "hot" side (high-voltage side)
- Isolation barrier
  - Isolated fly-buck-boost converter: Delivers supply voltage over isolation barrier to the gate driver and all other logic components
  - Digital signal isolator: Isolates the interface between the MCU and CAN transceiver

## 2.2 Highlighted Products

### 2.2.1 LM5160-Q1

The LM5160-Q1 is TI's synchronous Buck/Fly-Buck™ converter with a wide input voltage range. This device is capable of handling input voltages up to 65 V and has integrated high-side and low-side MOSFETs. An internal feedback amplifier maintains  $\pm 1\%$  output voltage regulation over the entire operating temperature range. The soft-start feature allows the converter to gradually reach a steady-state operation point, thereby reducing start-up stresses and current surges. The LM5160 contains a dual-level undervoltage lockout (EN/UVLO) circuit. When the EN/UVLO pin voltage is below 0.35 V, the regulator is in low-current shutdown mode. When the EN/UVLO pin voltage is greater than 0.35 V (typically) but less than 1.24 V (typically), the regulator is in standby mode. In standby mode, the  $V_{CC}$  bias regulator is active but the converter switching remains disabled. When the voltage at the VCC pin exceeds the  $V_{CC}$  rising threshold  $V_{CC}(UV) = 3.98$  V (typically) and the EN/UVLO pin voltage is greater than 1.24 V, normal switching operation begins. The designer can use an external resistor voltage divider from VIN to GND to set the minimum operating voltage of the regulator. Operate the LM5160 device such that the junction temperature does not exceed 150°C during normal operation. An internal thermal shutdown circuit has been provided to protect the LM5160 device in the event that the junction temperature rises higher than normal. When activated, typically at 175°C, the controller is forced into a low-power reset state, which disables the high-side buck switch and the  $V_{CC}$  regulator. This feature prevents failures from accidental device overheating. When the junction temperature falls below 155°C (typical hysteresis = 20°C), the  $V_{CC}$  regulator is enabled and operation resumes.

The main features of this device are as follows:

- Device temperature grade 1:  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  ambient operating temperature range
- Wide 4.5-V to 65-V input voltage range
- Integrated high- and low-side switches
  - No Schottky diode required
- 1.5-A maximum load current
- Programmable soft-start time
- Peak current limiting protection
- Adjustable input UVLO and hysteresis
- $\pm 1\%$  feedback voltage reference
- Thermal shutdown protection

### 2.2.2 TPS7B6750-Q1 and TPS7B6733-Q1

The TPS7B6750-Q1 and TPS7B6733-Q1 devices are LDOs designed for up to 40-V input voltage range operations. These devices have only 15- $\mu\text{A}$  quiescent current at a light load. The TPS7B750/33 drives loads up to 450 mA. In the TPS7B67xx-Q1 family of devices, the designer can implement the reset delay signal and power-good signal during power up to indicate that the output voltage is stable and is in regulation. An external capacitor programs the delay. By using the MCU I/O port, the designer can also control the enable function, which activates or deactivates the device.

The main features of these devices are as follows:

- Device temperature grade 1:  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  ambient operating temperature range
- 4-V to 40-V wide  $V_{IN}$  input-voltage range with up to 45-V transient
- Maximum output current: 450 mA
- Low quiescent current ( $I_Q$ ): 15  $\mu\text{A}$  typical at light loads
- Maximum dropout voltage: 450 mV at 400 mA
- Integrated fault protection:
  - Thermal shutdown
  - Short-circuit protection

### 2.2.3 TCAN1042-Q1

The TCAN1042-Q1 transceiver meets the ISO11898-2:2016 high-speed CAN physical layer standard. The device is designed for use in CAN FD networks up to 2 Mbps. This device has a low-power standby mode with a feature for remote wake-up request. Additionally, the TCAN1042-Q1 includes many protection features which enhance the network and device robustness.

The main features of this device are as follows:

- Meets the December 17th, 2015 draft of ISO11898-2 Physical Layer Update
- Junction temperatures from  $-55^{\circ}\text{C}$  to  $150^{\circ}\text{C}$
- Meets the released ISO 11898-2:2007 and ISO11898-2:2003 Physical Layer Standards
- I/O voltage range supports 3.3-V and 5-V MCUs
- Receiver common-mode input voltage:  $\pm 30\text{ V}$
- Typical loop delay: 110 ns
- Protection features
  - HBM ESD protection:  $\pm 16\text{ kV}$
  - IEC ESD protection up to  $\pm 15\text{ kV}$
  - Bus fault protection:  $\pm 58\text{ V}$  (non-H variants) and  $\pm 70\text{ V}$  (H variants)
  - Undervoltage protection on  $V_{\text{CC}}$  and VIO (V-variants only) supply terminals
  - Driver dominant time out (TXD DTO) – Data rates down to 10 kbps
  - Thermal shutdown protection (TSD)

### 2.2.4 ISO7731-Q1

The ISO7731-Q1 device is high-performance, triple-channel digital isolator with  $5000\text{ V}_{\text{RMS}}$  (DW package) and  $2500\text{ V}_{\text{RMS}}$  (DBQ package) isolation ratings per UL 1577. This device has reinforced insulation rating according to VDE, CSA, TUV, and CQC. The ISO7731-Q1 provides high electromagnetic immunity and low emissions at a low power consumption, while isolating CMOS or LVCMOS digital I/Os. Each isolation channel has a logic input and output buffer separated by a silicon dioxide ( $\text{SiO}_2$ ) insulation barrier. This device comes with enable pins which the designer can use to put the respective outputs in high impedance for multi-master driving applications and to reduce power consumption. The ISO7730-Q1 device has all three channels in the same direction and the ISO7731-Q1 device has two forward and one reverse-direction channel. If the input power or signal is lost, the default output is high for devices without suffix F and low for devices with suffix F. Used in conjunction with isolated power supplies, this device helps prevent noise currents on a data bus or other circuits from entering the local ground and interfering with or damaging sensitive circuitry.

The main features of this device are as follows:

- Device temperature grade 1:  $-40^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$  ambient operating temperature
- Signaling rate: Up to 100 Mbps
- Wide supply range: 2.25 V to 5.5 V
- 2.25-V to 5.5-V level translation
- Low-power consumption, typical 1.5 mA per channel at 1 Mbps
- Low propagation delay: 11 ns typical (5-V supplies)
- High common-mode transient immunity (CMTI):  $\pm 100\text{ kV}/\mu\text{s}$  typical
- Isolation barrier life: > 40 years
- Robust electromagnetic compatibility (EMC)
  - System-level electrostatic discharge (ESD), electrical fast transient (EFT), and surge immunity
  - Low emissions

### 2.2.5 TMS320F28052

The F2805x Piccolo™ family of MCUs provide the power of the C28x core and Control Law Accelerator (CLA) coupled with highly-integrated control peripherals in low pin-count devices.

An internal voltage regulator allows for single-rail operation. Analog comparators with internal 6-bit references can be routed directly to control the pulse-width modulation (PWM) outputs. The ADC converts from a 0-V to 3.3-V fixed full-scale range and supports ratio-metric VREFHI/VREFLO references.

The analog front end (AFE) contains up to seven comparators with up to three integrated digital-to-analog converters (DACs): one VREFOUT-buffered DAC, up to four programmable gain amplifiers (PGAs), and up to four digital filters. The PGAs can amplify the input signal in three discrete gain modes.

The TMS320F28052F includes the FAST™ software encoder and additional motor control functions required for cascaded speed and torque loops for efficient, three-phase, field-oriented motor control (FOC).

F28052F peripheral drivers in the user code enable a sensorless InstaSPIN-FOC™ solution which can identify, tune the torque controller, and efficiently control a motor in minutes, without the use of any mechanical rotor sensors. This entire package is called InstaSPIN-FOC. The FAST estimator is called from protected ROM, while the rest of the functions required for InstaSPIN-FOC reside in user memory (FLASH and RAM). InstaSPIN-FOC has been designed for flexibility to accommodate a range of system software architectures and customization.

The main features of this device are as follows:

- High-efficiency 32-Bit CPU (TMS320C28x)
- Three 32-Bit CPU timers
- Independent 16-bit timer in each ePWM module
- Serial port peripherals
  - Three serial communications interface (SCI)
  - Dual-zone security module (universal asynchronous receiver/transmitter (UART)) modules
  - One serial peripheral interface (SPI) module
  - One inter-integrated-circuit (I<sup>2</sup>C) bus
  - One enhanced controller area network (eCAN) bus
- Analog peripherals
  - One 12-bit ADC
  - One on-chip temperature sensor for oscillator compensation
  - Up to seven comparators with up to three integrated DACs
  - One buffered reference DAC
  - Up to four PGAs
  - Up to four digital filters

### 2.2.6 UCC27712-Q1

The UCC27712-Q1 is a 620-V high-side and low-side gate driver with 1.8-A source, 2.8-A sink current, which is targeted to drive power MOSFETs or IGBTs. The UCC27712-Q1 includes protection features where the outputs are held low when the inputs are left open or when the minimum input pulse width specification is not met. Interlock and dead time functions prevent both outputs from being turned on simultaneously. In addition, the device accepts a wide bias supply range from 10 V to 22 V and offers UVLO protection for both the VDD and HB bias supply. The device features a robust drive with excellent noise and transient immunity including large negative voltage tolerance on its inputs, high dV/dt tolerance, wide negative transient safe operating area (NTSOA) on the switch node (HS), and interlock. The device consists of one ground-referenced channel (LO) and one floating channel (HO), which is designed for operating with bootstrap or isolated power supplies. The device features fast propagation delays and excellent delay matching between both channels. On the UCC27712-Q1, each channel is controlled by its respective input pins, HI and LI.

The main features of this device are as follows:

- High-side and low-side configuration
- Dual inputs with output interlock and 150-ns dead time
- Fully operational up to 620 V, 700-V absolute maximum on HB pin
- 10-V to 20-V VDD recommended range
- Peak output current 2.8-A sink, 1.8-A source
- dV/dt immunity of 50 V/ns
- Small propagation delay (100 ns, typical)
- Delay matching (12-ns, max)
- Low quiescent current
- UVLO protection for both channels
- All parameters specified over temperature range,  $-40^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$

### 2.2.7 OPA365-Q1

The OPA365-Q1 zero-crossover, rail-to-rail, high-performance, CMOS operational amplifier is optimized for very-low-voltage, single-supply applications. Rail-to-rail input and output, low noise ( $4.5 \text{ nV}/\sqrt{\text{Hz}}$ ), and high-speed operation make this device ideal for sampling shunt voltages to detect overcurrent in a very short period of time, which can prevent damage to other components of the circuit.

The main features of this device are as follows:

- Device temperature grade 1:  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  ambient operating temperature range
- Gain bandwidth: 50 MHz
- Low noise:  $4.5 \text{ nV}/\sqrt{\text{Hz}}$  at 100 kHz
- Slew rate: 25 V/ $\mu\text{s}$
- Fast settling: 0.3  $\mu\text{s}$  to 0.01%
- Precision
  - Low offset: 100  $\mu\text{V}$
  - Low input bias current: 0.2 pA
- 2.2-V to 5.5-V operation

### 2.2.8 TLV314-Q1

The TLV314-Q1 represents a new generation of low-power, operational amplifier. Rail-to-rail input and output swings (RRIO) and low quiescent current (150  $\mu$ A typically at 5 V) combine with a wide bandwidth of 3 MHz to make this device very attractive for a variety of battery-powered applications that require a good balance between cost and performance. The TLV314-Q1 achieves a low-input bias current of 1 pA.

The TLV314-Q1 incorporates: high unity gain stability, RRIO, capacitive loads of up to 300 pF, an integrated radio frequency (RF) and electromagnetic interference (EMI) rejection filter, no phase reversal in overdrive conditions, and high electrostatic discharge (ESD) protection (4-kV human-body model (HBM)).

The main features of this device are as follows:

- Device temperature grade 1:  $-40^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$  ambient operating temperature range
- Low input bias current: 1 pA (typical)
- Rail-to-rail input and output
- Gain bandwidth: 3 MHz
- Low  $I_Q$ : 250  $\mu\text{A}/\text{Ch}$  (maximum)
- Low noise: 16  $\text{nV}/\sqrt{\text{Hz}}$  at 1 kHz
- Internal RF and EMI filter

### 2.2.9 LMV393-Q1

The LMV393-Q1 device is a low-voltage (2.7-V to 5.5-V) comparator, which operates from 5 V to 30 V.

The LMV393-Q1 is the most cost-effective solution for applications where low-voltage operation, low power, space saving, and price are the primary specifications in circuit design.

The main features of this device are as follows:

- 2.7-V and 5-V performance
- Low supply current (100  $\mu\text{A}$  typical)
- Input common-mode voltage range includes ground
- Low output saturation voltage: 200 mV typical
- Open-collector output for maximum flexibility

### 2.2.10 SN74LVC2G74-Q1

This single, positive-edge-triggered, D-type flip-flop is designed for 1.65-V to 5.5-V  $V_{CC}$  operation.

A low level at the preset (PRE) or clear (CLR) input sets or resets the outputs, regardless of the levels of the other inputs. When PRE and CLR are inactive (high), data at the data (D) input that meets the setup time requirements is transferred to the outputs on the positive-going edge of the clock pulse. Clock triggering occurs at a voltage level and is not related directly to the rise time of the clock pulse. Following the hold-time interval, data at the D input can be changed without affecting the levels at the outputs.

The main features of this device are as follows:

- Supports 5-V  $V_{CC}$  operation
- Inputs accept voltages to 5.5 V
- Low power consumption, 10-mA max  $I_{CC}$
- $\pm 24$ -mA output drive at 3.3 V
- Typical  $V_{OLP}$  (output ground bounce)  $< 0.8$  V at  $V_{CC} = 3.3$  V,  $T_A = 25^{\circ}\text{C}$
- Typical  $V_{OHV}$  (output  $V_{OH}$  undershoot)  $> 2$  V at  $V_{CC} = 3.3$  V,  $T_A = 25^{\circ}\text{C}$
- $I_{OFF}$  supports partial-power-down mode operation
- Latch-up performance exceeds 100 mA per JESD 78, Class II

### 2.2.11 SN74LVC541A-Q1

The SN74LVC541A octal buffer/driver is designed for 2.7-V to 3.6-V  $V_{CC}$  operation. The device is ideal for driving bus lines. This device features inputs and outputs on opposite sides of the package to facilitate printed-circuit board (PCB) layout. The three-state control gate is a two-input AND gate with active-low inputs so that if either output enable input is high (OE1 or OE2), all eight outputs are in the high-impedance state. Drive the inputs from either 3.3-V or 5-V devices. This feature allows the use of this device as a translator in a mixed 3.3-V or 5-V system environment. This device is fully specified for partial-power-down applications using  $I_{OFF}$ . The  $I_{OFF}$  circuitry disables the outputs, which prevents damaging current backflow through the device during power down.

The main features of this device are as follows:

- Operates from 2 V to 3.6 V
- Inputs accept voltages to 5.5 V
- Max  $t_{pd}$  of 5.1 ns at 3.3 V
- Typical  $V_{OLP}$  (output ground bounce) < 0.8 V at  $V_{CC} = 3.3$  V,  $T_A = 25^\circ\text{C}$
- Typical  $V_{OHV}$  (output  $V_{OH}$  undershoot) > 2 V at  $V_{CC} = 3.3$  V,  $T_A = 25^\circ\text{C}$
- Supports mixed-mode signal operation on all ports (5-V input and output voltage with 3.3-V  $V_{CC}$ )
- $I_{OFF}$  supports partial-power-down mode operation

### 2.2.12 LMT87-Q1


The LMT87-Q1 device is a precision CMOS integrated-circuit temperature sensor with an analog output voltage that is linearly and inversely to temperature. The LMT87-Q1 features make it suitable for many general temperature sensing-applications. The device can operate down to a 2.7-V supply with a 5.4- $\mu\text{A}$  power consumption. Package options, which include the through-hole TO-92 package, allow the designer to mount the LMT87-Q1 on the board, off the board, to a heat sink, or on multiple unique locations in the same application. A class-AB output structure gives the LMT87-Q1 a strong output source and a sink current capability that can directly drive up to 1.1-nF capacitive loads. This quality means the device is well suited to drive an ADC sample-and-hold with its transient load requirements. The LMT87-Q1 accuracy is specified in the operating range of  $-50^\circ\text{C}$  to  $150^\circ\text{C}$ . The accuracy, three-lead package options, and other features also make the LMT87-Q1 an alternative to thermistors.

The main features of this device are as follows:

- Very accurate:  $\pm 0.3^\circ\text{C}$  typical
- Wide temperature range of  $-50^\circ\text{C}$  to  $150^\circ\text{C}$
- Low 5.4- $\mu\text{A}$  quiescent current
- Sensor gain of  $-13.6$  mV/ $^\circ\text{C}$
- Output is short-circuit protected
- Push-pull output with 50- $\mu\text{A}$  source current capability
- Cost-effective alternative to thermistors
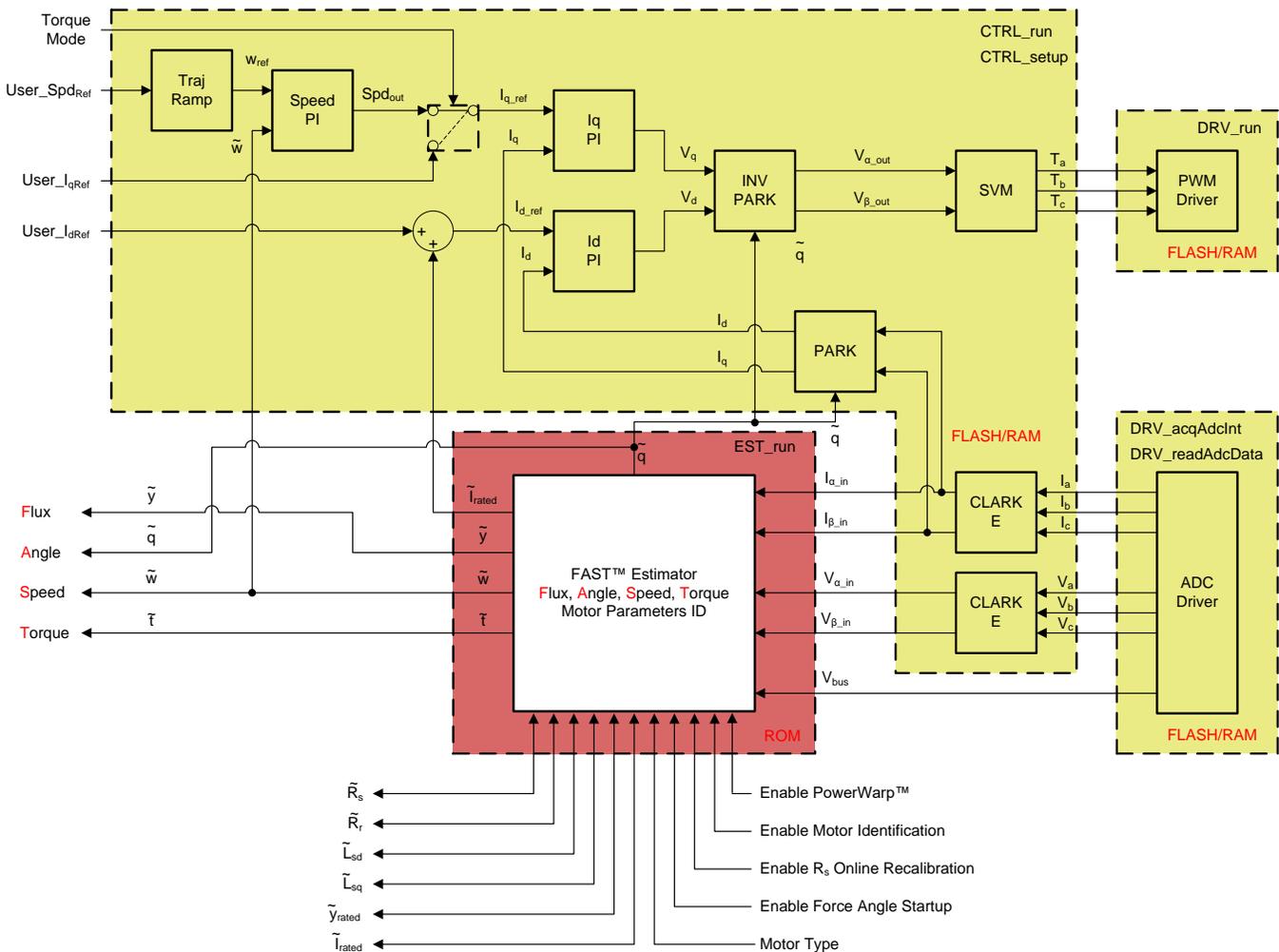
### 2.2.13 InstaSPIN-FOC™ for PMSM

TI's InstaSPIN-FOC technology enables designers to identify, tune, and fully control any type of three-phase, variable speed, sensorless synchronous, or asynchronous motor control system. This new technology removes the requirement for a mechanical motor rotor sensor to reduce system costs and improve operation using TI's new software encoder (sensorless observer) software algorithm, FAST™ (flux, angle, speed, and torque), embedded in the read-only memory (ROM) of Piccolo devices. This ROM enables premium solutions that improve motor efficiency, performance, and reliability in all variable-speed and variable-torque applications. [Figure 2](#) shows the block diagram of the InstaSPIN-FOC.



Copyright © 2017, Texas Instruments Incorporated


Figure 2. Block Diagram of InstaSPIN-FOC™

The main features of this device are as follows:

- Includes FAST estimator to measure rotor flux magnitude, rotor flux angle, motor shaft speed, and torque in a sensorless FOC system
- Automatic torque (current) loop tuning with option for user adjustments
- Automatic configuration of speed loop gains (Kp and Ki) provides stable operation for most applications and user adjustments required for optimum transient response
- Automatic or manual field weakening and field boosting
- Bus voltage compensation
- Automatic offset calibration ensures quality samples of feedback signals

### 3 System Design Theory


The primary goal of this reference design, with regards to the PCB in [Figure 3](#), is to make a compact solution that allows the option to drive three-phase BLDC motors for the AC compressor with a DC bus voltage up to 400 V. This reference design uses a minimum number of isolated parts, which are more expensive than non-isolated components. DC-link capacitors are not included in this PCB due to the small form factor. [Figure 3](#) shows that the MCU, as well as the entire digital logic, is located on the "hot" side (high-voltage side). The "cold" side delivers the supply voltage for the gate drivers as well as the MCU.

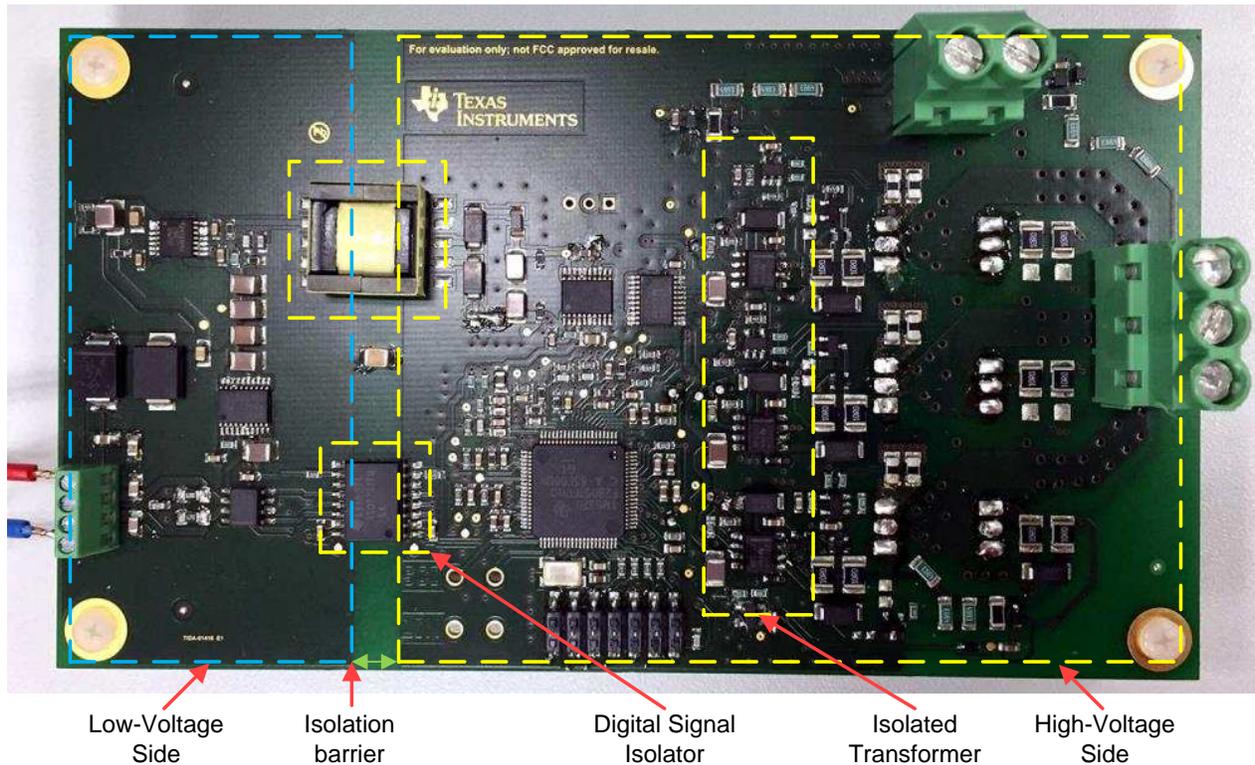

**Figure 3. TIDA-01418 PCB—Top View** <sup>(1)</sup>

<sup>(1)</sup> Uses only two isolated components: one is the digital signal isolator and the other is the isolated transformer for the power supply unit.

Figure 4 shows the bottom side of the TIDA-01418, where the current monitoring circuit is located.

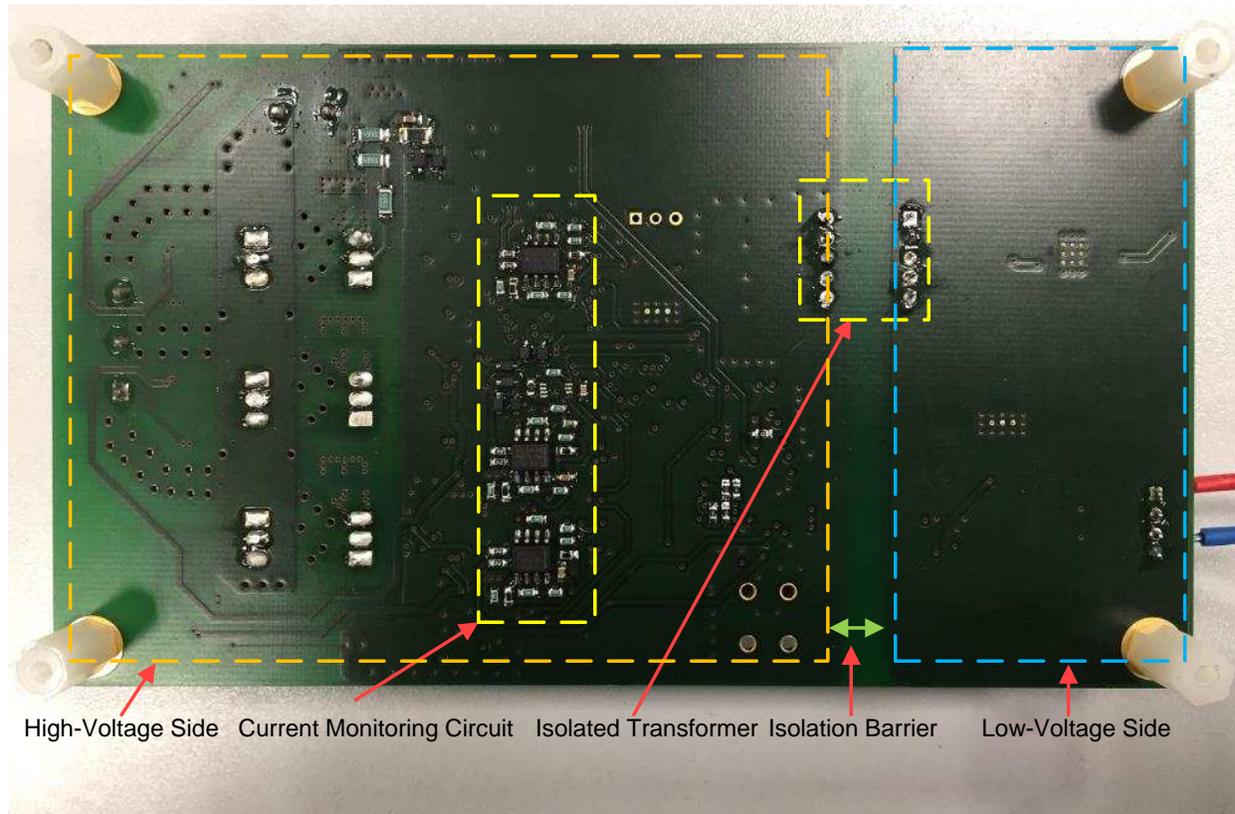

**Figure 4. TIDA-01418—Bottom View** <sup>(2)</sup>

<sup>(2)</sup> The current-monitoring circuit is located on the bottom side of the PCB. This image show the PCB with the IGBTs removed to provide a better view of the bottom side.

### 3.1 Protection Circuit and Power Supply

The supply voltage for the MCU, gate drivers, and the operational amplifiers (op amps), as well as all the other logic components located on the high-voltage side ("hot" side) of the PCB, travels through an isolated barrier from the low-voltage side (12-V battery). For this reason, the TIDA-01418 reference design uses an isolated power supply LM5160-Q1 in Fly-Buck-Boost topology, as Figure 5 shows.

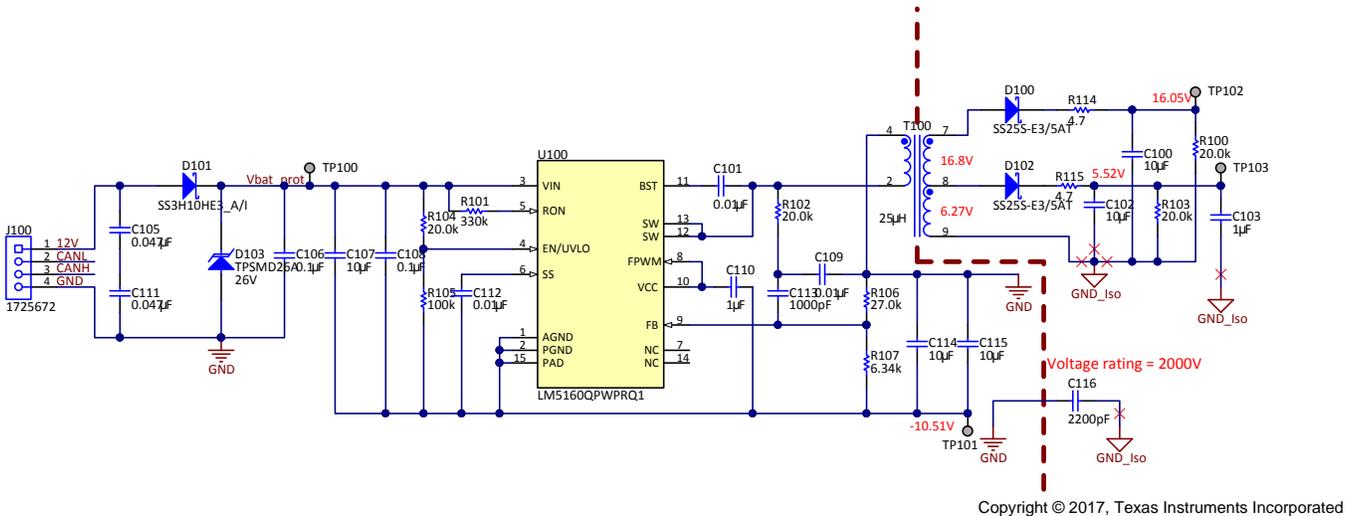


Figure 5. Power supply, Isolated Fly-Buck-Boost Converter

The Fly-Buck-Boost converter based on the LM5160-Q1 is implemented because it is cost-effective, easy to design, and has good flexibility. The LM5160-Q1 handles a wide input voltage ( $V_{IN}$ ) range up to 65 V.

One core component of the Fly-Buck-Boost power supply, not including the controller itself, is the isolated transformer, which has one primary winding and one secondary winding with center tapping (see Figure 6). Two output voltages are present on the power rails of the transformer on the secondary side, one of which is used to supply the gate drivers (16.8 V, unipolar supply). The other output voltage is followed by the LDO, which regulates an input of 6.27 V down to 3.3 V and supplies the MCU, op amps, and all other logic components.

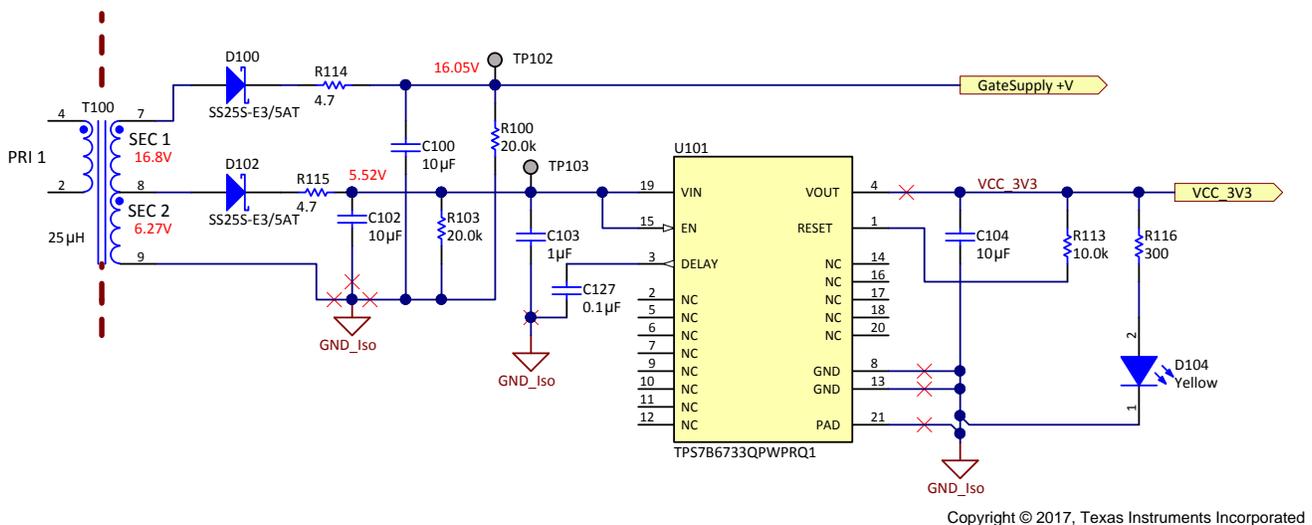


Figure 6. Isolated Transformer With Two Output Voltages on Secondary Side

The center-tapped transformer obtains the 16.8 V and 6.27 V and can provide better voltage balance and regulation because both rails can handle loads separately and the voltages do not collapse.


The protection circuit shown in [Figure 5](#) consists of an ESD protective part, reverse battery protection diode, transient voltage suppressor (TVS) diode, and one ceramic capacitor for better noise (ripple) filtering.

Two in-series capacitors with high-voltage rating values (100 V) are used for ESD protection. These capacitors are populated on the PCB in an L-shape (90° rotated from each other), which is a common technique in automotive applications. This way of arranging the ESD capacitors can prevent short circuit. When PCB bending occurs due to vibrations, the ceramic capacitor is subject to mechanical damage and inner layers of the capacitor are at the risk of being shorted.

A TVS diode protects the circuit against load dump transient, which occurs in the event of disconnecting a discharged battery while the alternator is generating charging current to the other loads which remain on the alternator circuit. Another important requirement for a TVS diode is the 24-V jump start (for 12-V systems). In this design, the TVS has been chosen in such a way that the standoff voltage value of the diode is above the voltage level, which can occur at the jump start of an event. In other words, below this voltage level, which is called reverse standoff voltage, the TVS diode is transparent for the rest of the circuit.
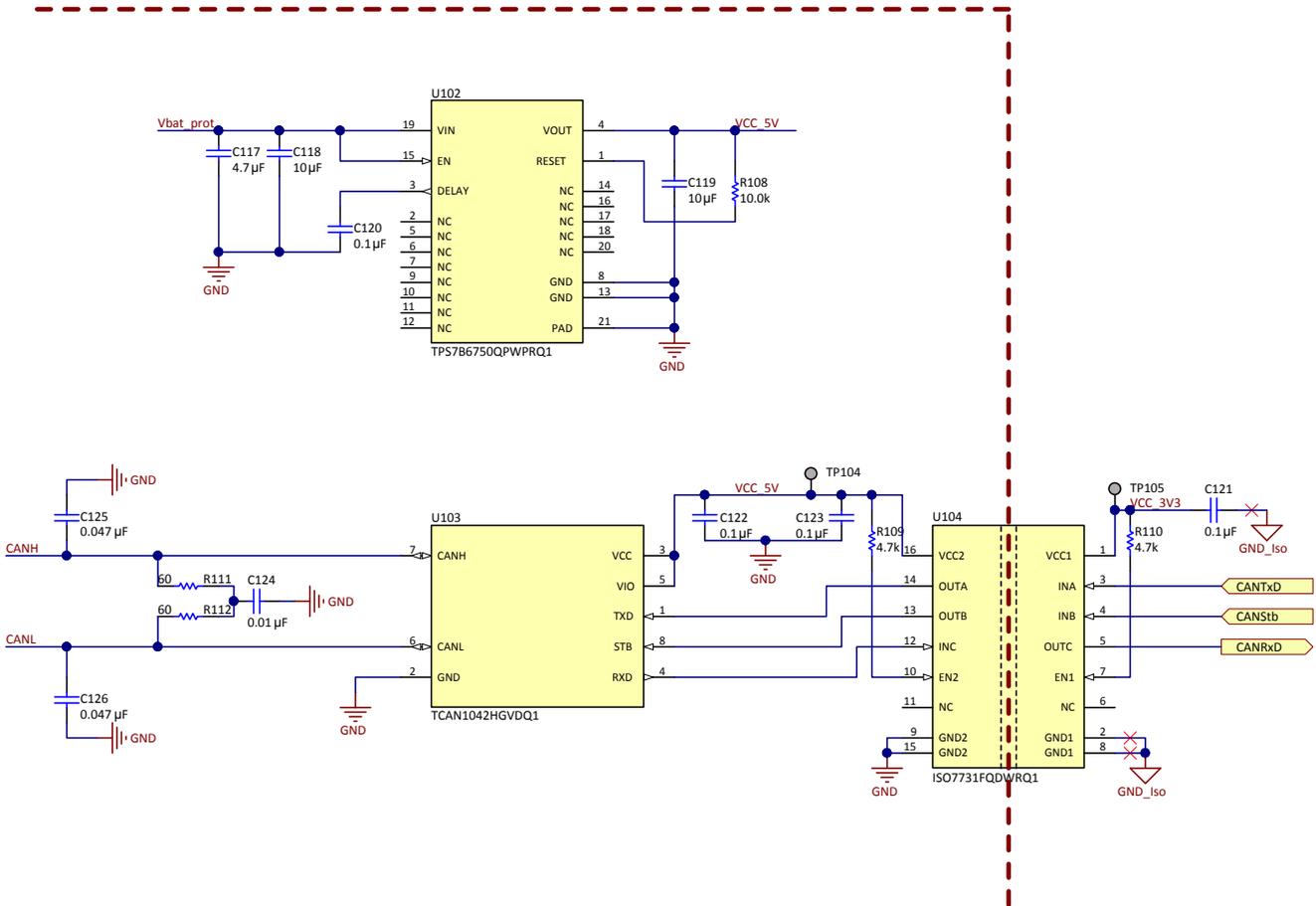
### 3.2 *Isolated Communication Interface*

The communication interface of this reference design is based on a controller area network (CAN bus) communication, where the interface between the CAN transceiver and MCU is isolated. [Figure 7](#) shows a schematic of the complete communication part of the TIDA-01418 reference design. The MCU is located on the high-voltage side of the PCB and the CAN transceiver is located on the low-voltage side; so, the only way to establish the interface connection between them is to use the digital signal isolator. An LDO with fixed output voltage (TPS7B6750-Q1) supplies the TCAN1042-Q1 transceiver as well as the primary side of the digital signal isolator (ISO7731-Q1) with 5 V. The input voltage of the LDO is also protected against reverse battery, ESD, and load dump transient.




Copyright © 2017, Texas Instruments Incorporated

**Figure 7. Isolated CAN Transceiver With 5-V Power Supply Delivered by LDO (Barrier is Dashed Line)**

The triple-channel digital isolator ISO7731-Q1 incorporates reinforced insulation with very-low propagation delay (11 ns typically) as well as high electromagnetic immunity and low emissions at low power consumption.

ISO7731-Q1 uses an ON-OFF keying (OOK) modulation scheme to transmit the digital data across an isolation barrier. Figure 8 shows the functional block diagram, which shows the transmitter and receiver part isolated by an SiO<sub>2</sub>-based capacitive-isolation barrier. The transmitter sends a high-frequency carrier across the barrier to represent one digital state and sends no signal, which represents the other digital state. On the receiver side, the signal is demodulated and a buffer stage generates the output.

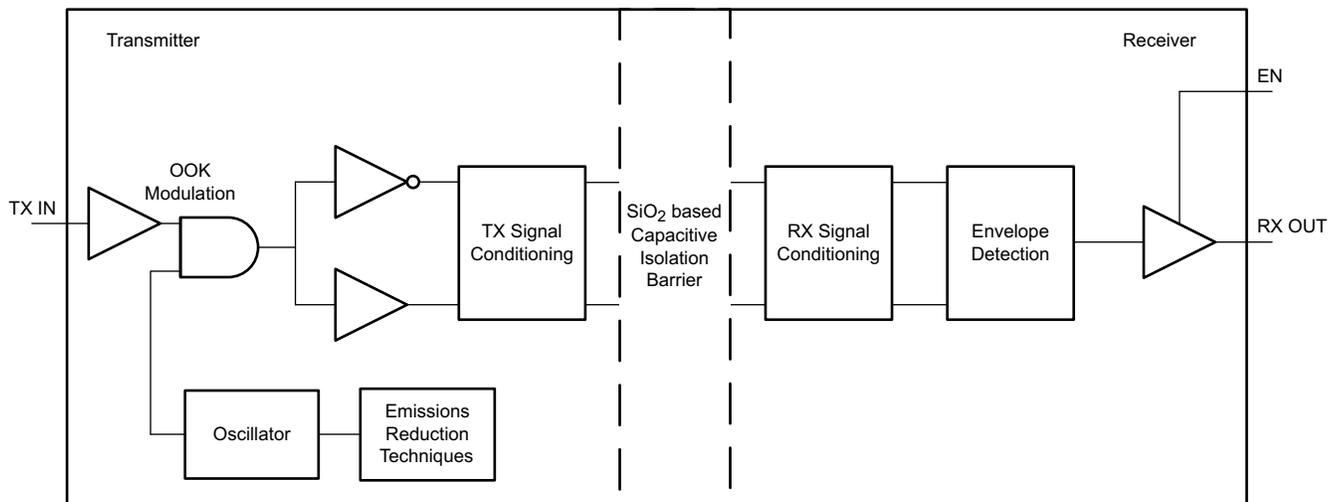


Copyright © 2016, Texas Instruments Incorporated

Figure 8. ISO7731-Q1 Functional Block Diagram
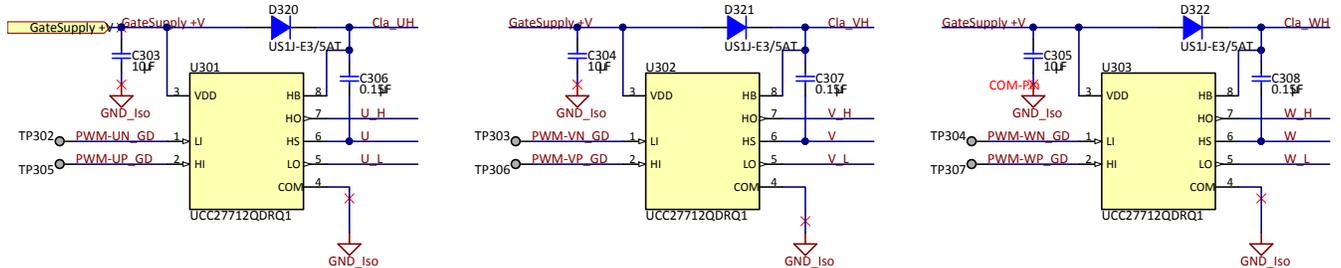
### 3.2.1 IGBT Gate Driver


This reference design uses non-isolated high- and low-side gate drivers with interlock (UCC27712-Q1), which are capable of 1.8-A/2.8-A source and sink peak current. According to the data sheet, the supply voltage for the gate drivers must be in the range of 10 V to 20 V. In this design, the UCC27712-Q1 drivers are supplied with 16 V.



Copyright © 2017, Texas Instruments Incorporated

Figure 9. UCC27712-Q1 High- and Low-Side Gate Drivers

In bridge topologies like half-bridge or full-bridge, the source and emitter pin of the top-side power IGBT switch is referenced to a node whose voltage changes dynamically; that is, not referenced to a fixed potential, so floating-driver devices are necessary in these topologies. As Figure 10 shows, the UCC27712-Q1 consists of one ground-referenced channel (LO) and one floating channel (HO), which is designed for operating with bootstrap or isolated power supplies and can handle up to 600 V. The driver can be used with 100% duty cycle as long as HB-HS can reach a value above the UVLO of the high side. The device features fast propagation delays and excellent delay matching between both channels. On the UCC27712-Q1, each channel is controlled by its respective input pins. The device features robust drive with large negative voltage tolerance on its inputs, high dV/dt tolerance, and wide negative transient safe operating area (NTSOA) on the switch node (HS).

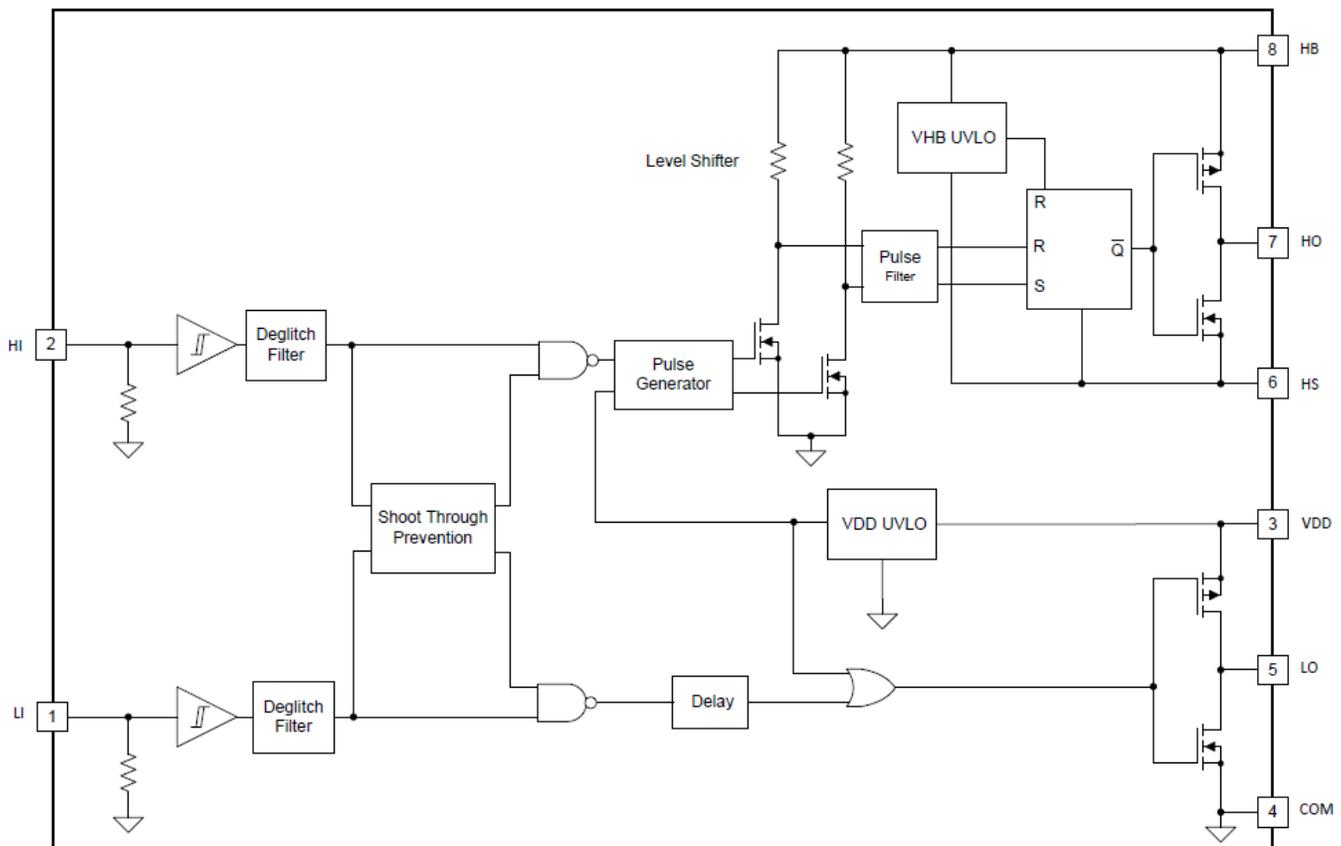


**Figure 10. UCC27712-Q1 Functional Block Diagram**

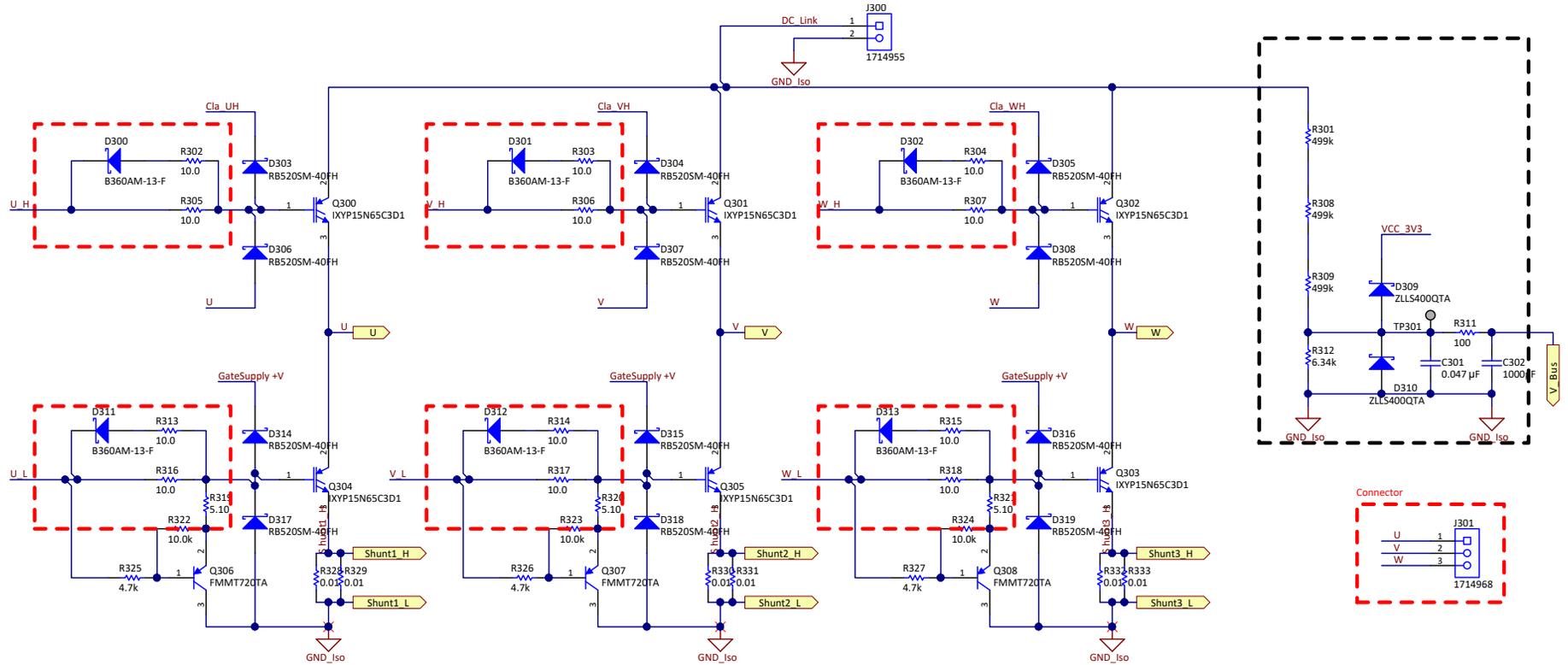The UCC27712-Q1 includes protection features where the outputs are held low when the inputs are floating or when the minimum input-pulse-width specification has not been met. Interlock and dead-time functions prevent both outputs from being turned on simultaneously. The device offers UVLO protection for both the VDD and HB bias supply.

### 3.3 IGBT Inverter


Figure 11 shows that the IGBT-based three-phase inverter consists of three half-bridges, where each half bridge is controlled by one UCC27712-Q1 driver. This reference design chooses the asymmetrical gate drive for the IGBTs, where the turnoff time is shorter than the turnon time. The series-connected fast-recovery diode is used to keep the gate resistance during turnoff lower than the gate resistance during turnon. This task is necessary because the turnoff delay time is often longer than the turnon delay time for some of the power devices. This safeguard is also helpful in preventing a parasitic turnon through the Miller capacitance. Alternatively, if the value chosen for the resistor in-series with the fast-recovery diode is too low, this action can lead to large voltage overshoot across the power devices, which results from  $di/dt$  being too high during turnoff. This relationship will always be a trade-off between switching speed and robustness. As a general rule, assume that  $R_{ON} = 2 \times R_{OFF}$ .



Copyright © 2017, Texas Instruments Incorporated

Figure 11. Three-Phase Inverter With Voltage Divider (Right Side) and Clamping Diodes to Measure Bus Voltage

The unipolar gate drivers control the IGBTs, which means that the IGBT gates must not encounter any negative voltage when switching them off. One possible risk is that the collector transient voltage can be coupled to the gate of the IGBT through the parasitic Miller capacitance, which leads to a false turnon of the IGBT. Resolve this issue by using an active Miller clamp circuit (see Figure 12). The Miller clamp provides a low impedance path to ground. The Miller clamp activates when the low-side IGBT is turned off. A Miller clamp circuit allows the use of a unipolar gate drive supply instead of a bipolar gate drive supply, which simplifies the power supply design for a more optimal solution at a reduced cost and smaller board size.

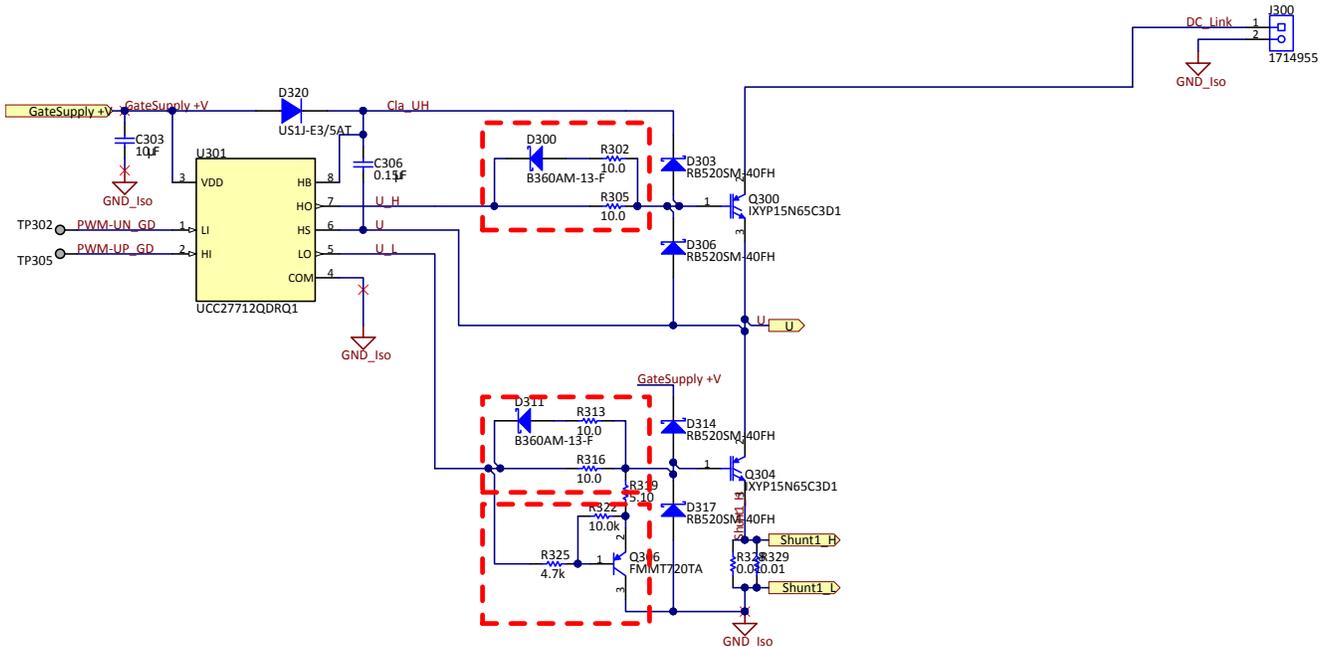


Copyright © 2017, Texas Instruments Incorporated

**Figure 12. UCC27712-Q1 With High- and Low-Side IGBTs** <sup>(3)</sup>

- <sup>(3)</sup> The low-side IGBT has an active Miller clamp circuit. All IGBTs are asymmetrical gate drives, for which the turnoff time is shorter than the turnon time.
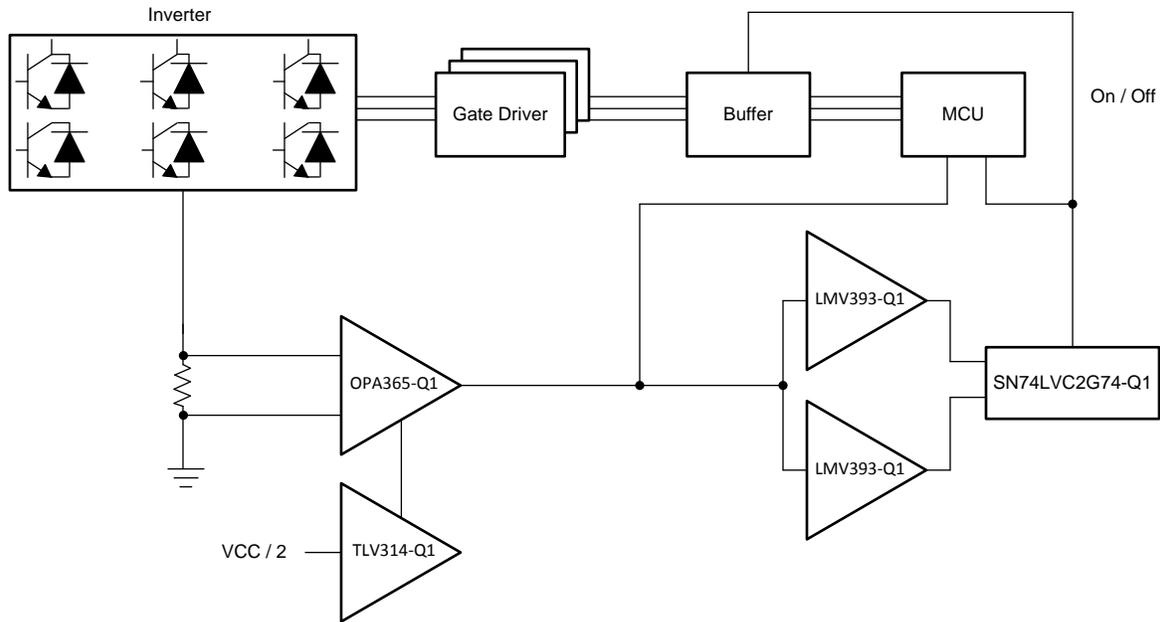
### 3.4 Current Monitoring


This reference design accomplishes overcurrent and short-circuit current protections by using the current monitor circuit shown in Figure 13. This circuit consists of one differential op amp, one op amp as a voltage follower generating reference voltage, two comparators, and one D-type flip-flop.



Copyright © 2017, Texas Instruments Incorporated

Figure 13. Block Diagram of Shunt Current-Monitoring Circuit


The op amp performs the differential voltage measurement across the shunt resistor. The voltage across the shunt resistor corresponds to the current that flows through the inverter. The requirements for the differential op amp in this application, while detecting overcurrent or short-circuit current, are: low noise, fast settling, low offset, and a slew rate, which has to be big enough to achieve the fast response time (typically a couple of  $\mu\text{s}$ ) for the whole system. This reference design uses the OPA365-Q1 (see Figure 14) as a differential op amp, which delivers excellent performance and meets all the previously-mentioned requirements (4.5 nV/ $\sqrt{\text{Hz}}$  at 100 kHz, 0.3  $\mu\text{s}$  to 0.01% settling time, 100- $\mu\text{V}$  offset, 25-V/ $\mu\text{s}$  slew rate). The TLV314-Q1 connected as a voltage follower functions as a source for the reference voltage. The level of the reference voltage, which TLV314-Q1 delivers to the differential op amps, is  $V_{\text{CC}} / 2$  (1.65 V). The output voltage range for the differential op amps (OPA365-Q1) varies from 1.65 V to 3.3 V for one direction of shunt current and from 1.65 V down to 0 V for the other direction of shunt current.

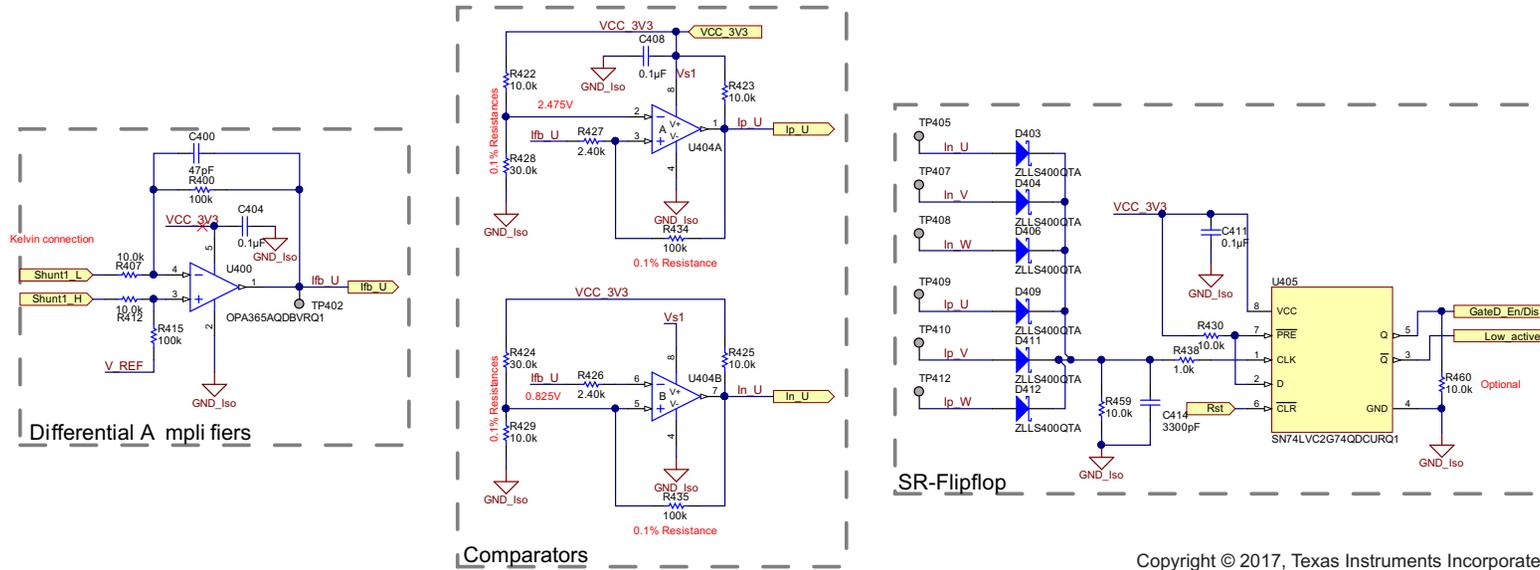

Copyright © 2017, Texas Instruments Incorporated

Figure 14. Overcurrent Protection Circuit

Monitoring the OPA365-Q1 output with an ADC from the MCU is not sufficient for detecting the short-circuit current and overcurrent in the inverter as fast as possible. For this reason, each differential op amp is followed by two comparators, one of which is always inverted. The comparators set the trigger levels, which are defined so that they correspond to the overcurrent. The inverted comparator makes it possible to detect current peaks in the shunt resistor in the opposite direction as well. When the overcurrent or short-circuit current occurs on one of the phases of the inverter, the responsible comparator detects it and changes its output state accordingly (which is connected to the flip-flop), the flip-flop latches its output, and disables the octal buffer between the MCU and gate drivers (see Figure 14). Figure 15 shows the SN74LVC541-Q1 octal buffer with tri-state outputs. As soon as the buffer is to be disabled from the flip-flop output signal ("GateD\_En/Dis"), the gate driver input signals are pulled down through the low-side resistors connected to each control line (on the right side), and thus the gate drivers force the IGBTs to turn off.

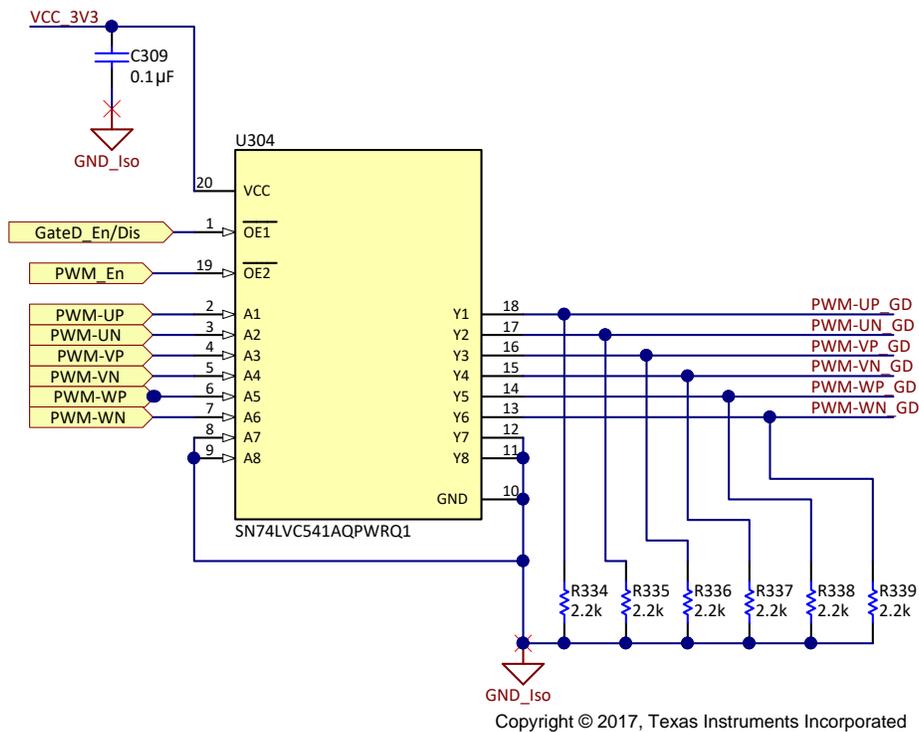

**Figure 15. SN74LVC541-Q1 Octal Buffer With Tri-State Outputs Connected Between MCU and Gate Drivers**

### 3.5 Motor Voltage Feedback Circuit

Figure 16 shows the voltage divider circuit, which is used to measure the back-electromotive force (back-EMF) of the unenergized winding. Back-EMF feedback is required for sensorless control to estimate the position of the rotor for accurate commutation. The voltage feedback circuit output is followed by clamping diodes to provide additional protection to the ADC pins of the MCU.

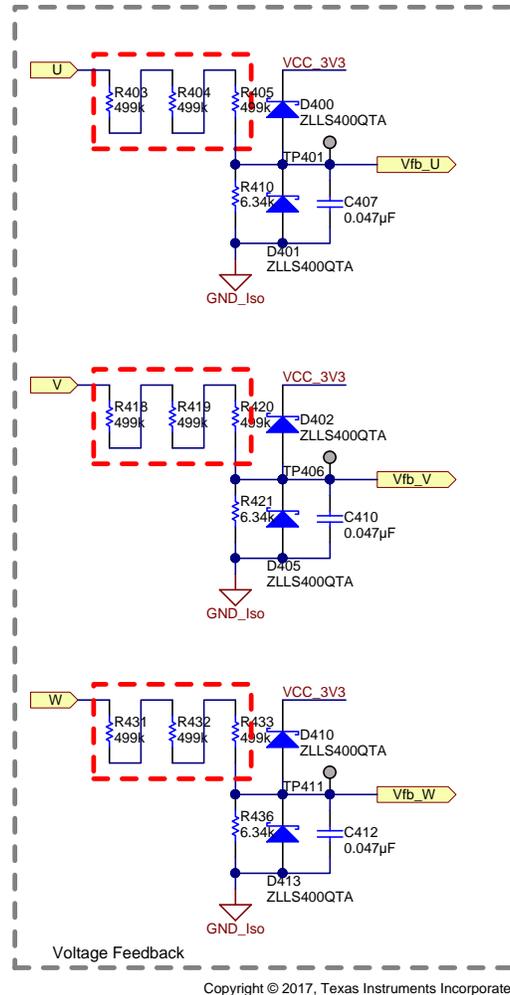


Figure 16. Motor Voltage Feedback Circuit


### 3.6 Microcontroller

The MCU selected for this reference design (TMS320F28052F) measures the phase voltage and current signals of the motor and generates the appropriate control signal for the power stage. The motor drive controller uses InstaSPIN-FOC, a sensorless field-oriented control algorithm for BLDC motors. Field-oriented control allows for optimal efficiency and noise performance from the motor being driven by the controller. InstaSPIN-FOC uses the signals from the motor back-EMF (voltage of each motor phase) and phase currents (each motor phase) to interpolate where the motor rotor is located and send the correct drive patterns.


## 4 Getting Started Hardware and Software

### 4.1 Hardware

This reference design allows control of three-phase, high-voltage BLDC motors with high power output. Testing for this design uses the following pictured test equipment. [Figure 17](#) shows the power analyzer and the high-voltage power supply, which supplies the TIDA-01418 reference design with 400 V. The power analyzer is used to monitor and analyze the efficiency of the inverter. The dynamometer controller (see [Figure 19](#)) controls the motor load and also measures the rotations per minute (RPM) of the running motor.

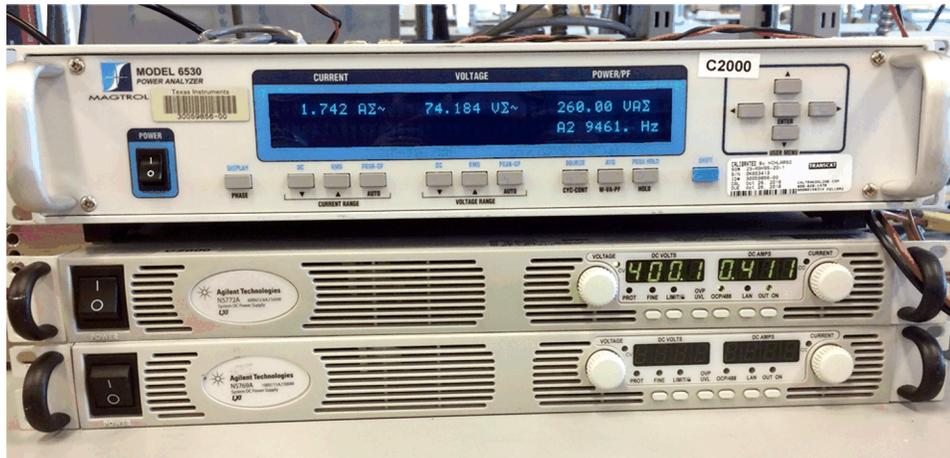

**Figure 17. High-Voltage Power Supply (Agilent NS772A) and Power Analyzer (Magtrol 6530)**

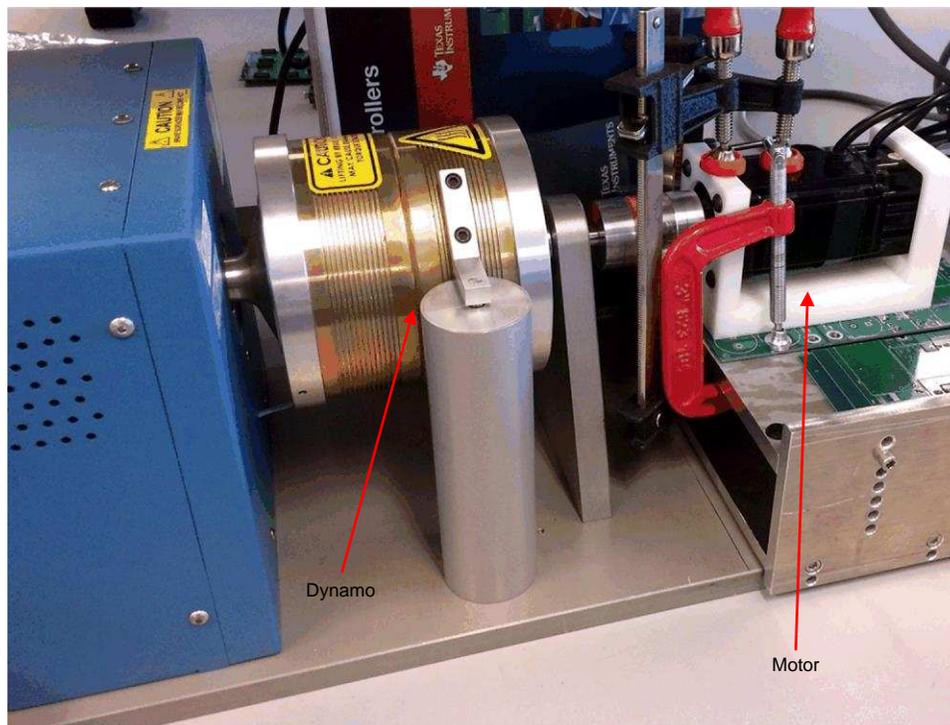

**Figure 18. Three-Phase BLDC Motor and Dynamometer (Magtrol)**



Figure 19. Dynamometer Controller



Figure 20. TIDA-01418 Test PCB Image

## 4.2 Software

### 4.2.1 Download and Install CCS™ Software and MotorWare™ Software


This reference design uses MotorWare™ Software for the BLDC motor control and system controllers. To get started, download the latest version from [Ti.com](http://www.ti.com).

See the resource for TI's Code Composer Studio™ (CCS) software at: <http://www.ti.com/tool/ccstudio> for information on downloading the integrated development environment for the C2000 code.

Download the MotorWare software from Texas Instruments at: <http://www.ti.com/tool/MOTORWARE>.

## 5 Testing and Results

Figure 21 shows the test setup of the TIDA-01418 reference design.

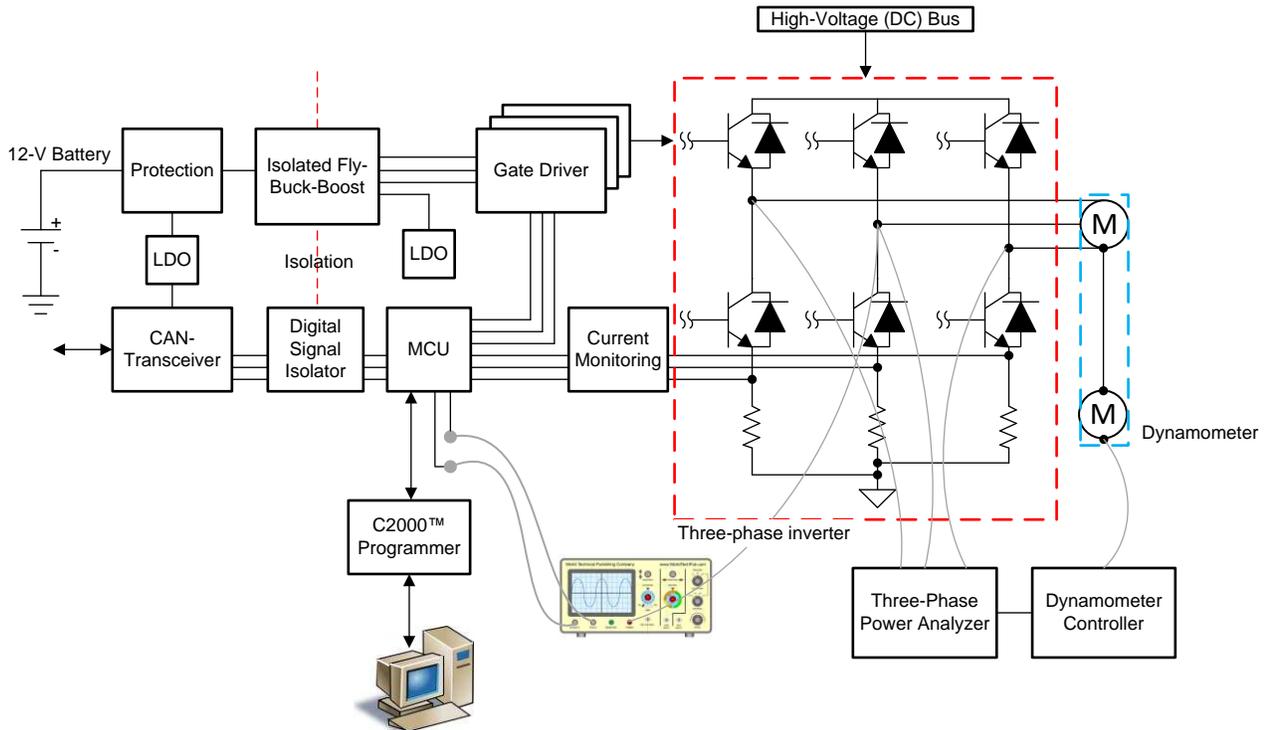

Copyright © 2017, Texas Instruments Incorporated

**Figure 21. TIDA-01418 Test Setup**

Several tests were conducted to verify the performance of the motor driver board:

- Loaded board
- Motor spins down to 100 RPM
- Overcurrent protection

Figure 22 shows an oscilloscope image of the running motor with a light load, where channel 4 represents the current in one phase of an inverter, channel 2 shows the angle of the rotor (as estimated by the MCU), and channel 1 represents motor phase voltage.

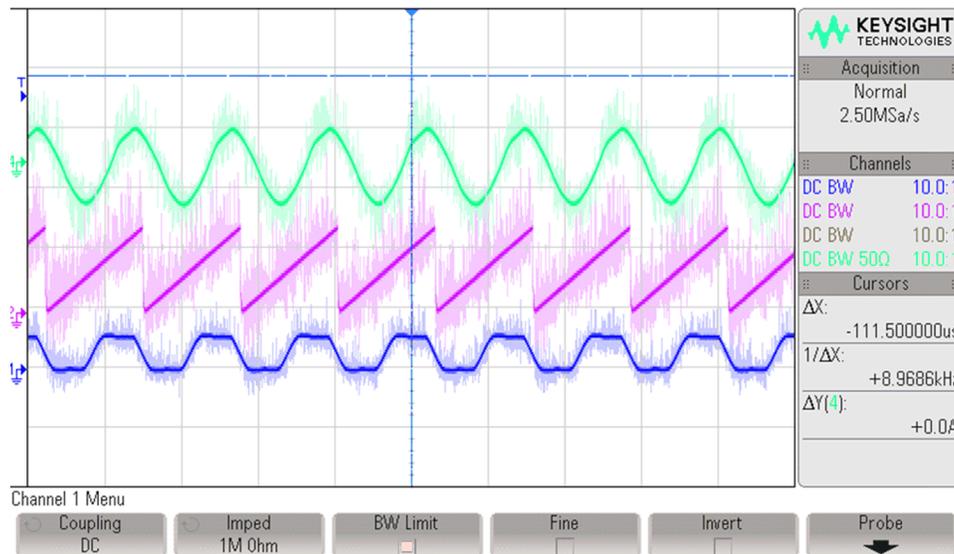


Figure 22. Ch2: MCU Simulated Angle of Rotor for Open-Loop Control; CH4: Motor Current (One Phase)

Figure 23 shows an oscilloscope image that corresponds to the 100 RPM of the light-loaded motor, where channel 4 represents the motor current and channel 1 shows the rotor angle.


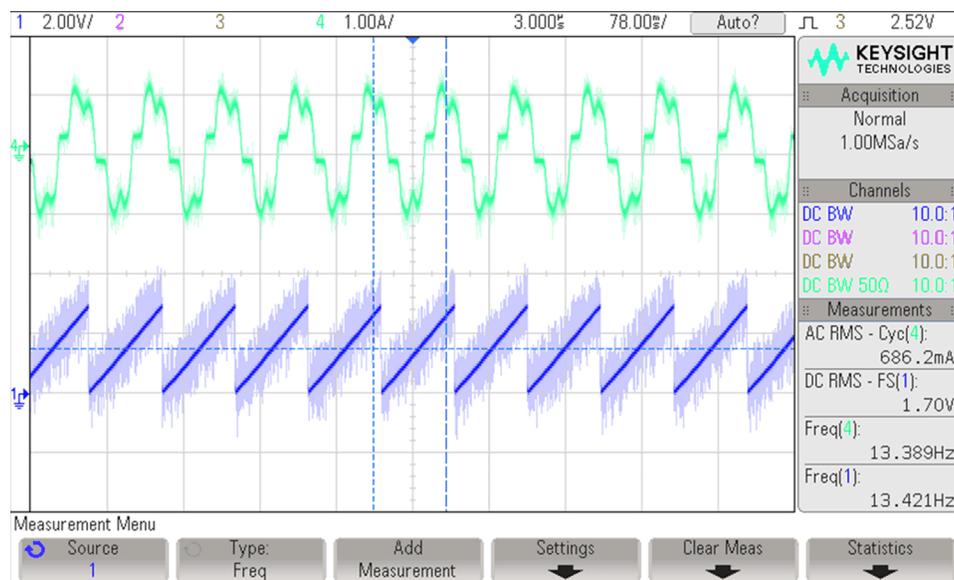


Figure 23. Motor Spinning With 100 RPM

Figure 25 shows the overcurrent condition, where channel 3 represents the waveform at the input of the SR-flip-flop (pin 1 in Figure 24). This trigger signal originates from one of the comparators, which is triggered (output HI) after the shunt current amplifier output reaches the voltage threshold. The voltage threshold corresponds to the preset high-current value.

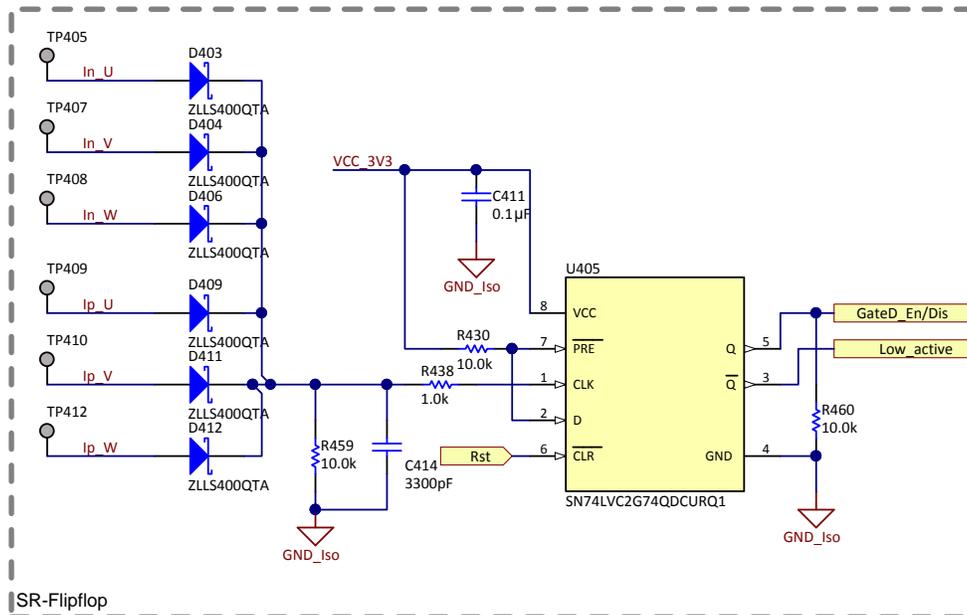

Copyright © 2017, Texas Instruments Incorporated

Figure 24. SR-Flipflop

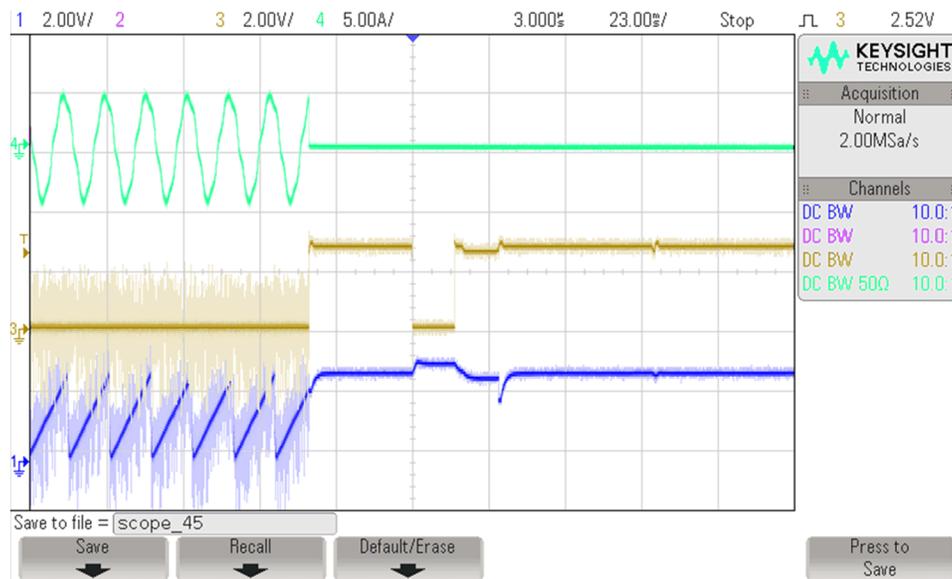


Figure 25. Overcurrent Condition

Since one of the goals for this TI-design was small PCB-size, the using of high voltage capacitors for each half bridge was avoided. Therefore the noise on the signal traces in Figure 22 and Figure 23 is visible.

To reduce the noise level significantly or eliminate it, it is strongly recommended to use high voltage foil capacitor for each half bridge as well as DC-Link capacitors on the high voltage DC bus connector.

## 6 Design Files

### 6.1 Schematics

To download the schematics, see the design files at [TIDA-01418](#).

### 6.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01418](#).

### 6.3 PCB Layout Recommendations

#### 6.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01418](#).

### 6.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01418](#).

### 6.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01418](#).

### 6.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01418](#).

### 6.7 Trademarks

InstaSPIN, Piccolo, E2E, C2000, Fly-Buck, FAST, InstaSPIN-FOC, MotorWare, Code Composer Studio are trademarks of Texas Instruments.

All other trademarks are the property of their respective owners.

## 7 Software Files

To download the software files, see the design files at [TIDA-01418](#).

## 8 About Author

**LEVAN BIDZISHVILI** is a systems engineer at Texas Instruments where he is responsible for developing reference design solutions for the automotive body and HVAC segment. Levan brings his extensive experience of more than 7 years of automotive analog and digital applications to this role. Levan earned his master's degree of engineering in sensor systems technology from the University of Applied Sciences in Karlsruhe, Germany.

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from Original (January 2018) to A Revision</b>	<b>Page</b>
• Updated incorrect part number .....	<a href="#">21</a>

---

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2018, Texas Instruments Incorporated