

## Design Guide: TIDA-070002

# 20- to 40- $V_{IN}$ , 50-W Space-Grade Isolated-Flyback DC-DC Over Current Protection Reference Design



### Description

Spacecraft bus voltages vary from the well-established 28-V to more than the 100-V typically used in high-power commercial communications satellites, this reference design shows an example for a space-grade 50-W isolated intermediary bus converter, while implementing over-current protection (OCP) limit function. This design features [INA901-SP](#) radiation hardened current monitor, [LM139AQML-SP](#) quad-comparator, and [UC1901-SP](#) to create an isolated feedback flyback with current sensing and overcurrent flags – the [UC1843A-SP](#) current mode PWM controller is used to switch the low side MOSFET of the flyback converter and provide voltage and current to the output, the UC1901-SP senses the output voltage and completes the loop for the isolated feedback. The INA901-SP senses the input current which is provided to the LM139AQML-SP to create an overcurrent flag.

### Features

- Isolated magnetic feedback using UC1901-SP
- Current sensing using INA901-SP
- Overcurrent comparison using LM139AQML-SP
- Pulse-by-pulse current limiting
- Double pulse suppression
- Multiple feedback paths supported

### Applications



- [Command and data handling](#)
- [Satellite electric power system \(EPS\)](#)
- [Optical imaging payload](#)
- [Radar imaging payload](#)
- [Communications payload](#)

### Resources

<a href="#">TIDA-070002</a>	Design Folder
<a href="#">UC1843A-SP</a>	Product Folder
<a href="#">UC1901-SP</a>	Product Folder
<a href="#">INA901-SP</a>	Product Folder
<a href="#">LM139AQML-SP</a>	Product Folder



[ASK Our E2E™ Experts](#)

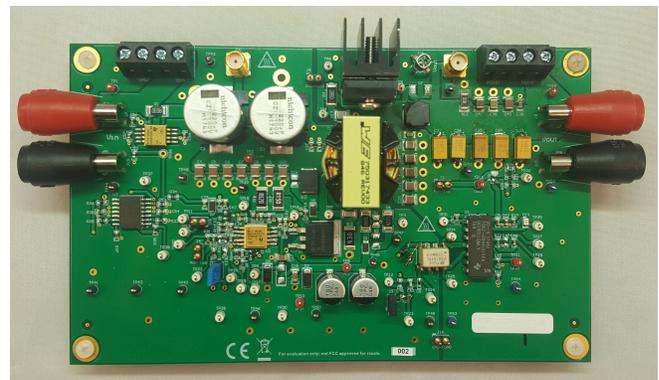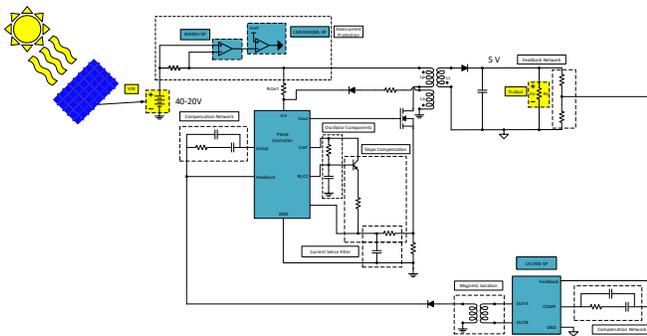



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 1 System Description

The TIDA-070002 uses the UC1843A-SP, INA901-SP, LM139AQML-SP, and UC1901-SP to create an isolated feedback flyback with current sensing and overcurrent flags. The UC1843A-SP is used to switch the low side MOSFET of the flyback converter and provides voltage and current to the output. The system uses the UC1843A-SP to provide 5-V and 10-A outputs. These outputs are not dependent on the UC1843A-SP itself, and can be increased or decreased depending on the design. The UC1901-SP senses the output voltage and provides isolated feedback to the UC1843A-SP to complete the control loop. The INA901-SP senses the input current which is then provided to the LM139AQML-SP to create an overcurrent flag. In a full system, this flag could be used to shutdown the UC1843A-SP and turn off the converter.

### 1.1 Key System Specifications

**Table 1. Key System Specifications**

PARAMETER	SPECIFICATIONS	DETAILS
Input Power Supply	20 to 40 VDC	<a href="#">Table 2</a>
Output Voltage	5 VDC	<a href="#">Table 2</a>
Output Current	0 to 10 A	<a href="#">Table 2</a>
Output Current Pre-load	100 mA	<a href="#">Table 2</a>
Operating Temperature	25°C	<a href="#">Table 2</a>
Switching Frequency of UC1843A-SP	200 kHz	<a href="#">Section 2.4.1</a>
Switching Frequency of UC1901-SP	1 MHz	<a href="#">Table 2</a>
Peak Input Current Limit	12 A	<a href="#">Section 2.4.7</a>
Bandwidth	~2 kHz	<a href="#">Section 3.2.2.3</a>
Phase Margin	~70°	<a href="#">Section 3.2.2.3</a>

## 2 System Overview

### 2.1 Block Diagram


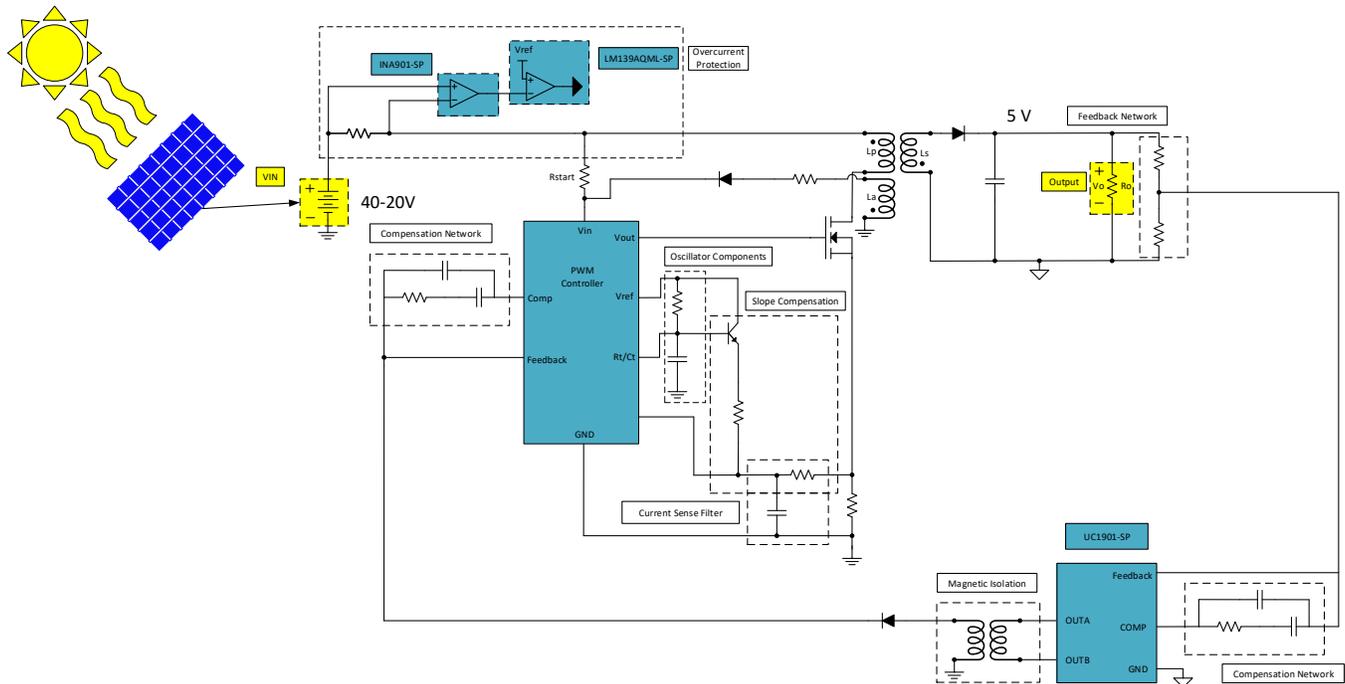


Figure 1. TIDA-070002 Block Diagram

### 2.2 Design Considerations

When using the INA901-SP and LM139AQML-SP as a way to implement an input overcurrent flag, care has to be taken to where the overcurrent point is set. Input current can vary widely due to duty cycle changes because of input voltage and efficiency changes over that input voltage. When using the UC1901-SP care has to be taken into account for the max minimum input voltage of 4.5 V. For low output voltages this can be a hard input voltage to maintain off of the output, so other methods may have to be used. One method is to charge pump the switch node and use diodes between that and the output voltage, while another method is simply have another source from a separate converter.

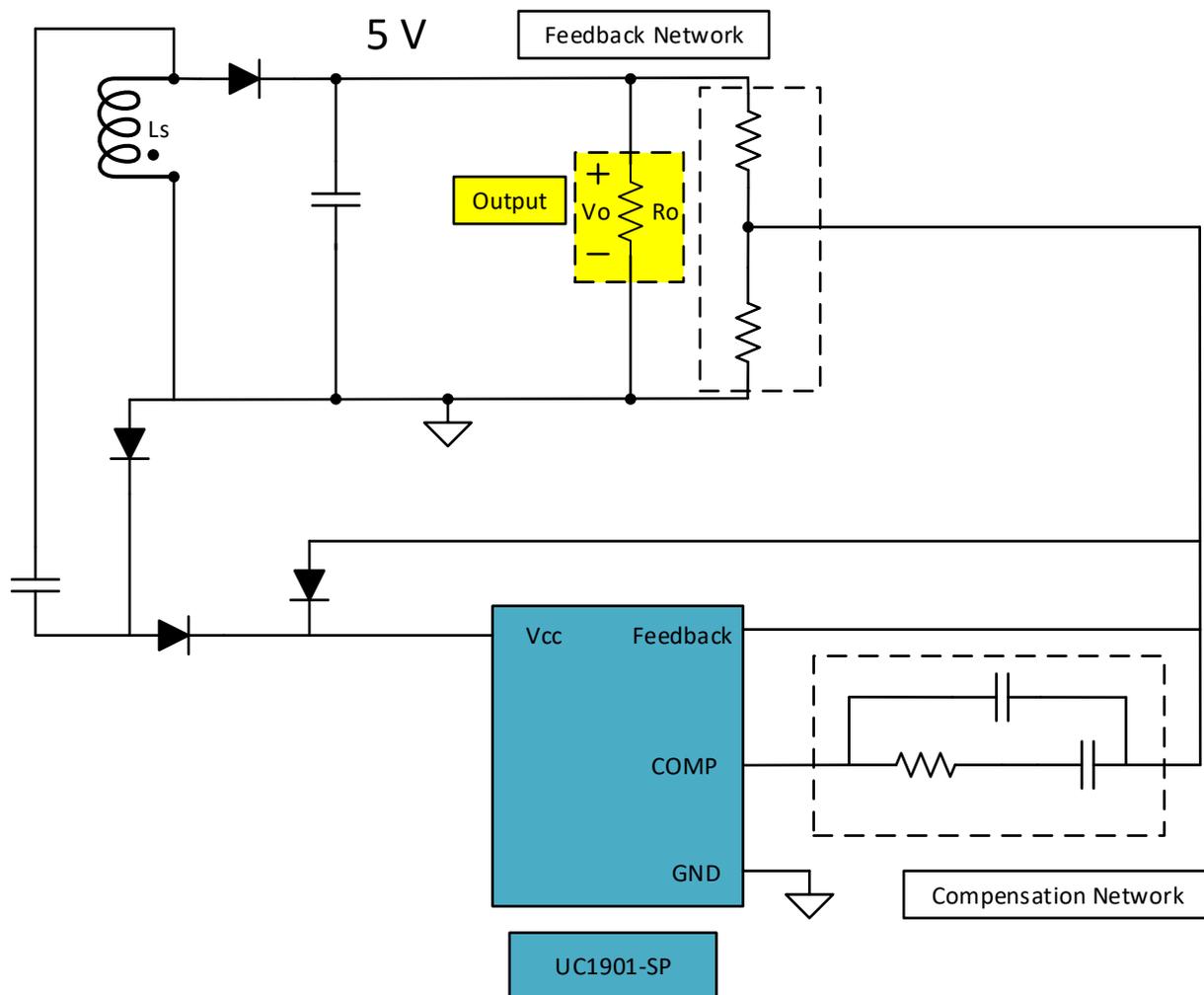

**Figure 2. Alternative Method to Create  $V_{cc}$  for UC1901-SP**

## 2.3 Highlighted Products

### 2.3.1 UC1843A-SP

- QML Class V (QMLV) Qualified, SMD 5962-86704
- 5962P8670409Vxx:
  - Radiation Hardness Assurance (RHA) up to 30-krad(Si) Total Ionizing Dose (TID)
  - Passes functional and specified post radiation parametric limits of 45 krad(Si) at LDR (10 mrad(Si)/s) per 1.5x over test as defined in MIL-STD-883 Test Method 1019.9 Paragraph 3.13.3.b
  - Exhibits LDR sensitivity but remains within the pre-radiation electrical limits at 30-krad(Si) Total Dose Level, as allowed by MIL-STD-883, TM1019
- Optimized for offline and DC-to-DC converters
- Low start-up current (< 0.5 mA)
- Trimmed oscillator discharge current
- Automatic feed forward compensation
- Pulse-by-pulse current limiting
- Enhanced load response characteristics
- Undervoltage lockout (UVLO) with hysteresis

- Double-pulse suppression
- High-current totem-pole output
- Internally-trimmed bandgap reference
- 500-kHz operation
- Low  $R_O$  error amplifier

### 2.3.2 UC1901-SP

- An amplitude-modulation system for transformer coupling an isolated feedback error signal
- Low-cost alternative to optical couplers
- Internal 1% reference and error amplifier
- Internal carrier oscillator usable to 5 MHz
- Modulator synchronizable to an external clock
- Loop status monitor

### 2.3.3 INA901-SP

- 5962-1821001
  - Radiation Hardness Assured (RHA) 100 krad(Si) at LDR
  - Single Event Latch-up (SEL) Immune to 93 MeV-cm<sup>2</sup>/mg at 125°C
  - Qualified over the Military Temperature Range (–55°C to 125°C)
  - High-performance 8-pin ceramic flat pack package (HKX)
- Wide common-mode range: –16 V to 80 V
- CMRR: 120 dB
- Accuracy:
  - ±0.5-mV offset
  - ±0.2% gain error
  - 2.5-μV/°C offset drift
  - 50-ppm/°C gain drift
- Bandwidth: Up to 130 kHz
- Gain: 20 V/V
- Quiescent current: 700 μA
- Power supply: 2.7 V to 18 V
- Provision for filtering

### 2.3.4 LM139AQML-SP

- Available with radiation ensured
  - TID 100 krad(Si)
  - ELDRS free 100 krad(Si)
- Wide supply voltage range
- LM139A Series 2 to 36  $V_{DC}$  or ±1 to ±18  $V_{DC}$
- Very-low supply current drain (0.8 mA)
- Low input biasing current: 25 nA
- Low input offset current: ±5 nA
- Offset voltage: ±1 mV
- Input common-mode voltage range includes GND
- Differential input voltage range equal to the power supply voltage
- Low output saturation voltage: 250 mV at 4 mA

- Output voltage compatible with TTL, DTL, ECL, MOS and CMOS logic systems

## 2.4 System Design Theory

### 2.4.1 Switching Frequency

Choosing a switching frequency has a trade off between efficiency and bandwidth. Higher switching frequencies will have larger bandwidth, but a lower efficiency than lower switching frequencies. A switching frequency of 200 kHz was chosen as a trade off between bandwidth and efficiency. Using equations provided by the datasheet for the UC1843A-SP,  $R_T$  and  $C_T$  were chosen to be 7.15 k $\Omega$  and 1200 pF, respectively. The equation from the datasheet are shown below:

$$f_{osc} \approx \frac{1.72}{R_{osc} \times C_{osc}} \quad (1)$$

$$f_{osc} \approx \frac{1.72}{7.15 \text{ k}\Omega \times 1200 \text{ pF}} = 200 \text{ kHz} \quad (2)$$

### 2.4.2 Transformer

The transformer of the design consists of two major values, turns ratio and primary side inductance. There is no minimum limit to the turns ratio of the transformer, just a maximum one. The equation below will give the turns ratio as a function of duty cycle which if you put in the maximum duty cycle of the converter will give you a maximum turns ratio. The UC1843A-SP design targeted a duty cycle of 50% which is somewhat low for this controller. The suggested value would be around 70% duty cycle to take advantage of the fact the UC1843A-SP has full duty cycle range. The equation of the turns ratio of the transformer is:

$$N_{psMAX} = \frac{V_{inMIN} \times D_{lim}}{(V_{out} + V_{Diode}) \times (1 - D_{lim})} \quad (3)$$

$$N_{psMAX} = \frac{20 \text{ V} \times 0.5}{(5 \text{ V} + 0.7 \text{ V}) \times (1 - 0.5)} = 3.5 \quad (4)$$

Often the turns ratio will slightly change in design due to how the transformer is manufactured. For the UC1843A-SP design a turns ratio of 3.33 was used. Another turns ratio that is important is the turns ratio of the auxiliary winding. The auxiliary winding is found by figuring out what positive voltage is needed from the auxiliary winding. Picking what voltage the auxiliary winding should have lets one pick the turns ratio from the secondary to the auxiliary winding, which in turn allows for the turns ratio from primary to auxiliary to be found.

$$N_{pa} = \frac{N_{ps} \times (V_{out} + V_{Diode})}{V_{aux}} \quad (5)$$

$$N_{pa} = \frac{3.33 \times (5 \text{ V} + 0.7 \text{ V})}{13 \text{ V}} = 1.46 \quad (6)$$

An auxiliary winding of 1.43 was used for the UC1843A-SP design due to manufacturing constraints. The primary inductance of the transformer is found from picking an appropriate ripple current. A higher inductance will often mean reduced current ripple, thus lower EMI and noise, but a higher inductance will also increase physical size and limit the bandwidth of the design. A lower inductance will do the opposite, increasing current ripple, lowering EMI, lowering noise, decreasing physical size, and increasing the limited bandwidth of the design. The percent ripple current can be anywhere from 20% to 80% depending on the design. The equation for finding the primary inductance from the percentage ripple current is:

$$L_{PRI} = \frac{V_{inMAX}^2 \times D_{MIN}^2}{V_{out} \times I_{out} \times f_{osc} \times \%Ripple} \quad (7)$$

$$\frac{(40 \text{ V})^2 \times 0.25^2}{5 \text{ V} \times 10 \text{ A} \times 200 \text{ kHz} \times 0.4} = 25 \mu\text{H} \quad (8)$$

There are quite a few physical limitations when making transformers, so often this inductance will change slightly. For the UC1843-SP design a primary inductance of 21  $\mu\text{H}$ . This corresponds to a percent ripple of around 0.475. The peak and primary currents of the transformer are also generally useful for figuring out the physical structure of the transformer, so equations are listed below.

$$I_{Ripple} = \frac{V_{out} \times I_{out} \times \%Ripple}{V_{inMAX} \times D_{MIN}} \quad (9)$$

$$I_{Ripple} = \frac{5 \text{ V} \times 10 \text{ A} \times 0.475}{40 \text{ V} \times 0.25} = 2.375 \text{ A} \quad (10)$$

$$I_{PriPeak} = \frac{V_{out} \times I_{out}}{V_{inMIN} \times D_{MAX} \times \eta} + \frac{I_{Ripple}}{2} \quad (11)$$

$$I_{PriPeak} = \frac{5 \text{ V} \times 10 \text{ A}}{20 \text{ V} \times 0.5 \times 0.8} + \frac{2.375}{2} = 7.44 \text{ A} \quad (12)$$

$$I_{PriRMS} = \sqrt{D \times \left( \frac{V_{out} \times I_{out}}{V_{in} \times D} \right)^2 + \frac{I_{ripple}^2}{3}} \quad (13)$$

$$I_{PriRMS} = \sqrt{0.5 \times \left( \frac{5 \text{ V} \times 10 \text{ A}}{20 \text{ V} \times 0.5} \right)^2 + \frac{(2.375 \text{ A})^2}{3}} = 3.79 \text{ A} \quad (14)$$

$$I_{SecRMS} = \sqrt{(1-D) \times I_{out}^2 + \frac{(I_{ripple} \times N_{ps})^2}{3}} \quad (15)$$

$$I_{SecRMS} = \sqrt{0.5 \times (10 \text{ A})^2 + \frac{(2.375 \text{ A} \times 3.33)^2}{3}} = 8.42 \text{ A} \quad (16)$$

### 2.4.3 RCD and Diode Clamp

For the UC1843-SP design a Zener diode was used which will clamp, often called the snubber, the voltage to around what the breakdown voltage of the Zener diode plus the input voltage of the design. Since Zener diodes take time to switch, the actual clamped voltage will often be above the Zener diode breakdown voltage plus the input voltage. Since using a resistor and capacitor are commonly used for the clamp for flybacks, the design philosophy for how to pick resistor and capacitor values will be covered. The resistor and capacitor is generally a value that is found through testing, but starting values can be obtained. To figure out the resistor and capacitor needed for the RCD clamp, one must first pick how much the node is allowed to overshoot. The equation for finding the voltage of the clamp is:

$$V_{clamp} = K_{clamp} \times N_{ps} \times (V_{out} + V_{Diode}) \quad (17)$$

Note that  $K_{clamp}$  is recommended to be 1.5 as this will allow for only around 50% overshoot. Knowing the parasitic inductance of the transformer and how much the snubber voltage is allowed to change over the switching cycle, can allow one to figuring out starting values for the resistor and capacitor using the following equations:

$$R_{clamp} = \frac{V_{clamp}^2}{\frac{1}{2} \times L_{leakage} \times I_{PriPeak}^2 \times \frac{V_{clamp}}{V_{clamp} - N_{ps} \times (V_{out} + V_{Diode})} \times f_{osc}} \quad (18)$$

$$C_{clamp} = \frac{V_{clamp}}{\Delta V_{clamp} \times V_{clamp} \times R_{clamp} \times f_{osc}} \quad (19)$$

A starting value of 10% is generally used for  $\Delta V_{clamp}$ .

### 2.4.4 Output Diode

The voltage stress by the converter on the diode can be found with the following equation:

$$V_{DiodeStress} = V_{out} + \frac{V_{inMAX}}{N_{ps}} \quad (20)$$

$$V_{DiodeStress} = 5 \text{ V} + \frac{40 \text{ V}}{3.33} = 17 \text{ V} \quad (21)$$

Note that any diode picked should have a voltage rating of well above this value as it does not include parasitic spikes in the equation. The UC1843-SP diode was picked to have a voltage rating of 60 V.

### 2.4.5 Output Filter and Capacitance

For most designs, a ripple voltage is picked and the output capacitance is figured out from that value. The UC1843A-SP design started similar to that using the equations:

$$C_{out} > \frac{I_{out} \times D_{MAX}}{V_{ripple} \times f_{osc}} \quad (22)$$

$$C_{out} > \frac{10 \text{ A} \times 0.5}{50 \text{ mV} \times 200 \text{ kHz}} = 500 \text{ } \mu\text{F} \quad (23)$$

$$C_{out} > \frac{\Delta I_{step}}{2\pi \times \Delta V_{out} \times f_{co}} \quad (24)$$

$$C_{out} > \frac{10 \text{ A}}{2\pi \times 0.7 \text{ V} \times 2.2 \text{ kHz}} = 1 \text{ mF} \quad (25)$$

A value of around 1145  $\mu\text{F}$  was chosen to keep output voltage ripple low. Note that the output voltage ripple in the design was further decreased by adding an output filter and by adding an inductor after a small portion of the output capacitance. Six ceramic capacitors were picked to be placed before the output filter and then the large tantalum capacitors with some small ceramics were added to be part of the output filter. The initial ceramics will help with the initial current ripple, but have a very large output voltage ripple. This voltage ripple will be attenuated by the inductor and capacitor combination placed between the ceramic capacitors and the output. The equations below allow for finding the amount of attenuation that will come from a specific output filter inductance. An inductance of 500 nH was chosen to attenuate the output voltage ripple.

$$F_{\text{resonant}} = \frac{1}{2\pi \times \sqrt{L_{\text{Filter}} \times C_{\text{oBulk}}}} \quad (26)$$

$$F_{\text{resonant}} = \frac{1}{2\pi \times \sqrt{0.5 \text{ nH} \times 1127 \mu\text{F}}} = 6.7 \text{ kHz} \quad (27)$$

$$F_{\text{Zero}} = \frac{1}{2\pi \times C_{\text{oBulk}} \times \text{ESR}_{\text{oBulk}}} \quad (28)$$

$$F_{\text{Zero}} = \frac{1}{2\pi \times 1127 \mu\text{F} \times 0.009 \Omega} = 15.69 \text{ kHz} \quad (29)$$

$$\text{Attenuation}_{f_{\text{SW}}} = 40 \times \log_{10}\left(\frac{f_{\text{osc}}}{f_{\text{resonant}}}\right) - 20 \times \log_{10}\left(\frac{f_{\text{osc}}}{f_{\text{zero}}}\right) \quad (30)$$

$$\text{Attenuation}_{f_{\text{SW}}} = 40 \times \log_{10}\left(\frac{200 \text{ kHz}}{6.7 \text{ kHz}}\right) - 20 \times \log_{10}\left(\frac{200 \text{ kHz}}{15.69 \text{ kHz}}\right) = 36.88 \text{ dB} \quad (31)$$

Sometimes the output filter can causing peaking at high frequencies, this can be damped by adding a resistor in parallel with the inductor. For the UC1843A-SP design 0.5  $\Omega$  was used as a very conservative value. The resistance needed to damp the peaking can be calculated using the following equations:

$$\omega_o = \sqrt{\frac{2(C_{\text{oCerm}} + C_{\text{oBulk}})}{L_{\text{Filter}} \times C_{\text{oCerm}} \times C_{\text{oBulk}}}} \quad (32)$$

$$\omega_o = \sqrt{\frac{2(19 \mu\text{F} + 1127 \mu\text{F})}{500 \text{ nH} \times 19 \mu\text{F} \times 1127 \mu\text{F}}} = 463 \text{ kHz} \quad (33)$$

$$R_{\text{Filter}} = \frac{R_o \times L_{\text{Filter}} \times (C_{\text{oCerm}} + C_{\text{oBulk}}) - \frac{L_{\text{Filter}}}{\omega_o}}{R_o \times (C_{\text{oCerm}} + C_{\text{oBulk}}) - L_{\text{Filter}} \times C_{\text{oCerm}}} \quad (34)$$

$$R_{\text{Filter}} = \frac{0.5 \times 500 \text{ nH} \times (19 \mu\text{F} + 1127 \mu\text{F}) - \frac{500 \text{ nH}}{463 \text{ kHz}}}{0.5 \times (19 \mu\text{F} + 1127 \mu\text{F}) - 500 \text{ nH} \times 19 \mu\text{F}} = 0.232 \Omega \quad (35)$$

## 2.4.6 Compensation

The poles and zeros of a flyback converter can be found with the following equations:

$$f_{\text{ZESR}} = \frac{1+D}{2\pi \times C_{\text{out}} \times R_{\text{ESR}}} \quad (36)$$

$$f_{\text{ZESR}} = \frac{1+0.5}{2\pi \times 1146 \mu\text{F} \times 0.009 \Omega} = 23.15 \text{ kHz} \quad (37)$$

$$f_{\text{P}} = \frac{1}{2\pi \times C_{\text{out}} \times R_o} \quad (38)$$

$$f_{\text{P}} = \frac{1}{2\pi \times 1146 \mu\text{F} \times 0.5} = 278 \text{ Hz} \quad (39)$$

$$f_{\text{RHPZ}} = \frac{R_{\text{out}} \times (1 - D_{\text{MAX}})^2}{2\pi \times \frac{L_{\text{PR}}}{N_{\text{ps}}^2} \times D_{\text{MAX}}} \quad (40)$$

$$f_{\text{RHPZ}} = \frac{0.5 \times (1 - 0.5)^2}{2\pi \times \frac{21 \mu\text{H}}{3.33^2} \times 0.5} = 21 \text{ kHz} \quad (41)$$

Type IIB compensation was selected to compensate the poles and zeros of the flyback converter. Since the RHPZ of the flyback converter is unable to be compensated, the crossover frequency of the converter should be between one fourth to a whole decade below the RHPZ of the converter. Type IIB compensation has 1 pole and 1 zero to help compensate the converter. The pole from the compensation is suggested to be placed by the RHPZ of the converter and the zero from compensation is suggested to be placed a decade before the expected crossover frequency. Using these guidelines the compensation values for the converter were picked for the converter. For the non-isolated portion of the board this means choosing the value of the compensation resistors and capacitors along these guidelines. For the

UC1901-SP, the compensation was placed using the same guidelines, however the UC1901-SP adds a static gain of 12 to the feedback loop. This increase in gain can be compensated for by dividing the resistor from compensation down and increasing the values of the capacitors by the same amount. This allows for the gain to be controlled in the system without changing the poles and zeros of the system. Optimization is needed for compensation values, and those values can be validated through testing.

### 2.4.7 Sense Resistor and Slope Compensation

The sense resistor is used to sense the ripple current from the transformer as well as shutdown the switching cycle if the peak current of the converter is allowed to get too high. The voltage threshold of the CS pin is around 1 V, thus the equation to find the sense resistor from the peak current is:

$$R_{cs} = \frac{V_{CS \text{ Threshold}} - V_{Slope \text{ Comp Offset}}}{I_{limit}} \quad (42)$$

$$R_{cs} = \frac{1 \text{ V} - 0.1 \text{ V}}{12 \text{ A}} = 0.075 \ \Omega \quad (43)$$

Note that  $I_{limit}$  should be greater than  $I_{PriPeak}$ , and that the voltage offset from the slope compensation will be dependant on the amount of slope compensation in the design. The value of  $0.075 \ \Omega$  for the sense resistance was found to be the optimum value adding some headroom for slope compensation offset of 0.1 V. Slope compensation was implemented with a BJT being turned off and on by the RC pin of the device. The BJT was placed between the REF pin and a resistor divider to the CS pin. The optimum slope compensation value can be found from the following equations after picking a value for the top of the divider:

$$S_c = \frac{V_{out} \times R_{cs} \times G_{cs}}{L_{PRI} \times N_{ps}} \quad (44)$$

$$S_c = \frac{5 \text{ V} \times 0.075 \ \Omega \times 3}{21 \ \mu\text{H} \times 3.33} = 16088 \quad (45)$$

$$S_{osc} = \frac{f_{osc} \times V_{oscpp}}{D_{MIN}} \quad (46)$$

$$S_{osc} = \frac{200 \text{ kHz} \times 1.7 \text{ V}}{0.25} = 1360000 \quad (47)$$

$$R_{csf} = \frac{R_{top}}{\frac{S_{osc}}{S_c} - 1} \quad (48)$$

$$R_{csf} = \frac{11.8 \text{ k}\Omega}{\frac{1360000}{16088} - 1} = 141 \ \Omega \quad (49)$$

The UC1843A-SP design uses a much higher resistor of 1.47 k $\Omega$ , but this is an attempt to be very conservative. Note that the bottom resistor can be used as part of a filter to the CS pin as well, which is implemented in the design using a capacitor near the CS pin. Care was taken such that the RC filter would not filter the switching frequency by having the RC time constant be a decade less than the switching frequency.

### 3 Hardware, Software, Testing Requirements, and Test Results

#### 3.1 Required Hardware and Software

##### 3.1.1 Hardware

A power supply is needed to provide voltage to the input from 20 to 40 V at 4 A. The output load needs to sink up to 10 A of current at 5 V. The output of the device can reach 7 V during start up so the output load must be able to handle up to 7 V for small portions of time.

### 3.2 Testing and Results

#### 3.2.1 Test Setup

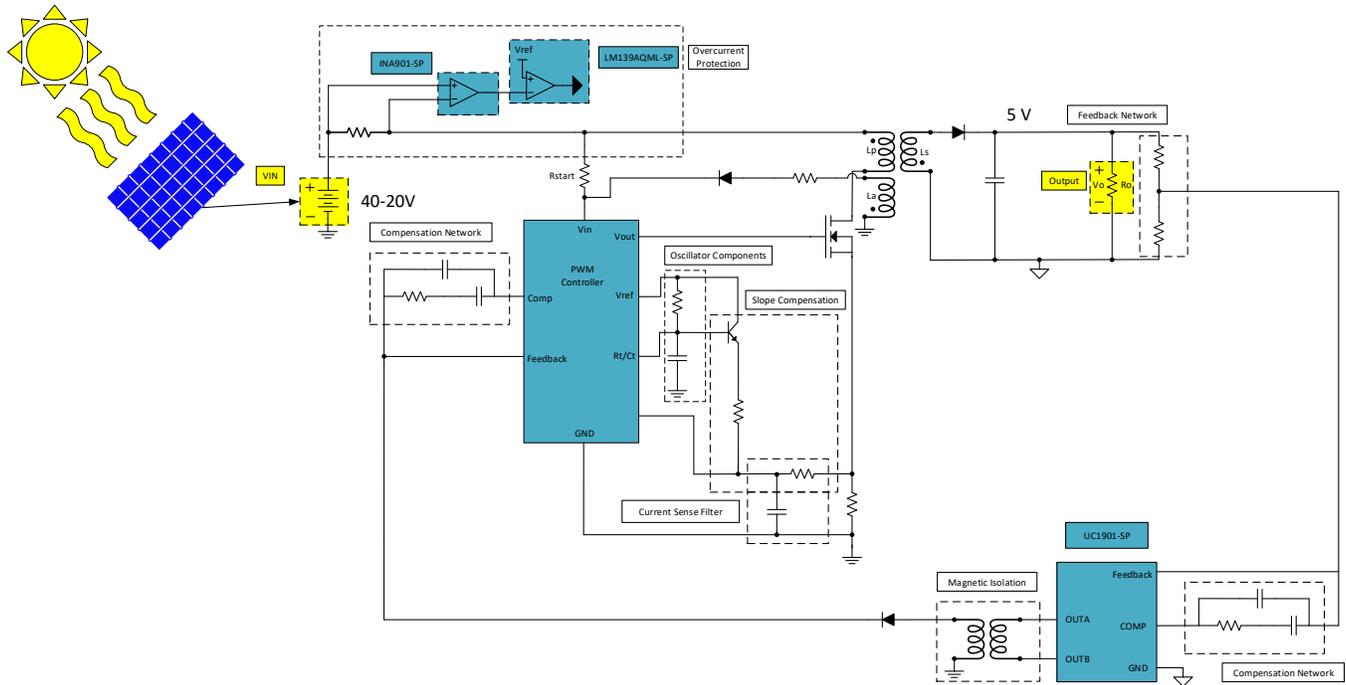


Figure 3. Test Setup

Table 2. Test Parameters

PARAMETER	SPECIFICATIONS
Input Power Supply	20 to 40 VDC
Output Voltage	5 VDC
Output Current	0 to 10 A
Output Current Pre-load	100 mA
Operating Temperature	25°C
Switching Frequency of UC1843A-SP	200 kHz
Switching Frequency of UC1901-SP	1 MHz
Peak Input Current Limit	12 A
Bandwidth	~2 kHz
Phase Margin	~70°

### 3.2.2 Test Results

#### 3.2.2.1 Efficiency

Efficiency measurement was taken after the board was run for 20 minutes at full output load. Values for input voltage, input current, output voltage, and output current were then taken starting at 10 A and decreasing the output load by 1 A down to no load. The output current does not include the 100-mA pre-load that is already included on the board.

**Table 3. Efficiency for 20 V<sub>in</sub>**

V <sub>in</sub>	I <sub>in</sub>	V <sub>out</sub>	I <sub>out</sub>	P <sub>in</sub>	P <sub>out</sub>	Efficiency
19.97	3.2	4.95	9.99	63.9	49.45	0.774
20	2.84	4.95	8.99	56.8	44.50	0.783
20.04	2.49	4.95	7.99	49.9	39.55	0.793
20.07	2.15	4.95	6.99	43.2	34.60	0.802
20.1	1.82	4.95	6	36.6	29.70	0.812
20.13	1.51	4.95	5	30.4	24.75	0.814
20.16	1.2	4.95	4	24.2	19.80	0.818
20.19	0.91	4.95	3	18.4	14.85	0.808
20.21	0.63	4.95	2	12.7	9.90	0.778
20.24	0.33	4.95	1	6.7	4.95	0.741
20.27	0.05	4.95	0	1.0	0.00	0.000

**Table 4. Efficiency for 40 V<sub>in</sub>**

V <sub>in</sub>	I <sub>in</sub>	V <sub>out</sub>	I <sub>out</sub>	P <sub>in</sub>	P <sub>out</sub>	Efficiency
40.39	1.5	4.95	9.99	60.59	49.45	0.816
40.4	1.34	4.95	8.99	54.14	44.50	0.822
40.42	1.19	4.95	7.99	48.10	39.55	0.822
40.43	1.04	4.95	6.99	42.05	34.60	0.823
40.45	0.89	4.95	6	36.00	29.70	0.825
40.46	0.75	4.95	5	30.35	24.75	0.816
40.45	0.61	4.95	4	24.67	19.80	0.802
40.49	0.46	4.95	3	18.63	14.85	0.797
40.5	0.32	4.95	2	12.96	9.90	0.764
40.52	0.18	4.95	1	7.29	4.95	0.679
40.53	0.03	4.95	0	1.22	0.00	0.000

#### 3.2.2.2 Load Regulation

Load regulation was taken after output voltage settled and after decreasing load in 1-A increments.

**Table 5. 20-V<sub>in</sub> Load Regulation**

V <sub>out</sub>	I <sub>out</sub>
4.9495	9.99
4.9498	8.99
4.95	7.99
4.9504	6.99
4.9507	6


**Table 5. 20-V<sub>in</sub> Load Regulation (continued)**

V <sub>out</sub>	I <sub>out</sub>
4.509	5
4.9513	4
4.9516	3
4.952	2
4.9523	1
4.9526	0

**Table 6. 40-V<sub>in</sub> Load Regulation**

V <sub>out</sub>	I <sub>out</sub>
4.9495	9.99
4.9497	8.99
4.95	7.99
4.9503	6.99
4.9507	6
4.951	5
4.9513	4
4.9516	3
4.9519	2
4.9523	1
4.9526	0

**3.2.2.3 Frequency Response**

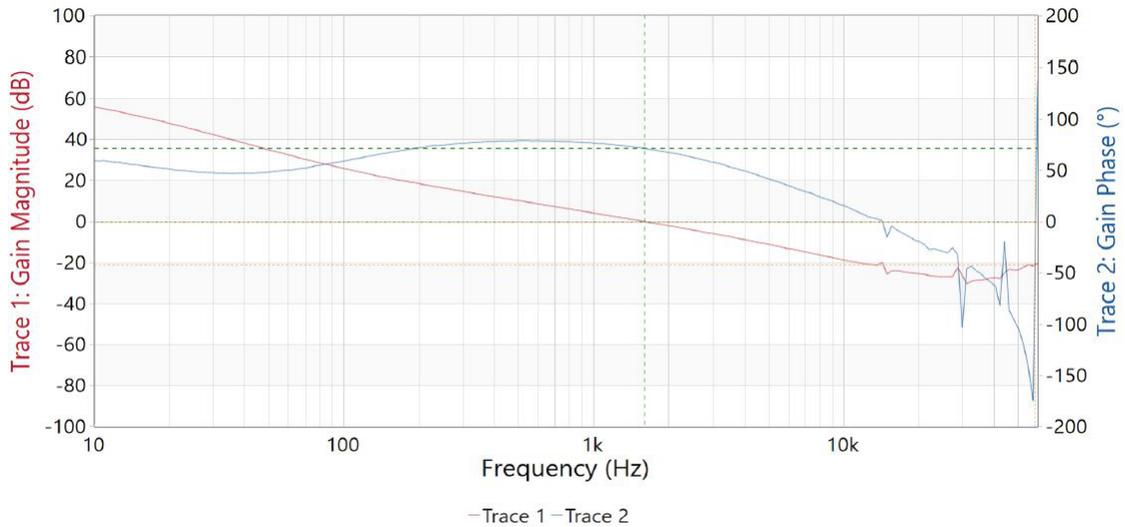


**Figure 6. 20 V<sub>in</sub> Frequency Response**

Frequency response was taken with 10-A output current and 20 V<sub>in</sub>.

**Table 7. Frequency Response Characteristics for 20 V<sub>in</sub>**

PARAMETER	VALUE
Crossover Frequency	1.61 kHz
Phase Margin	71.3°
Phase Crossover	58.9 kHz
Gain Margin	-20.95 dB

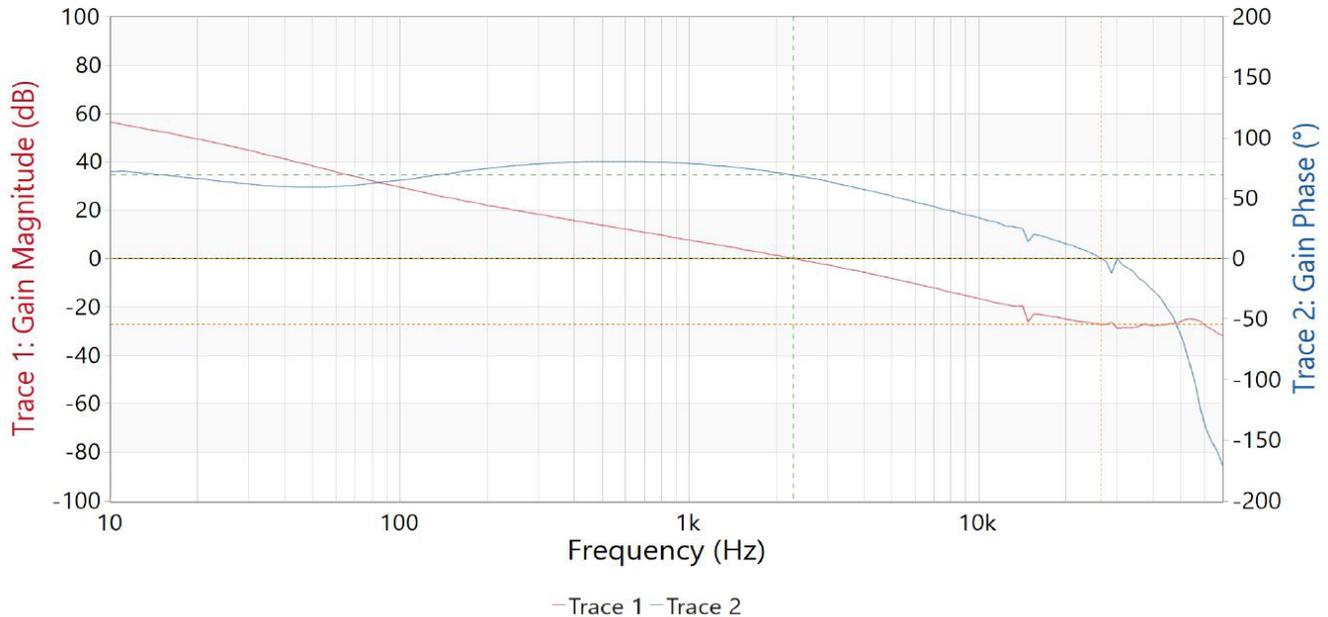


**Figure 7. 40 V<sub>in</sub> Frequency Response**

Frequency response was taken with 10-A output current and 40 V<sub>in</sub>.

**Table 8. Frequency Response Characteristics for 40 V<sub>in</sub>**

PARAMETER	VALUE
Crossover Frequency	2.31 kHz
Phase Margin	68.96°
Phase Crossover	26.6 kHz
Gain Margin	-27.2 dB

**3.2.2.4 Thermal Characteristics**

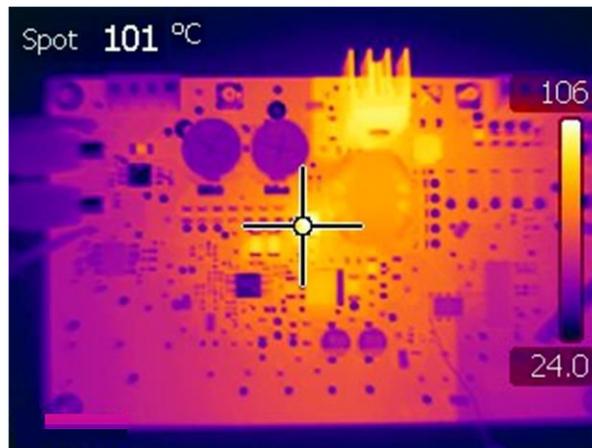


**Figure 8. Thermal Characteristics for 20 V<sub>in</sub>**

Thermal measurement was done with 20 V<sub>in</sub> after 20 minutes of running with full load on the output.

**Table 9. Notable Thermal Values for 20 V<sub>in</sub>**

Area	Temperature
Zener Diode Clamp (D4)	101°C
Output Diode (D2)	92.3°C
Output Filter Inductor (L1)	77.7°C
Main Switching MOSFET (Q1)	71.8°C
Sense Resistors (R17 and R18)	72.7°C
Transformer (T1)	61.7°C

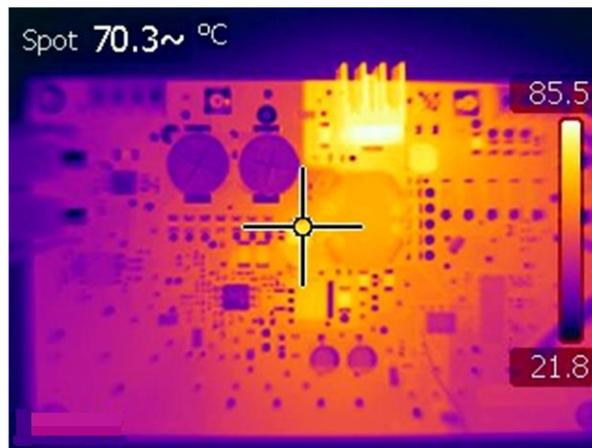

**Figure 9. Thermal Characteristics for 40 V<sub>in</sub>**

Thermal measurement was done with 40 V<sub>in</sub> after 20 minutes of running with full load on the output.


**Table 10. Notable Thermal Values for 40 V<sub>in</sub>**

Area	Temperature
Zener Diode Clamp (D4)	70.3°C
Output Diode (D2)	84.9°C
Output Filter Inductor (L1)	73.8°C


**Table 10. Notable Thermal Values for 40 V<sub>in</sub> (continued)**

Area	Temperature
Main Switching MOSFET (Q1)	61.4°C
Sense Resistors (R17 and R18)	54.7°C
Transformer (T1)	59.8°C

### 3.2.2.5 Output Voltage Ripple

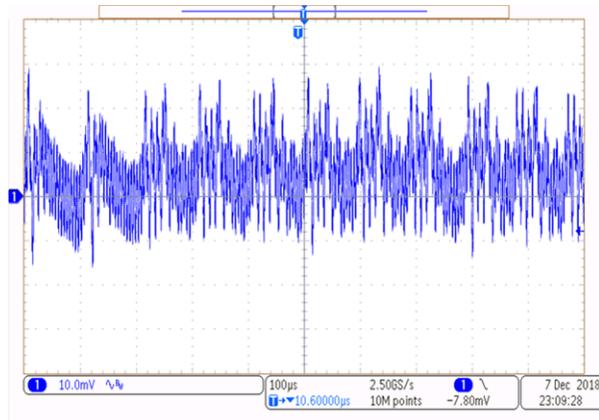

**Figure 10. Output Voltage Ripple 20 V<sub>in</sub>**

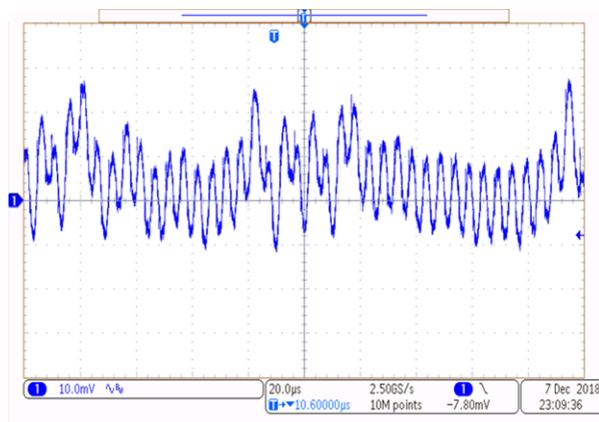

**Figure 11. Output Voltage Ripple 20 V<sub>in</sub> With Smaller Time Scale**

Output voltage ripple was taken with 20 V<sub>in</sub> and a fully loaded output. Ripple from the UC1843A-SP can be seen in [Figure 10](#) and ripple from the UC1901-SP can be seen in [Figure 11](#).

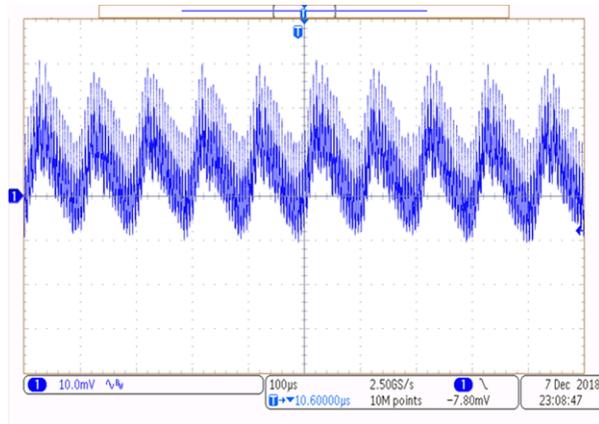


Figure 12. Output Voltage Ripple 40 V<sub>in</sub>

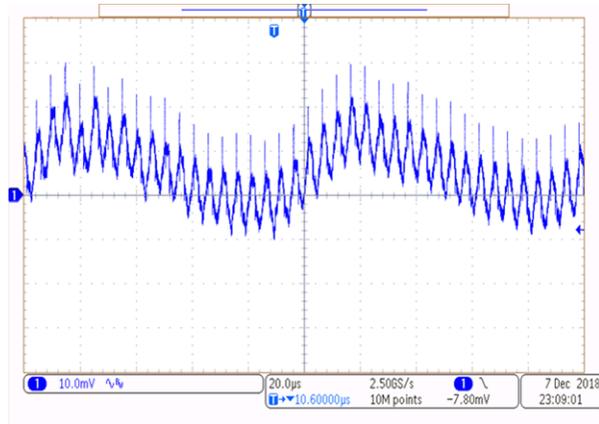


Figure 13. Output Voltage Ripple 40 V<sub>in</sub> With Smaller Time Scale

Output voltage ripple was taken with 20 V<sub>in</sub> and a fully loaded output. Ripple from the UC1843A-SP can be seen in Figure 12 and ripple from the UC1901-SP can be seen in Figure 13. The additional ripple from the output can be filtered out by POL converters that are supplied from the 5-V rail.


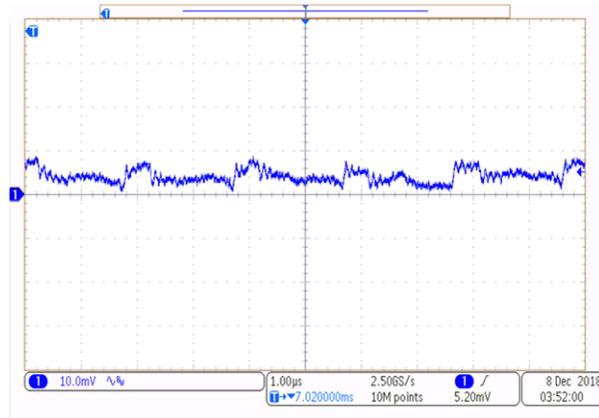



Figure 14. Output Voltage Ripple of TPS50601A-SP EVM Supplied From UC1843A-SP

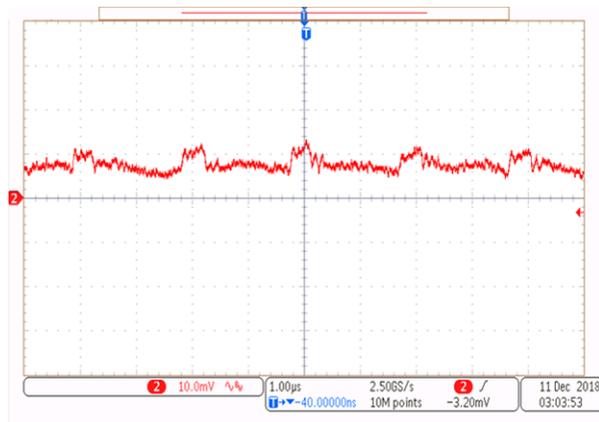


**Figure 15. Output Voltage Ripple of TPS50601A-SP EVM Supplied From 5-V Power Supply**

For the figure displayed in Figure 14, the UC1843A-SP and UC1901-SP design supplied a TPS50601A-SP EVM using a 40-V rail. For the figure displayed in Figure 15, the TPS50601A-SP EVM was supplied using a 5-V lab power supply. The additional ripple added to the line by the UC1843A-SP and the UC1901-SP had a negligible impact on the output ripple of the TPS50601A-SP EVM.

### 3.2.2.6 Load Step

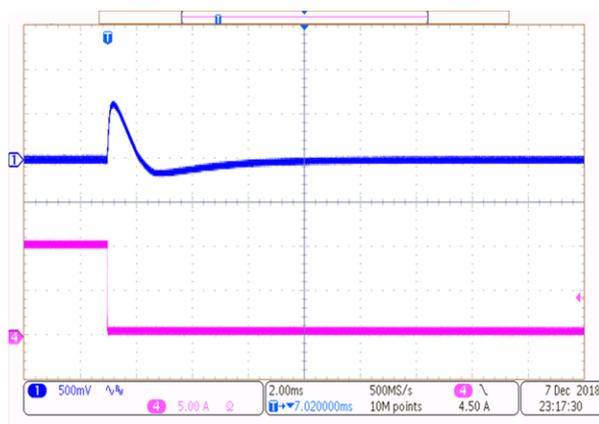


**Figure 16. Partial Load Step Down With 20 V<sub>in</sub>**

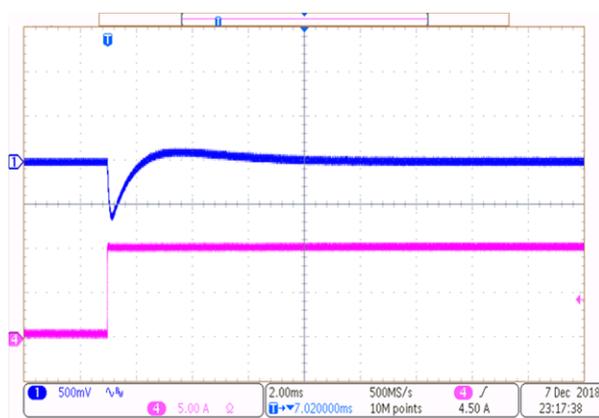


**Figure 17. Partial Load Step Up With 20 V<sub>in</sub>**

For tests shown in [Figure 16](#) and [Figure 17](#), 20 V was applied to the input and a load step was applied to the output. The load step applied was from 0.6 A to 10 A and 10 A to 0.6 A. Note that those currents do not include the 0.1-A pre-load. The 0.6 A was found to be the minimum output current in order to avoid light load conditions with the design.

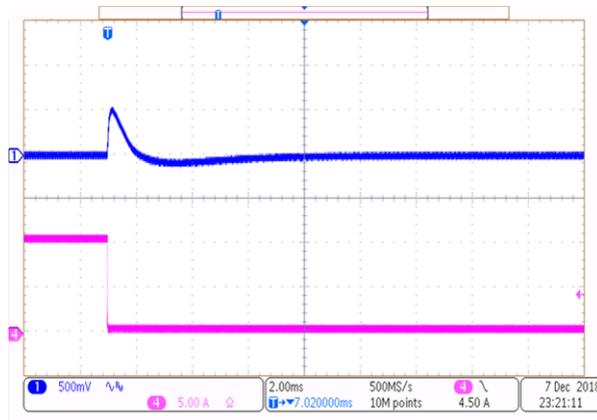

**Figure 18. Partial Load Step Down With 40 V<sub>in</sub>**

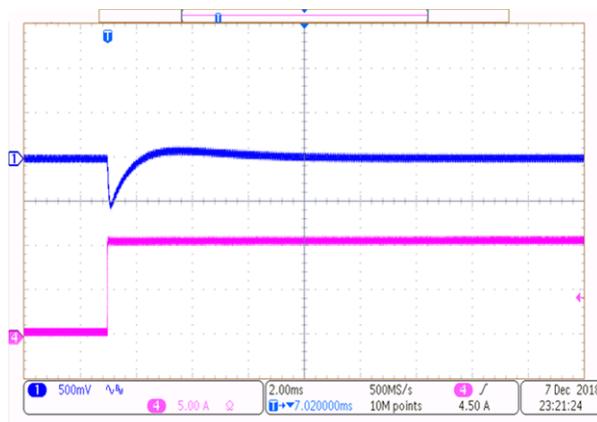

**Figure 19. Partial Load Step Up With 40 V<sub>in</sub>**

For tests shown in [Figure 18](#) and [Figure 19](#), 40 V was applied to the input and a load step was applied to the output. The load step applied was from 0.5 A to 10 A and 10 A to 0.5 A. Note that those currents do not include the 0.1-A pre-load. The 0.5 A was found to be the minimum output current in order to avoid light load conditions with the design.

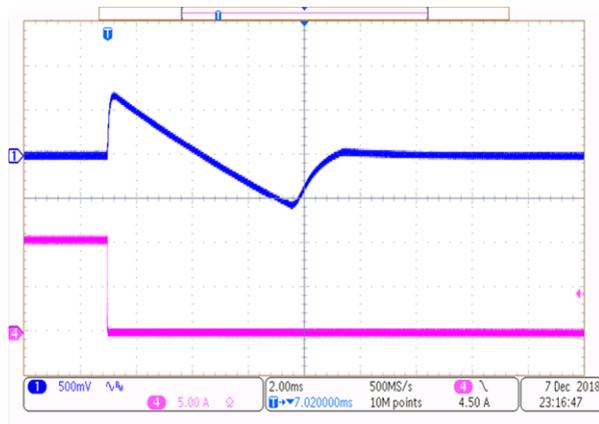


Figure 20. Load Step Down With 20 V<sub>in</sub>

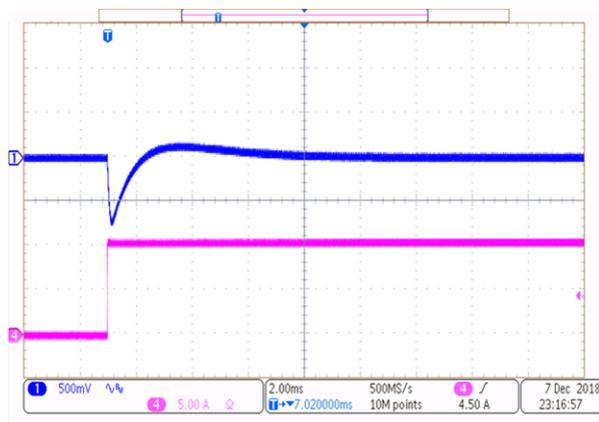


Figure 21. Load Step Up With 20 V<sub>in</sub>

For tests shown in Figure 20 and Figure 21, 20 V was applied to the input and a load step was applied to the output. The load step applied was from 0 A to 10 A and 10 A to 0 A. Note that those currents do not include the 0.1-A pre-load.

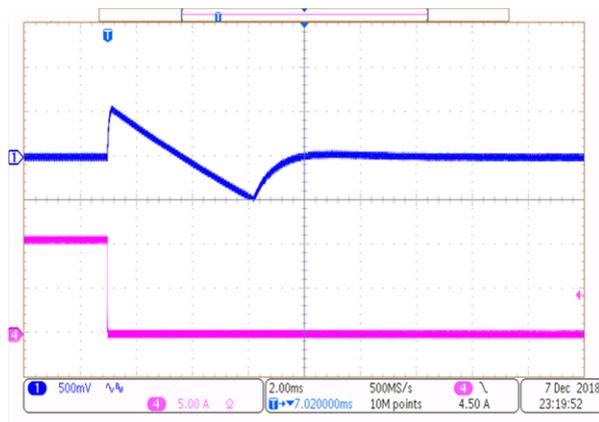


Figure 22. Load Step Down With 40 V<sub>in</sub>

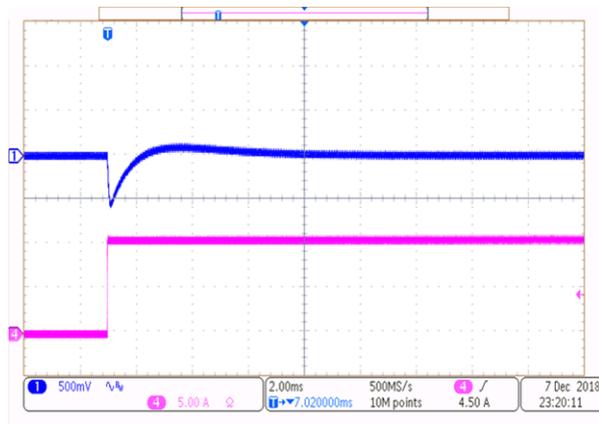


Figure 23. Load Step Up With 40 V<sub>in</sub>

For tests shown in Figure 22 and Figure 23, 40 V was applied to the input and a load step was applied to the output. The load step applied was from 0 A to 10 A and 10 A to 0 A. Note that those currents do not include the 0.1-A pre-load.

### 3.2.2.7 Start-up

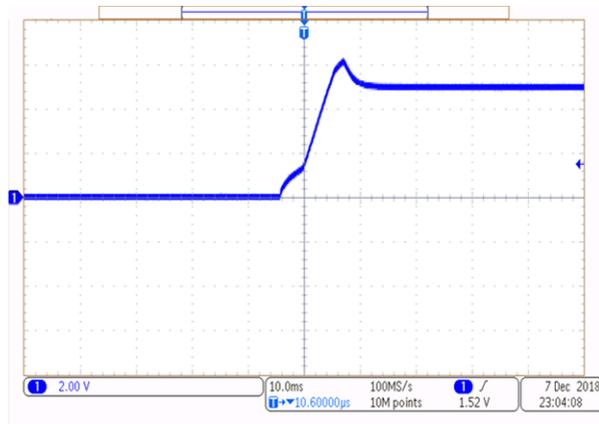


Figure 24. Start-up 20 V<sub>in</sub> With Fully Loaded Output



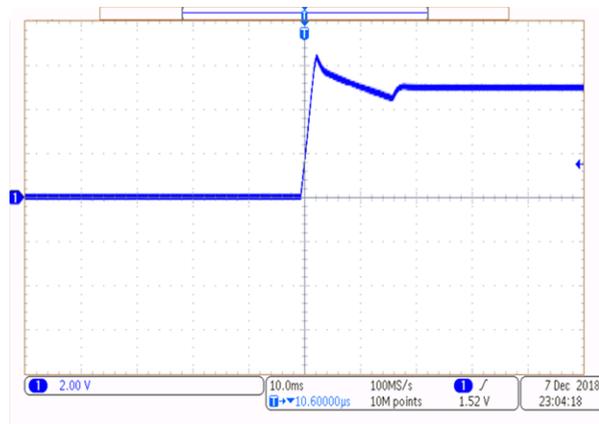


Figure 25. Start-up 20 V<sub>in</sub> With No Load on Output

For tests shown in [Figure 24](#) and [Figure 25](#), 20 V was applied to the input from 0 V initially. The output was either loaded with 0 A on the output or 10 A. Note that those currents do not include the 0.1-A pre-load.

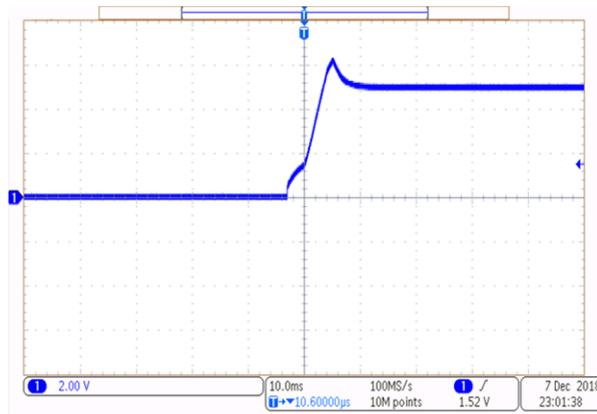

**Figure 26. Start-up 40 V<sub>in</sub> With Fully Loaded Output**

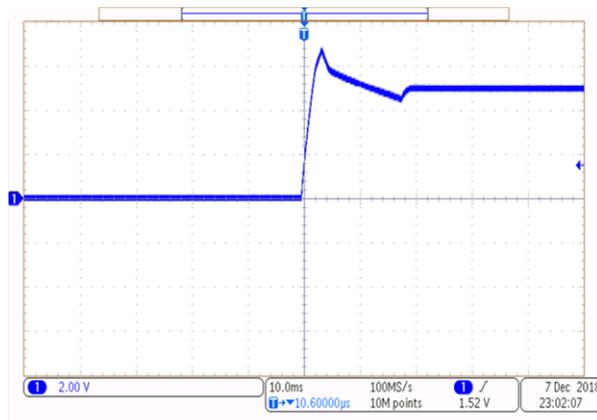

**Figure 27. Start-up 40 V<sub>in</sub> With No Load on Output**

For tests shown in [Figure 26](#) and [Figure 27](#), 40 V was applied to the input from 0 V initially. The output was either loaded with 0 A on the output or 10 A. Note that those currents do not include the 0.1-A pre-load.

3.2.2.8 Shutdown

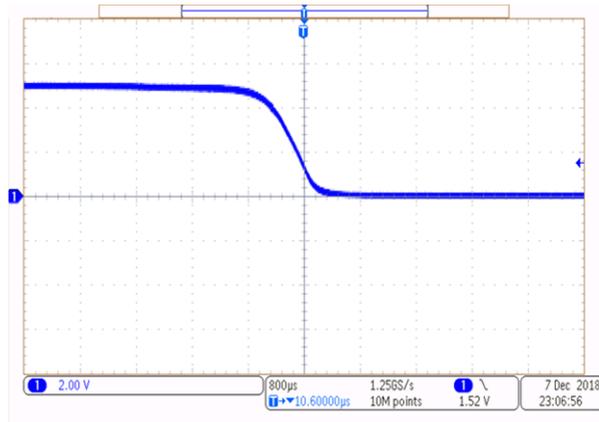


Figure 28. Start-up 20 V<sub>in</sub> With Fully Loaded Output

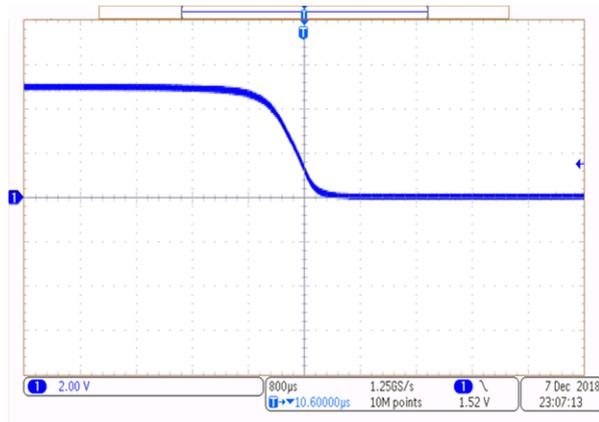


Figure 29. Start-up 40 V<sub>in</sub> With Fully Loaded Output

For tests shown in Figure 28 and Figure 29, 20 V or 40 V was applied to the input and then disconnected. The output was loaded with 10 A on the output. Note that those currents do not include the 0.1-A pre-load.

3.2.2.9 Component Stresses


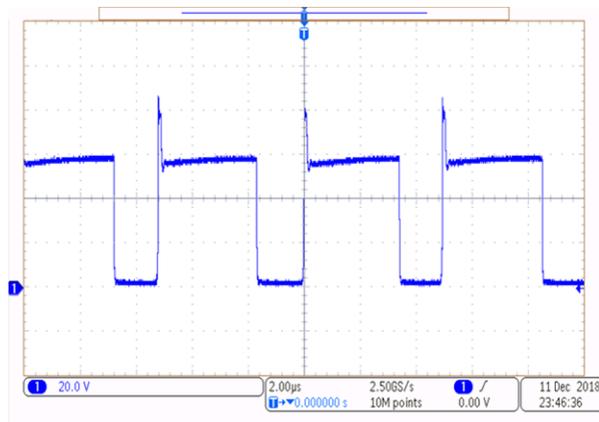


Figure 30. Voltage Stress on Main Switching MOSFET (Q1)

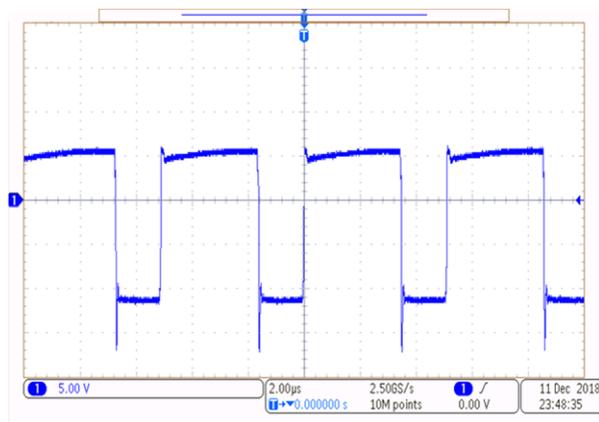

**Figure 31. Output Diode Stress (D2)**

For the test in [Figure 30](#) and [Figure 31](#), 40 V was applied to the input and 10 A was drawn from the output. For the output diode stress, the voltage was measured with respect to ground so the output voltage would have to be added to show the true stress on the output diode.

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-070002](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-070002](#).

### 4.3 PCB Layout Recommendations

Make all of the power (high current) traces as short, direct, and thick as possible. It is good practice on a standard PCB to make the traces an absolute minimum of 15 mils (0.381 mm) per ampere. The inductor, output capacitors, and output diode should be as close as possible to each other. This helps reduce the EMI radiated by the power traces due to the high-switching currents through them. This also reduces lead inductance and resistance, which in turn reduces noise spikes, ringing, and resistive losses that produce voltage errors. The grounds of the IC, input capacitors, output capacitors, and output diode (if applicable) should be connected close together directly to a ground plane. It would also be a good idea to have a ground plane on both sides of the PCB. This reduces noise by reducing ground loop errors. For multi-layer boards with more than two layers, a ground plane can be used to separate the power plane (where the power traces and components are) and the signal plane (where the feedback and compensation and components are) for improved performance. On multi-layer boards, vias are required to connect traces and different planes. Arrange the components so that the switching current loops curl in the same direction. Due to the way switching regulators operate, there are two power states: one state when the switch is on and one when the switch is off. During each state there is a current loop made by the power components that are currently conducting. Place the power components so that during each of the two states the current loop is conducting in the same direction. This prevents magnetic field reversal caused by the traces between the two half-cycles and reduces radiated EMI.

#### 4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-070002](#).

### 4.4 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA-070002](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-070002](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-070002](#).

## 5 Related Documentation

1. [Using The DRV3204EVM To Evaluate The DRV3203-Q1 application note](#), SLVA559
2. [INA901-SP Radiation Hardened, -16-V to 80-V Common Mode, Unidirectional Current-Shunt Monitor data sheet](#), SBOS938
3. [UC1843A-SP QML Class V, Radiation Hardened Current-Mode PWM Controller data sheet](#), SLUSCI6

## 5.1 Trademarks

E2E is a trademark of Texas Instruments.

Altium Designer is a registered trademark of Altium LLC or its affiliated companies.

All other trademarks are the property of their respective owners.

## 5.2 Third-Party Products Disclaimer

TI'S PUBLICATION OF INFORMATION REGARDING THIRD-PARTY PRODUCTS OR SERVICES DOES NOT CONSTITUTE AN ENDORSEMENT REGARDING THE SUITABILITY OF SUCH PRODUCTS OR SERVICES OR A WARRANTY, REPRESENTATION OR ENDORSEMENT OF SUCH PRODUCTS OR SERVICES, EITHER ALONE OR IN COMBINATION WITH ANY TI PRODUCT OR SERVICE.

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from A Revision (March 2019) to B Revision</b>	<b>Page</b>
• Changed title from "50-W flyback space reference design with overcurrent limit function" to "20- to 40-V <sub>IN</sub> , 50-W Space-Grade Isolated-Flyback DC-DC Over Current Protection Reference Design" .....	1
• Changed Description paragraph .....	1
• Added UC1843A-SP link .....	1
• Deleted Space satellite isolated power supplies; Radiation hardened applications; and Space satellite payloads applications.....	1
• Added Command and Data Handling; Satellite Electric Power System (EPS); Optical Imaging Payload; Radar Imaging Payload, and Communications Payload application links.....	1

---

Changes from Original (December 2018) to A Revision	Page
• Changed UCC1843-SP to UC1843-SP .....	6
• Changed UCC1843-SP to UC1843-SP .....	7
• Changed the Test Setup image.....	11

---

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated