

## Design Guide: TIDA-020014

# HEV/EV Traction Inverter Power Stage With 3 Types of IGBT/SiC Bias-Supply Solutions Reference Design



### Description

This reference design presents a traction inverter single-phase power stage with three 12-V car battery inputs, 4.2-W bias supply solutions for hybrid electric vehicle and electric vehicle (HEV/EV) systems. All bias-supply solutions accept a wide input range of 4.5 V to 42 V DC from a 12-V car battery, and generate outputs as +15 V, -8 V or +20 V, -4 V configurable and up to 180-mA output current. The power stage includes the isolated gate drivers with 5.7-kV<sub>RMS</sub> reinforced isolation and designed in 100-mm × 62-mm form factor fitting on SiC/IGBT half bridge modules. It includes isolated DC bus sensing, isolated temperature sensing, logic shoot-through protection and diagnostic features. Apart from startup, efficiency, load regulation tests under low voltage input, all bias supplies are also connected with power stage and IGBT module for CMTI, double pulse, and short-circuit tests under high voltages.

### Resources

<a href="#">TIDA-020014</a>	Design Folder
<a href="#">TIDA-020015</a>	Design Folder
<a href="#">LM5180-Q1</a>	Product Folder
<a href="#">TPS40210-Q1</a>	Product Folder
<a href="#">LM46002-Q1</a>	Product Folder
<a href="#">SN6505B-Q1</a>	Product Folder
<a href="#">ISO5852S-Q1</a>	Product Folder
<a href="#">AMC1311-Q1, AMC1301-Q1</a>	Product Folder

### Features



- Traction-inverter, single-phase, power-stage design includes dual-channel isolated gate driver, isolated DC bus voltage sensing, and isolated temperature sensing.
- Three types of SiC/IGBT bias-supply solutions for IGBT/SiC isolated gate drivers
- Wide- $V_{IN}$  converters over the input voltage of 4.5-V to 42-V DC
- Output configurable as +15 V, -8 V or +20 V, -4 V at loads up to 180 mA for driving Si IGBT and SiC MOSFET modules
- Protection for clamping high-voltage conducted transients to safe levels for downstream circuitry
- Primary-side regulation with no optocoupler for extended lifetime and small form factor

### Applications

- [Inverter and motor control](#)
- [Onboard \(OBC\) and wireless charger](#)
- [Gasoline and diesel engine platform](#)
- [DC/DC converter](#)



ASK Our E2E™ Experts

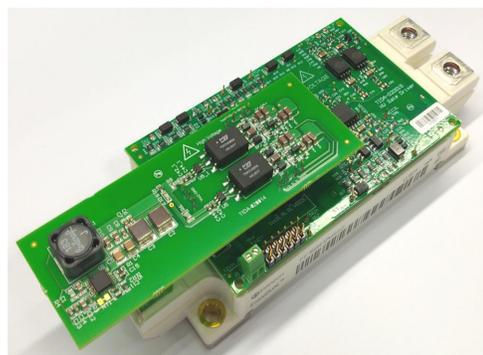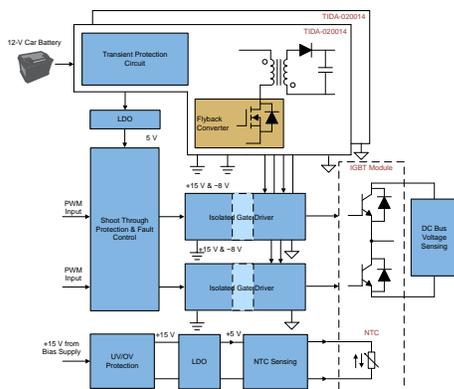



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.


## 1 System Description

This reference design presents an HEV, EV traction inverter, single-phase power-stage with three bias-supply solutions. The supply solutions power a single channel of the IGBT/SiC isolated gate driver, and could be driven directly from the 12-V car battery with a wide input range of 4.5-V to 42-V DC. The bias supplies provide +15-V and –8-V isolated rails up to 180-mA output current. The architecture follows:

- Bias supply solution 1: Compact, primary-side regulated (PSR) flyback converter (based on the LM5180-Q1 device) with integrated switch and internal compensation.
- Bias supply solution 2: Low-cost, primary-side regulated (PSR) flyback converter (based on the TPS40210-Q1 device) with external switch and external compensation.
- Bias supply solution 3: Two stage approach of using two buck converters in redundancy as the front stage, and a push-pull transformer driver supply as the following stage (based on the LM46002-Q1 and SN6505-Q1 devices).

This design targets at powering IGBT/SiC isolated gate drivers implemented in hybrid electric vehicle and electric vehicle (HEV/EV) systems. [Figure 1](#) shows a traction inverter reference diagram where the positions of the TIDA-020014 design are highlighted. The isolated gate drivers galvanically isolate the high-voltage power switches from the low-voltage control signals. Each isolated gate driver requires a pair of positive-supply and negative-supply rails to fully turn on and off the IGBT/SiC power modules.

Figure 1. HEV/EV Traction Inverter Reference Block Diagram and the Position of TIDA-020014

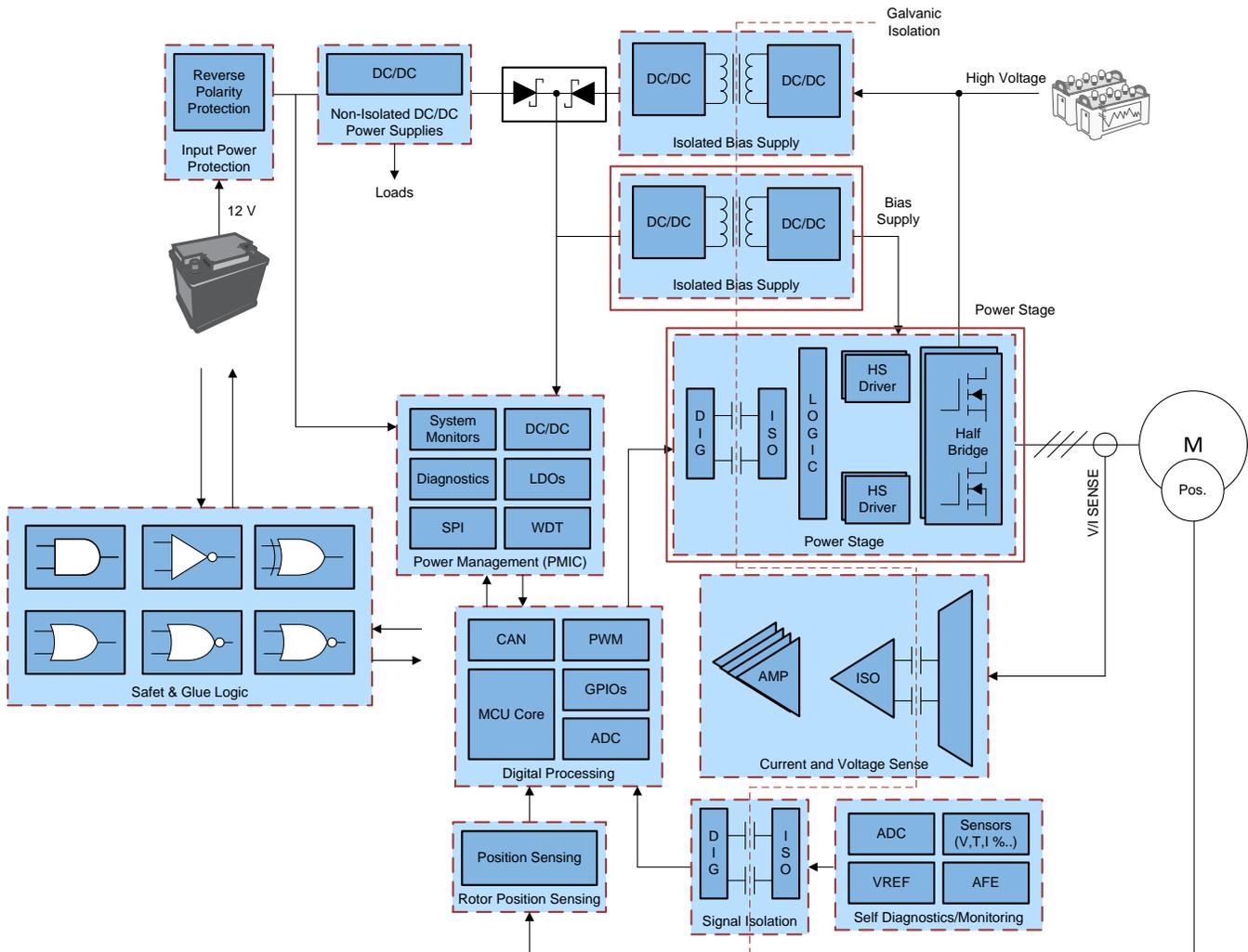

Do not leave the device powered when unattended.



High voltage! There are accessible high voltages present on the board. Electric shock is possible. The board operates at voltages and currents that may cause shock, fire, or injury if not properly handled. Use the equipment with necessary caution and appropriate safeguards to avoid injury or damage to property. For safety, use of isolated equipment with overvoltage and overcurrent is highly recommended. TI considers it the user's responsibility to confirm that the voltages and isolation requirements are identified and understood before energizing the board or simulation. When energized, do not touch the design or components connected to the design.



Hot surface! Contact may cause burns. Do not touch! Some components may reach high temperatures > 55°C when the board is powered on. The user must not touch the board at any point during operation or immediately after operating, as high temperatures may be present.

## 1.1 Key System Specifications

Table 1 details the key system specifications of the bias supplies.

**Table 1. Key System Specifications**

PARAMETER		COMMENTS	MIN	TYP	MAX	UNIT
System Input						
$V_{IN}$	Input voltage	Battery voltage range (DC)	4.5	13.5	42	V
$F_{SW}$	Switching frequency	Solution 1	10	350	350	kHz
$F_{SW}$	Switching frequency	Solution 2		100		kHz
$F_{SW}$	Switching frequency	Solution 3		450		kHz
Output Voltage						
$V_{OUT1}$		System output voltage, across load	+13	+15	+17	V
$V_{OUT2}$		System output voltage, across load	-6.5	-8	-8.2	V
Output Current						
$I_{OUT}$		Maximum output current. Drawing more than 180 mA is not recommended for thermal reasons. See the Thermal Images testing to see the temperature rise at full load		180		mA


## 2 System Overview

### 2.1 Block Diagram

#### 2.1.1 Bias Supply Solution 1

Figure 2 shows the system implementation block diagram of the bias supply solution 1. The three-phase traction inverter requires six IGBT/SiC switches through isolated gate drivers that galvanically isolate the high-voltage gate driver outputs from the low-voltage PWM signals. Hence six times of this design are required to power all six gate drivers: each power supply is connected to each and every gate driver, respectively. The input can be fed directly from a 12-V car battery. The output voltage levels can be configured to the required voltage levels for driving IGBT or SiC MOSFETs.


Figure 2. System Implementation Block Diagram of Bias Supply Solution 1

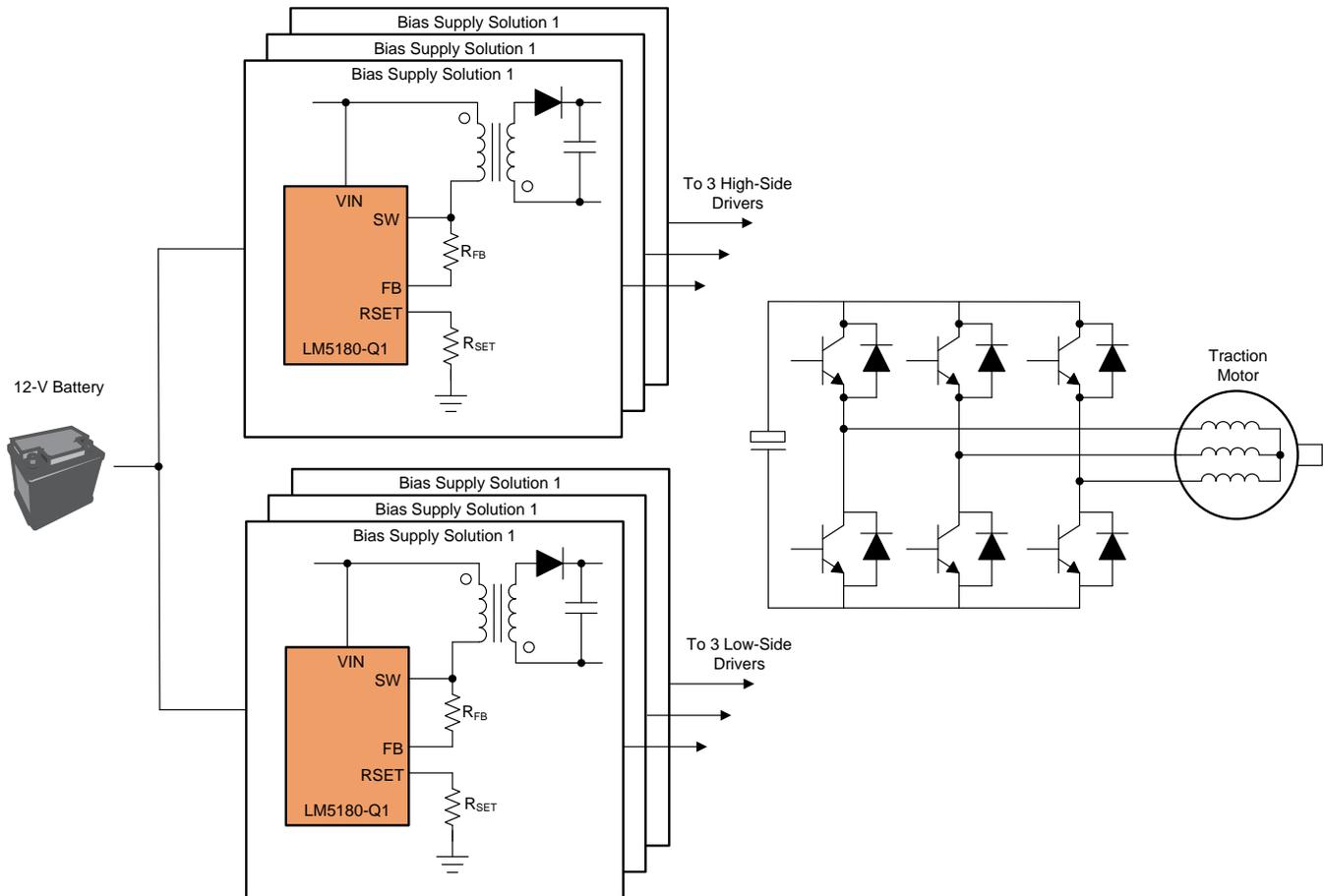

#### 2.1.2 Bias Supply Solution 2


Figure 3 shows the system implementation block diagram of the bias supply solution 2. A flyback converter with an external MOSFET and compensation network has been used. The same traction inverter block diagram is shown.

Figure 3. System Implementation Block Diagram of Bias Supply Solution 2

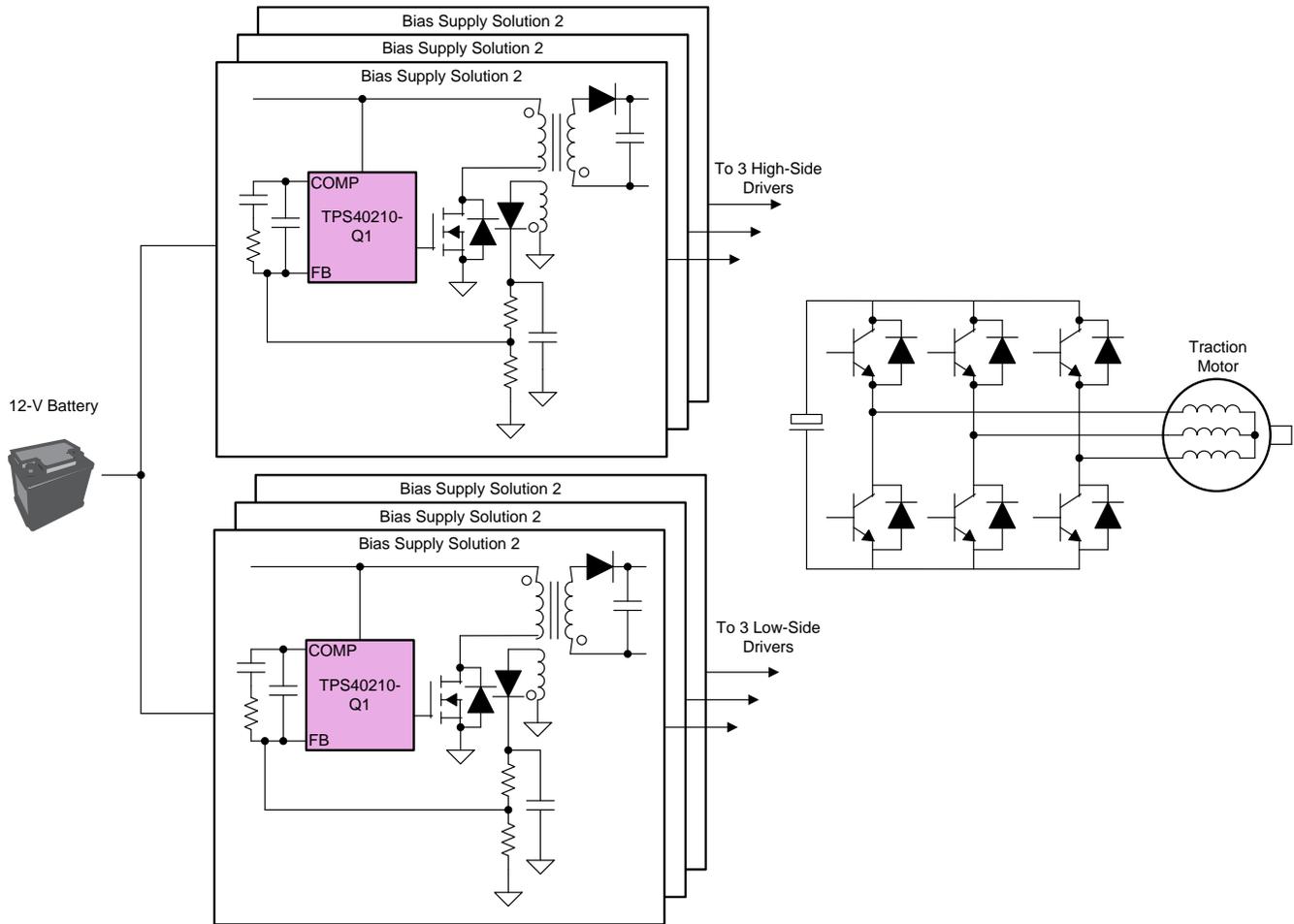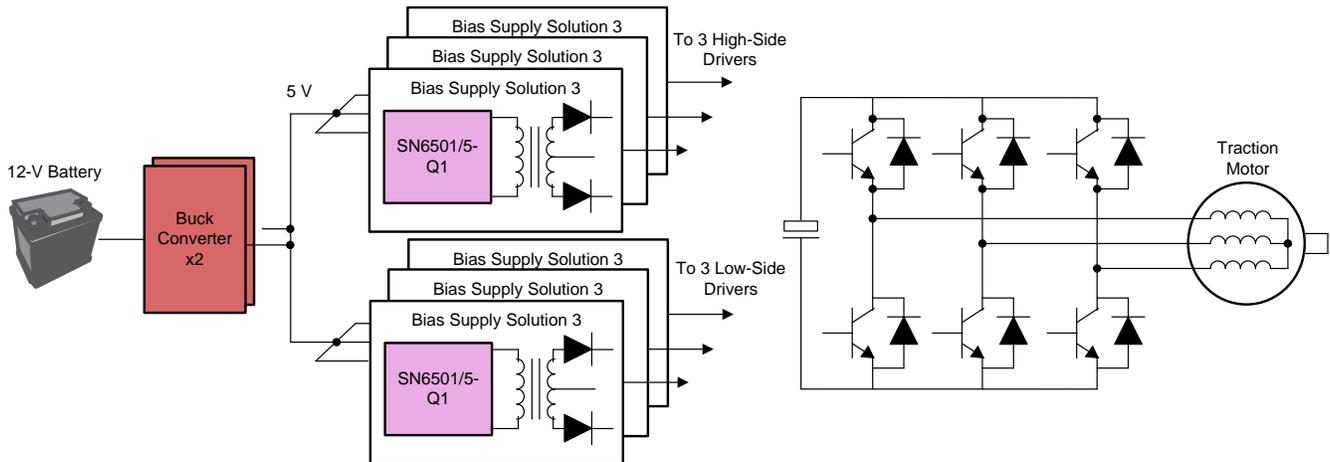

### 2.1.3 Bias Supply Solution 3

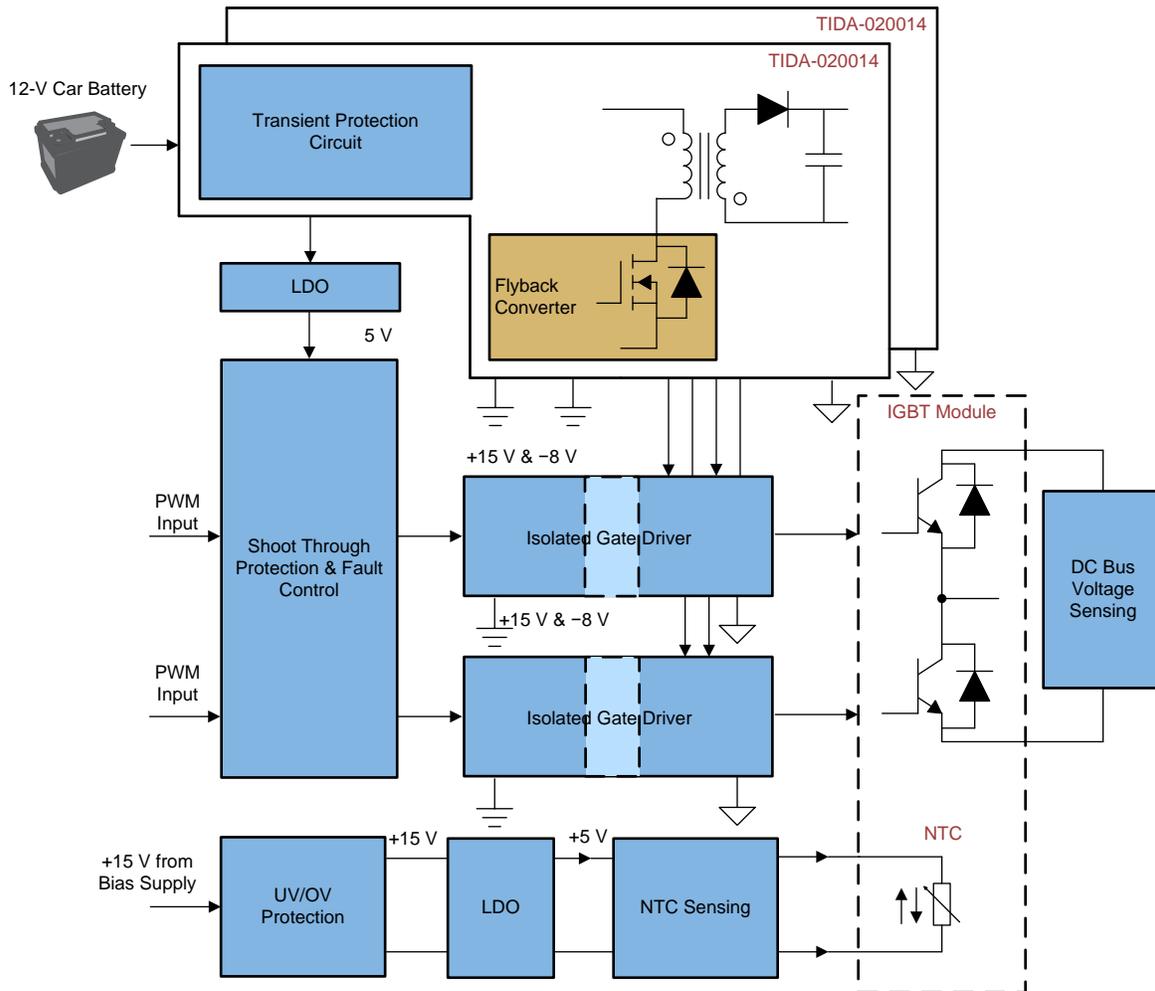
Figure 4 shows the system implementation block diagram of the bias supply solution 3 which is the two-stage architecture in redundancy for an increased level of safety. Two buck converters are connected in parallel and convert the 12-V battery input to 5-V output. Then the 5-V rail is fed into the push-pull transformer driver supply where the isolation is provided. The same traction inverter block diagram is shown.

**Figure 4. System Implementation Block Diagram of Bias Supply Solution 3**


### 2.1.4 Inverter Power Stage Block Diagram

The power stage board is designed in a compact form factor. It includes gate drive, bias voltages, protection, and diagnostic needed for half-bridge SiC MOSFET and Si IGBT power modules housed in 150-mm × 62-mm × 17-mm packages. It consists of the high-side and low-side isolated gate drivers, the DC bus voltage sensing, the shoot-through protection and fault control, the high voltage input LDO, and the NTC sensing circuit. The connectors allow for plug-in connection to the gate drivers for easy evaluation. [Figure 5](#) shows the power stage board block diagram. The features are listed as follows:

- 20-A peak split sink and source drive current from external buffer to optimize turn on and turn off switching time
- Robust noise-immune solution with CMTI >100 V/ns
- Supports 5 kV<sub>RMS</sub> reinforced isolation for input rail up to 1700 V
- Programmable short-circuit sensing and soft turn-off protection with the de-saturation circuit
- 2-A active Miller clamp
- Output short-circuit clamp
- Fault feedback with reset
- NTC temperature and DC bus voltage sensing

**Figure 5. TIDA-020014 Power Stage Block Diagram**


## 2.2 Highlighted Products

The TIDA-020014 reference design features the following Texas Instruments devices.

### 2.2.1 LM5180-Q1

The LM5180-Q1 device is a primary-side regulated (PSR) flyback converter with high efficiency over a wide input voltage range of 4.5 V to 65 V. The isolated output voltage is sampled from the primary-side flyback voltage, eliminating the need for an optocoupler, voltage reference, or third winding from the transformer for output voltage regulation. The high level of integration results in a simple, reliable and high-density design with only one component crossing the isolation barrier. Boundary conduction mode (BCM) switching enables a compact magnetic solution and better than  $\pm 1\%$  load regulation and line regulation performance. An integrated 100-V power MOSFET provides output power up to 7 W with enhanced headroom for line transients.

### 2.2.2 TPS40210-Q1

The TPS40210-Q1 is a peak current-mode control low-side controller with a built-in 400-mA gate driver designed to drive N-channel MOSFETs at a fixed frequency. The frequency is adjustable from 35 kHz to 1000 kHz. A small size combined with complete functionality makes the part both versatile and easy to use. The controller uses a low-value current-sensing resistor in series with the source connection of the power MOSFET to detect switching current. When the voltage drop across this resistor exceeds 150 mV, the part enters a hiccup fault mode with a time period set by the external soft-start capacitor.

### 2.2.3 LM74700-Q1

The LM74700-Q1 device is an ideal diode controller device that operates in conjunction with an external N-channel MOSFET as an ideal diode rectifier for low loss reverse polarity protection. The wide supply input range of 3 to 65 V allows control of many popular DC bus voltages. The device can withstand and protect the loads from negative supply voltages down to -65 V. With a low  $R_{DS(on)}$  external N-channel MOSFET, a very low forward voltage drop can be achieved while minimizing the amount of power dissipated in the MOSFET.

### 2.2.4 TPS3700-Q1

The TPS3700-Q1 device is a wide-supply voltage window comparator which operates over a 1.8-V to 18-V range. The device has two high-accuracy comparators with an internal 400-mV reference and two open-drain outputs rated to 18 V for overvoltage and undervoltage detection. The TPS3700-Q1 device can be used as a window comparator or as two independent voltage monitors; the monitored voltage can be set with the use of external resistors.

### 2.2.5 LM46002-Q1

The LM46002 regulator is an easy to use synchronous step-down DC/DC converter that operates from 3.5-V to 60-V supply voltage. It is capable of delivering up to 2 A DC load current with exceptional efficiency and thermal performance in a very small solution size. An extended family is available in 0.5-A and 1.0-A load options in pin-to-pin compatible packages.

Optional features are included for more comprehensive system requirements, including power-good flag, precision enable, and synchronization to external clock, extendable soft-start time, and output voltage tracking. These features provide a flexible and easy to use platform for a wide range of applications. Protection features include over temperature shutdown, VCC undervoltage lockout (UVLO), cycle-by-cycle current limit, and short-circuit protection with hiccup mode.

### 2.2.6 SN6505-Q1

The SN6505-Q1 device is a monolithic push-pull transformer driver, specifically designed for small factor, isolated power supplies. It drives a low profile, center-tapped transformer from a 3.3-V or 5-V DC power supply. The SN6505x-Q1 consists of an oscillator followed by a gate drive circuit that provides the complementary output signals to drive ground referenced N-channel power switches. The device includes two 1-A Power-MOSFET switches to ensure start-up under heavy loads. The internal protection features include a 1.7-A current limiting, under-voltage lockout, thermal shutdown, and break-before-make circuitry.

### 2.2.7 TL431-Q1

The TL431-Q1 device is a three-pin adjustable shunt regulator with specified thermal stability over applicable automotive temperature ranges. The TL431-Q1 can be used as a single voltage reference, error amplifier, voltage clamp, or comparator with integrated reference. The TL431-Q1 consists of an internal reference and amplifier that outputs a sink current based on the difference between the reference pin and the virtual internal pin. The sink current is produced by the internal Darlington pair, which allows this device to sink a maximum current of 100 mA.

### 2.2.8 ISO5852S-Q1

The ISO5852S-Q1 device is a reinforced, isolated gate driver that is capable of driving a 1200-V IGBT module with current ratings from 50 A to 200 A. The device offers:

- High isolation ratings in the industry
  - 5.7-kV<sub>RMS</sub> isolation voltage
  - 8000-Vpk Maximum transient isolation voltage
  - 2121-Vpk Maximum transient isolation voltage
- Split outputs
- 2.5-A Peak source and 5-A peak sink currents
- 100-kV/ $\mu$ s Minimum common-mode transient

- The device also includes the Miller clamp, soft turnoff, UVLO, DESAT detect, fault feedback, and Ready-status feedback features.

### 2.2.9 AMC1301-Q1

The AMC1301 is a fully-differential, precision, isolated amplifier. The input stage of the device consists of a fully-differential amplifier that drives a second-order, delta-sigma ( $\Delta\Sigma$ ) modulator. The modulator uses the internal voltage reference and clock generator to convert the analog input signal to a digital bit stream. The drivers transfer the output of the modulator across the isolation barrier that separates the high-side and low-side voltage domains.

### 2.2.10 AMC1311-Q1

The AMC1311-Q1 is a precision, isolated amplifier with an output separated from the input circuitry by an isolation barrier that is highly resistant to magnetic interference. This barrier is certified to provide reinforced galvanic isolation of up to 7 kV peak according to VDE V 0884-11 and UL1577. Used in conjunction with isolated power supplies, this isolated amplifier separates parts of the system that operate on different common-mode voltage levels and protects lower-voltage parts from damage. The high-impedance input of the AMC1311-Q1 is optimized for connection to high-voltage resistive dividers or other voltage signal sources with high output resistance.

### 2.2.11 TPS7B8250-Q1

The TPS7B82-Q1 device is a 40- $V_{IN}$ , 300-mA low-dropout linear regulator with ultra-low quiescent current. This voltage regulator consumes only 3  $\mu$ A of quiescent current at light load, and is quite suitable for the automotive always on application. The device operates with a wide input-voltage range from 3 V to 40 V (45-V load dump protection).

## 2.3 System Design Theory


### 2.3.1 Reverse Polarity Protection

Reverse battery protection is required in every electronic subsystem of a vehicle, both by OEM standards, as well as ISO 16750-2, an international standard pertaining to supply quality. The goal is to prevent reverse-biasing components which are sensitive to polarity, like polarized capacitors and most integrated circuits.

Figure 6 shows the reverse polarity protection circuit schematic. It consists of a N-channel MOSFET (Q3) which is driven by the LM74700-Q1 smart diode controller. The traditional method which implements blocking diode results in large power dissipation due to the typical 400–700 mV forward-voltage drop. The smart diode solution decreases the losses as per the  $R_{DS(on)}$  of the MOSFET. The LM74700-Q1 controller provides a gate drive for an external N-Channel MOSFET and a fast response internal comparator to discharge the MOSFET Gate in the event of reverse polarity. A unique advantage of this scheme is that it is not referenced to ground and thus has zero  $I_Q$ . The N channel MOSFET is selected according to the following criteria:

- Continuous current rating higher than 10 A which is the maximum input current at minimum input voltage in this design.
- The VGS threshold should be 2.5-V maximum
- Source-to-drain voltage  $V_{SD}$  should be at least 0.48 V at 2 A

Figure 6. Reverse Polarity Protection Circuit Schematic

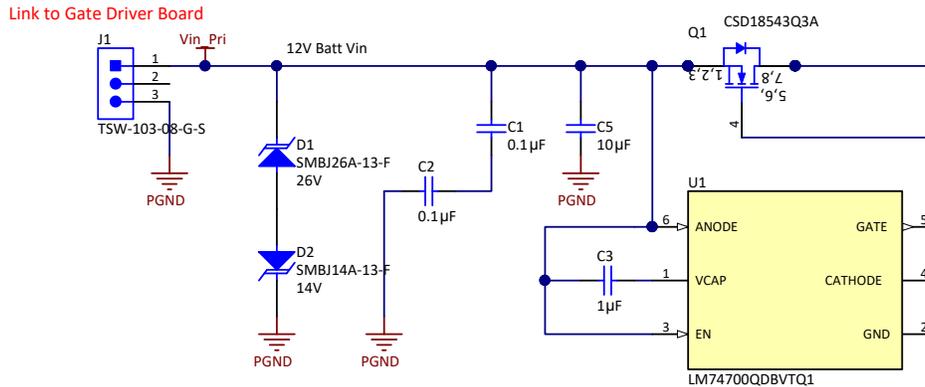

### 2.3.2 LM5180-Q1 Flyback Converter

The bias supply solution 1 is the flyback converter based on the LM5180-Q1 device which has integrated MOSFET and internal compensation. The converter provides isolated output voltages with tight regulation crossing load. The design specifications are shown in Table 2. Highlights of the converter are summarized as:


- Boundary conduction mode (BCM) control architecture provides fast line and load transient response
  - Peak current-mode control
  - Quasi-resonant switching for reduced power loss
  - Internal loop compensation
- Integrated 100-V flyback power MOSFET
  - Provides large headroom for input voltage transients
- Cycle-by-cycle overcurrent protection (OCP)
- Low transformer primary-to-secondary (inter-winding) capacitance to accommodate high dv/dt secondary-side common-mode swings.

Figure 7 shows the schematic of the converter.

Table 2. LM5180-Q1 Based Flyback Converter Specifications

PARAMETER	SPECIFICATION
Input voltage ( $V_{in}$ )	4.5 V–65 V DC (For flyback converter only, TVS limits the system input to 26 V DC)
Output voltage ( $V_{OUT}$ )	+15 V, –9 V
Output ripple	±3%
Maximum output current ( $I_{out\_max}$ )	180 mA
Switching frequency	< 350 kHz
Output power ( $P_{out\_max}$ )	4.14 W
Efficiency	> 90% peak, 88% at full load


Figure 7. LM5180-Q1 Based Flyback Converter Schematic

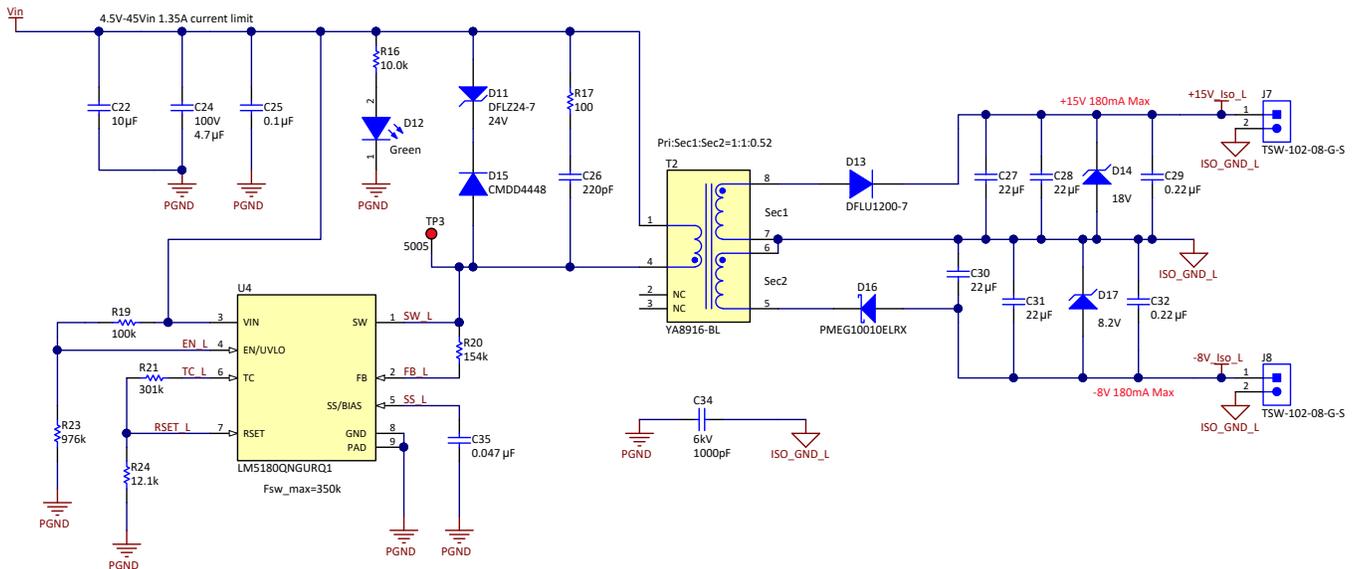

### 2.3.2.1 Modes of Operation and Switching Frequency

The LM5180-Q1 device uses a variable-frequency, peak current-mode (VFPCM) control architecture with three possible modes of operation as Figure 8 illustrates.

Figure 8. Operation Mode of the LM5180-Q1 Flyback Converter

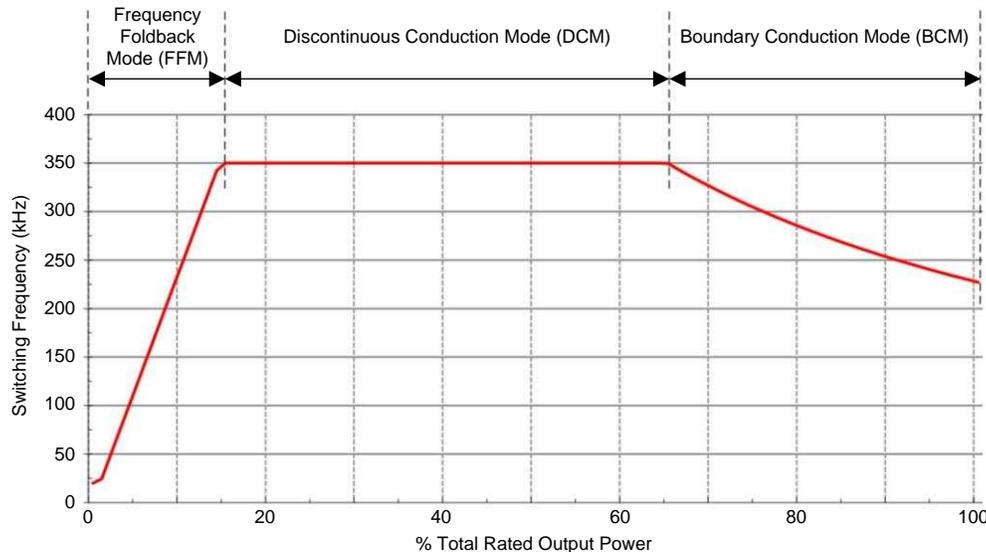

At high loads, the LM5180-Q1 device operates in Quasi-Resonant Boundary Conduction Mode. The power MOSFET turns on when the current in the secondary winding reaches zero. The MOSFET turns off when the peak primary current reaches the level dictated by the output of the internal error amplifier. As the load is decreased, the peak current decreases and the frequency increases to maintain BCM operation.

### 2.3.2.2 Transformer Design

Key parameters to design the transformer include turns ratio, primary side inductance, switching frequency, saturation current, and so forth.

If ignoring the drop voltage across the switching MOSFET the winding turns ratio is calculated as:

$$V_{IN\_Min} \times T_{on} = (V_{OUT} + V_D) \times T_{off} \times N_{PS}$$

where

- $V_{IN\_Min}$  is the minimum input voltage
- $T_{on}$  is the switch-on time of the switching MOSFET
- $T_{off}$  is the off time of the switching MOSFET
- $N_{PS}$  is the turns ratio of the transformer
- $V_D$  is the output rectification diode

(1)

Considering

$$D = \frac{T_{on}}{T_{on} + T_{off}}$$

is the duty cycle, and choosing the maximum duty cycle 75% at minimum input voltage, the turns ratio of the transformer primary winding to the secondary winding is calculated as:

$$N_{PS} = \frac{V_{IN\_Min}}{V_{OUT} + V_D} \times \frac{D}{1-D} = 0.65$$

(2)

Select a magnetizing inductance based on the minimum off-time constraint according to:

$$L_{MAG} \geq \frac{(V_{OUT} + V_D) \times N_{PS} \times t_{OFF\_MIN}}{I_{PRI\_PK}} = 26.5 \mu\text{H}$$

where

- $V_D$  is the forward drop voltage of the output rectification diode
- $I_{PRI\_PK}$  is the primary winding current when converter operates in frequency fold back mode (1.5 A according to the data sheet)

(3)

The built-in MOSFET of the LM5180-Q1 device is rated at 100 V. In the off cycle, when the secondary (flyback) diode is on, the voltage on the drain ( $V_{DS}$ ) is calculated as:

$$V_{DS} = V_{IN(MAX)} + V_{REF} + V_{RING} = 82 \text{ V}$$

where

- $V_{IN(MAX)}$  is the maximum input voltage
- $V_{REF}$  is the voltage reflected from the secondary side
- $V_{RING}$  is the excited spike due to resonance

(4)

The voltage across the secondary side diode is calculated as:

$$V_{Diode} = V_{OUT} + \frac{V_{IN(MAX)}}{N_{PS}} + V_{SPIKE} = 112 \text{ V}$$

where

- $V_{OUT}$  is the maximum output voltage
- $V_{SPIKE}$  is the excited spike due to resonance

(5)

The inductance of the transformer primarily determines the modes of operation in the LM5180-Q1 as the load is varied from the minimum load to full load. An increase in the magnetic inductance generally leads to an increase in the leakage inductance of the transformer. The LM5180-Q1 device has a minimum off-time ( $T_{OFF(MIN)}$ ) of 500 ns: the magnetizing current should not decrease to zero in less than 500 ns.

Therefore the minimum primary side inductance is calculated as:

$$L_{PRI} \geq \frac{(V_{out} + V_{FWD}) \times T_{OFF(MIN)} \times N_{PS}^2}{I_{PRI\_MIN} \times N_{PS}} = 30 \mu\text{H}$$

where

- $V_{OUT}$  is the nominal output voltage which is 24 V
- $T_{OFF(MIN)}$  is the minimum off time of LM5180-Q1
- $I_{PRI\_MIN}$  is the minimum peak current flowing at primary side for the LM5180-Q1 device which is 0.27 A
- $N_{PS}$  is the primary to secondary turns ratio

(6)

Thus, the designed transformer should have the minimum primary inductance of 30  $\mu\text{H}$ . [Table 3](#) lists the specifications of the designed flyback transformer.

**Table 3. Flyback Transformer Specifications**

PARAMETER		SPECIFICATION
Power rating		4.2 W
Input voltage		4.5 V–65 V
Maximum output current ( $I_{out\_max}$ )		180 mA
Switching frequency		< 300 kHz
Maximum duty cycle		75%
Primary side inductance		30 $\mu$ H $\pm$ 10% at 300 kHz
Leakage inductance		< 1% of primary inductance
Parasitic capacitance primary to secondary		< 20 pF
Output voltage and current		+15 V and –9 V at 180-mA average current
Turns ratio		1:1:0.52
Peak current	Primary	1.45 A
	Secondary	1 A
RMS current	Primary	1.1 A
	Secondary	380 mA

TI recommends the flyback transformer UA8916-BL from CoilCraft® for the LM5180-Q1-based flyback converter. The transformer features parasitic capacitance of 17 pF from the primary to secondary side.

### 2.3.2.3 Input Capacitors

The input capacitor must supply the input current during the input voltage dip from the 12-V battery. Input capacitors are essential in limiting the ripple voltage while supplying most of the switch current during the MOSFET switch on-time.

The input capacitance is calculated as:

$$C_{in} = \frac{I_{pri\_pk} \times D_{on}}{f_{SW} \times \Delta V_{ripple}} = \frac{1.45 \text{ A} \times 0.75}{300 \text{ k} \times 4.5 \text{ V} \times 3\%} = 26.8 \text{ } \mu\text{F} \quad (7)$$

### 2.3.2.4 Output Capacitors

The output capacitance ensures the converter has a small transient deviation to a step change of the load transient. The minimum needed capacitance is calculated as to maintain the output voltage drop less than 3% of the nominal voltage when the output current changes abruptly from the maximum to half ( $I_{step}$ ):

$$I_{step} = \frac{I_{out}}{2} = \frac{180 \text{ mA}}{2} = 90 \text{ mA} \quad (8)$$

$$V_{drop} = V_{out} \times 3\% = 24 \text{ V} \times 1\% = 0.24 \text{ V} \quad (9)$$

As any forward converters, the Right-Half-Plan-Zero (RHPZ) limits the bandwidth of the flyback. The frequency of the RHPZ is calculated as:

$$f_{RHPZ} = \frac{R_{OUT} \times (V_{in}/V_{out})^2}{L_{PRI} \times 2\pi} = 24.8 \text{ kHz}$$

where

- $R_{OUT}$  is the load impedance
  - $L_{PRI}$  is the primary inductance of the transformer
- (10)

The bandwidth of the system is estimated as 1/5 of the RHPZ:

$$f_{bandwidth} = \frac{1}{5} \times f_{RHPZ} = \frac{1}{5} \times 24.8 \text{ kHz} = 4.96 \text{ kHz} \quad (11)$$

As the result, the output capacitance at bandwidth frequency is calculated as:

$$C_{out\_min} = \frac{1}{2 \times \pi \times f_{bandwidth}} \times \frac{1}{\Delta V_{out} / \Delta I_{loadstep} - ESR_{out}} = 12 \text{ } \mu\text{F} \quad (12)$$


Therefore a minimum of 12- $\mu$ F capacitance is required for this design.

### 2.3.2.5 RC Snubber Design

When the MOSFET turns off, a high-voltage spike occurs at the drain (switch node) because of the resonances between the leakage inductor of the main transformer and the parasitic capacitance in the circuit. This causes excessive voltage on the drain of the MOSFET which can lead to breakdown and eventually failure of the device. The parasitic capacitance is composed of 3 components: (1) output capacitance of the MOSFET, (2) junction capacitance of the output diode which reflects to the primary side, (3) parasitic capacitance of the transformer winding.

The transformer used in this design has relatively less leakage inductance. A Zener clamp is used in this reference design as Figure 9 shows, due to ease-of-design and higher light load efficiency than the RCD snubber.

Figure 9. Snubber Circuit Schematic

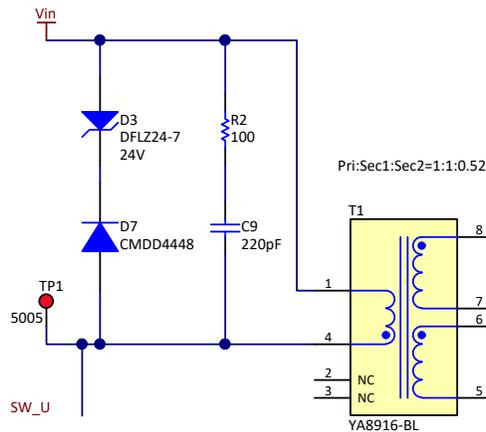

The power dissipated in the snubber can be calculated as:

$$P_{sub} = \frac{1/2 \times L_{Lk} \times I_{PK}^2 \times F_{SW}}{1 - V_{FBK} / V_{Ze}}$$

where

- $L_{Lk}$  is the leakage inductance of the transformer
- $I_{PK}$  is the primary peak current
- $F_{SW}$  is the switching frequency
- The Zener diode is selected as 24 V

(13)

### 2.3.2.6 Verification on Input Voltage Range

The LM5180-Q1 device integrates a 100-V power MOSFET with maximum current of 1.5 A. The maximum drain-to-source voltage ( $V_{ds\_max}$ ) is calculated as:

$$V_{ds\_max} = n \times \frac{N_p}{N_s} \times (V_{out} + V_f) + V_{in\_max} = 102.5 \text{ V}$$

where

- $n$  is the safe margin which is normally 1.5 or 2 times of the nominal value.
- $N_p/N_s$  is the turn ratio of the transformer primary winding to the secondary winding.
- $V_{OUT}$  is the output voltage
- $V_f$  is the forward voltage of the output diode
- $V_{IN\_max}$  is the maximum input voltage

(14)

Therefore, the selected MOSFET breaking voltage must be larger than 102.5 V.

### 2.3.2.7 LM5180-Q1 Settings

Figure 10 shows the schematic with components surrounding the LM5180-Q1 device. The UVLO is connected to  $V_{IN}$  directly for the lowest undervoltage lockout. With the designed turns ratio of the transformer and forward voltage of the secondary diode, the ratio between R20 ( $R_{FB}$ ) and R24 ( $R_{RST}$ ) determines the output voltage. R24 ( $R_{RST}$ ) is selected as 12.1 k $\Omega$  according to the data sheet. The output voltage is 24 V, the forward voltage drop of the secondary diode is 0.7 V.  $R_{FB}$  is calculated as:

$$R_{FB} = \frac{(V_{OUT} + V_{FD}) \times N_{PS}}{0.1 \text{ mA}} = 154 \text{ k}\Omega \tag{15}$$


The LM5180-Q1 device employs a thermal-compensation circuit that adjusts the feedback reference based on the forward voltage thermal coefficient of the flyback diode. The thermal compensation resistor value is determined by R21 ( $R_{TC}$ ) which is calculated as:

$$R_{TC} = \frac{R_{FB}}{N_{PS}} \times \frac{3 \text{ mV}/^\circ\text{C}}{TC_{Diode}} = 301 \text{ k}\Omega$$

where

- $TC_{Diode}$  is the absolute value of the temperature coefficient of the flyback diode (16)

**Figure 10. LM5180-Q1 Settings Schematic**

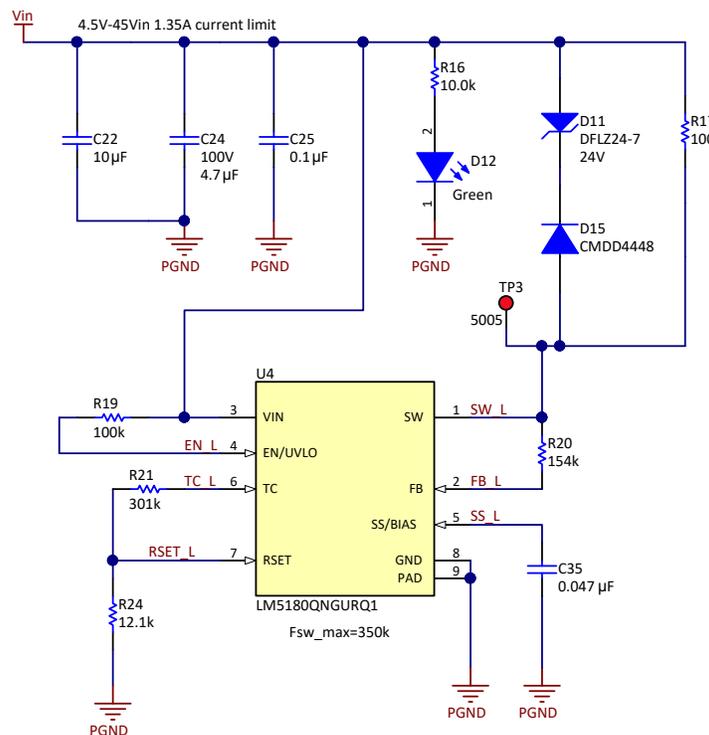


### 2.3.3 Overvoltage and Undervoltage Detection

The IGBT gate is driven from the 15-V rail to turn on the IGBT. The 15-V rail should not drop below the minimum gate voltage to properly turn on the IGBT. Driving the IGBT with lower gate voltage causes excessive power dissipation. Conversely, excessive higher gate voltage will destroy the IGBT.

The overvoltage and undervoltage detection is designed with the window comparator TPS3700-Q1. It has two high-accuracy comparators with an internal 400-mV reference and two open-drain outputs. Figure 11 shows the schematic of the detection circuit. The INA+ / INB– implements open-drain output. OUTA is driven low when the voltage at INA+ is below ( $V_{ITP} - V_{HYS}$ ) (according to the TPS3700-Q1 data sheet). The output goes high when the sense voltage returns above the respective threshold. OUTB is driven low when the voltage at this comparator exceeds  $V_{ITP}$ . The output goes high when the sense voltage returns

below the respective threshold. The undervoltage threshold is set as 13 V, and the overvoltage threshold is set as 17 V for this design. The OR logic is implemented by connecting the two open-drain outputs of the TPS3700-Q1 device. OUTA and OUTB can merge into one logic signal that goes low if either output is asserted. The 49.9-k $\Omega$  pullup resistor is used to hold these lines high when the output goes to high impedance.

**Figure 11. Overvoltage and Undervoltage Detection Schematic**

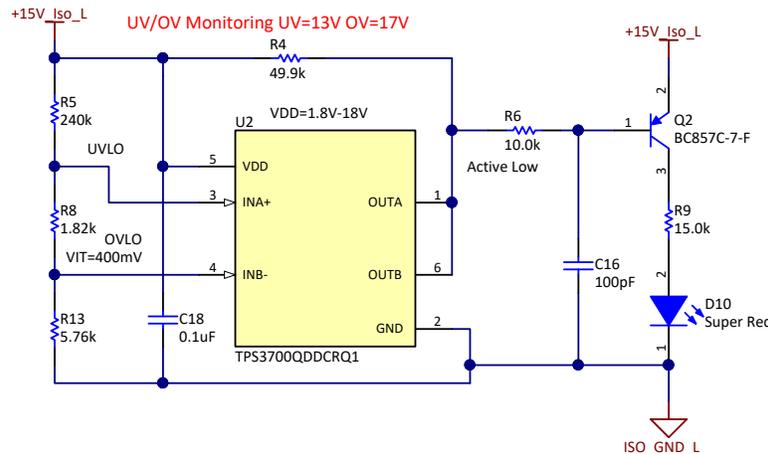


### 2.3.4 TPS40210-Q1 Flyback Converter

The bias supply solution 2 is the flyback converter based on the TPS40210-Q1 device which implements external MOSFET and primary side regulation. The procedure and calculations for designing the flyback converter are discussed in this section. Table 4 lists the design specification.

**Table 4. TPS40210-Q1 Based Flyback Converter Specifications**

PARAMETER	SPECIFICATION
Input voltage ( $V_{IN}$ )	5 V–42 V DC (52-V transient)
Output voltage ( $V_{OUT}$ )	+15 V, –9 V
Output ripple	$\pm 3\%$
Maximum output current ( $I_{out\_max}$ )	180 mA
Switching frequency	100 kHz
Output power ( $P_{out\_max}$ )	4.14 W
Efficiency	> 81% peak, 80% at full load

Figure 12. TPS40210-Q1 Flyback Converter Schematic

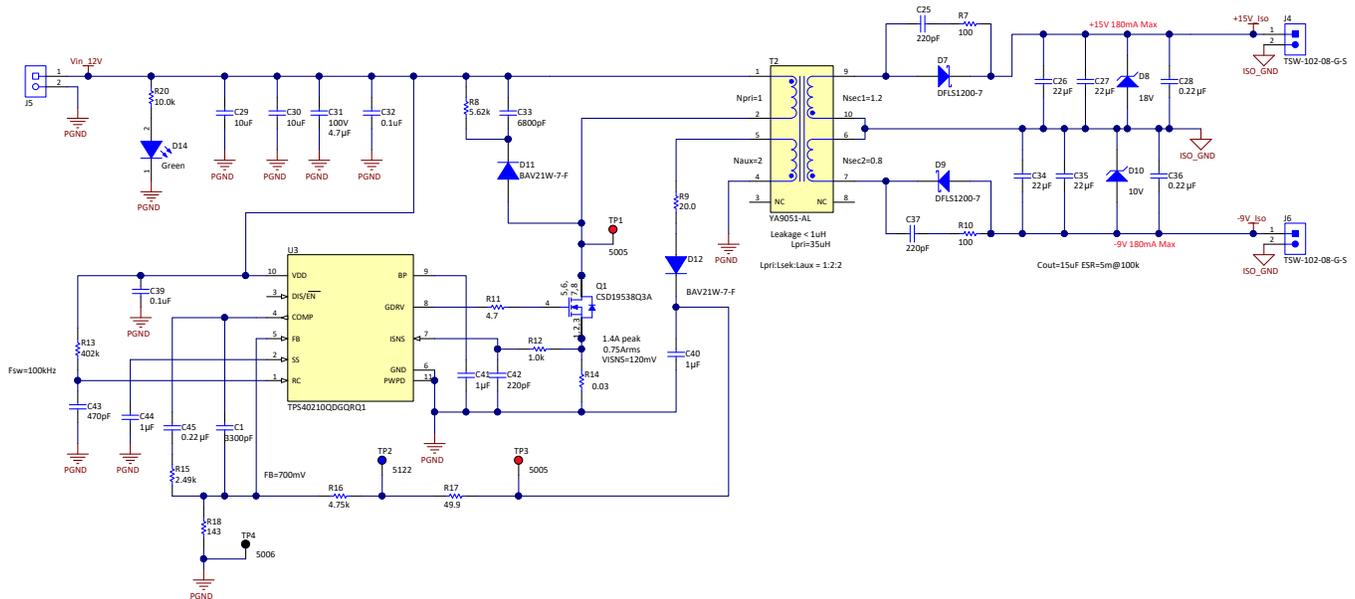

### 2.3.4.1 Switching Frequency

The oscillator frequency is determined by a resistor and capacitor connected to the RC pin of TPS40210-Q1 device. A switching frequency of 100 kHz is selected as a compromise between component size, EMI, and efficiency. The required resistor for a given oscillator frequency is calculated from:

$$R_T = \frac{1}{5.8 \times 10^{-8} \times F_{SW} \times C_T + 8 \times 10^{-10} \times F_{SW}^2 + 1.4 \times 10^{-7} \times F_{SW} - 1.5 \times 10^{-4} + 1.7 \times 10^{-6} \times C_T - 4 \times 10^{-9} \times C_T^2}$$

where

- $R_T$  is the timing resistance in k $\Omega$
- $F_{SW}$  is the switching frequency in kHz
- $C_T$  is the timing capacitance in pF

(17)

$C_T$  and  $R_T$  are selected as 470 pF and 402 k $\Omega$ , respectively for the 100-kHz switching frequency.

### 2.3.4.2 Transformer Design

A transformer is one of the most important elements to ensure the flyback converter operates reliably and efficiently. A flyback transformer is used as an energy storage device. The energy is stored in the air-gap of the core. The flyback converter is designed for continuous-conduction mode. In comparison with the discontinuous mode, the advantages are lower peak currents, lower output voltage spikes, and lower core losses.

If ignoring the drop voltage across the switching MOSFET, and output rectification diode, the winding turns ratio is calculated as:

$$V_{IN\_Min} \times T_{on} = V_{OUT} \times T_{off} \times N_{PS}$$

where

- $V_{IN\_Min}$  is the minimum input voltage
- $T_{on}$  is the switch-on time of the switching MOSFET
- $T_{off}$  is the off time of the switching MOSFET
- $N_{PS}$  is the turn ratio between the primary turns and secondary turns of the transformer.

(18)

Considering:

$$D = \frac{T_{on}}{T_{on} + T_{off}}$$

is the duty cycle, and choosing the maximum duty cycle as 70%. Therefore, the turn ratio of the transformer primary winding to the secondary winding is calculated as:

$$N_{PS} = \frac{V_{IN\_Min}}{V_{OUT}} \times \frac{D}{1-D} = 0.49 \quad (19)$$

Hence,  $N_{PS}$  is selected as 1:2. The actual duty cycle ( $D_{ON\_act}$ ) is calculated as:

$$D_{ON\_act} = \frac{(V_{out} + V_f) \times N_{PS}}{V_{IN\_min} + (V_{out} + V_f) \times N_{PS}} = 0.71$$

where

- $V_f$  is the forward drop voltage of the output rectification diode (20)

The turn-off time duty cycle of the MOSFET is calculated as:

$$D_{OFF\_act} = 1 - D_{ON\_act} = 0.29 \quad (21)$$

The average peak current ( $I_{sec\_avgpk}$ ) at the transformer secondary side is:

$$I_{sec\_avgpk} = I_{sec\_avg} / D_{OFF\_act} = 180 \text{ mA} / 0.29 = 620 \text{ mA} \quad (22)$$

The peak current at the transformer secondary side ( $I_{sec\_pk}$ ) is calculated as:

$$I_{sec\_pk} = \frac{2 \times I_{sec\_avgpk}}{2 - D_{OFF\_act}} = 0.73 \text{ A} \quad (23)$$

The average current flowing into the transformer secondary side is 180 mA. Therefore, the RMS current at the transformer secondary side ( $I_{sec\_rms}$ ) is calculated as:

$$I_{sec\_rms} = I_{sec\_avgpk} \times \sqrt{D_{OFF\_act}} = 0.39 \text{ A} \quad (24)$$

The average peak current ( $I_{pri\_avgpk}$ ) at the transformer primary side is calculated as:

$$I_{pri\_avgpk} = \frac{I_{sec\_avgpk}}{N_{PS}} = \frac{0.73 \text{ A}}{0.5} = 1.46 \text{ A} \quad (25)$$

The peak current at the transformer primary side ( $I_{pri\_pk}$ ) is calculated as:

$$I_{pri\_pk} = \frac{2 \times I_{pri\_avgpk}}{2 - D_{on\_act}} = \frac{2 \times 1.46 \text{ A}}{2 - 0.3} = 1.72 \text{ A} \quad (26)$$

The RMS current at the transformer primary side ( $I_{pri\_rms}$ ) is calculated as:

$$I_{pri\_rms} = I_{pri\_avgpk} \times \sqrt{D_{ON\_act}} = 1.46 \times \sqrt{0.71} = 1.23 \text{ A} \quad (27)$$

The RMS current of the bias winding is selected as 50 mA according to the current limit of the internal regulator. The turn ratio of the transformer bias winding to the secondary winding is selected as 1:1 for better regulation. As the result, output voltage of the bias winding is  $V_{bias} = V_{OUT} = 24 \text{ V}$ .

[Table 7](#) details the specifications of the designed flyback transformer.

**Table 5. Flyback Transformer Specifications**

PARAMETER	SPECIFICATION
Qualification	AEC-Q200 Grade 1 qualified
Safety insulation	Reinforced
Power rating	4.2 W
Input voltage	4.5 V–42 V
Switching frequency	100 kHz
Maximum output current ( $I_{out\_max}$ )	180 mA
Maximum duty cycle	71%
Primary-side inductance	35 $\mu\text{H} \pm 10\%$ at 100 kHz
Leakage inductance	< 2% of primary inductance
Parasitic capacitance primary to secondary	< 20 pF
Output voltage and current	24 V at 180 mA average current
Auxiliary winding output	24 V at 50 mA
Turns ratio (Pri:Sec:Aux)	1:2:2

**Table 5. Flyback Transformer Specifications (continued)**

PARAMETER		SPECIFICATION
Peak current	Primary	1.72 A
	Secondary	0.8 A
RMS current	Primary	1.2 A
	Secondary	350 mA

TI recommends the automotive grade AEC-Q200 qualified flyback transformer YA9051-AL from CoilCraft for the TPS40210-Q1-based design. The transformer features parasitic capacitance of 20 pF from primary to secondary side.

### 2.3.4.3 Input Capacitors

The input capacitor must supply the input current during the input voltage dip from the 12-V battery. Input capacitors are essential in limiting the ripple voltage while supplying most of the switch current during the MOSFET switch on-time.

The input capacitance is calculated from 6-V minimum input voltage with 10% ripple:

$$C_{in} = \frac{I_{pri, pk} \times D_{on}}{F_{SW} \times \Delta V_{ripple}} = \frac{1.72 \text{ A} \times 0.75}{100 \text{ k} \times 6 \text{ V} \times 10\%} = 20 \mu\text{F} \quad (28)$$

### 2.3.4.4 Output Capacitors

The output capacitance ensures the converter have a small transient deviation to a step change of the load transient. The minimum needed capacitance is calculated as to maintain the output voltage drop less than 3% of the nominal voltage when the output current changes abruptly from the maximum to half ( $I_{step}$ ):

$$I_{step} = \frac{I_{out}}{2} = \frac{180 \text{ mA}}{2} = 90 \text{ mA} \quad (29)$$

$$V_{drop} = V_{out} \times 3\% = 24 \text{ V} \times 1\% = 0.24 \text{ V} \quad (30)$$

As any forward converters, the RHPZ limits the bandwidth of the flyback. The frequency of the RHPZ is calculated as:

$$f_{RHPZ} = \frac{R_{OUT} \times (V_{in} / V_{out})^2}{L_{PRI} \times 2\pi} = 24.8 \text{ kHz}$$

where

- $R_{OUT}$  is the load impedance
  - $L_{PRI}$  is the primary inductance of the transformer
- (31)

The bandwidth of the system is estimated as 1/5 of the RHPZ:

$$f_{bandwidth} = \frac{1}{5} \times f_{RHPZ} = \frac{1}{5} \times 24.8 \text{ kHz} = 4.96 \text{ kHz} \quad (32)$$

As the result, the output capacitance at bandwidth frequency is calculated as:

$$C_{out, min} = \frac{1}{2 \times \pi \times f_{bandwidth}} \times \frac{1}{\Delta V_{out} / \Delta I_{loadstep} - ESR_{out}} = 12 \mu\text{F} \quad (33)$$


Therefore, a minimum of 12- $\mu\text{F}$  capacitance is required for this design.

### 2.3.4.5 RC Snubber Design

When the MOSFET turns off, a high-voltage spike occurs at the drain (switch node) because of the leakage inductor of the main transformer and the parasitic capacitance in the circuit. The parasitic capacitance is composed of 3 components: (1) output capacitance of the MOSFET, (2) junction capacitance of the output diode which reflects to the primary side, (3) parasitic capacitance of the transformer winding.

As the result, implementation of an RC snubber circuit is very important to avoid MOSFET from avalanche breakdown and damage. [Figure 13](#) shows the schematic of the RC snubber circuit.

Figure 13. RC Snubber of the TPS40210-Q1 Flyback DC/DC Converter

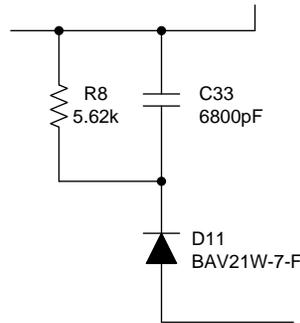

Voltage rating of the damping capacitance is calculated as:

$$V_{SN} = 3 \times n \times V_{out} = 3 \times 0.5 \times 24 \text{ V} = 36 \text{ V} \quad (34)$$

The damping resistance ( $R_{SN}$ ) is calculated as:

$$R_{SN} = \frac{V_{SN}^2}{\frac{1}{2} \times L_{lk1} \times I_{pri\_pk}^2 \times \frac{V_{SN}}{V_{SN} - n \times V_{out}} \times F_{SW}} = 8.3 \text{ k}\Omega$$

where

- $L_{lk1}$  is the leakage inductance of the primary side
- $I_{pri\_pk}$  is the peak current flowing into the transformer primary side
- $V_{SN}$  is the voltage across the snubber capacitor. It is determined at the minimum input load and full-load condition.
- $F_{SW}$  is the switching frequency of the converter
- $n$  is the turns ratio of the transformer primary to the secondary
- $V_{OUT}$  is the output voltage

(35)

A 5.6-k $\Omega$  resistor is selected for higher power dissipation. The power rating of the damping resistor is calculated as:

$$P_{RSN} = \frac{V_{SN}^2}{R_{SN}} \times D = \frac{36 \text{ V}^2}{5.6 \text{ k}\Omega} \times 0.2 = 0.05 \text{ W}$$

where

- $V_{SN}$  is the voltage across the snubber capacitor. It is determined at the minimum input load and full-load condition.
- $D$  is the maximum duty cycle of the voltage spike.

(36)

The damping capacitance is calculated as:

$$C_{SN} = \frac{V_{SN}}{DV_{SN} \times R_{SN} \times F_{SW}} = \frac{36 \text{ V}}{36 \text{ V} \times 15\% \times 5.6 \text{ k}\Omega \times 100 \text{ kHz}} = 11 \text{ nF} \quad (37)$$

The higher the damping capacitance is, the lower the voltage spike is, and the longer the voltage spike duration will be.

Current flow through the freewheeling diode (D2) is calculated as:

$$i_D = C_{SN} \times \frac{dv}{dt} = 6.8 \text{ nF} \times \frac{42 \text{ V} + 0.5 \times 24 \text{ V}}{0.3 \times \frac{1}{100 \text{ kHz}}} = 0.12 \text{ A} \quad (38)$$

A Schottky diode with 200-V reverse blocking voltage, 0.2-A average current, and 2.5-A repetitive current flow is chosen in this design.

### 2.3.4.6 Selection of MOSFETs

Selection of the MOSFET is very important for a high efficient, size optimized, and thermally enhanced power supply design. The MOSFET drain-to-source breakdown voltage must be higher than the voltage imposed on the switch node. The maximum drain-to-source voltage ( $V_{ds\_max}$ ) is calculated as:

$$V_{ds\_max} = n \times \frac{N_p}{N_s} \times (V_{out} + V_f) + V_{in\_max} = 66.7 \text{ V}$$

where

- $n$  is the safe margin which is normally 1.5 or 2 times of the nominal value
  - $N_p/N_s$  is the turn ratio of the transformer primary winding to the secondary winding
  - $V_{OUT}$  is the output voltage
  - $V_f$  is the forward voltage of the output diode
  - $V_{IN,max}$  is the maximum input voltage
- (39)

Therefore, a MOSFET with maximum drain-to-source voltage rating larger than 66.7 V must be chosen. Calculations on losses are done at the 12-V nominal input because this is the condition under which the MOSFET mostly works. Four components must be taken into account when selecting the MOSFET:

- On-state conduction losses
- Gate driver losses
- Switching losses
- Output capacitance losses

The CSD19538Q3A, 100-V, 15-A MOSFET is selected for this reference design. The conduction losses of the MOSFET ( $P_{on}$ ) are calculated as:

$$P_{on} = I_D^2 \times R_{DS(on)} \times D_{on} = (0.63 \text{ A})^2 \times 59 \text{ m}\Omega \times 46.5\% = 0.01 \text{ W}$$

where

- $I_D$  is the conducting current during the turn-on of the switch
  - $R_{DS(on)}$  is the channel resistance when the switch is turned on
  - $D_{on}$  is the duty cycle at 12-V input
- (40)

The gate driver losses ( $P_{drive}$ ) are calculated as:

$$P_{drive} = Q_g \times V_{driver} \times F_{SW} = 4.3 \text{ nC} \times 8 \text{ V} \times 100 \text{ kHz} = 0.003 \text{ W}$$

where

- $Q_g$  is the gate charge
  - $V_{driver}$  is the gate driver voltage
  - $F_{SW}$  is the switching frequency
- (41)

Switching losses of the MOSFET ( $P_{SW}$ ) are calculated as:

$$P_{SW} = \frac{1}{2} \times F_{SW} \times (V_{DSr} \times t_r \times I_{on} + V_{DSf} \times t_{off} \times I_{off}) = 0.02 \text{ W}$$

where

- $V_{DSr}$  is the drain-to-source voltage when MOSFET is switching at rising edge
  - $V_{DSf}$  is the drain-to-source voltage when MOSFET is switching at falling edge
  - $F_{SW}$  is the switching frequency
  - $t_r$  is the switching rise time
  - $I_{on}$  is the current built up level during turn on
  - $t_{off}$  is the switching fall time
  - $I_{off}$  is the current level at the moment of turn off
- (42)

The output capacitance losses ( $P_{COSS}$ ) are calculated as:

$$P_{COSS} = \frac{1}{2} \times C_{OSS} \times V_{DS}^2 \times F_{SW} = 0.003 \text{ W}$$

where

- $C_{OSS}$  is the output capacitance of the MOSFET
  - $V_{DS}$  is the Drain-to-Source voltage when MOSFET is switching
  - $F_{SW}$  is the switching frequency
- (43)

Therefore, the total losses in the MOSFET are calculated as:

$$P_{total} = P_{on} + P_{SW} + P_{COSS} = 0.01 \text{ W} + 0.02 \text{ W} + 0.003 \text{ W} = 0.023 \text{ W}$$
(44)

### 2.3.5 Buck Converter

The bias supply solution 3 implements a buck converter as the front stage and a push-pull transformer driver supply as the following stage. The synchronous step-down DC/DC converter LM46002-Q1 with integrated switch is selected as the front stage. It is capable of driving up to 2 A of load current from an input voltage ranging from 3.5 V to 60 V.

#### 2.3.5.1 Switching Frequency

The switching frequency can be programmed by the impedance  $R_T$  from the RT pin to ground. The frequency is inversely proportional to the  $R_T$  resistance. The LM46002-Q1 device is operated at 480-kHz switching frequency in this design.  $R_T$  is calculated as:

$$R_T = \frac{40200}{F_{SW}} - 0.6 = 83.2 \text{ k}\Omega \quad (45)$$

#### 2.3.5.2 Output Inductor

The buck converter inductance is calculated according to the switching frequency. The selected value compromises between the size of the inductor and the peak-to-peak output ripple current. A higher inductance gives lower ripple current, which then gives a lower output voltage ripple with the same output capacitors. An inductance that gives a ripple current of 20% to 40% at the maximum current is a good starting point. The minimum inductor value is calculated based on input voltage range, output voltage, maximum output current, and the switching frequency:

$$\frac{(V_{IN} - V_{OUT}) \times D}{0.4 \times F_{SW} \times I_{OUT}} \leq L_{min} \leq \frac{(V_{IN} - V_{OUT}) \times D}{0.2 \times F_{SW} \times I_{OUT}}$$

where

- $V_{IN}$  is the maximum input voltage in 12-V battery nominal condition
- $V_{OUT}$  is the output voltage
- $F_{SW}$  is the switching frequency
- $I_{OUT}$  is the output current
- $D$  is the duty cycle at 16-V input

(46)

Hence, the calculated inductance is between 10 $\mu$ H and 20 $\mu$ H. For this design, 18- $\mu$ H inductance is chosen. Besides the inductor size, the rated saturation current needs to be specified as:

$$I_{Ripple} = \frac{(V_{IN} - V_{OUT}) \times D}{L \times F_{SW}} \quad (47)$$

$$I_{L-peak} = I_{OUT} + \frac{I_{Ripple}}{2} \quad (48)$$

Hence, the inductor peak current is calculated as 3.6 A. The MSS1260-183MLB from Coilcraft with 5.22-A saturation current rating is selected for this design. A good practice is to use an inductor with the saturation current around 1.5 to 2 times higher than calculated.

In general, it is preferable to choose lower inductance in switching power supplies, because it usually corresponds to faster transient response, smaller DCR, and reduced size. However, inductance that is too low leads to high-output voltage ripple with the same output capacitance. It also generates more conduction loss because the RMS current is slightly higher relative that with a lower current ripple at the same DC current. As the LM46002-Q1 device implements peak current mode control, it is not recommended to have too small of an inductor current ripple. Enough of an inductor current ripple improves the signal-to-noise ratio on the current comparator and makes the control loop more immune to noise.

#### 2.3.5.3 Output Capacitors

The value of output capacitors are calculated based on the maximum desired output voltage ripple, and the transient response:

$$C_{OUT} \geq \frac{1}{F_{SW} \times \frac{\Delta I_L}{I_{OUT}} \times \frac{\Delta V_{OUT}}{\Delta I_{OUT}}} \times \left[ \frac{\Delta I_L}{I_{OUT} \times 12} \times (1 + (1 - D)) + (1 - D) \times \left(1 + \frac{\Delta I_L}{I_{OUT}}\right) \right]$$

where

- $\Delta I_{OUT}$  is the load step change

- $\Delta V_{OUT}$  is the target output voltage undershoot
- $\Delta I_L$  is the inductor ripple current
- $I_{OUT}$  is the output current

(49)

As a result, the output capacitance should be larger than 20  $\mu\text{F}$ . Two 22- $\mu\text{F}$  ceramic capacitors are connected in parallel to meet the requirement. The second requirement is the maximum ESR of the capacitor, which is calculated from:


$$ESR \leq \frac{1-D}{F_{SW} \times C_{OUT}} \times \left( \frac{I_{OUT}}{\Delta I_L} + 0.5 \right) \quad (50)$$

The maximum ESR is calculated to meet the required maximum output ripple. The equivalent ESR of the output capacitors should be lower than 0.288  $\Omega$ .

### 2.3.5.4 Loop Compensation

The LM46002-Q1 device is internally compensated with  $RC = 400 \text{ k}\Omega$  and  $CC = 50 \text{ pF}$ . The internal compensation is designed such that the loop response is stable over the entire operating frequency and output voltage range. Depending on the output voltage, the compensation loop phase margin can be low with all ceramic capacitors. An external feed-forward cap  $C_{FF}$  is recommended to be placed in parallel with the top resistor divider  $R_{FBT}$  for optimum transient performance.

**Figure 14. Feed-Forward Capacitor for Loop Compensation**

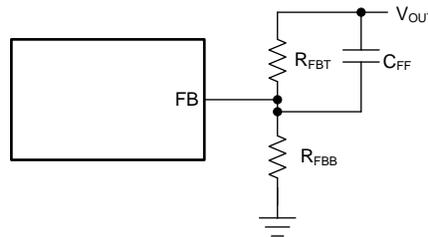

$C_{FF}$  is chosen such that the phase margin is boosted at the crossover frequency. The crossover frequency without  $C_{FF}$  can be calculated as:

$$F_X = \frac{\Delta I_{OUT}}{2 \times \pi \times \Delta V_{OUT} \times C_{OUT}} \quad (51)$$

The  $C_{FF}$  should be selected such that the bandwidth of the control loop without the  $C_{FF}$  is centered between the zero and pole frequencies caused by the feedforward capacitor. Therefore:

$$C_{FF} = \frac{1}{2 \times \pi \times F_X} \times \frac{1}{\sqrt{R_{FBT} \times (R_{FBT} \parallel R_{FBB})}} \quad (52)$$

A 100-pF feedforward capacitor is selected for this design.


The LM46002 device needs a bootstrap capacitor between CBOOT and the SW pin. The recommended bootstrap capacitor is 0.47  $\mu\text{F}$  and rated at 50 V. The bootstrap capacitor must be a high-quality ceramic type with X7R or X5R grade dielectric for temperature stability.

The VCC pin is the output of an internal LDO for the LM46002 device. The input for this LDO comes from either  $V_{IN}$  or bias. To ensure stability of the part, a minimum of a 2.2- $\mu\text{F}$ , 10-V capacitor is connected from VCC to ground.

### 2.3.6 SN6505-Q1 Push-Pull Transformer Driver

The second stage implements a push-pull transformer driver to transfer power from the primary side to the secondary side. Figure 15 shows the converter operation theory.

**Figure 15. Push-Pull Converter Theory of Operation**

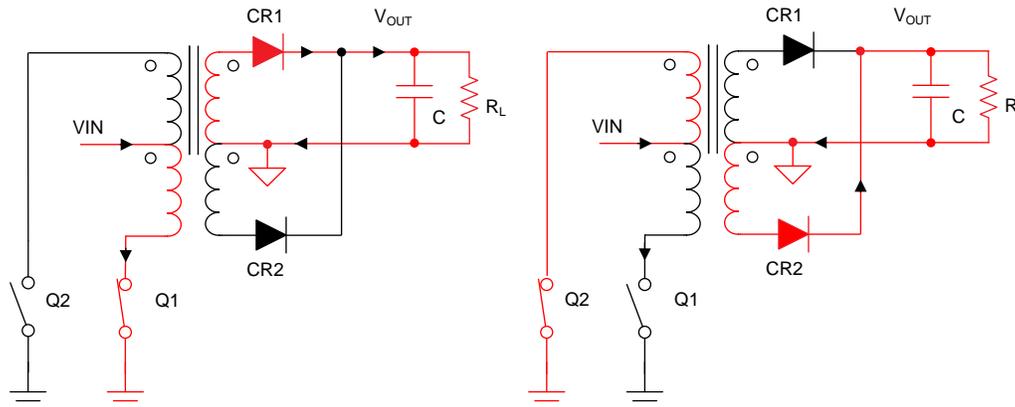

When Q1 conducts, current is sourced from VIN into the ground through the lower half of the transformer primary, this creates a potential at the lower half of the primary winding with the primary center tap as the positive. This voltage transfers to the transformer secondary according to the transformer polarity and turns ratio. CR1 is now forward-biased and CR2 is reverse-biased, causing a current to flow through the upper half of the secondary winding. Similarly, when Q2 conducts, the transformer primary and secondary polarities reverse. CR1 is reverse-biased and CR2 is forward-biased, which causes a current to flow from the bottom half of the secondary through CR2 into the load. Q1 and Q2 switch alternatively, with approximately 50% duty cycle to transfer power from the primary to the secondary of the transformer.

Before either switch is turned ON, there must be a short period during which both transistors are high impedance. This short period, known as break-before-make time, is required to avoid shorting out both ends of the primary.

The SN6505-Q1 push-pull transformer driver has integrated MOSFET switches. The positive temperature co-efficient of these switches has a self-correcting effect on the V-t imbalance. During a slightly longer on-time, the prolonged current flow through a FET gradually heats the MOSFET, which leads to an increase in  $R_{DS(on)}$ . The higher resistance then causes the drain-source voltage, VDS, to increase. Because the voltage at the primary is the difference between the constant input voltage, VIN, and the voltage drop across the MOSFET is gradually reduced and V-t balance is restored.


### 2.3.6.1 Power Supply Specification

Specifications of the designed push-pull power supply are summarized in Table 6. Figure 16 shows the designed schematic. The required external discrete components are: center-tapped transformer, rectifier diodes, and input and output bulk capacitors.

**Table 6. Push-Pull Transformer Driver Power Supply Specifications**

PARAMETER	SPECIFICATION
Input voltage	5 V $\pm$ 5%
Output voltage	+15 V, -8 V
Output current	180 mA
Output voltage ripple	< 200 mV peak to peak at full load
Output power	4.14 W

**Figure 16. Push-Pull Transformer Driver Power Supply Schematic**

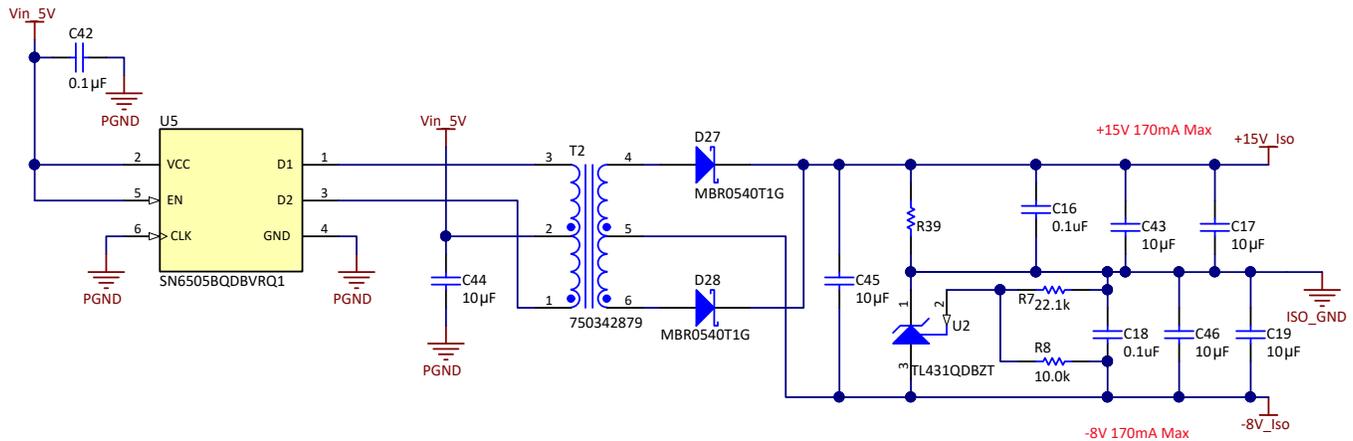

### 2.3.6.2 Transformer Design

The input peak current was calculated from Equation 53. The factor 0.97 accounts for typical transformer power transfer efficiency.

$$I_{in\_peak} = \frac{P_{out\_max} / \eta}{V_{in\_min}} = \frac{4.32 \text{ W} / 0.97}{4.75 \text{ V}} = 882 \text{ mA}$$

where

- $P_{out\_max}$  is the maximum output power
- $V_{in\_min}$  is the minimum input voltage

The SN6505-Q1 device switches the internal dual MOSFETs with approximately 50% duty cycle each. Therefore, the AC current flowing through transformer primary ( $I_{pri}$ ) can be calculated from:

$$I_{pri} = \frac{I_{in\_peak}}{2} = \frac{882 \text{ mA}}{2} = 441 \text{ mA}$$

The transformer turns ratio ( $N_{ps}$ ) is calculated from:

$$N_{ps} = \frac{V_{pri}}{V_{sec} + V_f} = \frac{5 \text{ V}}{23 \text{ V} + 0.35 \text{ V}} = 1:4.67$$

where

- $V_{sec}$  is the voltage across the secondary winding
- $V_f$  is the forward voltage of the diode
- $V_{pri}$  is the voltage across the primary winding

The V-t product of the transformer must be greater than  $Vt_{min}$ . Failure to meet these criteria will lead to transformer core saturation:

$$Vt_{min} = V_{IN\_max} \times \frac{T_{max}}{2} = \frac{V_{IN\_max}}{2 \times F_{min}} = \frac{5 \text{ V} \times 1.05}{2 \times 300 \text{ kHz}} = 8.75 \text{ V } \mu\text{s}$$

where

- $V_{IN\_max}$  is the maximum input voltage
- $F_{min}$  is the minimum switching frequency

The 750342879 transformer from Würth Electronics is selected for this design. Table 7 summarizes the specifications.

**Table 7. Push-Pull Transformer Specifications**

PARAMETER	SPECIFICATION
Turns ratio (6 – 4):(1 – 3)	3.5 : 1, ±2%
DC resistance (1 – 3)	0.33 Ω maximum at 20°C
DC Resistance (6 – 4)	0.75 Ω maximum at 20°C
Inductance (1 – 2)	50-µH minimum at 100 kHz, 10 mVac

**Table 7. Push-Pull Transformer Specifications (continued)**

PARAMETER	SPECIFICATION
Dielectric (1 – 6)	5000 V <sub>RMS</sub> , 1 minute
Operating temperature range	-40°C to 125°C
Clearance distance	8 mm

**2.3.6.3 Rectifier Diode**

To increase the efficiency of the push-pull forward converter, the forward voltage drop of the secondary side rectifier diodes must be minimized. This design implements the SN6505B version which has the high-switching frequency and the diodes are subject to excessive reverse recoveries. Schottky diodes are selected as they meet the requirements of low forward-voltage drop and fast recovery time. The diode should withstand a reverse voltage of twice the output voltage.

The forward current flowing through the diode is the rated output current which is 180 mA. The reverse blocking voltage of the diode is calculated as:

$$V_b = V_{out} + V_{in} \times \frac{N_{sec}}{N_{pri}} = 36 \text{ V} \tag{57}$$

Two 40-V, 500-mA Schottky diodes are chosen for this design.

**2.3.6.4 Capacitor Selection**

Considering two 22-μF ceramic capacitors being placed at output of the buck converter, one ceramic bypass capacitor of 100 nF is placed as close as possible to the V<sub>CC</sub> pin for high frequency noise filtering.

The output capacitor is required to filter the output ripple. The output ripple specification is calculated as:

$$\Delta V = V_{out} \times 10\% = 23 \text{ V} \times 1\% = 0.23 \text{ V} \tag{58}$$

The required peak current which is delivered to the gate driver is 20 A, according to the isolated gate driver board. The required capacitance is calculated as:


$$C \geq \frac{I_{peak} \times dt}{\Delta V} = 13 \text{ } \mu\text{F} \tag{59}$$

Considering it could also be used to drive SiC MOSFETs with higher total gate charge, a total of two 10-μF ceramic capacitors are connected in parallel at the positive and negative supply outputs.

**2.3.6.5 Generation of the Negative Supply**

The power supply output is separated into the positive rail of +15 V and the negative rail of -8 V through the TL431-Q1 device which reacts as a shunt regulator. Figure 17 shows the schematic.

**Figure 17. Generation of Negative Voltage Rail Through TL431-Q1 Shunt Reference**

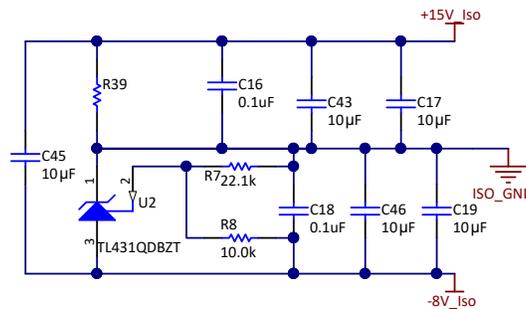

To program the cathode voltage to a regulated voltage, a resistive bridge is shunted between the cathode and anode pins with the mid-point tied to the reference pin. The cathode voltage is calculated as:

$$V_{neg} = \left(1 + \frac{R_7}{R_8}\right) \times V_{ref} = \left(1 + \frac{22.1 \text{ k}\Omega}{10 \text{ k}\Omega}\right) \times 2.5 \text{ V} = 8 \text{ V} \tag{60}$$


For this equation to be valid, the TL431-Q1 device must be fully biased so that it has enough open loop gain to mitigate any gain error. The cathode current is set to:

$$I_{\text{cat}} = \frac{V_{\text{out}} - V_{\text{neg}}}{R_{39}} = \frac{23 \text{ V} - 8 \text{ V}}{15.4 \text{ k}\Omega} = 0.97 \text{ mA} \quad (61)$$

### 3 Hardware, Testing Requirements, and Test Results

#### 3.1 Required Hardware

Figure 18 shows the inverter power stage board and connectors pin description. The placement of components and corresponding circuits are also described. Figure 19 shows the PCB board image of LM5180-Q1 based flyback converter from top side and bottom side, respectively. The input and output connectors are indicated.

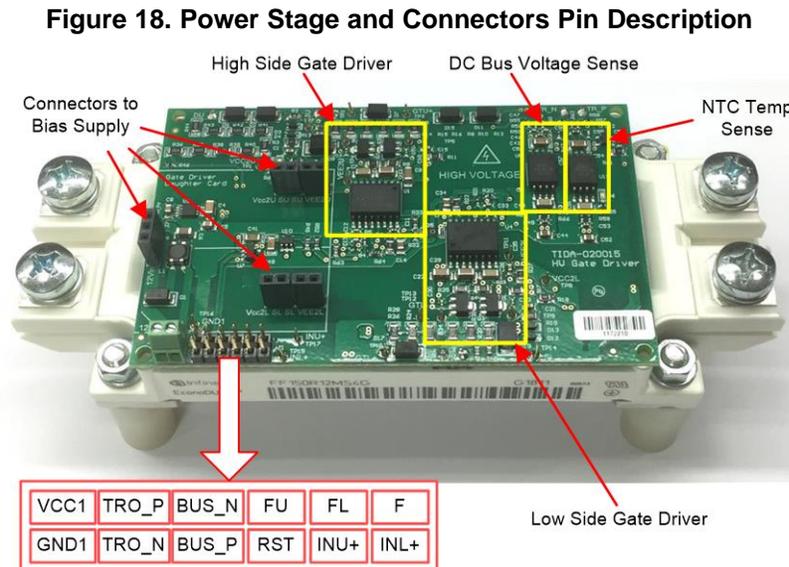

**Figure 19. LM5180-Q1 Based Flyback PCB Board**

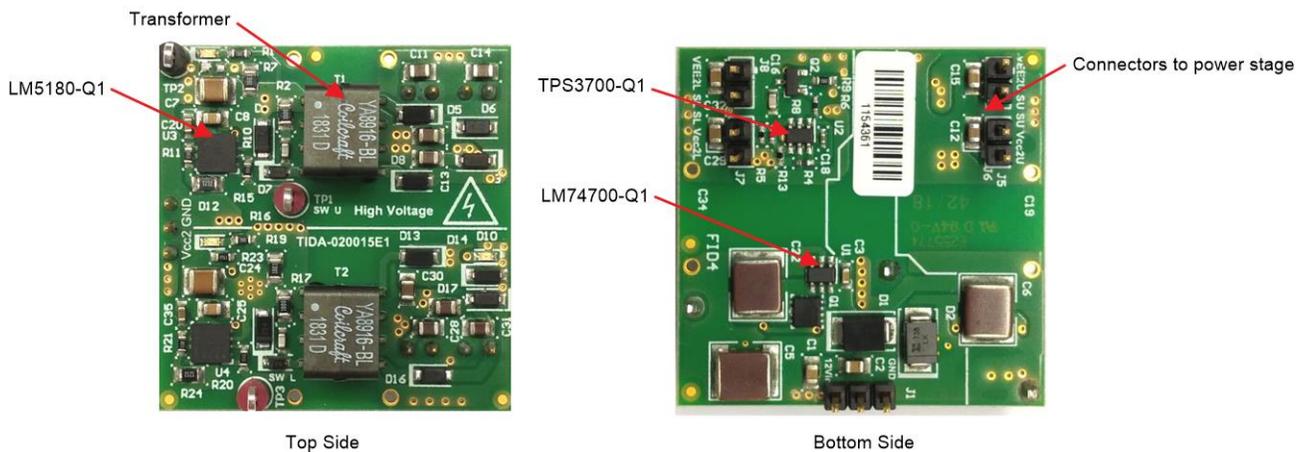


Figure 20 shows the LM5180-Q1 based flyback PCB board connected to the power stage.

**Figure 20. LM5180-Q1 Based Bias Supply Connected to the Power Stage**



Figure 21 shows the PCB board image of TPS40210-Q1 based flyback converter from top side and bottom side, respectively.

**Figure 21. TPS40210-Q1 Based Flyback PCB Board Image**

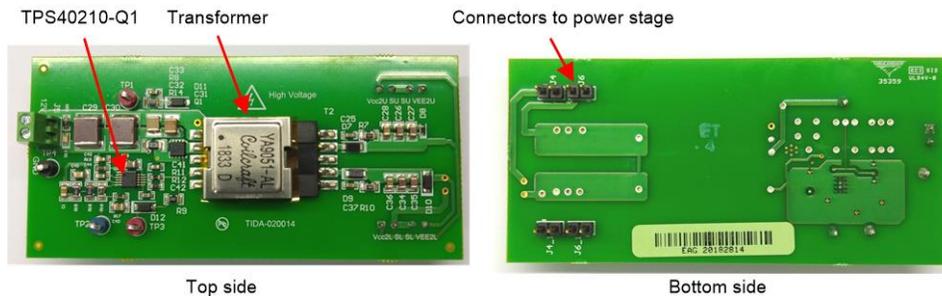


Figure 22 shows the PCB board image of buck with push-pull power supply from top side and bottom side, respectively.

**Figure 22. Buck With Push-Pull Power Supply PCB Board**

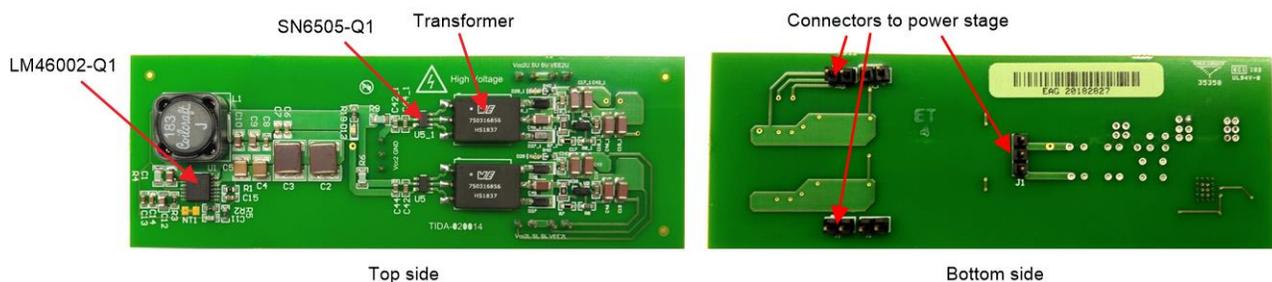


Figure 23 shows the buck with push-pull converter board implemented on top of the power stage and connected with the IGBT module.

**Figure 23. Buck With Push-Pull Bias Supply Connected to the Power Stage**



## 3.2 Testing and Results


### 3.2.1 Low-Voltage Tests on the LM5180-Q1 Flyback Converter

This section presents the experimental results of the bias supply solution 1 which is the flyback converter based on the LM5180-Q1 device.

#### 3.2.1.1 Startup


The start-up waveforms of the flyback converter designed with the LM5180-Q1 device are measured under 5- and 12-V inputs, respectively. The 15-V and -9-V rails are measured separately.

**Figure 24. Start-up Waveform of the 15-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With LM5180-Q1)**

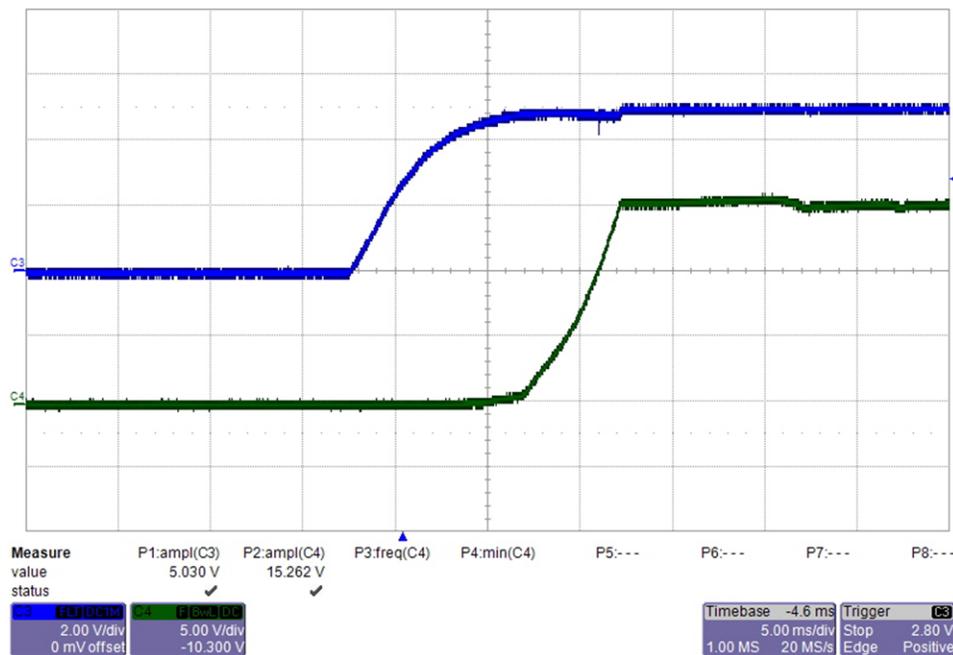


From top to bottom: CH3: input voltage 2 V/div, CH4: output voltage 5 V/div, 5 ms/div

**Figure 25. Start-up Waveform of the -9-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With LM5180-Q1)**

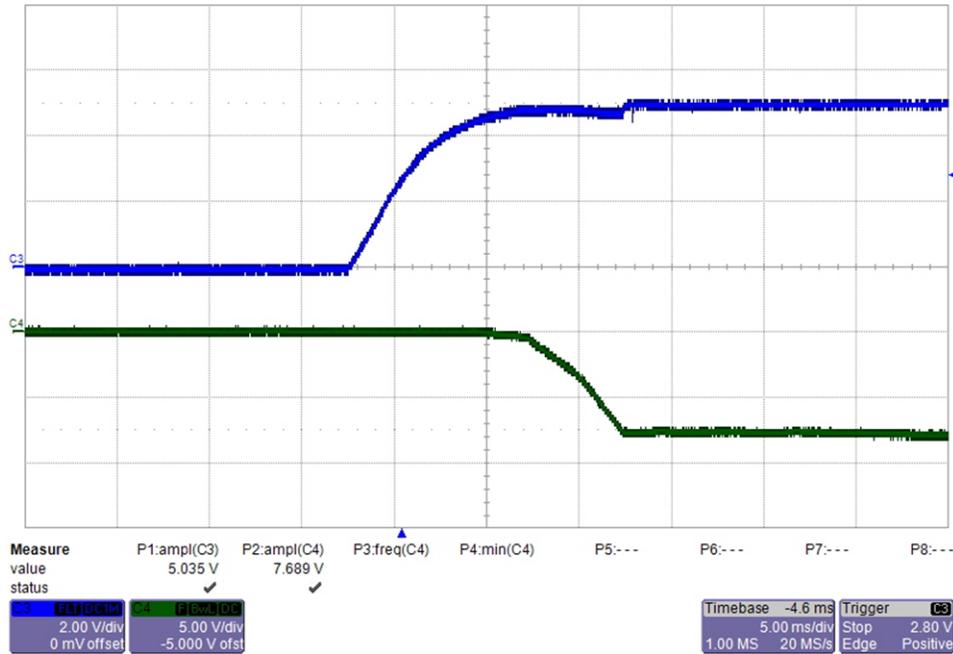


From top to bottom: CH3: input voltage 2 V/div, CH4: output voltage 5 V/div, 5 ms/div

**Figure 26. Start-up Waveform of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With LM5180-Q1)**

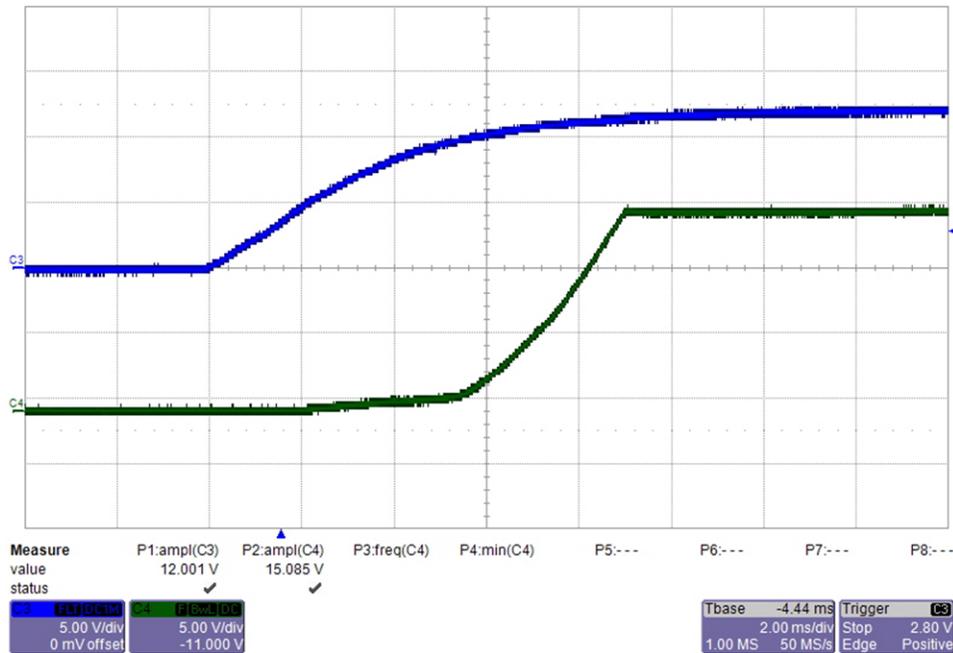

From top to bottom: CH3: input voltage 5 V/div, CH4: output voltage 5 V/div, 2 ms/div

**Figure 27. Start-up Waveform of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With LM5180-Q1)**

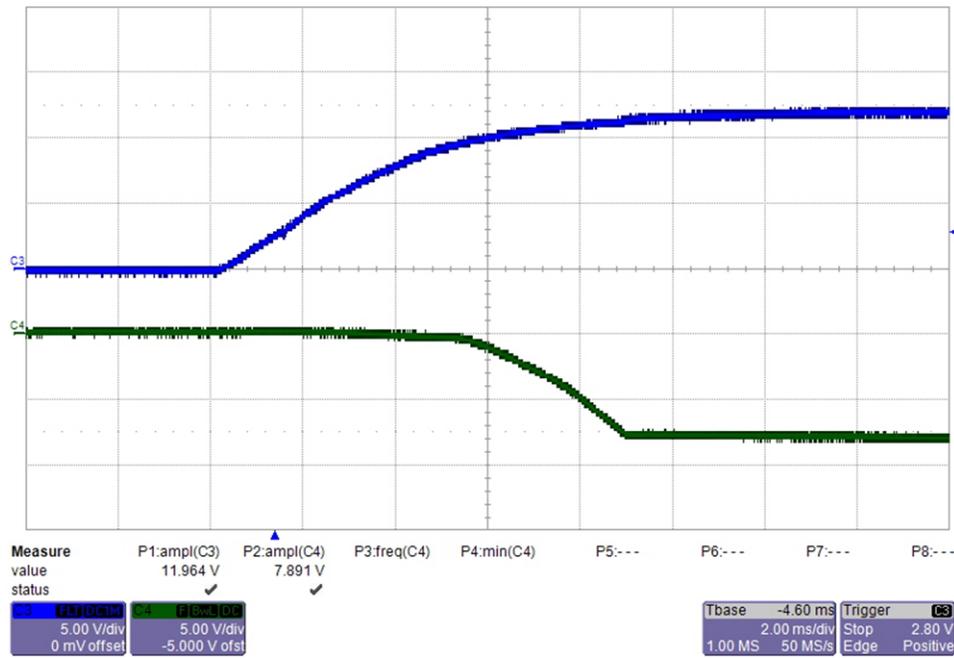


From top to bottom: CH3: input voltage 5 V/div, CH4: output voltage 5 V/div, 2 ms/div

### 3.2.1.2 Power Down


The power-down waveforms of the flyback converter designed with the LM5180-Q1 device are measured under 5- and 12-V inputs, respectively. The 15-V and -9-V rails are measured separately.

**Figure 28. Power-Down Waveform of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With LM5180-Q1)**

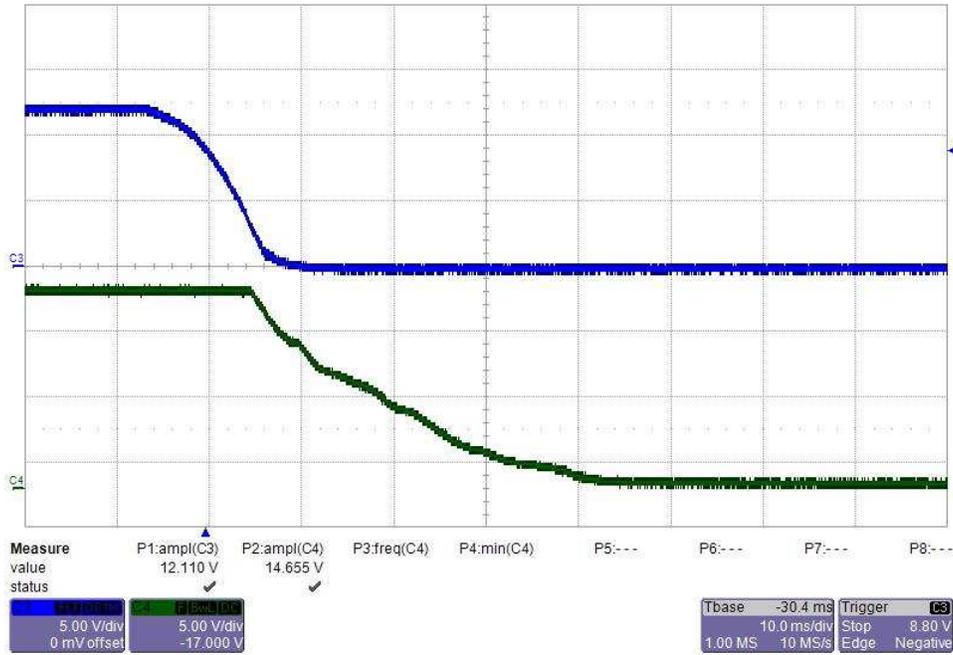

From top to bottom: CH3: input voltage 5 V/div, CH4: output voltage 5 V/div, 10 ms/div

**Figure 29. Power-Down Waveform of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With LM5180-Q1)**

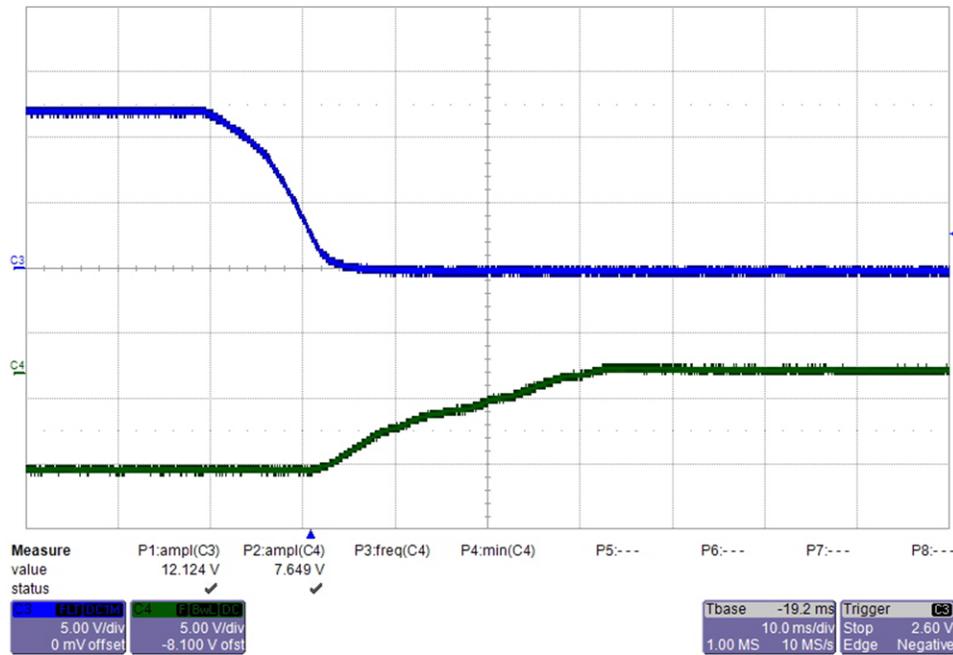


From top to bottom: CH3: input voltage 5 V/div, CH4: output voltage 5 V/div, 10 ms/div

### 3.2.1.3 Switch Node and Output Voltage Ripple


The switch node and output voltage ripple of the flyback converter designed with the LM5180-Q1 device are measured under 5-, 12-, and 18-V inputs, respectively. The +15-V and -9-V rails are measured separately.

**Figure 30. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With LM5180-Q1)**

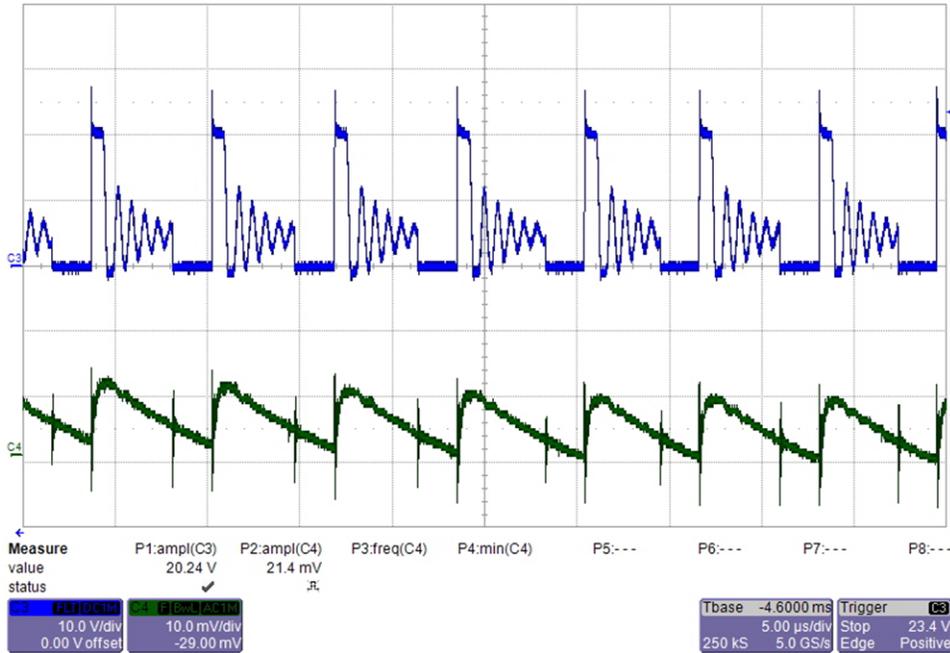


From top to bottom: CH3: switch node 10 V/div, CH4: output voltage ripple 10 mV/div, 5 μs/div

**Figure 31. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 5\text{ V}$  and 85-mA Load (Bias Supply With LM5180-Q1)**

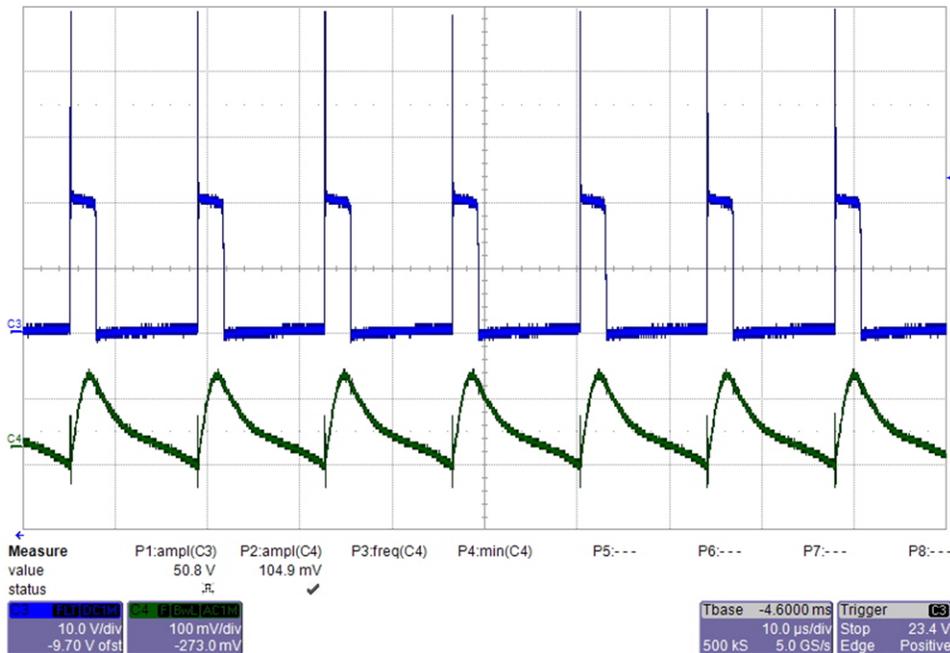


From top to bottom: CH3: switch node 10 V/div, CH4: output voltage ripple 100 mV/div, 10 μs/div

**Figure 32. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With LM5180-Q1)**

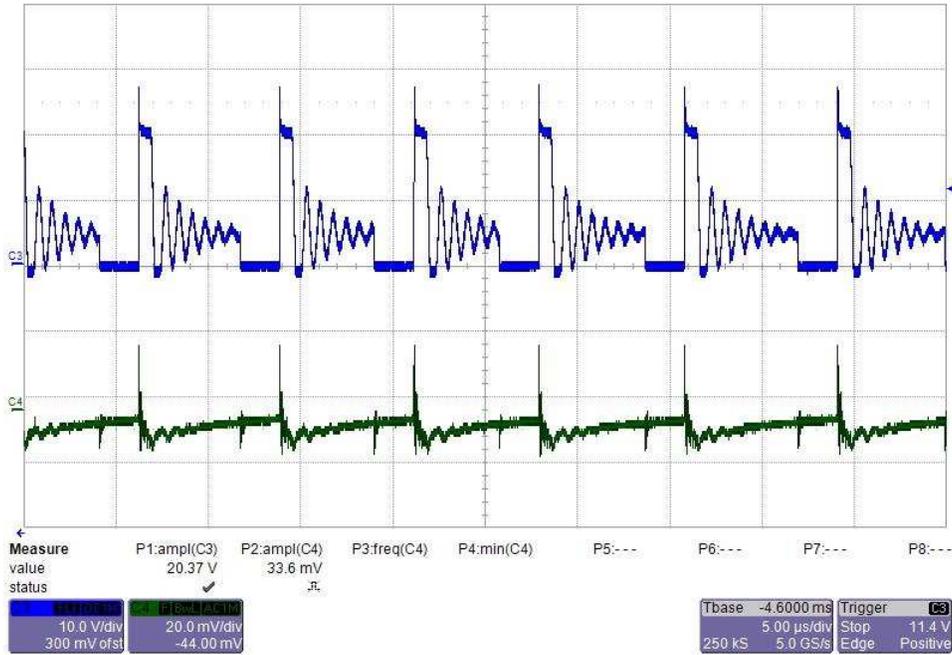


From top to bottom: CH3: switch node 10 V/div, CH4: output voltage ripple 20 mV/div, 5 µs/div

**Figure 33. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 5\text{ V}$  and 85-mA Load (Bias Supply With LM5180-Q1)**

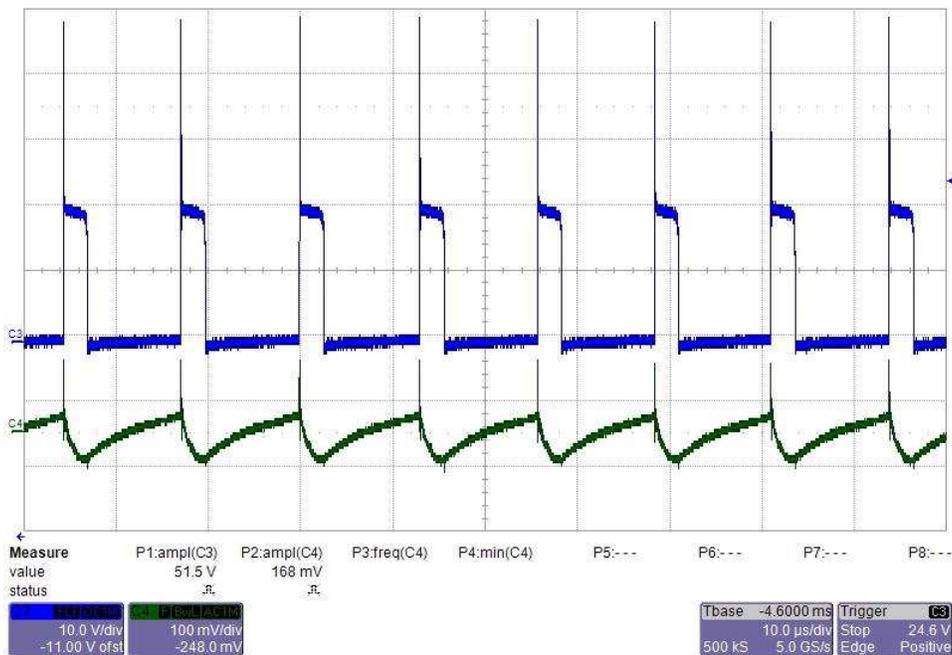


From top to bottom: CH3: switch node 10 V/div, CH4: output voltage ripple 100 mV/div, 10 µs/div

**Figure 34. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With LM5180-Q1)**

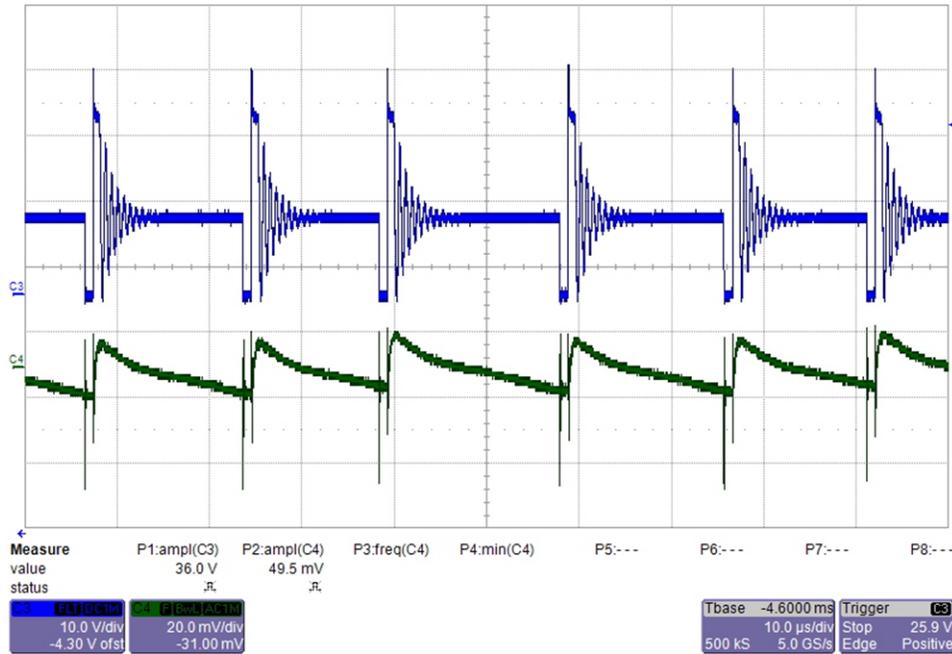


From top to bottom: CH3: switch node 10 V/div, CH4: output voltage ripple 20 mV/div, 10  $\mu\text{s}$ /div

**Figure 35. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With LM5180-Q1)**

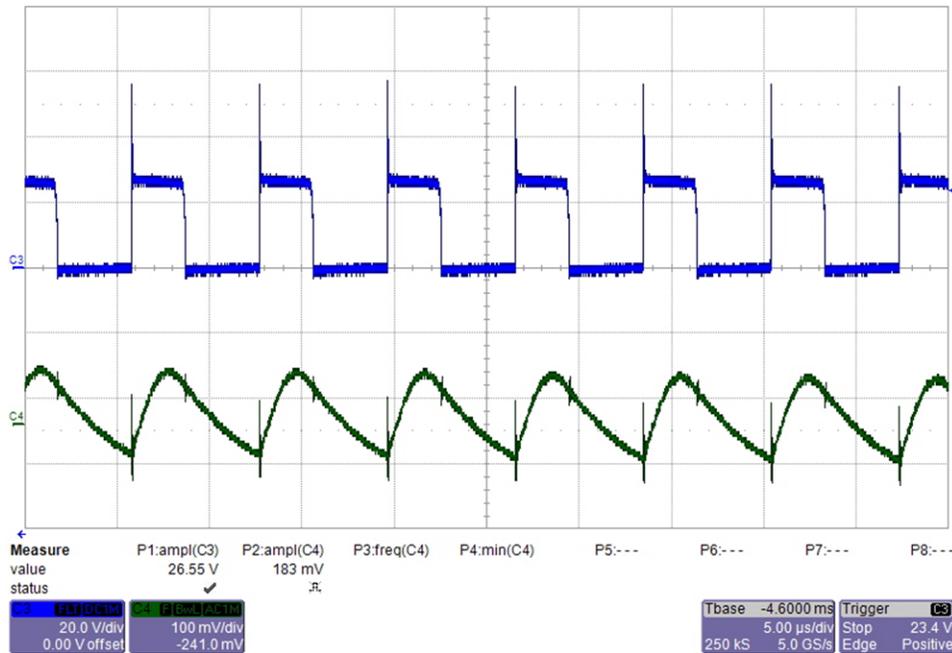


From top to bottom: CH3: switch node 20 V/div, CH4: output voltage ripple 100 mV/div, 5  $\mu\text{s}$ /div

Figure 36. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With LM5180-Q1)

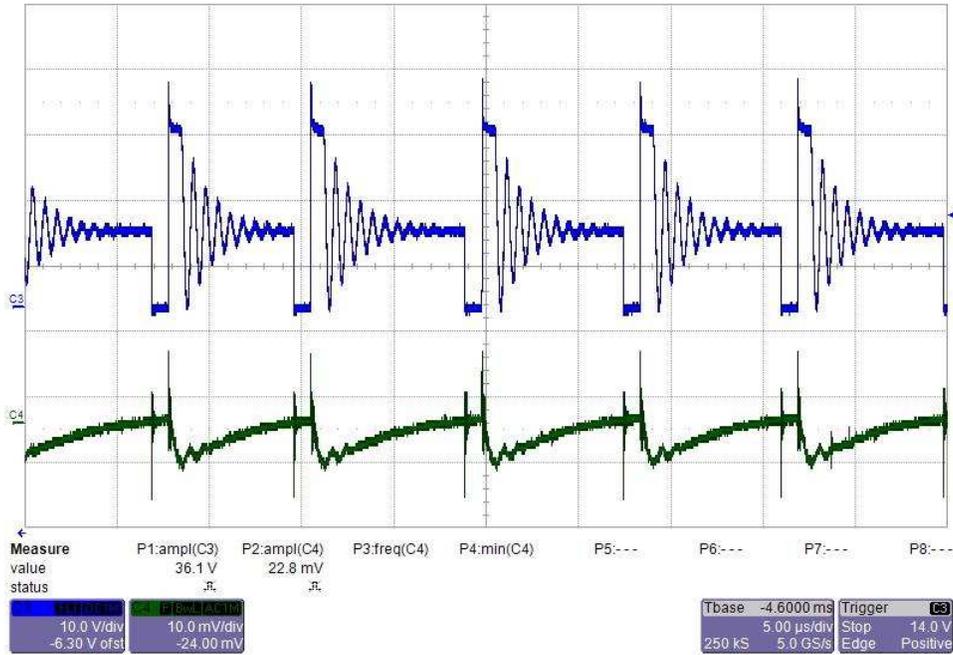


From top to bottom: CH3: switch node 10 V/div, CH4: output voltage ripple 10 mV/div, 5  $\mu$ s/div

Figure 37. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With LM5180-Q1)

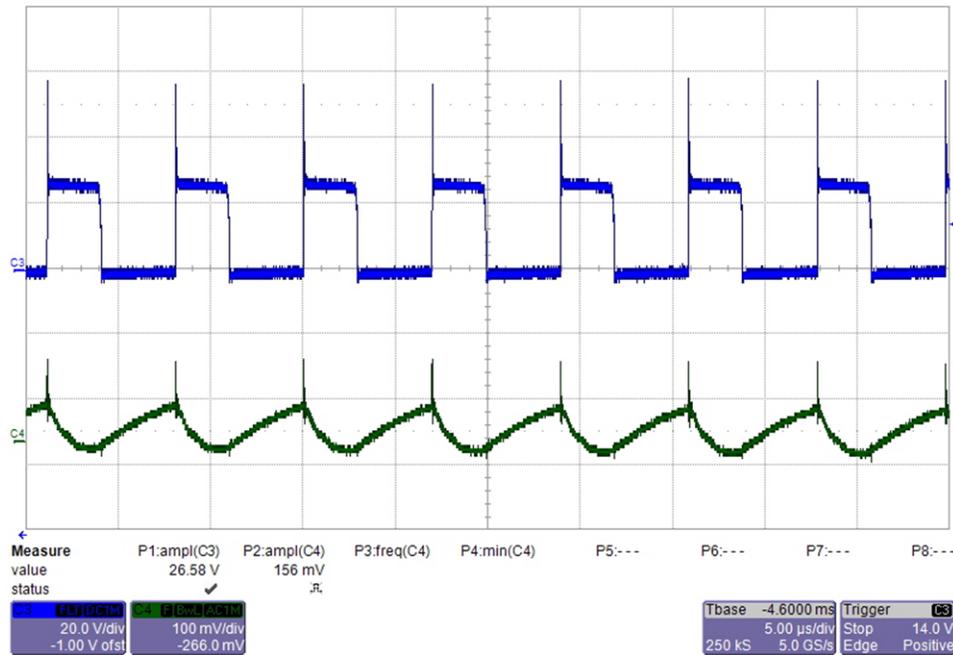


From top to bottom: CH3: switch node 20 V/div, CH4: output voltage ripple 100 mV/div, 5  $\mu$ s/div

**Figure 38. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 18\text{ V}$  and no Load (Bias Supply With LM5180-Q1)**

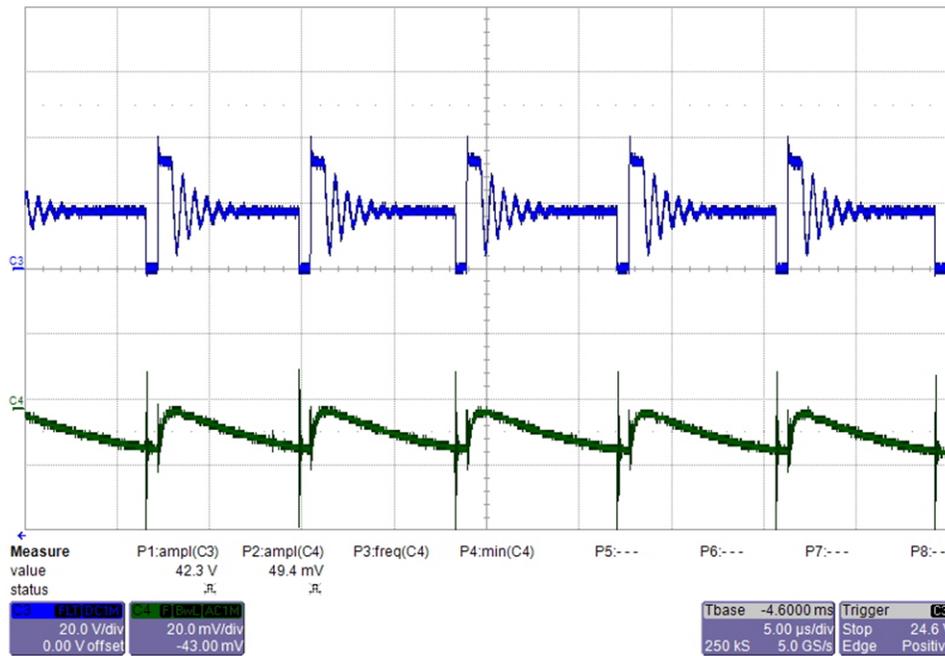


From top to bottom: CH3: switch node 20 V/div, CH4: output voltage ripple 20 mV/div, 5 μs/div

**Figure 39. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 18\text{ V}$  and 180-mA Load (Bias Supply With LM5180-Q1)**

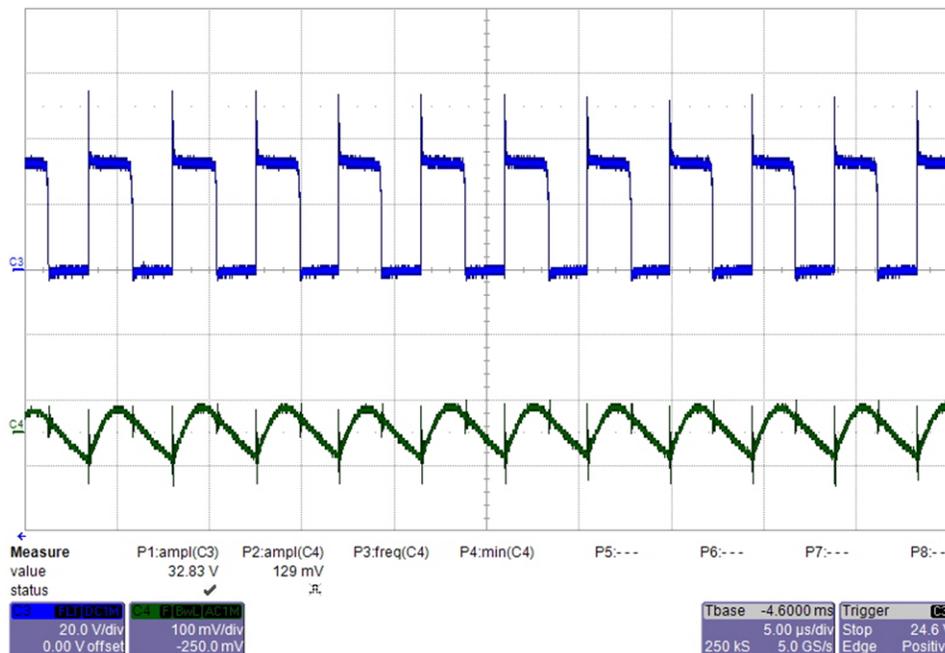


From top to bottom: CH3: switch node 20 V/div, CH4: output voltage ripple 100 mV/div, 5 μs/div

**Figure 40. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 18\text{ V}$  and no Load (Bias Supply With LM5180-Q1)**

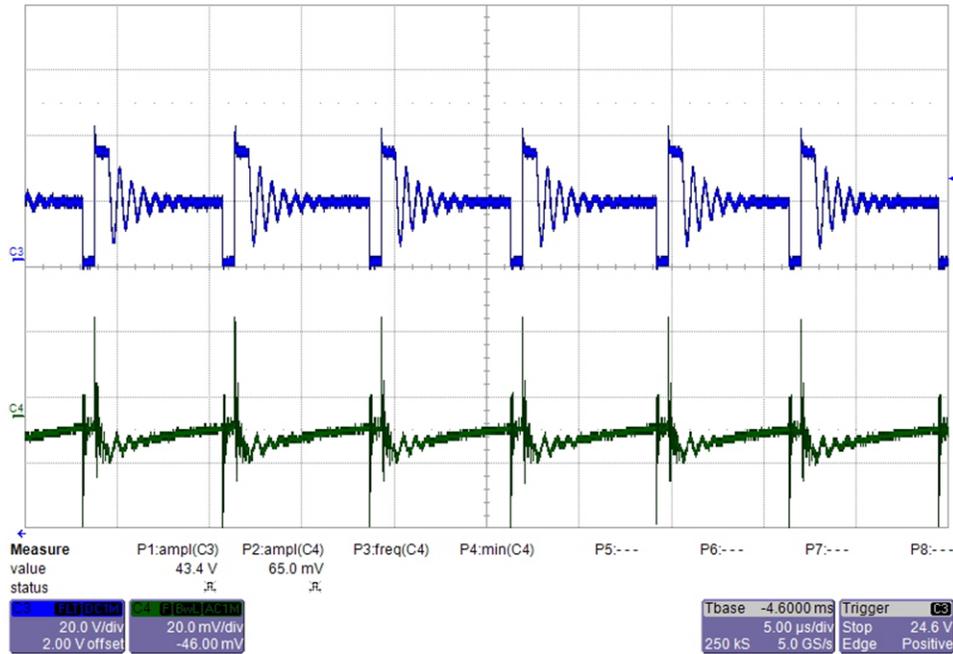

From top to bottom: CH3: switch node 20 V/div, CH4: output voltage ripple 20 mV/div, 5 μs/div

**Figure 41. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 18\text{ V}$  and 180-mA Load (Bias Supply With LM5180-Q1)**

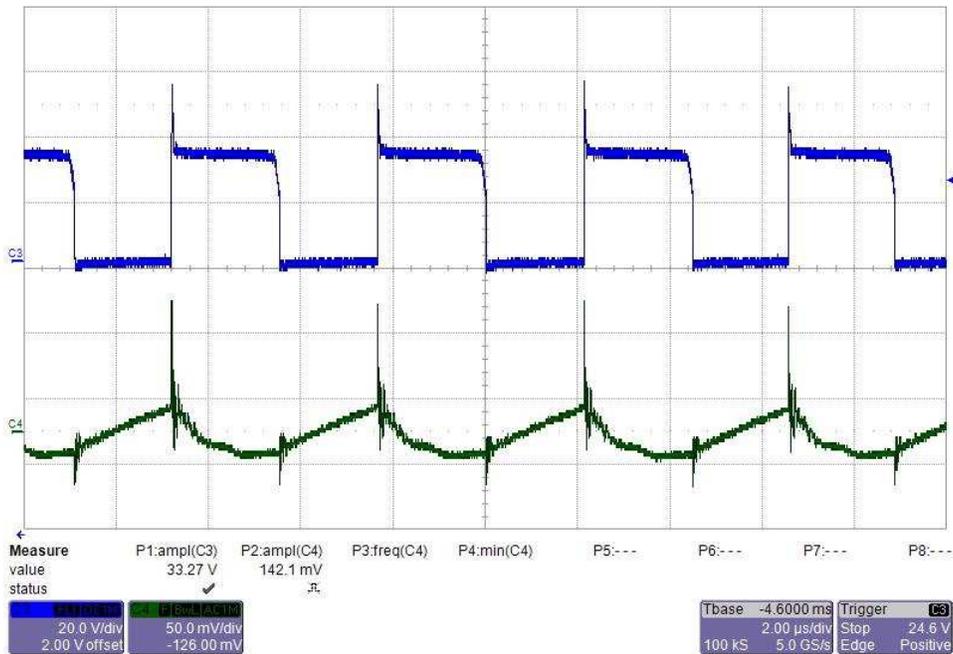


From top to bottom: CH3: switch node 20 V/div, CH4: output voltage ripple 50 mV/div, 2 μs/div

### 3.2.1.4 Efficiency

Figure 42 shows the measured efficiency of the flyback converter designed with the LM5180-Q1 device over the full-load range. As can be seen, around 86% peak efficiency is achieved with the input voltages of 5 V, 12 V, and 18 V, respectively.


**Figure 42. Measured Efficiency Under Input Voltages of 5 V, 12 V, and 18 V (Bias Supply With LM5180-Q1)**

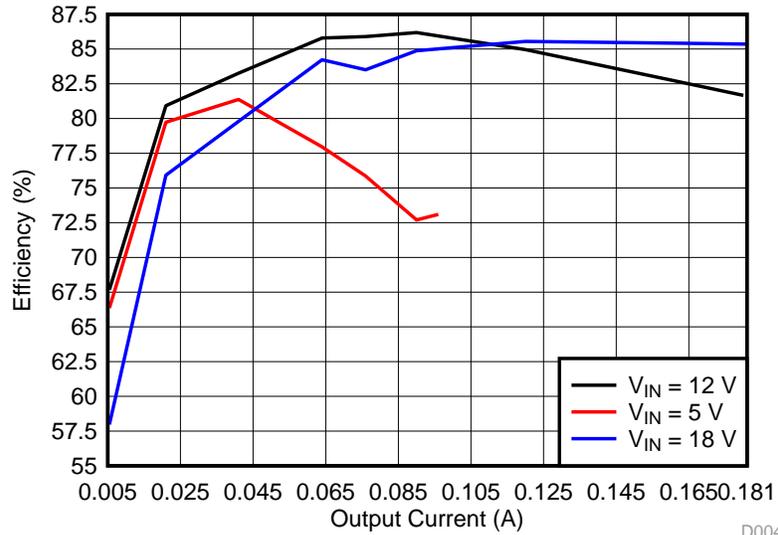

### 3.2.1.5 Load Regulation

Load regulation measurements show the % deviation from nominal output voltage as a function of output current. The measured result of the flyback converter designed with LM5180-Q1 is shown in Figure 43. The load regulation is measured with the input voltages of 5 V, 12 V, and 18 V, respectively.


**Figure 43. Load Regulation Under Input Voltages of 5 V, 12 V, and 18 V (Bias Supply With LM5180-Q1)**

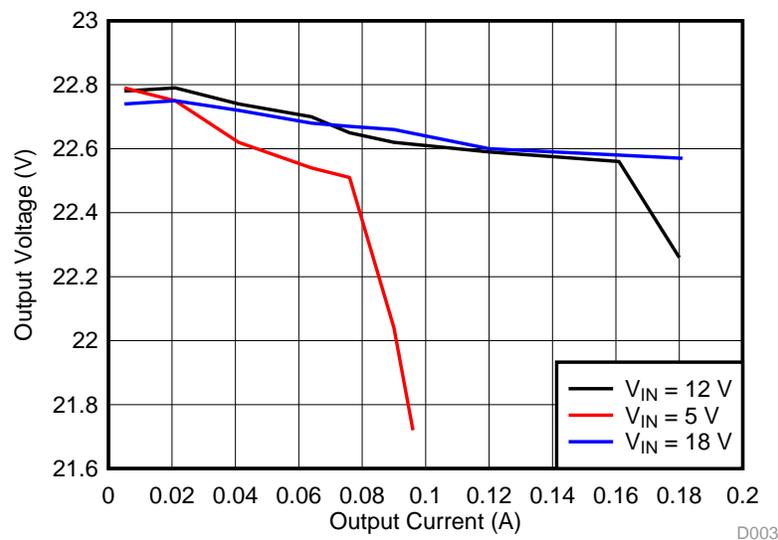

### 3.2.1.6 Load Transients


This section shows the load transient measurements of the flyback converter designed with the LM5180-Q1 device. The load transient response presents how well a power supply copes with the changes in the load-current demand. During the test, the load is switching from 0 to full under input voltages of 5 V, 12 V, and 18 V, respectively.

**Figure 44. Load Transient Response of the 15-V Rail Under  $V_{IN} = 5\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 80 mA (Bias Supply With LM5180-Q1)**

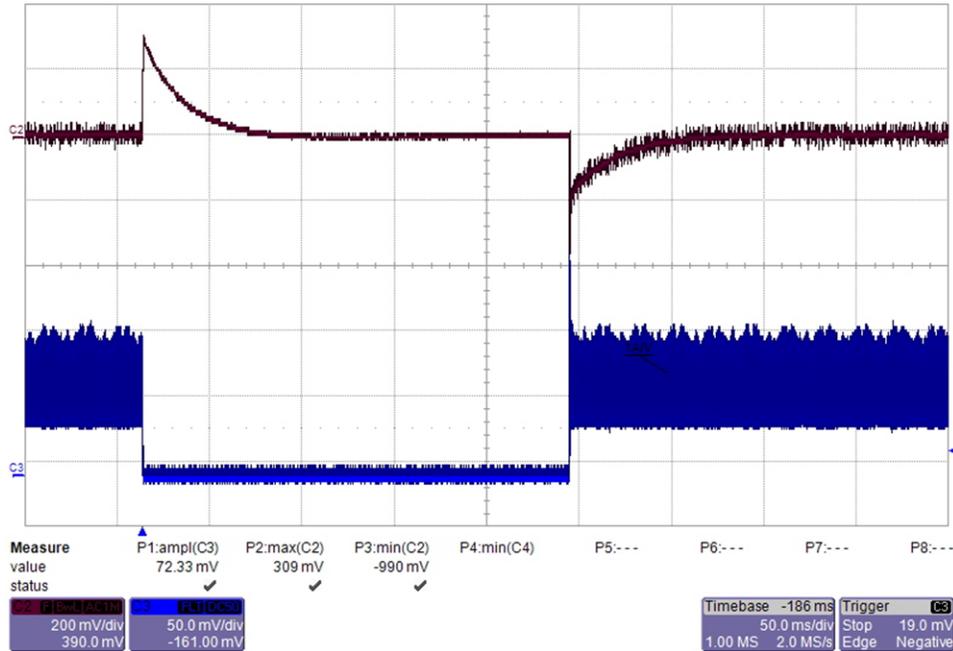


From top to bottom: CH2: output voltage 200 mV/div, CH3: load current 500 mA/div, 50 ms/div

**Figure 45. Load Transient Response of the -9-V Rail Under  $V_{IN} = 5\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 80 mA (Bias Supply With LM5180-Q1)**

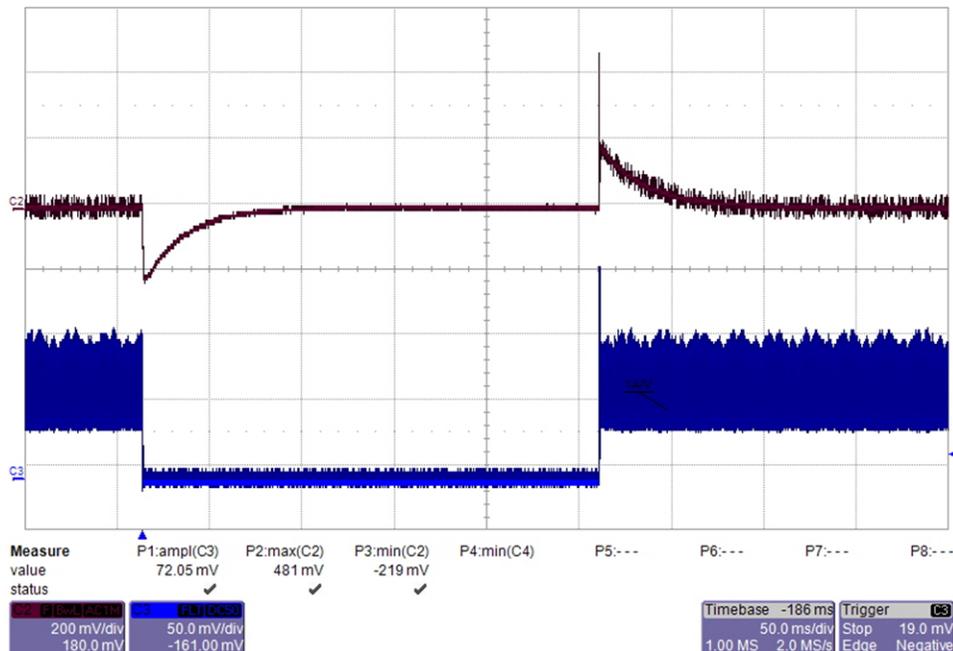


From top to bottom: CH2: output voltage 200 mV/div, CH3: load current 500 mA/div, 50 ms/div

**Figure 46. Load Transient Response of the 15-V Rail Under  $V_{IN} = 12\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With LM5180-Q1)**

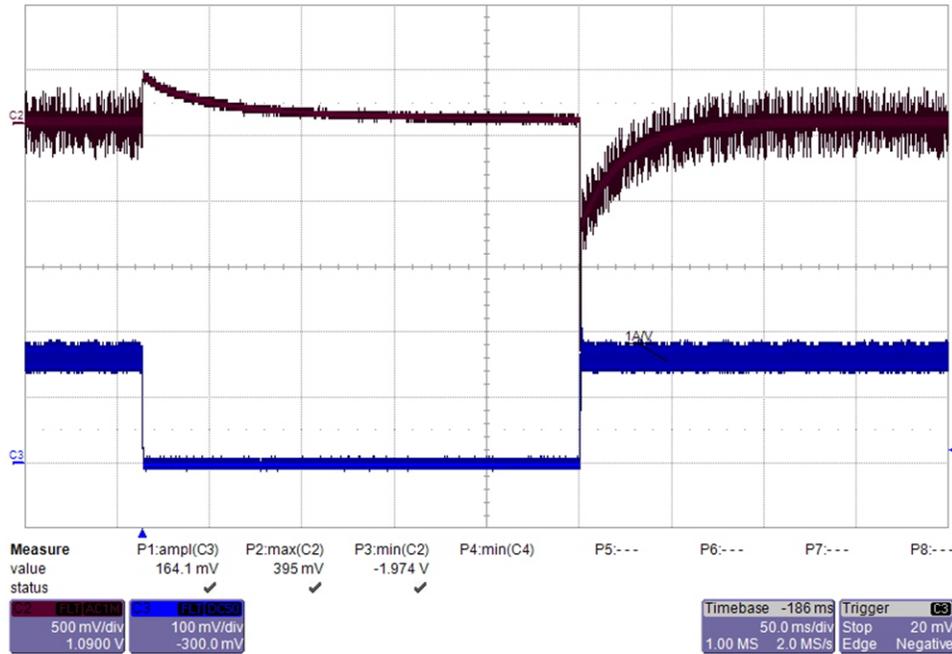


From top to bottom: CH2: output voltage 500 mV/div, CH3: load current 1 A/div, 50 ms/div

**Figure 47. Load Transient Response of the -9-V Rail Under  $V_{IN} = 12\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With LM5180-Q1)**

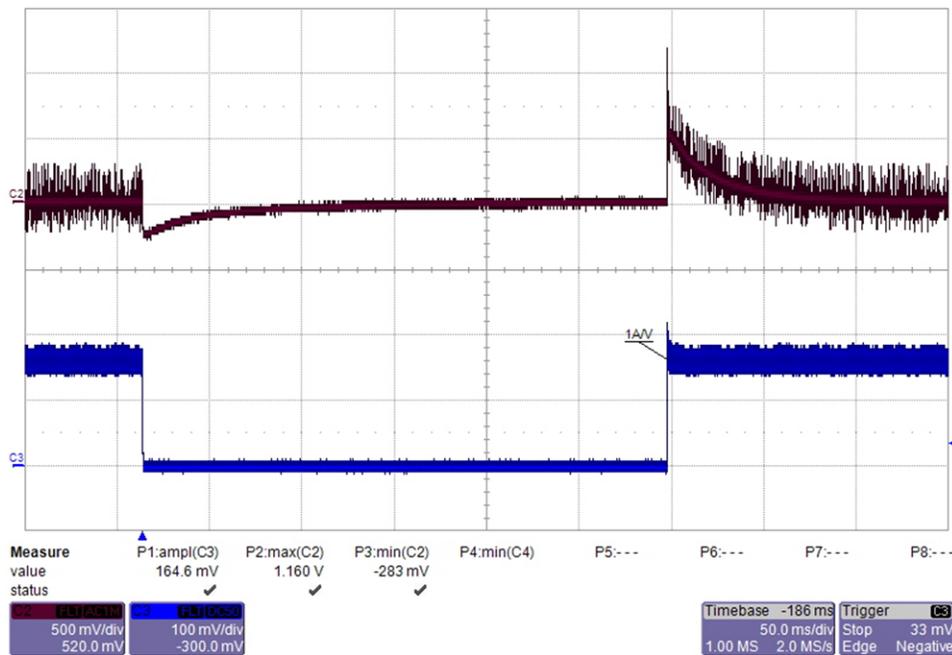


From top to bottom: CH2: output voltage 500 mV/div, CH3: load current 1 A/div, 50 ms/div

Figure 48. Load Transient Response of the 15-V Rail Under  $V_{IN} = 18\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With LM5180-Q1)

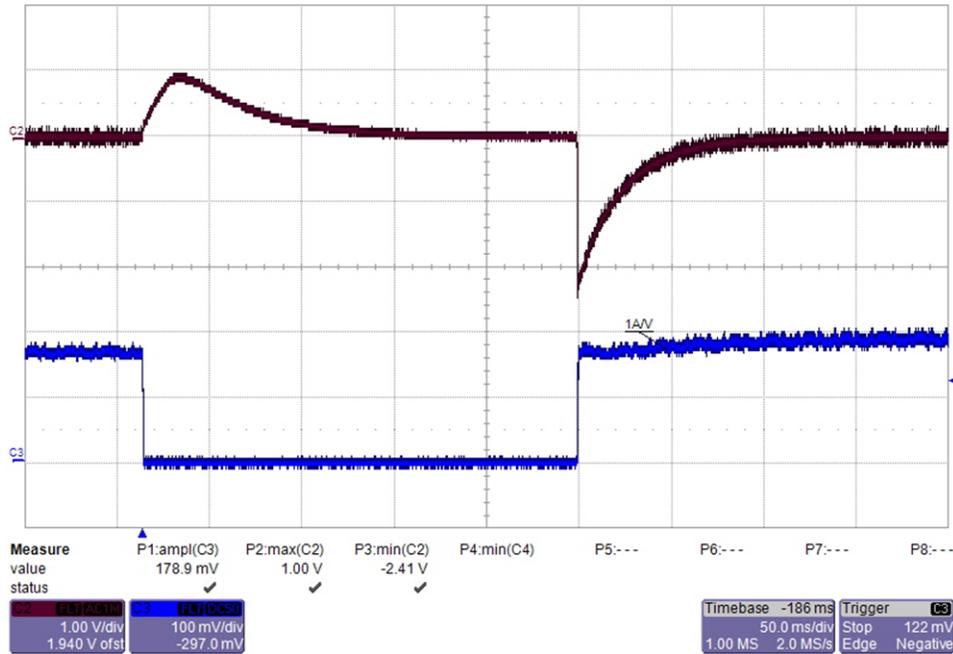

From top to bottom: CH2: output voltage 1 V/div, CH3: load current 1 A/div, 50 ms/div

Figure 49. Load Transient Response of the -9-V Rail Under  $V_{IN} = 18\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With LM5180-Q1)

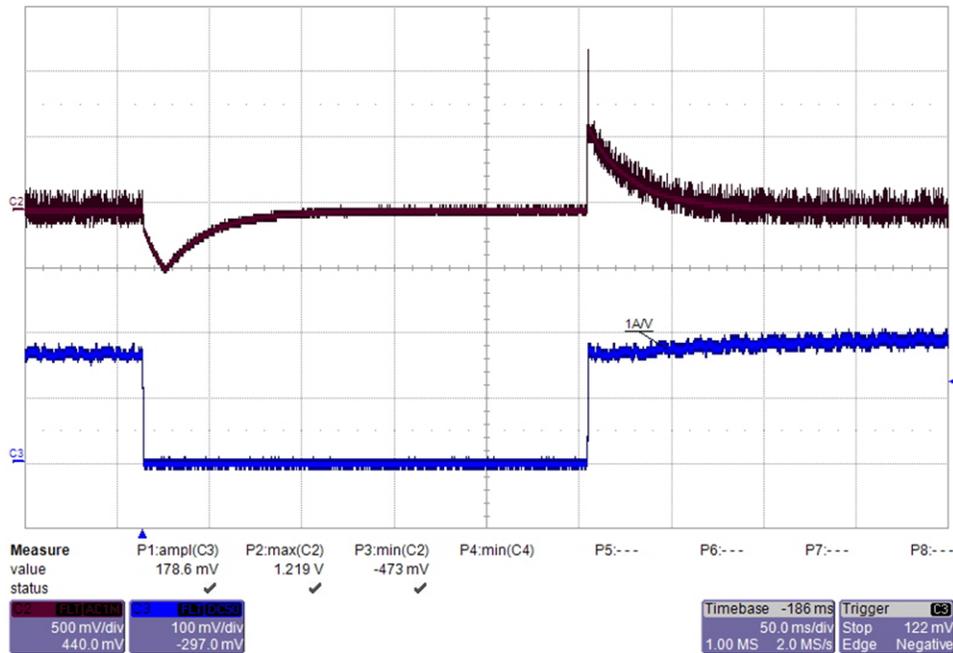


From top to bottom: CH2: output voltage 500 mV/div, CH3: load current 1 A/div, 50 ms/div

### 3.2.1.7 Voltage Ripple While Switching IGBT


The flyback converter designed with the LM5180-Q1 device is connected to the isolated gate drivers (ISO5852S-Q1) and the 1200-V IGBT module (FF150R12MS4G) for checking the voltage ripple during the switching transients. The IGBTs are switched at 20- and 50-kHz frequencies, respectively.

**Figure 50. Voltage Ripple of the 15-V Rail While Switching the IGBT Module at 20 kHz (Bias Supply With LM5180-Q1)**

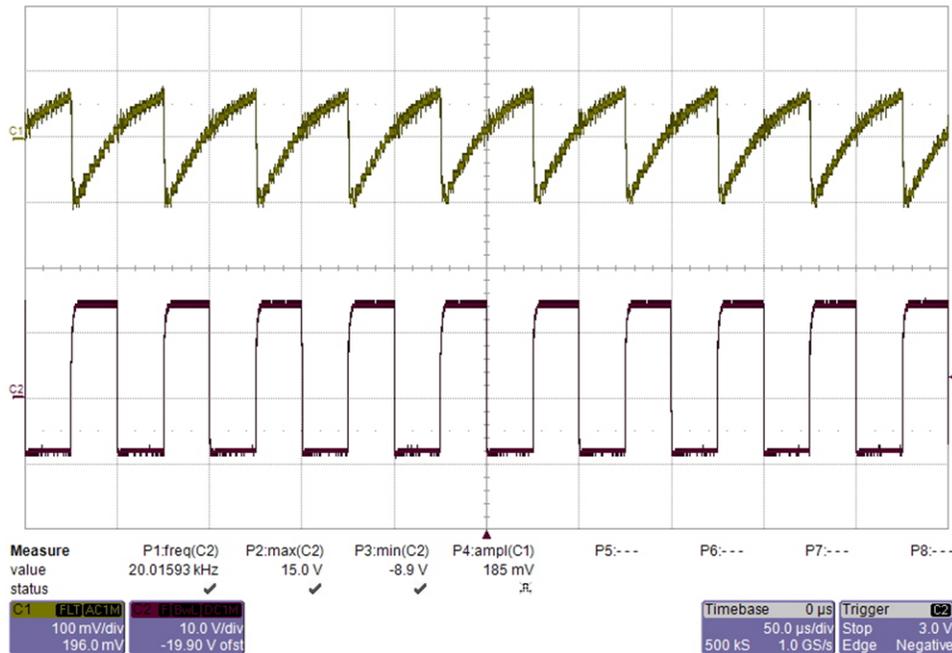


From top to bottom: CH1: output voltage 100 mV/div, CH2: gate PWM signal 10 V/div, 50 μs/div

**Figure 51. Voltage Ripple of the -9-V Rail While Switching the IGBT Module at 20 kHz (Bias Supply With LM5180-Q1)**

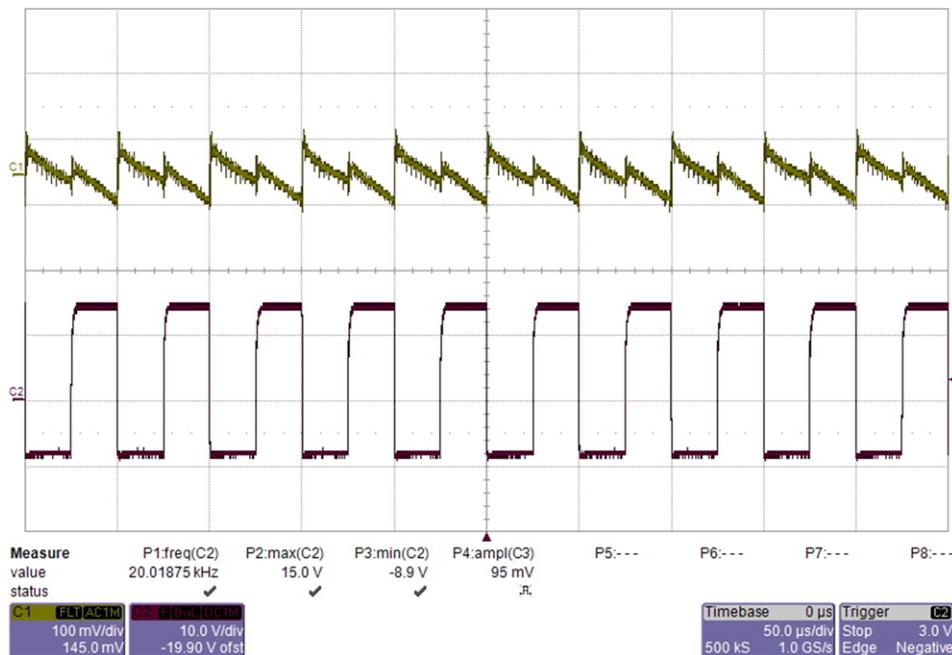


From top to bottom: CH1: output voltage 100 mV/div, CH2: gate PWM signal 10 V/div, 50 μs/div

**Figure 52. Voltage Ripple of the 15-V Rail While Switching the IGBT Module at 50 kHz (Bias Supply With LM5180-Q1)**

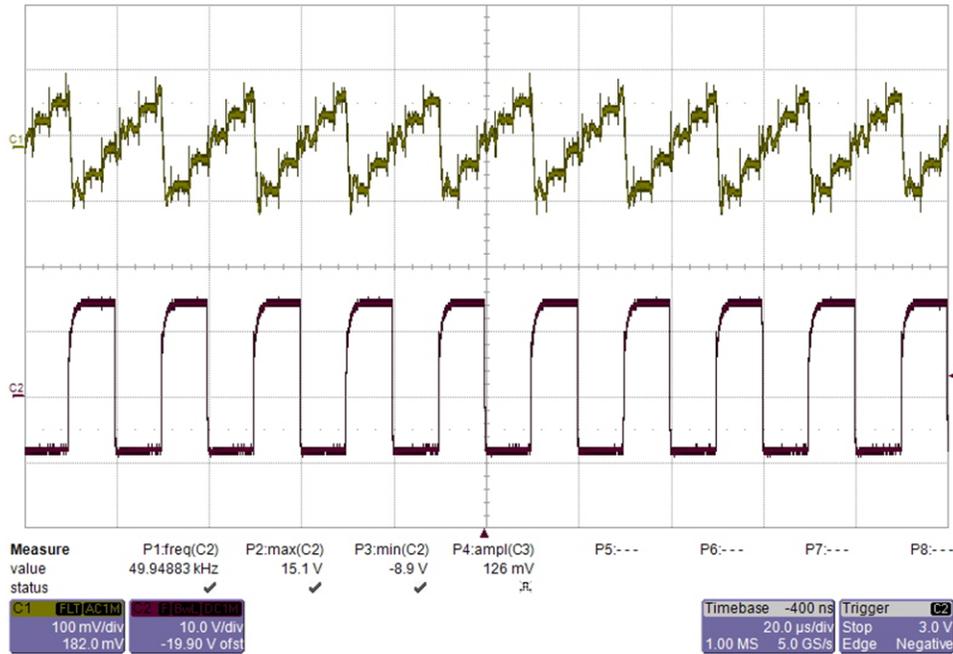

From top to bottom: CH1: output voltage 100 mV/div, CH2: gate PWM signal 10 V/div, 20  $\mu$ s/div

**Figure 53. Voltage Ripple of the -9-V Rail While Switching the IGBT Module at 50 kHz (Bias Supply With LM5180-Q1)**

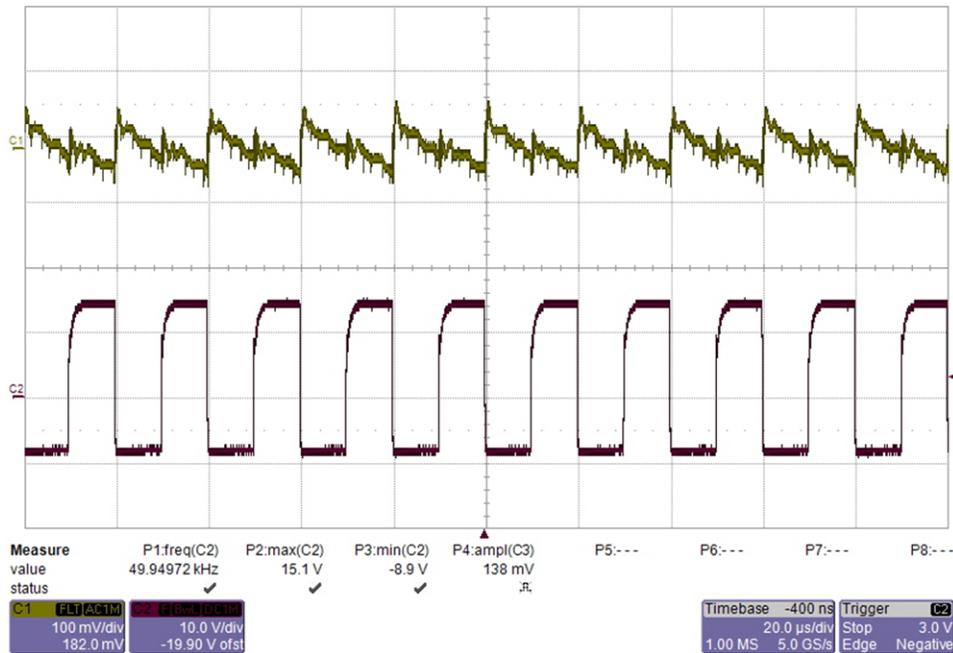


From top to bottom: CH1: output voltage 100 mV/div, CH2: gate PWM signal 10 V/div, 20  $\mu$ s/div

### 3.2.1.8 Thermal Image

The thermal of the flyback converter designed with the LM5180-Q1 device is measured under the full-load conditions. The circuit runs at the room temperature for 30 minutes. A 12-V nominal voltage is applied. The converter is loaded with 180 mA. [Figure 54](#) shows the thermal image of the board.

**Figure 54. Thermal Image With  $V_{IN} = 12\text{ V}$  and  $I_{OUT} = 180\text{ mA}$  (Bias Supply With LM5180-Q1)**

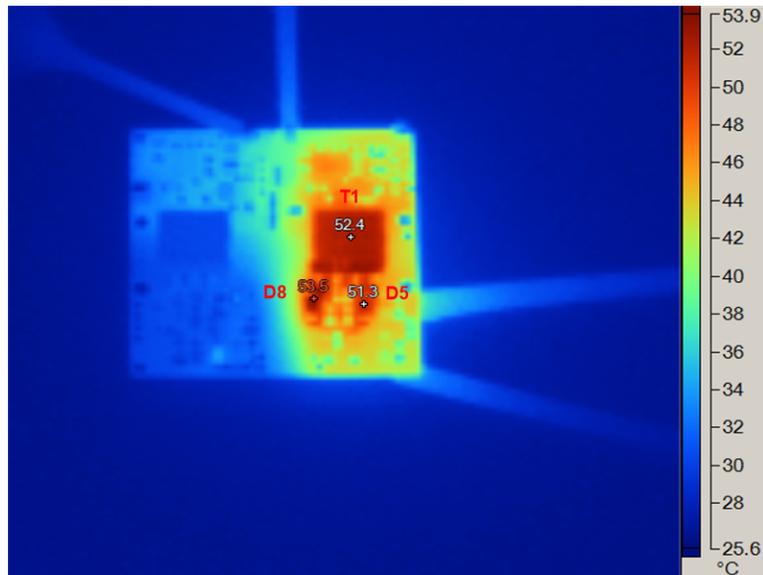

T1: Flyback transformer, D8 and D5: secondary rectification diode


### 3.2.2 Low-Voltage Tests on the TPS40210-Q1 Flyback Converter

This section presents the experimental results of the bias supply solution 2 which is the flyback converter based on the TPS40210-Q1 device.

#### 3.2.2.1 Startup


The startup waveforms of the flyback converter designed with the TPS40210-Q1 device are measured under 5- and 12-V inputs, respectively. The +15-V and -9-V rails are measured separately.

**Figure 55. Start-up Waveform of the 15-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With TPS40210-Q1)**

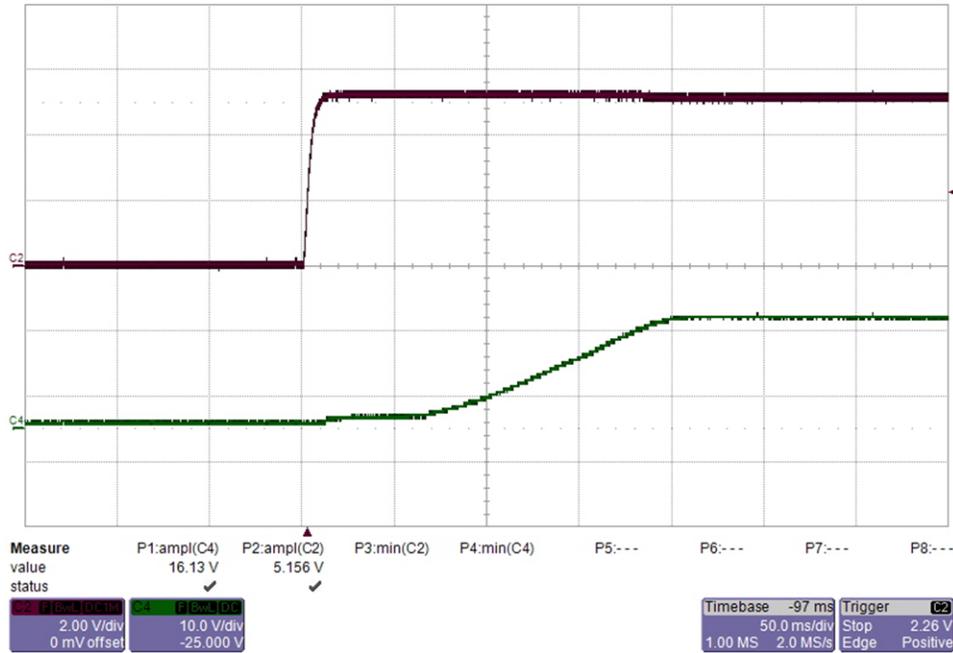


From top to bottom: CH2: input voltage 2 V/div, CH4: output voltage 10 V/div, 50 ms/div

**Figure 56. Start-up Waveform of the -9-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With TPS40210-Q1)**

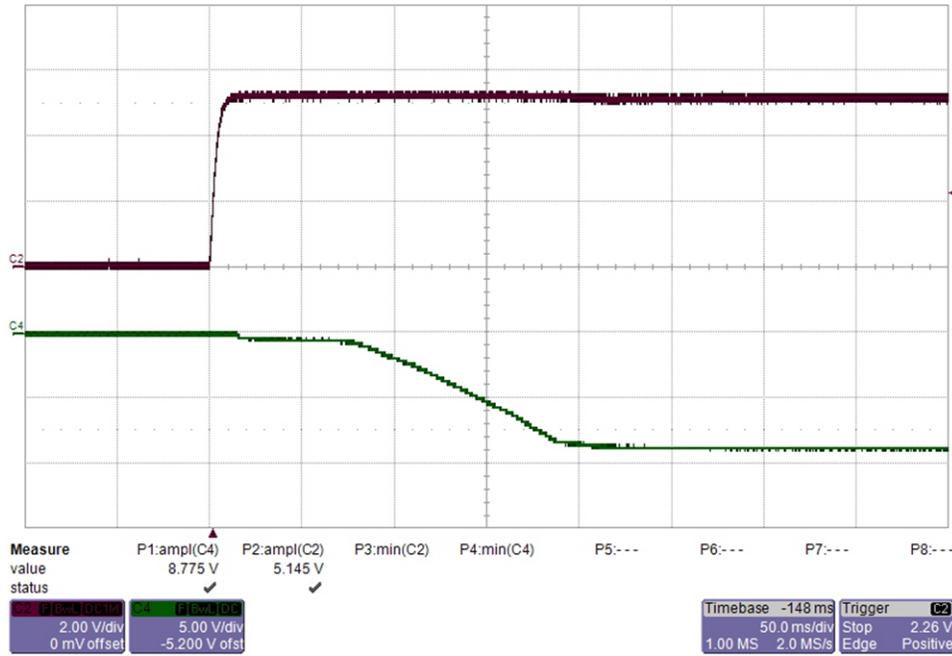


From top to bottom: CH2: input voltage 2 V/div, CH4: output voltage 5 V/div, 50 ms/div

**Figure 57. Start-up Waveform of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With TPS40210-Q1)**

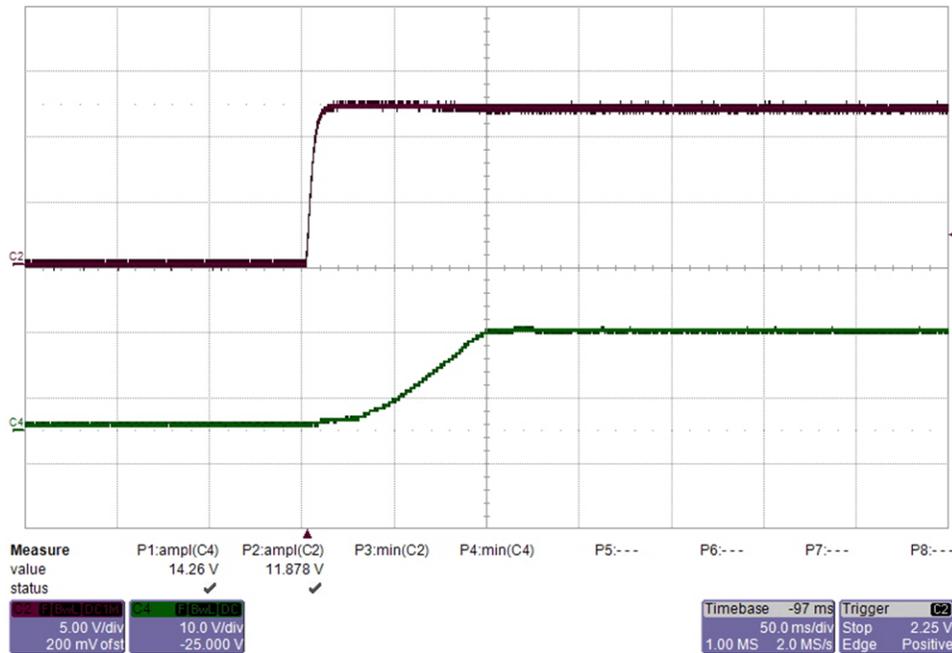

From top to bottom: CH2: input voltage 5 V/div, CH4: output voltage 10 V/div, 50 ms/div

**Figure 58. Start-up Waveform of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With TPS40210-Q1)**

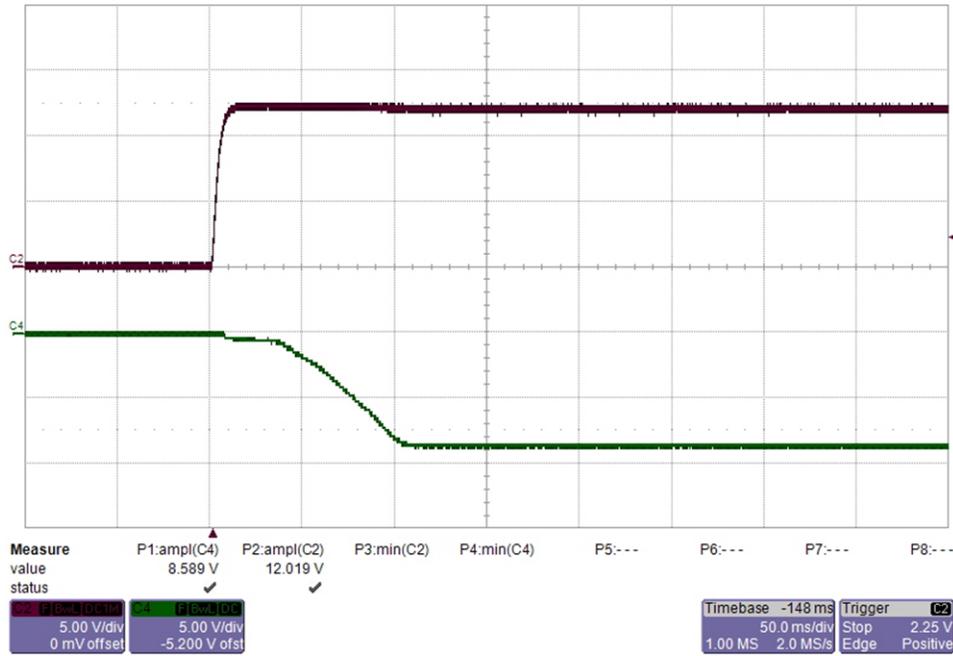


From top to bottom: CH2: input voltage 5 V/div, CH4: output voltage 5 V/div, 50 ms/div

### 3.2.2.2 Power Down

The power down waveforms of the flyback converter designed with the TPS40210-Q1 device are measured under 5- and 12-V inputs, respectively. The +15-V and -9-V rails are measured separately.

**Figure 59. Power-Down Waveform of the 15-V Rail With  $V_{IN} = 12$  V and no Load (Bias Supply With TPS40210-Q1)**

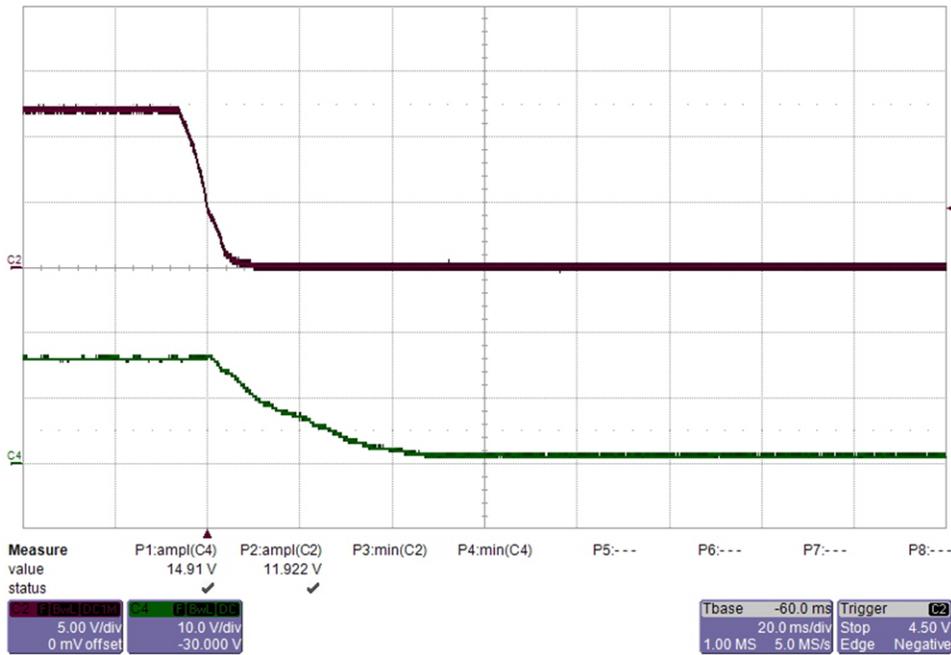

From top to bottom: CH3: input voltage 5 V/div, CH4: output voltage 10 V/div, 20 ms/div

**Figure 60. Power-Down Waveform of the -9-V Rail With  $V_{IN} = 12$  V and no Load (Bias Supply With TPS40210-Q1)**




From top to bottom: CH3: input voltage 5 V/div, CH4: output voltage 5 V/div, 20 ms/div

### 3.2.2.3 Switch Node and Output Voltage Ripple


The switch node and output voltage ripple of the flyback converter designed with the TPS40210-Q1 device are measured under 5-, 12-, and 18-V inputs, respectively. The 15-V and -9-V rails are measured separately.

**Figure 61. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 5$  V and no Load (Bias Supply With TPS40210-Q1)**

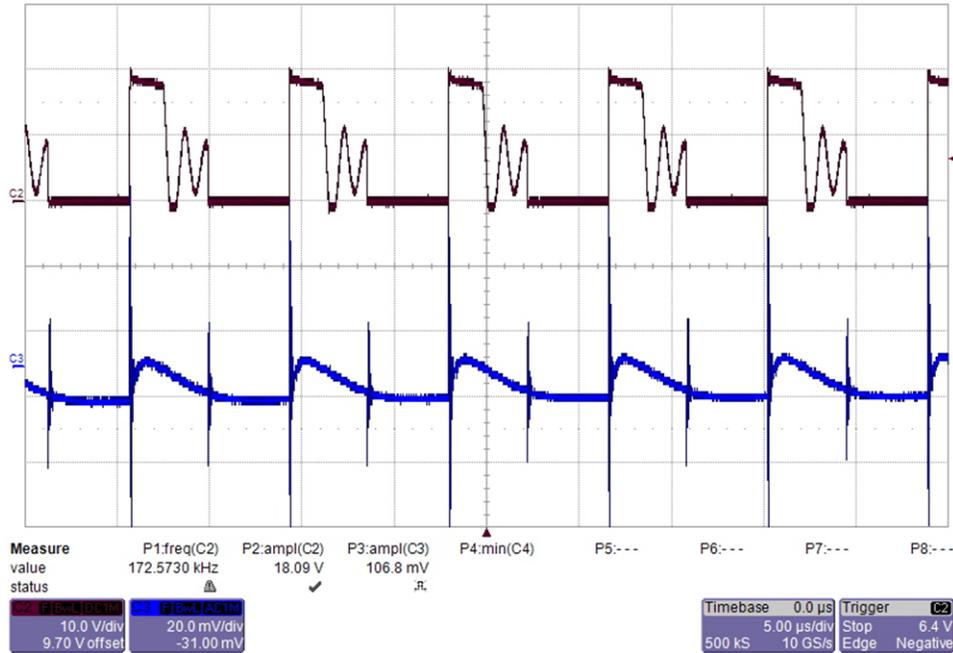


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 20 mV/div, 5 μs/div

**Figure 62. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 5$  V and 80-mA Load (Bias Supply With TPS40210-Q1)**

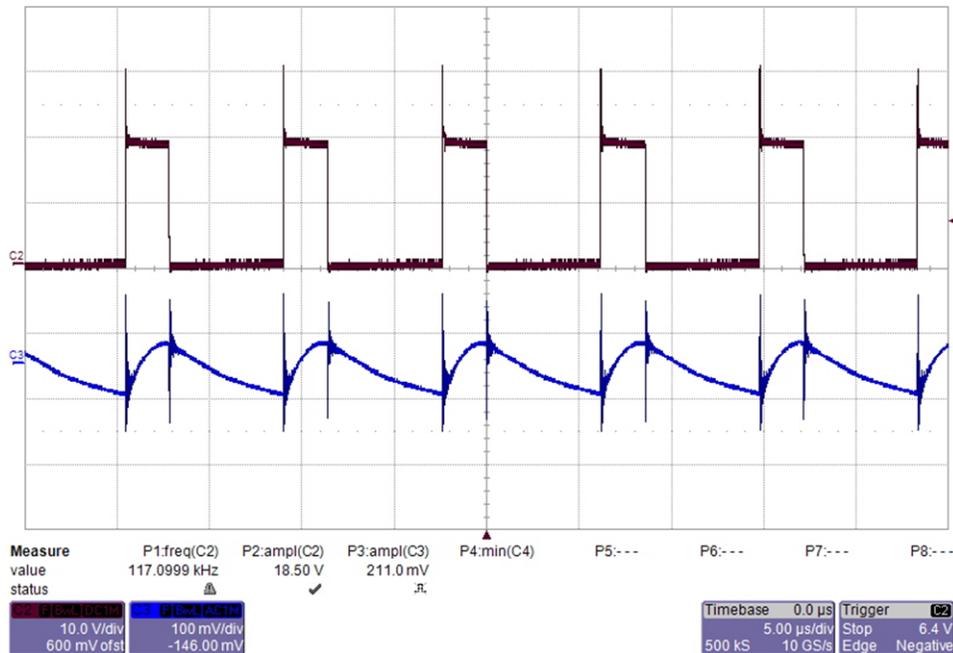


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 100 mV/div, 5 μs/div

**Figure 63. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With TPS40210-Q1)**

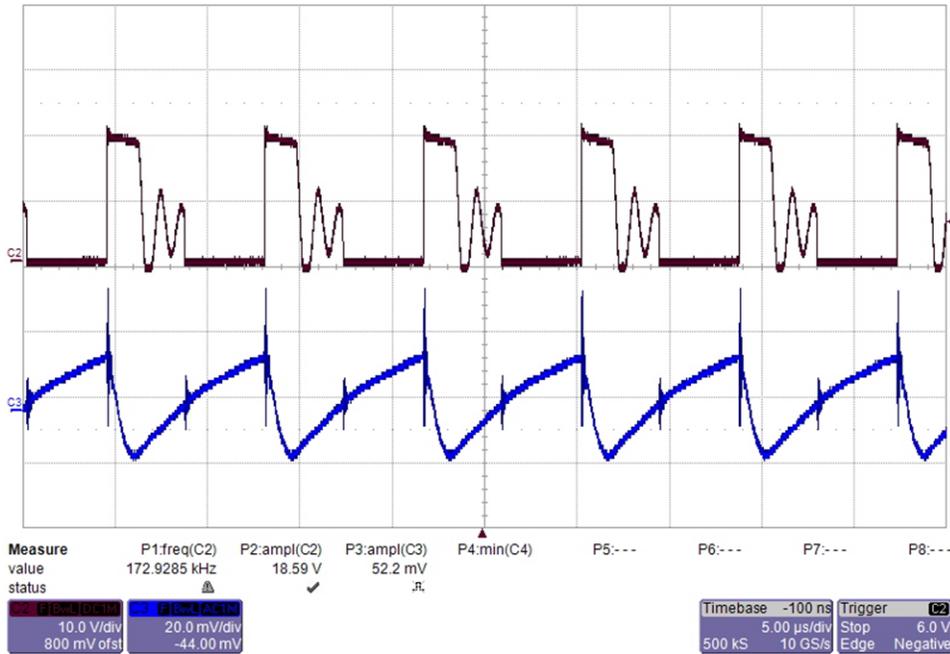


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 20 mV/div, 5  $\mu$ s/div

**Figure 64. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 5\text{ V}$  and 80-mA Load (Bias Supply With TPS40210-Q1)**

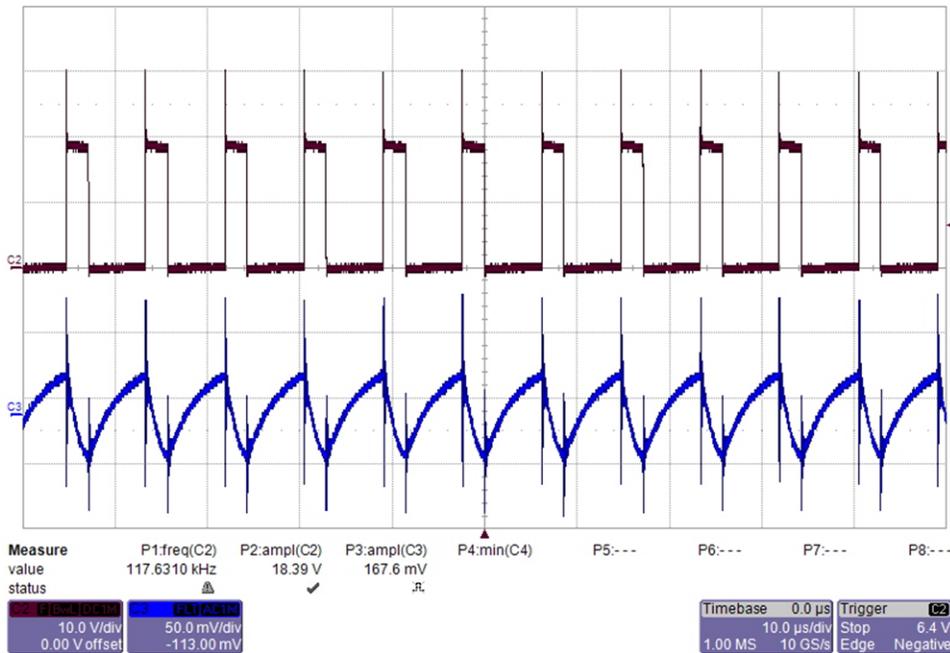


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 50 mV/div, 10  $\mu$ s/div

Figure 65. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With TPS40210-Q1)

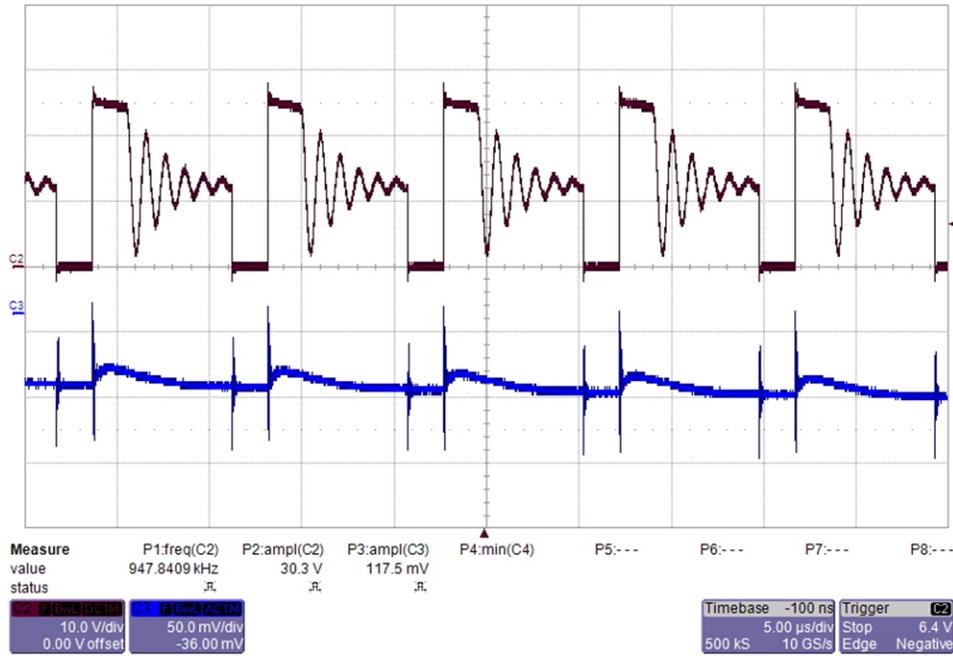


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 50 mV/div, 5  $\mu$ s/div

Figure 66. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With TPS40210-Q1)

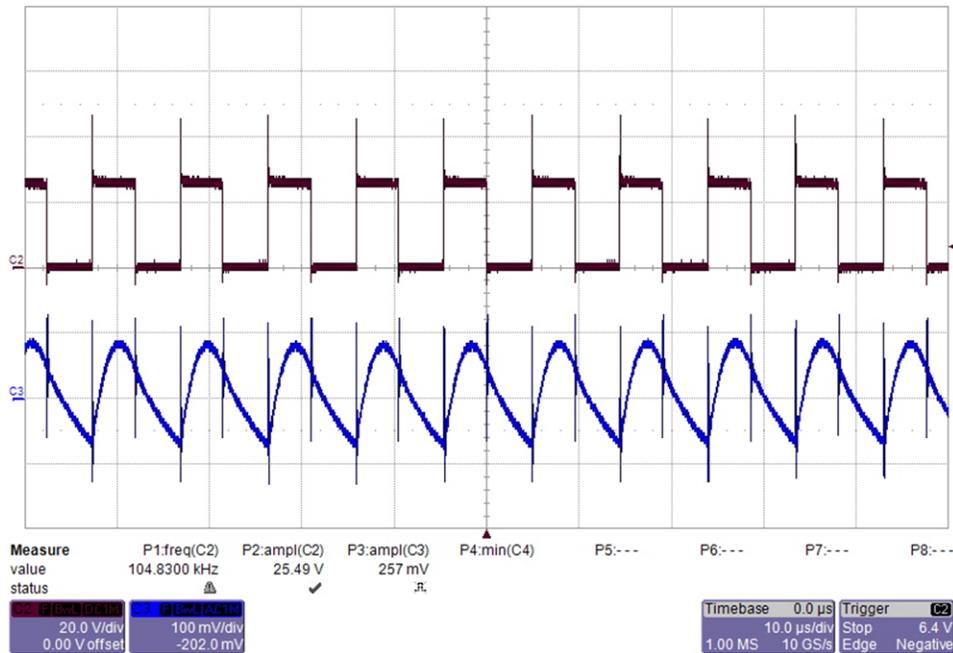


From top to bottom: CH2: switch node 20 V/div, CH3: output voltage ripple 100 mV/div, 10  $\mu$ s/div

**Figure 67. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With TPS40210-Q1)**

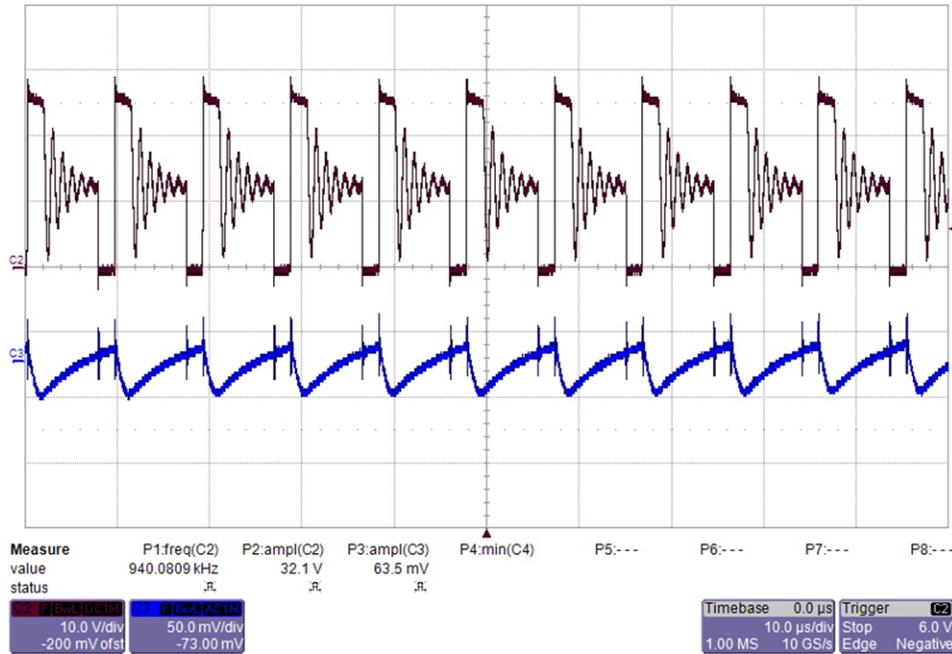


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 50 mV/div, 10 μs/div

**Figure 68. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With TPS40210-Q1)**

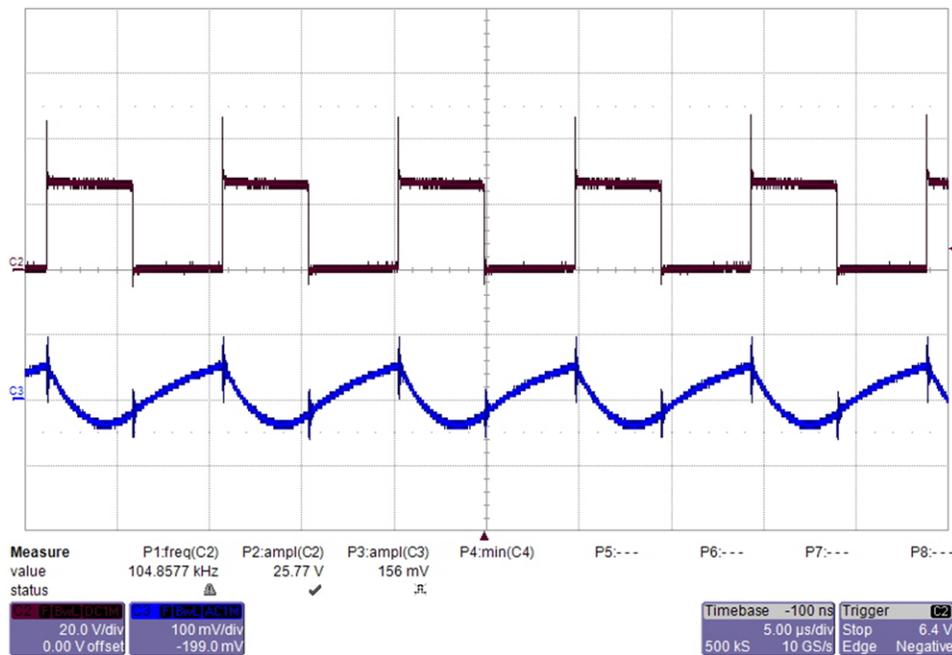


From top to bottom: CH2: switch node 20 V/div, CH3: output voltage ripple 100 mV/div, 5 μs/div

**Figure 69. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 18\text{ V}$  and no Load (Bias Supply With TPS40210-Q1)**

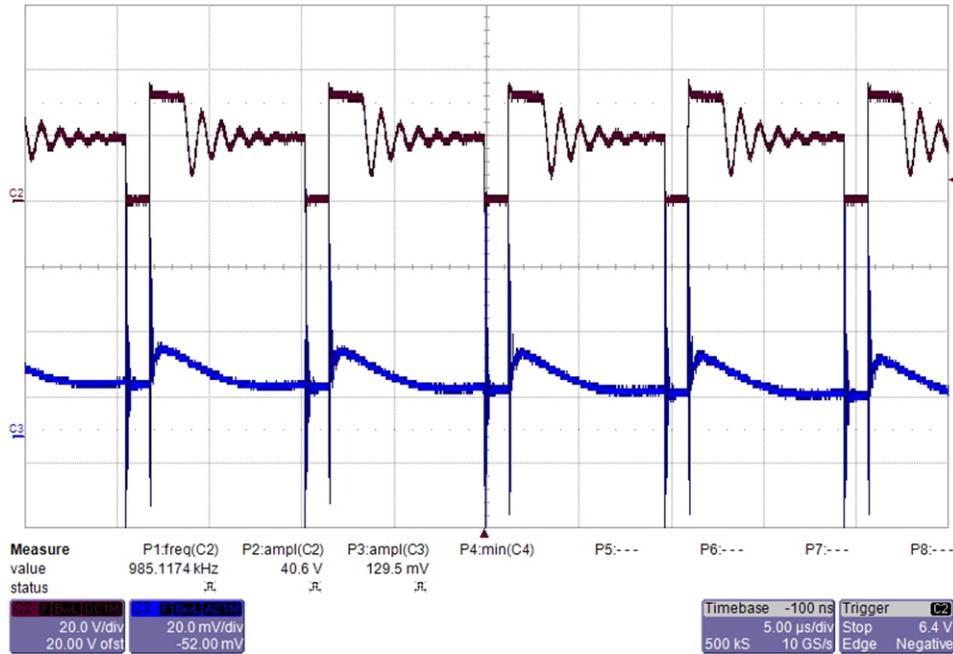


From top to bottom: CH2: switch node 20 V/div, CH3: output voltage ripple 20 mV/div, 5  $\mu$ s/div

**Figure 70. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 18\text{ V}$  and 180-mA Load (Bias Supply With TPS40210-Q1)**

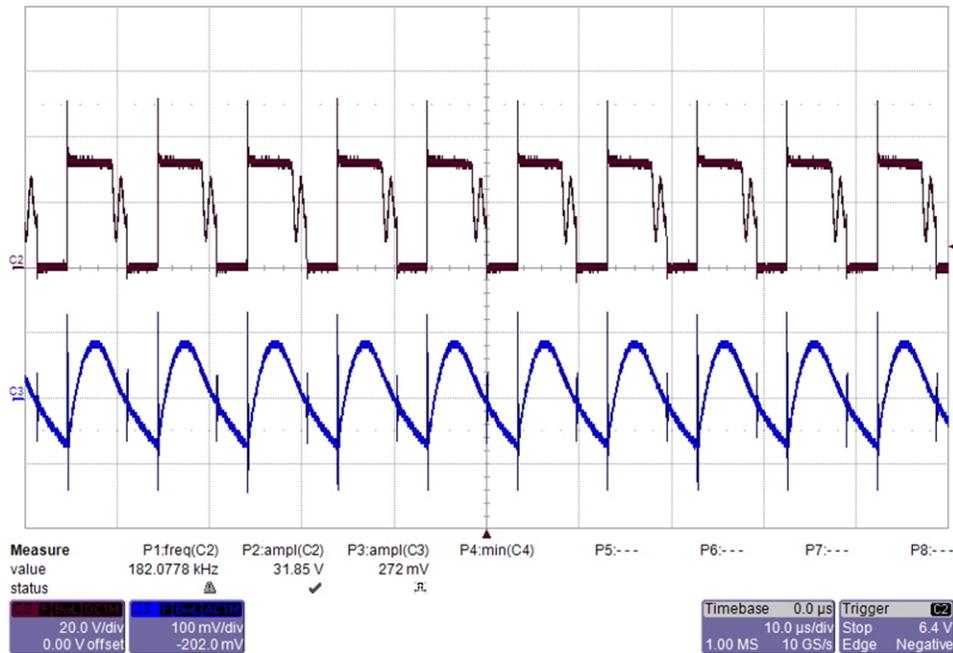


From top to bottom: CH2: switch node 20 V/div, CH3: output voltage ripple 100 mV/div, 10  $\mu$ s/div

**Figure 71. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 18\text{ V}$  and no Load (Bias Supply With TPS40210-Q1)**

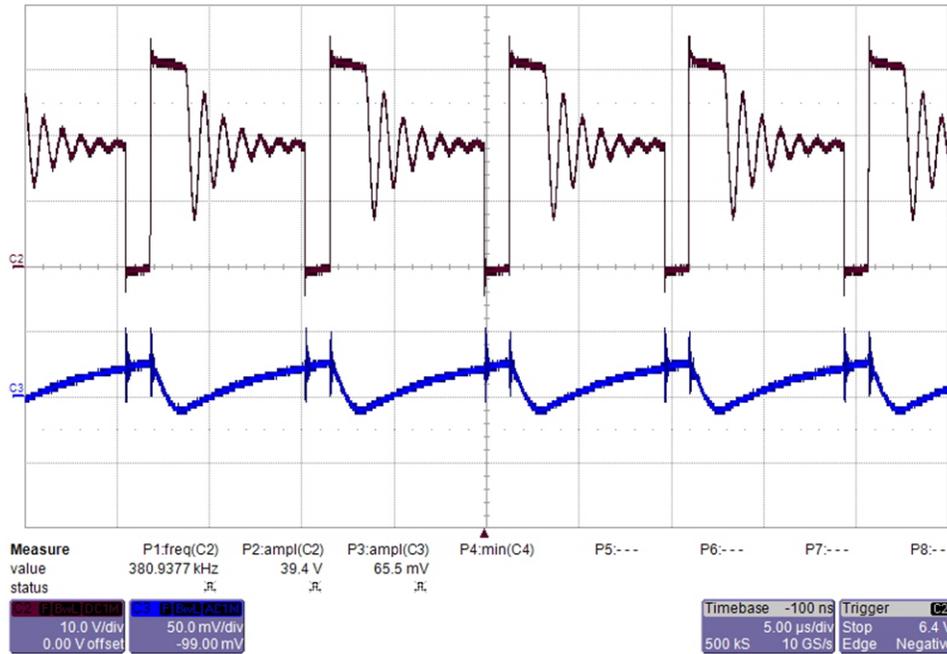

From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 50 mV/div, 5  $\mu$ s/div

**Figure 72. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 18\text{ V}$  and 180-mA Load (Bias Supply With TPS40210-Q1)**

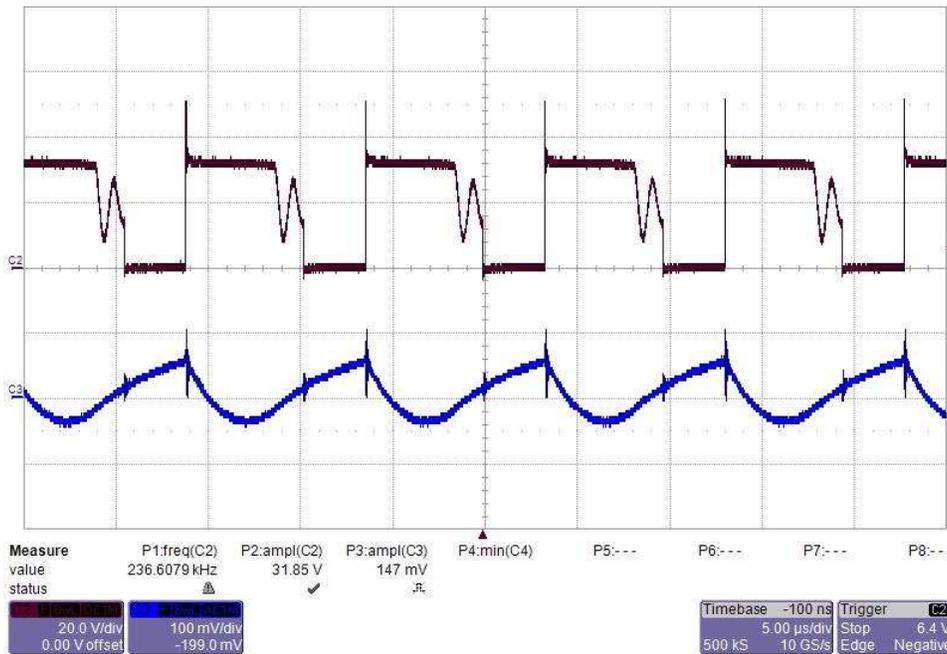


From top to bottom: CH2: switch node 20 V/div, CH3: output voltage ripple 100 mV/div, 5  $\mu$ s/div

### 3.2.2.4 Efficiency

Figure 73 shows the measured efficiency of the flyback converter designed with the TPS40210-Q1 device over the full load range. As can be seen, around 81.5% peak efficiency is achieved with the input voltages of 5 V, 12 V, and 18 V, respectively.


**Figure 73. Measured Efficiency Under Input Voltages of 5 V, 12 V, and 18 V (Bias Supply With TPS40210-Q1)**

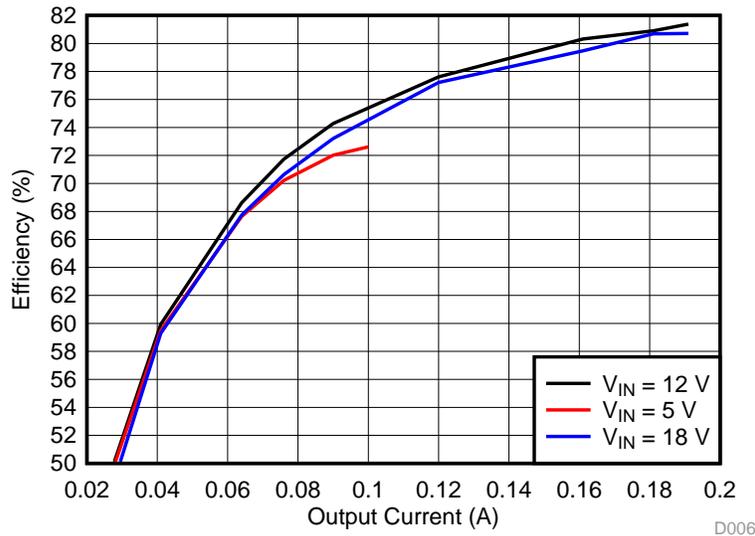

### 3.2.2.5 Load Regulation

Load regulation measurements show the % deviation from nominal output voltage as a function of output current. Figure 74 shows the measured result of the flyback converter designed with the TPS40210-Q1 device. The load regulation is measured with the input voltages of 5 V, 12 V, and 18 V, respectively.


**Figure 74. Load Regulation Under Input Voltages of 5 V, 12 V, and 18 V (Bias Supply With TPS40210-Q1)**

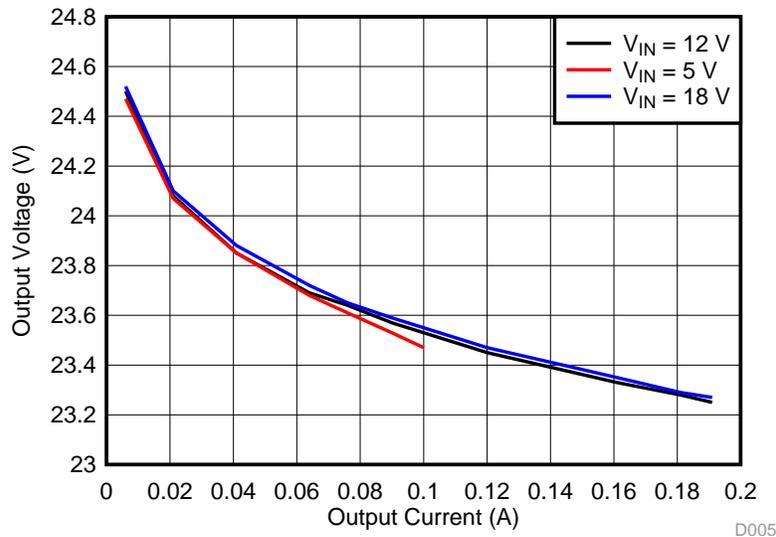

### 3.2.2.6 Load Transients


This section shows load transient measurements of the flyback converter designed with the TPS40210-Q1 device. Load transient response presents how well a power supply copes with the changes in the load-current demand. During the test, the load is switching from 0 to full, under input voltages of 5 V, 12 V, and 18 V, respectively.

**Figure 75. Load Transient Response of the 15-V Rail Under  $V_{IN} = 5\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 80 mA (Bias Supply With TPS40210-Q1)**

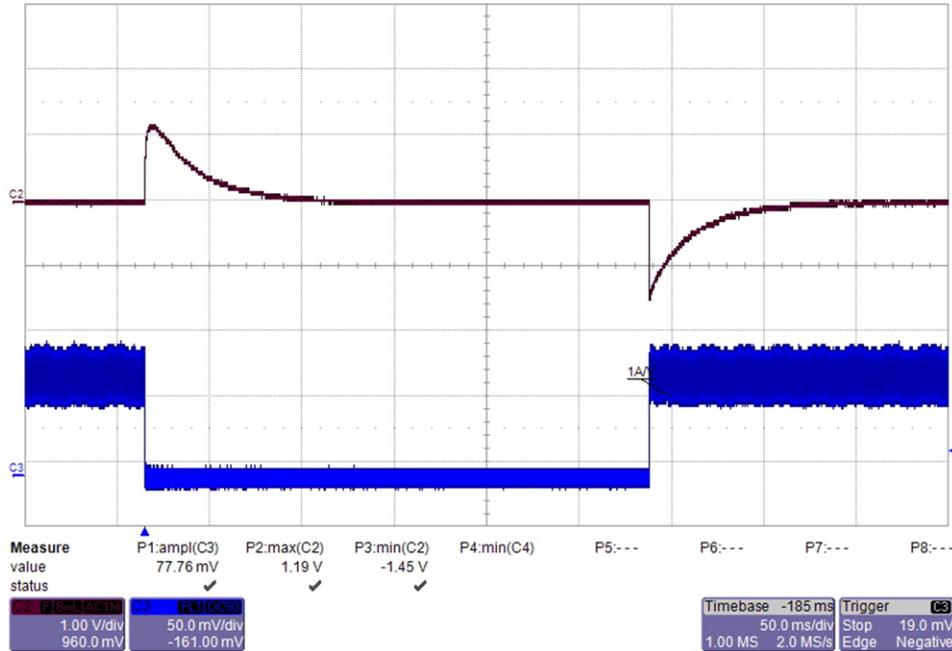


From top to bottom: CH2: output voltage 1 V/div, CH3: load current 500 mA/div, 50 ms/div

**Figure 76. Load Transient Response of the -9-V rail Under  $V_{IN} = 5\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 80 mA (Bias Supply With TPS40210-Q1)**

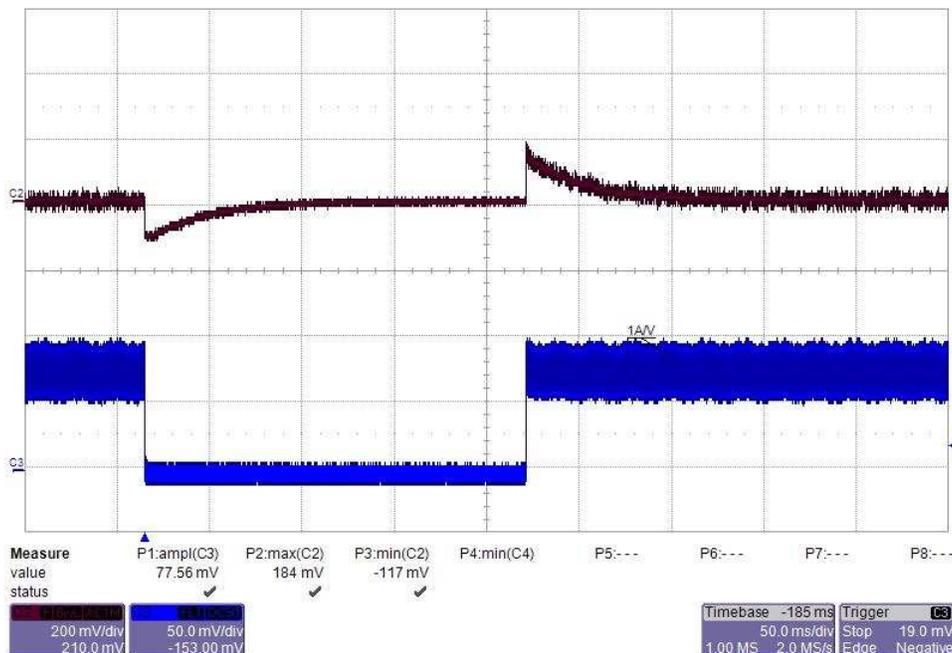


From top to bottom: CH2: output voltage 200 mV/div, CH3: load current 500 mA/div, 50 ms/div

**Figure 77. Load Transient Response of the 15-V Rail Under  $V_{IN} = 12\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With TPS40210-Q1)**

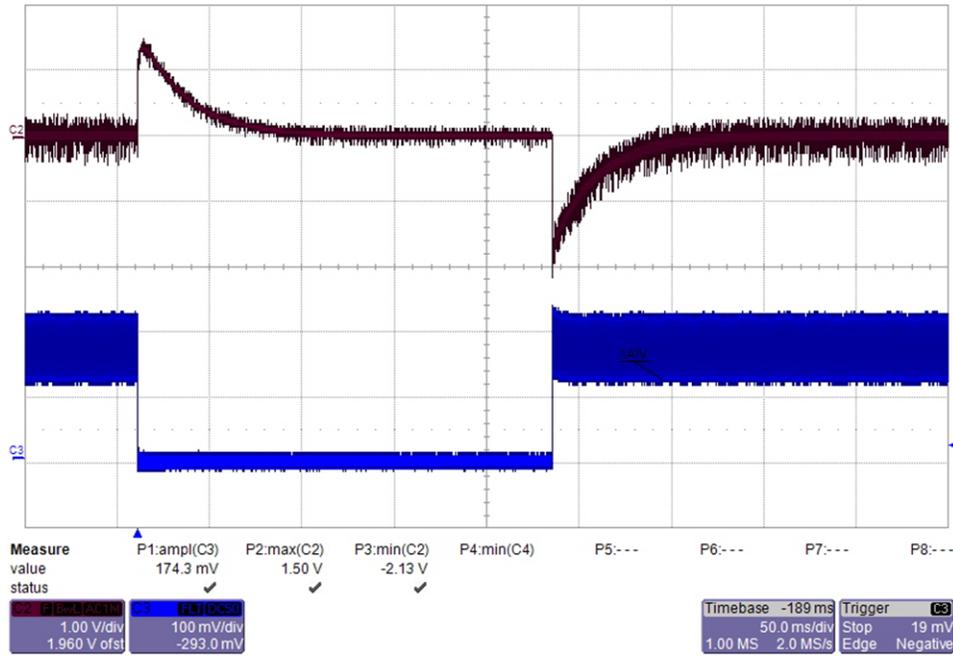


From top to bottom: CH2: output voltage 1 V/div, CH3: load current 1 A/div, 50 ms/div

**Figure 78. Load Transient Response of the -9-V Rail Under  $V_{IN} = 12\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With TPS40210-Q1)**

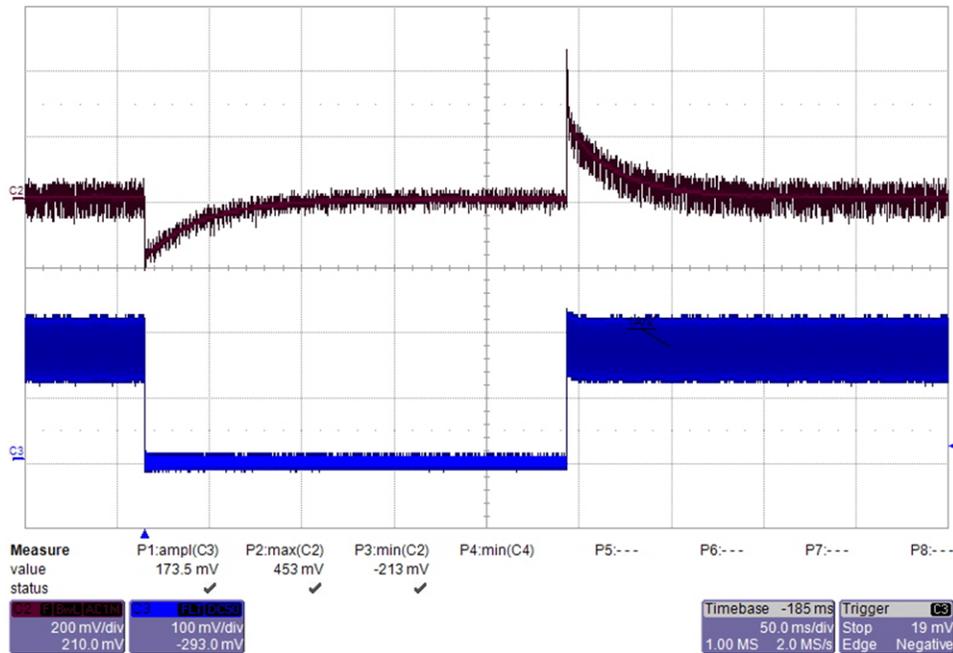


From top to bottom: CH2: output voltage 200 mV/div, CH3: load current 1 A/div, 50 ms/div

**Figure 79. Load Transient Response of the 15-V Rail Under  $V_{IN} = 18\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With TPS40210-Q1)**

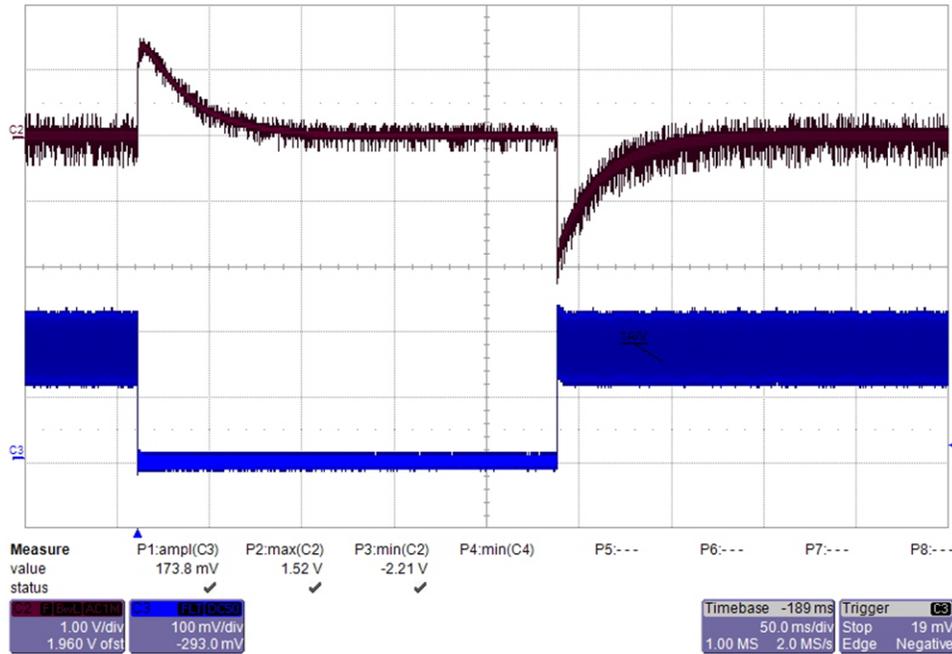

From top to bottom: CH2: output voltage 1 V/div, CH3: load current 1 A/div, 50 ms/div

**Figure 80. Load Transient Response of the -9-V Rail Under  $V_{IN} = 18\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With TPS40210-Q1)**

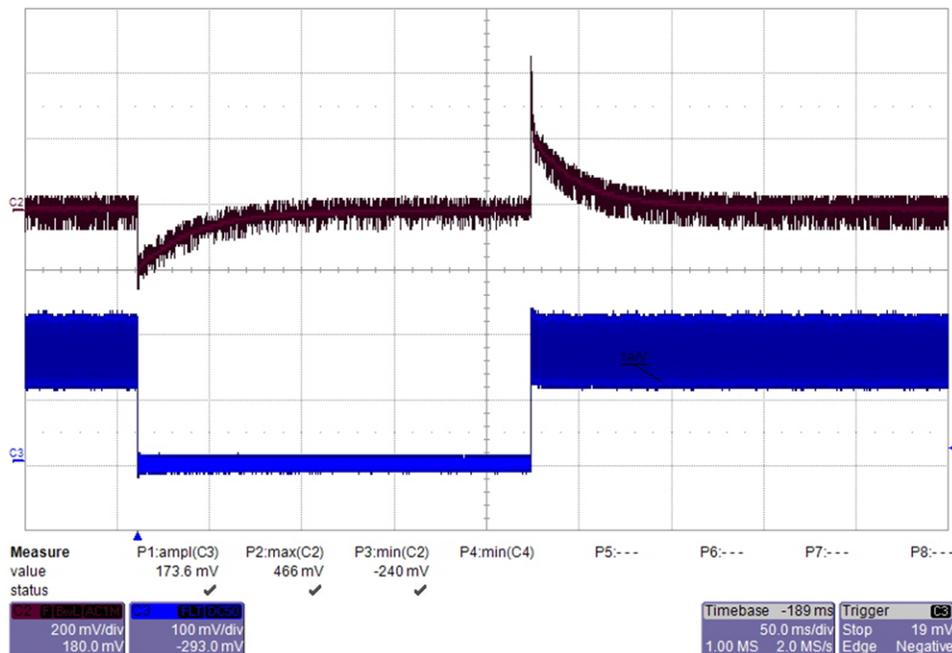


From top to bottom: CH2: output voltage 200 mV/div, CH3: load current 1 A/div, 50 ms/div

### 3.2.2.7 Voltage Ripple While Switching IGBT


The flyback converter designed with the TPS40210-Q1 device is connected to the isolated gate drivers (ISO5852S-Q1) and the 1200-V IGBT module (FF150R12MS4G) for checking the voltage ripple during the switching transients. The IGBTs are switched at 20- and 50-kHz frequencies, respectively.

**Figure 81. Voltage Ripple of the 15-V Rail While Switching the IGBT Module at 20 kHz (Bias Supply With TPS40210-Q1)**

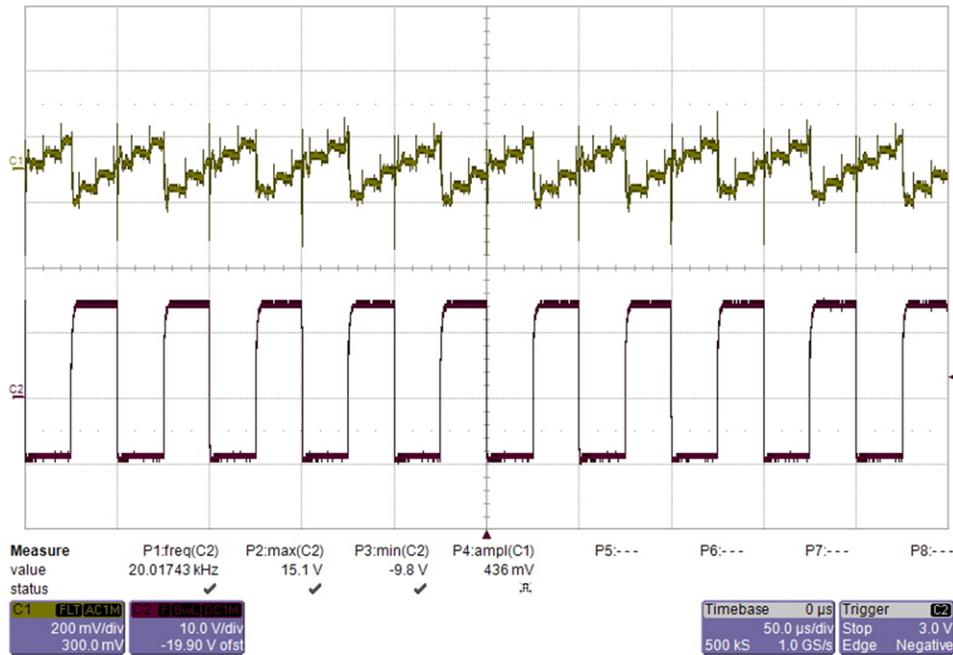


From top to bottom: CH1: output voltage 200 mV/div, CH2: gate PWM signal 10 V/div, 50 μs/div

**Figure 82. Voltage Ripple of the -9-V Rail While Switching the IGBT Module at 20 kHz (Bias Supply With TPS40210-Q1)**

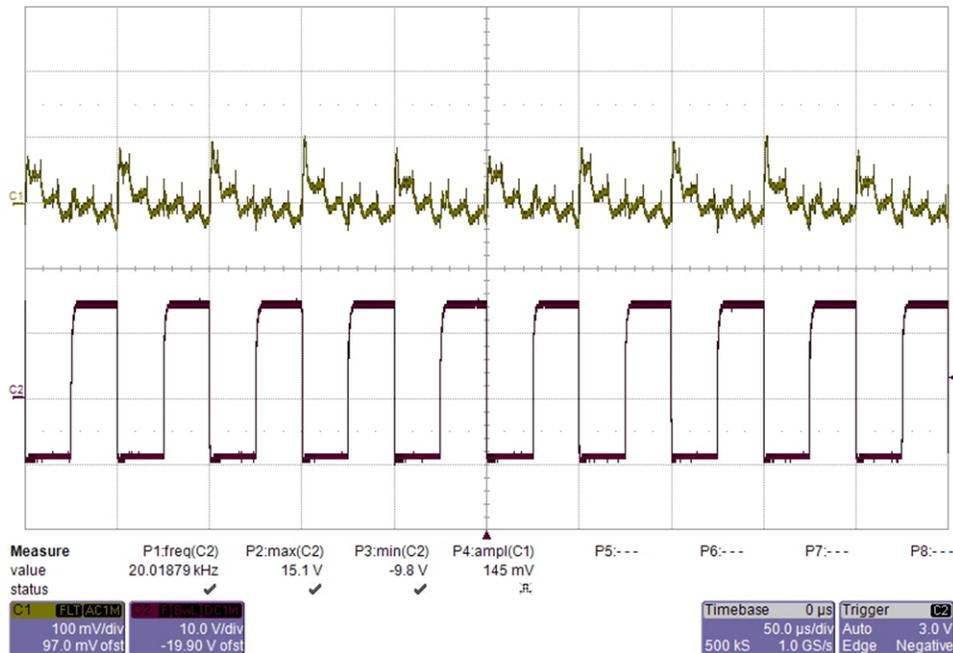


From top to bottom: CH1: output voltage 100 mV/div, CH2: gate PWM signal 10 V/div, 50 μs/div

**Figure 83. Voltage Ripple of the 15-V Rail While Switching the IGBT Module at 50 kHz (Bias Supply With TPS40210-Q1)**

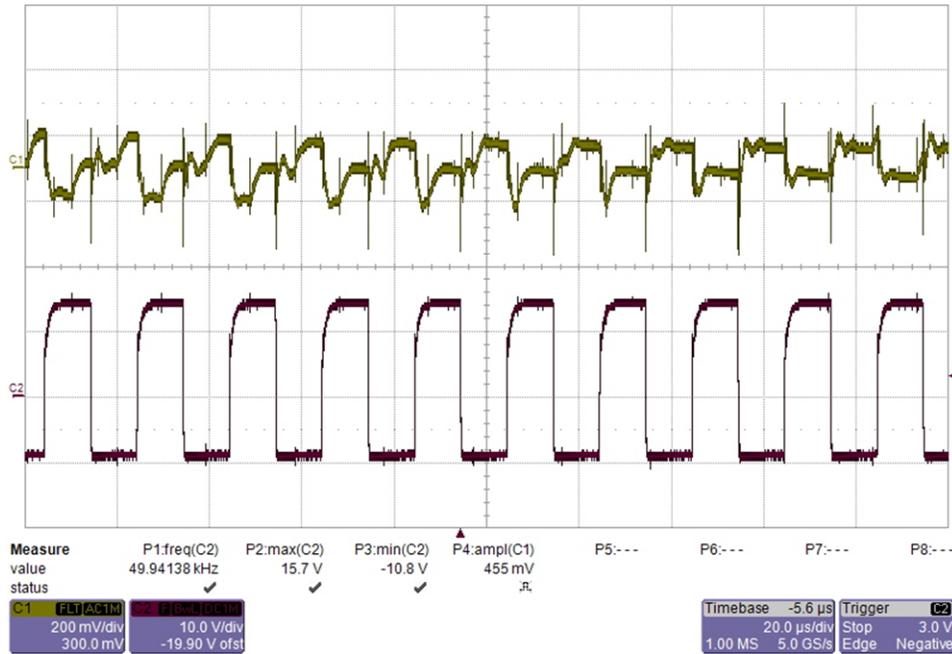

From top to bottom: CH1: output voltage 200 mV/div, CH2: gate PWM signal 10 V/div, 20  $\mu$ s/div

**Figure 84. Voltage Ripple of the -9-V Rail While Switching the IGBT Module at 50 kHz (Bias Supply With TPS40210-Q1)**

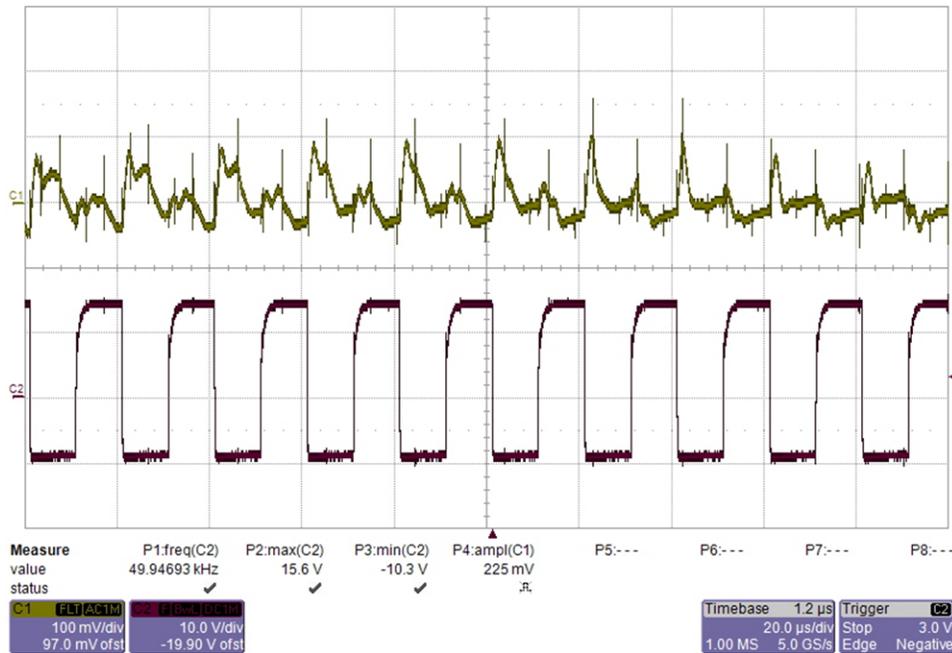


From top to bottom: CH1: output voltage 100 mV/div, CH2: gate PWM signal 10 V/div, 20  $\mu$ s/div

### 3.2.2.8 Control-Loop Frequency Response

The control loop frequency response represents the stability of the power-supply system. The TPS40210-Q1-based flyback converter loop frequency response is measured under various loads and input voltages, respectively. The measurement setup is shown in Figure 85. The output of the network analyzer is connected to the injection resistor. The outputs are also connected to the input channel A and channel B, respectively.


Figure 85. Control-Loop Frequency Response Measurement Setup

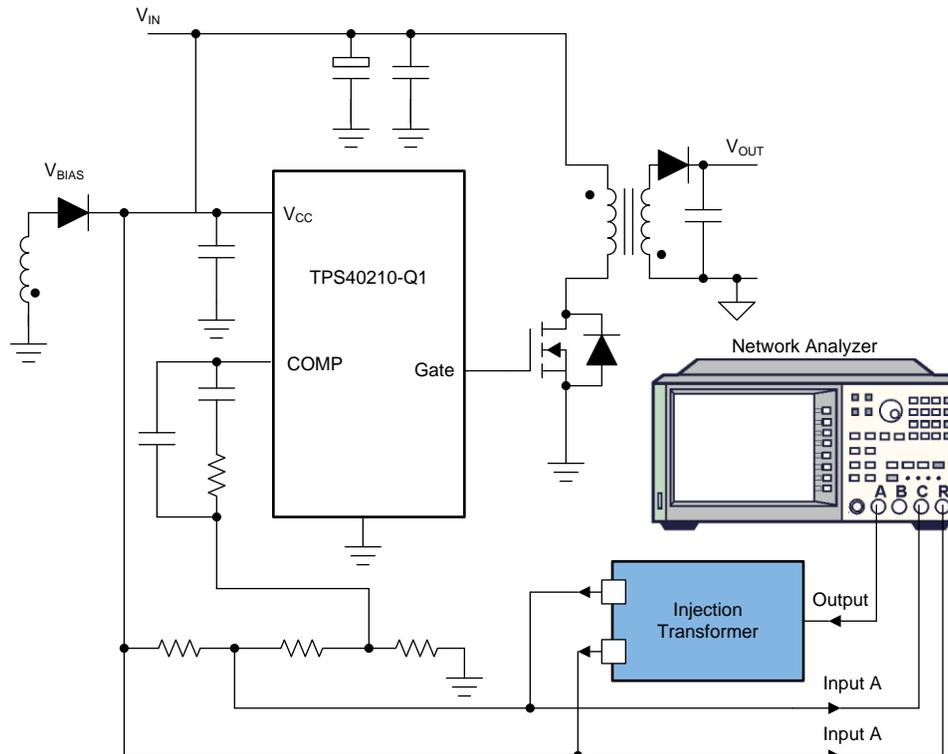

For TPS40210-Q1 based flyback converter only


The loop frequency response of the buck converter is tested under various conditions. The measured results are shown from Figure 86 to Figure 91.

Figure 86. Loop Frequency Response With  $V_{IN} = 5\text{ V}$  and  $I_{OUT} = 10\text{ mA}$  (Bias Supply With TPS40210-Q1)

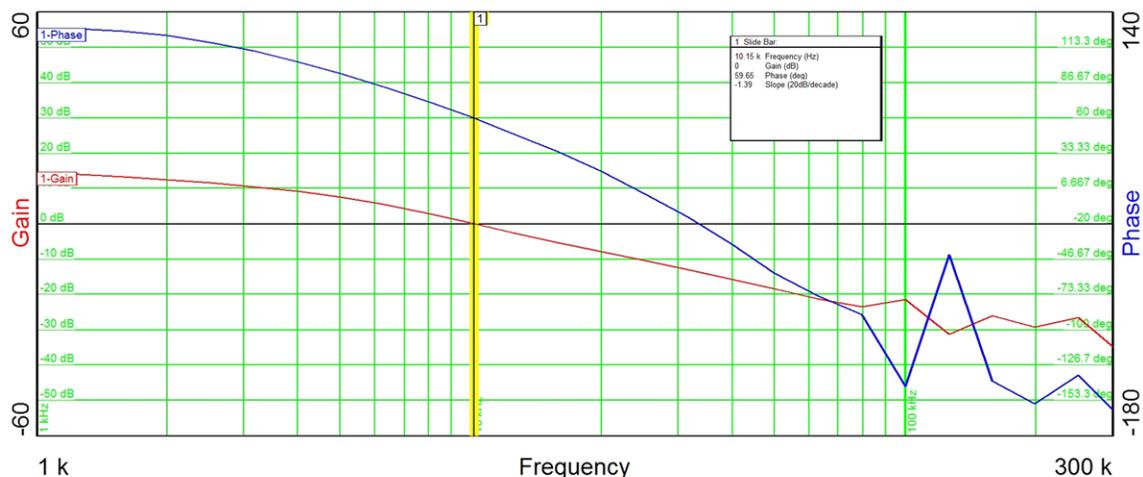


Crossover frequency: 10.15 kHz, achieved phase margin: 59 deg, achieved gain margin: 15 dB

Figure 87. Loop Frequency Response With  $V_{IN} = 5\text{ V}$  and  $I_{OUT} = 80\text{ mA}$  (Bias Supply With TPS40210-Q1)

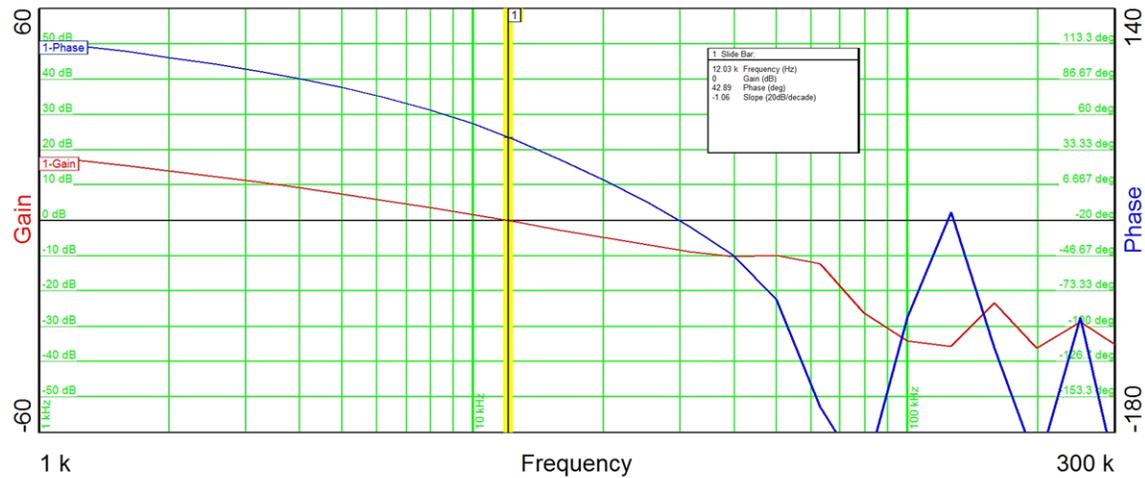


Crossover frequency: 12.03 kHz, achieved phase margin: 42.9 deg, achieved gain margin: 10 dB

Figure 88. Loop Frequency Response With  $V_{IN} = 12\text{ V}$  and  $I_{OUT} = 10\text{ mA}$  (Bias Supply With TPS40210-Q1)

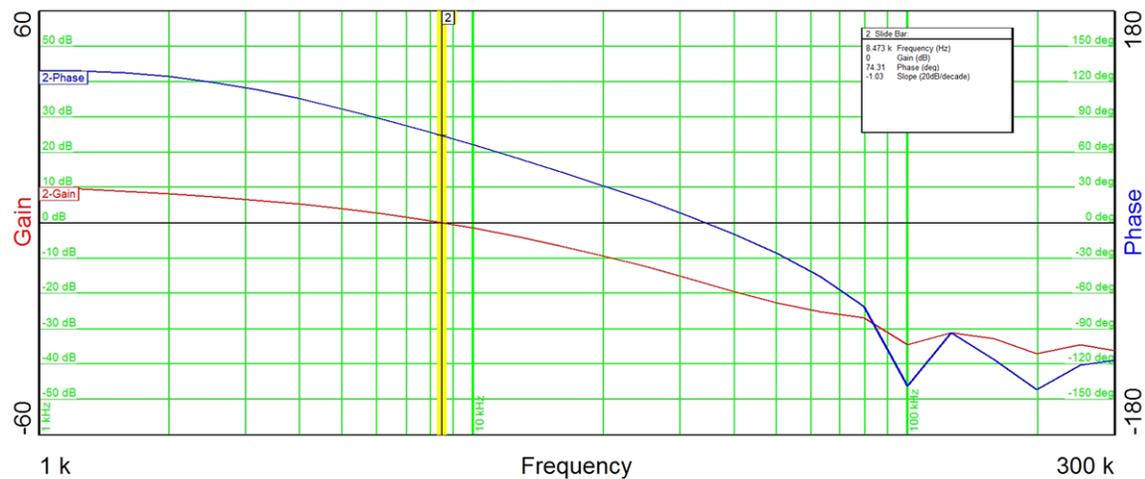


Crossover Frequency: 8.5 kHz, achieved phase margin: 74.3 deg, achieved gain margin: 18 dB

Figure 89. Loop Frequency Response With  $V_{IN} = 12\text{ V}$  and  $I_{OUT} = 180\text{ mA}$  (Bias Supply With TPS40210-Q1)

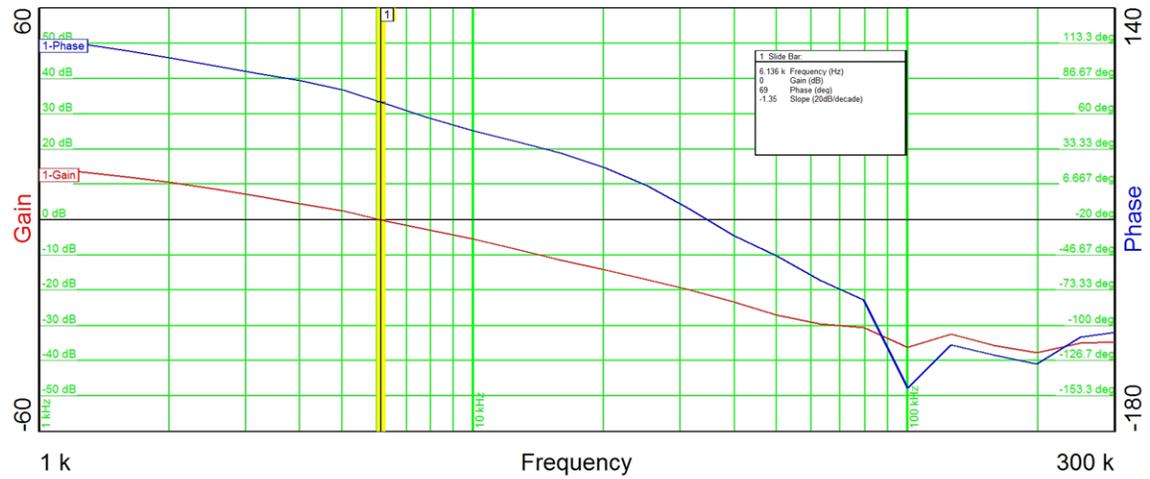


Crossover frequency: 6.1 kHz, achieved phase margin: 69 deg, achieved gain margin: 23 dB

Figure 90. Loop Frequency Response With  $V_{IN} = 18\text{ V}$  and  $I_{OUT} = 10\text{ mA}$  (Bias Supply With TPS40210-Q1)

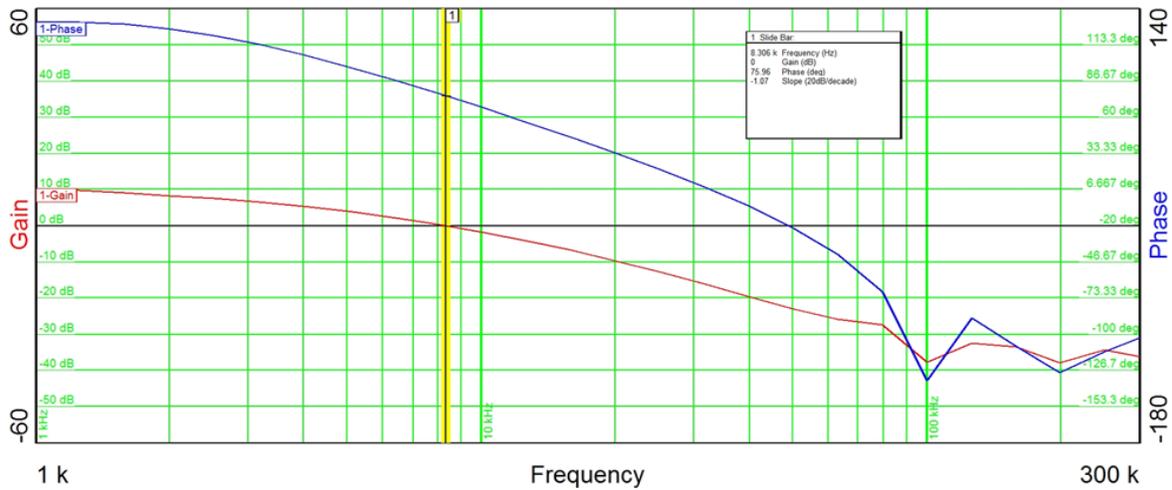

Crossover frequency: 8.3 kHz, achieved phase margin: 76 deg, achieved gain margin: 23 dB

Figure 91. Loop Frequency Response With  $V_{IN} = 18\text{ V}$  and  $I_{OUT} = 180\text{ mA}$  (Bias Supply With TPS40210-Q1)

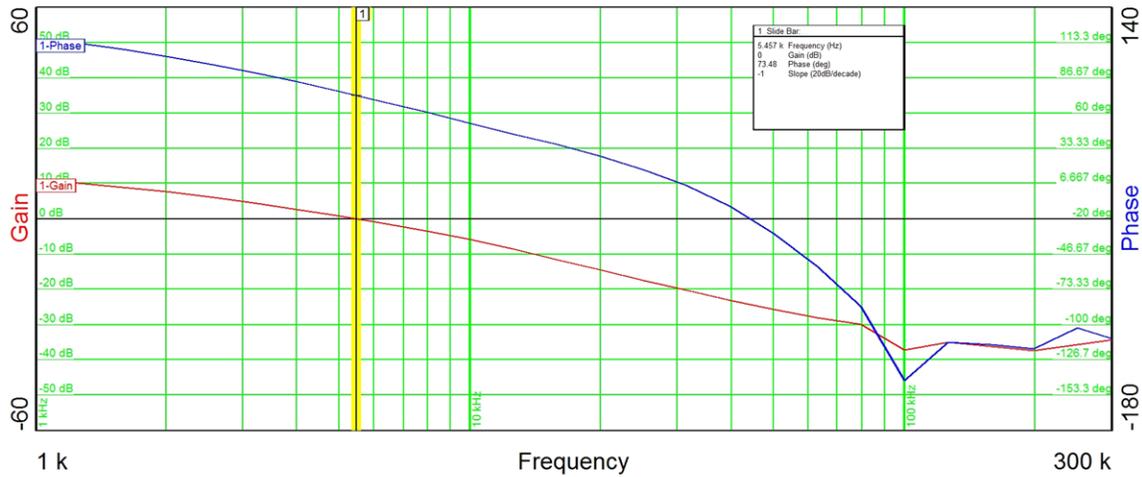


Crossover frequency: 5.5 kHz, achieved phase margin: 73.4 deg, achieved gain margin: 25 dB

### 3.2.2.9 Thermal Image

The thermal of the flyback converter designed with the TPS40210-Q1 device is measured under the full-load conditions. The circuit runs at the room temperature for 30 minutes. A 12-V nominal voltage is applied. The converter is loaded with 180 mA. Figure 92 shows the thermal image of the board.

Figure 92. Thermal Image With  $V_{IN} = 12\text{ V}$  and  $I_{OUT} = 180\text{ mA}$  (Bias Supply With TPS40210-Q1)

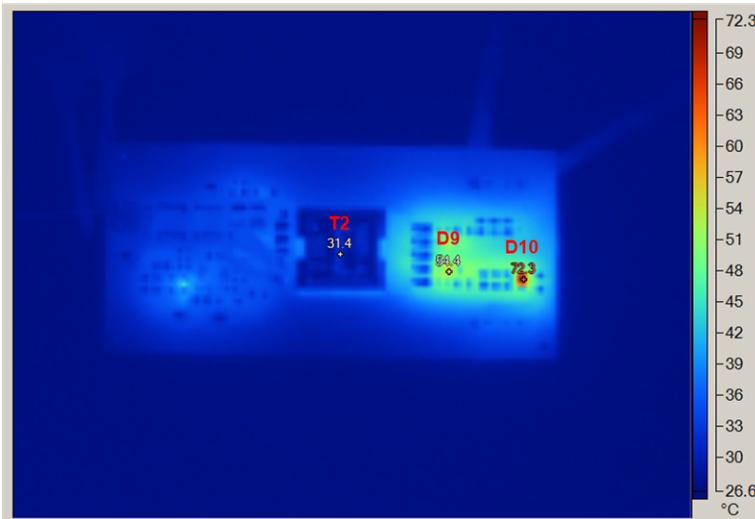

T2: Flyback transformer, D9: secondary rectification diode, D10: output Zener diode


### 3.2.3 Low Voltage Tests on Buck With Push-Pull Transformer Driver Supply

This section presents the experimental results of the bias supply solution 3 which is the buck converter plus the push-pull transformer driver supply based on the LM46002-Q1 and SN6505-Q1 devices.

#### 3.2.3.1 Startup


The start-up waveforms of the buck with push-pull transformer driver supply are measured under 5- and 12-V inputs, respectively. The +15-V and -9-V rails are measured separately.

**Figure 93. Start-up Waveform of the 15-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With Buck and Push Pull)**

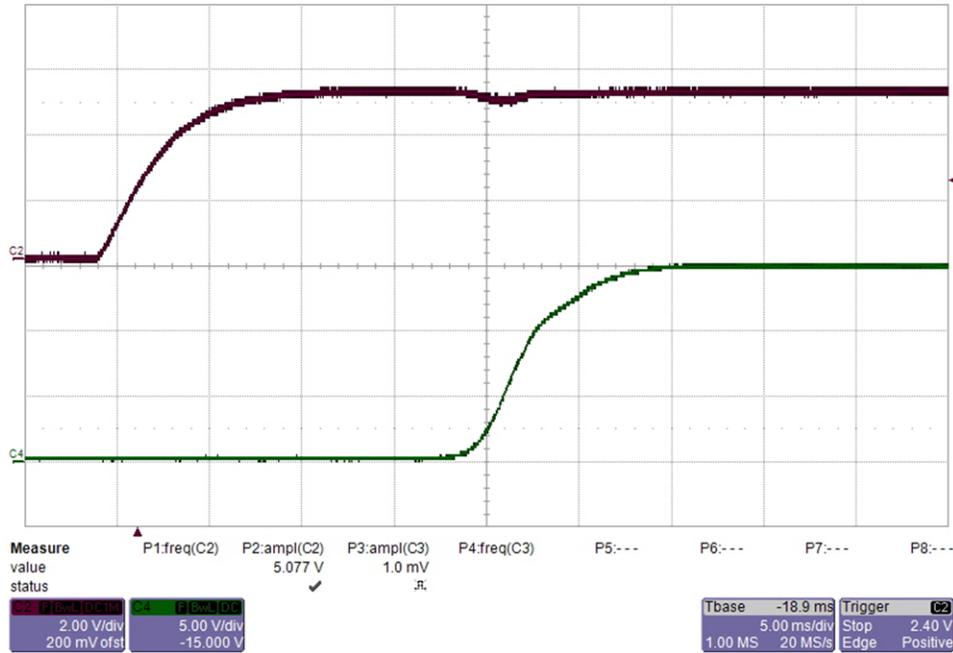


From top to bottom: CH2: input voltage 2 V/div, CH4: output voltage 5 V/div, 5 ms/div

Figure 94. Start-up Waveform of the -9-V Rail With  $V_{IN} = 5V$  and no Load (Bias Supply With Buck and Push Pull)

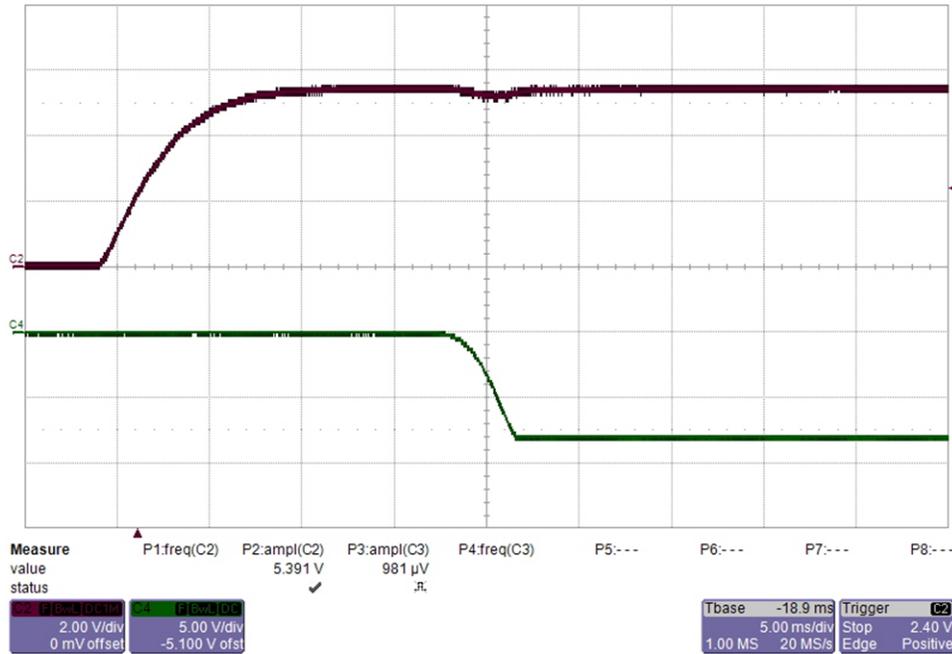


From top to bottom: CH2: input voltage 2 V/div, CH4: output voltage 5 V/div, 5 ms/div

Figure 95. Start-up Waveform of the 15-V Rail With  $V_{IN} = 12V$  and 180-mA Load (Bias Supply With Buck and Push Pull)

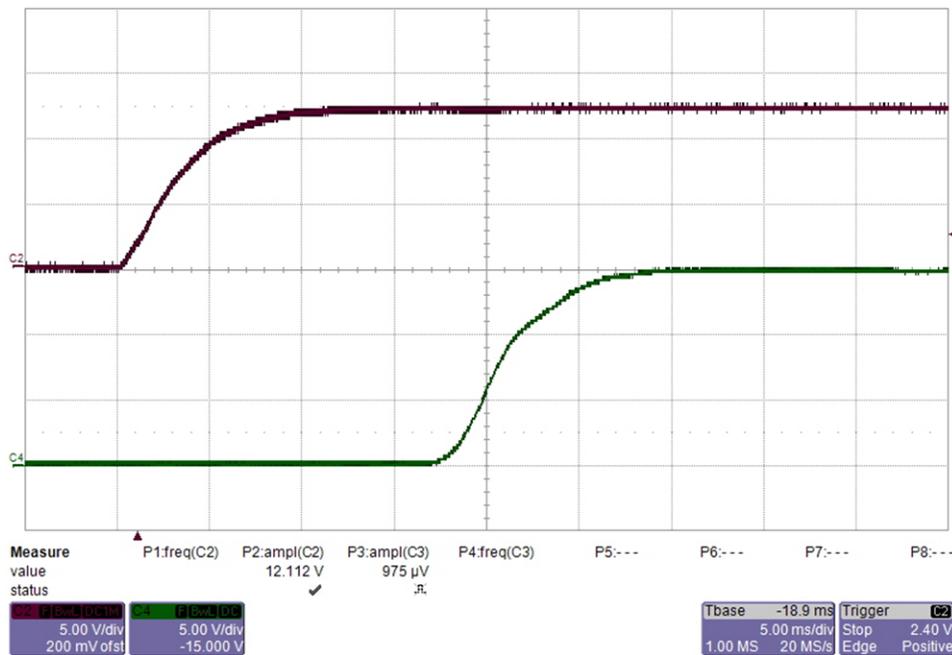

From top to bottom: CH2: input voltage 5 V/div, CH4: output voltage 5 V/div, 5 ms/div

Figure 96. Start-up Waveform of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With Buck and Push Pull)

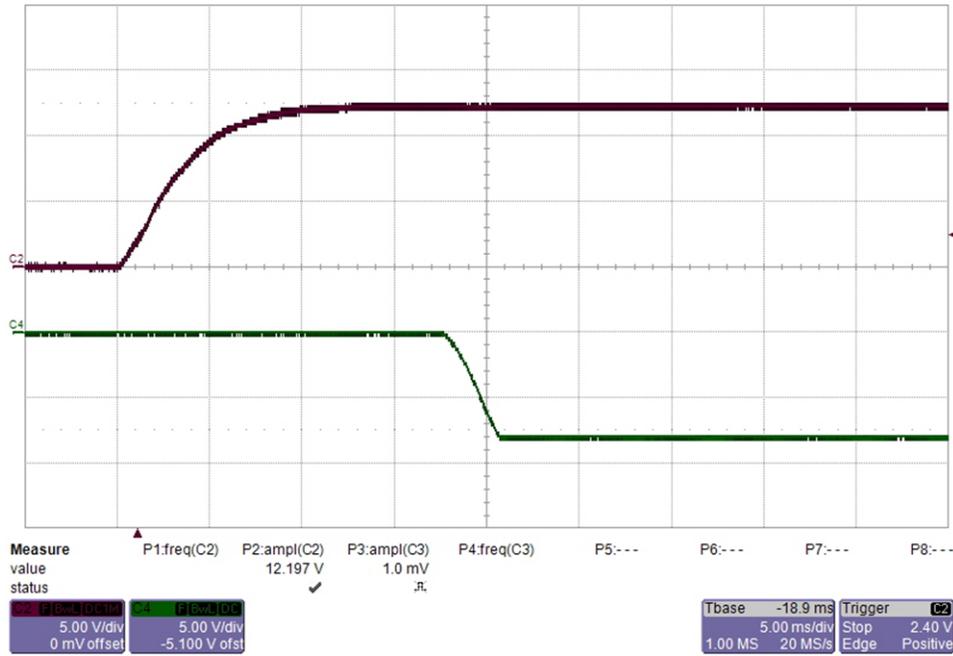


From top to bottom: CH2: input voltage 5 V/div, CH4: output voltage 5 V/div, 5 ms/div

### 3.2.3.2 Power Down


The power down waveforms of the buck with push-pull transformer driver supply are measured under 12-V input. The +15-V and -9-V rails are measured separately.

**Figure 97. Power-Down Waveform of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With Buck and Push Pull)**

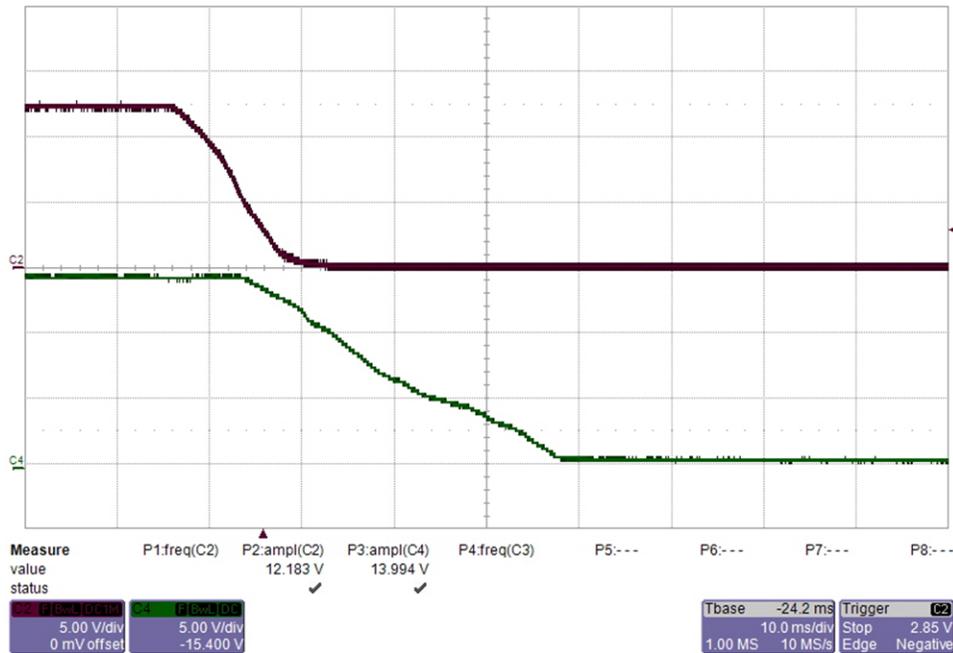

From top to bottom: CH2: input voltage 5 V/div, CH4: output voltage 5 V/div, 10 ms/div

**Figure 98. Power-Down Waveform of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With Buck and Push Pull)**

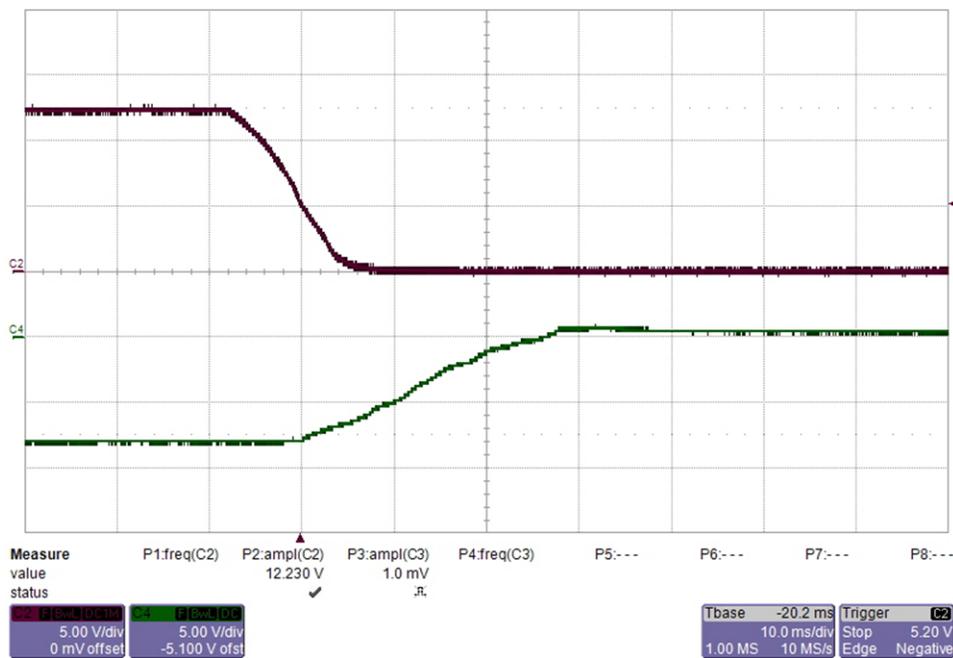


From top to bottom: CH2: input voltage 5 V/div, CH4: output voltage 5 V/div, 10 ms/div

### 3.2.3.3 Switch Node and Output Voltage Ripple


The switch node of the buck converter and output voltage ripple of the push-pull converter are measured under 5-, 12-, and 18-V inputs, respectively. The +15-V and -9-V rails are measured separately.

**Figure 99. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With Buck and Push Pull)**

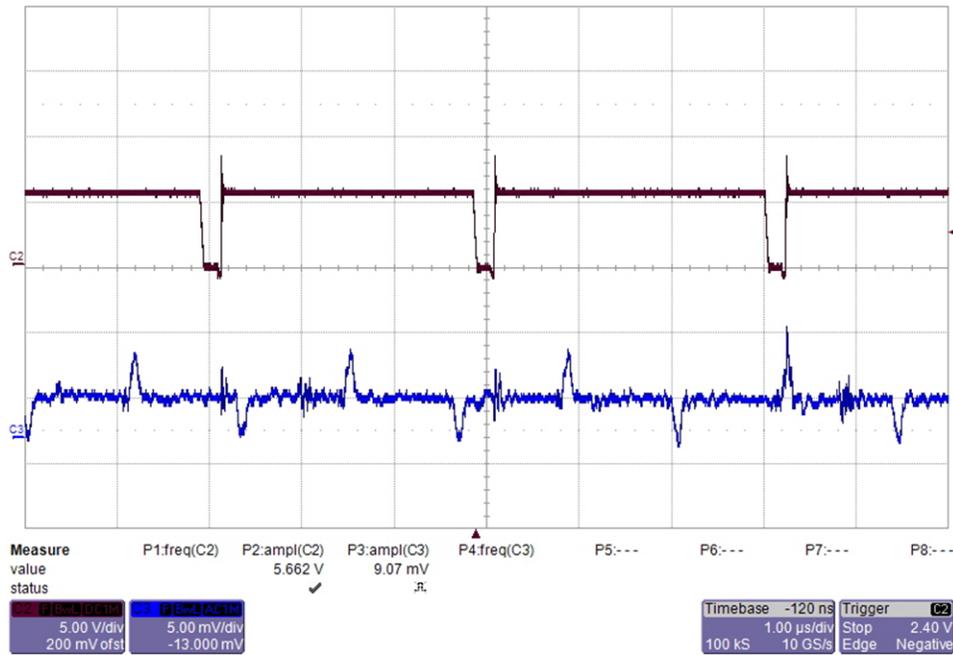


From top to bottom: CH2: switch node 5 V/div, CH3: output voltage ripple 5 mV/div, 1  $\mu\text{s}/\text{div}$

**Figure 100. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 5\text{ V}$  and 180-mA Load (Bias Supply With Buck and Push Pull)**

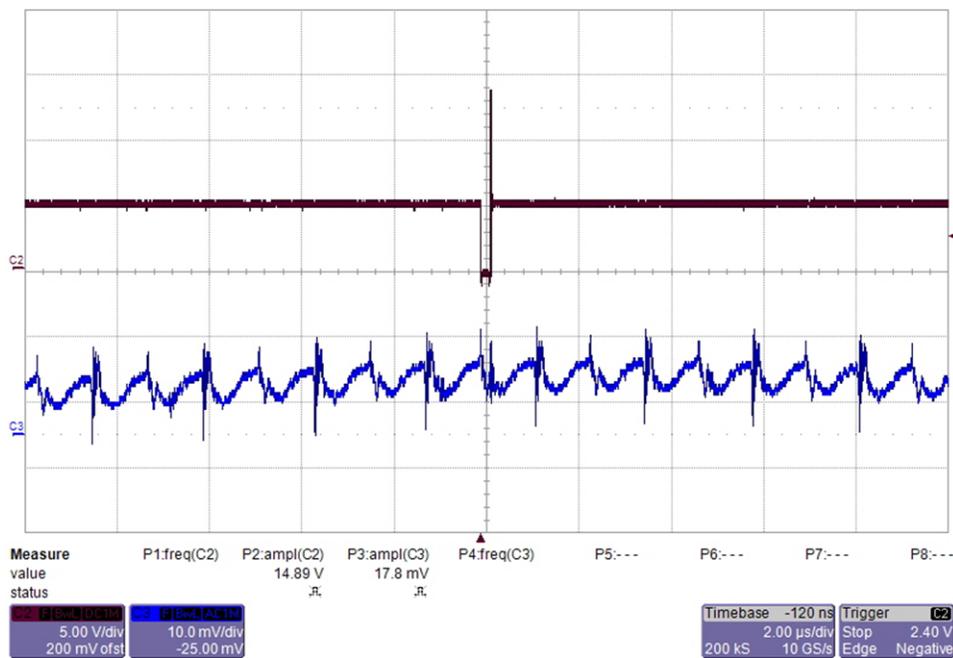


From top to bottom: CH2: switch node 5 V/div, CH3: output voltage ripple 10 mV/div, 2  $\mu\text{s}/\text{div}$

Figure 101. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 5\text{ V}$  and no Load (Bias Supply With Buck and Push Pull)

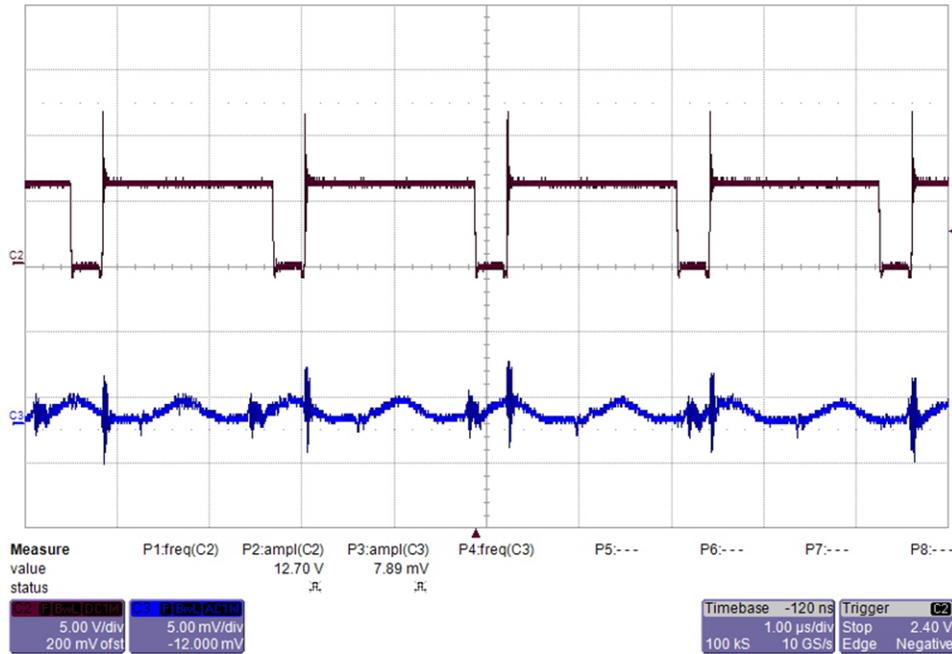


From top to bottom: CH2: switch node 5 V/div, CH3: output voltage ripple 5 mV/div, 1  $\mu$ s/div

Figure 102. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 5\text{ V}$  and 180-mA Load (Bias Supply With Buck and Push Pull)

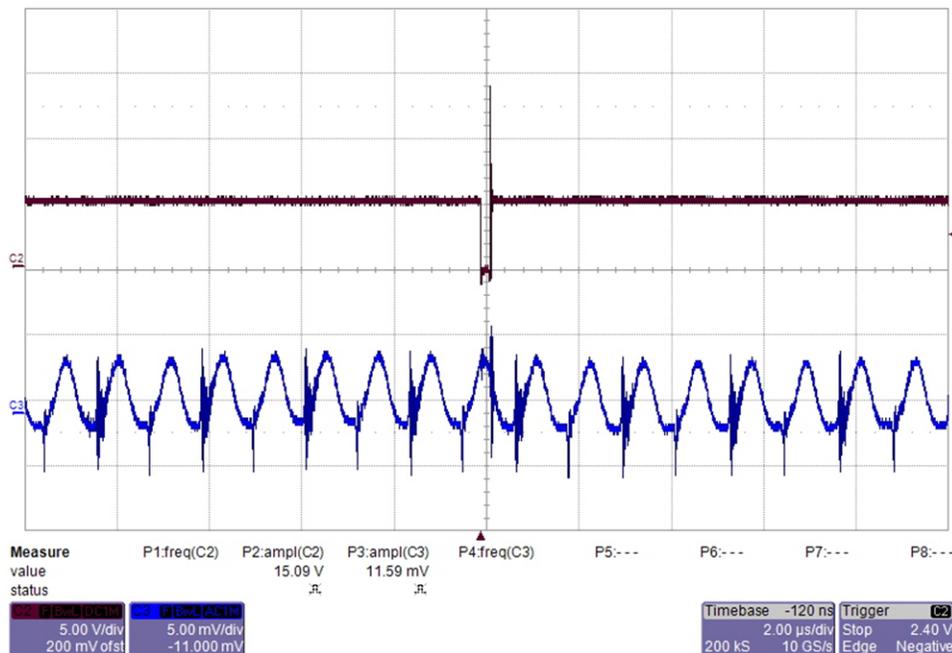


From top to bottom: CH2: switch node 5 V/div, CH3: output voltage ripple 5 mV/div, 2  $\mu$ s/div

**Figure 103. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With Buck and Push Pull)**

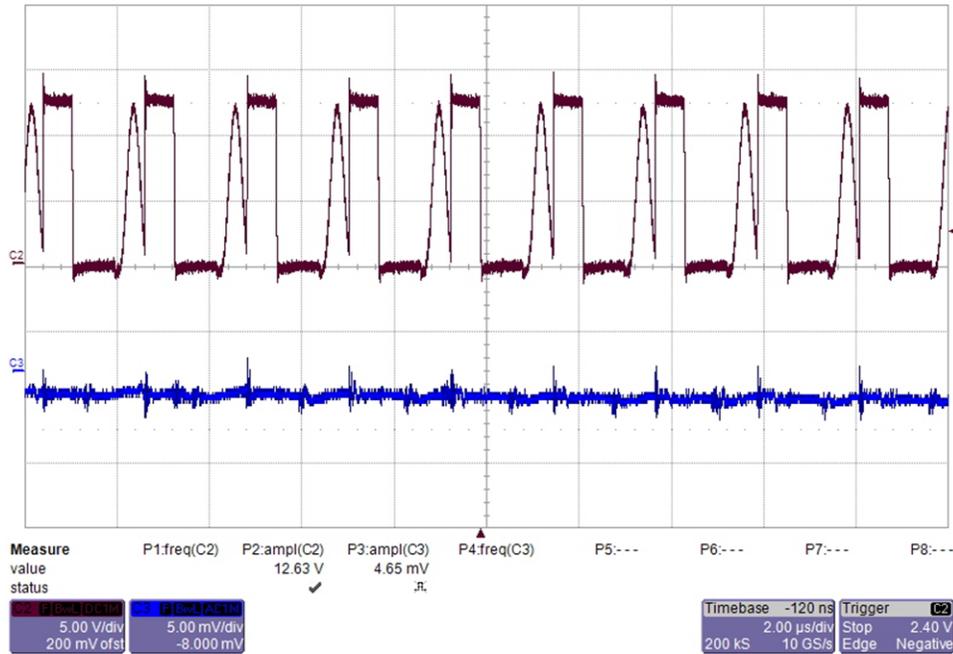


From top to bottom: CH2: switch node 5 V/div, CH3: output voltage ripple 5 mV/div, 2  $\mu$ s/div

**Figure 104. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With Buck and Push Pull)**

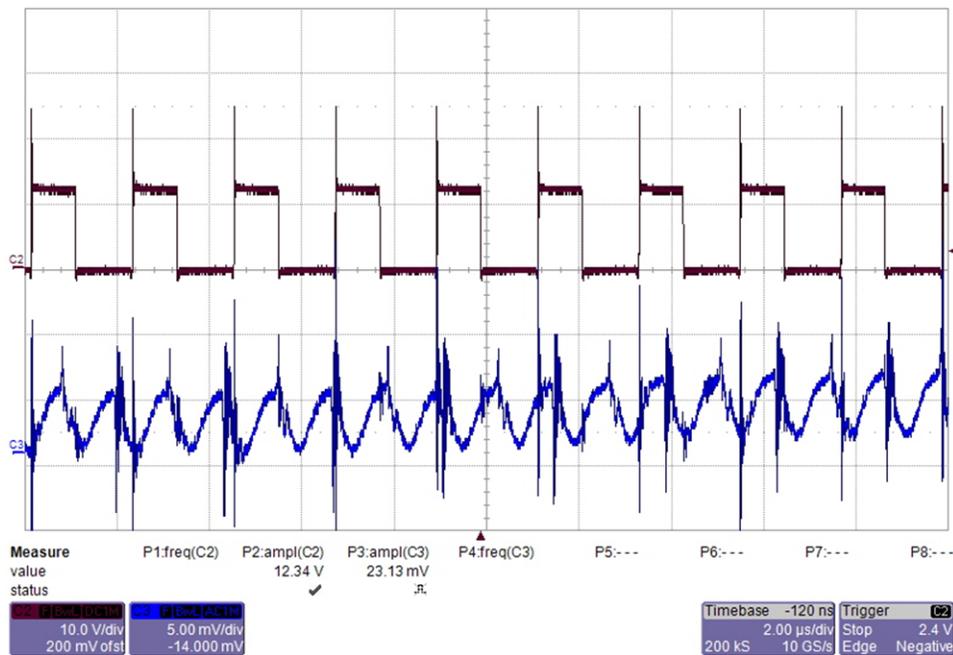


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 5 mV/div, 2  $\mu$ s/div

**Figure 105. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and no Load (Bias Supply With Buck and Push Pull)**

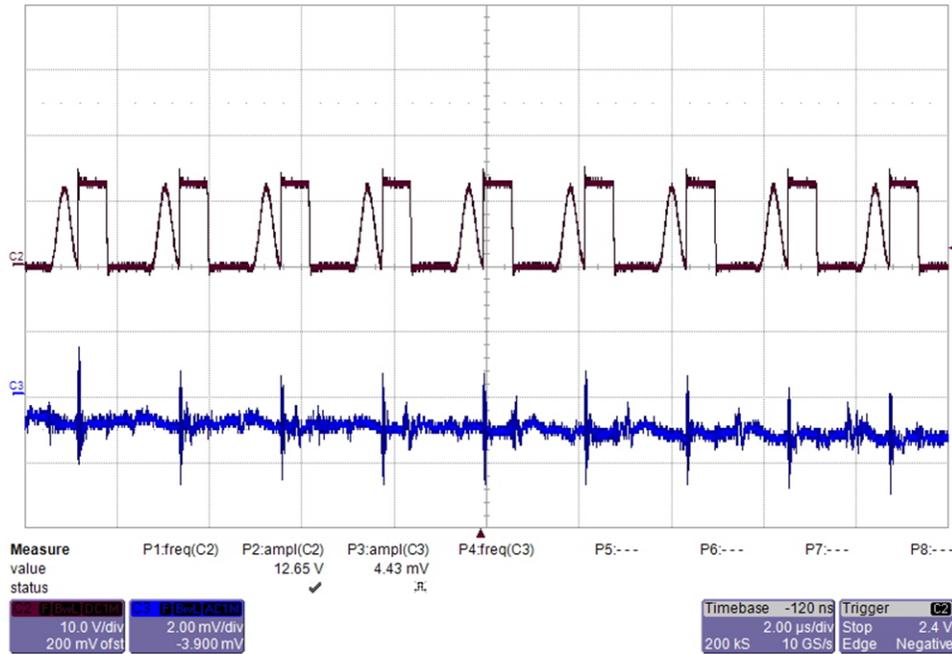


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 2 mV/div, 2 μs/div

**Figure 106. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 12\text{ V}$  and 180-mA Load (Bias Supply With Buck and Push Pull)**

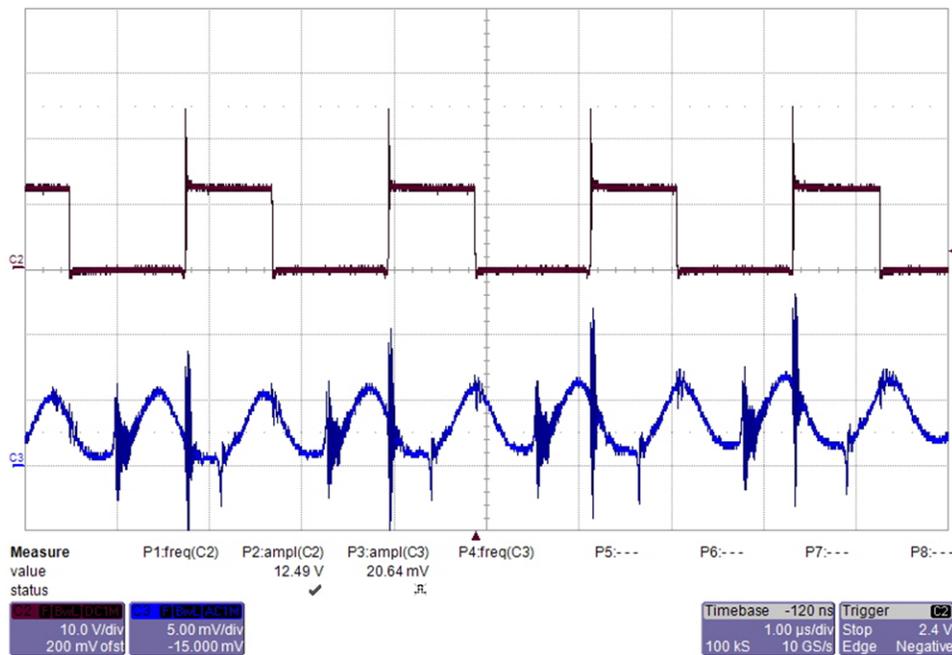


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 5 mV/div, 1 μs/div

**Figure 107. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 18\text{ V}$  and no Load (Bias Supply With Buck and Push Pull)**

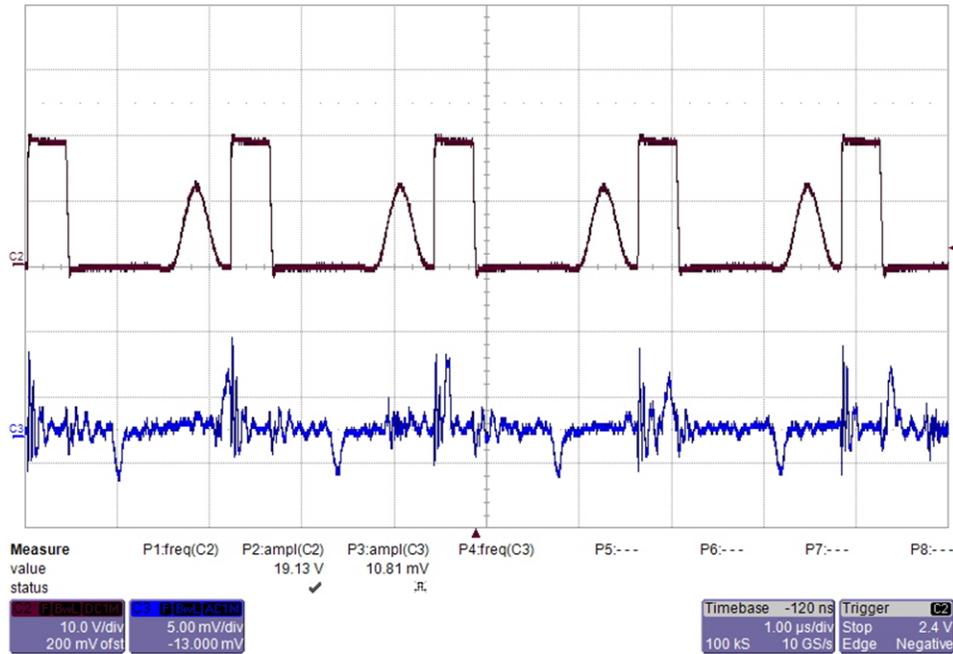


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 5 mV/div, 1  $\mu$ s/div

**Figure 108. Switch Node and Output Ripple of the 15-V Rail With  $V_{IN} = 18\text{ V}$  and 180-mA Load (Bias Supply With Buck and Push Pull)**

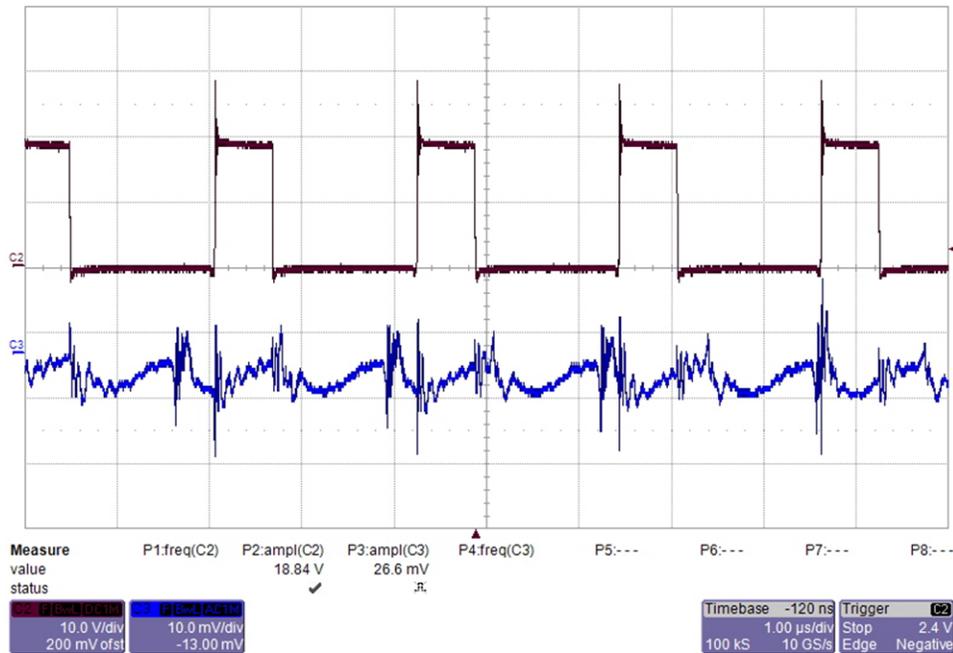


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 10 mV/div, 1  $\mu$ s/div

**Figure 109. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 18\text{ V}$  and no Load (Bias Supply With Buck and Push Pull)**

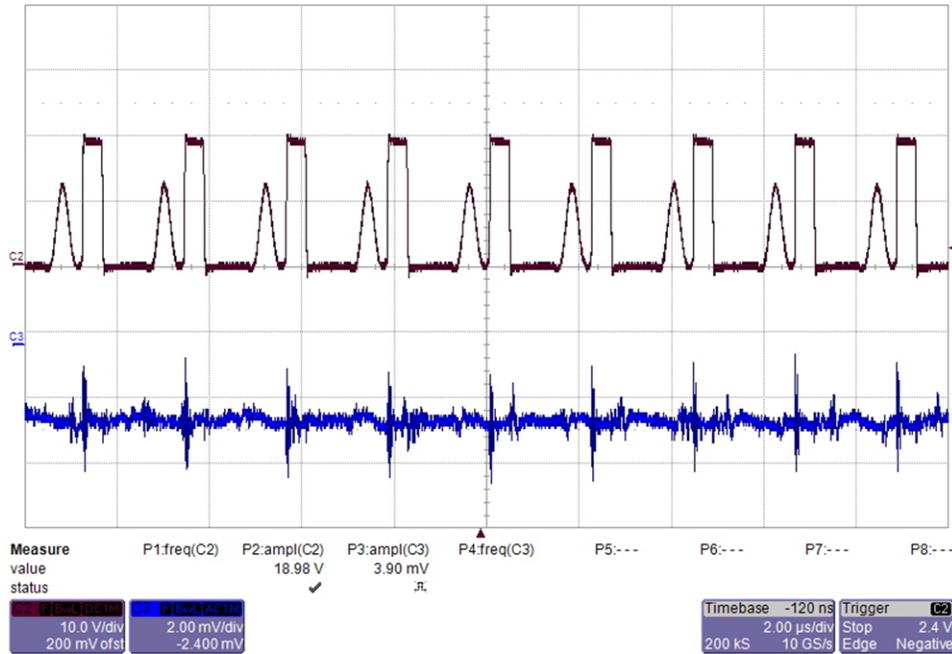

From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 2 mV/div, 2  $\mu\text{s}/\text{div}$

**Figure 110. Switch Node and Output Ripple of the -9-V Rail With  $V_{IN} = 18\text{ V}$  and 180-mA Load (Bias Supply With Buck and Push Pull)**

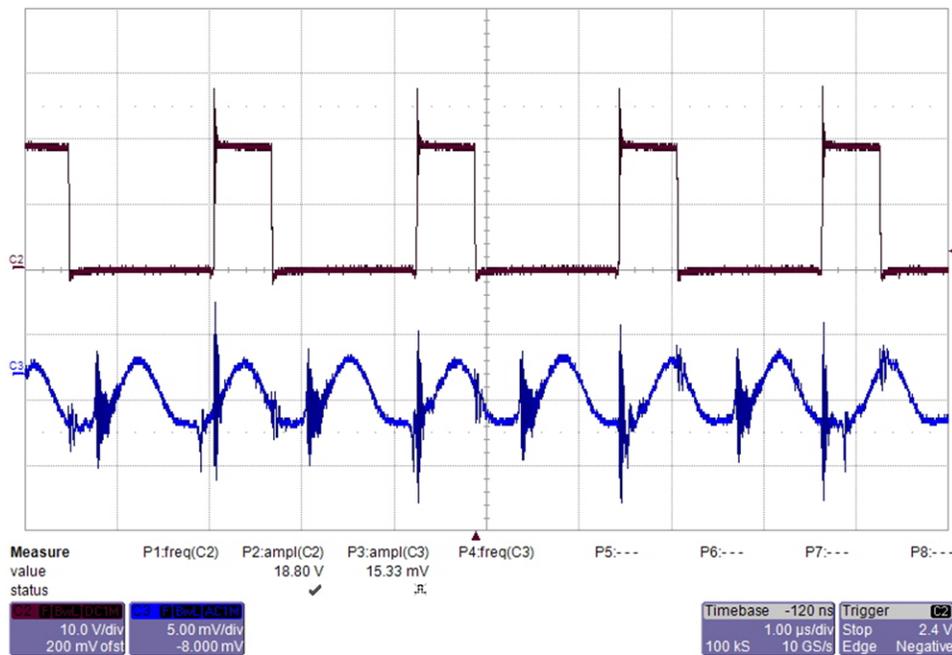


From top to bottom: CH2: switch node 10 V/div, CH3: output voltage ripple 5 mV/div, 1  $\mu\text{s}/\text{div}$

### 3.2.3.4 Efficiency

Figure 111 shows the measured efficiency of the buck with push-pull transformer driver supply over the full load range. As can be seen around 80% peak efficiency is achieved with the input voltages of 5 V, 12 V, and 18 V, respectively.


**Figure 111. Measured Efficiency Under Input Voltages of 5 V, 12 V, and 18 V (Bias Supply With Buck and Push Pull)**

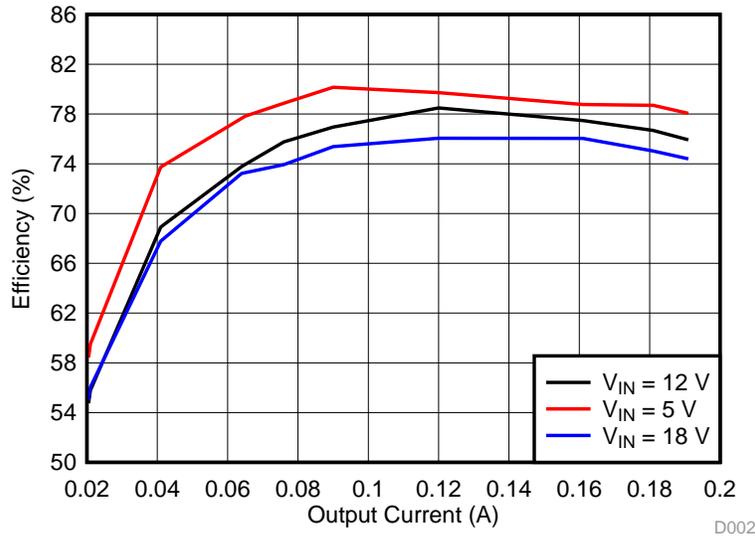

### 3.2.3.5 Load Regulation

Load regulation measurements show the % deviation from nominal output voltage as a function of output current. Figure 112 shows the measured result of the buck with push-pull transformer driver supply. The load regulation is measured with the input voltages of 5 V, 12 V, and 18 V, respectively.


Figure 112. Load Regulation Under Input Voltages of 5 V, 12 V, and 18 V (Bias Supply With Buck and Push Pull)

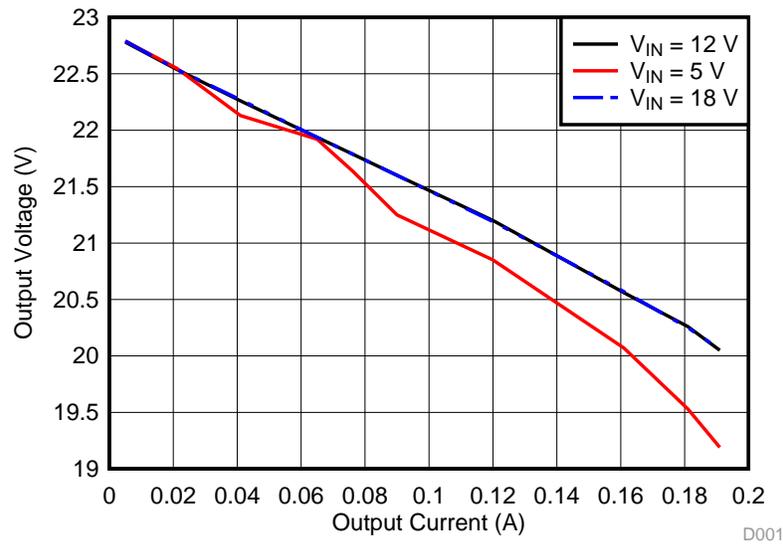

### 3.2.3.6 Load Transients


This section shows load transient measurements of the buck with push-pull transformer driver supply. Load transient response presents how well a power supply copes with the changes in the load current demand. During the test, the load is switching from 0 to full under input voltages of 5 V, 12 V, and 18 V, respectively.

Figure 113. Load Transient Response of the 15-V Rail Under  $V_{IN} = 5\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With Buck and Push Pull)

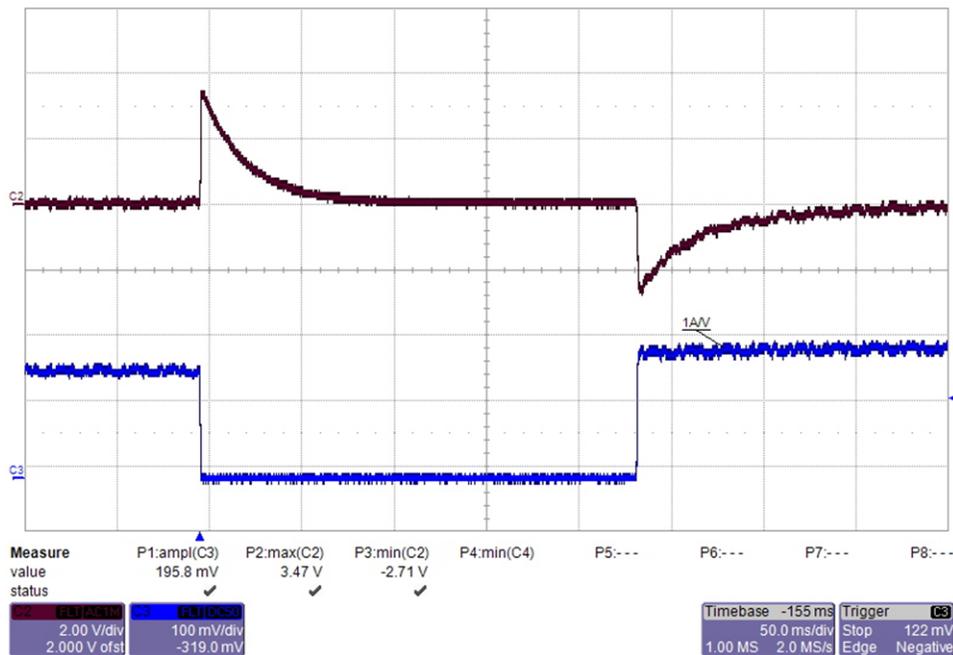


From top to bottom: CH2: output voltage 2 V/div, CH3: load current 1 A/div, 50 ms/div

Figure 114. Load Transient Response of the -9-V Rail Under  $V_{IN} = 5\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With Buck and Push Pull)

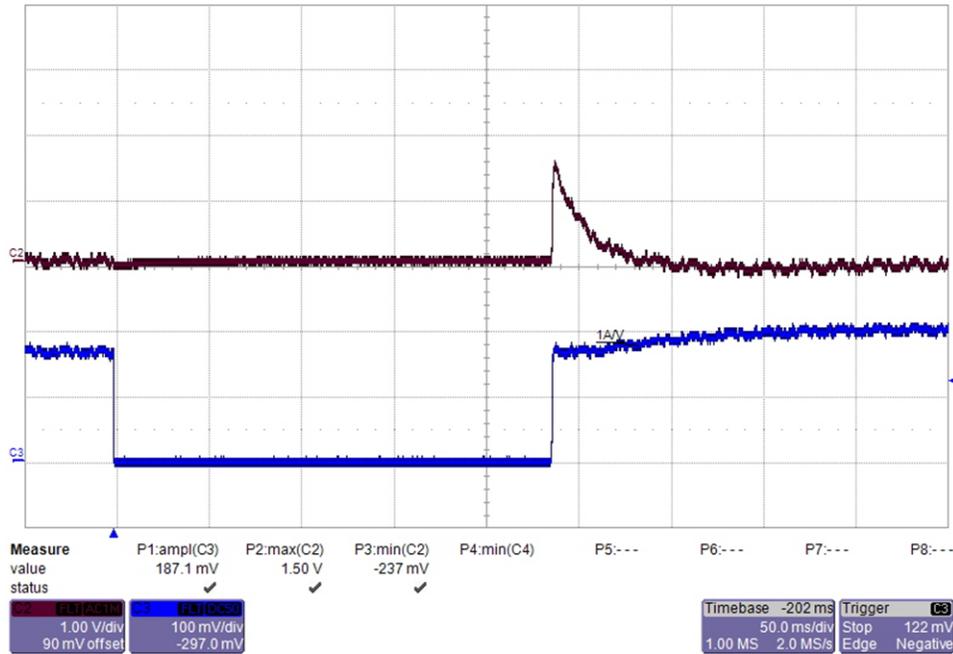


From top to bottom: CH2: output voltage 1 V/div, CH3: load current 1 A/div, 50 ms/div

Figure 115. Load Transient Response of the 15-V Rail Under  $V_{IN} = 12\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With Buck and Push Pull)

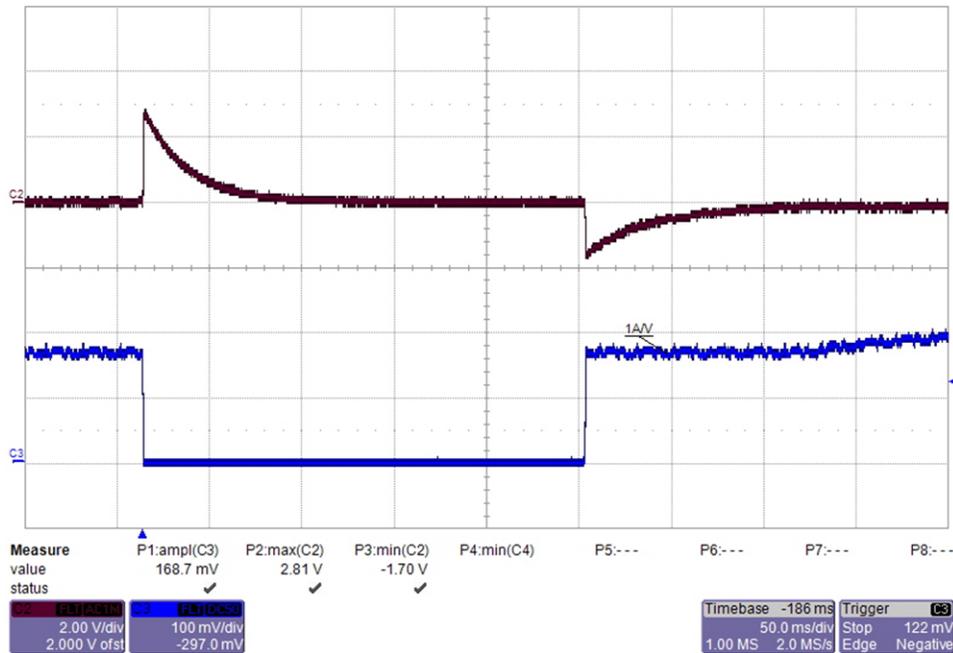


From top to bottom: CH2: output voltage 2 V/div, CH3: load current 1 A/div, 50 ms/div

**Figure 116. Load Transient Response of the -9-V Rail Under  $V_{IN} = 12\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With Buck and Push Pull)**

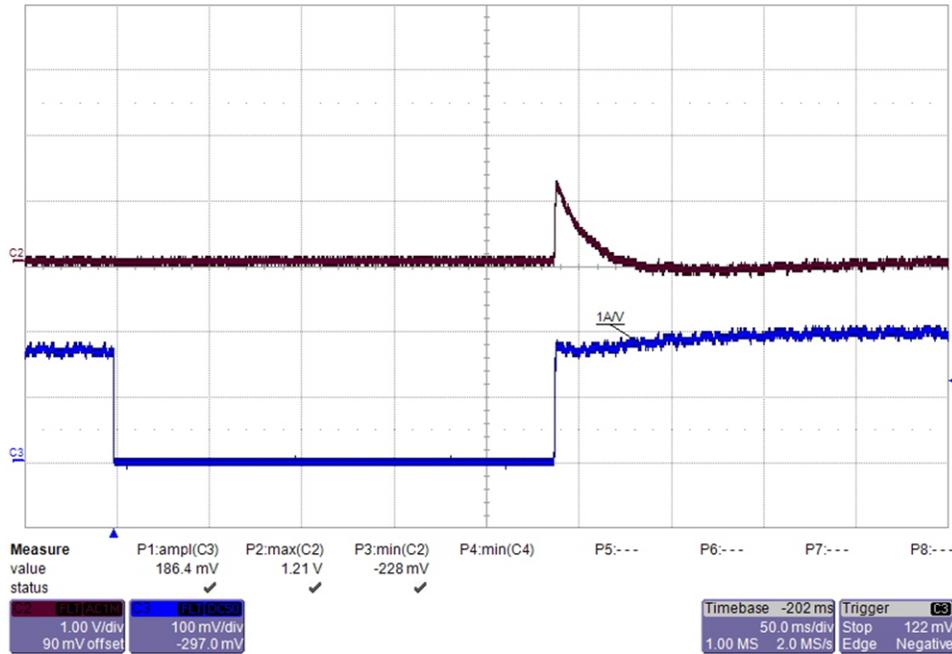


From top to bottom: CH2: output voltage 1 V/div, CH3: load current 1 A/div, 50 ms/div

**Figure 117. Load Transient Response of the 15-V Rail Under  $V_{IN} = 18\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With Buck and Push Pull)**

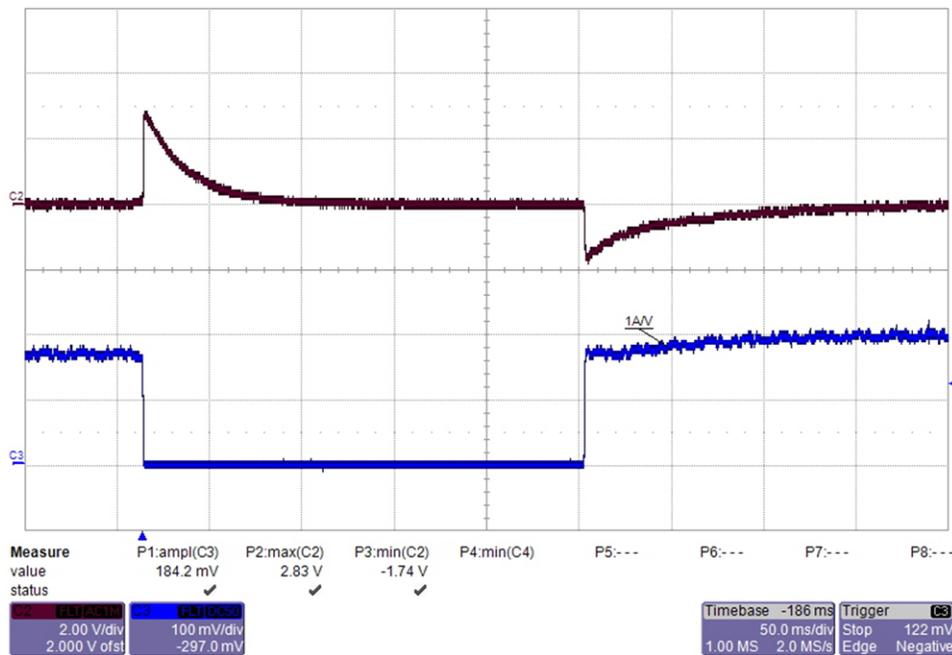

From top to bottom: CH2: output voltage 2 V/div, CH3: load current 1 A/div, 50 ms/div

Figure 118. Load Transient Response of the -9-V Rail Under  $V_{IN} = 18\text{ V}$  and  $I_{OUT}$  Switching Between 0 and 180 mA (Bias Supply With Buck and Push Pull)

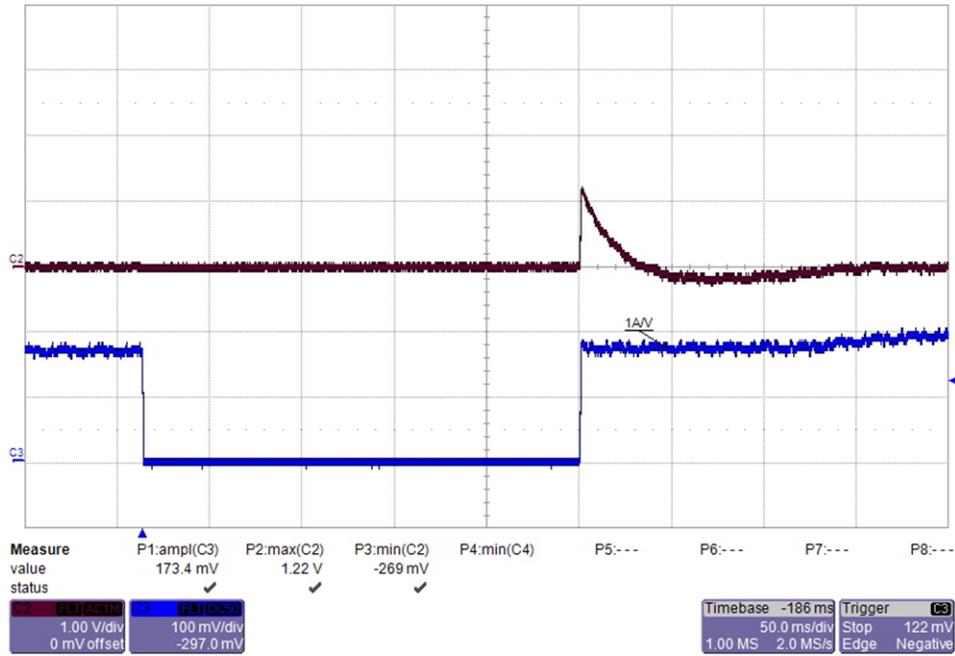


From top to bottom: CH2: output voltage 1 V/div, CH3: load current 1 A/div, 50 ms/div

### 3.2.3.7 Voltage Ripple While Switching IGBT


The buck converter with push-pull transformer driver supply is connected to the isolated gate drivers (ISO5852S-Q1) and the 1200-V IGBT module (FF150R12MS4G) for checking the voltage ripple during the switching transients. The IGBTs are switched at 20- and 50-kHz frequencies, respectively.

**Figure 119. Voltage Ripple of the 15-V Rail While Switching the IGBT Module at 20 kHz (Bias Supply With Buck and Push Pull)**

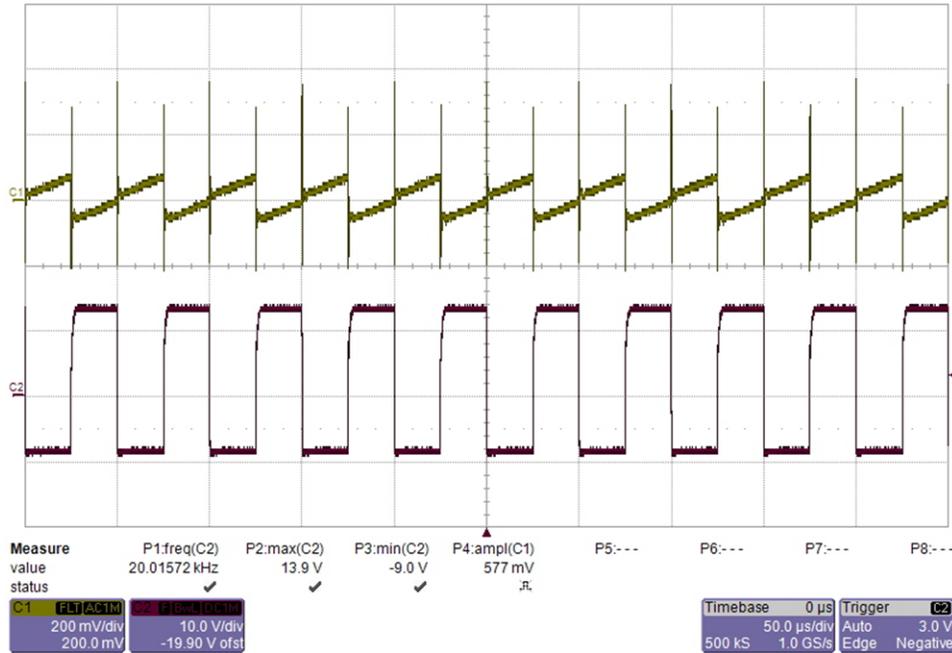


From top to bottom: CH1: output voltage 200 mV/div, CH2: Gate PWM signal 10 V/div, 50 μs/div

**Figure 120. Voltage Ripple of the -9-V Rail While Switching the IGBT Module at 20 kHz (Bias Supply With Buck and Push Pull)**

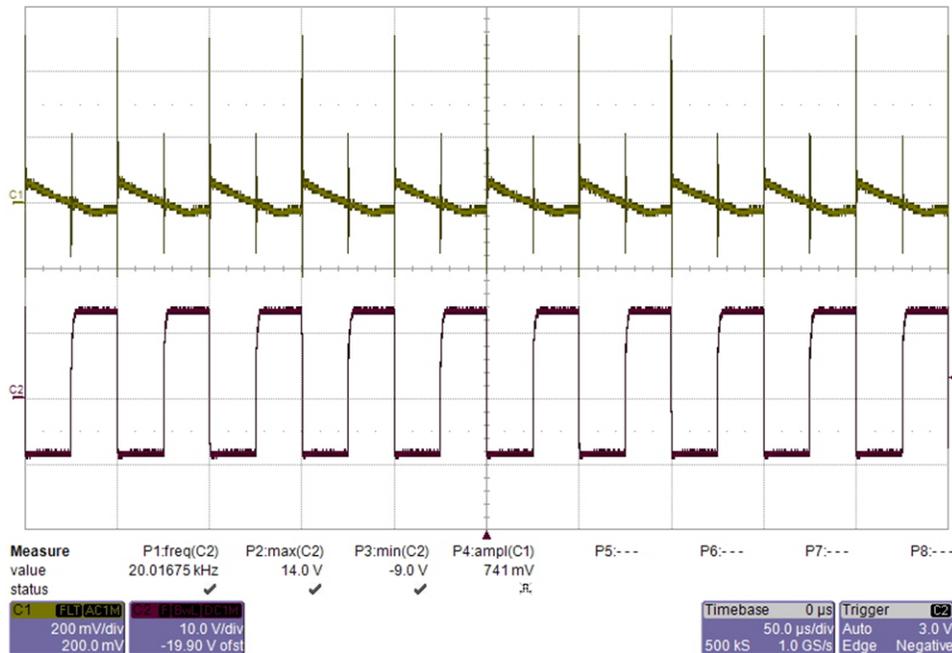


From top to bottom: CH1: output voltage 200 mV/div, CH2: Gate PWM signal 10 V/div, 50 μs/div

Figure 121. Voltage Ripple of the 15-V Rail While Switching the IGBT Module at 50 kHz (Bias Supply With Buck and Push Pull)

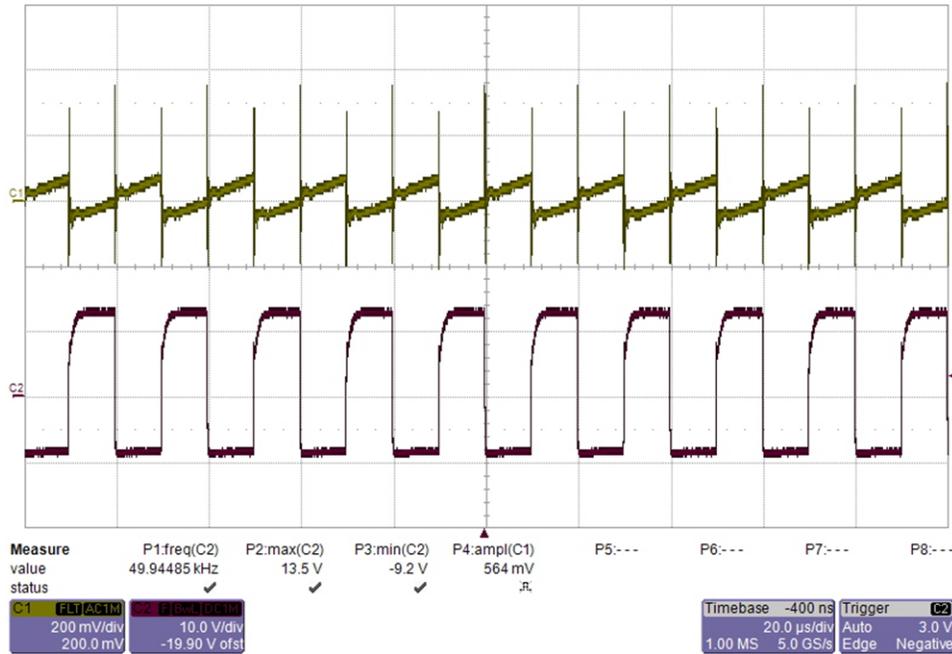

From top to bottom: CH1: output voltage 200 mV/div, CH2: Gate PWM signal 10 V/div, 20  $\mu$ s/div

Figure 122. Voltage Ripple of the -9-V Rail While Switching the IGBT Module at 50 kHz (Bias Supply With Buck and Push Pull)

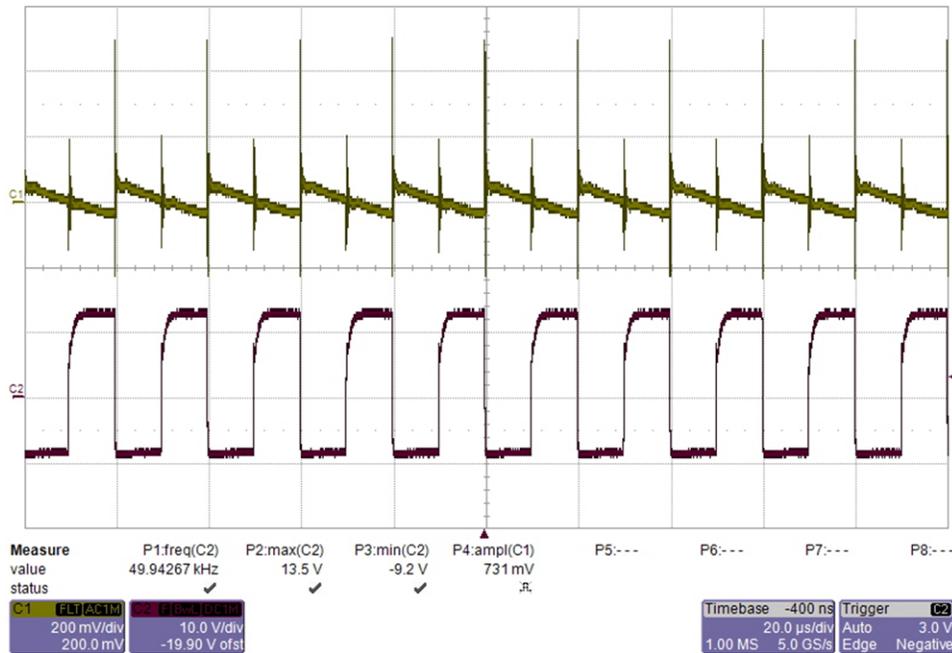


From top to bottom: CH1: output voltage 200 mV/div, CH2: Gate PWM signal 10 V/div, 20  $\mu$ s/div

### 3.2.3.8 Thermal Image

The thermal of the buck converter with a push-pull transformer driver supply is measured under the full-load conditions. The circuit runs at the room temperature for 30 minutes. A 12-V nominal voltage is applied. The converter is loaded with 180 mA. Figure 123 shows the thermal image of the board.

**Figure 123. Thermal Image With  $V_{IN} = 12\text{ V}$  and  $I_{OUT} = 180\text{ mA}$  (Bias Supply With Buck and Push Pull)**

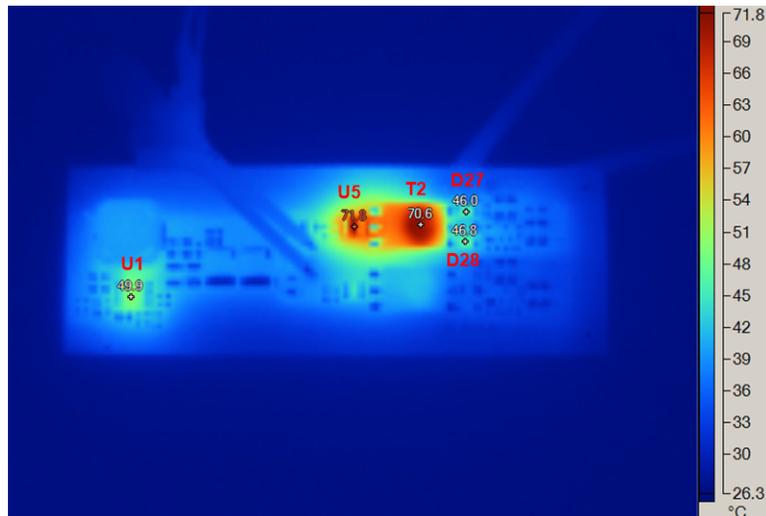

U1: LM46002-Q1, T2: push-pull converter transformer, U5: SN6505-Q1, D27 and D28: secondary rectification diode of the push-pull converter


## 3.2.4 High-Voltage Testing With the IGBT Power Stage

### 3.2.4.1 Double Pulse Test

The double pulse test is performed under high voltage to evaluate the switching parameters of the IGBT and the performance of the gate driver. The test is considered as one periodical snapshot of the system, and it is done with a purely inductive load. The driver parameters of switching speed, thermal, and oscillation or no oscillation can be observed.


A 500-V voltage is applied on the DC bus. The pulse train consists of two pulses with a repetition frequency of about 100 kHz. The widths of two pulses are both 4.5  $\mu\text{s}$ . The delay is set to be 5.5  $\mu\text{s}$  for the voltage and currents to settle out. The rise and fall time of the pulses are set as 5 ns.

Figure 124. Double Pulse Test on the Power Stage

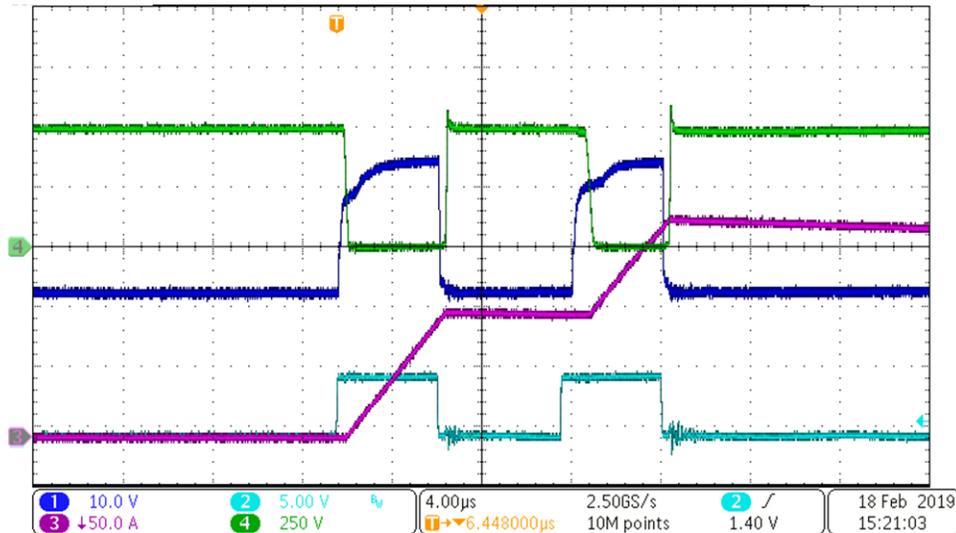

From top to bottom: CH4: IGBT Vds voltage 250 V/div, CH1: IGBT gate signal, 10 V/div, CH2: PWM signal at ISO5852s-Q1 input, 5 V/div, CH3: Inductor current, 50 A/div, 4 µs/div

Figure 125. Generated dv/dt at the IGBT Vds Voltage Turn-off Transient (6 V/ns)

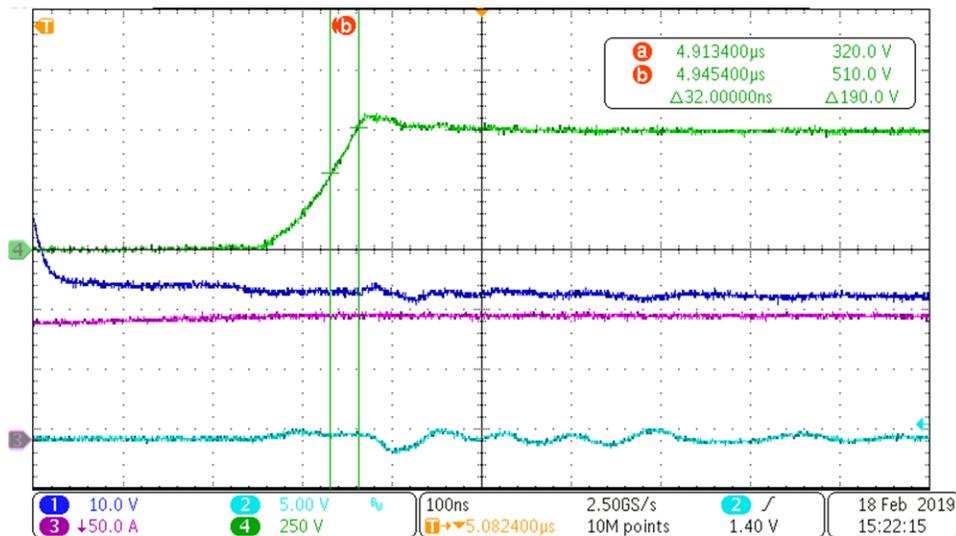

CH4: IGBT Vds voltage 250 V/div, 100 ns/div

### 3.2.4.2 CMTI Test


This reference design is connected to a high-voltage DC bus for high-voltage dv/dt immunity test. Common-mode transient immunity (CMTI) is a maximum tolerable rate of rise or fall of the common-mode voltage applied between two isolated circuits. The unit is normally in kV/us or V/ns. High CMTI means that the two isolated circuits, both transmitter side and receiver side, when striking the insulation barrier with very high rise (positive) slew rate, or high fall (negative) slew rate. For CMTI testing, the peak common-mode voltage should not exceed the allowed maximum repetitive working voltage between the two isolated circuits.

For CMTI testing, 570-V DC bus voltage is applied on the DC bus (limited by the DC link capacitor). 20- $\mu$ H air core inductor is connected between DC bus+ and IGBT half bridge neutral to by pass the high side IGBT. The DC bus- terminal is connected to the low-voltage ground at the bias supply primary side. The low-side IGBT is pulsed twice. Hence, a pulsed high voltage is imposed between the primary and secondary grounds of the high-side bias supply. The switch node of the high-side bias supply is measured.

### 3.2.4.2.1 LM5180-Q1 Flyback Converter


This section shows the CMTI test with LM5180-Q1 based supply. The bias supply is connected to the power stage. The IGBT is switched with 570-V DC bus voltage and at 10.8 V/ns speed of dv/dt. Figure 126 through Figure 128 illustrate that the supply operates smoothly without interruption.

**Figure 126. CMTI Test on the Bias Supply Solution 1 (Bias Supply With LM5180-Q1)**

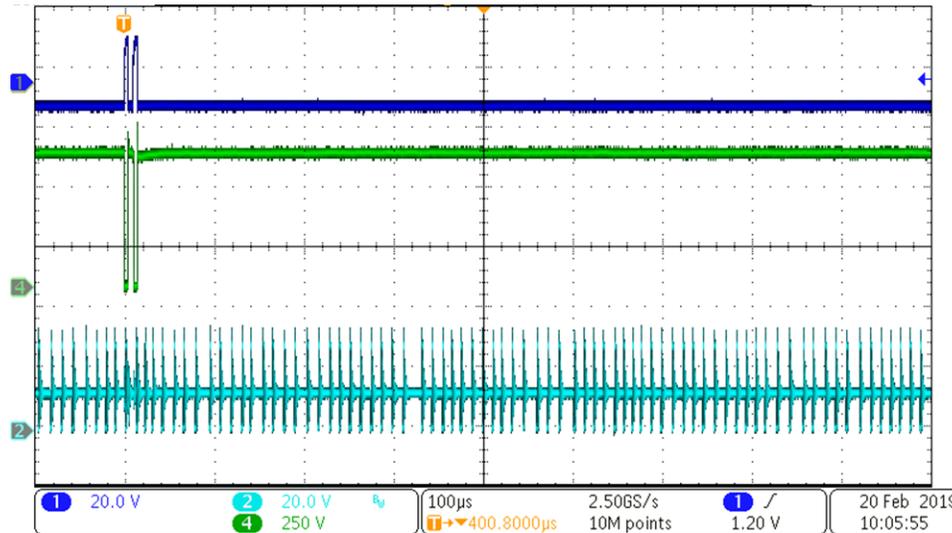


From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 250 V/div, CH2: LM5180-Q1 switch node voltage, 20 V/div, 100  $\mu$ s/div

**Figure 127. CMTI Test Waveform Zoom in (Bias Supply With LM5180-Q1)**

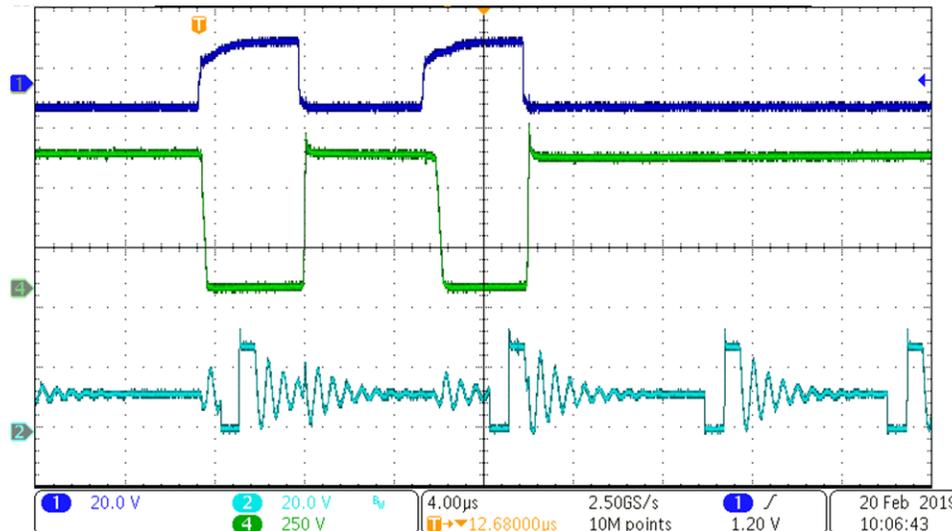

From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 250 V/div, CH2: LM5180-Q1 switch node voltage, 20 V/div, 4  $\mu$ s/div

Figure 128. dv/dt Transient of the CMTI -- 10.8 V/ns (Bias Supply With LM5180-Q1)

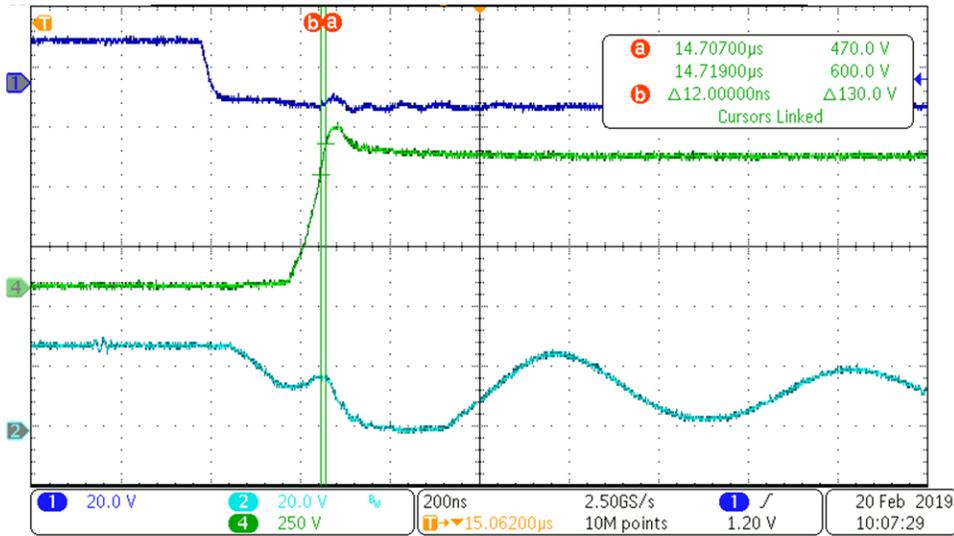


From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 250 V/div, CH2: LM5180-Q1 switch node voltage, 20 V/div, 200 ns/div

### 3.2.4.2.2 TPS40210-Q1 Flyback Converter


This section shows the CMTI test with TPS40210-Q1 based supply. The bias supply is connected to the power stage. The IGBT is switched with 570 V DC bus voltage and at 9.16 V/ns speed of dv/dt. Figure 129 through Figure 131 show that the supply operates smoothly without interruption.

Figure 129. CMTI Test on the Bias Supply Solution 2 (Bias Supply With TPS40210-Q1)

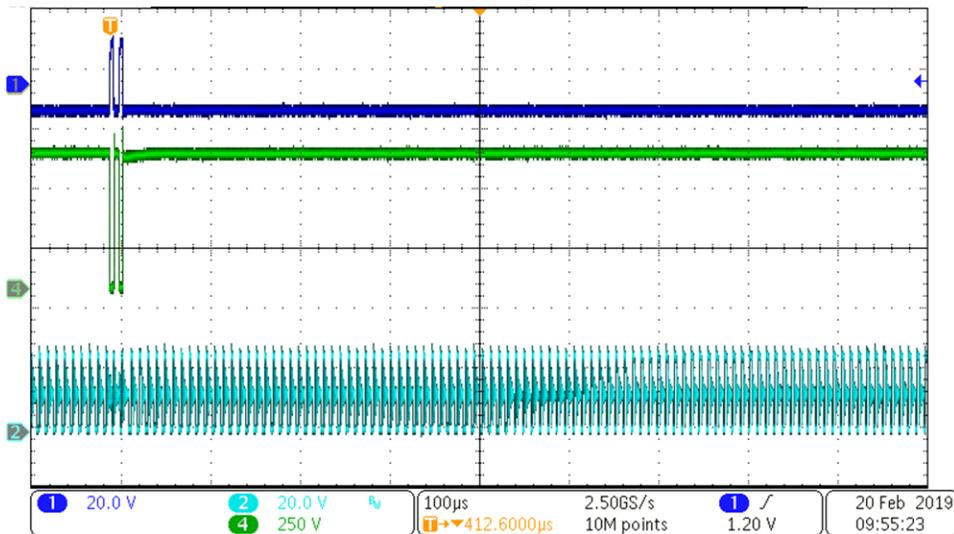


From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 250 V/div, CH2: TPS40210-Q1 switch node voltage, 20 V/div, 100 µs/div

Figure 130. CMTI Test Waveform Zoomed in (Bias Supply With TPS40210-Q1)

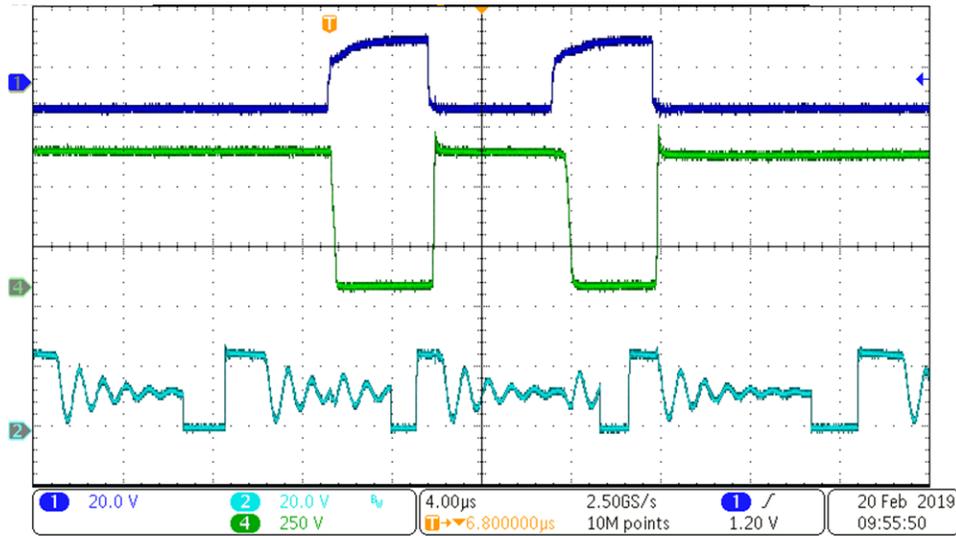

From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 250 V/div, CH2: TPS40210-Q1 switch node voltage, 20 V/div, 4 μs/div

Figure 131. dv/dt Transient of the CMTI -- 9.16 V/ns (Bias Supply With TPS40210-Q1)

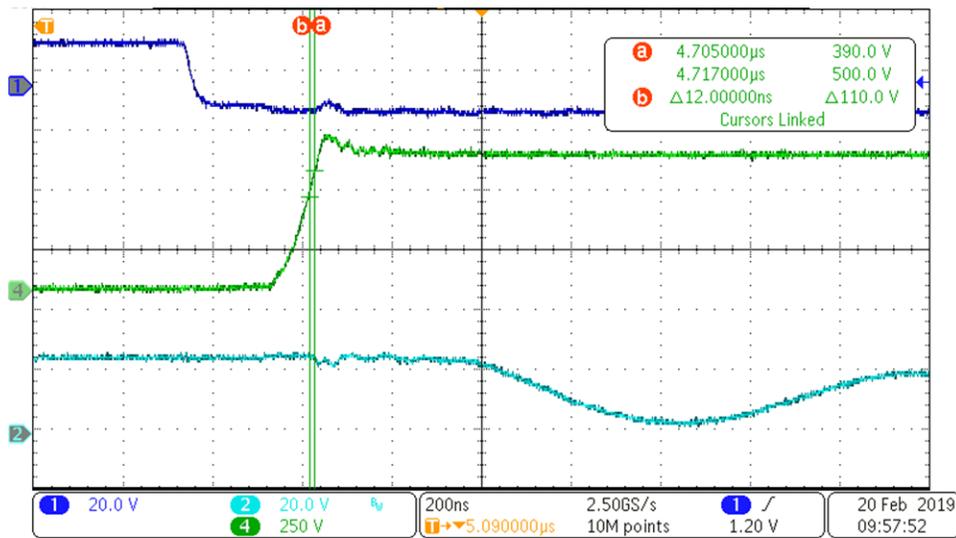


From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 250 V/div, CH2: TPS40210-Q1 switch node voltage, 20 V/div, 200 ns/div

### 3.2.4.2.3 SN6505-Q1 Push-Pull Converter


This section shows the CMTI test with SN6505-Q1-based supply. The bias supply is connected to the power stage. The IGBT is switched with 570 V DC bus voltage and at 10.26 V/ns speed of  $dv/dt$ . Figure 132 through Figure 134 illustrate that the supply operates smoothly without interruption.

Figure 132. CMTI Test on the Bias Supply Solution 3 (Bias Supply With Buck and Push Pull)

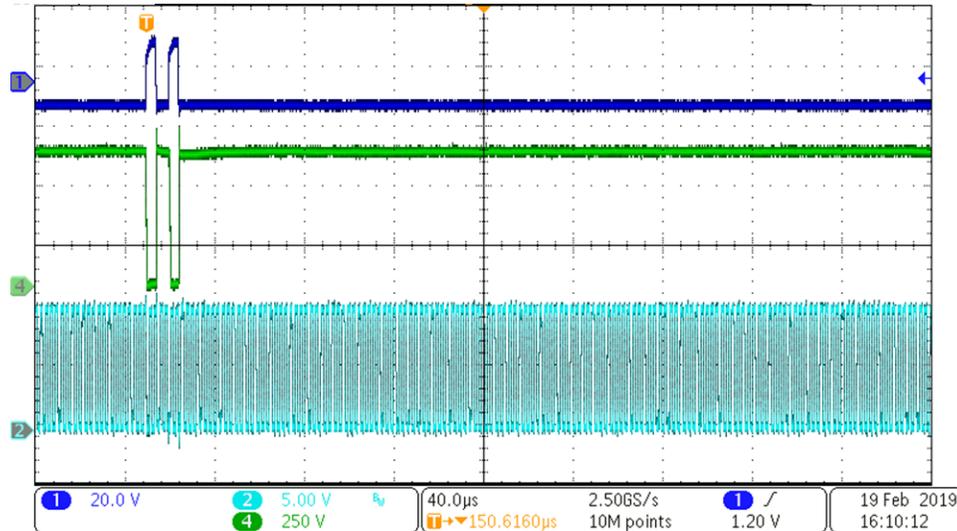


From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 250 V/div, CH2: SN6505-Q1 switch node voltage, 5 V/div, 40 μs/div

Figure 133. CMTI Test Waveform Zoomed in (Bias Supply With Buck and Push Pull)

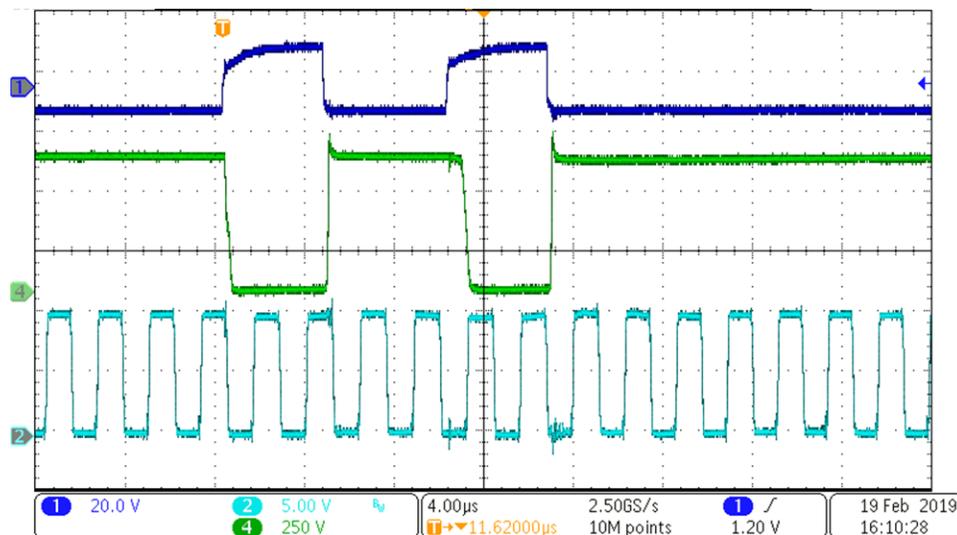

From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 250 V/div, CH2: SN6505-Q1 switch node voltage, 5 V/div, 4 μs/div

Figure 134. dv/dt Transient of the CMTI -- 10.26 V/ns (Bias Supply With Buck and Push Pull)

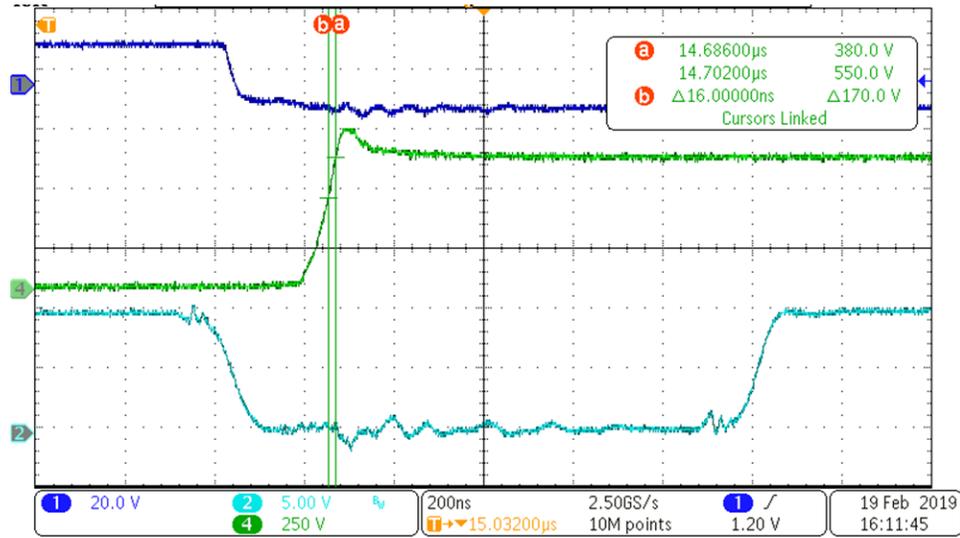

From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 250 V/div, CH2: SN6505-Q1 switch node voltage, 5 V/div, 200 ns/div


### 3.2.4.3 Short-Circuit Test

The IGBT module is turned on into short to measure the performance of power stage and the immunity of bias supplies to the high di/dt. The high side IGBT is shorted with low impedance cable. A 500-V DC bus voltage is applied. The low-side IGBT is pulsed once and turned on into short. Switch node of the high side bias supplies are measured.

#### 3.2.4.3.1 LM5180-Q1 Flyback Converter


This section shows the short-circuit test with LM5180-Q1 based supply. The IGBT is switched with 500-V DC bus voltage and at 4 A/ns speed of di/dt. As can be seen the supply operates smoothly without interruption.

Figure 135. Short-Circuit Test Waveforms (Bias Supply With LM5180-Q1 Flyback)

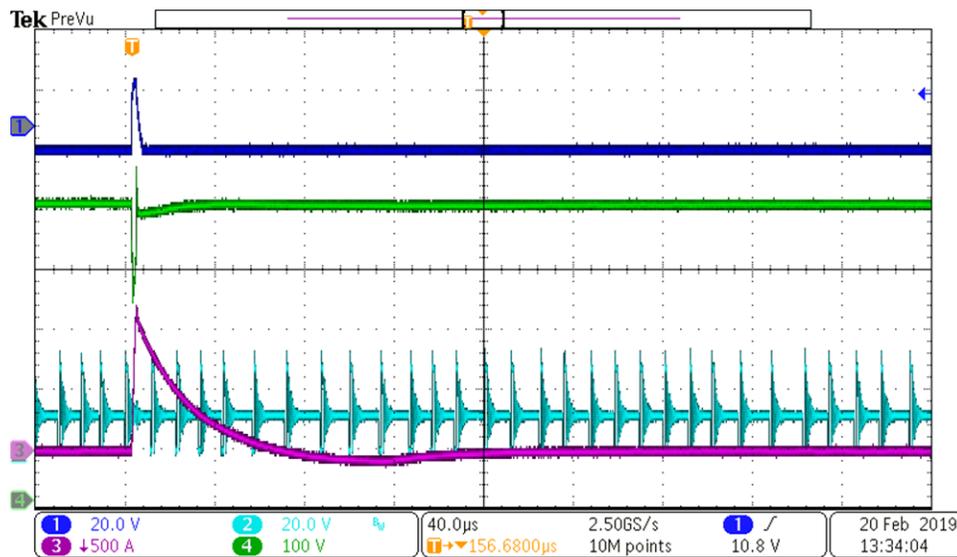

From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 100 V/div, CH2: LM5180-Q1 switch node voltage, 20/div, CH3: Load current flowing from drain to source of the IGBT, 500 A/div, 40 µs/div

Figure 136. di/dt Transient During Short Circuit (Bias Supply With LM5180-Q1 Flyback)

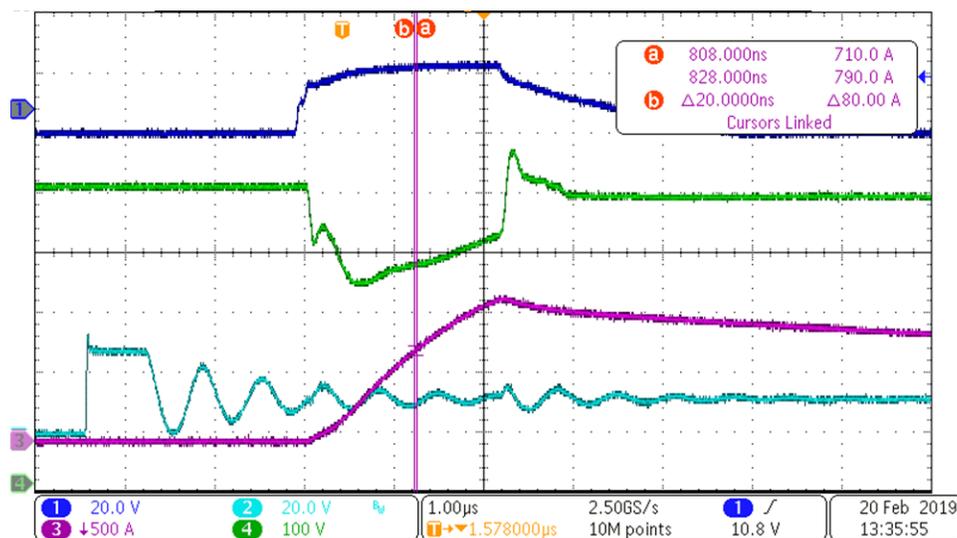


From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 100 V/div, CH2: LM5180-Q1 switch node voltage, 20/div, CH3: Load current flowing from drain to source of the IGBT, 500 A/div, 1 µs/div

3.2.4.3.2 TPS40210-Q1 Flyback Converter


This section shows the short-circuit test with TPS40210-Q1 based supply. The bias supply is connected to the power stage. The IGBT is switched with 500 V DC bus voltage and at 1 A/ns speed of di/dt. Figure 137 and Figure 138 illustrate that the supply operates smoothly without interruption.

Figure 137. Short-Circuit Test Waveforms (Bias Supply With TPS40210-Q1 Flyback)

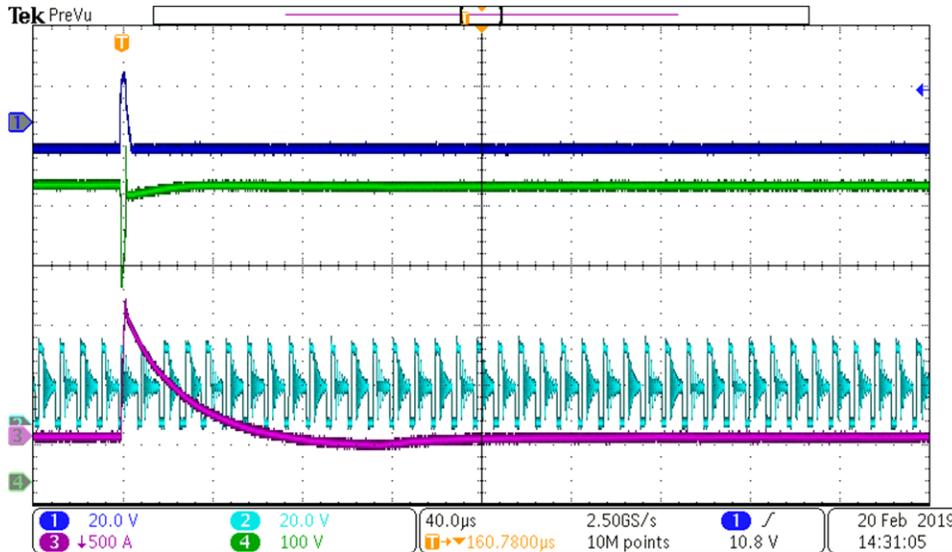

From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 100 V/div, CH2: LM5180-Q1 switch node voltage, 20/div, CH3: Load current flowing from drain to source of the IGBT, 500 A/div, 40 μs/div

Figure 138. di/dt Transient During Short-Circuit (Bias Supply With TPS40210-Q1 Flyback)

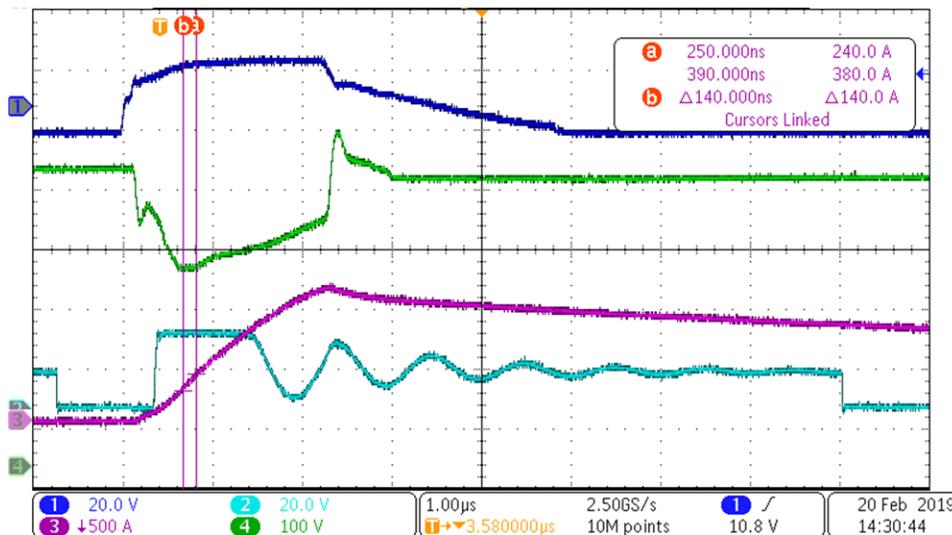


From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 100 V/div, CH2: TPS40210-Q1 switch node voltage, 20/div, CH3: Load current flowing from drain to source of the IGBT, 500 A/div, 1 μs/div

### 3.2.4.3.3 SN6505-Q1 Push-Pull Converter


This section shows the short-circuit test with SN6505-Q1-based supply. The bias supply is connected to the power stage. The IGBT is switched with 500-V DC bus voltage and at 0.7 A/ns speed of di/dt. The waveforms in Figure 139 and Figure 140 illustrate that the supply operates smoothly without interruption.

**Figure 139. Short-Circuit Test Waveforms (Bias Supply With Buck and Push Pull)**

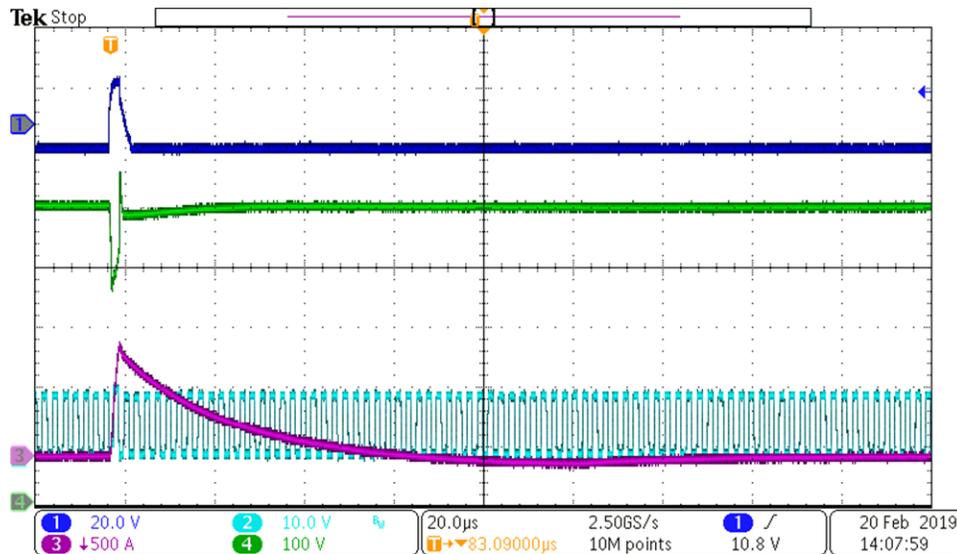

From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 100 V/div, CH2: SN6505-Q1 switch node voltage, 20/div, CH3: Load current flowing from drain to source of the IGBT, 500 A/div, 20 µs/div

**Figure 140. di/dt Transient During Short Circuit (Bias Supply With Buck and Push Pull)**

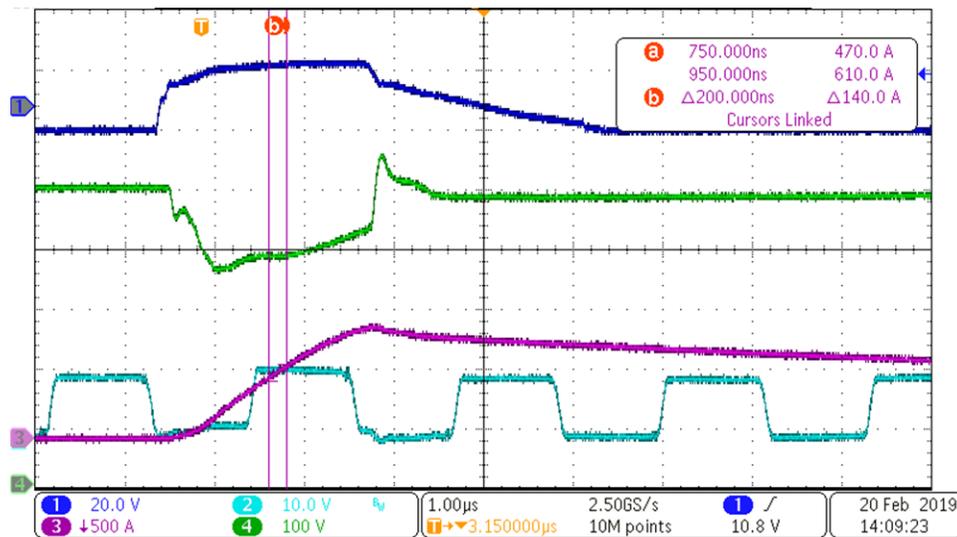

From top to bottom: CH1: IGBT gate signal, 20 V/div, CH4: IGBT Vds voltage, 100 V/div, CH2: SN6505-Q1 switch node voltage, 20/div, CH3: Load current flowing from drain to source of the IGBT, 500 A/div, 1 µs/div

## 4 Design Files

### 4.1 Schematics

To download the schematics, see the design files at [TIDA-020014](#).

### 4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-020014](#).

### 4.3 PCB Layout Recommendations

#### 4.3.1 Layout Prints

The power stage of TIDA-020014 implements a 4-layer PCB. All bias supplies of TIDA-020014 implement 2-layer PCBs. To download the layer plots, see the design files at [TIDA-020014](#).

### 4.4 Altium Project

To download the Altium Designer® project files, see the design files at [TIDA-020014](#).

### 4.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-020014](#).

### 4.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-020014](#).

## 5 Software Files

To download the software files, see the design files at [TIDA-020014](#).

## 6 Related Documentation

1. Texas Instruments, [Automotive Wide  \$V\_{IN}\$  Front-End Power Reference Design w/Cold Crank Operation & Transient Protection](#)
2. Texas Instruments, [4.5V to 65V input bias supply with power stage reference design for automotive IGBT/SiC gate drivers](#)
3. Texas Instruments, [98.6% Efficiency, 6.6-kW Totem-Pole PFC Reference Design for HEV/EV Onboard Charger](#)
4. Texas Instruments, [Automotive Dual Channel SiC MOSFET Gate Driver Reference Design with Two Level Turn-off Protection](#)

### 6.1 Trademarks

E2E is a trademark of Texas Instruments.  
Altium Designer is a registered trademark of Altium LLC or its affiliated companies.  
CoilCraft is a registered trademark of Coilcraft Inc..  
All other trademarks are the property of their respective owners.

### 6.2 Third-Party Products Disclaimer

TI'S PUBLICATION OF INFORMATION REGARDING THIRD-PARTY PRODUCTS OR SERVICES DOES NOT CONSTITUTE AN ENDORSEMENT REGARDING THE SUITABILITY OF SUCH PRODUCTS OR SERVICES OR A WARRANTY, REPRESENTATION OR ENDORSEMENT OF SUCH PRODUCTS OR SERVICES, EITHER ALONE OR IN COMBINATION WITH ANY TI PRODUCT OR SERVICE.

## 7 Terminology

**AFE**— Analog Front End

**AEC**— Automotive Electronics Council

**ESR**— Equivalent Series Resistance

**EMI**— Electromagnetic Interference

**EMC**— Electromagnetic Compatibility

**DM**— Differential Mode

**CM**— Common Mode

**UVLO**— Undervoltage Lockout

**MOSFET**— Metal Oxide Semiconductor Field Effect Transistor

**CISPR**— International Special Committee on Radio Interference

**PE**— Protective Earth

**RMS**— Root Mean Square

**ISO**— International Organization for Standardization

**BOM**— Bill of Material

**OEM**— Original Equipment Manufacturer

**AN**— Artificial Network

**LISN**— line impedance stabilization network

**EUT**— Equipment Under Test

**PCB**— Printed Circuit Board

**HEV**— Hybrid Electric Vehicle

**EV**— Electric Vehicle

## 8 About the Author

**Xun Gong** is an Automotive Systems Engineer at Texas Instruments, where he is responsible for developing reference design solutions for HEV/EV powertrain applications. Xun brings to this role expertise in the field of onboard charger, DC/DC converter, and traction inverter with IGBT and SiC (Silicon Carbide) power transistors. Xun achieved his Ph.D. in electrical engineering from Delft University of Technology in Delft, Netherlands. Xun Gong has more than 10 technical paper publications and he won the 1st prize paper of the *Academic Journal IEEE Transactions on Power Electronics* in 2014.

**Xiong Li** is a systems engineer from the high power drivers team. Xiong is responsible for defining high-voltage isolated gate drivers for high-power IGBTs and SiC MOSFETs. Prior joining TI, Xiong completed his PhD degree from the University of Texas at Dallas in electrical engineering with focus on power electronics. Xiong did summer internship with Tesla Motors in 2015 and Emerson Network Power in 2011.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2019, Texas Instruments Incorporated