

Series Resistance Temperature Detector (RTD) Sensing Reference Design



Description

This reference design demonstrates a fully space graded ratiometric temperature sensing circuit using [ADS1282EVM-PDK](#). This circuit measures temperature at up to 10 different locations without any use of buffers. The majority of space applications require temperature measurement in multiple sub-systems that will benefit from this multi-location circuit.

Resources

TIDA-060042	Design Folder
ADS1282-SP	Product Folder
LMP7704-SP	Product Folder
TPS7A4501-SP	Product Folder

Features


- Measure temperature at up to 10 different locations
- Ratiometric temperature sensing
- 99.93% accuracy
- No use of buffer
- Small size and low cost

Applications

- [Satellite electrical power system \(EPS\)](#)
- [Radar imaging payload](#)
- [Communications payload](#)
- [Command and data handling \(C&DH\)](#)



[Ask our TI E2E™ support experts](#)

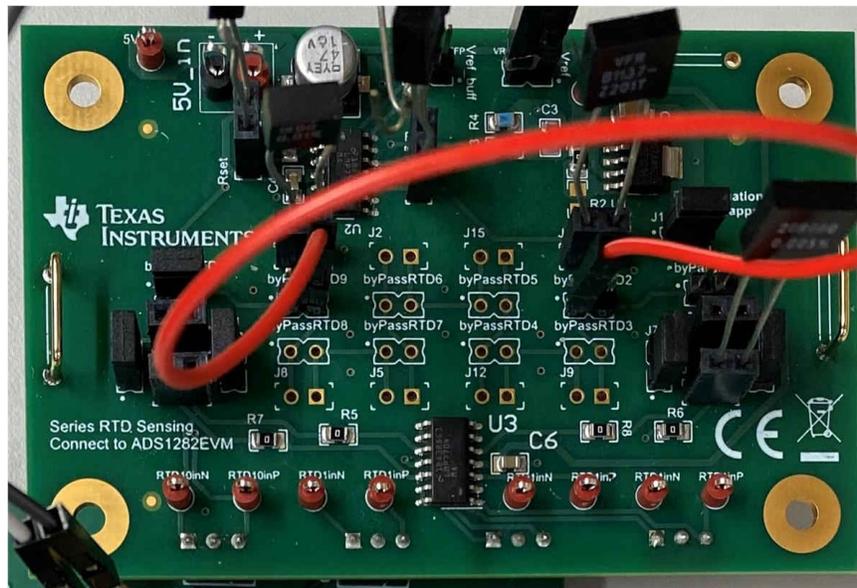

1 System Description

This reference design demonstrates a temperature sensing system that can measure temperature at 10 different locations. The system consists of [TIDA-060042](#) and [ADS1282EVM-PDK](#). [TIDA-060042](#) is a *Resistance Temperature Detector* (RTD) board that connects 10 RTDs in a series. Shown in [Figure 2-1](#), each of the RTD outputs a differential signal proportional to its resistance, and is captured by [ADS1282EVM-PDK](#) for temperature calculation. Due to the large input impedance of [ADS1282-SP](#), the accuracy of the measurement is greater than 99.93% without calibration or using any buffers. Compare to traditional space temperature measurement circuits, this circuit is not only more flexible and accurate, but also has smaller size and lower cost for reducing use of buffers.

2 System Overview

[Table 2-1](#) details the system specifications of [TIDA-060042](#), the RTD board, which is designed to connect to [ADS1282EVM-PDK](#) for temperature measurement.

Table 2-1. TIDA-060042 System Specification

	Net name	Description	Value	Unit	Error [%]
Power Supply	5V_in	RTD board power supply	5	V	N/A
Input	Rref	Sets the Vref for ADS1282EVM	4.76 for $I_{RTD}^1 \approx 0.5$ mA	kOhm	0.05%
			2.18 for $I_{RTD} \approx 1$ mA		
			1.1 for $I_{RTD} \approx 1.5$ mA		
	Rset	Sets the current at all RTDs and Rref	1.5k for $I_{RTD} \approx 0.5$ mA	Ohm	0.05%
			750 for $I_{RTD} \approx 1$ mA		
			500 for $I_{RTD} \approx 1.5$ mA		
RTD1 to RTD10	10 RTDs located at different locations	0 to 135	Ohm	0.05%	
Output	ADCin1	Voltage across RTD1	0 to $V_{ref}^2/(2*gain^3)$	V	0.1%
	ADCin2	Voltage across RTD2	0 to $V_{ref}/(2*gain)$	V	0.1%

2.1 Block Diagram

This reference design uses equivalent commercial components on the PCB instead of the full space grade ICs for electrical performance evaluation. Compare to space grade IC, commercial devices have similar electrical characteristics but is not radiation tolerant. In addition, [ADS1282-SP](#) is not placed on [TIDA-060042](#). Instead, [TIDA-060042](#) is designed to connect to [ADS1282EVM-PDK](#) for temperature measurement. [Figure 2-1](#) illustrates the recommended comprehensive block diagram, and [Figure 2-2](#) illustrates how [TIDA-060042](#), the RTD board, is connects to [ADS1282EVM-PDK](#) for temperature measurement.

¹ Current of all RTDs, Rset, and Rref as shown in [Figure 2-1](#)

² Vref is the voltage across Rref in [Figure 2-1](#)

³ [ADS1282-SP](#) programmable gain amplifier (PGA) gain, which could be set to 1, 2, 4, 8, 16, 32, and 64

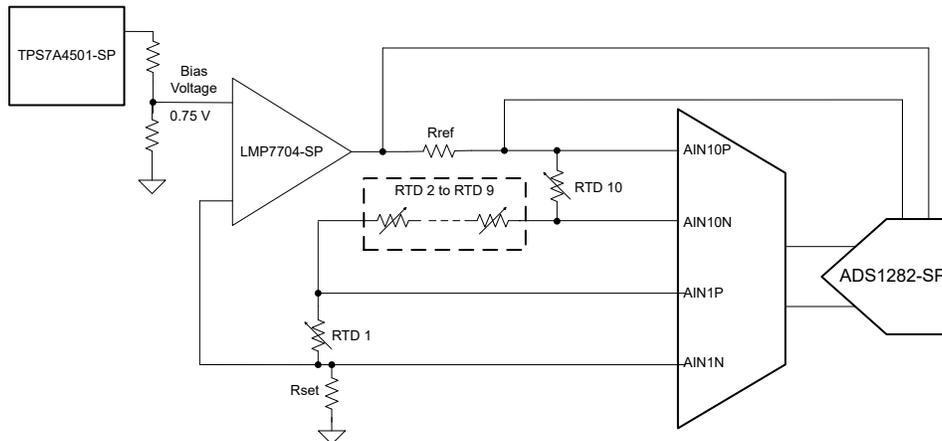


Figure 2-1. Temperature Sensing Application Block Diagram

LMP7704-SP, a rail-to-rail input and output op-amp, supplies a fixed current to each of the RTDs as well as to Rset and Rref. The value of Rset will set the current drawn by the series resistances, thus to adjust the current, Rset needs to be modified. The bias voltage is set to 0.75 V. Voltage across Rref is the ADS1282-SP reference voltage for setting the ADC Full Scale Range (FSR). Compared to Figure 2-1, Figure 2-2 has the mux removed. Only RTD1 and RTD10 are connected to ADS1282EVM-PDK for evaluating the effect of common mode voltage (Vcm) on the measured result.

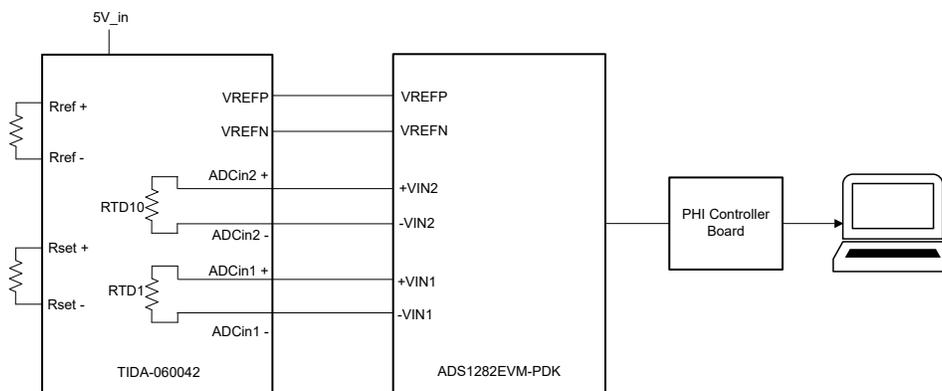


Figure 2-2. Connection Between TIDA-060042 and ADS1282EVM-PDK

2.2 Design Considerations

As Figure 2-2 illustrates, TIDA-060042 is designed to connect to ADS1282EVM-PDK to monitor voltage across RTD1 and RTD10. TIDA-060042 can measure the RTD voltages in two different ways: with or without buffers. Buffers are provided as an option but the main focus in this reference design is to evaluate ADS1282-SP without using any buffers. The following sections describe the formulas to calculate Rset, Rref, and the internal ADC gain, as well as simulations showing the effect of analog multiplexer connecting between TIDA-060042 and ADS1282EVM-PDK.

2.2.1 Rset, Rref, and Gain Calculation

ADS1282-SP input ranges from 0.7 V above AVSS and 1.25 V below AVDD. With AVDD set to 5 V, ADS1282EVM-PDK accepts inputs from 0.7 V to 3.75 V. In TIDA-060042, the Bias Voltage in Figure 2-1 is set to 0.75V. Based on the desired RTD current (I_{RTD}), Rset is calculated with Equation 1.

$$R_{set} = \frac{0.75 \text{ V}}{I_{RTD}} \quad (1)$$

Using the maximum RTD resistance, in this design is 135 Ω , Rref and Gain are calculated with the two formulas (Equation 2 and Equation 3).

$$R_{ref} > 135 \Omega \times 2 \times \text{Gain} \tag{2}$$

$$R_{ref} < \frac{5V}{I_{RTD}} - R_{set} - 135 \Omega \times 10 \tag{3}$$

Once Rset, Rref, and gain are confirmed, the percentage of positive ADC FSR used by each RTD is calculated with Equation 4. For highest performance, Rref is preferred to be as small as possible to maximize the use of positive FSR.

$$\% \text{ positive FSR used} = \frac{135 \Omega \times 2 \times \text{Gain}}{R_{ref}} \times 100\% \tag{4}$$

2.2.2 Analog Multiplexer Effect

Analog multiplexer (Mux) is not implemented in the design hardware, but the Mux is considered through simulation.

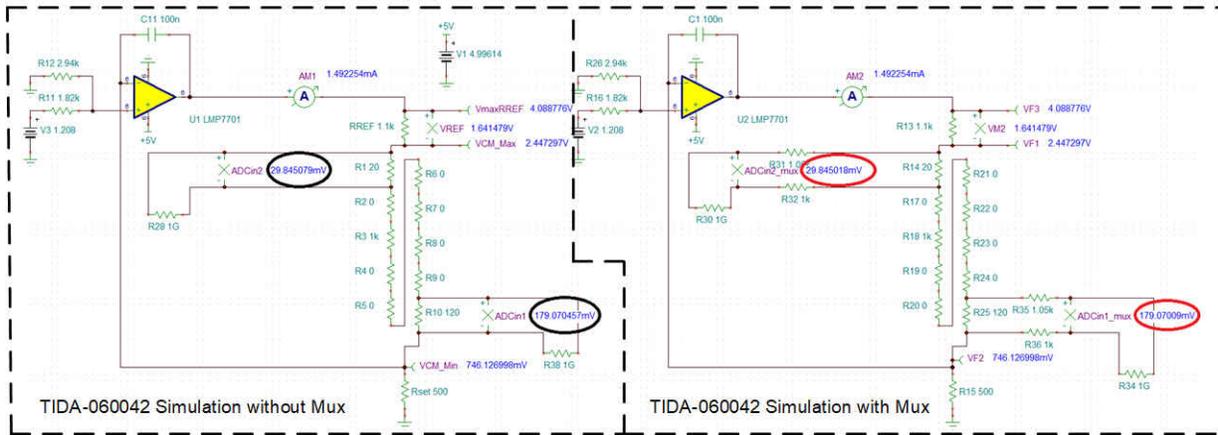


Figure 2-3. Analog Multiplexer Effect Simulation

Table 2-2. Analog Multiplexer Effect Simulation Results

	Without Mux	With mux	% difference
ADCin1 [mV]	179.070457	179.07009	0.0002%
ADCin2 [mV]	29.845079	29.845018	0.0002%

As shown in Figure 2-3 and Table 2-2, the RTD board is simulated with and without mux, and their schematic are shown on the right and left side of the figure, along with simulation result circled in red and black. To simulate a mux, a resistor to represent the MUX on-resistance is added and set to 1 kΩ allowing 50 Ω difference between each channel. Since ADS1282-SP has one GΩ differential input impedance with PGA chopping enabled, there are only about 0.0002% difference between the two circuits output. Compare this error with the error causing by the RTD itself, the error from mux is negligible and does not affect the overall performance.

2.3 Highlighted Products

The following sections describe the highlighted products used in this design.

2.3.1 ADS1282-SP

The [ADS1282-SP](#) is an extremely high-performance, single-chip analog-to-digital converter (ADC) with an integrated, low-noise programmable gain amplifier (PGA) and two-channel input multiplexer (mux). The [ADS1282-SP](#) is suitable for the demanding needs of energy exploration and seismic monitoring environments.

2.3.2 LMP7704-SP

The LMP7704-SP is a precision amplifier with low input bias, low offset voltage, 2.5-MHz gain bandwidth product, and a wide supply voltage. The device is radiation hardened and operates in the military temperature range of -55°C to $+125^{\circ}\text{C}$. The high DC precision of this amplifier, specifically the low offset voltage of $\pm 60\ \mu\text{V}$ and ultra-low input bias of $\pm 500\ \text{fA}$, make this device an excellent choice for interfacing with precision sensors with high output impedance. This amplifier can be configured for transducer, bridge, strain gauge, and trans-impedance amplification.

2.3.3 TPS7A4501-SP

The TPS7A4501-SP is a low-dropout (LDO) regulator optimized for fast-transient response. The 5962-1222402VHA can supply 750 mA of output current with a dropout voltage of 300 mV. The 5962R1222403VXC can supply 1.5 A of output current with a dropout voltage of 320 mV. Quiescent current is well controlled; it does not rise in dropout, as with many other regulators. In addition to fast transient response, the TPS7A4501-SP regulator has very-low output noise, which makes it better for sensitive RF supply applications.

Radiation reports for all the listed TI devices in [Table 2-3](#) are found on their TI.com product folder.

Table 2-3. Radiation Qualification

PART NUMBER	TOTAL IONIZATION DOSAGE (kRAD)	Single Event Latch-Up Immune (MeV-cm ² /mg)
ADS1282-SP	50	50 at 125°C, 60 at 80°C
LMP7704-SP	100	85
TPS7A4501-SP	100	86

3 Hardware, Software, Testing Requirements, and Test Results

3.1 Hardware Requirements

The following three pieces of hardware needed to evaluate the accuracy of the series RTDs temperature sensing system:

- TIDA-060042: the RTD board that connects 10 RTDs in series and outputs differential RTD voltages as well as the reference voltage. [Figure 3-1](#) shows the schematic of TIDA-060042.

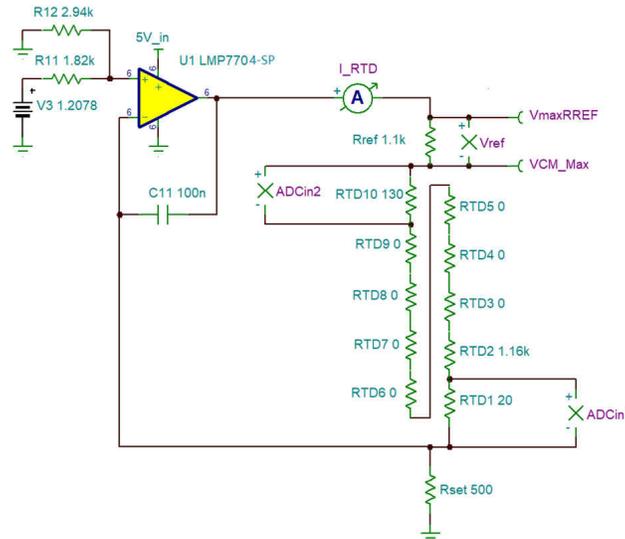


Figure 3-1. TIDA-060042 Schematic

- [ADS1282EVM-PDK](#): the [ADS1282-SP](#) evaluation module. Modification is needed on the evaluation module such that Analog Front End (AFE) is bypass and Vref is directly provided by TIDA-060042.
- PHI Controller board: this board comes with [ADS1282EVM-PDK](#). The board provides a convenient communication interface to [ADS1282EVM-PDK](#) over a USB 2.0 (or higher) for power delivery as well as digital input and output

[Figure 3-2](#) shows an image with all three pieces of hardware connected.

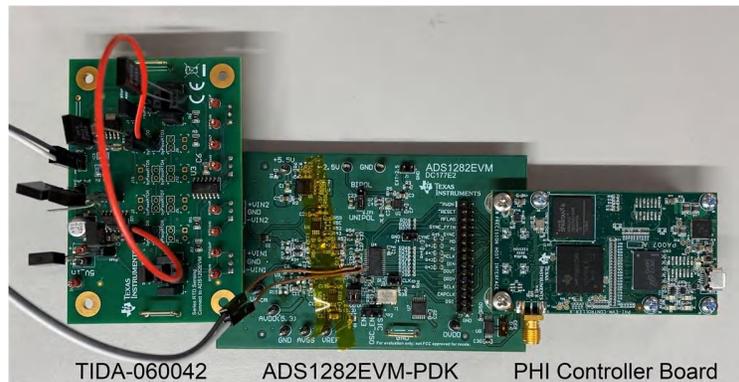


Figure 3-2. Hardware Setup

3.2 Software Requirements

The [ADS1282EVM-PDK](#) graphical user interface (GUI) is needed to evaluate TIDA-060042. This GUI software includes graphical tools for data capture, histogram analysis, spectral analysis, and linearity analysis. This GUI also has a provision for exporting data to a text file for post-processing. Refer to the [ADS1282EVM-PDK](#) user guide for more information.

3.3 Test Setup

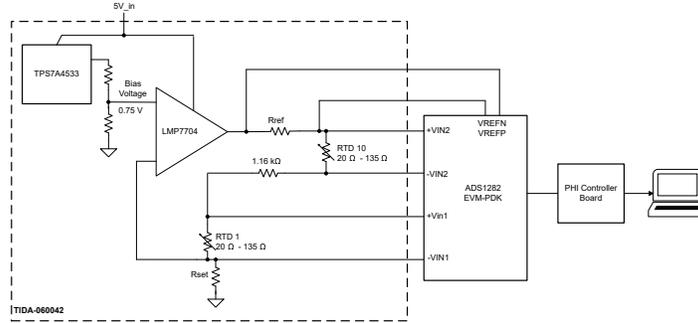


Figure 3-3. Lab Setup to Simulate Temperature Measurement

Figure 3-3 illustrates the block diagram of the lab setup for simulating temperature measurement. The purpose of this setup is to record RTD1 and RTD10's differential voltages. These two RTDs have the highest (High Vcm) and lowest (Low Vcm) common mode voltages, respectively. All RTDs are connected in series and current is biased by Rset. During data collection, Rset is set to three different values thus three sets of data are collected.

Following equations in Section 2.2.2, with I_{RTD} set to 0.497 mA, 0.995 mA, and 1.49 mA, the Rset, Rref, Gain, and % positive FSR used are calculated and illustrates in Table 3-1.

Table 3-1. Test Setup with Different I_{RTD}

	Setup 1	Setup 2	Setup 3
I _{RTD} [mA]	0.497	0.995	1.49
Rset [Ω]	4.5k	750	500
Rref [Ω]	4.76k	2.18k	1.1k
Gain	16	8	4
% positive FSR used	90.8%	99.1%	98.2%

Figure 3-4 illustrates how (circled in red) to modify PGA gain, configure mux, and read the returned codes on GUI.

Figure 3-4. ADS1282EVM-PDK GUI Setting

The ADS1282EVM-PDK GUI returns values with 2 formats, codes and voltage. The codes is a 31 bits data and is used to calculate RTD resistance with the following equation, and the calculated value is compared with the actual resistor value for error analysis.

$$\text{RTD Resistance} = \frac{\text{Codes}}{\text{Gain} \times 2^{31}} \times \text{Rref} \quad (5)$$

3.4 Test Results

Figure 3-5 to Figure 3-7 illustrates the RTD resistance measurement percent error. Through out all three sets of collected data, the common mode voltage (Vcm) have a small effect on the result. All captured data shown in Figure 3-7 have percent error less than 0.07% error. Therefore, it is recommended to bias the RTD current at around 1.5 mA for the best performance.

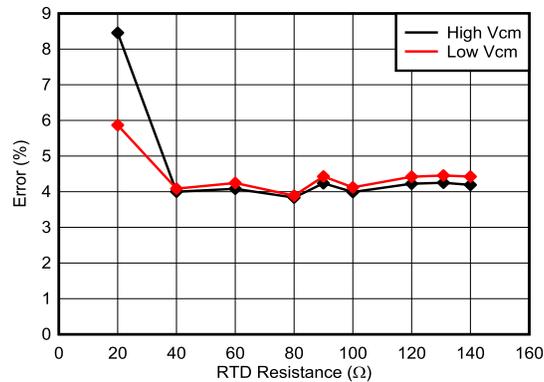


Figure 3-5. Temperature Measurement Accuracy with $I_{RTD} = 0.5$ mA

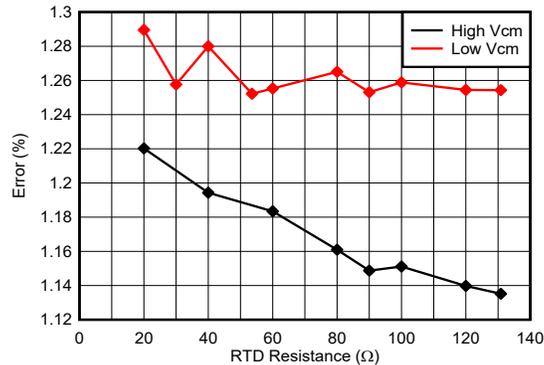


Figure 3-6. Temperature Measurement Accuracy with $I_{RTD} = 1$ mA

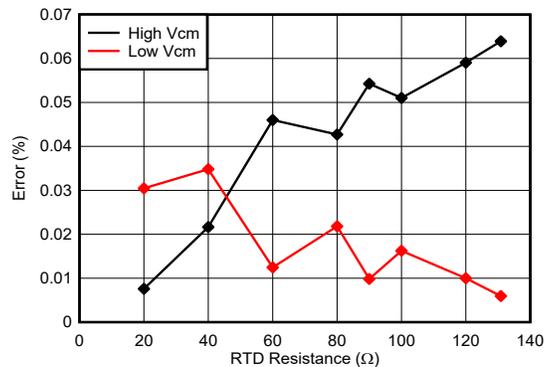


Figure 3-7. Temperature Measurement Accuracy with $I_{RTD} = 1.5$ mA

4 Design and Documentation Support

4.1 Design Files

4.1.1 Schematics

To download the schematics, see the design files at [TIDA-060042](#).

4.1.2 BOM

To download the bill of materials (BOM), see the design files at [TIDA-060042](#).

4.2 Documentation Support

1. Texas Instruments, [ADS1282-SP High-resolution analog-to-digital converter \(ADC\)](#) data sheet
2. Texas Instruments, [ADS1282EVM-PDK ADS1282 performance demonstration kit](#) data sheet

4.3 Support Resources

[TI E2E™ support forums](#) are an engineer's go-to source for fast, verified answers and design help — straight from the experts. Search existing answers or ask your own question to get the quick design help you need.

Linked content is provided "AS IS" by the respective contributors. They do not constitute TI specifications and do not necessarily reflect TI's views; see TI's [Terms of Use](#).

4.4 Trademarks

TI E2E™ are trademarks of Texas Instruments.
All trademarks are the property of their respective owners.

5 About the Author

Jiajun Guan is a system engineer at Texas Instruments, where he is responsible for developing system designs for the Aerospace and Defense sector. Jiajun has been with TI since 2021. Jiajun earned his Electrical Engineering Bachelor and Masters degrees from California Polytechnic State University.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated