

Brush up on the Latest Motor Design Considerations for Appliances



Richard Wang11



Variable-frequency home appliances such as washing machines, air conditioners and refrigerators are commonly using brushless DC motors (BLDCs). These motors are popular in home appliances because of their high efficiency, low audible noise and stepless speed regulation.

There are still many low-power motors – such as drain pumps in washing machines and dishwashers or fans in air conditioners and refrigerators – that BLDC motors cannot replace completely because of driver design complexity and cost. Because the power of these motors is often less than 50W, developing a BLDC motor driver is too time-consuming even for experienced engineers, and extends time to market as well. TI helps you simplify driver designs by using a highly integrated BLDC motor driver single chip IC which has an embedded proprietary 180 degree sensorless control scheme inside the device. Low-voltage BLDC motors are more suitable for low-power applications instead of high-voltage ones, using a high-voltage solution for a low-power application is like a big horse pulling a small cart. Compared to high-voltage BLDC motors, a low-voltage motor for the pump in your appliance design has these advantages:

- **Compatibility.** An AC/DC switch power converter enables system operation over universal voltage input conditions (110/220V_{AC}) in different regions.
- **Safety.** The extra-low-voltage power supply simplifies insulation design for motors, eliminates the risk of insulation breakthrough of the driver board, reduces the risk of electrical shock and is especially suitable for high-humidity environments where drain pumps are located.
- **Reliability.** Protection features include overcurrent protection, lock detection, voltage surge protection, undervoltage lockout protection, thermal shutdown protection and auto restart. Lower switching and conduction losses make motors easier to control and more efficient.

- **Small form factor.** The driver board easily fits into the motor, saving printed circuit board (PCB) space. (See [Figure 1](#) & [Figure 2](#))
- **Better electromagnetic interference (EMI) performance.** The EMI feature enables customers to easily pass EMI testing requirements.
- **Cost savings.** Low-voltage DC link capacitors are cheaper than their high-voltage counterparts. Sensorless implementations simplify motor assembly; make startup more reliable; and reduce wiring harness, Hall effect sensor and related cable costs.

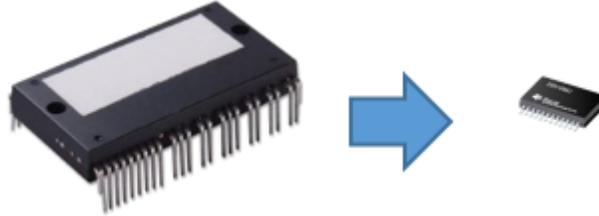


Figure 1. Variation of Driver in Form Factor

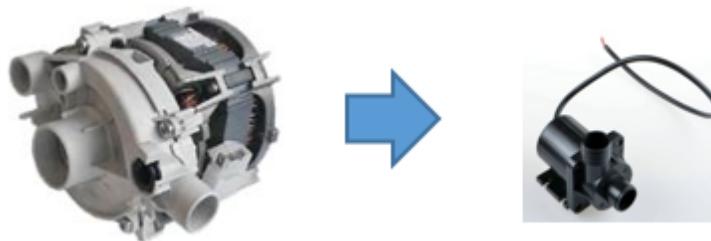


Figure 2. Variation of Motor in Form Factor

Overall, a motor with an integrated small-form-factor driver reduces design complexity, saves R&D time and accelerates time to market.

TI's [Integrated 30-W Sensorless BLDC Motor Drive Retrofit Reference Design with 90- to 265-V AC Input](#) uses low-voltage (24V) BLDC motor drivers instead of high-voltage (above 300V) motors. The reference design provides an optimized compact AC/DC flyback power supply and a highly integrated sinusoidal BLDC motor driver with full protection. [Figure 3](#) shows the system block diagram.

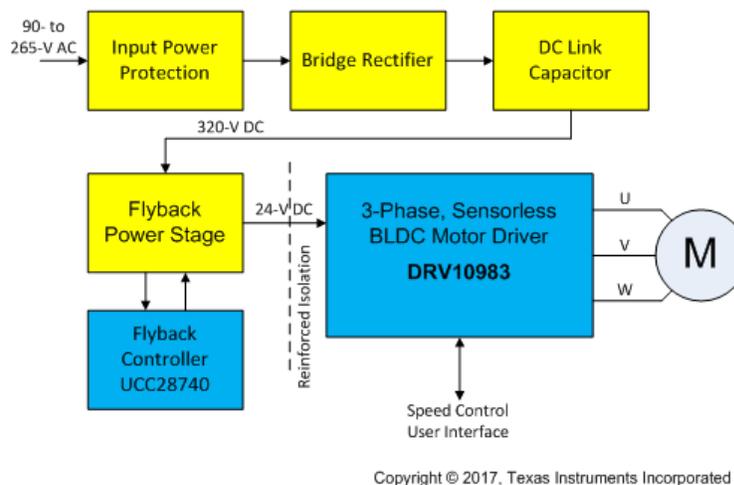


Figure 3. System Block Diagram

The reference design's very small form factor enables integration of the driver board inside the motor and provides a retrofitted solution. The AC/DC flyback power supply converts 90V to 265V, 50Hz or 60Hz AC inputs to a regulated 24V_{DC} output with reinforced isolation between the high and low side, with the UCC28740 serving as the AC/DC flyback controller. The designed power output is 36W maximum. The 24V_{DC} generated by the power supply powers the [DRV10983](#) three-phase, sensorless BLDC motor controller, which drives the motor and controls the motor speed. For appliance designs that require wider operating voltage support and enhanced protection features, a BLDC motor driver like DRV10987 can be used 24V systems for different power requirements. You don't have to be expert on BLDC technology to still develop a BLDC system perfectly. We have many easy-to-use motor drivers that integrate control logic, gate drive and FETs to help minimize the development time, save cost and cut PCB board space.

TI's proprietary sensorless control scheme to provide continuous sinusoidal drive. This integrated motor control significantly reduces the pure tone acoustics that typically occur as a result of commutation. [Figure 4](#) shows the driving waveform of DRV10983.

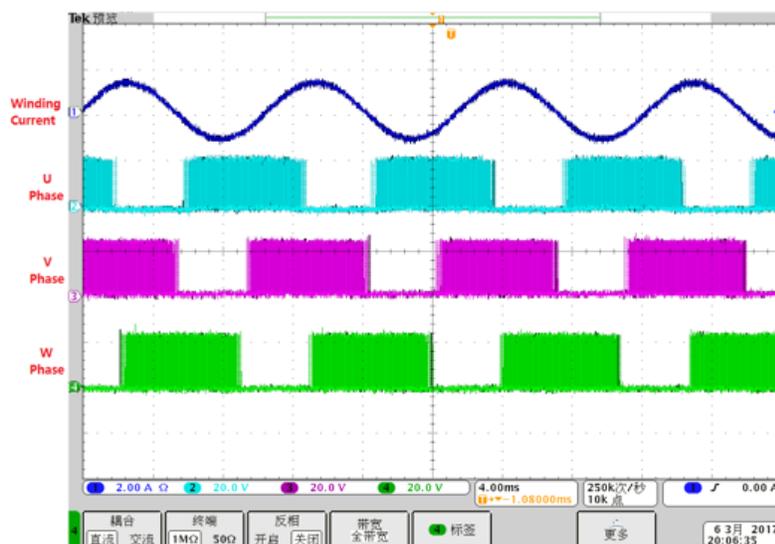


Figure 4. Driving Waveform

If you are concerned about the extra switch power cost, you just need to upgrade your previous switch power level from 5W or 10W to 35W; the cost increase is quite limited. The system-level cost is cheaper because smaller motor and driver ICs are cheaper than high-voltage solutions.

Additional Resources

- Find the best solutions for your [next-generation appliance designs](#).
- Watch a training video about [sensorless techniques](#) for driving three-phase brushless DC motors.
- Check out our blog series on the [integrated intelligence features](#) of TI's motor drivers.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated