

Overclocking the ADS1240 and ADS1241

Sean Chuang and Jason Bridgmon

ABSTRACT

The ADS1240 and ADS1241 are precision, wide dynamic range, delta-sigma ($\Delta\Sigma$) Analog-to-Digital Converters (ADCs) with 24-bit resolution. These devices are very competitively priced. Considering their low speed and low current consumption parameters, designers may find it advantageous to know that both devices are capable of running considerably faster while maintaining performance at the expense of current consumption.

Contents

| | |
|----------------------------------|----------|
| Theory of Operation | 2 |
| Overclocking Procedure | 2 |

List of Figures

| | |
|---|----------|
| Figure 1. Input Waveform to Change Current Consumption | 2 |
| Figure 2. Typical Integral Nonlinearity versus Current Consumption at Various Standard Clock Frequencies | 2 |
| Figure 3. Input Waveform to Reset Current Consumption | 3 |
| Figure 4. Analog Current Consumption vs Code at 2.4576MHz | 3 |
| Figure 5. Analog Current Consumption vs Code at 4.9152MHz | 3 |
| Figure 6. Analog Current Consumption vs Code at 10MHz | 4 |
| Figure 7. Analog Current Consumption vs Code at 18MHz | 4 |
| Figure 8. Digital Current Consumption vs Frequency | 4 |

Theory of Operation

In order to run the ADS1240 or ADS1241 converter at speeds above those specified in the product data sheet (SBAS173) while maintaining reasonable performance, extra bias current to the modulator is needed. This additional current can be obtained by adjusting a protected register value. To adjust the value, a special bit pattern must be written to the device and a pin toggled.

Overclocking Procedure

First, substitute the faster crystal, resonator, or oscillator on the board. Then configure the device for your application as usual (including channel selection, PGA setting, digital I/O lines, buffer on/off, etc). To unprotect the special register, raise pin 8 from DGND to DV_{DD}. This pin must be held at DV_{DD} for the modulator to obtain the extra current required; however, to change the configuration of the normal, unprotected registers of this device, this pin must be returned to DGND while WREG and RREG opcodes are issued.

While pin 8 is set to DV_{DD}, input the bit pattern shown in Figure 1. The xxxx placeholder stands for 4 *don't care* bits which may be any value. The nnnn placeholder is 00000 for a default setting, but the normal operating analog current usually corresponds to a higher code. Note that the code is considerably higher for higher PGA settings. As analog current increases, performance improvements can be observed. Figure 2 shows how INL improves with higher current at various master clock frequencies.

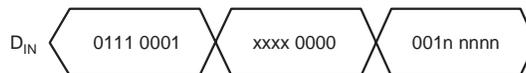


Figure 1. Input Waveform to Change Current Consumption

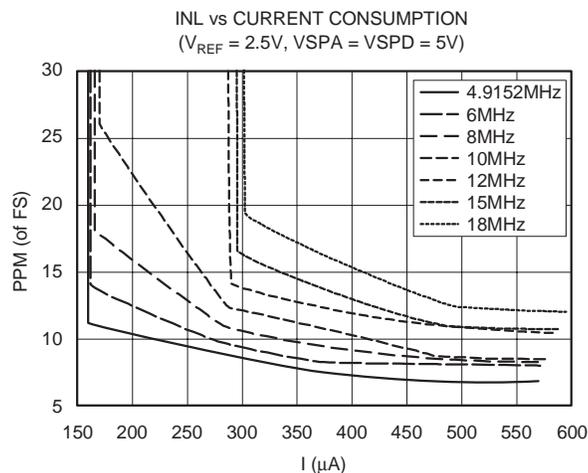


Figure 2. Typical Integral Nonlinearity versus Current Consumption at Various Standard Clock Frequencies

Once an appropriate value for *nnnn* is selected and input, the current will increase and remain at this higher level until one of the following conditions are met: the part is reset; a new value of *nnnn* is input; pin 8 is set back to DGND; or the bit pattern shown in Figure 3 is applied.



Figure 3. Input Waveform to Reset Current Consumption

Refer to Figure 4 through Figure 7 to select a clock frequency and appropriate code to program for increased current consumption. These figures show nominal current consumption at the selected frequency, and the results of changing the code in the protected register.

These graphs do not give an indication of performance at the selected code, only the current consumption. It is recommended to start with the lowest overclocking frequency that the application can support. It is also recommended to start with the highest code (for highest current consumption) that the application can support. This will give the best performance under the new conditions. If the performance at these settings is acceptable, try reducing the code or increasing the speed for additional time or current savings.

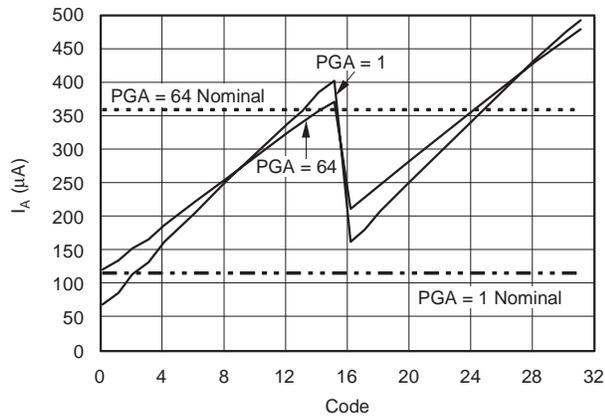


Figure 4. Analog Current Consumption vs Code at 2.4576MHz

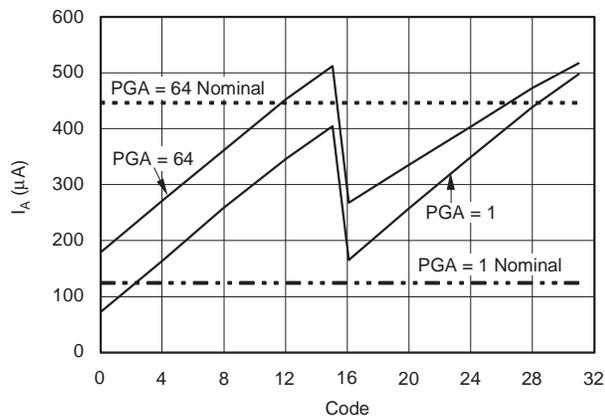


Figure 5. Analog Current Consumption vs Code at 4.9152MHz

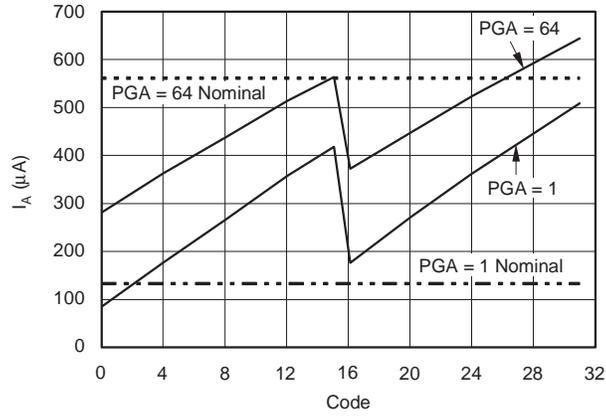


Figure 6. Analog Current Consumption vs Code at 10MHz

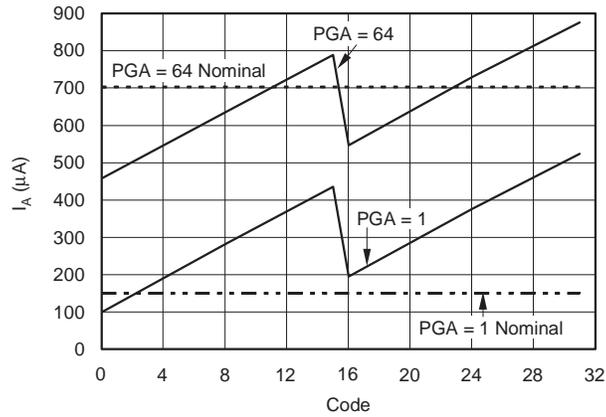


Figure 7. Analog Current Consumption vs Code at 18MHz

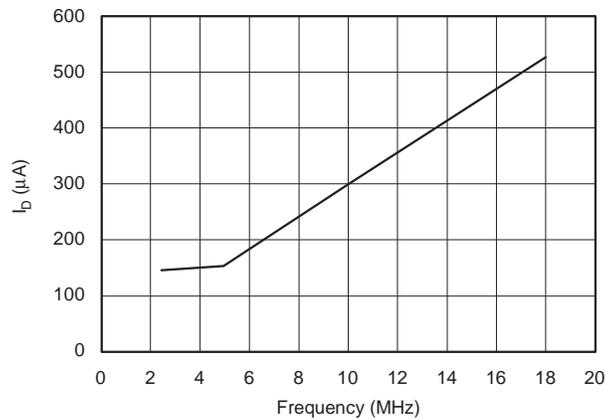


Figure 8. Digital Current Consumption vs Frequency

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| Products | | Applications | |
|------------------|--|---------------------|--|
| Amplifiers | amplifier.ti.com | Audio | www.ti.com/audio |
| Data Converters | dataconverter.ti.com | Automotive | www.ti.com/automotive |
| DSP | dsp.ti.com | Broadband | www.ti.com/broadband |
| Interface | interface.ti.com | Digital Control | www.ti.com/digitalcontrol |
| Logic | logic.ti.com | Military | www.ti.com/military |
| Power Mgmt | power.ti.com | Optical Networking | www.ti.com/opticalnetwork |
| Microcontrollers | microcontroller.ti.com | Security | www.ti.com/security |
| | | Telephony | www.ti.com/telephony |
| | | Video & Imaging | www.ti.com/video |
| | | Wireless | www.ti.com/wireless |

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2004, Texas Instruments Incorporated