

# ADC Wake and Transmit on Threshold Using MSP430™ MCUs



## Introduction

Many applications, such as battery monitors and thermostats, require sampling analog signals periodically so action can be taken based on the behavior of those signals. Analog-to-digital convertors (ADCs) can be triggered with precise timers to provide a solution to this requirement. This consumes a lot of microcontroller (MCU) resources and also causes higher power consumption as the timer needs to be active along with the ADC. Alternatively, many ADCs allow signals to be monitored continuously, but doing so can also require high power consumption. Operating the ADC integrated in the MCU independently of the CPU allows the CPU and all clocks other than the one being used by the ADC to be disabled to save power. The ADC also includes logic to determine conditions that require the CPU and the rest of the MCU to wake up. This is achieved by the ADC generating an interrupt to wake up the CPU when a configurable threshold is crossed. In addition, interrupts can be used to also send out ADC conversion data serially without having to power on the CPU.

This implementation uses UART to set the ADC threshold value, which when crossed will result in waking up the CPU, setting a GPIO and transmitting ADC data over the UART. It has been optimized for lowest code size, fitting in a low-cost 1KB MSP430FR2100 MCU, and for lowest power while still able to continuously monitor analog signals using the internal ADC. To get started, [download project files and a code example](#) demonstrating this functionality.

## Implementation

The solution uses the default auxiliary clock (ACLK) supply from the internal trimmed low-frequency oscillator (REFO), which operates at approximately 32 kHz, to operate the internal 10-bit SAR ADC, as well as the universal serial communication interface (eUSCI) UART peripheral and Timer\_B. Samples are taken continuously from P1.3 (A3), with each conversion taking place immediately after the preceding one has finished, with a periodicity of 2.7307 kHz. After configuring all necessary peripherals, the device goes into low-power mode 3 (LPM3). The ADC continually monitors the analog input to the MCU in this mode, while the CPU and all clocks other than ACLK are tuned off to reduce power

consumption. When the set voltage threshold is reached by the analog input to the ADC, P1.0 is set to indicate that the threshold has been reached, and a timer is started to send out the ADC conversion results over UART at a defined interval.

Figure 1 shows the block diagram for this implementation. The MSP-TS430PW20 target development board was used for connecting the peripherals to the MSP430FR2100 MCU. To set up the target board to run the demo, first ensure that jumpers JP14 and JP15 are populated (leave JP13 unpopulated), that jumper J16 is set to UART, and that jumpers JP11, JP17, and JP18 are all removed. These jumper settings will enable the back-channel UART interface on the MSP-FET programmer and debugger. For the MSPFR2100 MCU, make sure that the jumpers on JP11 are connected on 1-3 and 2-4.

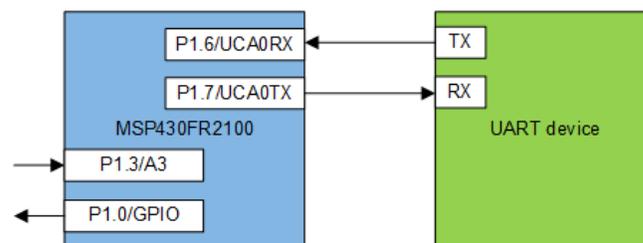


Figure 1. ADC Wake and Transmit on Threshold Block Diagram

A terminal program was used to provide a simple method for controlling the ADC threshold value and receiving the ADC conversion data. The eUSCI\_A0 peripheral was used in UART mode to enable commands to be received on P1.6/UCA0RXD and transmitted on P1.7/UCA0TXD. The MSP-FET was used for evaluation. A baud rate of 4800 must be selected with one stop bit and no parity. Two hexadecimal inputs must be sent to the MCU individually. The first specifies the high byte of the ADC threshold value, and the second specifies the low byte. The maximum value that can be represented by the ADC is 0x03FF, and the minimum is 0x0000. All ADC values are represented by unsigned 16-bit integers. The high threshold value is stored in FRAM, so it is retained on reset of the device. When the ADC threshold value is reached, ADC conversion values are sent over UART with a period that is set by default to 1 second. To change this, modify the value of the TB0CCR0 register, keeping in mind that the timer is using a clock of 32768 Hz. So, for example, a

TB0CCR0 value of 32768 results in a timer period of 1 second. Because the ADC produces a 10-bit unsigned integer, the data is sent over UART in two bytes, with the high byte first. This is illustrated in Figure 2. Two UART transmissions are shown. The red boxes show the high bytes, and the green boxes show the low bytes. These UART transmissions occurred after a threshold of 0x01FF was reached.

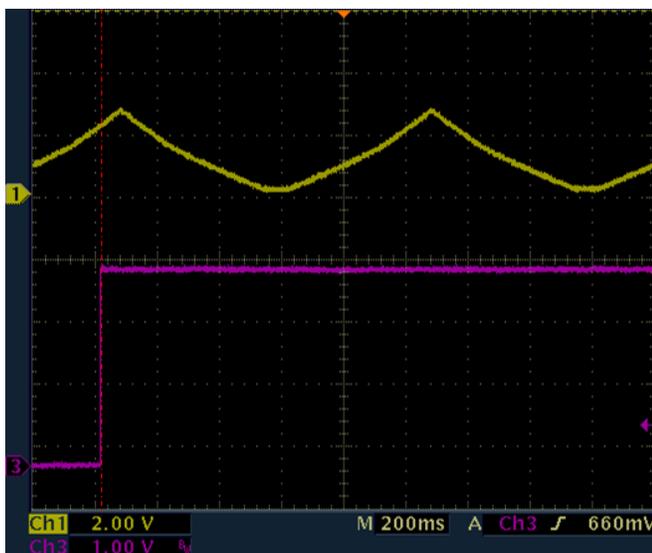


**Figure 2. Two Sample UART Transmissions**

### Performance

The operation of the demo can be run as described in the implementation section regarding the use of UART to control the threshold value and receive ADC conversion values. P1.3 (A3) is used for the analog input to the ADC, and a voltage can be applied to this pin to trigger the high threshold value of the ADC.

Figure 3 shows an oscilloscope shot that illustrates this. Channel 1 shows a triangular wave input to A3 on the MSP430FR2100 MCU, and channel 3 shows the output of P1.0 (GPIO). That GPIO gets set high when the triangular wave input hits a voltage equivalent to 0x01FF (the set threshold) for the ADC conversion value. This point is represented by the dashed red line.



**Figure 3. Oscilloscope View**

An important metric in measuring the performance of this implementation is power consumption. Power numbers were taken using the Keysight Technologies N6705B DC Power Analyzer. A 3 V supply was used, and the average current consumption of operating the ADC continuously in LPM3 was compared to that of operating in active mode (with the CPU and all clocks powered on). Table 1 lists the results.

**Table 1. Current Consumption in Active Mode and LPM3**

Power Mode	Average Current Consumption at 3 V (µA)
Active	97
LPM3	25

It can be seen that operating the ADC while in LPM3 and waiting for an interrupt from the ADC reduces the power consumption significantly. Another low power alternative would be to put the device into low-power mode 3.5 (LPM3.5), which also shuts down ACLK, and use the real time clock (RTC) to wake up the CPU and ADC at specified intervals to take a sample, and then go back to LPM3.5. This would require relatively large wakeup intervals in order to get the power as low as it is in the LPM3 implementation, which would not be ideal for applications that need high sampling rates.

### Device Recommendations

The device used in this example is part of the MSP430 Value Line Sensing portfolio of low-cost MCUs, designed for sensing and measurement applications. This example can be used with the devices shown in Table 2 with minimal code changes. For more information on the entire Value Line Sensing MCU portfolio, visit [www.ti.com/MSP430ValueLine](http://www.ti.com/MSP430ValueLine).

**Table 2. Device Recommendations**

Part Number	Key Features
MSP430FR2000	0.5KB FRAM, 0.5KB RAM, eComp
MSP430FR2100	1KB FRAM, 0.5KB RAM, 10-bit ADC, eComp
MSP430FR2110	2KB FRAM, 1KB RAM, 10-bit ADC, eComp
MSP430FR2111	3.75KB FRAM, 1KB RAM, 10-bit ADC, eComp

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated