

Simplifying Pulse Oximeter Designs With Low-Cost Highly Integrated MSPM0 MCUs



Introduction

Pulse oximeters are medical instruments for monitoring blood oxygenation. The oxygen level and heart rate measured by the instrument is critical to monitoring patient health and helping medical professionals detect and diagnose medical conditions. Low-cost MSPM0 microcontrollers (MCUs) can help engineers optimize the design and performance of pulse oximeters with MSPM0 Arm® Cortex®-M0+ MCUs like high-performance MSPM0G15xx devices or low-cost MSPM0Lxx devices.

Theory of operation

A pulse oximeter is a noninvasive device that monitors the pulse rate and peripheral oxygen saturation (SpO₂ %) of blood.

As [Figure 1](#) shows, when red and IR light emitting diodes (LEDs) are driven alternately through a finger, the unabsorbed light received at the other end of the finger (where a photodiode is used as the sensing element) corresponds to the concentration of Hb and HbO₂ in the blood.


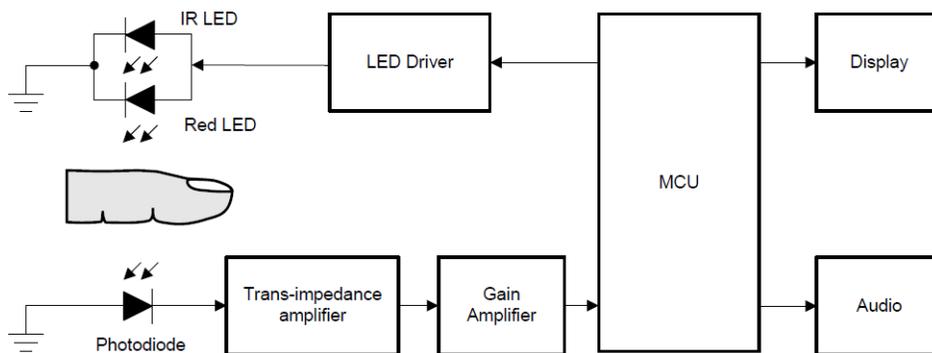


Figure 1. Block Diagram of Pulse Oximeter

These measurements include both DC and AC components. The application treats the DC component as the result of absorption by the body tissue and veins and the AC component as the result of absorption by the arteries.

Why are MSPM0 MCUs suitable for pulse oximeter designs?

MCUs in TI's **scalable** MSPM0 MCU portfolio feature a M0+ core, with a maximum CPU speed of 32 or 80 MHz. This pin-to-pin compatible portfolio provides memory options from 4KB to 512KB of flash memory with scalable analog integration. With extended analog and interface integration, the MSPM0 portfolio provides **low power**, **high performance**, **low cost**, and **reliable** options for pulse oximeter designs.

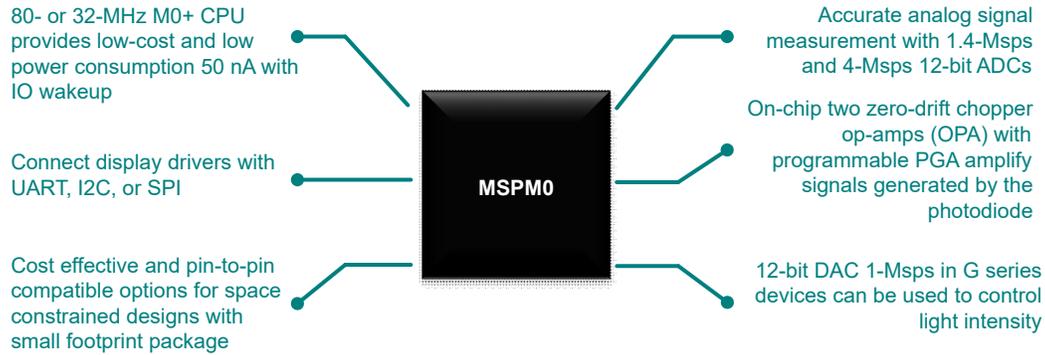

MSPM0 design for pulse oximeter

Figure 2 shows a proposed block diagram of an MSPM0G15xx-based pulse oximeter design. The two on-chip zero-drift chopper op-amps (OPA) amplify signals generated by the photodiode. The 8-bit DAC is used as an adjustable bias for the two OPAs. The IR LED and red LED are controlled by the DAC12 to provide different light intensities for different test conditions when taking a reading. An internal timer can be used to trigger the ADC and update the output value of DAC12.

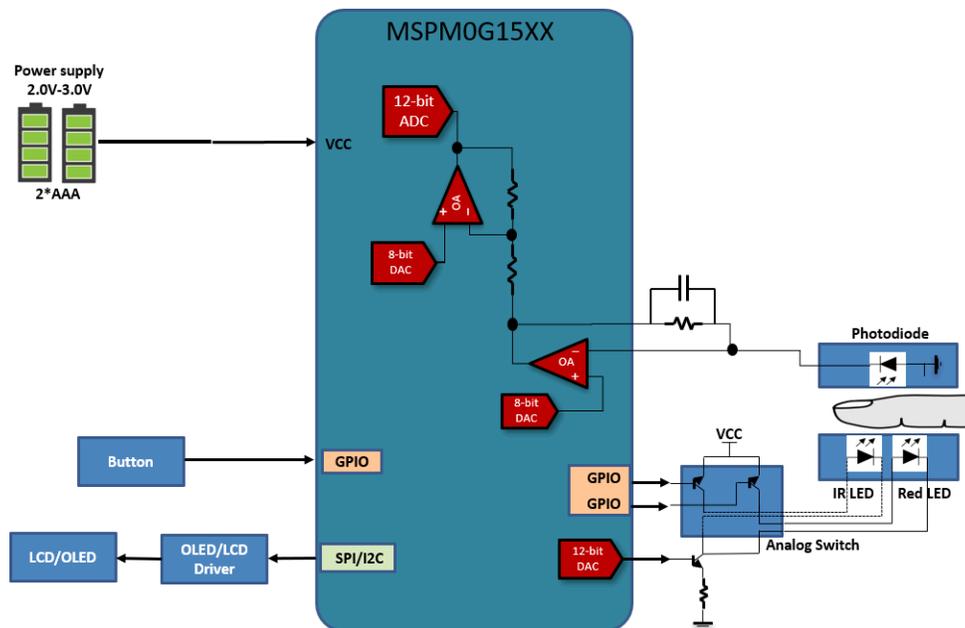


Figure 2. MSPM0G15xx Block Diagram for Pulse Oximeter

Key feature requirements for MCUs in these applications:

- Two on-chip zero-drift chopper op-amps (OPA)
- Internally used 8-bit DAC
- 12-bit DAC
- SPI, I2C, and UART

Software functions on MSPM0:

- IR and red LED control by DAC12 and GPIO
- Bias adjustment for OPAs
- ADC12 sample control
- Sample data process
- Display result on LCD or OLED

Two options are described below for using MSPM0L series devices in a pulse oximeter design. Figure 3 shows one proposed block diagram of a MSPM0L series application. For this application, two op-amps (OPA) control

the LED intensity. The single 8-bit DAC is shared by the two op-amps, so the DAC must be set to different values depending on the currently selected LED. Finally, the light sensor uses a light-to-frequency converter to generate a frequency signal captured by a timer.

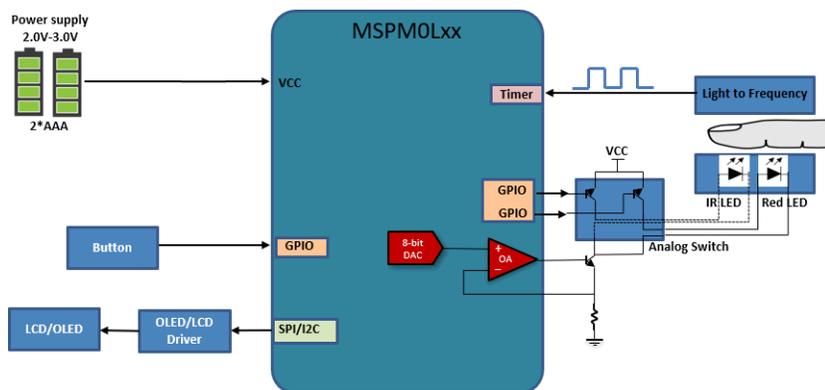


Figure 3. Option 1: MSPM0L Series Block Diagram for Pulse Oximeter

Key feature requirements for MCU in these applications:

- On-chip zero-drift chopper op-amps (OPA)
- Internally used 8-bit DAC
- Timer capture
- SPI, I2C, or UART

Software functions on MSPM0:

- IR and Red LED control by OA and GPIO
- Timer capture of the frequency
- Data process
- Display results on an LCD or OLED

Figure 4 shows the other proposed block diagram of a MSPM0L series application. The two on-chip zero-drift chopper op-amps (OPA) amplify the signals generated by the photodiode. The 8-bit DAC is used as an adjustable bias for the second OPA. The first stage OPA uses an external fixed bias. The IR LED and red LED are controlled directly by GPIOs. To ensure the LED intensity remains consistent even as battery voltage changes over the lifetime of the product, a boost converter is needed.

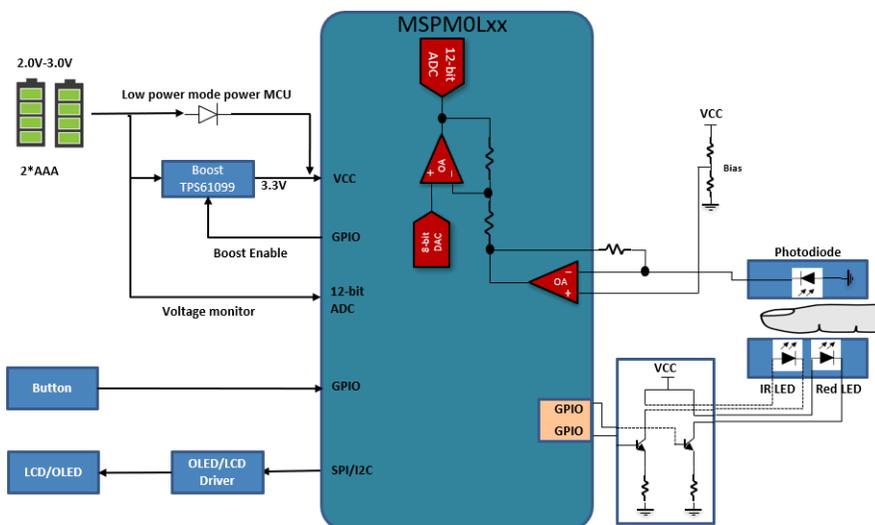


Figure 4. Option 2: MSPM0L Series Block Diagram for Pulse Oximeter

Key feature requirements for MCUs in these applications:

- Two on-chip zero-drift chopper op-amps (OPA)
- Internally used 8-bit DAC
- SPI, I2C, or UART

Software functions on MSPM0:

- IR and red LEDs controlled by GPIO
- Bias adjust for second stage OPA
- ADC12 sample control
- Sample data process
- Display results on an LCD or OLED

Resources

Order an [MSPM0 LaunchPad development kit](#) today to start evaluating MSPM0 for your pulse oximeter. Jump start your pulse oximeter design with MSPM0 code examples and interactive online trainings. The following additional resources are available.

- [MSPM0 Academy](#)
- [MSPM0 landing page](#)
- [Single-Chip Pulse Oximeter Designs Based on MSP430FR2355 application note](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated