Industrial Communications Solutions featuring MSP Microcontrollers





www.ti.com/msp 2015

Overview

Monitoring and maintaining process variables at the appropriate levels is extremely critical in industrial automation and process control. Another important aspect to complete the feedback loop is industrial communications. The vast majority of industrial applications rely on wired solutions that can either be powered through the communication loop or through a separate power line. The basic signal chain of an industrial system is shown in Figure 1.

MSP microcontrollers have a broad portfolio of products catering to industrial sensing, that meet the highest standards and that are optimized for industrial environments and extend product life cycles. These microcontrollers not only provide an ultra-low power advantage, but also have various communication interfaces that are needed for wired communications.

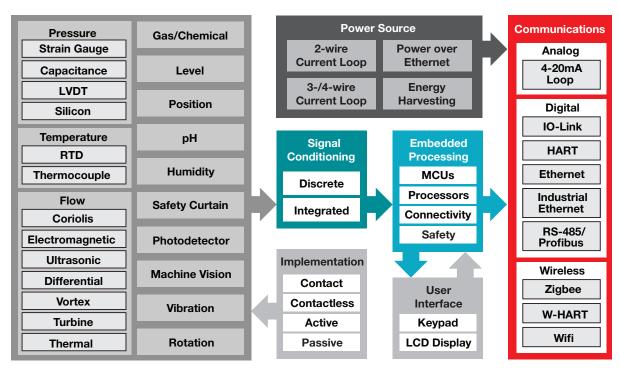


Figure 1. Industrial system signal chain

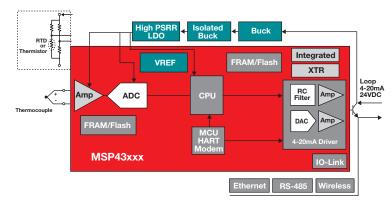


Figure 2: Industrial transmitter = Sensing + Control + Data logging + Communication

Application Problem

How MSP Enables

Application Energy Budget Industrial 4-20mA wired loop solutions maintain a maximum current budget of 3.5mA. The low power performance of the MSP430 provides a larger margin for sensor solutions.

Complete Solutions

TI offers complete 4-20mA, IO-Link and HART solutions. TI DESIGNS Available.

System Cost MSP430 Single chip solutions based on smart integrated analog (OPA/DAC/ADC) provide the lowest system cost.

Future Development Provide a scalable portfolio for customers to leverage hardware and software investments in future projects.

Industrial communication can be broken down into the following:

- 4-20mA wired loop
 - Single chip solution
 - Multi-chip 4-20mA solution
- I/O Link
- HART® Protocol
 - HART modem (PHY)
 - HART field transmitter

4-20mA Wired Loop Communication

The transmitter can either be powered through the communication loop via a 2-wire implementation or through a separate power line not associated directly with the 4-20mA current loop, typically classified as a 3-wire or 4-wire solution. In both cases, a low-dropout (LDO) regulator steps down the current loop supply voltage to power the transmitter. In the 2-wire solution,

it is important to maintain a current threshold below the 3.5mA in order to ensure the minimum transmitted measurement value of 4mA is achieved with margin for alarm low levels. The low active current capability of the MSP microcontroller provides for very low transmitter currents and enables a larger power budget for multiple sensors on a single field transmitter.

Single-chip MSP System Solution

The integrated smart analog on the MSP product family of devices provides for a single-chip solution. The onboard operational amplifier can be configured to carry out signal conditioning of the sensor signal and drive the 4-20mA communication loop. The integrated ADC is used to digitize the sensor signal and processed by the microcontroller while the pulse width modulator (PWM) is used to modulate the current in the 4-20mA loop. This single-chip solution drives the most cost effective system solution.

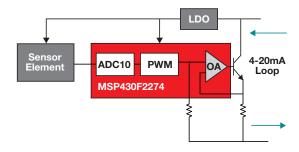


Figure 3. Single chip MSP430F2274 system solution

Device	MCU Speed (MHZ)	Non-Volatile Memory (kbytes)	SRAM (kbytes)	GPIO Pins	GAIN	THD (db)	Offset (mV)	Setting Time (µs)
MSP430FG4619	8	120	8	80	1	-70	-10	7
MSP430FG479	8	60	2	48	_	_	-10	_
MSP430F2274	16	32	1	32	1	-70	-10	7

Get more information: www.ti.com/tool/TIDA-00247

Multi-chip Solution

In this implementation, the MSP microcontroller manages all of the system requirements for the field transmitter solution - from managing the sensor output signal to handling

the protocol requirements for the wired communication loop. This multi-chip solution provides for the highest possible resolution.


ADC									ıts and Out			
MSP™ MCU Family	Slope	10-Bit SAR	12-Bit SAR	16-Bit Sigma Delta	24-Bit Sigma Delta	DAC	Comp	Temp Sensor	1.8V	5V	CapTouch	Voltage Monitoring
F1xx	~	~	~				~	~				~
F2xx	~	V	V	V	~	~	V	~				✓
G2xx/i2xx	~	~			~		~	~			~	~
F4xx	~	V	V	V	~	~	V	~				✓
F5xx	~	~	~			~	~	~	~	~		~
F6xx	V	~	V		V	V	V	~				✓
FR5xx	~	~					~	~			~	~

Get more information: www.ti.com/tool/TIDA-00165

IO-Link PROTOCOL

The other communication protocol for industrial applications is the IO-Link. IO-Link is known as the USB of Factory Automation since it is a simple & cheap point to point protocol that can be broken down into master and slaves. The masters can have multiple ports and on each port only

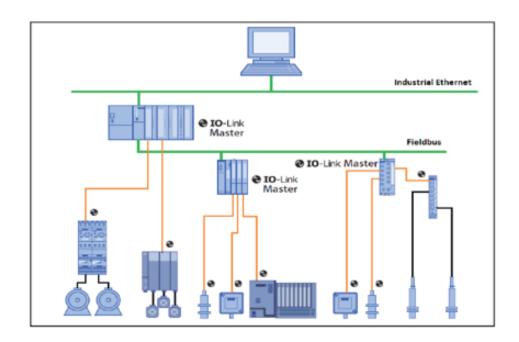one device is connected. The IO-LINK devices can be: sensors, RFID readers, valve, motors. The IO-LINK reuses the cables and connectors from installed base of industrial sensors & actuators that reduces cost for this option of communication.



ADC								Inpu	ıts and Out			
MSP™ MCU Family	Slope	10-Bit SAR	12-Bit SAR	16-Bit Sigma Delta	24-Bit Sigma Delta	DAC	Comp	Temp Sensor	1.8V	5V	CapTouch	Voltage Monitoring
FR5xx	~	~	~	~	~	~	~	~	~	~	~	~

Get more information: www.ti.com/tool/TIDA-00188

HART® Protocol

The HART communications protocol is a digital industrial automation protocol. It's most notable advantage is that it can communicate over legacy 4-20 mA analog instrumentation wiring. Thus, the HART Protocol is one of the most popular industrial protocols today since it has made a good transition protocol for users who were comfortable using the legacy 4-20 mA signals, but wanted to implement a

"smart" protocol. HART uses low frequencies (1200Hz and 2200Hz representing 1 and 0). The single-chip implementation integrates handling of the protocol and providing PHY layer support. Figure 5 shows a typical implementation where the PHY layer (or Modem) is provided by a separate chip. Figure 6 shows the HART protocol and PHY layer running on a single MSP device.

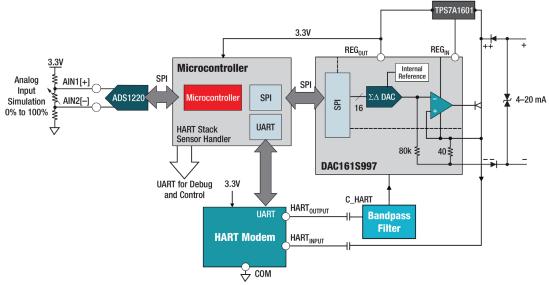


Figure 5. Typical HART field transmitter design with standalone modem.

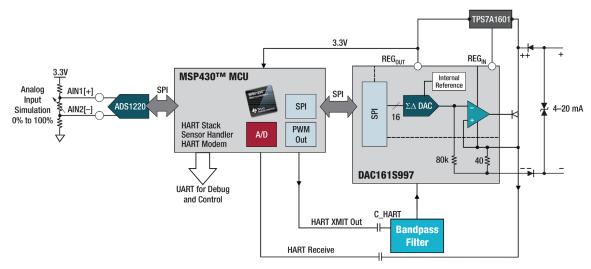


Figure 6. HART protocol and Modem running on a single chip MSP solution.

				Inputs and Outputs								
MSP™ MCU Family	Slope	10-Bit SAR	12-Bit SAR	16-Bit Sigma Delta	24-Bit SigmaDelta	DAC	Comp	Temp Sensor	1.8V	5V	CapTouch	Voltage Monitoring
F5xx	V	~	~			~	~	~	~	~		~
FR5xx	V	V					v	v			v	v

TIDesignsNow more

powerful

Industry's largest reference design library

• Over 1,000 power management reference desgins

• Enhanced search tool: Parameters, topologies. keyword, application, or product

· Direct access to fully tested analog, embedded processor, and connectivity reference designs

This robust tool offers complete solutions across the baord.



TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas Phone +1(512) 434-1560 Brazil Phone 0800-891-2616 Mexico Phone 0800-670-7544

> Fax +1(972) 927-6377

Internet/Email support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

European Free Call 00800-ASK-TEXAS

(00800 275 83927)

International +49 (0) 8161 80 2121 Russian Support +7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the

international number above

Fax +(49) (0) 8161 80 2045 Internet www.ti.com/asktexas asktexas@ti.com Direct Email

Japan

Fax International +81-3-3344-5317

0120-81-0036 Domestic

Internet/Email International support.ti.com/sc/pic/japan.htm

Domestic www.tij.co.jp/pic

Asia

Phone Toll-Free Number Note: Toll-free numbers may not support

mobile and IP phones

1-800-999-084 Australia China 800-820-8682 800-96-5941 Hong Kong India 000-800-100-8888 Indonesia 001-803-8861-1006 080-551-2804 Korea Malaysia 1-800-80-3973 0800-446-934 New Zealand Philippines 1-800-765-7404 800-886-1028 Singapore 0800-006800 Taiwan Thailand 001-800-886-0010

+86-21-23073444 International +86-21-23073686

Email tiasia@ti.com or ti-china@ti.com Internet support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. IT assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute Ti's approval, warranty or endorsement thereof.

The platform bar is a trademark of Texas Instruments

All other trademarks are the property of their respective owners.



B021014

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2024, Texas Instruments Incorporated