

# **Management of the TRF7960, -60A Startup Sequence**

---

*Josh Wyatt, Kostas Aslanidis*

## **ABSTRACT**

System developers concerned about minimizing the current draw of TRF7960, -60A (and their variants) systems at startup time need guidance about handling the Regulator Control register (0x0B) value. Guidance is necessary due to the conditions under which the TRF796x/-6xA starts up with the automatic (default) setting of this register, after the EN line (pin 28) is asserted from the controlling MCU in the system. Valid application use case for utilizing this guidance would be battery-powered RFID application where controlling the entire system current draw over time is of the utmost concern. The scope of this application report is limited to providing direction to the embedded developer for the specific handling of the condition at startup.

---

## **Contents**

1	Automatic Regulator Register (0x0B) Setting .....	2
2	Manual Regulator Register (0x0B) Setting .....	3
3	TRF79xx Startup Sequence Flow .....	4
4	C Code Change Example .....	5
5	References .....	7

## **List of Figures**

1	TX Out Behavior When EN is Line Raised (Register 0x0B left at default) .....	2
2	TX Out Behavior When EN is Line Raised (Register 0x0B set to 0x07) .....	3
3	Startup Sequence Flow .....	4

## 1 Automatic Regulator Register (0x0B) Setting

### Register 0x0B = 0x87 (automatic, default)

When the Register 0x0B is left at default setting at the time the EN line is asserted (pin 28), the output of the transmitter can be observed turning on for a period of time before the crystal oscillator starts up.

This observed activity is the automatic regulator adjustment module performing its task after power-up as its function is to switch on all the current consumption modules inside the TRF79xx (including the TX output) and perform a regulator adjustment for best noise performance.

Once the adjustment is complete, all the current consuming modules (including the transmitter) are switched off. For an actual example of this burst of TX activity while the automatic adjustment is being performed, see [Figure 1](#).

Yellow trace is EN line, blue trace is 13.56 MHz clock, pink trace is TX.

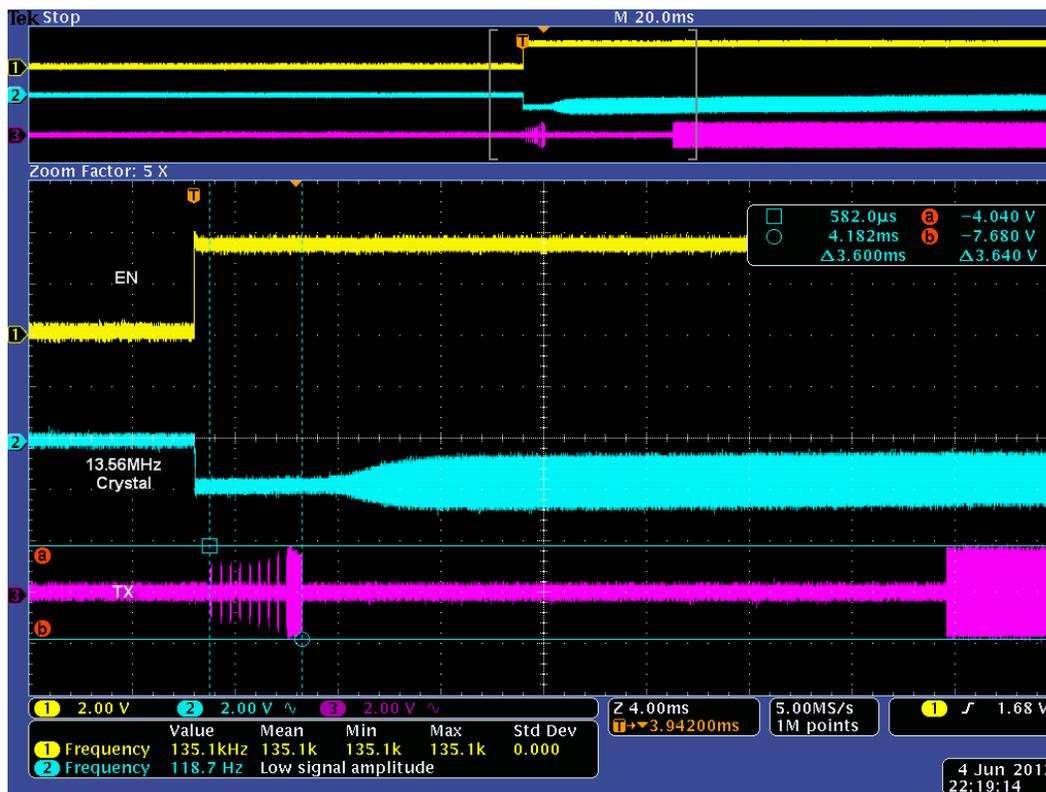


Figure 1. TX Out Behavior When EN is Line Raised (Register 0x0B left at default)

## 2 Manual Regulator Register (0x0B) Setting

### Register 0x0B = 0x0x (manual setting)

For system designers and developers who do not want this TX activity to occur directly after raising the EN line, the behavior of the TX out can be changed if the Regulator Register (0x0B) is written to with a value other than B7=1 in the time between the power-up and the time the crystal oscillator is stable. This is a simple code change, which is described in [Section 4](#).

For an example of this behavior, with the change (described above) made to the MCU firmware, see [Figure 2](#).

Yellow trace is EN line, blue trace is 13.56 MHz clock, pink trace is TX out.


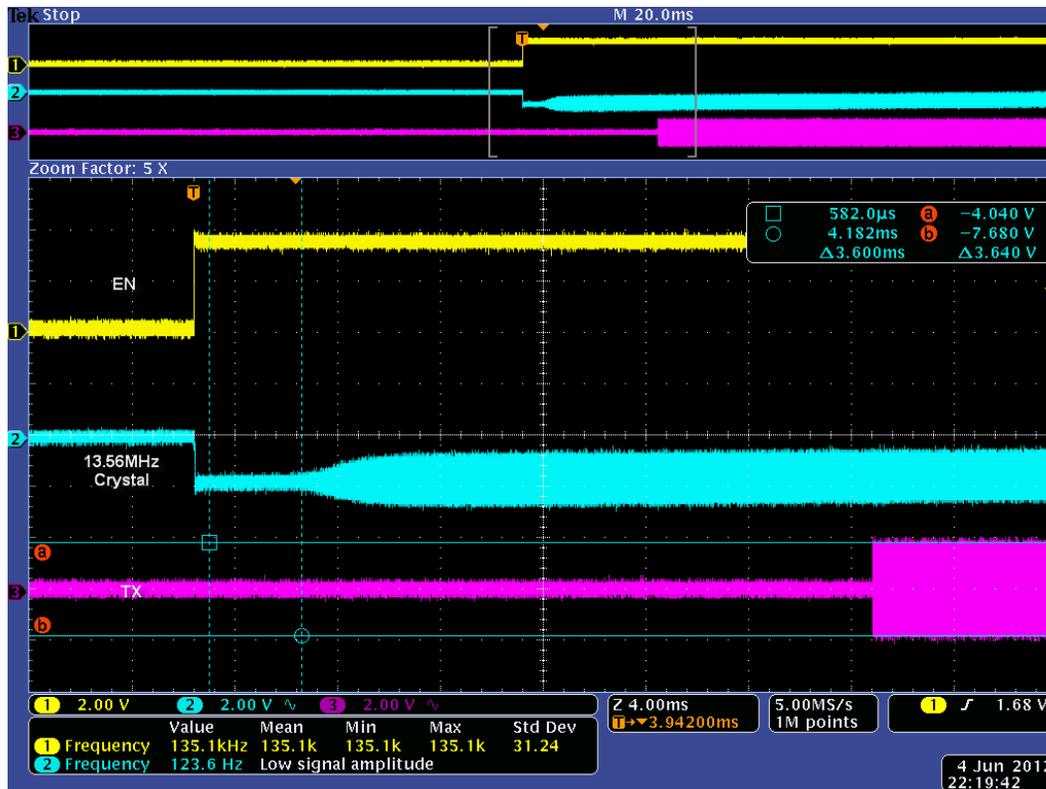


Figure 2. TX Out Behavior When EN is Line Raised (Register 0x0B set to 0x07)

Note that the burst of TX activity is removed. The TX on after that is normal as Register 0x00 has been written to with a value of 0x21 (for example, to turn the transmitter on) prior to starting RFID operations.

### 3 TRF79xx Startup Sequence Flow

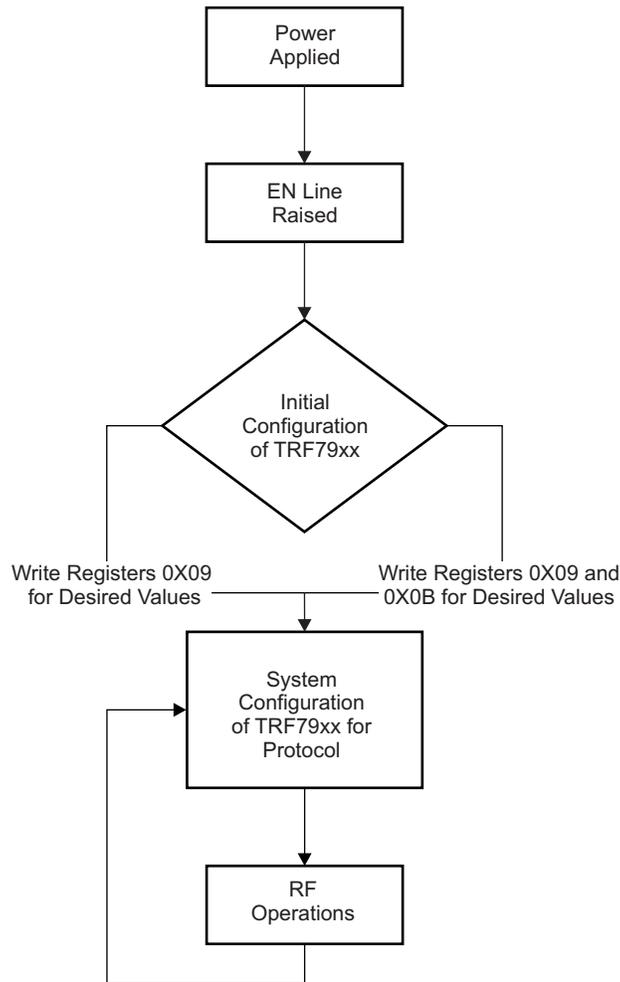

**Figure 3. Startup Sequence Flow**

## 4 C Code Change Example

The following code examples show where the InitialSettings function call resides in the firmware and how to implement the write to Register 0x0B in that function.

```

void main(void) //code snippet from top of main.c function
{
    // initialize peripherals
    WDTCTL = WDTPW + WDTHOLD;           // Stop WDT

    UARTset();

    //sets MCU Port Pin for TRF79xx EN line (pin 28 on TRF) direction to OUT (#define in hardware.h)
    EnableSet;
    TRFDisable; //sets MCU Port Pin for EN (pin 28 on TRF) to low (#define in hardware.h)
    delay_ms(1);
    TRFEnable; //sets MCU Port Pin for EN (pin 28 on TRF) to high (#define in hardware.h)

    //Add logic for SPI/parallel selection.
    if (SPIMODE)
    { //Set Port Functions for Serial Mode
        EnableSet;
        irqPINset;
        irqEDGEset;                       /* rising edge interrupt */

        LEDalloFF;
        LEDportSET;
        TRFDirOUT;
    }
    else
        PARset(); //Set Port Functions for Parallel Mode

    /* Use the DCO to program the SPI first*/
    if (SPIMODE)
    {
        #ifndef SPI_BITBANG
            USARTset(); //Set the USART */
        #else
            SlaveSelectPortSet // P3.0 - Slave Select
            SlaveSelectHIGH // Slave Select - inactive ( high)
            SIMOSet
            clkPOUTset;
        #endif
    }

    InitialSettings(); // Write Register 0x09 and 0x0B(if desired)
}

```

Where InitialSettings example function is:

```
void InitialSettings(void)
{
    /*~~~~~*/
    unsigned char  command[2];
    /*~~~~~*/

    command[0] = ModulatorControl; //Register 0x09
    command[1] = 0x21; //6.78 MHz SYS_CLK OUT
    WriteSingle(command, 2);

    command[0] = RegulatorControl; //Register 0x0B
    command[1] = 0x07; //manual setting example, to eliminate TX spike at startup
    WriteSingle(command, 2);
}
```

## 5 References

- *TRF7960, TRF7961 Multi-Standard Fully Integrated 13.56 MHz RFID Analog Front End and Data-Framing Reader System Data Manual* ([SLOU186](#))
- *TRF7960 Firmware Source Code* ([SLOC136](#))
- *TRF7960A Multi-Protocol Fully Integrated 13.56 MHz RFID Reader/Writer IC Data Manual* ([SLOS732](#))
- *TRF7960A C Code Samples* ([SLOC251](#))

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2012, Texas Instruments Incorporated