

Differences Between the TPS54340/360/540/560 and TPS54340B/360B/540B/560B for Q1 and Non-Q1 Devices

1 Trademarks

PowerPAD is a trademark of Texas Instruments.
All other trademarks are the property of their respective owners.

2 Introduction

This document highlights the improvements made to the TPS54340, TPS54360, TPS54540, and TPS54560 in their B versions. The TPS54340B, TPS54360B, TPS54540B, and TPS54560B from Texas Instruments are pin-to-pin drop in upgrade to the existing TPS54340, TPS54360, TPS54540, and TPS54560 buck converter family. The TPS54340B, TPS54360B, TPS54540B, and TPS54560B are available in an eight-terminal, thermally-enhanced HSOIC PowerPAD™ package, like the current generation TPS54340, TPS54360, TPS54540, and TPS54560.

As TI continues to innovate and improve its manufacturability and processes, the TPS54340B, TPS54360B, TPS54540B, and TPS54560B offer higher reliability and performance. Hence, TI recommends the TPS54340B, TPS54360B, TPS54540B, and TPS54560B for new designs to our customers in the industrial, automotive, and communications markets. TI also recommends to update the status of TPS54340, TPS54360, TPS54540, and TPS54560 to NRND (Not Recommended for New Designs). The status of the TPS54340, TPS54360, TPS54540, and TPS54560 will not be changed to EOL (End Of Life).

3 Differences - TPS54340 and TPS54340B (Q1 and Non-Q1)

The following are the differences between the TPS54340 and TPS54340B:

- Addition of Poly-Imide (PI) coat on the top layer of the IC

4 Differences - TPS54360 and TPS54360B (Q1 and Non-Q1)

The following are the differences between the TPS54360 and TPS54360B:

- Addition of Poly-Imide (PI) coat on the top layer of the IC

5 Differences - TPS54540 and TPS54540B (Q1 and Non-Q1)

The following are the differences between the TPS54540 and TPS54540B:

- Addition of Poly-Imide (PI) coat on top layer of the IC
- Increased reliability: Improved output OVP (overvoltage) circuit for high load transients (5 A to 0 A) at greater than 800 kHz switching frequency
- Increased current limit: 7.5 A to 7.9 A (typical), 8.8 A to 9.5 A (maximum)

6 Differences - TPS54560 and TPS54560B (Q1 and non-Q1)

The following are the differences between the TPS54560 and TPS54560B:

- Addition of Poly-Imide (PI) coat on the top layer of the IC
- Increased reliability: Improved output OVP (overvoltage) circuit for high load transients (5 A to 0 A) at greater than 800 kHz switching frequency
- Increased current limit: 7.5 A to 7.9 A (typical), 8.8 A to 9.5 A (maximum)

7 References

- Texas Instruments, [TPS54340B 42-V Input, 3.5-A, Step-Down DC/DC Converter With Eco-Mode™ Data Sheet](#)
- Texas Instruments, [TPS54360B 60-V Input, 3.5-A, Step-Down DC/DC Converter With Eco-Mode™ Data Sheet](#)
- Texas Instruments, [TPS54540B 4.5-V to 42-V Input, 5-A step-down dc/dc converter with Eco-mode™ Data Sheet](#)
- Texas Instruments, [TPS54560B 4.5-V to 60-V Input, 5-A step-down dc/dc converter with Eco-mode™ Data Sheet](#)
- Texas Instruments, [TPS54340B-Q1 4.5-V to 42-V Input, 3.5-A, Step-Down DC-DC Converter With Eco-Mode™ Data Sheet](#)
- Texas Instruments, [TPS54360B-Q1 60 V Input, 3.5 A, Step Down DC-DC Converter with Eco-mode™ Data Sheet](#)
- Texas Instruments, [TPS54540B-Q1 4.5-V to 42-V Input, 5-A, Step-Down DC-DC Converter With Eco-mode™ Data Sheet](#)
- Texas Instruments, [TPS54560B-Q1 4.5 V to 60 V Input, 5 A, Step Down DC-DC Converter with Eco-mode™ Data Sheet](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated