

How Switching Above the AM Band Eases Automotive Class-D Amplifier EMC Designs



Gregg Burke

As I recall riding in my dad's 1957 Chevy, every time he would change the radio to a new station in the AM band, I could hear a lot of static. This loud buzzing sound represents noise from the car's alternator or ignition system, which either gets transferred into the power supply of the radio or interferes with the radio's antenna. The noise naturally interferes with the AM broadcast radio signal, which can be heard by the occupants of the vehicle. This is a simple example of electromagnetic interference (EMI).

Back then, audio designs were not sophisticated enough to adequately avoid this interference. Today, car manufacturers are designing vehicles with more and more electronics mounted behind the dashboard in a relatively tight space. This increases the possibility that these electronic circuits can emit interfering signals in close proximity to each other. Ultimately, modern radios and audio amplifiers must provide better immunity from EMI in the AM band to meet these challenges.

In the U.S., AM radio stations broadcast in the 535 kHz to 1705 kHz frequency band. Existing Class-D audio amplifier designs typically operate with a fundamental switching frequency in the 400-500 kHz range. These Class-D amplifier designs create harmonics that lay directly within the AM band, as shown in [Figure 1](#) below.

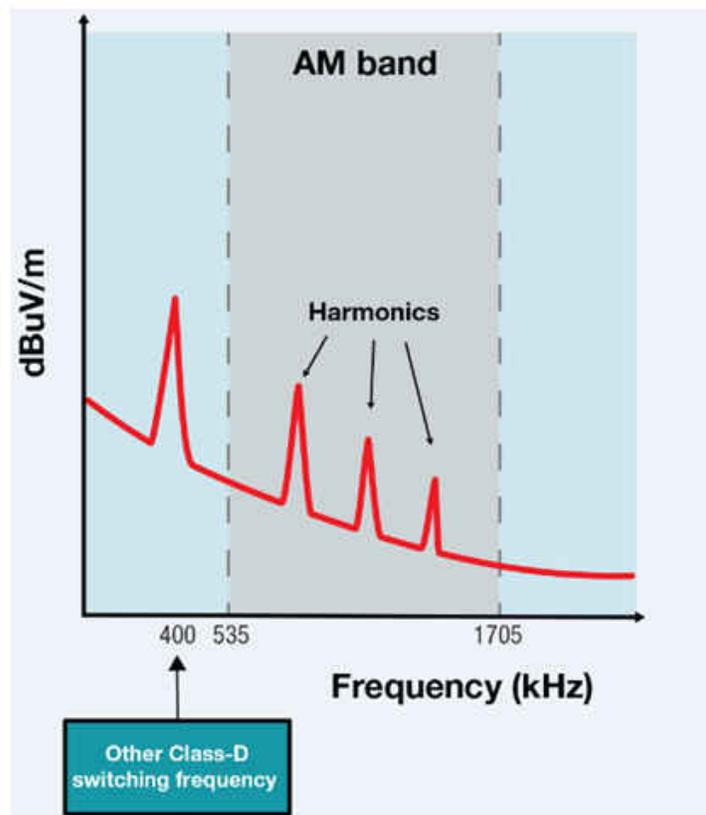


Figure 1. Typical Class-D Amplifier Harmonics

The harmonics create interfering signals that reduce the sensitivity of the AM receiver, thereby hindering the AM radio station's reception. Some type of EMI avoidance scheme must be implemented on these Class-D amplifier designs to mitigate the effects of these harmonics.

Class-D audio amplifiers need output filters to help maintain a high efficiency. These output filters are made with inductors and capacitors that minimize EMI from the high speed switching transients on the output stages of Class-D amplifiers. The copper-trace lengths on the printed circuit board (PCB) from the amplifier output pins to these output filters create current loops that can act as antennas to also transmit unwanted EMI.

So as car manufacturers add more and more electronics (which increases the possibility of unwanted EMI), infotainment designs need to either implement complex AM avoidance schemes or look for new amplifier designs that address these issues in an innovative manner.

The TAS6424-Q1 is the industry's first automotive Class-D audio amplifier that operates at 2.1 MHz, providing significant margin above the AM band, as shown in Figure 2 below. This design is also free of any lower-frequency spikes that would interfere in the AM band.

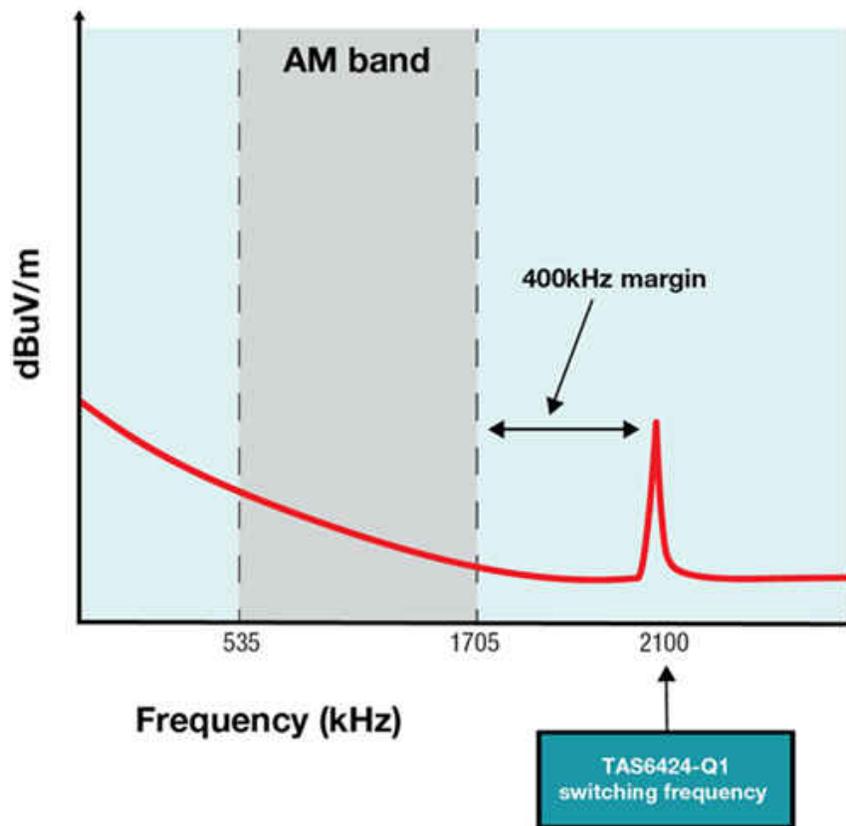


Figure 2. TAS6424-Q1 Switching Frequency

A 2.1 MHz switching frequency enables a lower inductance value for the output filter. Since the size of the inductor used in the output filter can be smaller for an equivalent current rating, there is less likelihood of creating additional disruptive current loops. Figure 3 shows the relative size advantage of the 3.3 μH inductors used for the TAS6424-Q1's output filters, compared to the 10 μH inductors traditionally used on Class-D designs.

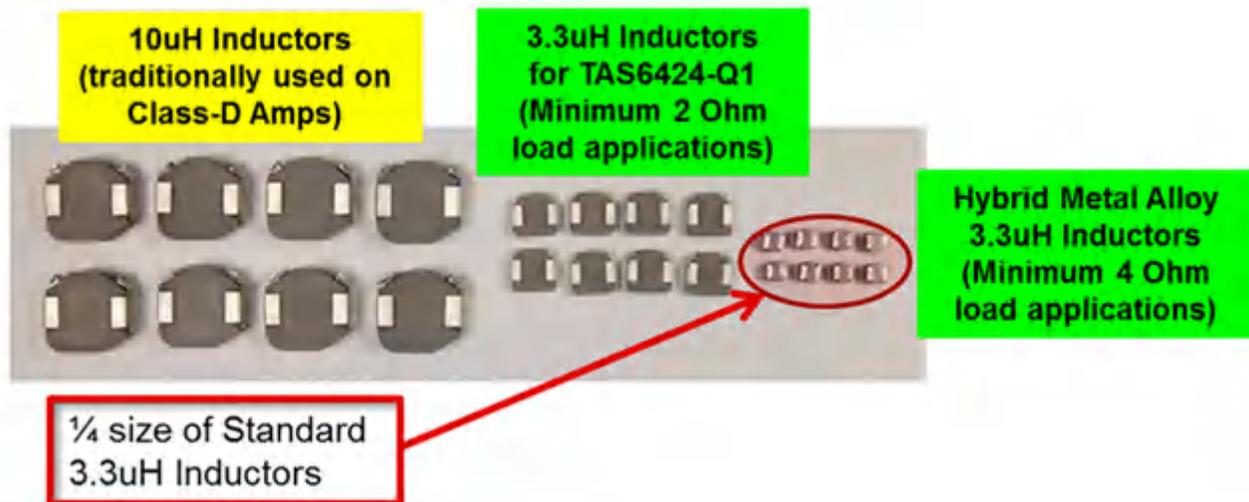


Figure 3. Comparison of Inductor Sizes

Automotive designs will continue to demand solutions that deliver high resolution audio quality in the smallest footprint possible. Technology advancements in Class-D amplifiers continue to improve towards this goal. The high bandwidth feedback loop enabled by the innovative high switching frequency of the TAS6424-Q1, combined with the integrated digital to analog conversion, drives a high quality [audio solution](#).

If you're starting an automotive infotainment design, be sure to check out the [TAS6424-Q1 evaluation module \(EVM\)](#) that can help you kick-start your next head unit or external amplifier design. The TAS6424-Q1 EVM design will not only help you to demonstrate and evaluate the capabilities of this innovative device, but the schematics, design files and layout guidance can help you rapidly design for optimal EMC performance. I encourage you to hook up your favorite speakers and play your personal music on the TAS6424-Q1 EVM to hear for yourself.

Additional Resources

- Watch a video to learn more about the [features of the TAS6424-Q1](#).
- Download an [IBIS model](#) that can help you simulate your device.
- Explore additional [mid-power audio amplifiers](#) to suit your design needs.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated