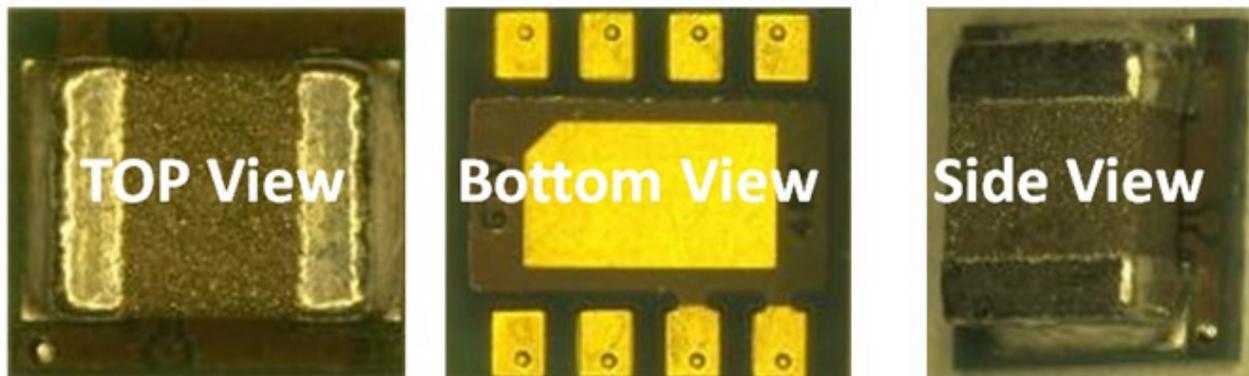


Chris Glaser

Jun 3, 2015



Are you space constrained? Does your next design have less printed circuit board (PCB) area available than the previous one? Are you tired of managing 10 or even 20 components for just a single power supply? If you answered yes to any of these questions, occupy less space and simplify your life with a [MicroSiP module](#)!

Cramming [3A of output current into a 2-mm by 2-mm package](#) with over 90% efficiency was already quite a feat for our design teams. But taking this same integrated circuit (IC), adding just an extra 4.4 mm<sup>2</sup> of PCB space, and incorporating the power inductor (which normally occupies between 5 and 15 mm<sup>2</sup> of PCB area)? Now that is an accomplishment. In fact, the recent evolution of 3A converters looks like this:

- 2010: [TPS54319](#): 13 total components occupying > 200 mm<sup>2</sup>
- 2012: [TPS62090](#): 8 total components occupying 100 mm<sup>2</sup>
- 2013: [TPS62085](#): 6 total components occupying 64 mm<sup>2</sup>
- 2015: [TPS82085](#): 5 total components occupying 35 mm<sup>2</sup>

When using the new [TPS82085](#) MicroSiP module, designers can reduce the total PCB area required to less than 35 mm<sup>2</sup> and the bill of materials (BOM) to just five total components. This module could be a great option for optical networking systems, solid-state drives (SSDs) and other space-constrained applications needing 3A output currents.

The TPS82085 module incorporates a DC/DC step-down converter plus the power inductor required to deliver 3A of continuous output current. You merely need to provide the input capacitor, output capacitor and two feedback resistors to set the output voltage. The power-good output pull-up resistor is not required if you don't use the PG pin. With the recommended component values in the [data sheet](#), what could be simpler?

[Figure 1](#) shows a typical application circuit for a 1.8V output voltage providing 3A of current. In which of your applications would you appreciate such small size and high output current?

## 1.8V Output Application

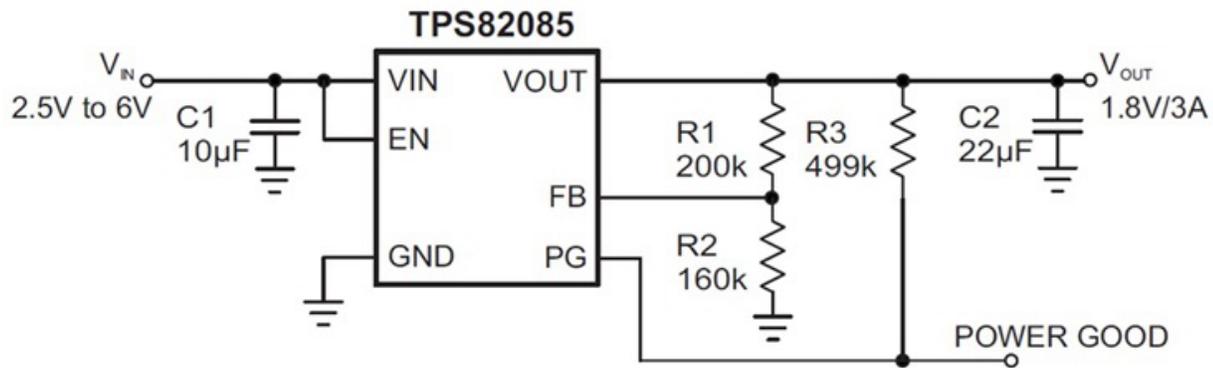


Figure 1. Typical Schematic of the TPS82085 MicroSiP Module

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated