



**PMP10852 Rev B Synchronous Buck Converter  
Test Report  
3/11/15**

The tests performed were as follows:


A. LM5117

1. Turn-On (No Load)
2. Turn-Off (10 m $\Omega$  Load)
3. Switch Node (Full Load, Ringing, No Load)
4. Output Voltage Ripple (No Load and Full Load)
5. Transient Response (100mA to 2.4A Load Step)
6. Efficiency
7. Bode Plot
8. Board Photos
9. Thermal Images
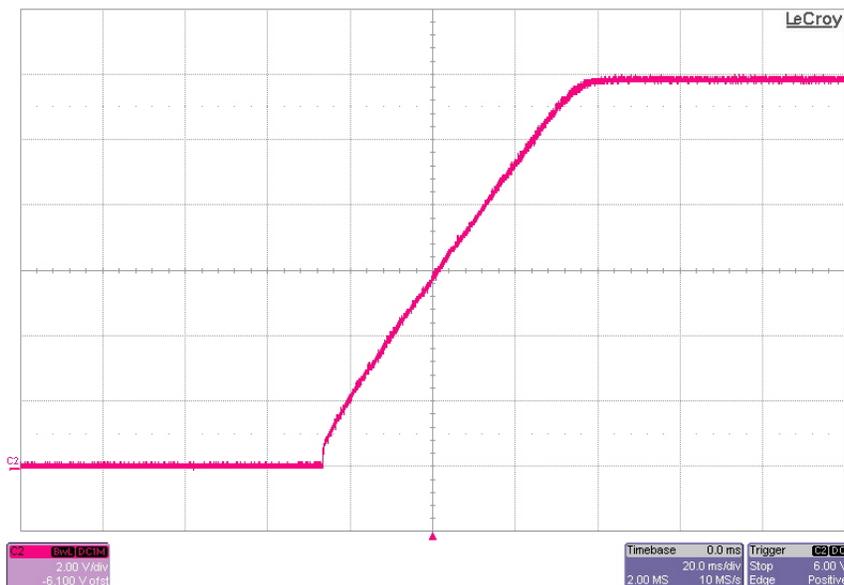
## 1 Startup – (LM5117– No Load)

The photo below shows the startup waveform. The input voltage is 34V, the output is not loaded. The time-base is set to 20ms/Division.

Channel 2 – Pink: Output Voltage – (2V/Division)




Turn on Waveform
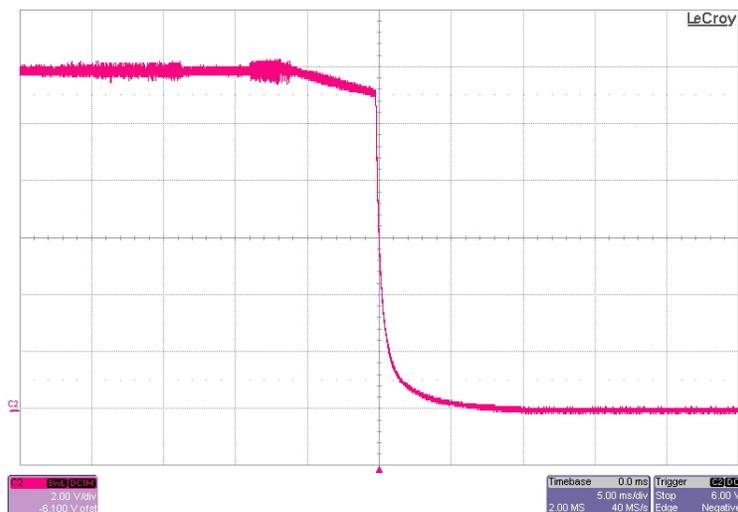
## 2 Shutdown – (LM5117– 10 mΩ load)

The photo below shows the turn off waveform. The input voltage is 34V, the output is loaded with 10 mΩ load. The time-base is set to 5ms/Division.

Channel 2 – Pink: Output Voltage – (2V/Division)




Turn off Waveform
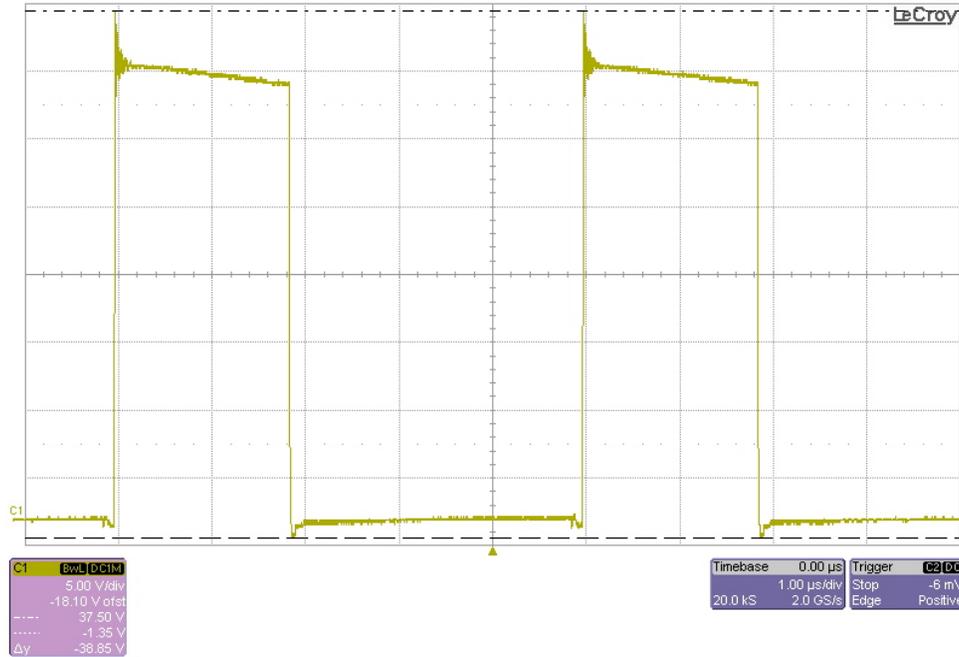
## 3 Switch Node – (LM5117– 12V @ 15A)

The picture below shows the switching node waveform for the converter. The input voltage is 34V. The time-base is set to 1us/Division


Channel 1 – Yellow: Switch Node – (5V/Division)



Switch Node Ringing: There is a total change of 38.85V

The picture below zooms in on the ringing on the rising edge of the switching node. The time-base is set to 50ns/Division

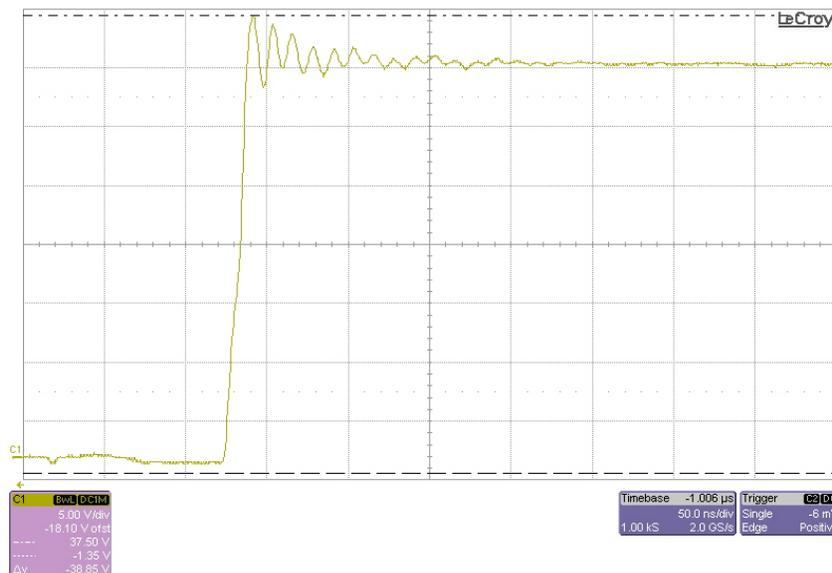Channel 1 – Yellow: Switch Node – (5V/Division)



Switch Node Ringing: There is a total change of 38.85V


# PMP10852 Test Results Rev. B

## 4 Output Voltage Ripple – (LM5117– 12V @ 15A)

The output voltage ripple of the converter is shown in the figures below. The input voltage is 34V. The time-base is set to 2us/div. The first image is Vrip without a load, and the second image is Vrip with a 15A load.

Channel 2 – Pink: Output Voltage (10mV/div; AC Coupled)


Channel 3 – Blue: Output Load

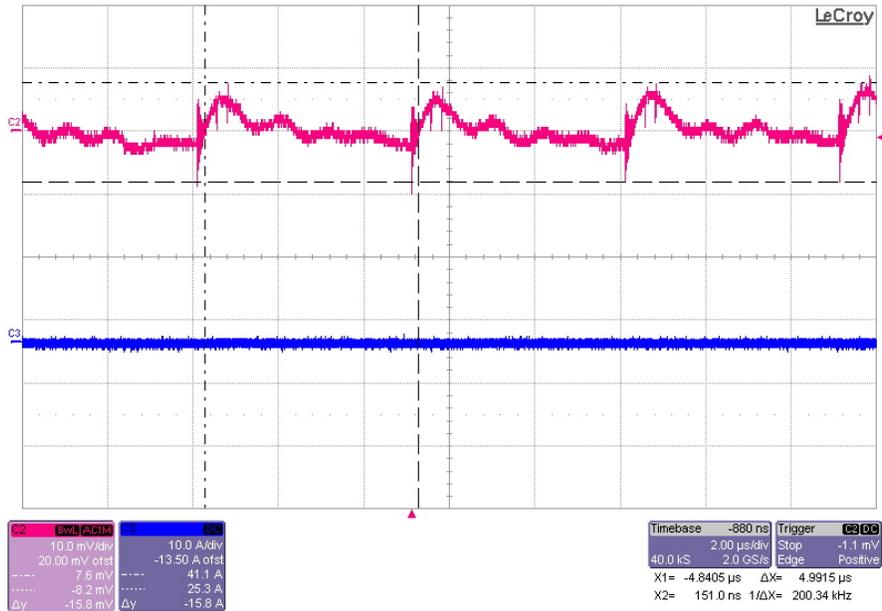

No Load: Vrip = 15.8mV

Channel 2 – Pink: Output Voltage (50mV/div; AC Coupled)

Channel 3 – Blue: Output Load (10A/div)

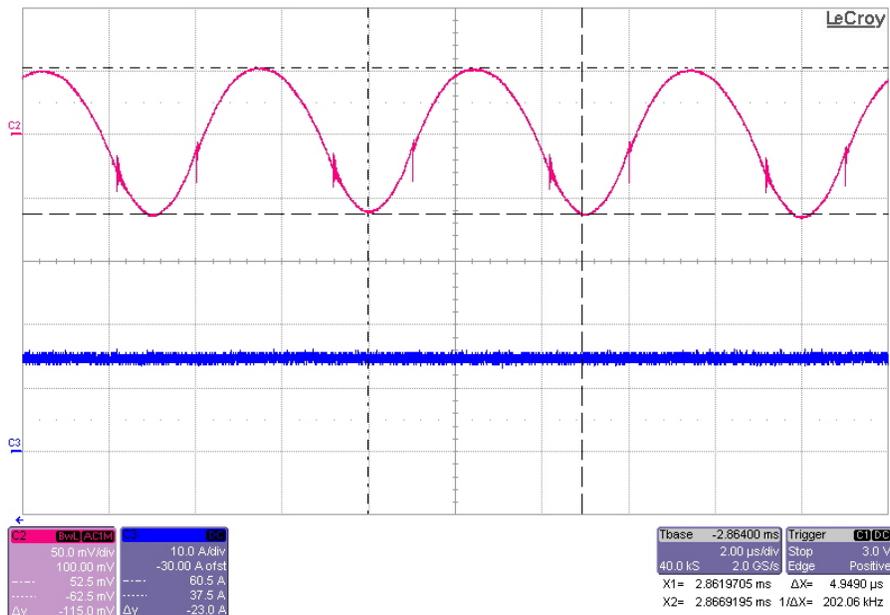

15A Load: Vrip = 115mV

# PMP10852 Test Results Rev. B




## 5 Transient Response – (LM5117– 12V @ 15A)

The transient response of the converter is shown in the figures below. The input voltage is 34V. The load is stepped from 3.75A to 11.25A. The time-base is set to 200us/div.

Channel 2 – Pink: Output Voltage : (500mV/Division; AC Coupled)

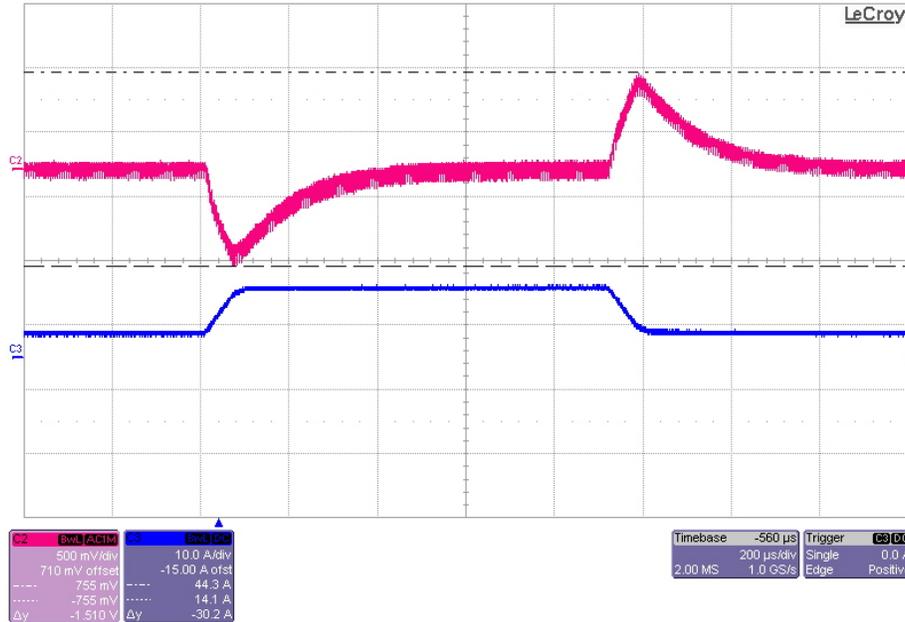
Channel 3 – Blue: Output Current – (10A/Division; DC Coupled)



Transient Response – There is a total change of 1.51V to the output voltage

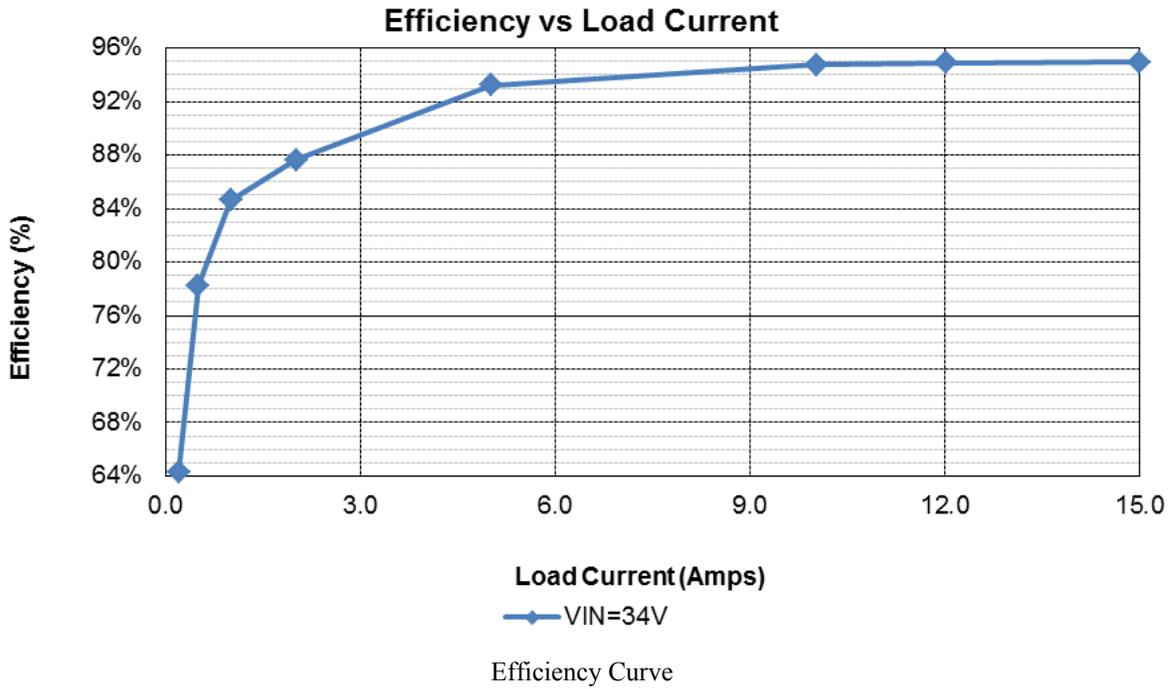
## 6 Efficiency – (LM5117– 12V Output)

The efficiency of the board measured at the output of switching converter is shown in the picture below.



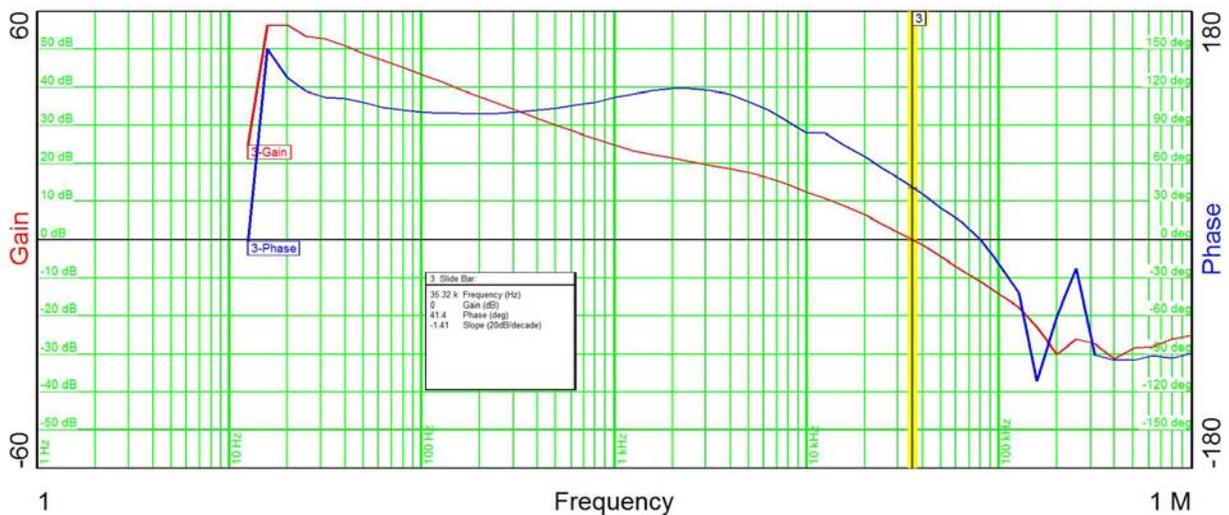
## 7 Bode Plot – (LM5117– 12V @ 15A)

The Bode Plot of the converter is shown in the figure below. The input is 34V.



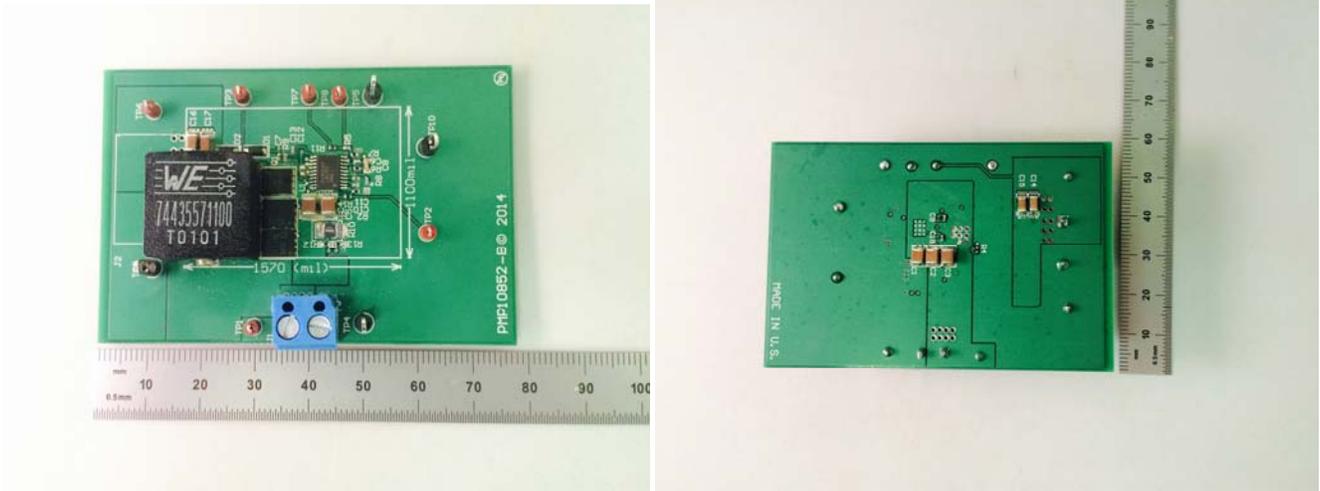
## 8 Board Photos

The images below show the PMP10852 Rev. B board which was used for testing.


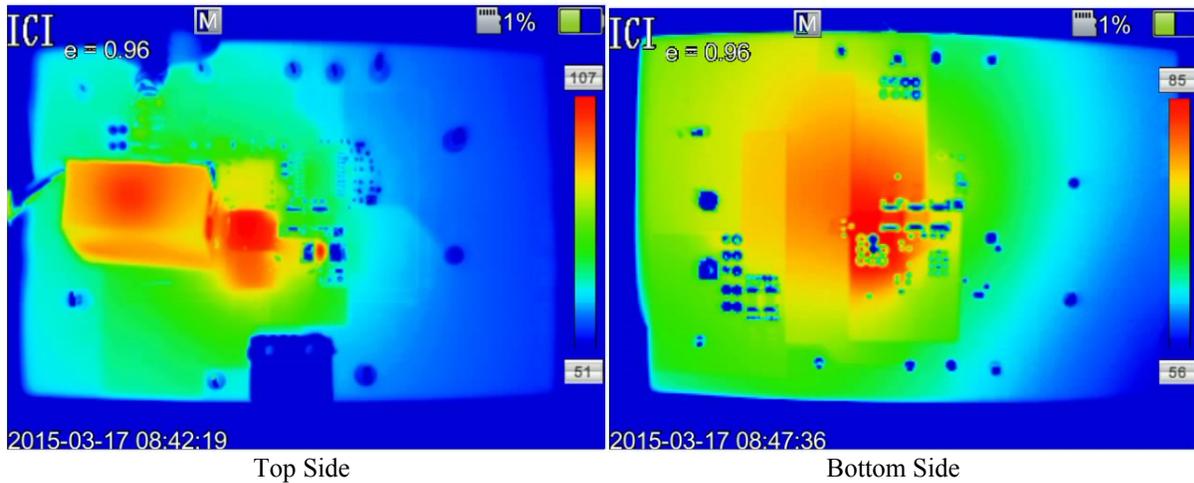
## 9 Thermal Images

The images below show the thermal performance of the design. It is important to note that thermal performance is directly proportional to power loss and board size. Different sized and shaped boards will perform differently. The input voltage is 34V, the output current is 15A.



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated