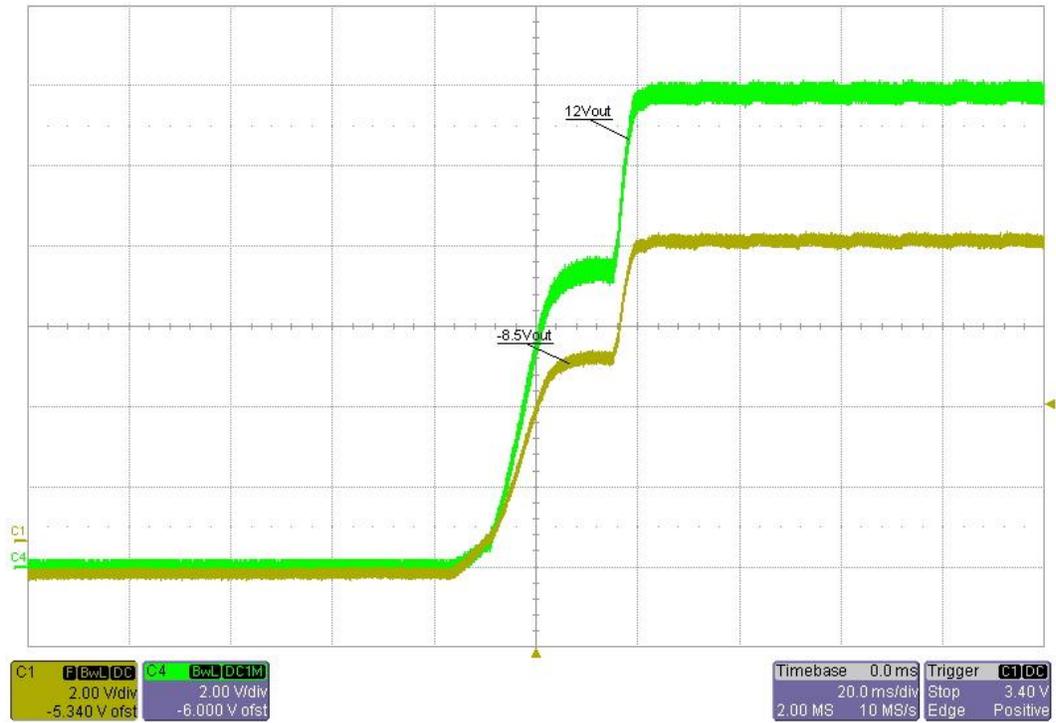


1 Startup


Input voltage = 85VAC

Load current 12Vout = 2.5A


Load current 8.5Vout = 0.05A



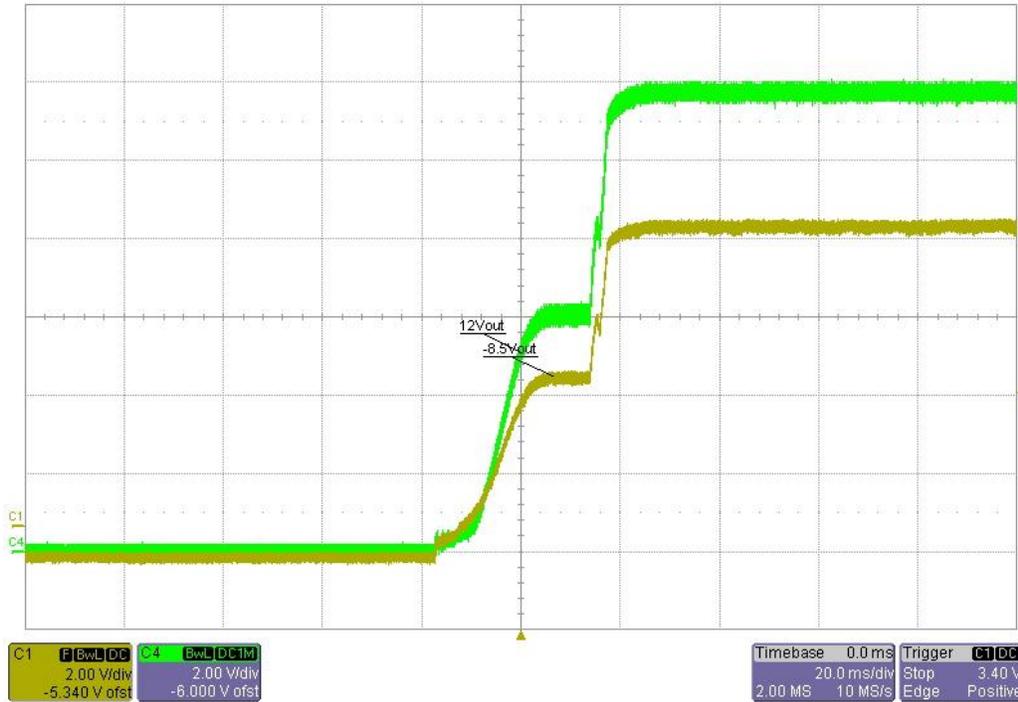Input voltage = 230VAC
Load current 12Vout = 2.5A
Load current 8.5Vout = 0.05A



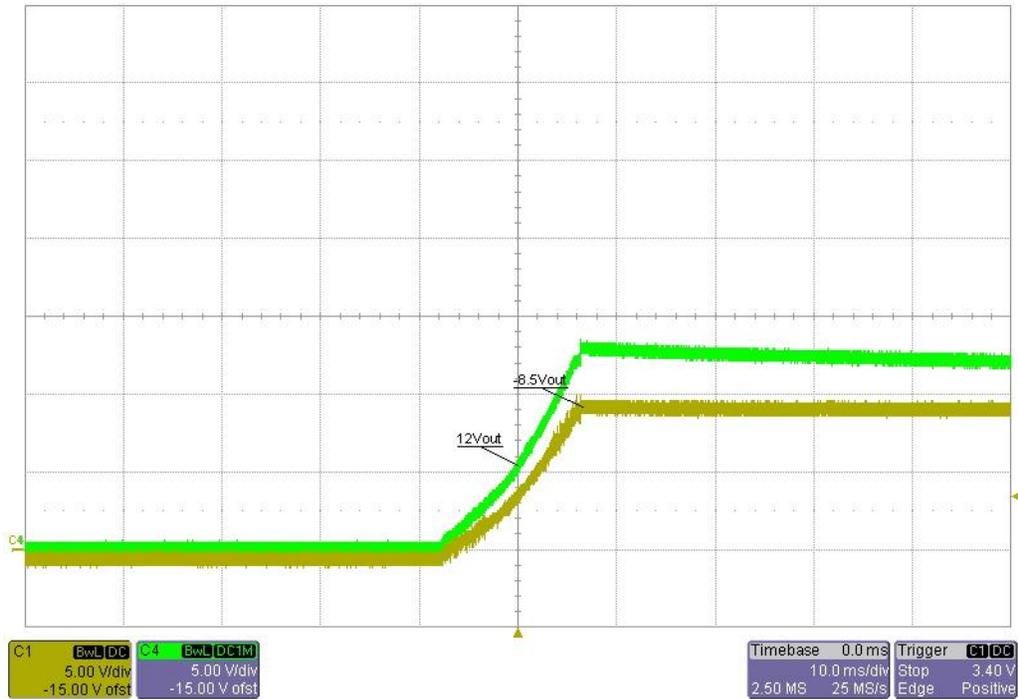Input voltage = 230VAC
Load current 12Vout = 0A
Load current 8.5Vout = 0A




2 Shutdown


Input voltage = 230VAC

Load current 12Vout = 2.5A


Load current 8.5Vout = 0.05A

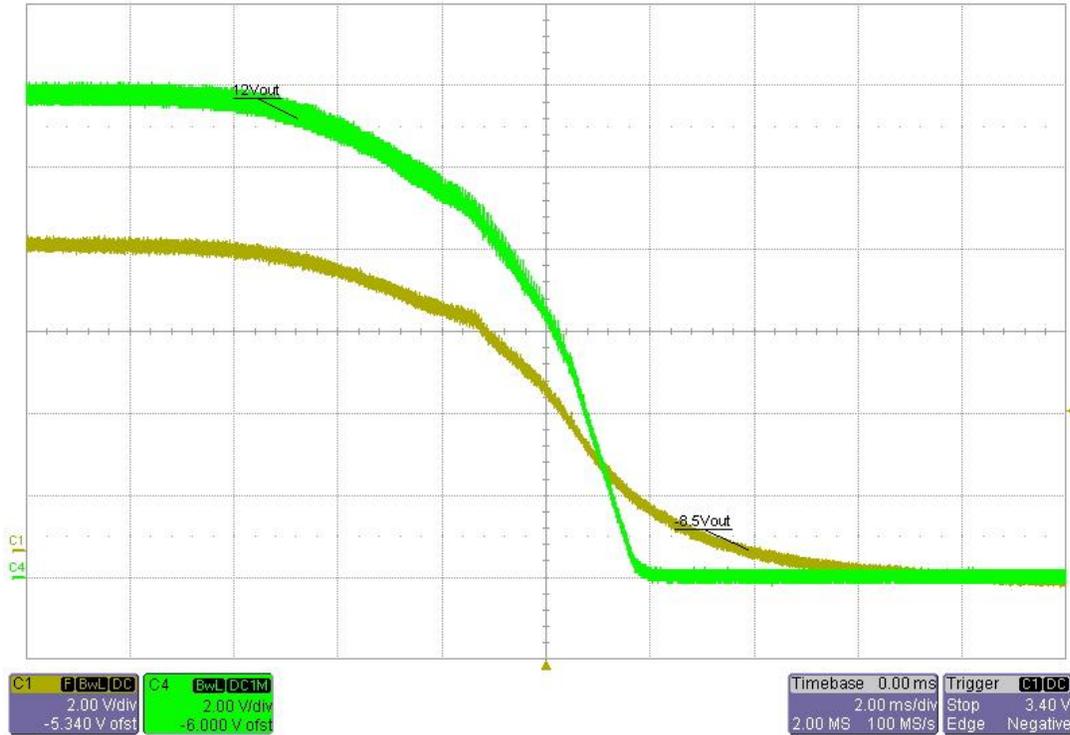


3 Efficiency

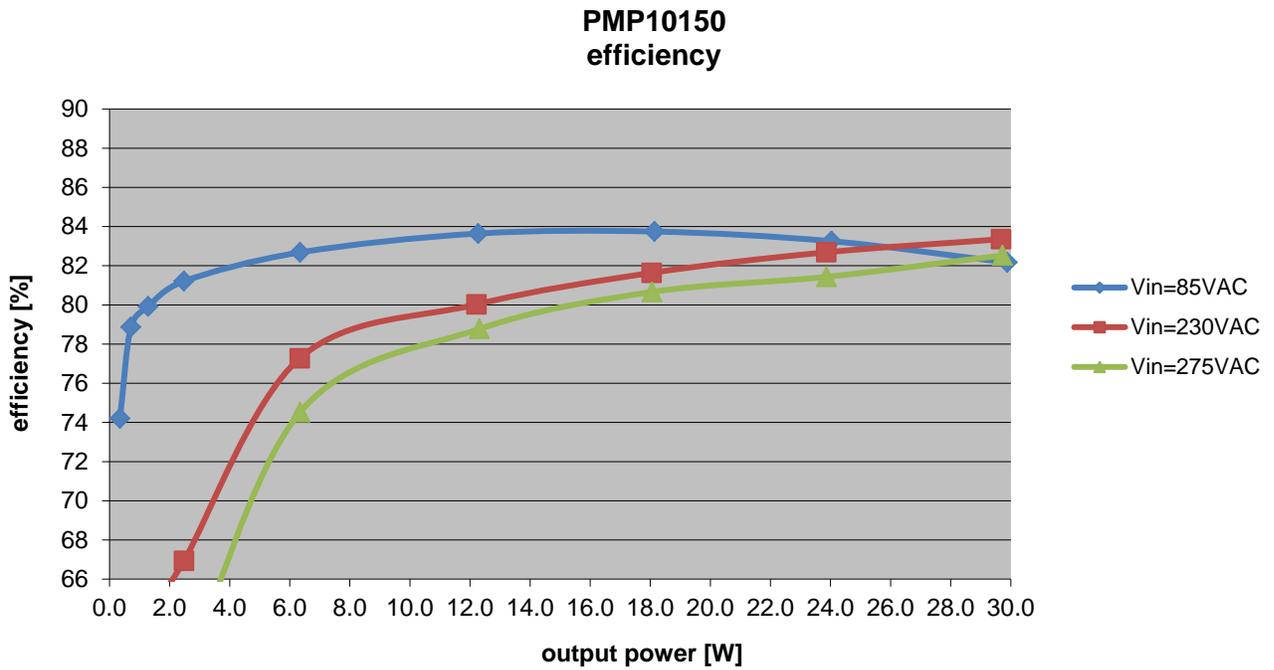

4 Load regulation

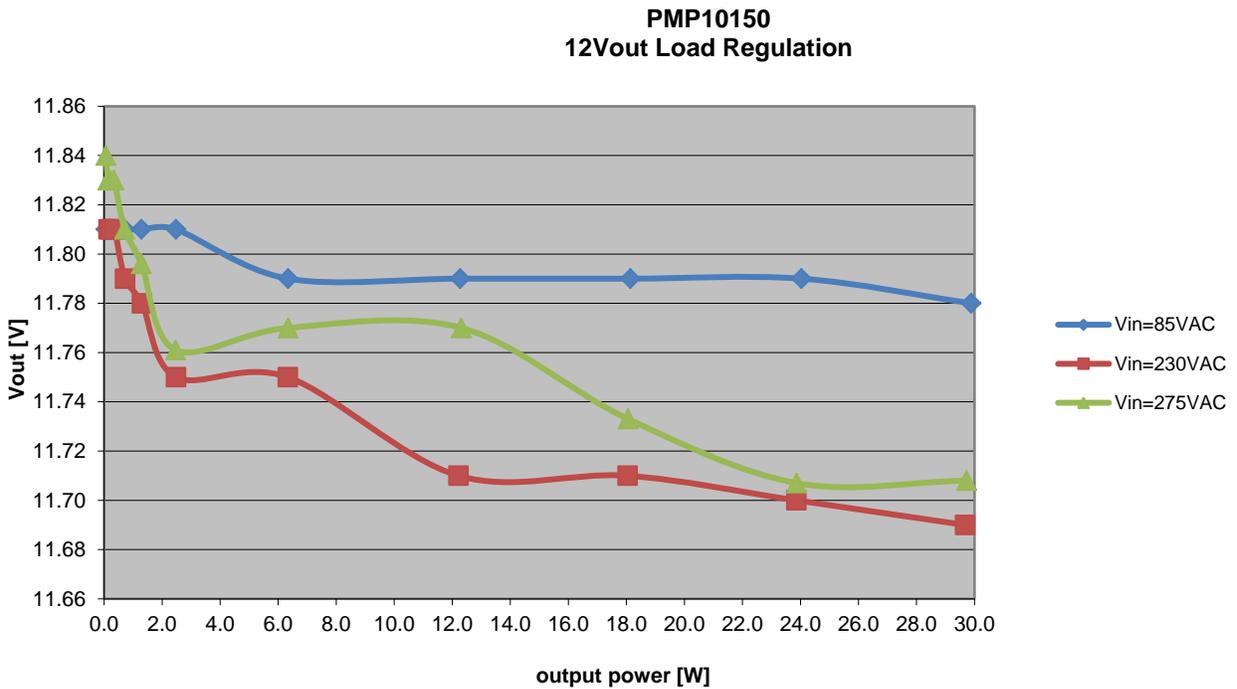

5 Control Loop Frequency Response

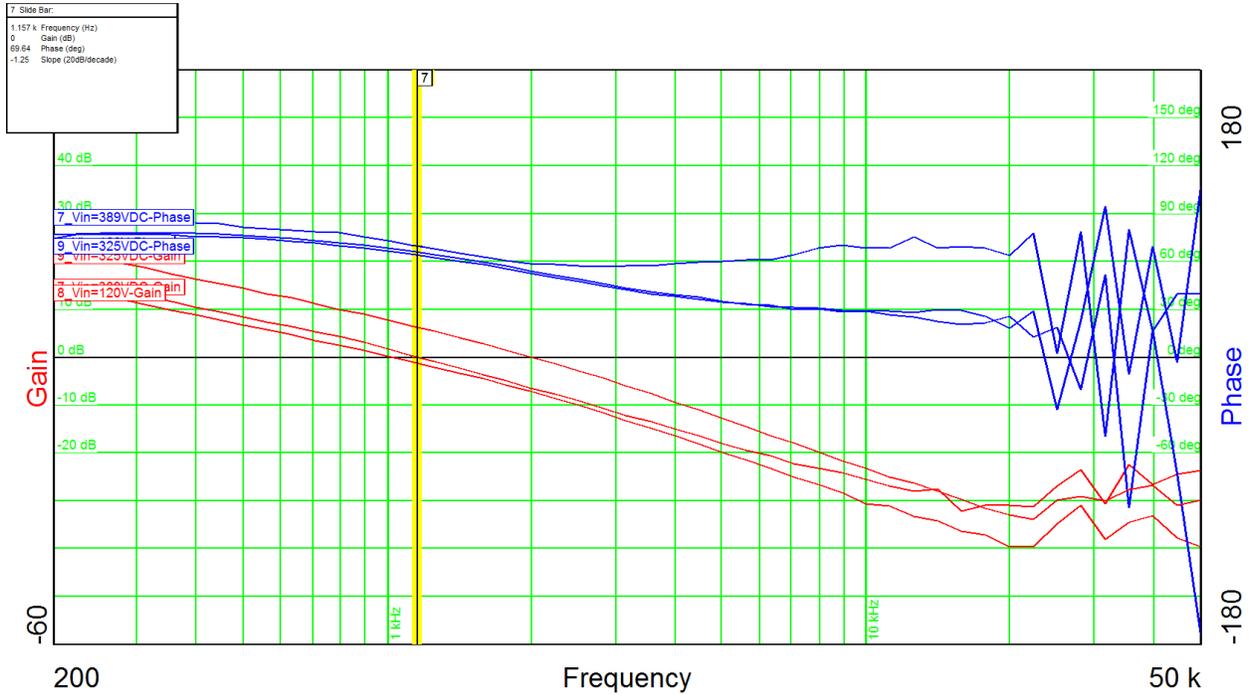

Output power = 30W
 Input voltage = 120VDC
 Phase margin = 68°
 Bandwidth = 1.0kHz

Output power = 30W
 Input voltage = 325VDC
 Phase margin = 53°
 Bandwidth = 2.0kHz


Output power = 30W
 Input voltage = 390VDC
 Phase margin = 70°
 Bandwidth = 1.2kHz

6 Switch Node

Input voltage = 390VDC

Load current 12Vout = 2.5A


Load current 8.5Vout = 0.05A

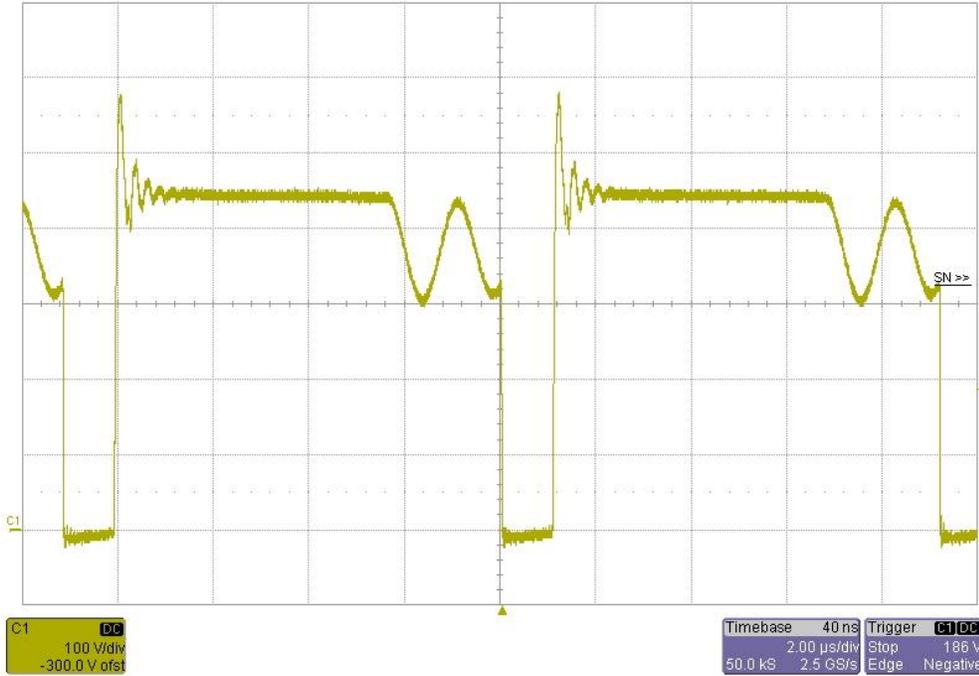

Input voltage = 85VDC

Load current 12Vout = 2.5A


Load current 8.5Vout = 0.05A

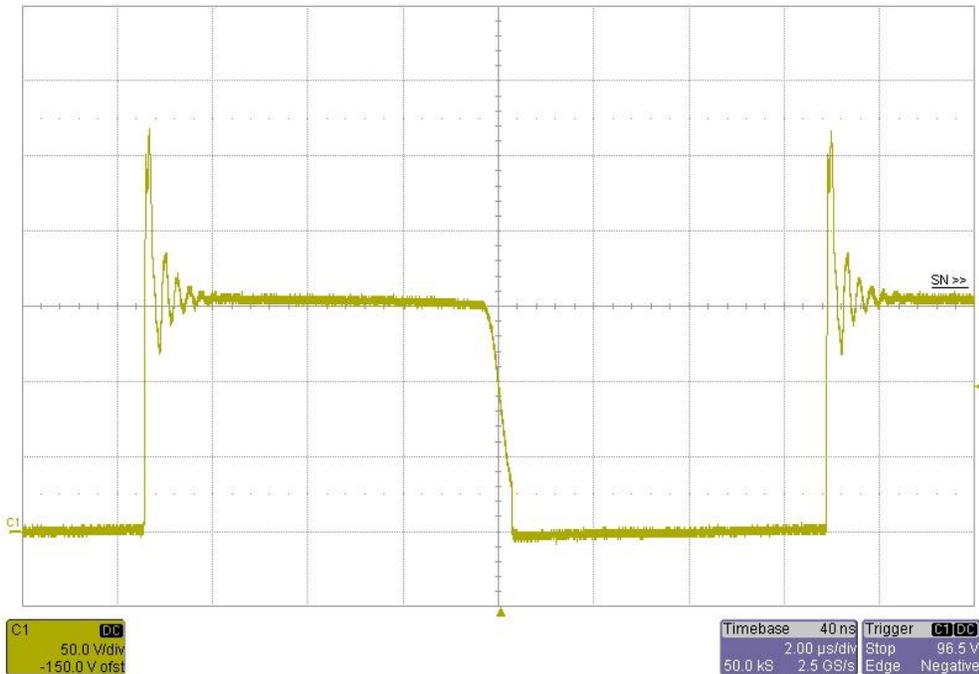

7 Switch Node secondary side (12Vout)


Input voltage = 85VDC

Load current 12Vout = 2.5A

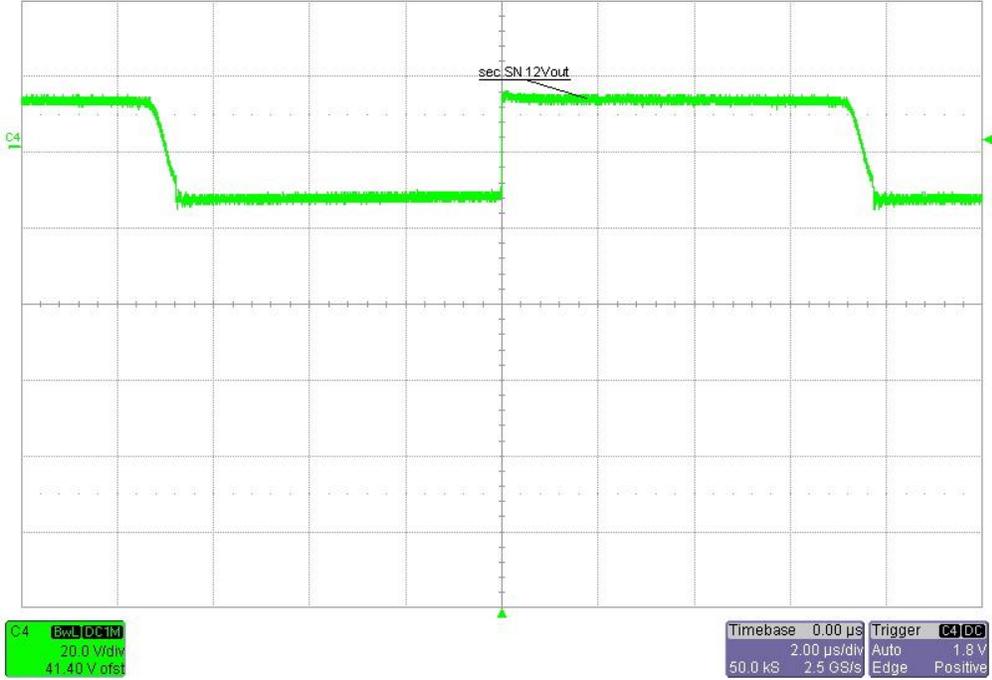

Input voltage = 390VDC

Load current 12Vout = 2.5A

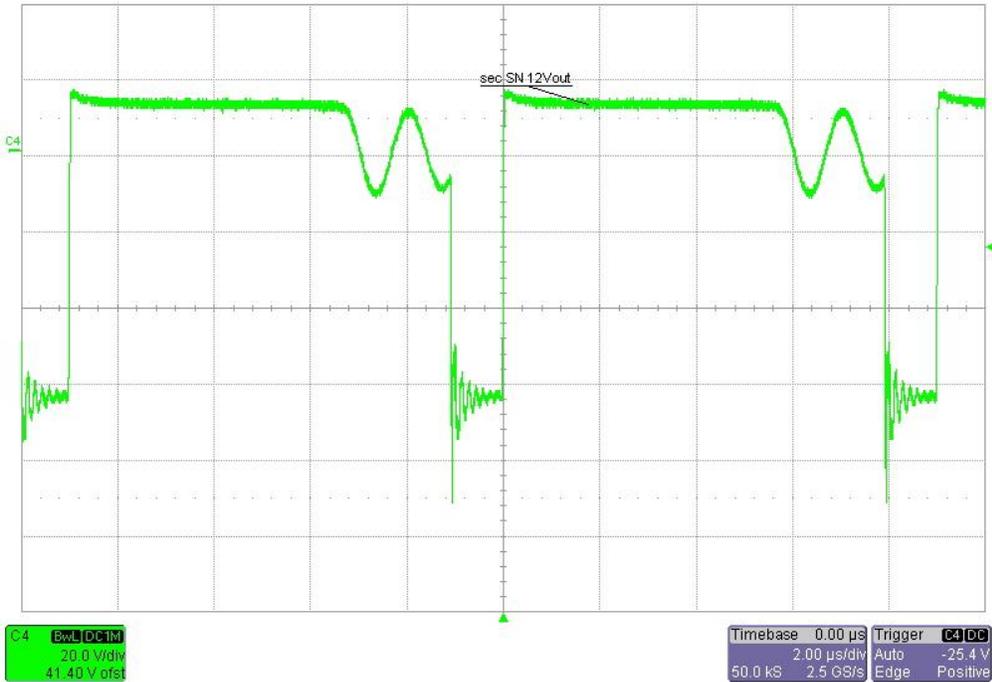


8 Output ripple voltage (12Vout)

Input voltage = 230VAC


Load current 12Vout = 2.5A

Load current 8.5Vout = 0.05A

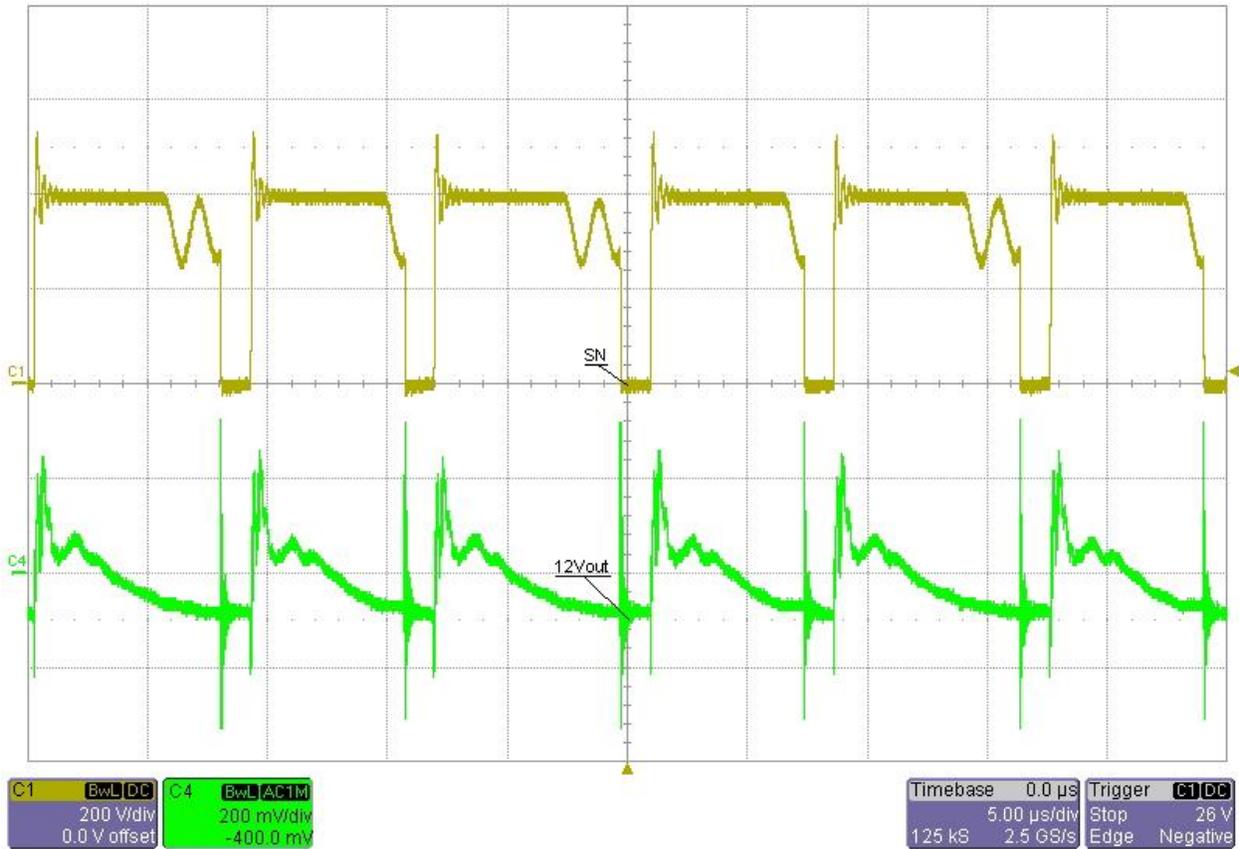


9 Load Transients (12Vout)

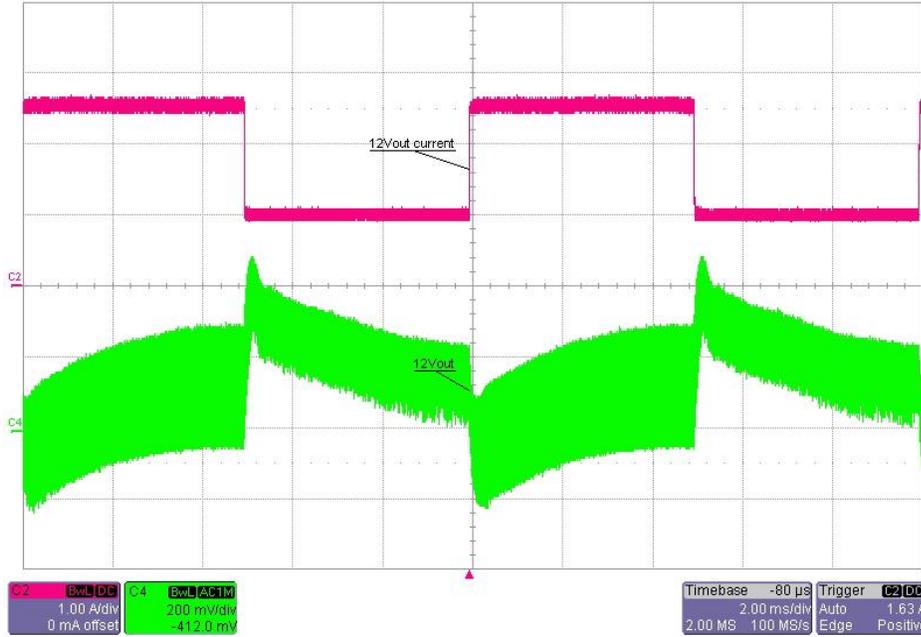Input voltage = 85VAC
Load current 12Vout = 1A to 2.5A




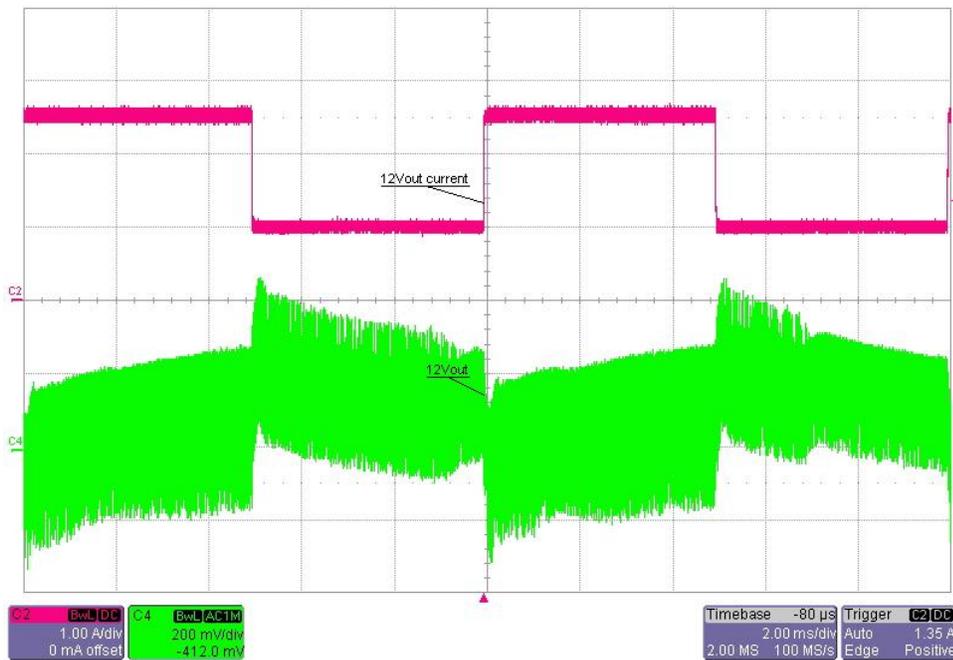Input voltage = 230VAC
Load current 12Vout = 1A to 2.5A



Input voltage = 265VAC


Load current 12Vout = 1A to 2.5A

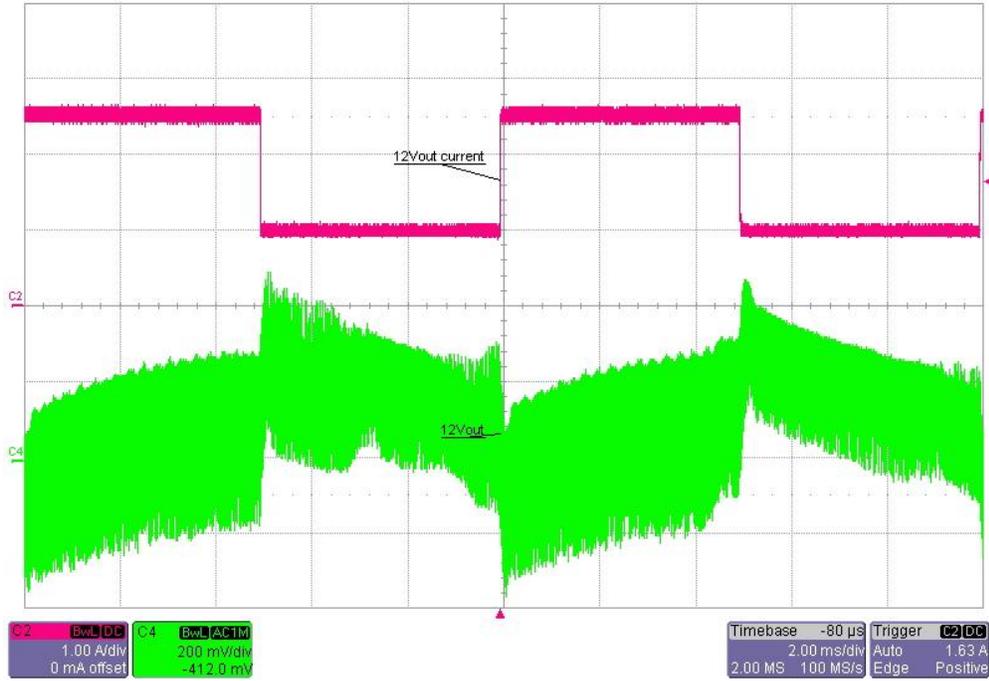

10 Thermal Analysis

The images below show the infrared images taken from the FlexCam after 15min at 18.5W output power.

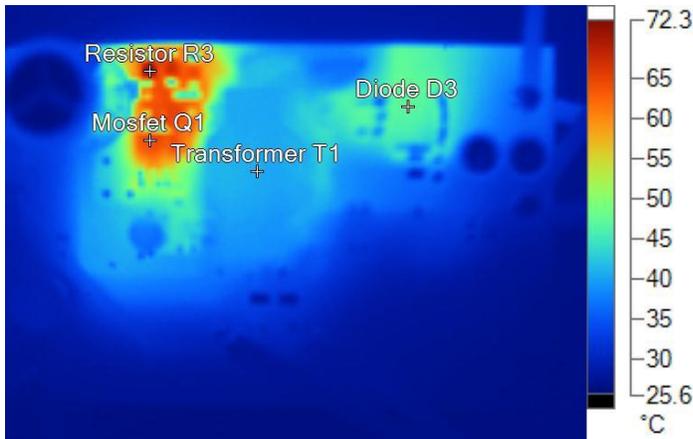
Input voltage = 230VAC
 Output power = 18.5W
 Ambient temperature = 25°C
 No heatsink, no airflow



Name	Temperature
Mosfet Q1	64.6°C
Resistor R3	72.3°C
Transformer T1	40.8°C
Diode D3	47.1°C

**IR20150409_0555 Vin=230VAC 8.5V@50mA
 12V@1.5A.is2**

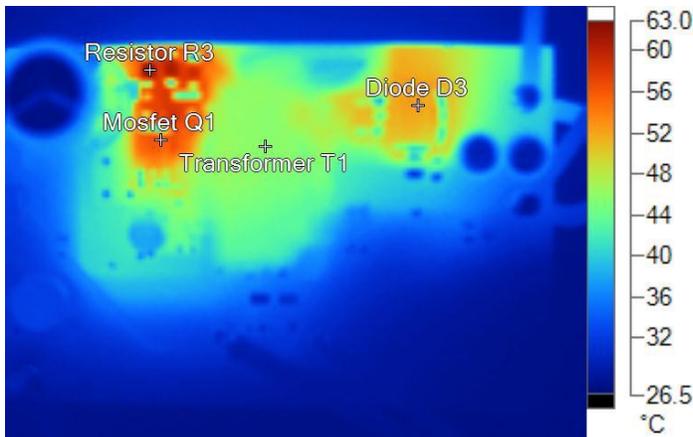Input voltage = 120VAC
 Output power = 18.5W
 Ambient temperature = 25°C
 No heatsink, no airflow




Name	Temperature
Mosfet Q1	56.1°C
Resistor R3	63.0°C
Transformer T1	45.8°C
Diode D3	52.1°C

**IR20150409_0558 Vin=120VAC 8V@50mA
 12V@1.5A.is2**

11 EMI Measurement

The graph below shows the conducted emission EMI noise and the EN55022 Class-B Quasi-Peak limits (measurement from the worst case line). The load was connected to a LISN and an isolation transformer; the load was a power resistor (12V@1.5A), while the input voltage was 230Vac. The resistor R1 was not populated. The receiver was set to Quasi-peak detector, 10 KHz bandwidth. The secondary side GND of the converter was connected to the ground of the LISN.

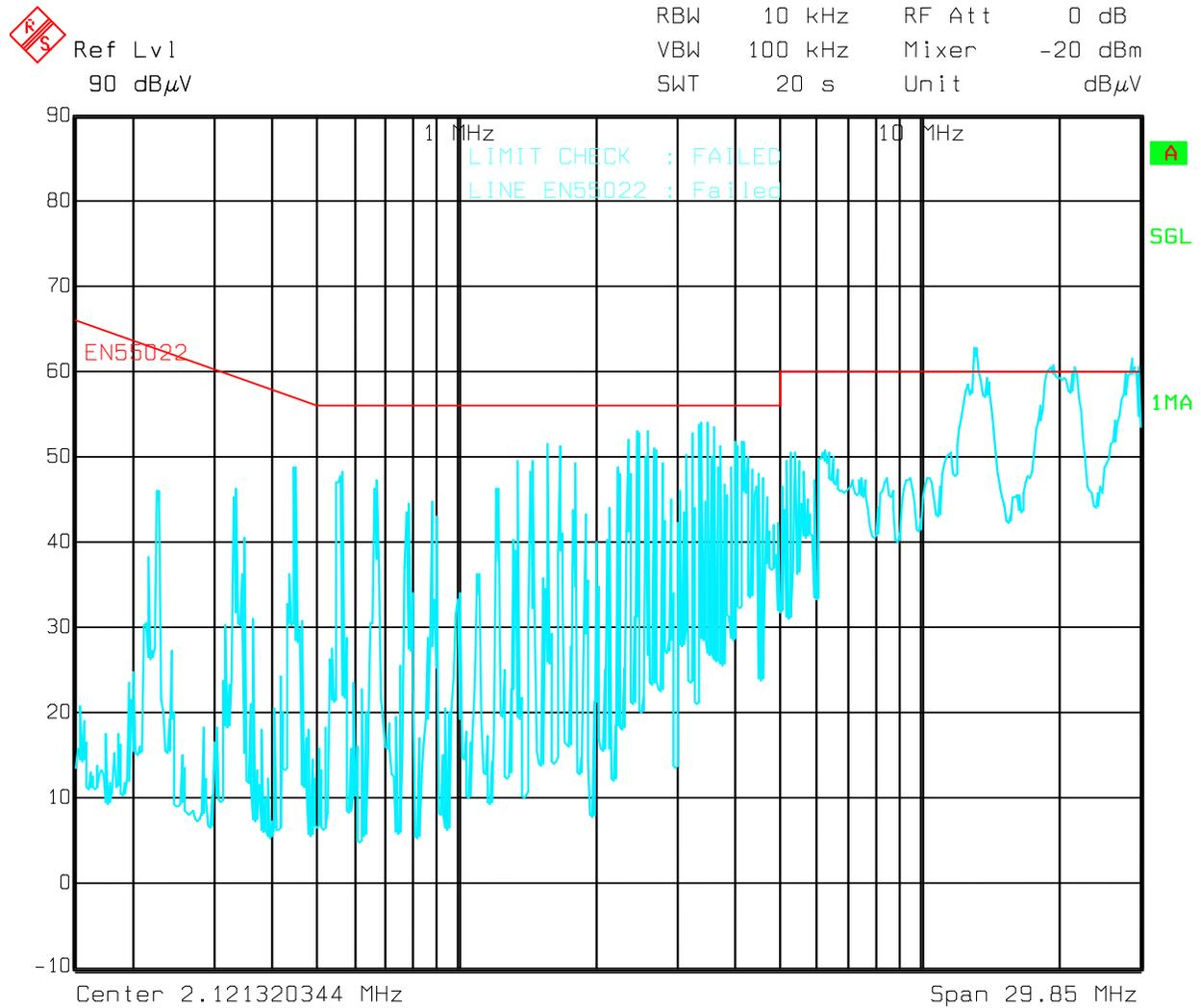

Date: 10.APR.2015 12:35:48

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated