

**TIDA-00783
Test Report
10/13/2015**



Table of Contents

I.	Overview	3
II.	Power Specification.....	3
III.	Reference Board	4
IV.	Efficiency	5
V.	Input Current at No Load	5
VI.	Thermal	6
VII.	Power Up.....	7
VIII.	Switching Waveforms	8
IX.	Load Transients	9
X.	Output Voltage Ripples	10

I. Overview

The TIDA-00783 reference design is a triple output wide V_{in} power module reference design. It provides three output voltages: 3.3V, 1.8V and 1.2V, and total 6W power, and has a wide input range of 4.5V to 40V. The reference design features the LMZ36002 wide V_{in} power module and LMZ20502 nano module from SIMPLE SWITCHER®. The layout is optimized for space constrained application, and the total solution size is about 400 mm².

II. Power Specification

Input Voltage: 4.5V – 40V

Output: 3.3V @ 0.9A, 1.8V @ 1A, 1.2V @ 1A

Total output power: 6W

Switching frequency: 400 kHz (LMZ36002), 3 MHz (LMZ20502)

III. Reference Board

The board size is 38 x 38 mm (1.5 x 1.5 inch). The solution size is about 400 mm².



Figure 1 Reference board top view

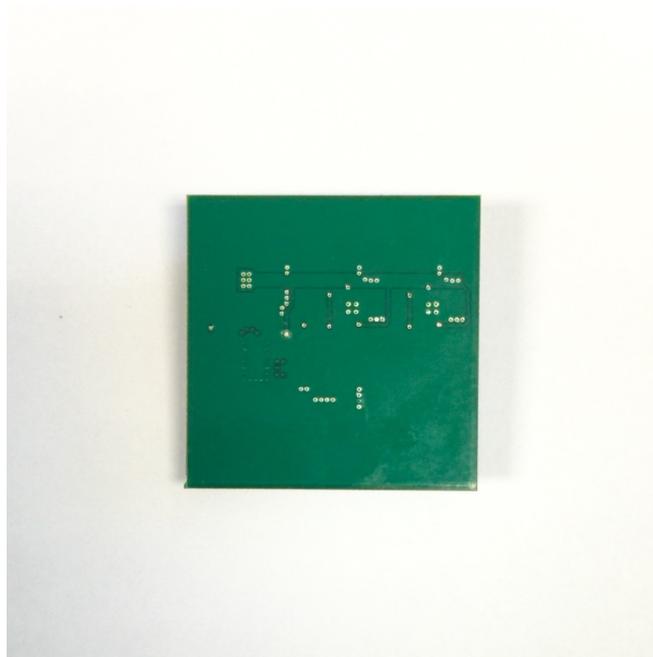


Figure 2 Reference board bottom view

IV. Efficiency

The efficiency was measured with equal load current on each output. Note that at 1A load for each output, the LMZ36002 module operated at overcurrent condition, and the design should not operate in this condition for too long.

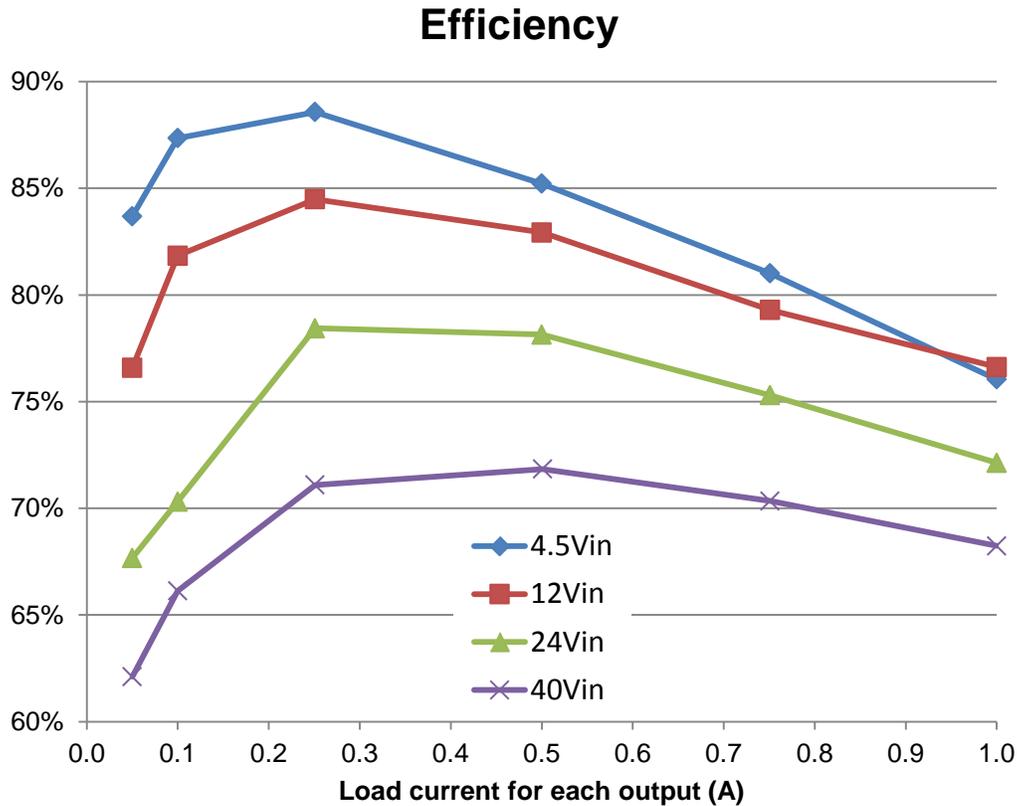


Figure 3 Power efficiency with the input filter

V. Input Current at No Load

The input current was measured at no load condition. The modules operated in PFM, and drew low input current at no load condition.

V _{in} (V)	I _{in} (μA)	3V3 (V)	1V8 (V)	1V2 (V)
4.509	330	3.341	1.809	1.201
12.004	201	3.339	1.809	1.201
24.003	178	3.334	1.809	1.201
40.007	189	3.340	1.809	1.201

VI. Thermal

The thermal image was taken at 23°C room temperature, no air flow. The board was operating at 24V input, full load condition.

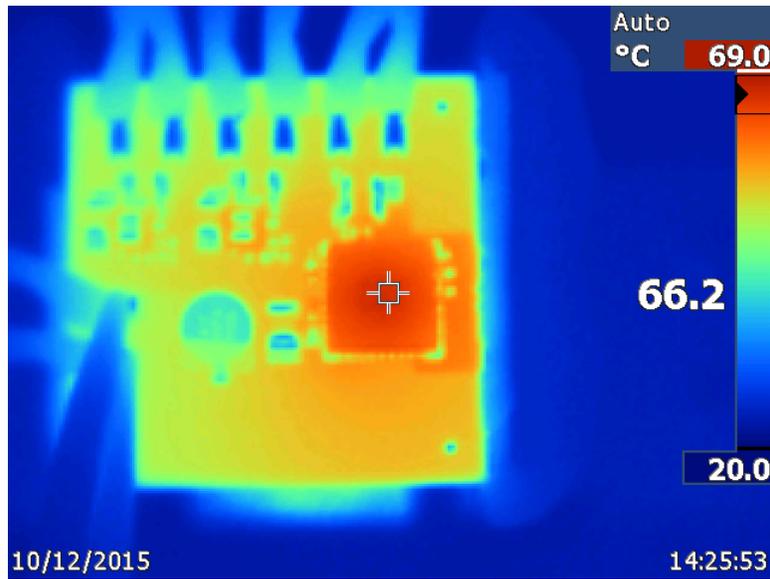


Figure 4 Thermal image from top view

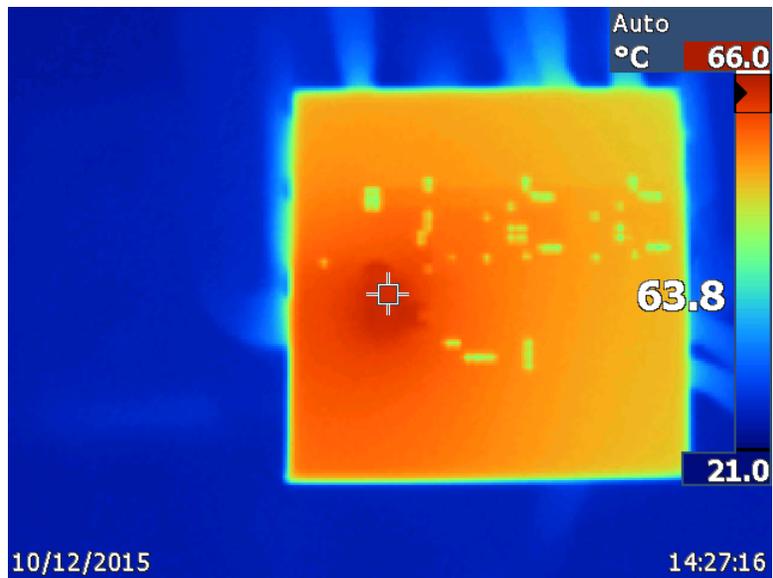


Figure 5 Thermal image from bottom view

VII. Power Up

The reference board was tested under no load and full load at 24V input. Ch1 (yellow) is the input voltage, Ch2 (magenta) is the 3.3V output voltage, Ch3 (blue) is the 1.8V output voltage, and Ch4 (green) is the 1.2V output voltage.

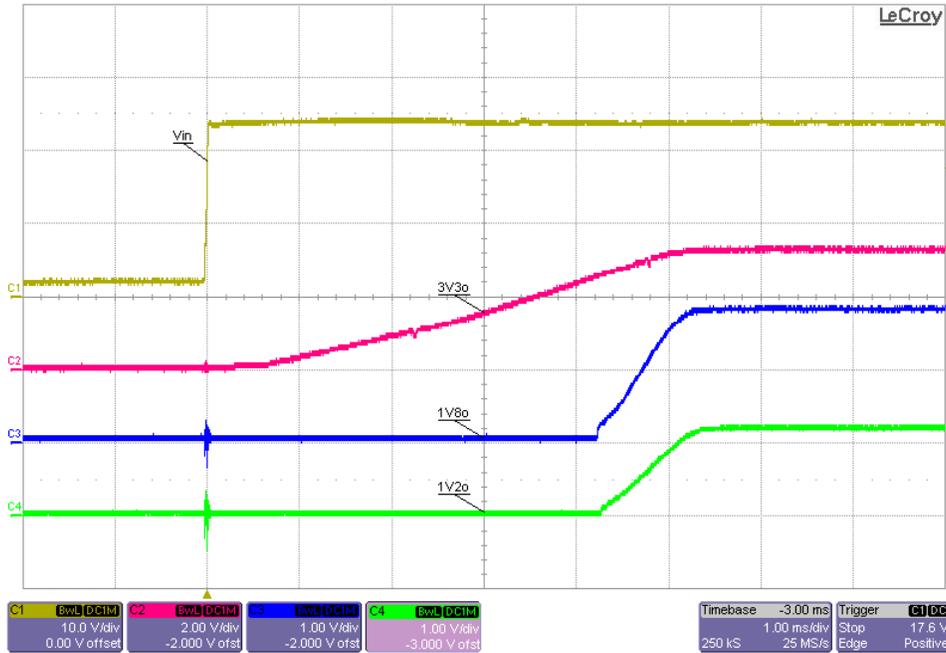


Figure 6 Power up into no load at 24V input

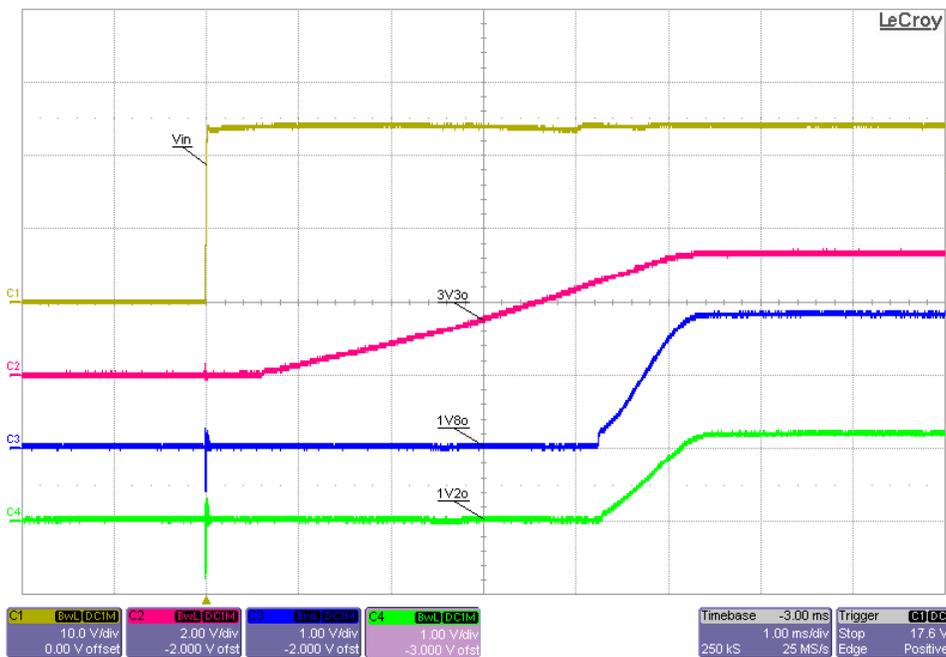


Figure 7 Power up into full load at 24V input

VIII. Switching Waveforms

The switching waveform of the 3.3V output LMZ36002 module was measured at the PH pins. For 1.8V and 1.2V output LMZ20502 module, the switching nodes were probed at the top of the integrated inductors. Ch1 (yellow) is the switch node voltage.

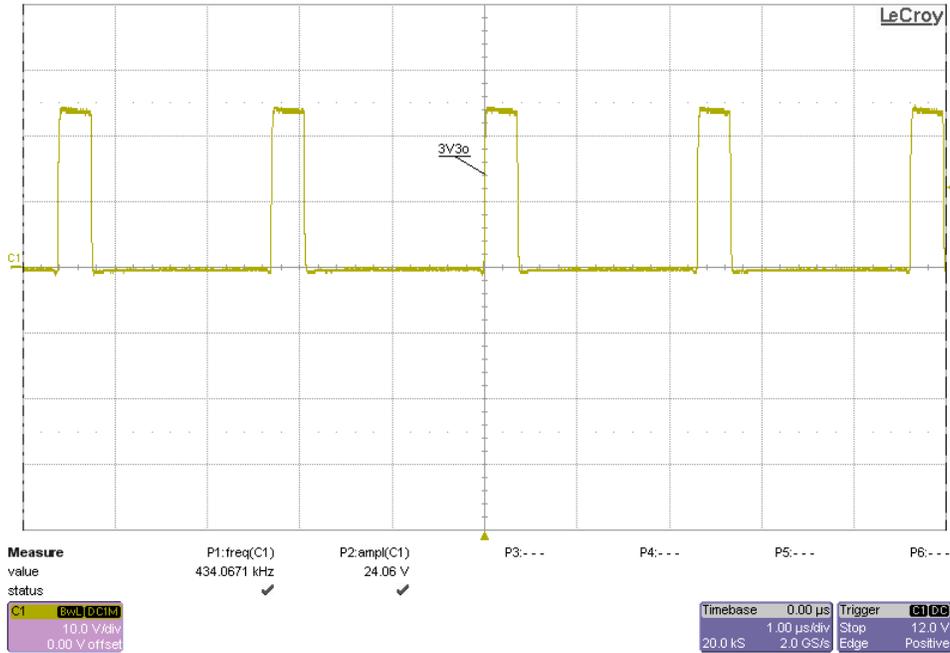


Figure 8 3.3V output switching waveform at full load, 24V input

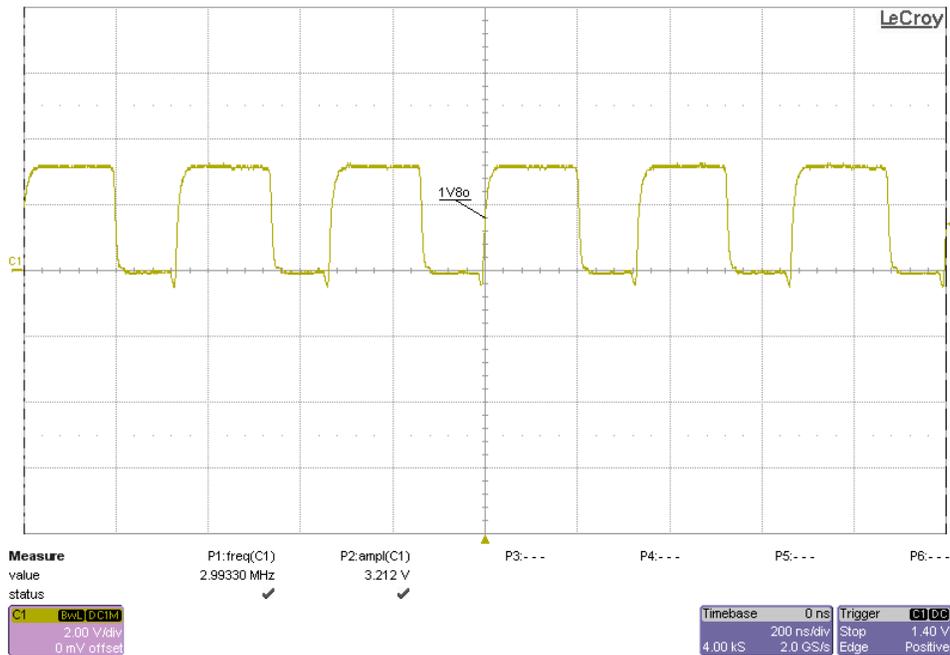


Figure 9 1.8V output module switching waveform at 1A load

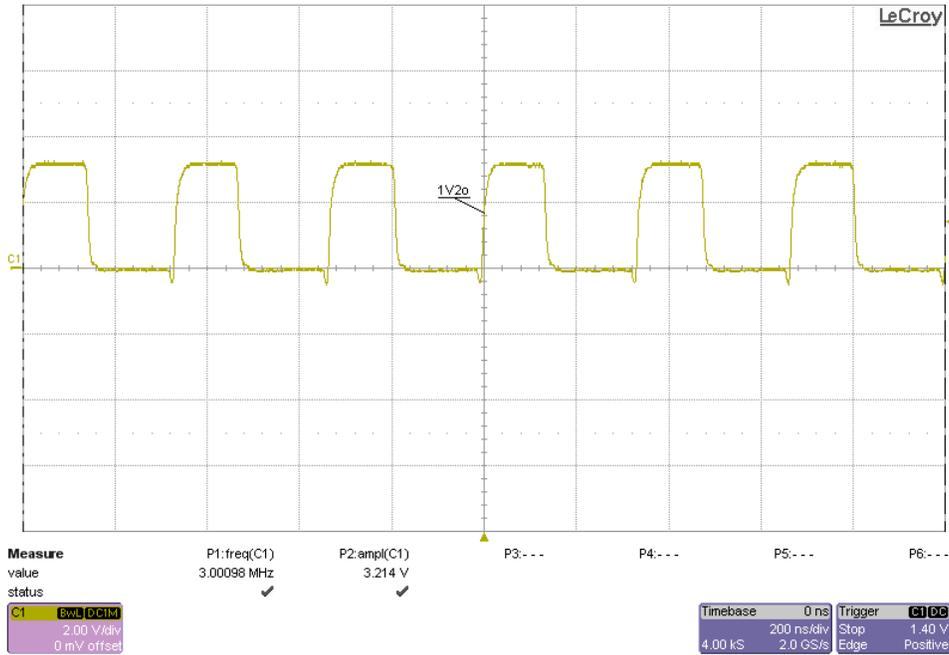


Figure 10 1.2V output module switching waveform at 1A load

IX. Load Transients

The load transient responses were tested by applying output load steps from 0 to 1A to the 3.3V output module. Ch1 (yellow) is the 3.3V output voltage in AC mode, and Ch4 (green) is the 3.3V output current.

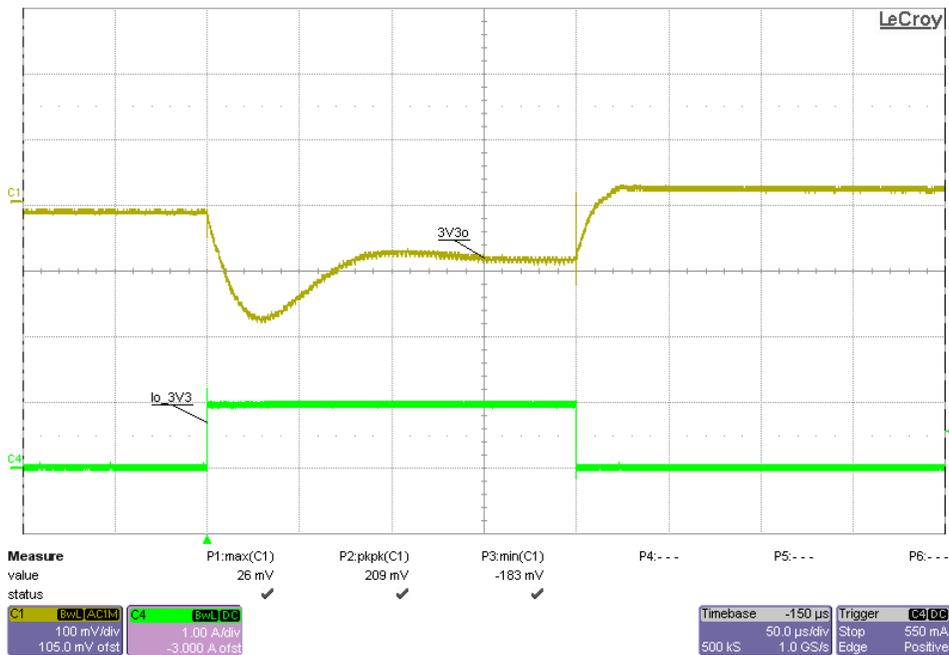


Figure 11 3.3V output load transient at 24V input, no load on other outputs

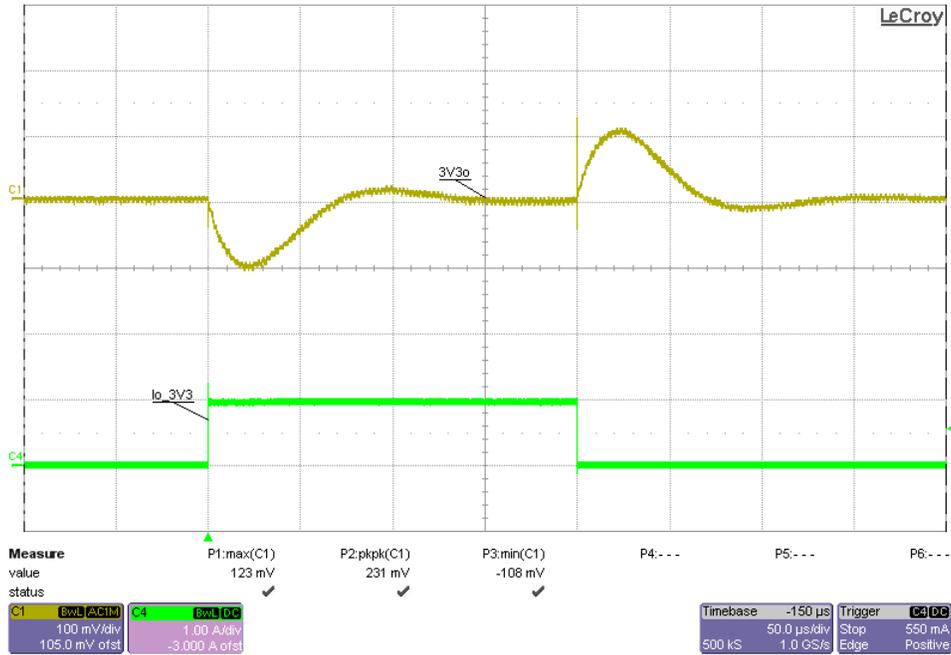


Figure 12 3.3V output load transient at 24V input, full load on other outputs

X. Output Voltage Ripples

The output ripples were measured directly at the output capacitors at full load condition. Ch1 (yellow) is the output voltage ripple in AC mode.

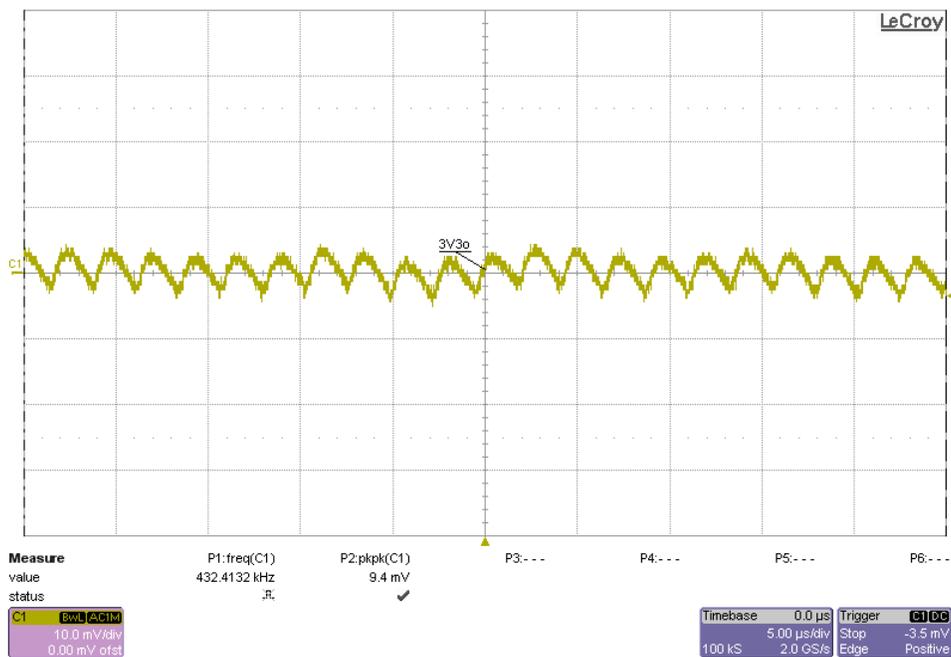


Figure 13 3.3V output ripple at full load, 24Vin

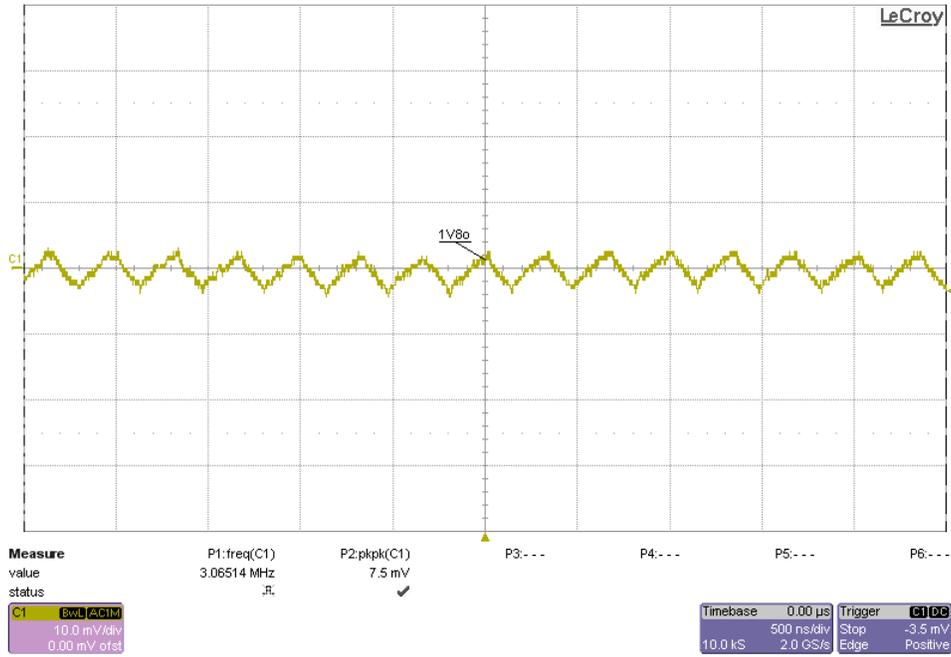


Figure 14 1.8V output ripple at full load, 24Vin

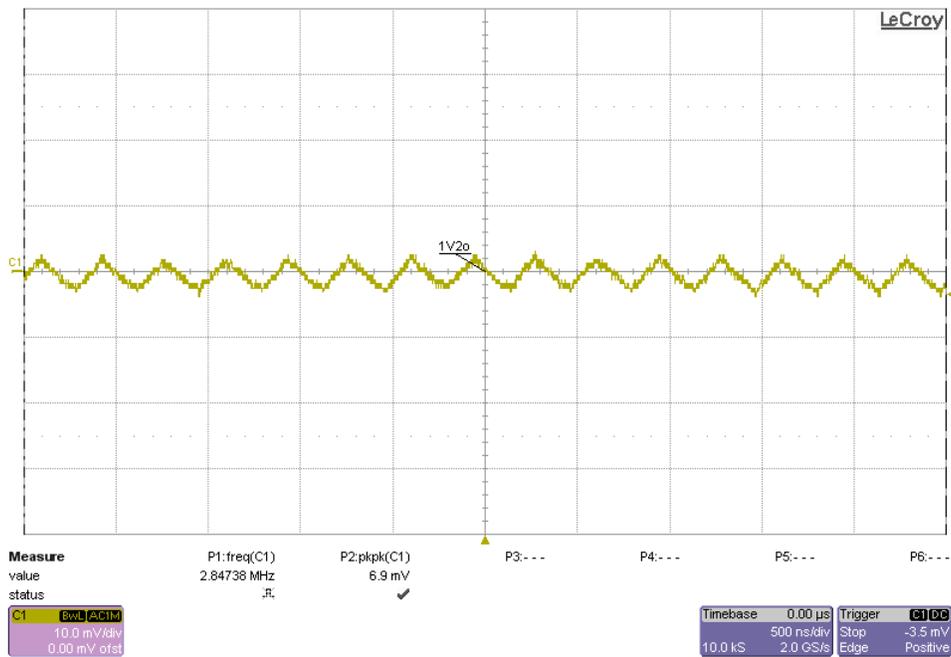


Figure 15 1.2V output ripple at full load, 24Vin

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.